

ITI1100B

CHAPTER-6

H. Ural

1

REGISTER

A SEQUENTIAL CIRCUIT WHICH CONSISTS OF A GROUP OF FF'S AND (POSSIBLY) EXTERNAL GATES CONTROLLING THE FF INPUTS WHERE

- **FF'S** HOLD BINARY INFO
AND

- **EXTERNAL GATES** CONTROL WHEN & HOW
NEW BINARY INFO IS TRANSFERRED TO FF'S

- * (THE CONTENT OF A REGISTER = **WORD** = BIT STREAM STORED IN FF'S)

- * (THE LENGTH OF A REGISTER = **WORD LENGTH** = # OF FF'S IN A REGISTER)

- * ALL REGISTERS (EXCEPT GATED LATCHES) ARE BUILT BY USING FF'S
THAT ARE SENSITIVE TO **PULSE TRANSITION** RATHER THAN TO **PULSE DURATION**

H. Ural

2


* THE TRANSFER OF NEW BINARY INFO INTO A REGISTER IS CALLED **LOADING**

* **SERIAL LOAD** (TRANSFER IN SERIAL MODE)

TRANSFER OF NEW BINARY INFO INTO A REGISTER BIT BY BIT

(# OF CLOCK PULSES NEEDED TO LOAD THE REGISTER = # OF FF'S IN THE REGISTER)

e.g., Let A and B be two 5-bit registers

 


* **PARALLEL LOAD** (TRANSFER IN PARALLEL MODE)

TRANSFER OF NEW BINARY INFO INTO A REGISTER AS A WHOLE WORD

(# OF CLOCK PULSES NEEDED TO LOAD THE REGISTER = 1)

e.g., Let A and B be two 5-bit registers

 


H. Ural

3

e.g., 4-BIT REGISTER WITH PARALLEL LOAD

RESETTING

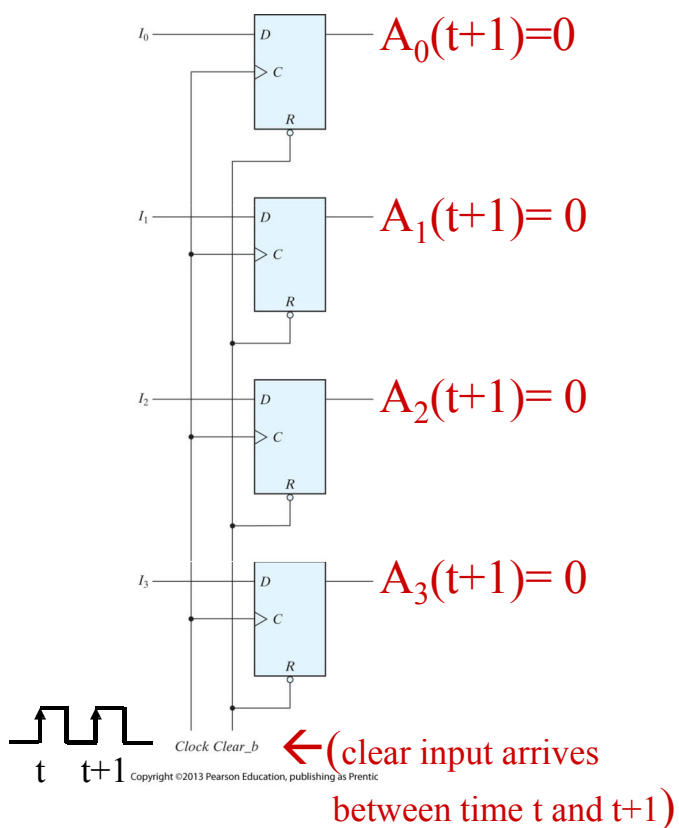


H. Ural

4

e.g., 4-BIT REGISTER WITH PARALLEL LOAD

REFRESHING

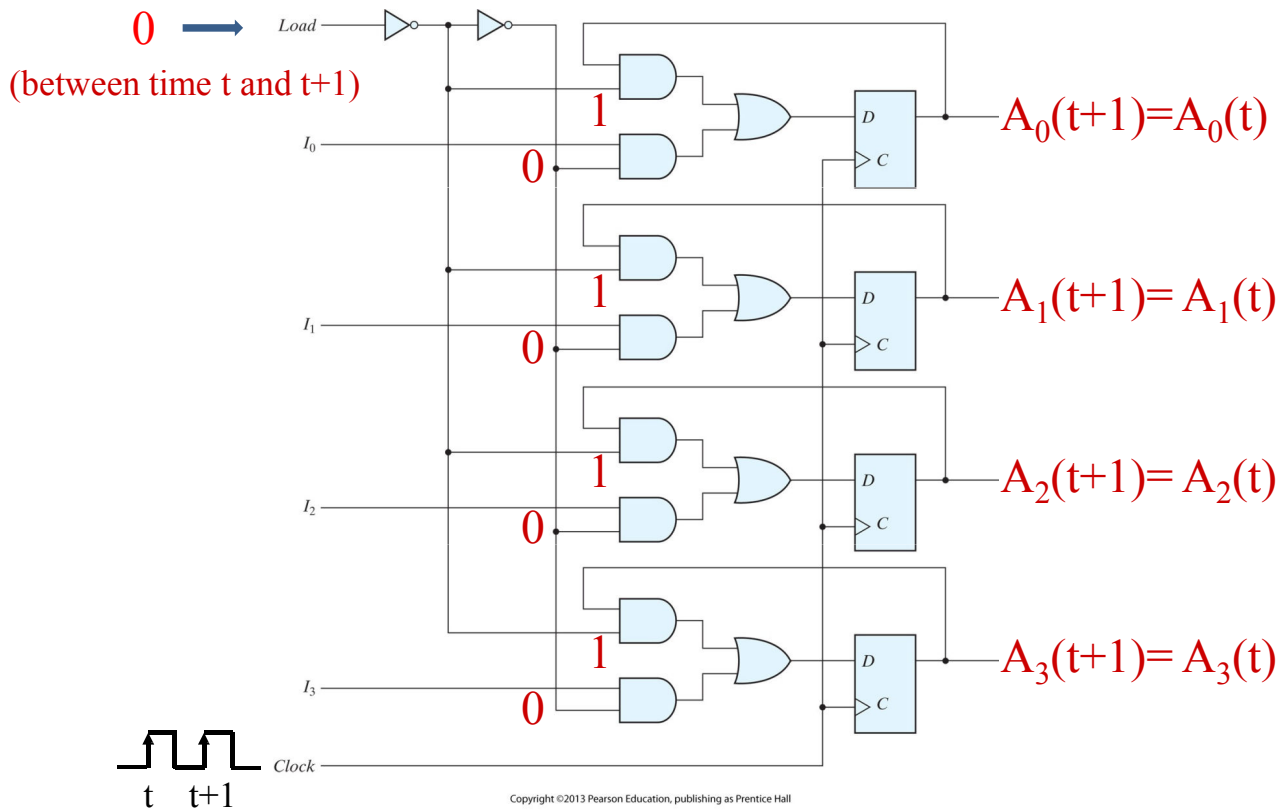


H. Ural

5

e.g., 4-BIT REGISTER WITH PARALLEL LOAD


LOADING

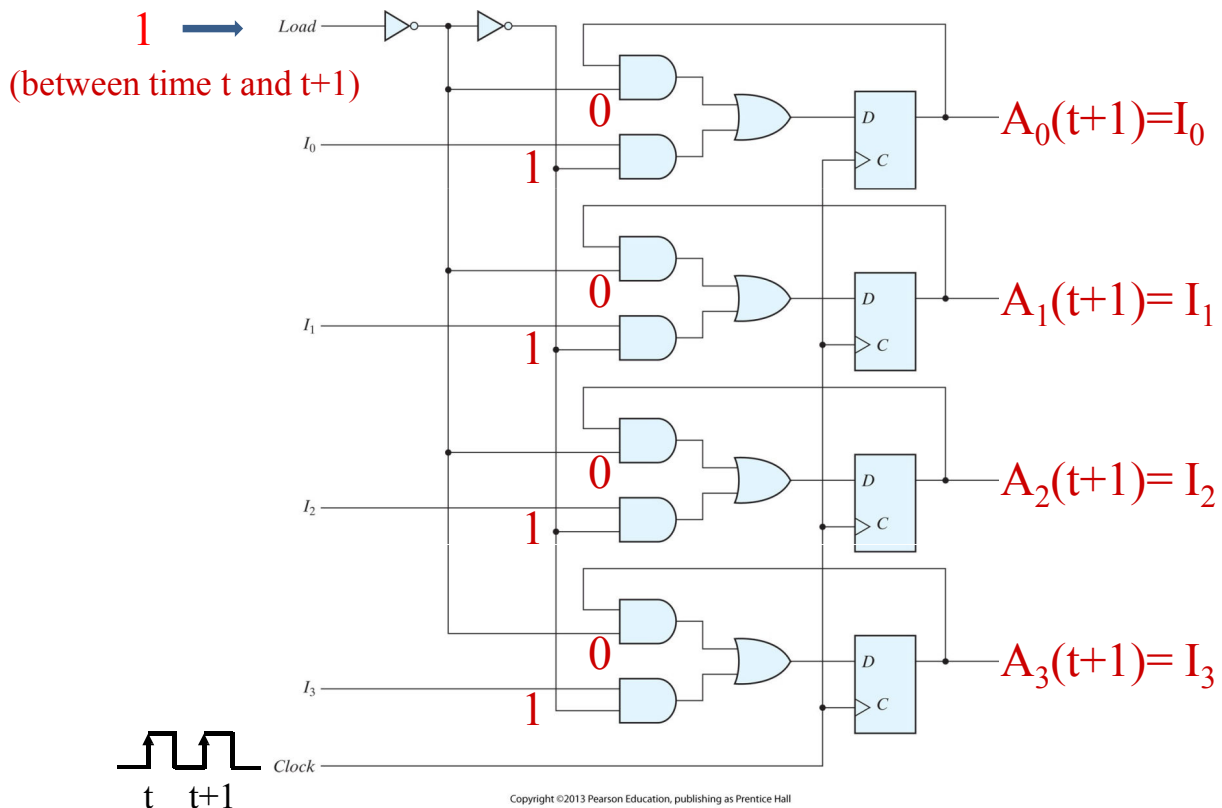

H. Ural

6


TRANSFER IN PARALLEL MODE

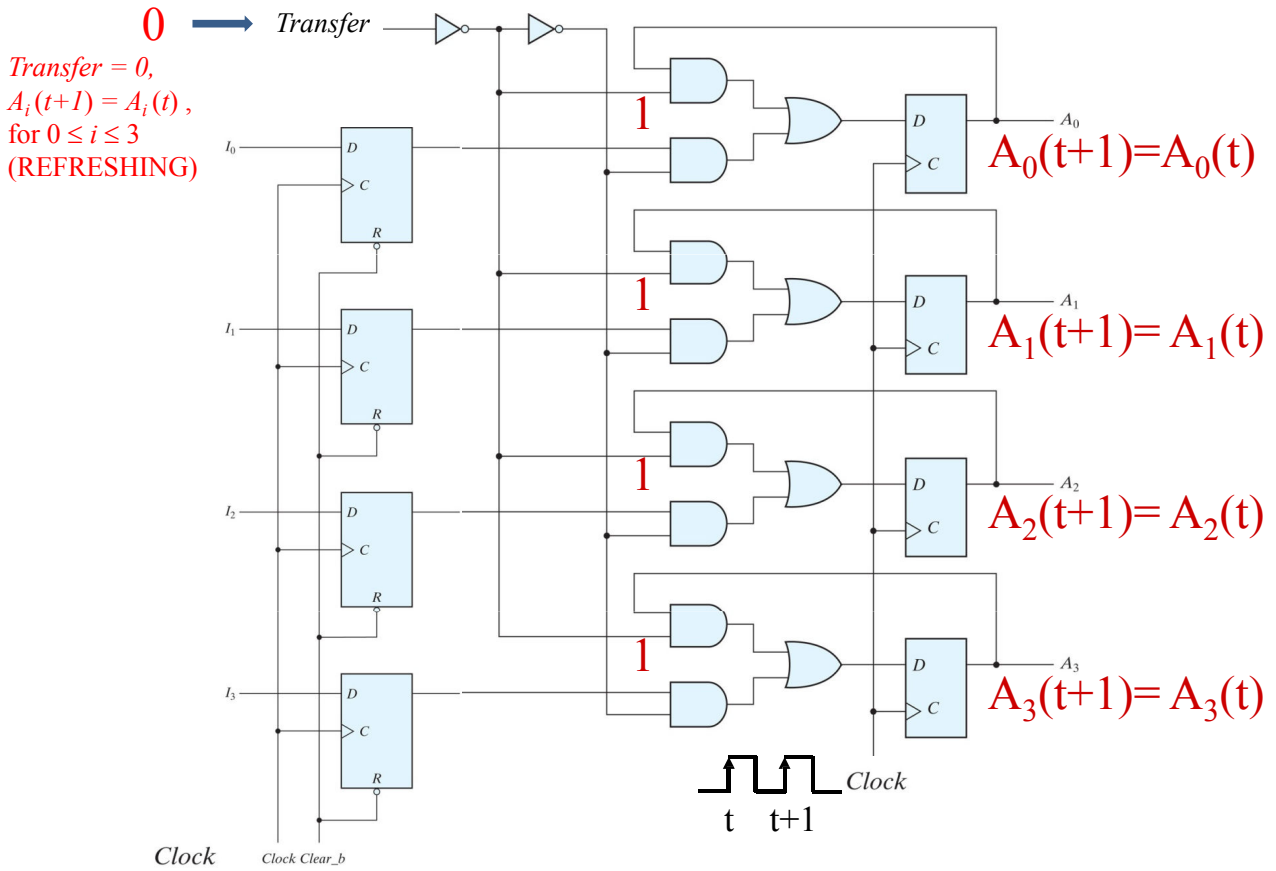

H. Ural

7

TRANSFER IN PARALLEL MODE

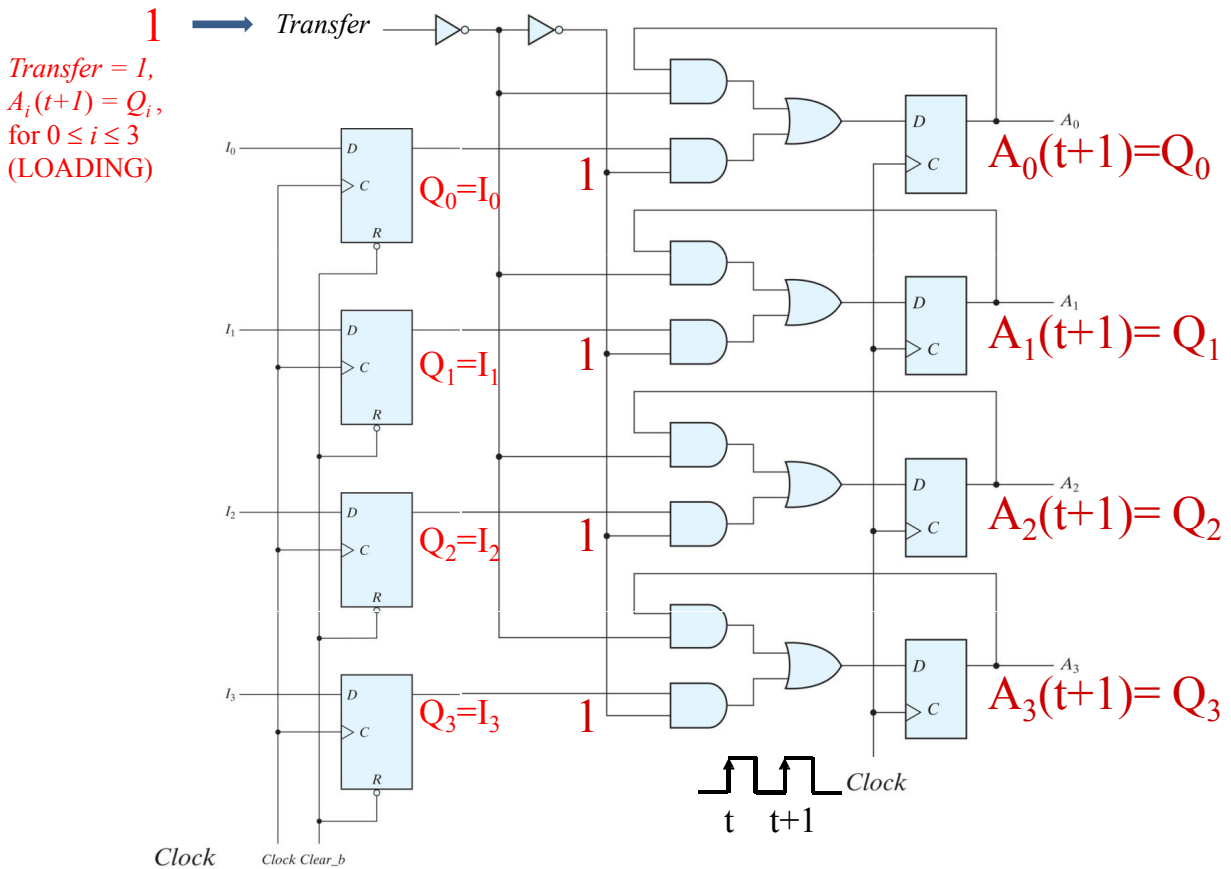

H. Ural

8


SHIFT REGISTER

A REGISTER CAPABLE OF SHIFTING ITS BINARY INFO TO ITS LEFT OR RIGHT

A REGISTER WHERE RS-FF OR D-FF'S ARE CONNECTED IN CASCADE

- UNIDIRECTIONAL
- BIDIRECTIONAL

 UNIDIRECTIONAL 4-BIT SHIFT REGISTER (Shifts RIGHT)




Copyright ©2013 Pearson Education, publishing as Prentice Hall

TRANSFER IN SERIAL MODE

(BIT TIME) : TIME INTERVAL BETWEEN CLOCK PULSES


(WORD TIME) : TIME INTERVAL NEEDED TO SHIFT THE ENTIRE CONTENT OF A REGISTER

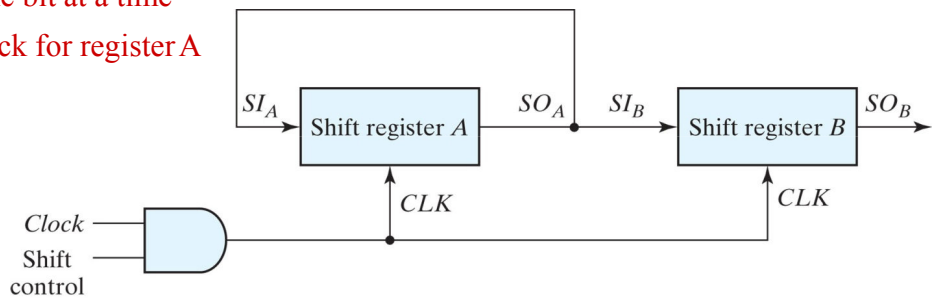- Data is transferred one bit at a time
- Note the data loop back for register A



(a) Block diagram

Time	A	B
T0	1011	0011
T1	1101	1001
T2	1110	1100
T3	0111	0110
T4	1011	1011

 

(b) Timing diagram

Copyright ©2013 Pearson Education, publishing as Prentice Hall

BIDIRECTIONAL SHIFT REGISTER WITH PARALLEL LOAD


 


Table 6.3
Function Table for the Register of Fig. 6.7


Mode Control		
s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

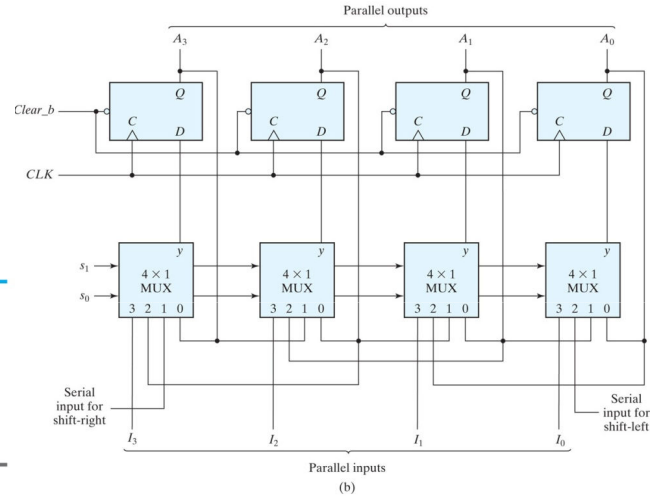

Copyright ©2013 Pearson Education, publishing as Prentice Hall
FIGURE 6.7 Four-bit universal shift register

$S_1 S_0 = 00 \rightarrow$ NO CHANGE

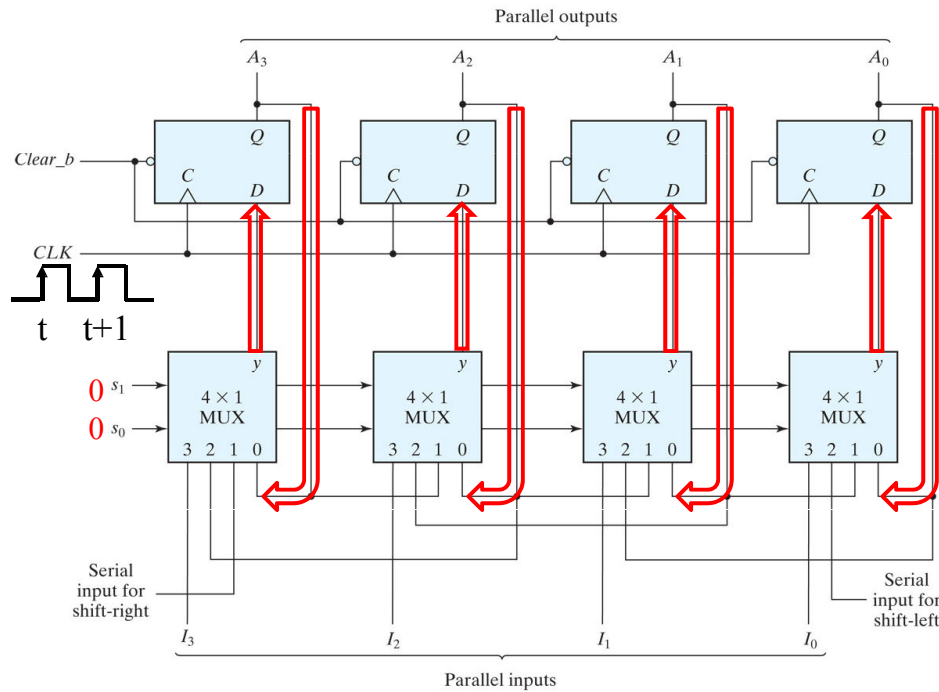
$A_i(t+1) = A_i(t)$ for $0 \leq i \leq 3$



$S_1 S_0 = 01 \rightarrow$ SHIFT RIGHT

$A_i(t+1) = A_{i+1}(t)$ for $0 \leq i \leq 2$

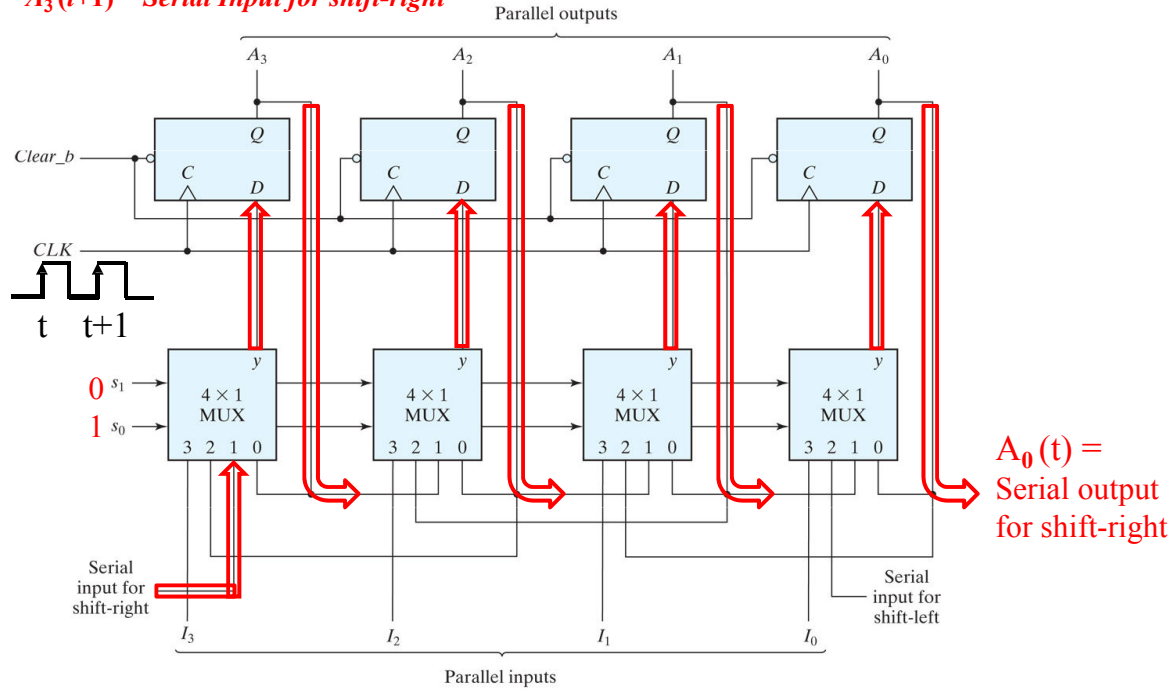$A_3(t+1) =$ Serial Input for shift-right




$S_1 S_0 = 10 \rightarrow$ SHIFT LEFT

$A_{i+1}(t+1) = A_i(t)$ for $0 \leq i \leq 2$


$A_0(t+1) =$ Serial Input for shift-left

$A_3(t) =$
Serial output
for shift-left

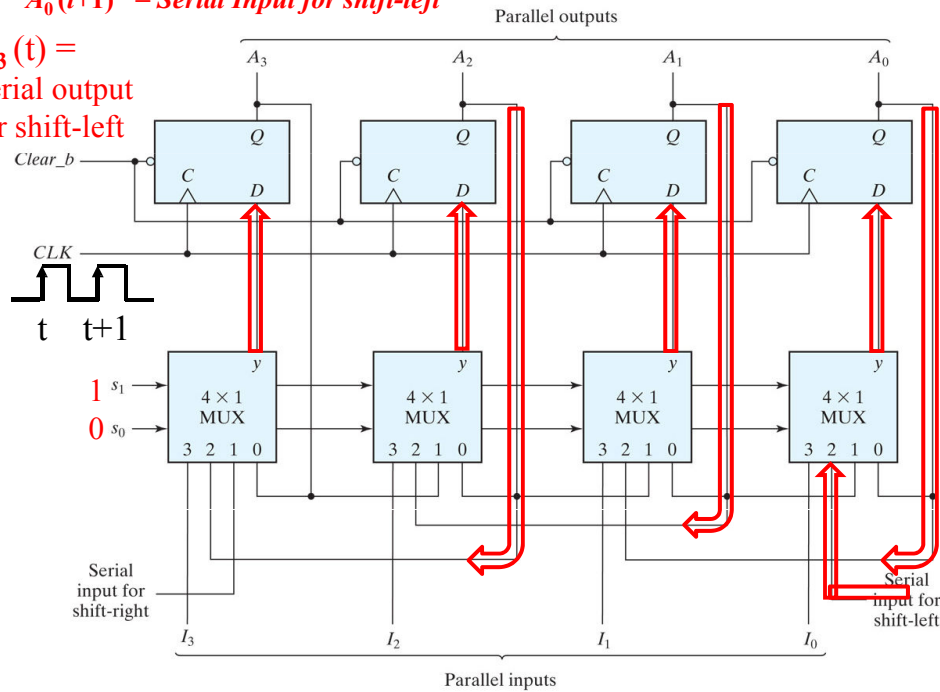

$S_1 S_0 = 11 \rightarrow$ PARALLEL LOAD

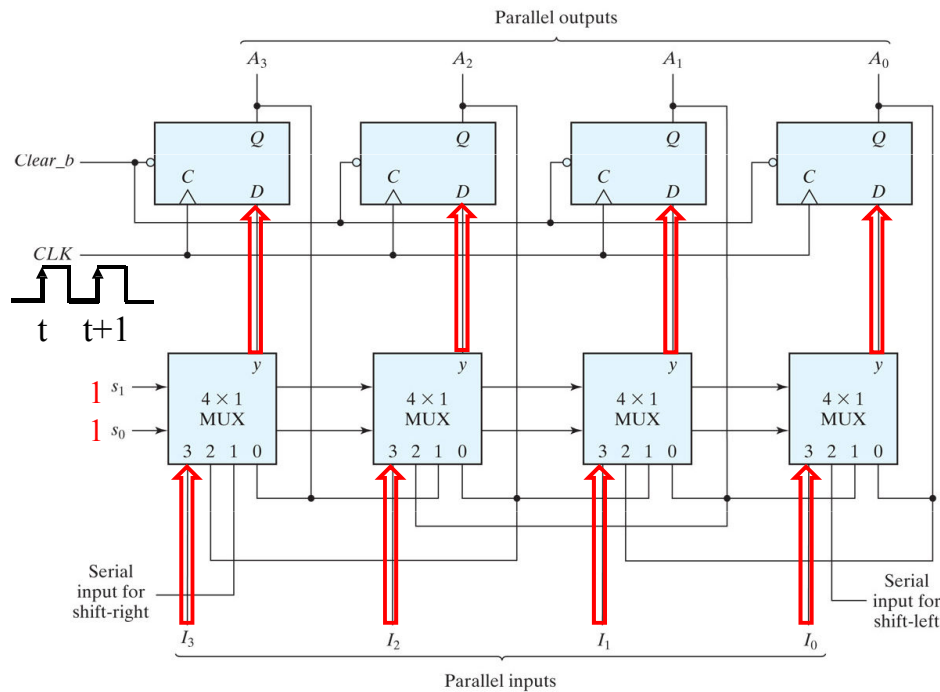$A_i(t+1) = I_i(t)$ for $0 \leq i \leq 3$



H. Ural

15

COUNTER

A SEQUENTIAL CIRCUIT

(a cascade of JK or T FF's, such as a register)

THAT GOES THROUGH A PREDETERMINED SEQUENCE OF STATES

A) RIPPLE COUNTER

A counter in which CP inputs of all FF's (except the 1st FF) are triggered not by incoming clock pulses but rather by state transitions that occur in the preceding FF's

B) SYNCHRONOUS COUNTER

A counter in which CP inputs of all FF's are triggered by incoming clock pulses

Terminology for Counters:

MODULUS (or MOD) : The number of states in the count sequence

Maximum MOD : The maximum number of states = 2^n

where n is the number of bits used to represent a state

e.g., Mod-8 Binary Counter : Count Sequence is 0, 1, 2, 3, 4, 5, 6, 7, and repeat

Each state requires 3 bits to be represented, thus $n=3$ which means that maximum MOD is 8.

Sequential count sequence : natural numeric count

e.g., Count Sequence 0, 1, 2, 3, 4, 5, 6, 7 is a sequential count sequence.

Up/Down count sequence: Increasing (up) or decreasing (down) count sequence

e.g., 0, 1, 2, 3, 4, 5, 6, 7 is Up and 7, 6, 5, 4, 3, 2, 1, 0 is Down count sequence

Full count sequence : The number of states = Maximum Mod.

e.g., Mod-8 Binary counter with 3 bits used for representing states.

Truncated count sequence : The number of states < Maximum Mod.

e.g., Mod-6 Binary counter (0, 1, 2, 3, 4, 5) with 3 bits used for representing states

where states 6 and 7 are not used (missing states).

A truncated count sequence may or may not be sequential:

0, 1, 2, 3, 4, 5 or 1, 3, 4, 5, 6, 7 or 0, 2, 3, 5, 6, 7, etc.

H. Ural

16

A) RIPPLE COUNTER

1) BINARY RIPPLE COUNTER

e.g., a binary ripple counter counting from 0 to 15 and repeating


Count Sequence

A ₃	A ₂	A ₁	A ₀
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Note that

- Count starts with binary 0 and increments by 1 with each clock pulse
- A₀ is alternating with each clock pulse
- Each time A₀ goes from 1 to 0, it complements A₁
- Each time A₁ goes from 1 to 0, it complements A₂
- Each time A₂ goes from 1 to 0, it complements A₃

FIGURE 6.8 Four-bit binary ripple counter

 

Note that

In both circuits ,

- FFs respond to the negative edge transition (from 1 to 0) (notice circle at C input of each FF)
- Output of each FF goes to the C input of the next FF
- A₀ (the FF holding the LSB) gets the count pulses
- When a FF goes from 1 to 0, it complements the next FF



In Figure 6.8.a),

T inputs of all FFs are connected to a permanent logic 1 which makes each FF complement if C input goes from 1 to 0 (this happens when the output of the previous FF goes from 1 to 0)

In Figure 6.8.b),

D input of each FFs is connected to its complement output which makes each FF complement its state if C input goes from 1 to 0 (this happens when the output of the previous FF goes from 1 to 0)

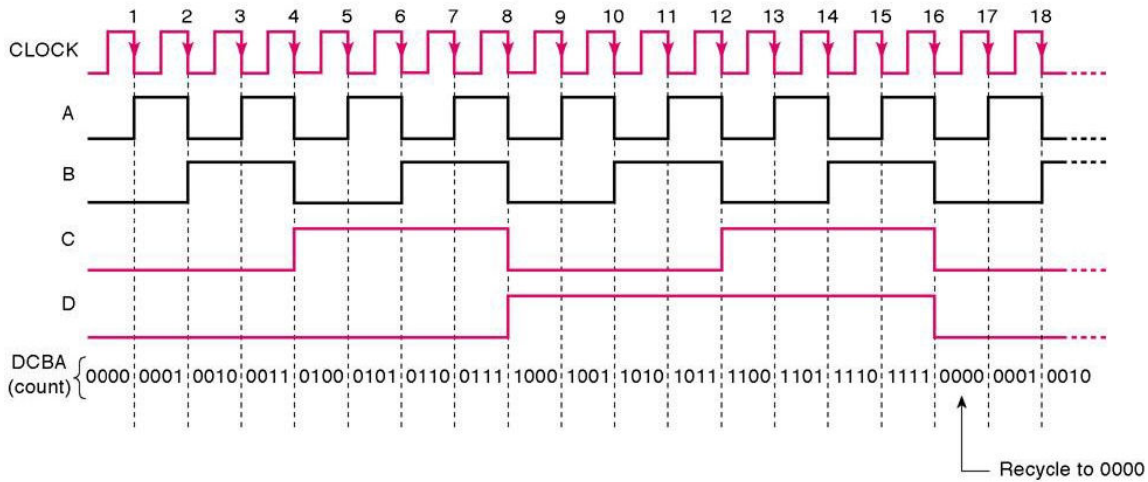 e.g., Four-bit binary ripple counter with JK-FFs
 (with J and K inputs of each FF is connected to Logic 1)
 Note that
 if $J=K=1$, then JK-FF toggles (like T FF toggles when $T=1$)



H. Ural

19

2) BCD RIPPLE COUNTER

 


FIGURE 6.9 State diagram of a decimal BCD counter

if $J = 1$, SET. if $K = 1$, RESET
 if $J=K=0$ then no change (**hold**)
 if $J=K=1$ then toggle (**complement**)

Note that in Figure 6.10,
 $K = 1$ for all FFs.

Thus, if $J=1$ also, the FF toggles
 when C goes from 1 to 0.

From Figure 6.9, observe that

Q_1 changes state after each count pulse.

Q_2 complements each time Q_1 goes from 1 to 0, as long as $Q_8 = 0$
 Q_2 remains at 0 when Q_8 becomes 1.

Q_4 complements each time Q_2 goes from 1 to 0.

Q_8 remains at 0 as long as Q_2 or Q_4 is 0.

When both Q_2 and Q_4 are 1, Q_8 complements when Q_1 goes from 1 to 0.

Q_8 is reset on the next transition of Q_1 .


 


FIGURE 6.10 BCD ripple counter

H. Ural

20

FIGURE 6.11 Block diagram of a three-decade decimal BCD counter

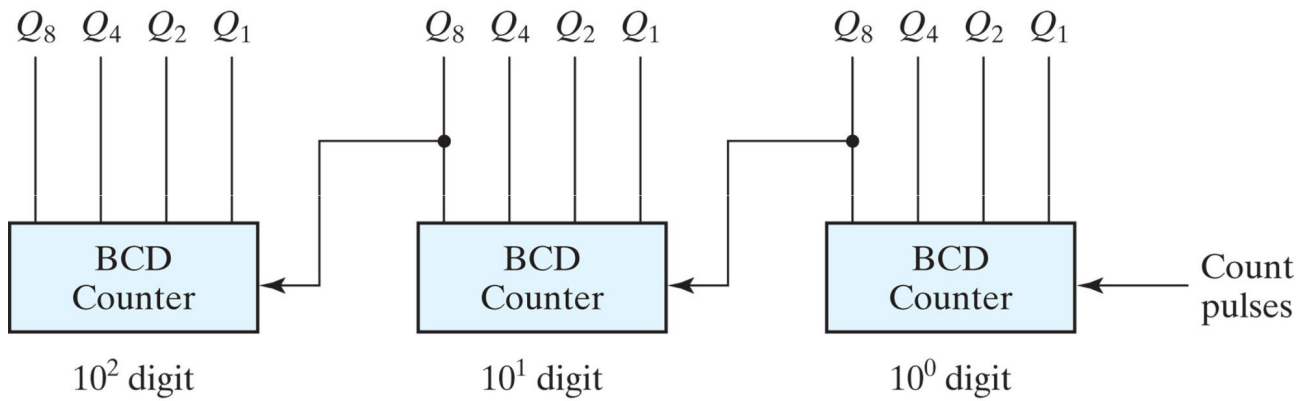

Copyright ©2013 Pearson Education, publishing as Prentice Hall

B) SYNCHRONOUS COUNTER

A counter in which CP inputs of all FF's are triggered by incoming clock pulses

1) BINARY SYNCHRONOUS COUNTER

LSB is complemented at each clock pulse.

Other bits are complemented when all of its lower significant bits are 1.

e.g., a binary synchronous counter counting from 0 to 7 and repeating

Count Sequence	Present State	Next State
	A B C	A B C
0 0 0	0 0 0	0 0 1
0 0 1	0 0 1	0 1 0
0 1 0	0 1 0	0 1 1
0 1 1	0 1 1	1 0 0
1 0 0	1 0 0	1 0 1
1 0 1	1 0 1	1 1 0
1 1 0	1 1 0	1 1 1
1 1 1	1 1 1	0 0 0

e.g., Using T FFs, design a mod-8 binary synchronous counter

Count Sequence	Present State	Next State	Flip - Flop Inputs		
			A B C	A B C	$T_A T_B T_C$
000	000	001	0	0	1
001	001	010	0	1	1
010	010	011	0	0	1
011	011	100	1	1	1
100	100	101	0	0	1
101	101	110	0	1	1
110	110	111	0	0	1
111	111	000	1	1	1

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

$$T_A = \Sigma m(3,7)$$


$$T_B = \Sigma m(1,3,5,7)$$

$$T_C = 1$$

$$T_A = \Sigma m(3,7) = BC \text{ (using K-Maps)}$$

$$T_B = \Sigma m(1,3,5,7) = C \text{ (using K-Maps)}$$


$$T_C = 1$$

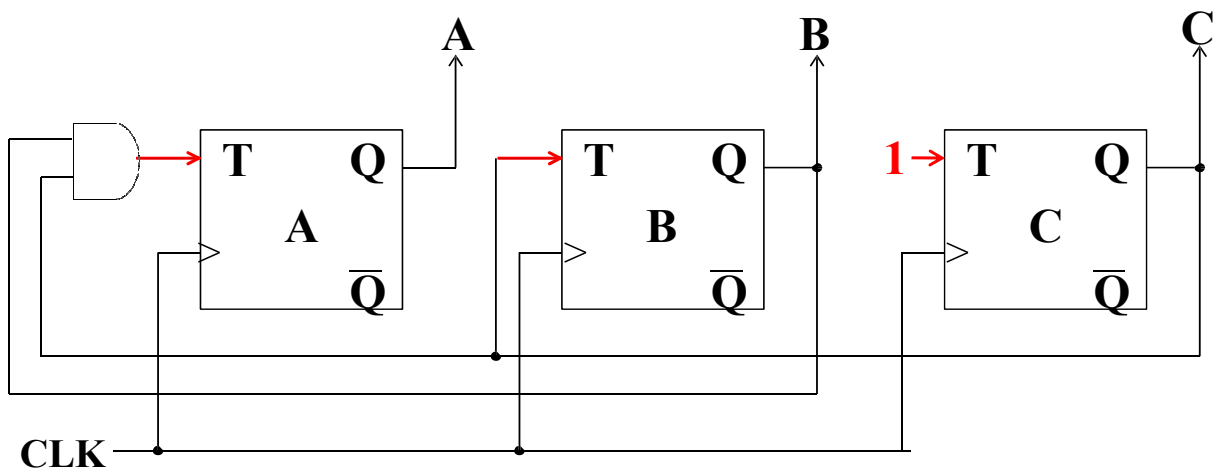

e.g., Using D FFs, design a mod-8 binary synchronous counter

Count Sequence	Present State	Next State	Flip - Flop Inputs		
			A B C	A B C	$D_A D_B D_C$
0 0 0	0 0 0	0 0 1	0	0	1
0 0 1	0 0 1	0 1 0	0	1	0
0 1 0	0 1 0	0 1 1	0	1	1
0 1 1	0 1 1	1 0 0	1	0	0
1 0 0	1 0 0	1 0 1	1	0	1
1 0 1	1 0 1	1 1 0	1	1	0
1 1 0	1 1 0	1 1 1	1	1	1
1 1 1	1 1 1	0 0 0	0	0	0

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

 


$$D_A = \Sigma m(3,4,5,6)$$

$$D_B = \Sigma m(1,2,5,6)$$

$$D_C = \Sigma m(0,2,4,6)$$


$$D_A = \Sigma m(3,4,5,6)$$

$$D_A = AB' + AC' + A'BC$$

 


$$D_B = \Sigma m(1,2,5,6)$$

$$D_B = BC' + B'C$$

 

$$D_C = \Sigma m(0,2,4,6)$$


$$D_C = C'$$

 

e.g., Using JK FFs, design a mod-8 binary synchronous counter

Count Sequence	Present State	Next State	Flip - Flop Inputs		
			A B C	A B C	$J_A K_A$ $J_B K_B$ $J_C K_C$
0 0 0	0 0 0	0 0 1	0 X	0 X	1 X
0 0 1	0 0 1	0 1 0	0 X	1 X	X 1
0 1 0	0 1 0	0 1 1	0 X	X 0	1 X
0 1 1	0 1 1	1 0 0	1 X	X 1	X 1
1 0 0	1 0 0	1 0 1	X 0	0 X	1 X
1 0 1	1 0 1	1 1 0	X 0	1 X	X 1
1 1 0	1 1 0	1 1 1	X 0	X 0	1 X
1 1 1	1 1 1	0 0 0	X 1	X 1	X 1

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 

$$J_A = \Sigma m(3), d(4,5,6,7) \quad K_A = \Sigma m(7), d(0,1,2,3)$$


$$J_B = \Sigma m(1,5), d(2,3,6,7) \quad K_B = \Sigma m(3,7), d(0,1,4,5)$$

$$J_C = 1 \quad K_C = 1$$


$$J_A = \Sigma m(3), d(4,5,6,7) \quad K_A = \Sigma m(7), d(0,1,2,3)$$

$$J_B = \Sigma m(1,5), d(2,3,6,7) \quad K_B = \Sigma m(3,7), d(0,1,4,5)$$


$$J_C = 1 \quad K_C = 1$$

 


$$J_A = BC$$

 


$$K_A = BC$$

 

$$J_B = C$$

 

$$K_B = C$$

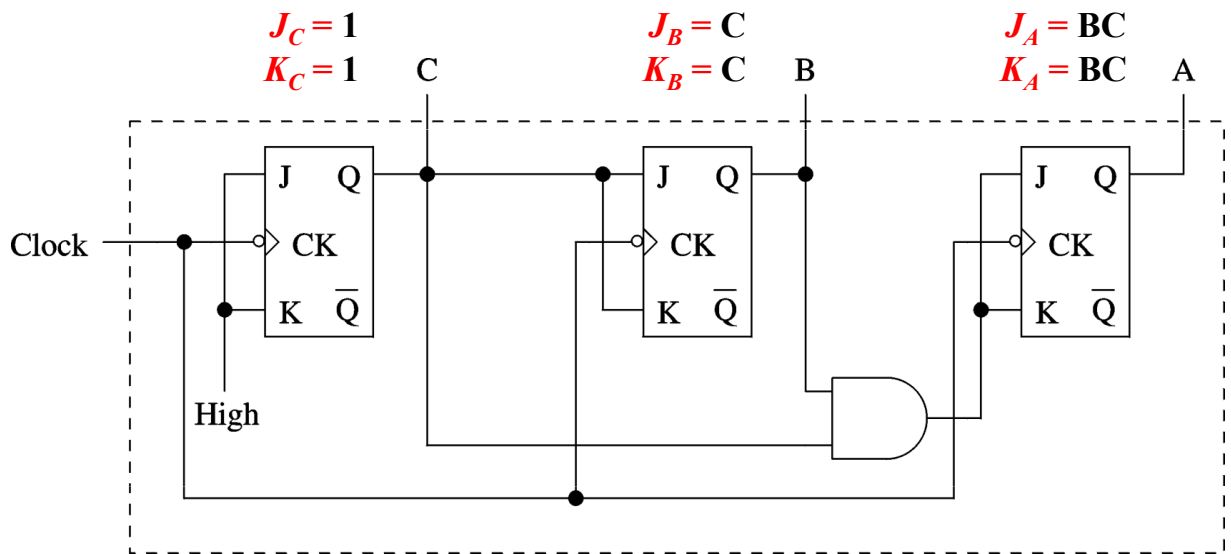


Binary Synchronous Counter with Missing States

e.g., Design a counter with count sequence 0, 1, 2, 4, 5, 6 (and repeat) by using JK-FFs

Note that states 3 and 7 (i.e., 011 and 111 are missing (not used))

State Diagram

 


State Table

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Minterms	Present State			Next State			Flip-Flop Inputs					
	A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	0	1	0	X	0	X	1	X
1	0	0	1	0	1	0	0	X	1	X	X	1
2	0	1	0	1	0	0	1	X	X	1	0	X
4	1	0	0	1	0	1	X	0	0	X	1	X
5	1	0	1	1	1	0	X	0	1	X	X	1
6	1	1	0	0	0	0	X	1	X	1	0	X
3							X	X	X	X	X	X
7							X	X	X	X	X	X

 
For minterms 3 and 7, J and K inputs of all FFs are DONT CARES



H. Ural

31

FIGURE 6.16 Counter with unused states

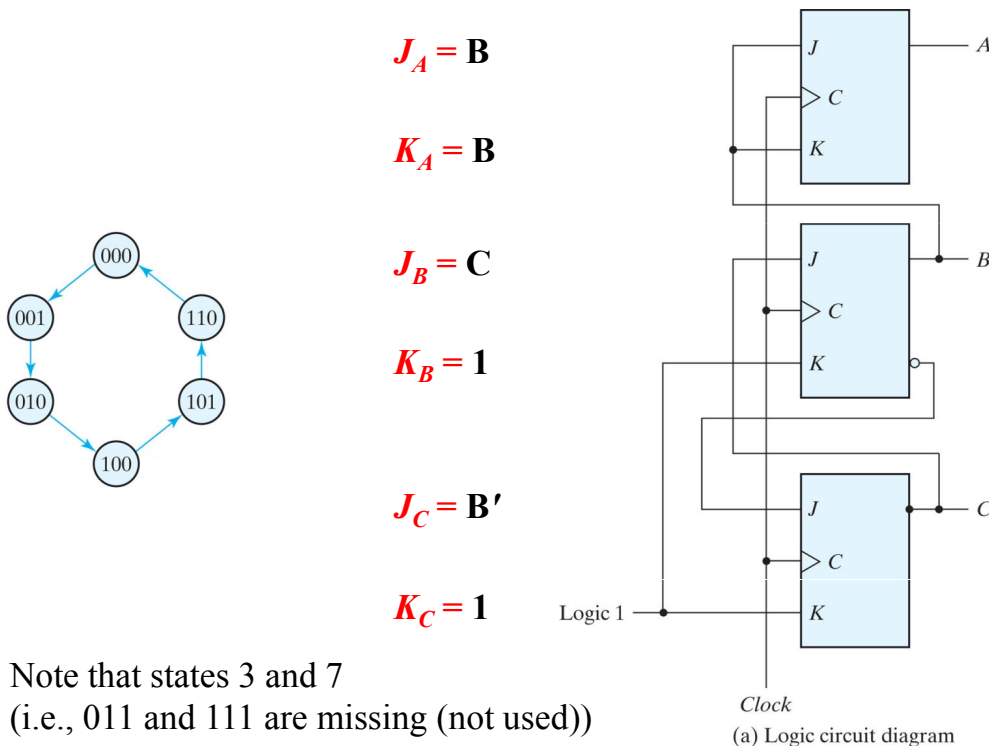

Copyright ©2013 Pearson Education, publish

H. Ural

32

What if the counter goes into state 3 or state 7?

Recall that states 3 and 7 (i.e., 011 and 111 are missing (not used))

If the counter goes into state 3 (i.e., 011) or state 7 (i.e. 11110), what is the next state, when the next clock pulse arrives?

$$J_A = B \quad J_B = C \quad J_C = B'$$


$$K_A = B \quad K_B = 1 \quad K_C = 1$$

For state 011, we put $A(t)=0, B(t)=1, C(t)=1$ into above FF input functions and come up with:
 $A(t+1)=A(t)'=1$ because $J_A=1$ and $K_A=1$.
 $B(t+1)=B(t)'=0$ because $J_B=1$ and $K_B=1$.
 $C(t+1)=0$ because $J_C=0$ and $K_C=1$.

For state 111, we put $A(t)=1, B(t)=1, C(t)=1$ into above FF input functions and come up with:
 $A(t+1)=A(t)'=0$ because $J_A=1$ and $K_A=1$.
 $B(t+1)=B(t)'=0$ because $J_B=1$ and $K_B=1$.
 $C(t+1)=0$ because $J_C=0$ and $K_C=1$.

Next state is 100

Next state is 000

 

SELF CORRECTING COUNTER

e.g., Using JK FFs, design a mod-16 binary synchronous counter

Present State	Next State	Flip Flop Input Functions			
$A_3 A_2 A_1 A_0$	$A_3 A_2 A_1 A_0$	$J_{A3} K_{A3}$	$J_{A2} K_{A2}$	$J_{A1} K_{A1}$	$J_{A0} K_{A0}$
0 0 0 0	0 0 0 1	0 X	0 X	0 X	1 X
0 0 0 1	0 0 1 0	0 X	0 X	1 X	X 1
0 0 1 0	0 0 1 1	0 X	0 X	X 0	1 X
0 0 1 1	0 1 0 0	0 X	1 X	X 1	X 1
0 1 0 0	0 1 0 1	0 X	X 0	0 X	1 X
0 1 0 1	0 1 1 0	0 X	X 0	1 X	X 1
0 1 1 0	0 1 1 1	0 X	X 0	X 0	1 X
0 1 1 1	1 0 0 0	1 X	X 1	X 1	X 1
1 0 0 0	1 0 0 1	X 0	0 X	0 X	1 X
1 0 0 1	1 0 1 0	X 0	0 X	1 X	X 1
1 0 1 0	1 0 1 1	X 0	0 X	X 0	1 X
1 0 1 1	1 1 0 0	X 0	1 X	X 1	X 1
1 1 0 0	1 1 0 1	X 0	X 0	0 X	1 X
1 1 0 1	1 1 1 0	X 0	X 0	1 X	X 1
1 1 1 0	1 1 1 1	X 0	X 0	X 0	1 X
1 1 1 1	0 0 0 0	X 1	X 1	X 1	X 1


$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Using K-Maps, one can simplify Flip Flop Input Functions

$$\begin{aligned} J_{A3} &= A_2 A_1 A_0 \\ K_{A3} &= A_2 A_1 A_0 \\ J_{A2} &= A_1 A_0 \\ K_{A2} &= A_1 A_0 \\ J_{A1} &= A_0 \\ K_{A1} &= A_0 \\ J_{A0} &= 1 \\ K_{A0} &= 1 \end{aligned}$$

FIGURE 6.12 Four-bit synchronous binary counter
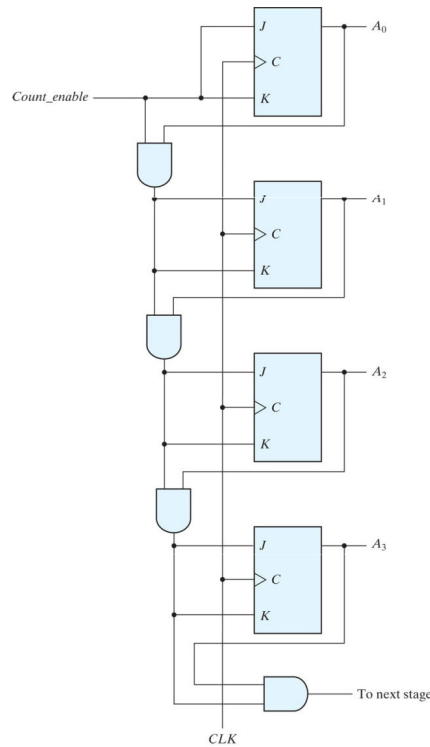
$$\begin{aligned}
 J_{A3} &= A_2 A_1 A_0 \\
 K_{A3} &= A_2 A_1 A_0 \\
 J_{A2} &= A_1 A_0 \\
 K_{A2} &= A_1 A_0 \\
 J_{A1} &= A_0 \\
 K_{A1} &= A_0 \\
 J_{A0} &= 1 \\
 K_{A0} &= 1
 \end{aligned}$$



Copyright ©2013 Pearson Education, publishing as Prentice Hall

H. Ural

35

2) BINARY SYNCHRONOUS UP-DOWN COUNTER

Count-Up Counter

Goes through the binary states in ascending (increasing) order.

LSB is complemented at each clock pulse.

Each other bit is complemented when all of its lower significant bits are 1.

e.g., all counters seen so far are countup counters

Count-Down Counter

Goes through the binary states in descending (decreasing) order

LSB is complemented at each clock pulse.

Each other bit is complemented when all of its lower significant bits are 0.

e.g., A mod-16 binary synchronous countdown counter with JK FFs

Same as the one shown in the previous slide (Figure 6.12),

except that

the inputs to the AND gates must come from

the complemented outputs, instead of the normal outputs of the FFs.


Up-Down Counter

A counter that counts either up or down

H. Ural

36

FIGURE 6.13 Four-bit up-down binary counter

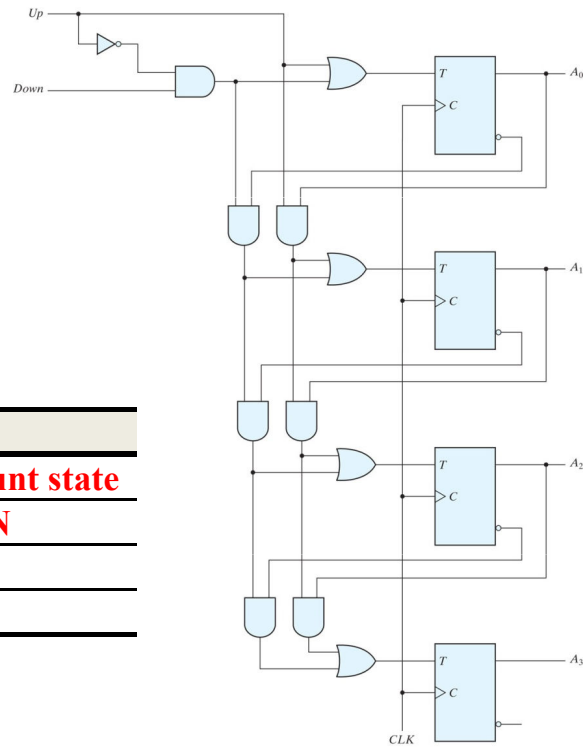

Copyright ©2013 Pearson Education, publishing as Prentice Hall

<i>Up</i>	<i>Down</i>	Circuit
0	0	Remains at the same count state
0	1	COUNTS DOWN
1	0	COUNTS UP
1	1	COUNTS UP

3) BCD SYNCHRONOUS COUNTER

Counts from 0 to 9

e.g., A BCD Synchronous Counter using T FFs

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Table 6.5
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Using the State Table in Table 6.5,
 where minterms m10, to m15 are DONT CARES are not explicitly shown
 one can form the K-Maps for flipflop input functions


$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$T_{Q4} = Q_2Q_1$$

$$T_{Q2} = Q_8'Q_1$$

$$T_{Q1} = 1$$

$$y = Q_8Q_1$$

 


$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$T_{Q4} = Q_2Q_1$$

$$T_{Q2} = Q_8'Q_1$$

$$T_{Q1} = 1$$

$$y = Q_8Q_1$$

 


4) BINARY SYNCHRONOUS COUNTER WITH PARALLEL LOAD

Table 6.6
Function Table for the Counter of Fig. 6.14

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

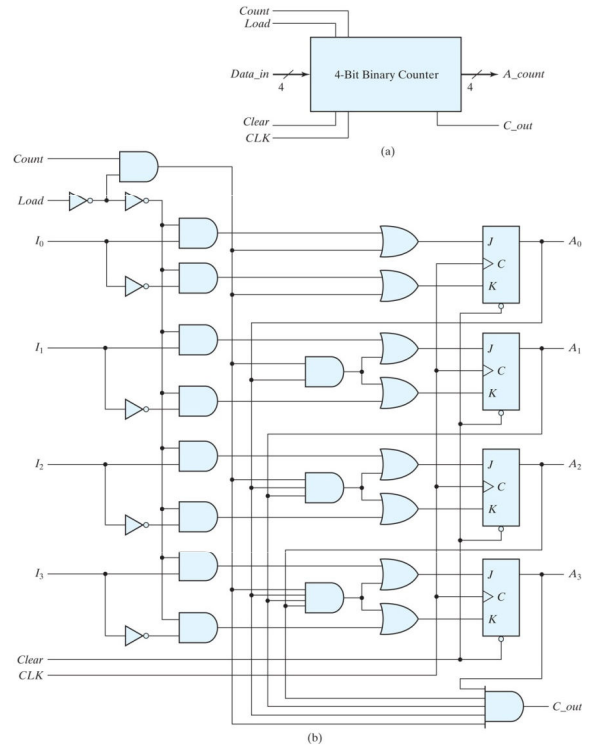Copyright ©2012 Pearson Education, publishing as Prentice Hall




Copyright ©2013 Pearson Education, publishing as Prentice Hall

FIGURE 6.14 Four-bit binary counter with parallel load

$$C\text{-out} = \text{Count } A_3 A_2 A_1 A_0$$


H. Ural

41

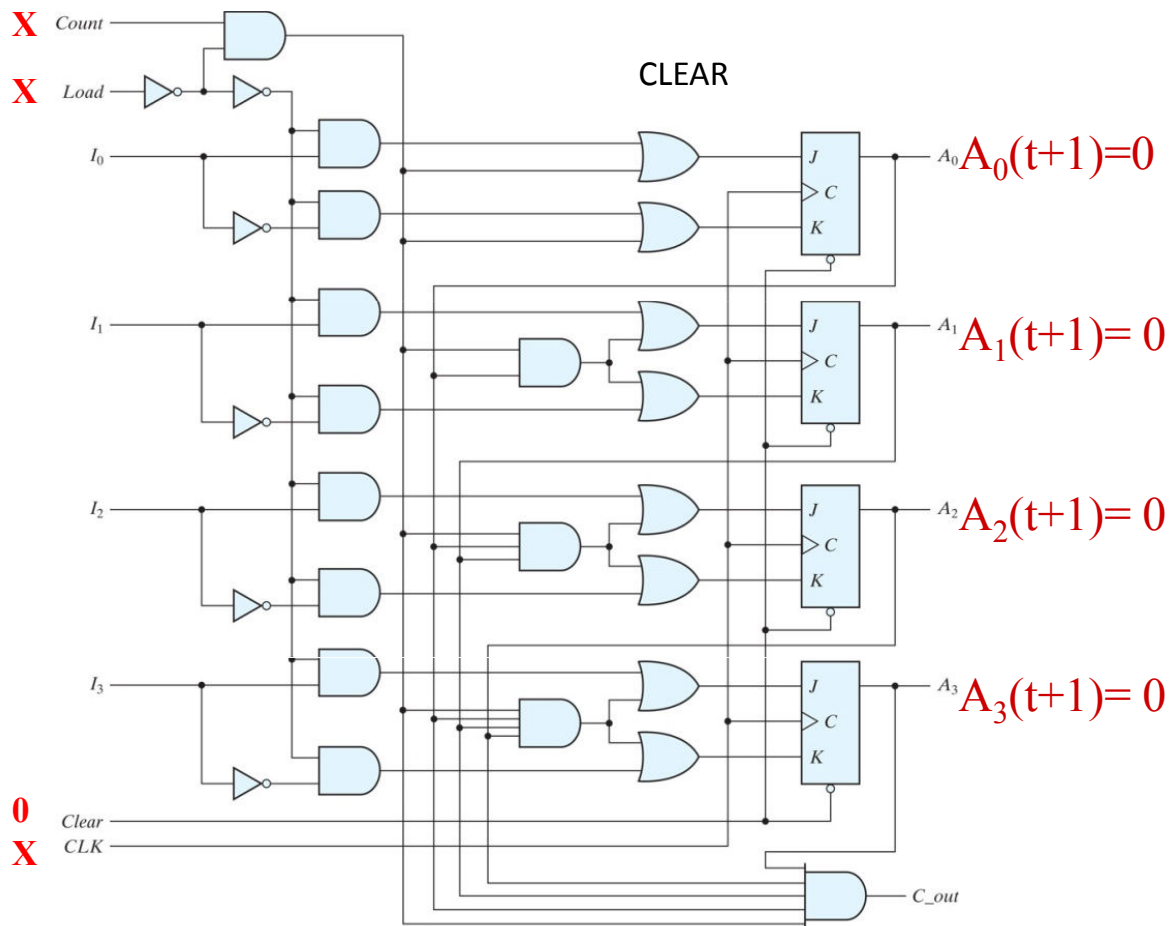


H. Ural

42

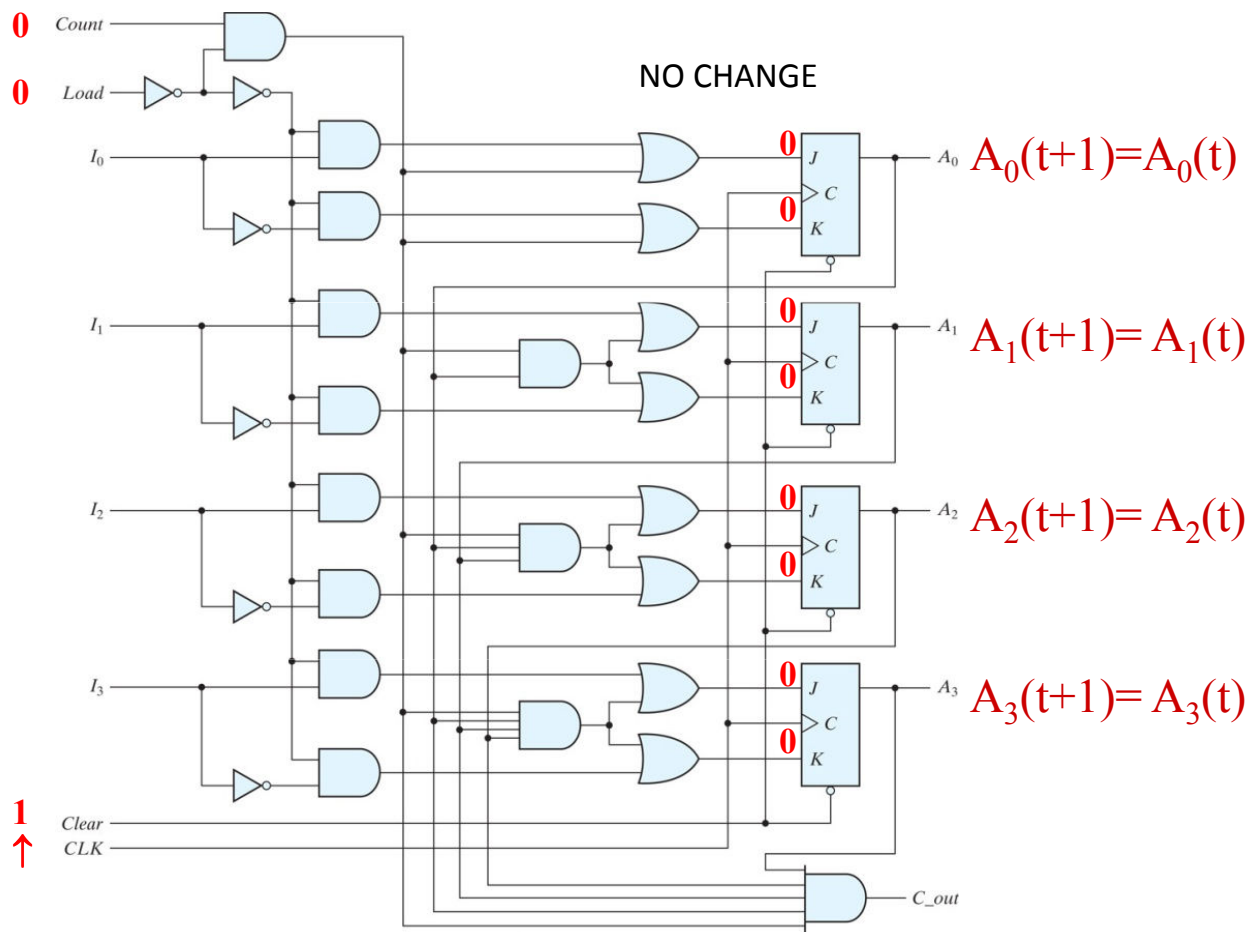


H. Ural

43

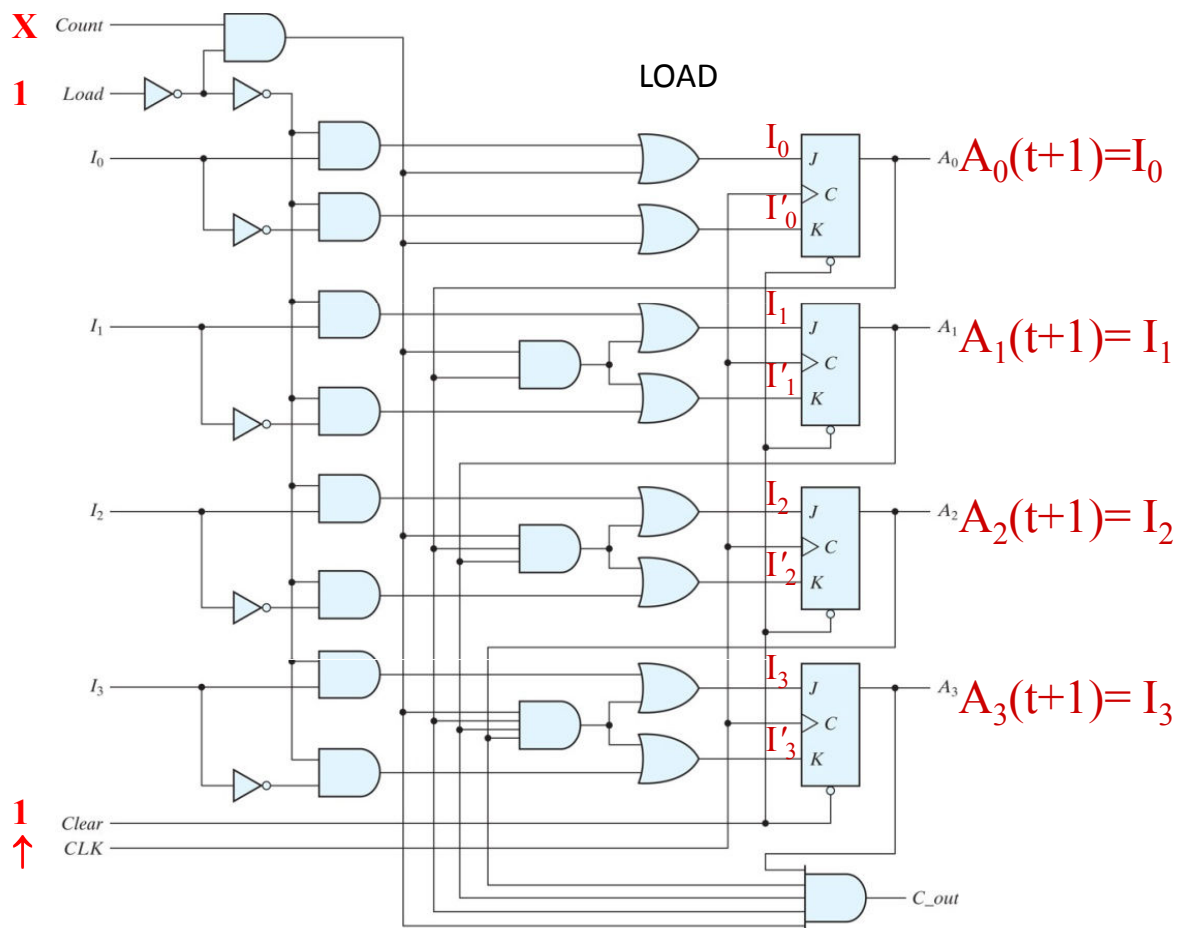

H. Ural


44

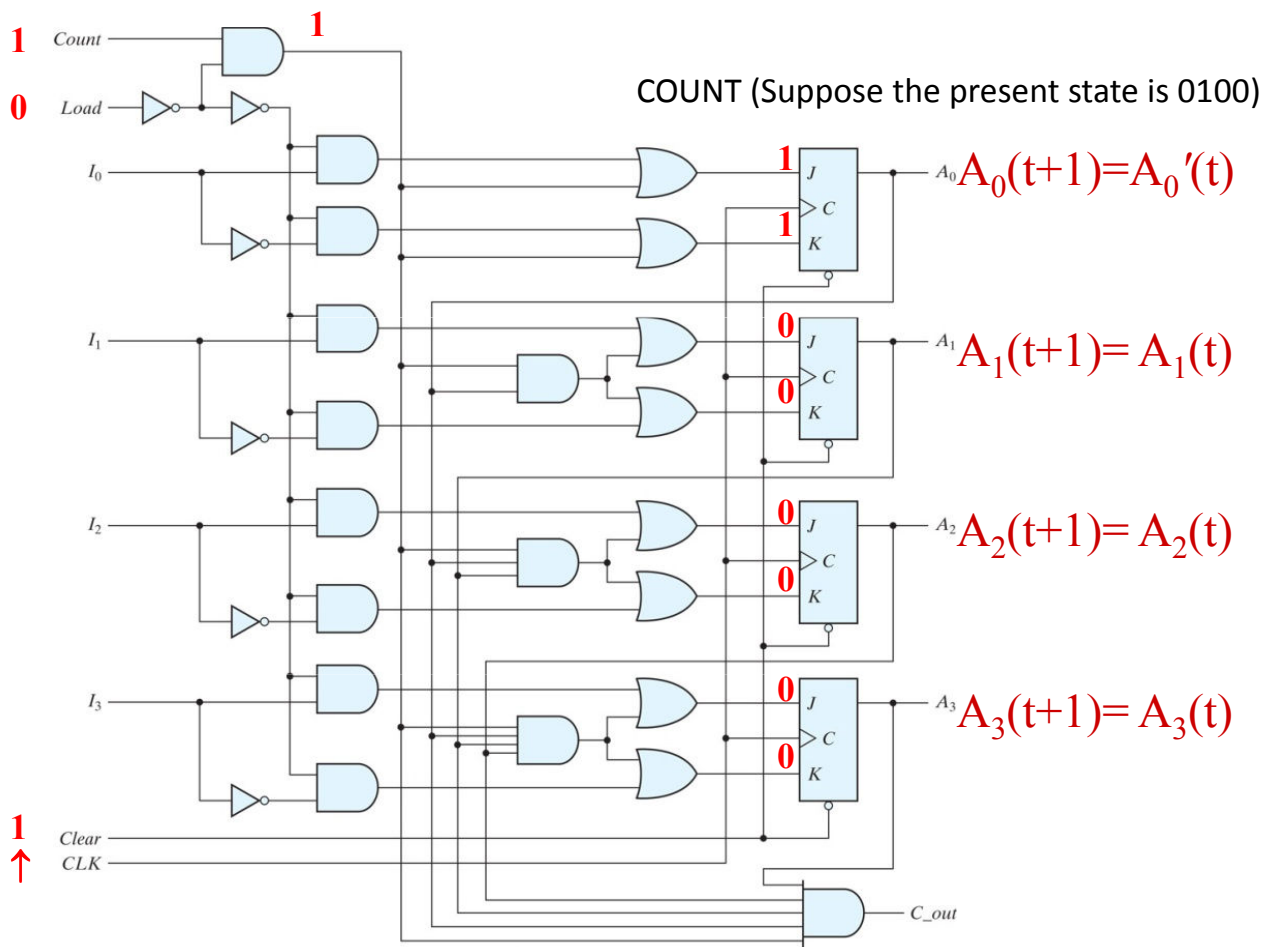

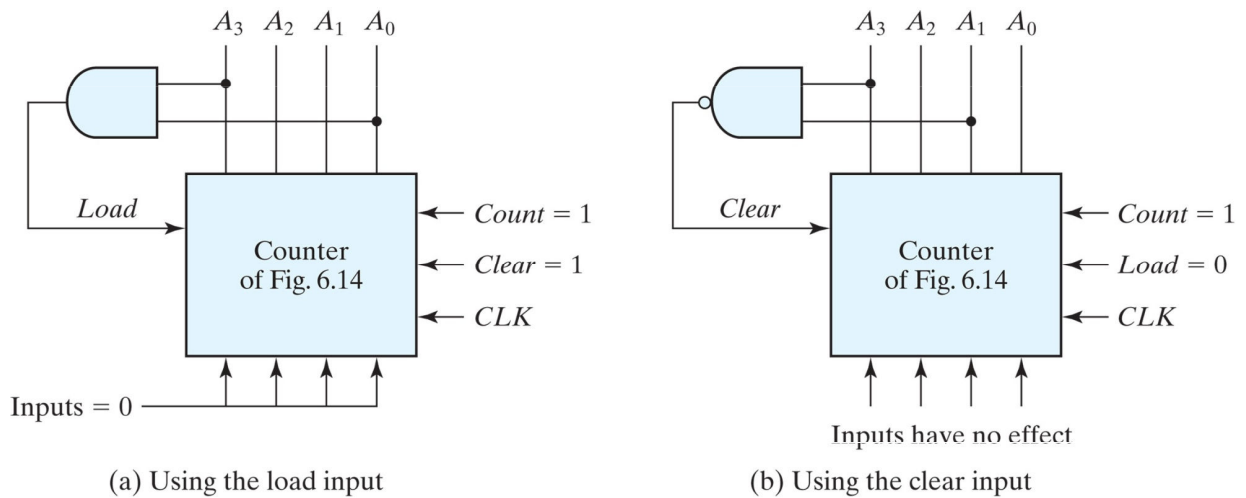H. Ural

45

A BINARY SYNCHRONOUS COUNTER WITH PARALLEL LOAD CAN BE USED TO CONSTRUCT ANY MOD-N COUNTER
e.g., BCD Synchronous Counter



Copyright ©2013 Pearson Education, publishing as Prentice Hall

FIGURE 6.15 Two ways to achieve a BCD counter using a counter with parallel load

H. Ural


46

RING COUNTER

A ring counter takes the serial output of the last Flip-Flop of a shift register and submits it to the serial input of the first Flip-Flop.

It is also called a re-circulating shift register where only one flip flop is set at any particular time while all other flip flops are cleared.

 
e.g., 4-bit shift register connected as a ring counter



Initial state is 1000.

1 is shifted right at each clock pulse and circulates from T3 to T0.

 Since each FF is 1 only once at every 4 clock pulses, it generates four timing signals:




Sequence of four timing signals

 
H. Ural

47

The same four timing signals can be generated by 2-bit counter :



Counter and decoder

 

Sequence of four timing signals

The 2-bit counter goes through states 00, 01, 10, 11 and the 2x4 decoder decodes these four states and generates the required timing sequence.


In summary, to generate 2^n timing signals we need either a shift register with 2^n FFs or an n-bit binary counter and an $n \times 2^n$ decoder.

H. Ural

48

JOHNSON COUNTER

 A Johnson Counter re-circulates the complement output of the last flip-flop back to the input of the first Flip-Flop.



(a) Four-stage switch-tail ring counter

A K-bit switch-tail ring counter goes through a sequence of $2K$ states (in contrast, a K-bit ring counter goes through a sequence of K states).

Sequence number	Flip-flop outputs			
	A	B	C	E
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1

Starting from all 0s, each shift operation inserts 1s from left until all FFs are filled with 1s.

Then, 0s are inserted from left until all FFs are filled with 0s.

Johnson counter can provide $2k$ timing signals with $2k$ decoding gates. Decoding gates are specified in the table below.

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

Johnson counter can be constructed for any no. of timing sequences.

Number of flip flops needed is half the number of timing signals.

Number of decoding gates is equal to number of timing signals and only 2-input gates are needed.