

ITI1100B

Chapter-3

H. Ural

1

GRAPHICAL SIMPLIFICATION (Using KARNAUGH MAPS)

Gate-level minimization refers to finding an optimal gate-level implementation of a Boolean function describing a digital circuit.

Algebraic minimization of a Boolean function may be hard to achieve due to lack of specific rules whereas graphical minimization is simple and straightforward.

Karnaugh Map of a Boolean function defined over n variables is a diagram made up of 2^n squares where each square represents one minterm.

Minterms are placed in a map such that any two neighbours (two adjacent squares) differ ONLY in one literal. e.g., xyz and xyz' are two squares sharing an edge, thus they are neighbours (they are adjacent)

* IN AN n -VARIABLE MAP, EACH SQUARE HAS n ADJACENT SQUARES.


* ANY 2^k ADJACENT SQUARES for $k=0,1,2,\dots,n$ IN AN n -VARIABLE MAP PRESENTS AN AREA THAT GIVES A TERM OF $n-k$ VARIABLES
IF $n = k \Rightarrow$ ENTIRE AREA OF THE MAP \Rightarrow IDENTITY FUNCTION

H. Ural


2

Two Variable Karnaugh Map

		Minterms	
x	y	Terms	Designation
0	0	$x'y'$	m0
0	1	$x'y$	m1
1	0	xy'	m2
1	1	xy	m3

 

(a)

 

(b)

Note that

-row 0 corresponds to x' and **row 1** corresponds to x

-column 0 corresponds to y' and **column 1** corresponds to y

In the 2-VARIABLE MAP, each square has 2 adjacent squares.

i.e., m1 and m2 are adjacent to m0; m1 and m2 are adjacent to m3.

m0 and m3 are adjacent to m1; m0 and m3 are adjacent to m2.

Any 2^k adjacent squares for $k=0,1,2$ in a 2 -VARIABLE MAP is an area that represents a term consisting of $2-k$ literals.

When $k=0$, $2^0=1$.

e.g., m3 is an area that represents a term consisting of 2 literals , i.e., xy .

When $k=1$, $2^1=2$.

e.g., m2 and m3 is an area that represents a term consisting of 1 literal , i.e., x .

e.g., m0 and m2 is an area that represents a term consisting of 1 literal , i.e., y' .

When $k=2$, $2^2=4$. $n=k$. The entire map represents a term with no literals, i.e., 1 (IDENTITY)

H. Ural

3

Forming groups of squares in Karnaugh Maps

Groups of squares are formed in considering the following rules:


- Every square containing 1 must be considered at least once**
- A square containing 1 can be included in as many groups as desired**
- A group must be as large as possible (i.e., largest number of squares)**
- The number of squares in a group must be equal to 2^k , i.e., 1, 2, 4, 8...**

The simplified Boolean expression obtained as a SOP from a Karnaugh map is not always unique because groups can be formed in different ways.

Examples of Two Variable Karnaugh Maps

	x	y	f1
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1

$$f1(x,y) = \Sigma m(3)$$

 


(a) xy

$$\begin{aligned} f1(x,y) &= \Sigma m(3) \\ &= m_3 \\ &= xy \end{aligned}$$

	x	y	f2
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

$$f2(x,y) = \Sigma m(1,2,3)$$

 

(b) $x + y$

$$\begin{aligned} f2(x,y) &= \Sigma m(1,2,3) \\ &= m_1 + m_2 + m_3 \\ &= x'y + xy' + xy = (x' + x)y + xy' \\ &= y + xy' = (y + x)(y + y') = (y + x) \\ &= x + y \end{aligned}$$

H. Ural


5

GIVEN $f = e$ in CSOP, OBTAIN MINIMAL SOP (CSOP to SOP Procedure)


- 1 - MARK **f** ON THE MAP
(i.e., PUT **1** INTO SQUARES CORRESPONDING TO MINTERMS FOR WHICH **f** TAKES VALUE **1**.)
- 2 - OBTAIN MINIMAL e FOR **f** IN SOP BY COMBINING ADJACENT **1**-SQUARES INTO LARGEST POSSIBLE AREAS OF SIZE 2^k where $k = 0, 1, 2, \dots$ SUCH THAT ALL **1**-SQUARES ARE COVERED WITH MINIMAL NUMBER OF TERMS.

e.g.,

$$f1(x,y) = \Sigma m(3)$$

 

$$f2(x,y) = \Sigma m(1,2,3)$$

 

Intersection of area x and area y (a) xy

(b) $x + y$ area x , area y

Note that if f is given in CPOS, first convert CPOS to CSOP and then apply the above procedure.

$$\text{e.g., } f1(x,y) = \Pi M(0,1,2) = \Sigma m(3)$$

$$f2(x,y) = \Pi M(0) = \Sigma m(1,2,3)$$


H. Ural

6

Three Variable Karnaugh Map

Minterms				
x	y	z	Terms	Designation
0	0	0	$x'y'z'$	m0
0	0	1	$x'y'z$	m1
0	1	0	$x'yz'$	m2
0	1	1	$x'yz$	m3
1	0	0	$xy'z'$	m4
1	0	1	$xy'z$	m5
1	1	0	xyz'	m6
1	1	1	xyz	m7

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

 

- Note that
- row 0 corresponds to x' and row 1 corresponds to x
 - columns 00 and 01 correspond to y' and column 11 and 10 corresponds to y
 - columns 00 and 10 correspond to z' and column 01 and 11 corresponds to z
 - column 00 corresponds to $y'z'$
 - column 01 corresponds to $y'z$
 - column 11 corresponds to yz
 - column 10 corresponds to yz'

In the 3-VARIABLE MAP, each square has 3 adjacent squares.

**e.g., m0, m3 and m5 are adjacent to m1; m3, m5 and m6 are adjacent to m7.
m1, m4 and m2 are adjacent to m0; m2, m7 and m4 are adjacent to m6.**

Any 2^k adjacent squares for $k=0,1,2,3$ in a 3 -VARIABLE MAP is an area that represents a term consisting of $3-k$ literals.

When $k=0$, $2^0=1$. e.g., m3 is an area that represents an term consisting of 3 literals , i.e., $x'yz$.

When $k=1$, $2^1=2$. e.g., m2 and m3 is an area that represents an term consisting of 2 literals , i.e., $x'y$.

When $k=2$, $2^2=4$. e.g., m0, m1, m4 and m5 is an area that represents an term consisting of 1 literal , i.e., y' .

When $k=3$, $2^3=8$. $n=k$. The entire map represents a term with no literals, i.e., 1 (IDENTITY)

FIGURE 3.4 Map for Example 3.1, $f(x, y, z) = \Sigma m(2, 3, 4, 5) = xy' + x'y$


 



FIGURE 3.5 Map for Example 3.2, $f(x, y, z) = \Sigma m(3, 4, 6, 7) = yz + xz'$

 

Note: $xy'z' + xyz' = xz'$

Copyright ©2013 Pearson Education, publishing as Prentice Hall


FIGURE 3.6 Map for Example 3.3, $f(x, y, z) = \Sigma m(0, 2, 4, 5, 6) = z' + xy'$

 

Note: $y'z' + yz' = z'$

Copyright ©2013 Pearson Education, publishing as Prentice Hall

FIGURE 3.7 Map of Example 3.4, $f(x, y, z) = \Sigma m(1, 2, 3, 5, 7) = C + A'B$

 

Copyright ©2013 Pearson Education, publishing as Prentice Hall

H. Ural

11

Four Variable Karnaugh Map

					Minterms	
w	x	y	z	Terms	Designation	
0	0	0	0	$w'x'y'z'$	m0	
0	0	0	1	$w'x'y'z$	m1	
0	0	1	0	$w'x'yz'$	m2	
0	0	1	1	$w'xyz$	m3	
0	1	0	0	$w'xy'z'$	m4	
0	1	0	1	$w'xyz'$	m5	
0	1	1	0	$w'xyz$	m6	
0	1	1	1	$w'xyz'$	m7	
1	0	0	0	$wx'y'z'$	m8	
1	0	0	1	$wx'y'z$	m9	
1	0	1	0	$wx'yz'$	m10	
1	0	1	1	$wx'yz$	m11	
1	1	0	0	$wxy'z'$	m12	
1	1	0	1	$wxy'z$	m13	
1	1	1	0	$wxyz'$	m14	
1	1	1	1	$wxyz$	m15	

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

wx		y			
		00	01	11	10
yz	00	m_0 $w'x'y'z'$	m_1 $w'x'y'z$	m_3 $w'x'yz$	m_2 $w'xyz'$
	01	m_4 $w'xy'z'$	m_5 $w'xyz'$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
	10	m_8 $wx'y'z'$	m_9 $wx'y'z$	m_{11} $wx'yz$	m_{10} $wx'yz'$

(b)

Note that

Copyright ©2013 Pearson Education, publishing as Prentice Hall

-rows 00 and 01 correspond to w' and rows 11 and 10 correspond to w
 -rows 00 and 10 correspond to x' and rows 01 and 11 correspond to x

-row 00 corresponds to $w'x'$

-row 01 corresponds to $w'x$

-row 11 corresponds to wx

-row 10 corresponds to wx'

-columns 00 and 01 correspond to y' and column 11 and 10 corresponds to y
 -columns 00 and 10 correspond to z' and column 01 and 11 corresponds to z

- column 00 corresponds to $y'z'$

- column 01 corresponds to $y'z$

- column 11 corresponds to yz

- column 10 corresponds to yz'

H. Ural

12

Four Variable Karnaugh Map

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

		y			
	yz	00	01	11	10
w	00	m_0 $w'x'y'z'$	m_1 $w'x'y'z$	m_3 $w'x'yz$	m_2 $w'x'yz'$
		m_4 $w'xy'z'$	m_5 $w'xy'z$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
		m_8 $wx'y'z'$	m_9 $wx'y'z$	m_{11} $wx'yz$	m_{10} $wx'yz'$
		z			

(b)

In the 4-VARIABLE MAP, each square has 4 adjacent squares.

e.g., m_0, m_3, m_5 and m_9 are adjacent to m_1 ; m_6, m_{10}, m_{15} and m_{12} are adjacent to m_{14} .
 m_1, m_4, m_2 and m_8 are adjacent to m_0 ; m_{11}, m_{14}, m_2 and m_8 are adjacent to m_{10} .

Any 2^k adjacent squares for $k=0,1,2,3,4$ in a 4 -VARIABLE MAP

is an area that represents a term consisting of $4-k$ literals.

When $k=0, 2^0=1$. e.g., m_3 is an area that represents an term consisting of 4 literals , i.e., $w'x'yz$.


When $k=1, 2^1=2$. e.g., m_2 and m_3 is an area that represents an term consisting of 3 literals , i.e., $w'x'y$.

When $k=2, 2^2=4$. e.g., m_0, m_1, m_4 and m_5 is an area that represents an term consisting of 2 literals, i.e., $w'y'$.

When $k=3, 2^3=8$. e.g., $m_0, m_1, m_2, m_3, m_4, m_5, m_6,$ and m_7 is an area representing a term with 1 literal, i.e., w' .

When $k=4, 2^4=16. n=k$. The entire map represents a term with no literals, i.e., 1 (IDENTITY)

FIGURE 3.9 Map for Example 3.5, $f(w, x, y, z) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
 $= y' + w'z' + xz'$

 

Note: $w'y'z' + w'yz' = w'z'$
 $xy'z' + xyz' = xz'$

Q: Is the simplified expression in SOP

we obtain from a map by following the above procedure unique?

A: Not necessarily!

There may be many expressions in SOP that are equally simplified.

Q: How can we be sure that we found one of the most simplified expressions?

A: Do the following:

1) Identify all prime implicants

(a **prime implicant** is a product term obtained by combining the maximum possible number of adjacent 1-squares)

2) Identify which prime implicants are essential prime implicants

(a prime implicant is **essential** if it is the only prime implicant that covers some 1-square)

3) A most simplified SOP is obtained by taking the logical OR of

all the essential prime implicants

and


prime implicants that may be needed to

cover any remaining 1-squares not covered by essential prime implicants.

 H. Ural

15

e.g., $f(A,B,C,D) = \Sigma m(0,2,5,7,8,10,13,15)$



Note: $A'B'C'D' + A'B'CD' = A'B'D'$

$AB'C'D' + AB'CD' = AB'D'$

$A'B'D' + AB'D' = B'D'$

(a) Essential prime implicants

BD and $B'D'$


Copyright ©2013 Pearson Education, Inc.

$$f(A,B,C,D) = BD + B'D'$$

 H. Ural

16

e.g., $f(A,B,C,D) = \Sigma m(0,2,3,5,7,8,9,10,11,13,15)$



Prime implicants : $BD, B'D', CD, B'C, AD, AB'$

Essential prime implicants : $BD, B'D'$

(b) Prime implicants $CD, B'C, AD,$ and AB'

(because **only** BD covers m_5 and **only** $B'D'$ covers m_0)

publishing as Prentice Hall

(1-squares not covered by BD and $B'D'$ are m_3, m_9, m_{11} .)

We must cover m_3, m_9, m_{11} by minimal number of other prime implicants.

There are four pairs of prime implicants to cover them:

These pairs are, $CD + AD, CD + AB', B'C + AD, B'C + AB'$

Thus, there are four equally (most) simplified SOP for $f(A,B,C,D)$:

$$\begin{aligned} f(A,B,C,D) &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$

H. Ural

17

GIVEN $f = e$ IN CSOP, OBTAIN MINIMAL POS (CSOP to POS Procedure)

1- MARK f ON THE MAP

(i.e., PUT **1** INTO SQUARES CORRESPONDING TO MINTERMS FOR WHICH f TAKES VALUE **1**.)

2- f' IS DEFINED BY THOSE SQUARES NOT MARKED AS **1**

(f' IS DEFINED BY THOSE SQUARES MARKED AS **0**)

3- OBTAIN A SIMPLIFIED EXPRESSION FOR f' IN SOP BY COMBINING ADJACENT **0**-SQUARES INTO LARGEST POSSIBLE AREAS OF SIZE 2^k where $k = 1, 2, \dots$ SUCH THAT

ALL **0**-SQUARES ARE COVERED WITH MINIMAL NUMBER OF TERMS

4- TAKE COMPLEMENT OF f' IN SOP WHICH GIVES f IN POS


e.g., $f(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$

$$\begin{aligned} f'(A,B,C,D) &= AB + CD + BD' \\ f(A,B,C,D) &= (f')' \\ &= (AB + CD + BD')' \\ &= (AB)' (CD)' (BD')' \\ &= (A' + B')(C' + D')(B' + D) \end{aligned}$$

NOTE: f in SOP is $B'D' + B'C' + A'C'D$

H. Ural

FIGURE 3.12 Map for Example 3.7

 

Note: $BC'D' + BCD' = BD'$

Copyright © 2013 Pearson Education, publishing as Prentice Hall

18


Let's summarize with an example:

Simplify $f(A,B,C,D) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$ into

(a) sum-of-products form


(b) product-of-sums form

(a) sum-of-products form

 

$$f(A,B,C,D) = B'D' + B'C' + A'C'D$$

(b) product-of-sums form

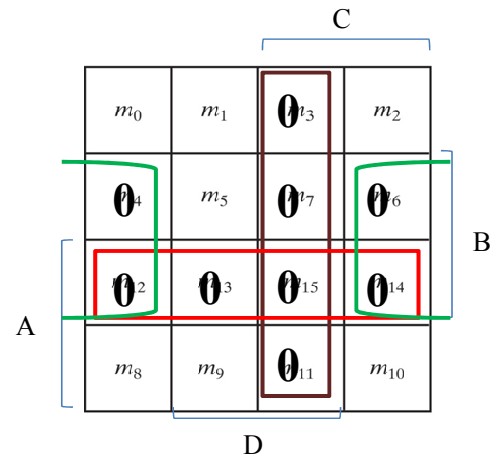

$$f'(A,B,C,D) = CD + BD' + AB$$


$$f(A,B,C,D) = (f')'$$

$$= (C' + D')(B' + D)(A' + B')$$

Q: How can we verify that what we were given is one of the most simplified expressions of a Boolean function f ?


A: Use Karnaugh map method. It will help you to determine whether f is in its most simplified form and if it is not then you can simplify it using the procedures we have seen.

 e.g., $f(A,B,C,D) = A'B'C' + B'CD' + A'BCD' + AB'C'$ in SOP



$$f(A,B,C,D) = B'D' + B'C' + A'CD'$$

in SOP by combining 1-squares

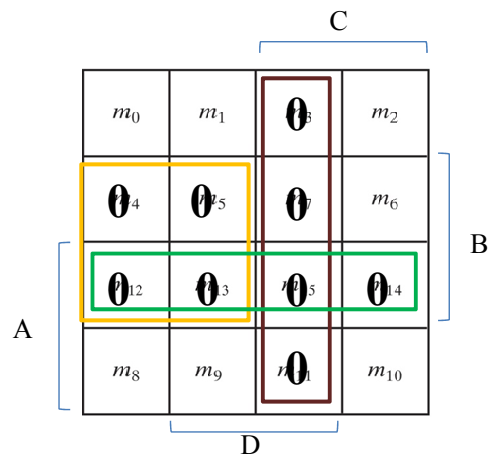

$$f'(A,B,C,D) = CD + BC' + AB$$

in SOP by combining 0-squares


$$f(A,B,C,D) = (CD + BC' + AB)'$$

$$= (C' + D')(B' + C)(A' + B')$$

in POS by taking complement of f'

e.g., $f(A,B,C,D) = (A+B+D')(B'+C'+D)(A'+B+D')(B'+C+D)$ in POS

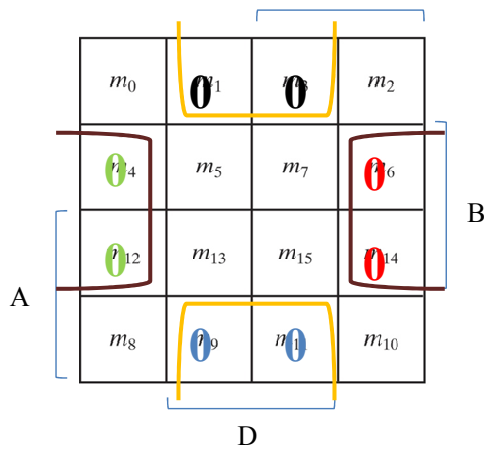$f'(A,B,C,D) = A'B'D + BCD' + AB'D + BC'D'$ in SOP by taking complement of f




$f'(A,B,C,D) = BD' + B'D$
in SOP by combining 0-squares

$$f(A,B,C,D) = (BD' + B'D)'$$

$$= (B' + D)(B + D')$$

in POS by taking complement of f'

 

$f(A,B,C,D) = BD + B'D'$
in SOP by combining 1-squares

SUMMARY

Given $f = e$ in CSOP, obtain minimal SOP
Apply CSOP to SOP Procedure

Given $f = e$ in CPOS, obtain minimal SOP
Obtain CSOP from the given CPOS
Apply CSOP to SOP Procedure

Given $f = e$ in CSOP, obtain minimal POS
Apply CSOP to POS Procedure

Given $f = e$ in CPOS, obtain minimal POS
Obtain CSOP from the given CPOS
Apply CSOP to POS Procedure


SIMPLIFICATION WITH DON'T CARE CONDITIONS

When the value of a function corresponding to a combination of values input variables is not specified, the corresponding minterm or maxterm is represented by DON'T CARE. For example, for a digital circuit whose input is a decimal digit coded in BCD code, we have four input variables: $w, x, y,$ and $z,$ taking 10 combinations of values from 0000 to 1001. The remaining 5 combination of values, 1010, 1011, 1100, 1101, 1111 are not expected to occur at the input lines of the circuit and thus when we define the functionality of the circuit by a Boolean function, the function can take a DON'T CARE value for each of these five combination of values.

A DON'T CARE

- is represented by X
- can take a value 0 or 1 depending on whether we can form a larger area of squares when we combine squares during the application of the Karnaugh Map method.

 e.g., $f(w,x,y,z) = \Sigma m(1,3,7, 11,15) + \Sigma d(0,2,5)$



Copyright © 2013 Pearson Education, publishing as Prentice Hall


FIGURE 3.15 Example with don't-care conditions

Two-Level Implementations of Boolean Expressions using non-degenerate forms

There are eight nondegenerate forms:


AND-OR	OR-AND
NAND-NAND	NOR-NOR
NOR-OR	NAND-AND
OR-NAND	AND-NOR

 Given f in minimal SOP,
implement it in AND-OR form



 (a) $F = B'D' + B'C' + A'C'D$

Given f in minimal POS,
implement it in OR-AND form




(b) $F = (A' + B')(C' + D')(B' + D)$


Remaining six nondegenerate forms for two-level implementations of Boolean expressions involve NAND or NOR gates.

Let's recall the NAND and NOR gates:

A) NAND gates = AND-INVERT / INVERT-OR

 



(a) AND-invert

 

  (b) Invert-OR

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Any Boolean expression can be implemented using only NAND gates:




These are also
NAND gates


Implementing Minimal SOP in NAND-NAND form

e.g., $F = AB + CD$

AND-OR Form

 


NAND-NAND Form

 

(a)

NAND-NAND Form

 


Copyright ©2013 Pearson Education, publishing as Prentice Hall


H. Ural

27

e.g., $F = xy' + x'y + z$

 


NAND-NAND Form

 

(a)

NAND-NAND Form

 

Copyright ©2013 Pearson Education, publishing as Prentice Hall


Note that z is primed

H. Ural

28


Let's recall the NAND and NOR gates:

B) NOR gates = OR-INVERT / INVERT-AND

 

Copyright ©2013 Pearson Education, publishing as Prentice Hall

 
Any Boolean expression can be implemented using only NOR gates:



Copyright ©2013 Pearson Education, publishing as Prentice Hall H. Ural

Implementing Minimal POS in NOR-NOR form

e.g.,: $F = (A + B)(C + D)E$

 

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Note that E is primed


AND-OR-INVERT (AOI) Implementations

NAND-AND = AND-NOR = AOI

e.g., $F = (AB + CD + E)'$

What is implemented is $(F)'$

Where $F' = AB + CD + E$ (in SOP form)

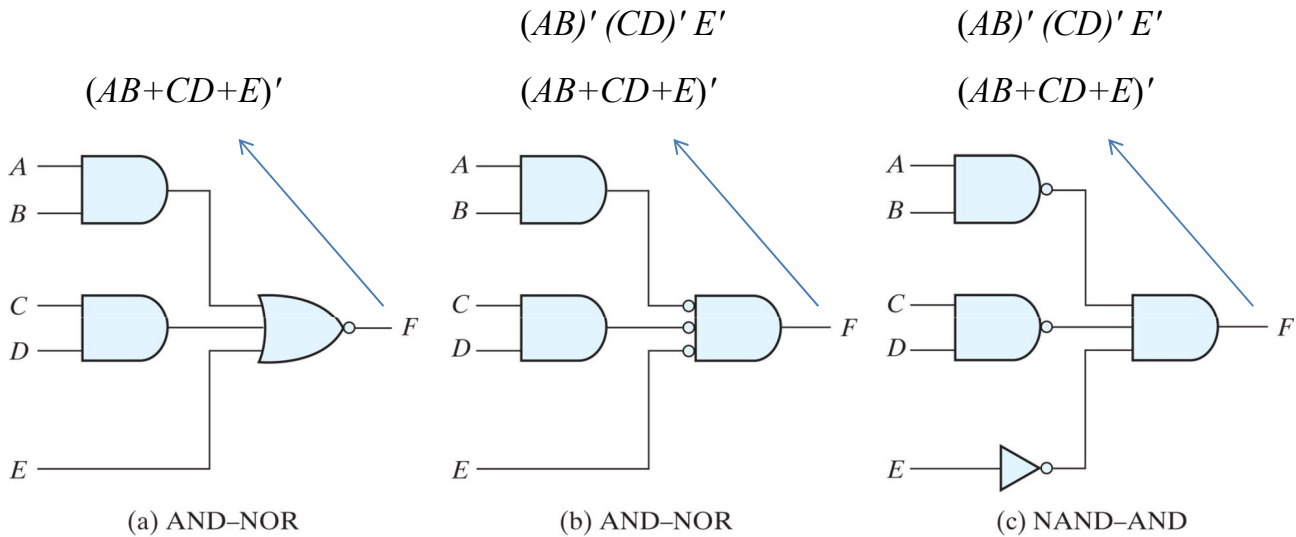

Copyright ©2013 Pearson Education, publishing as Prentice Hall

H. Ural

31


OR-AND-INVERT (OAI) Implementation

OR-NAND = NOR-OR = OAI

e.g., $F = ((A+B)(C+D)E)'$

What is implemented is $(F)'$

Where $F' = (A+B)(C+D)E$ (in POS form)

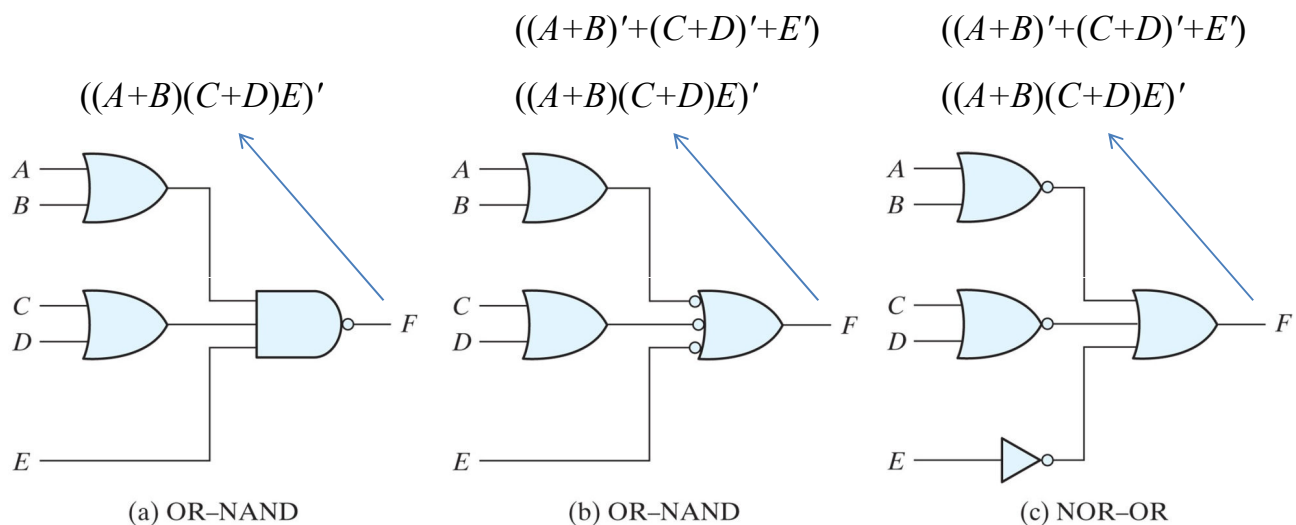

Copyright ©2013 Pearson Education, publishing as Prentice Hall

H. Ural

32

Table 3.2
Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify F' into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F


*Form (b) requires an inverter for a single literal term.

Copyright ©2012 Pearson Education, publishing as Prentice Hall

 
H. Ural

33


e.g., Two level implementations with AND-NOR, NAND-AND, OR-NAND, NOR-OR



 (a) Map simplification in sum of products



(b) $F = (x'y + xy' + z)'$

 


(c) $F = [(x + y + z)(x' + y' + z)]'$

Copyright ©2013 Pearson Education, publishing as Prentice Hall


H. Ural

34

Exclusive-OR implementations

 

(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Three-variable exclusive-OR functions

A	BC			
	00	01	11	10
0	m_0	1	m_3	m_2
1	m_4	m_5	1	m_6

Labels: m_0, m_1, m_3, m_2 for row 0; m_4, m_5, m_7, m_6 for row 1. Brackets indicate groupings for variables B and C.


(a) Odd function $F = A \oplus B \oplus C$

Copyright ©2013 Pearson Education, publishing as Prentice Hall


A	BC			
	00	01	11	10
0	1	m_1	1	m_2
1	m_4	1	m_7	m_6

Labels: m_0, m_1, m_3, m_2 for row 0; m_4, m_5, m_7, m_6 for row 1. Brackets indicate groupings for variables B and C.

 (b) Even function $F = (A \oplus B \oplus C)'$




(a) 3-input odd function

 


(b) 3-input even function

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Four-variable exclusive-OR functions

 

 (a) Odd function $F = A \oplus B \oplus C \oplus D$




(b) Even function $F = (A \oplus B \oplus C \oplus D)'$

Copyright ©2013 Pearson Education, publishing as Prentice Hall

e.g., Use of even parity in error detecting codes

Table 3.3
Even-Parity-Generator Truth Table


Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

3-bit even parity generator

Table 3.4
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

4-bit even parity checker

publishing as Prentice Hall

Copyright ©2012 Pearson Education, publishing as Prentice Hall

Summary

Implementation of $f(x,y,z) = x'y'z' + xyz'$ in SOP in
 AND-OR-INVERT form
 NAND-NAND form
 NOR-NOR form

Implementation of $f(x,y,z) = (x+y')(x'+y)z'$ in POS in
 AND-OR-INVERT form
 NAND-NAND form
 NOR-NOR form