

DIGITAL SYSTEM I

Lectures:

Professor : Dr A. Karmouch, office **CBY A508**

Chapter 6

Registers & Counters

Registers

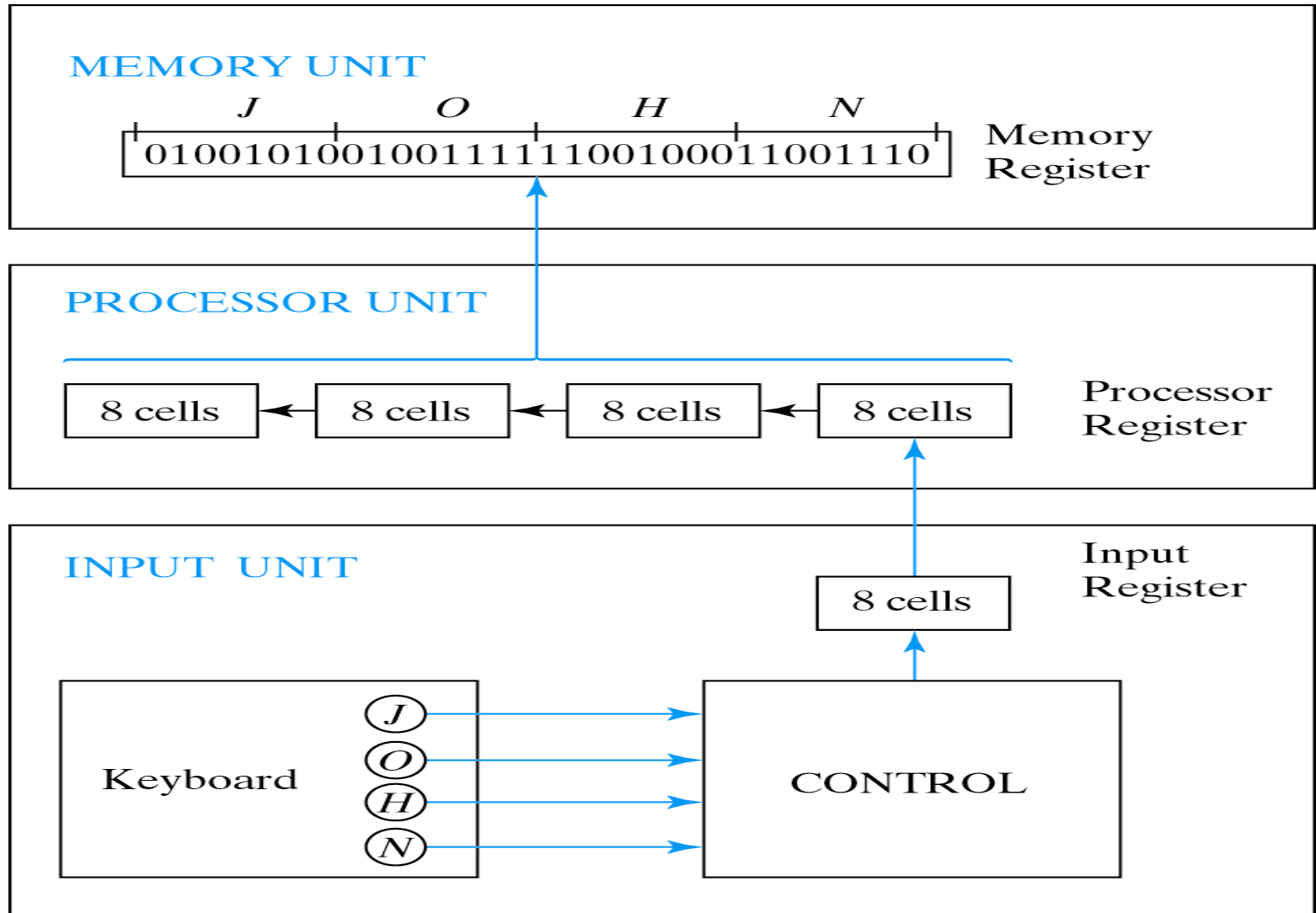



Fig. 1-1 Transfer of information with registers

Registers

- Multiple flip flops can be combined to form a **data register**
- **Shift registers** allow data to be transported one bit at a time
- **Registers** also allow for parallel transfer
 - Many bits transferred at the same time
- **Basic components of most computers**


Parallel versus Serial

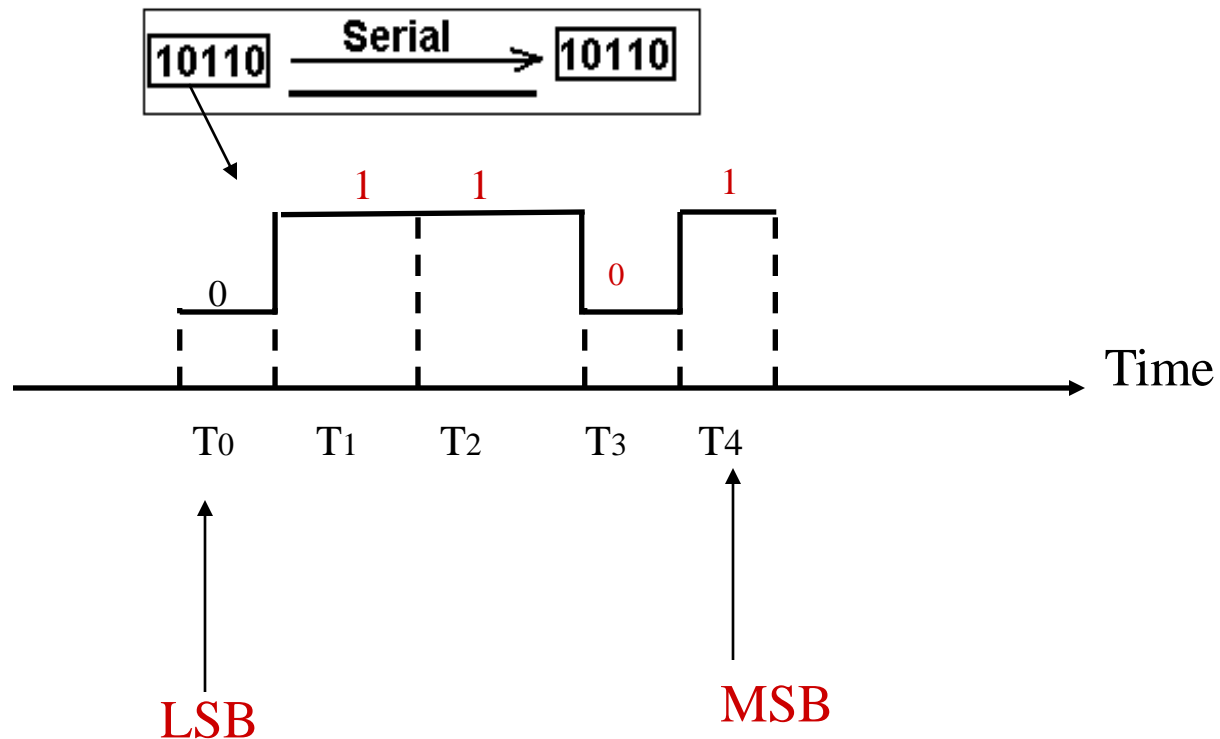- Serial communications, transfers a binary number as a sequence of binary digits, one after another, through one data line.
- One Circuit is necessary to represent any binary number




Parallel versus Serial

→ Parallel communications

 


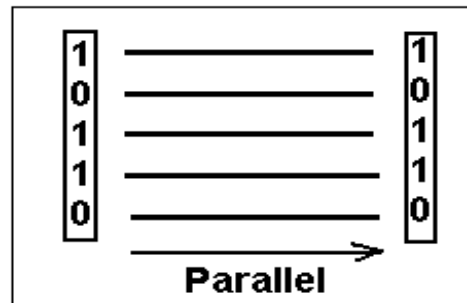–Transfers a binary number through multiple data lines at the same time.



Parallel Data Transfer

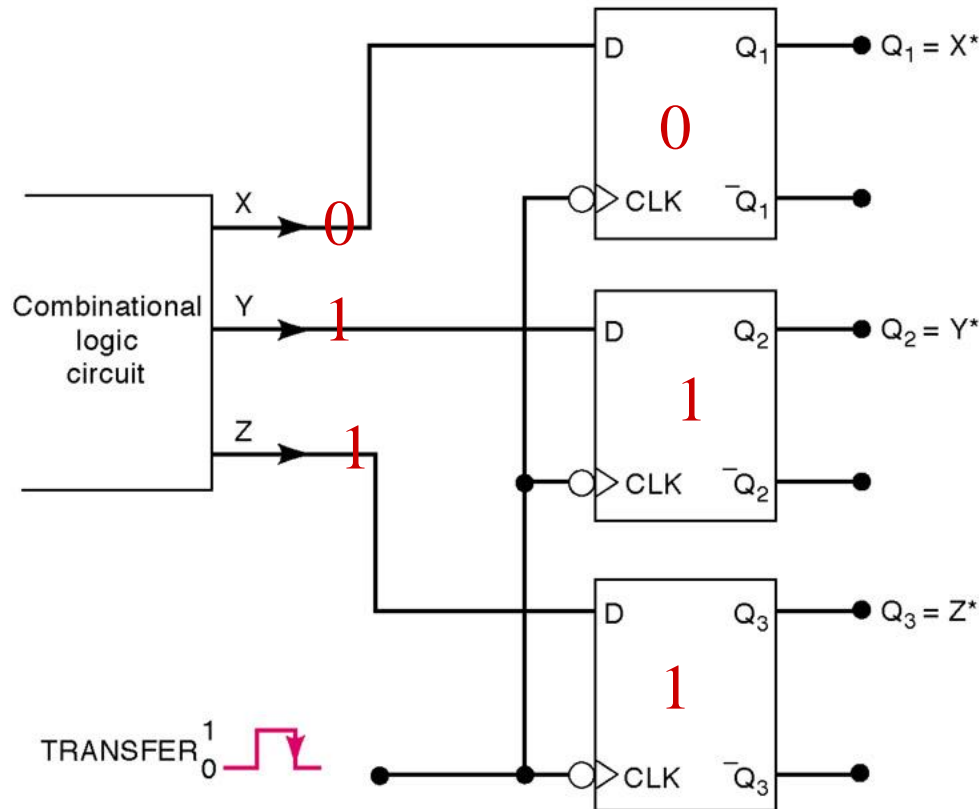
- In this example Flip flops D store outputs from combinational logic that has 3 outputs. **3 flip flops are required**
- Multiple flops can store a collection of binary data



*After occurrence of NGT


Register with Parallel Load

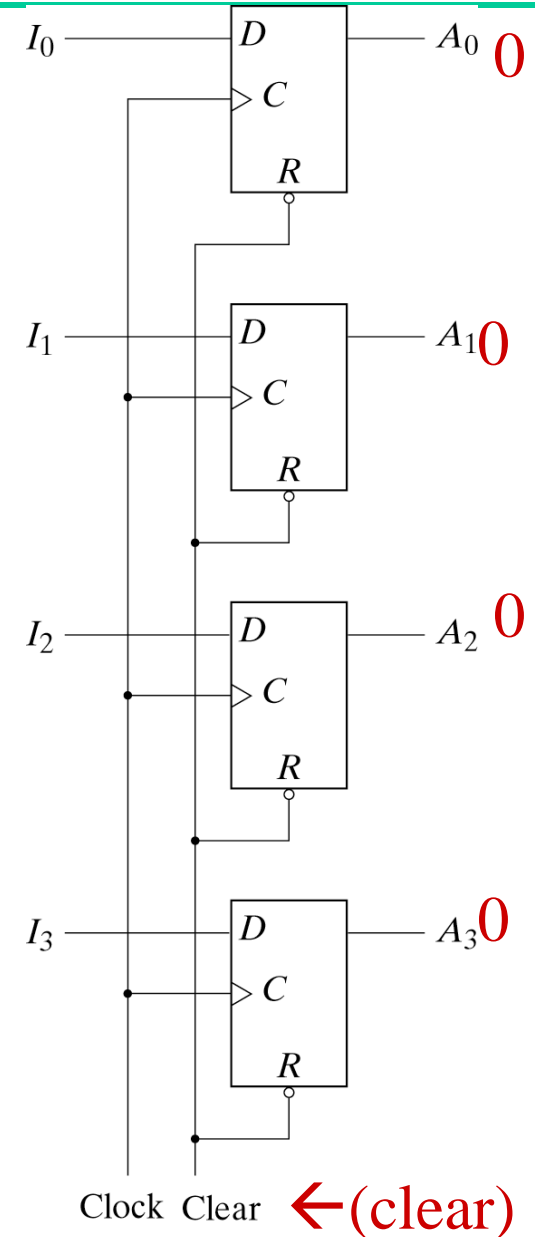- Register: **Group of Flip-Flops**
- Ex: D Flip-Flops
- **Holds 4 bits of Data**
- Loads in Parallel on Clock Transition
- **Asynchronous Clear (Reset)**




Register with Parallel Load

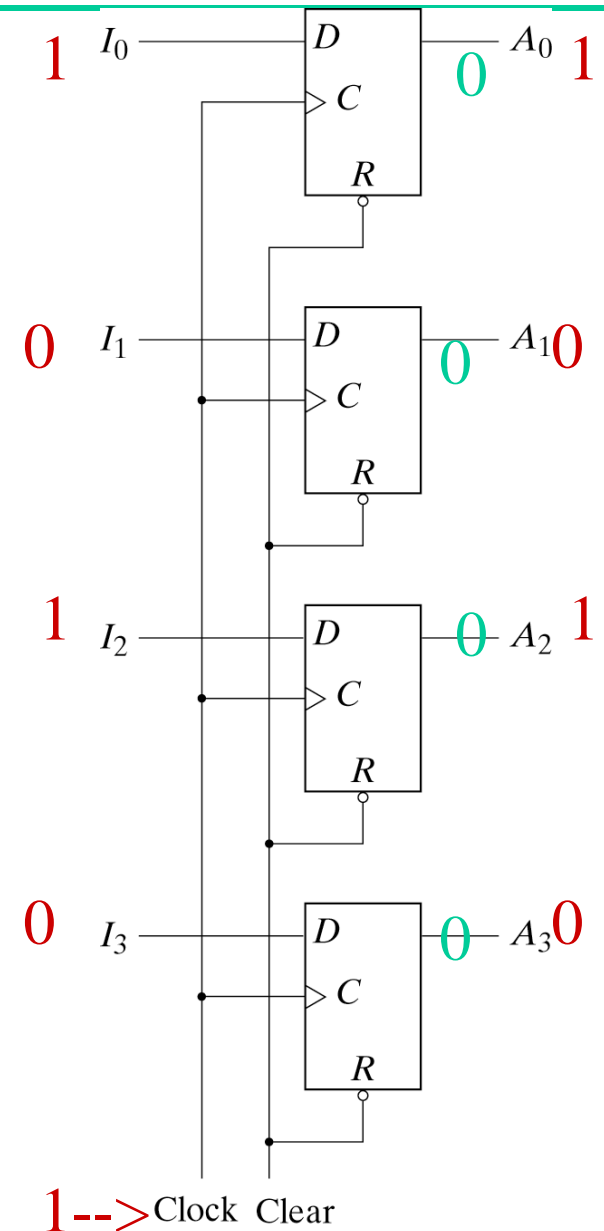- Register: **Group of Flip-Flops**
- Ex: D Flip-Flops
- **Holds 4 bits of Data**
- Loads in Parallel on Clock Transition
- **Asynchronous Clear (Reset)**




Parallel Data Transfer

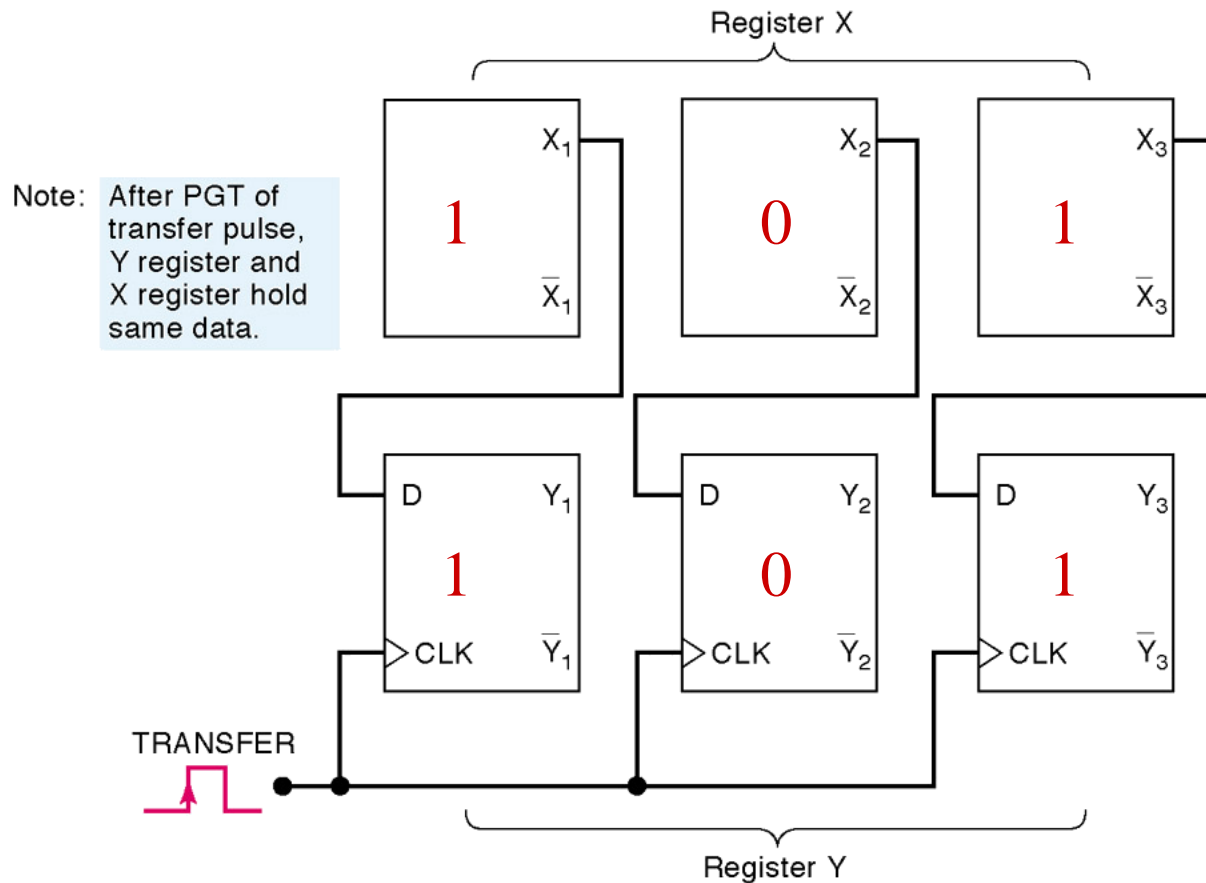- All data is transferred on one positive edge
- Data stored into register Y



Serial Transfer

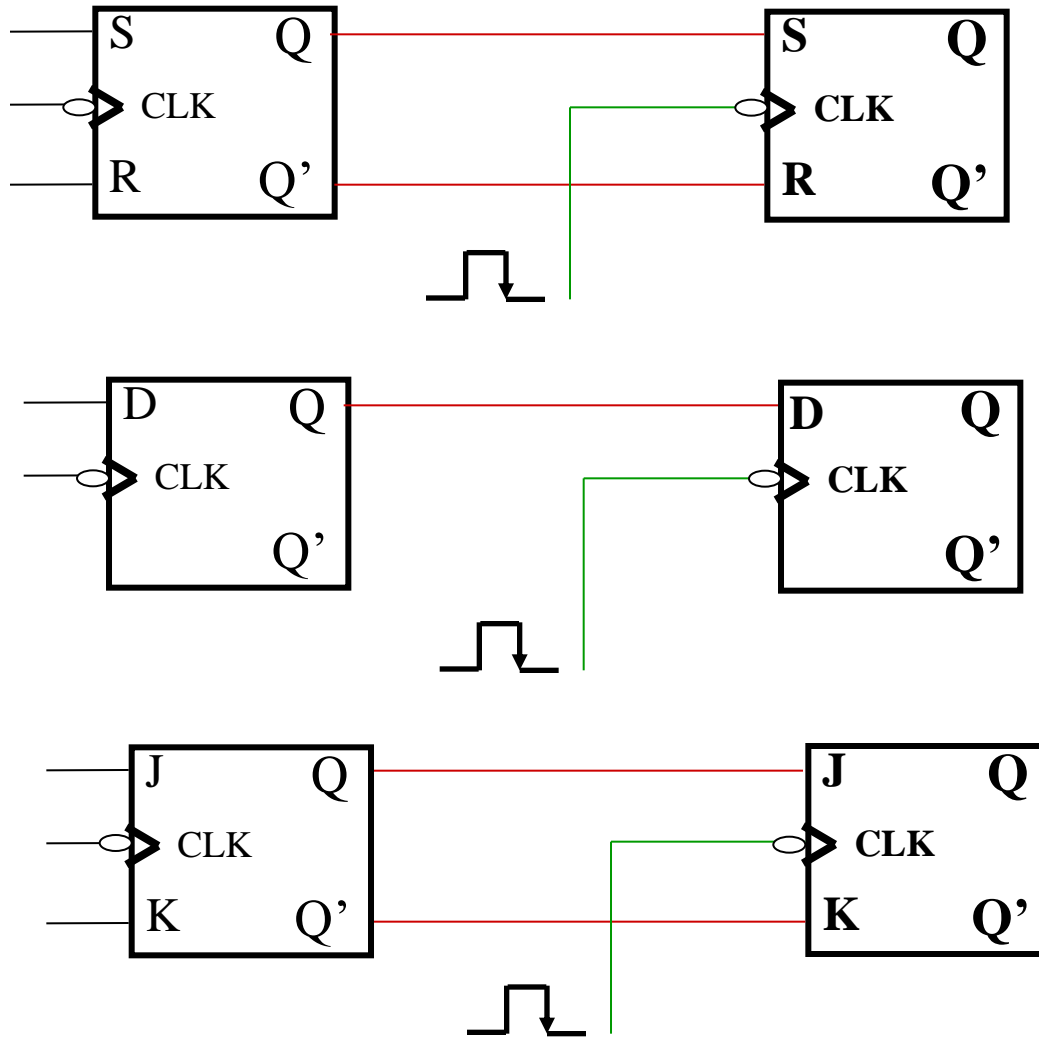

Shift Registers

- Cascade chain of Flip-Flops
- Bits travel on positive edges (in this example)
- Serial in (SI) – Serial out (SO)


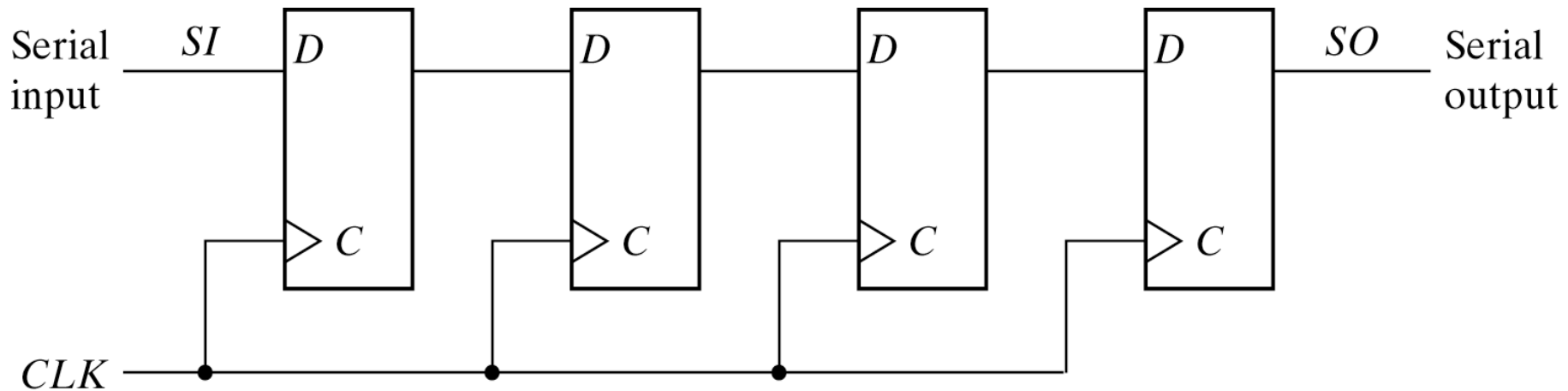


Fig. 6-3 4-Bit Shift Register


Serial Transfer

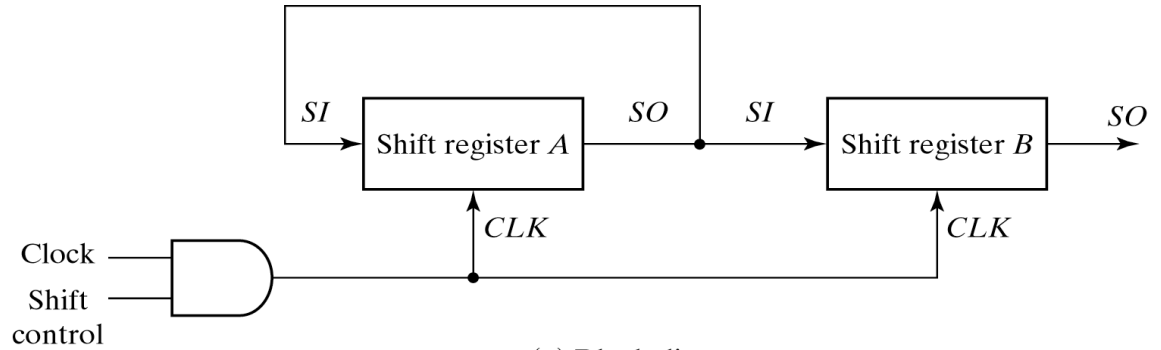- Data is transferred one bit at a time
- Note the data loop back for register A



(a) Block diagram

Time	A	B
T0	1011	0011
T1		
T2		
T3		
T4		

 


(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B


Serial Transfer

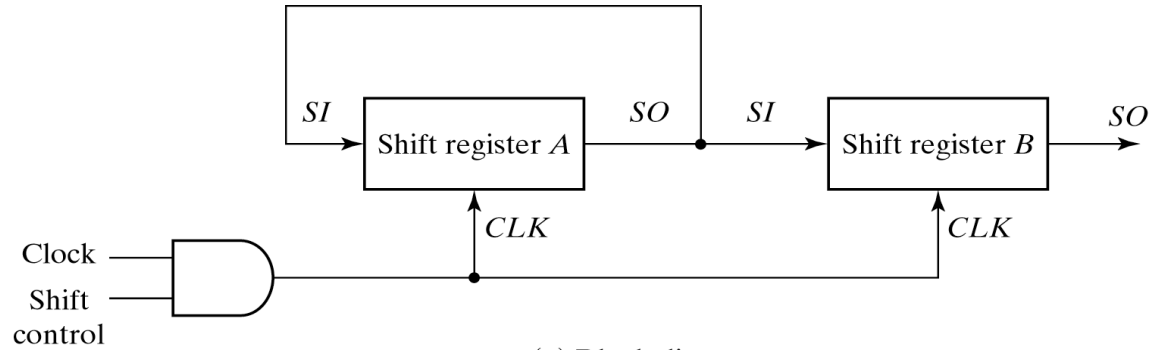- Data is transferred one bit at a time
- Note the data loop back for register A



(a) Block diagram

Time	A	B
T0	1011	0011
T1	1101	1001
T2	1110	1100
T3	0111	0110
T4	1011	1011

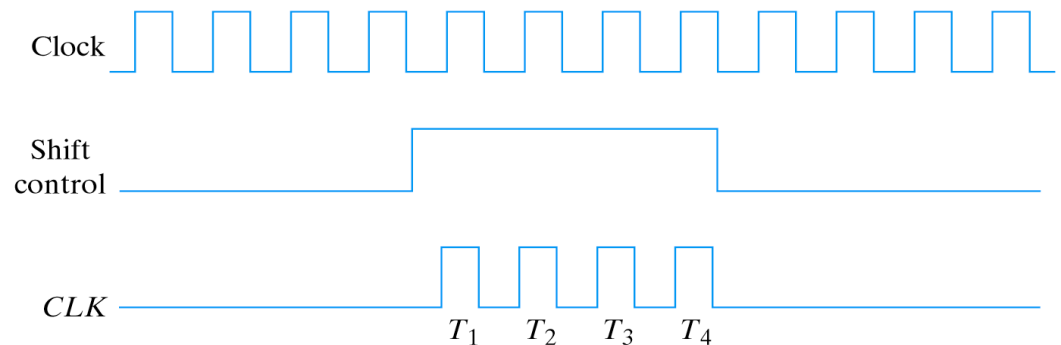


(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B


Serial transfer of Data

Transfer from register X to register Y

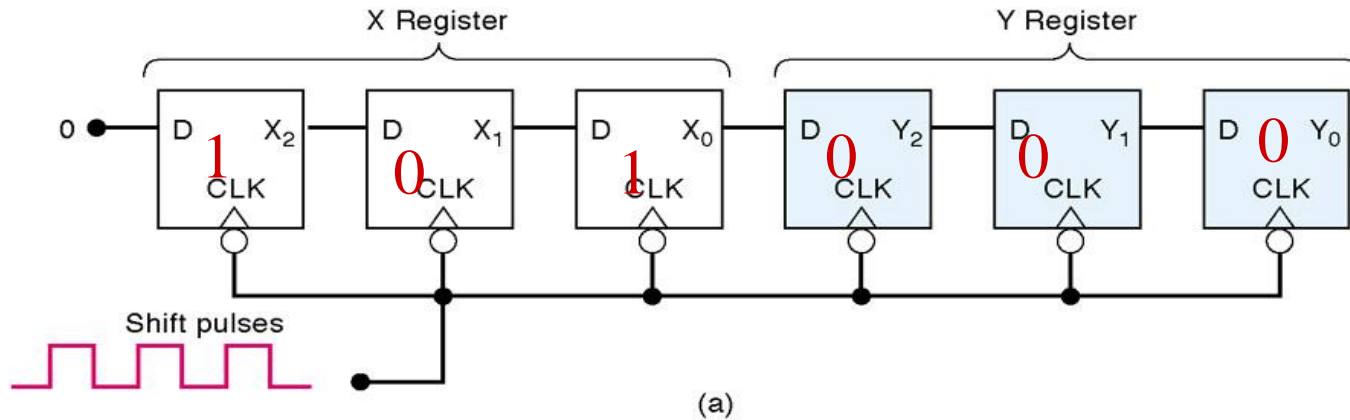

Serial transfer of Data

Transfer from register X to register Y

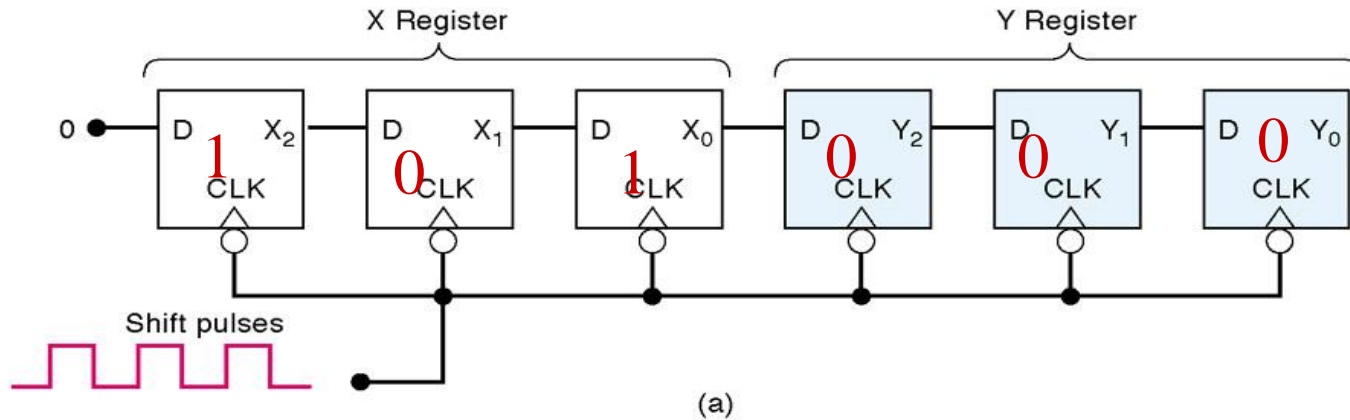


X ₂	X ₁	X ₀	Y ₂	Y ₁	Y ₀	
1	0	1	0	0	0	← Before pulses applied
0	1	0	1	0	0	← After first pulse
0	0	1	0	1	0	← After second pulse
0	0	0	1	0	1	← After third pulse

(b)

Full Adder (see other implementations in Chap. 2)

Truth Table				
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

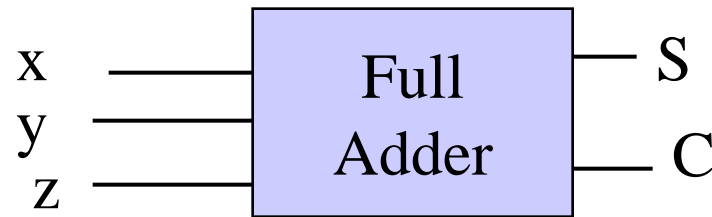→ The Full-adder is combinational circuit



Full Adder (see other implementations in Chap. 2)

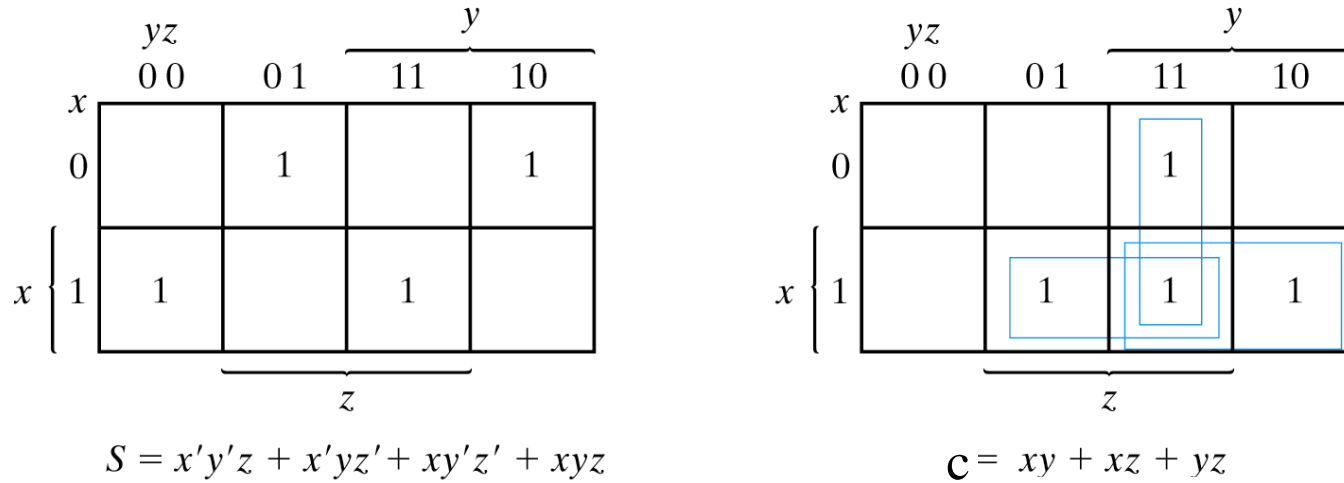


Fig. 4-6 Maps for Full Adder

Full Adder (see other implementations in Chap. 2)

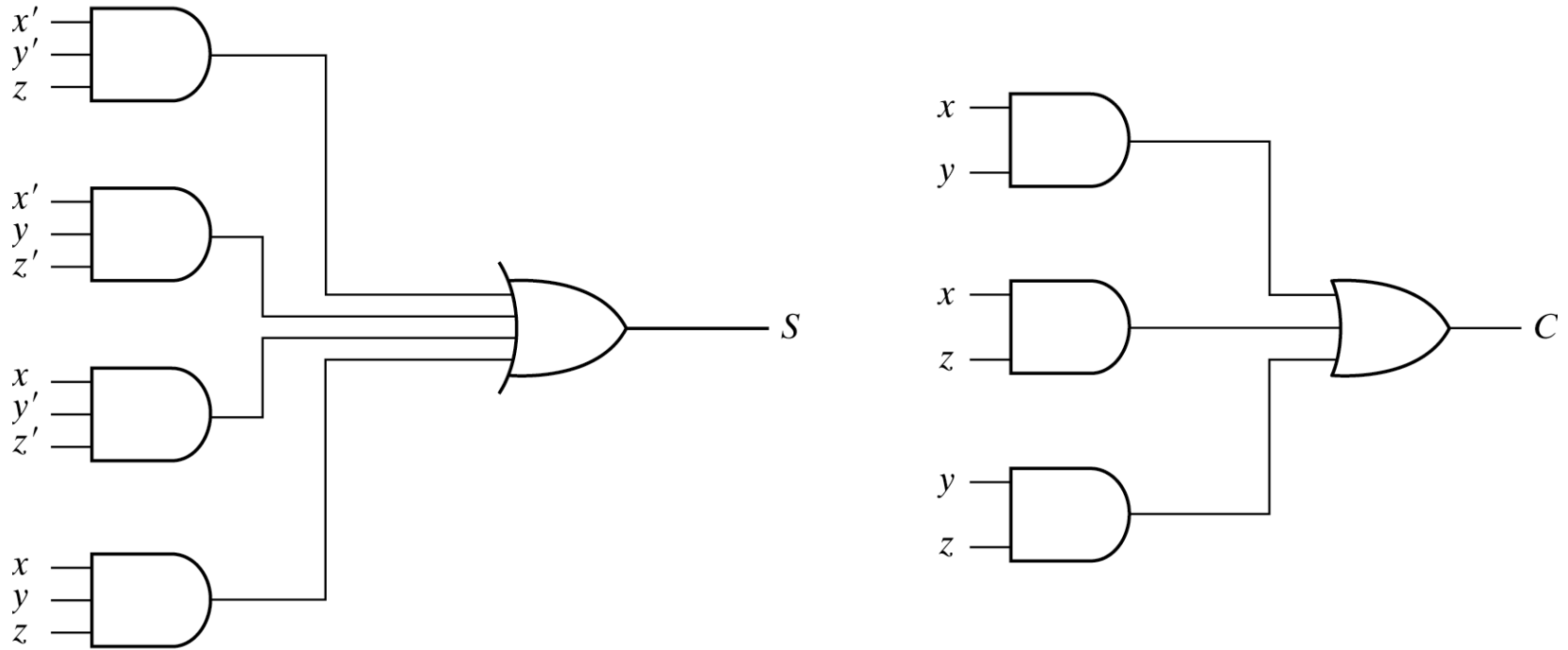


Fig. 4-7 Implementation of Full Adder in Sum of Products

Full Adder (same as in Chap. 2)


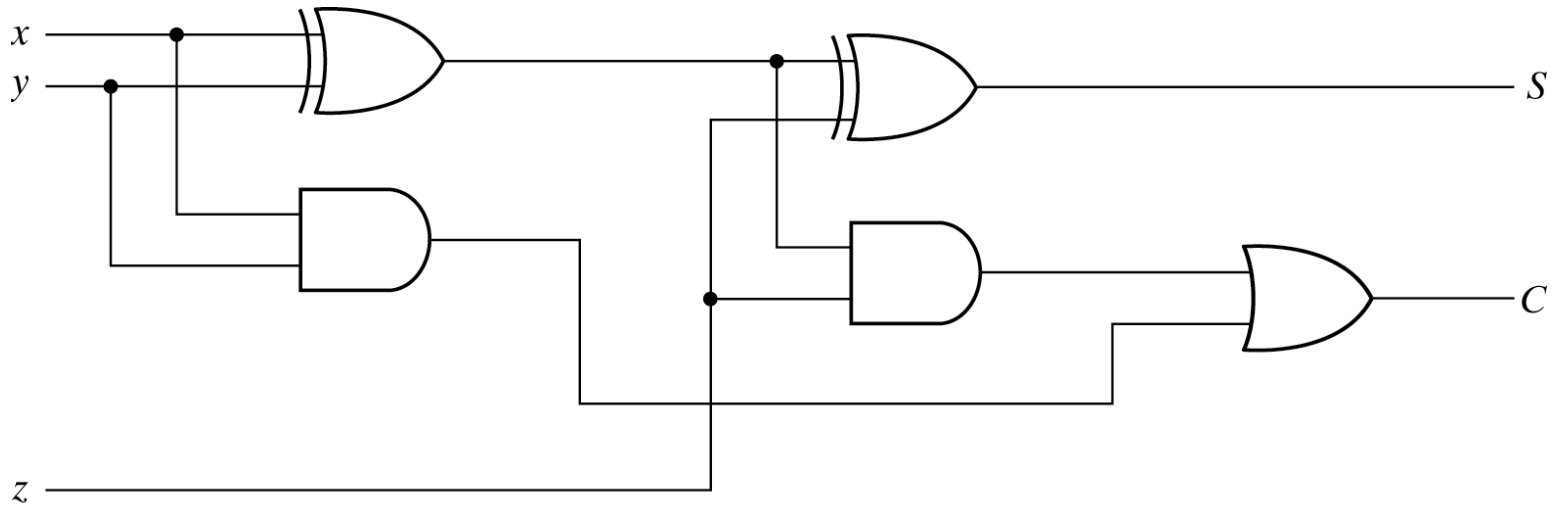


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Full Adder (see other implementations in Chap. 2)

Truth Table				
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

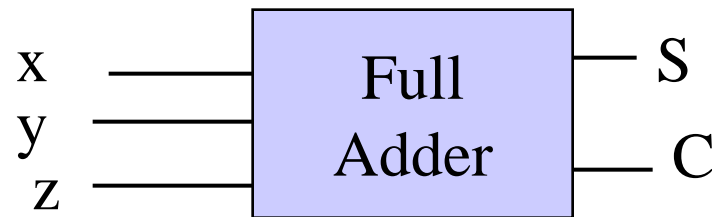→ The Full-adder is combinational circuit



Serial Addition (D Flip-Flop)

- Slower than parallel
- Low cost
- Share fast hardware on slow data

 


Fig. 6-5 Serial Adder

Transition Tables

J-K Flip-Flop Transition Table

J	K	Q_{n+1}	Function
0	0	Q_n	No change
0	1	0	RESET
1	0	1	SET
1	1	Q'_n	complement (also Toggle)

- we indicate the present and next Q-output. If the flip-flop toggles or holds, we indicate that binary value.
- Also note that we need to determine both the J and K inputs.
- The “X” indicates “Don’t Care” states (can be ‘1’ or ‘0’ input).

J-K FLIP-FLOP		
Present	Next	Input J K
0	→ 0	0 X
0	→ 1	1 X
1	→ 0	X 1
1	→ 1	X 0

Designing a JK Serial Adder

- $J_Q = x \cdot y$
- $K_Q = x' \cdot y' = (x+y)'$
- $S = x \oplus y \oplus Q$

Present State	Inputs		Next State	Output	Flip_Flop Inputs	
Q	x	y	Q	S	J_Q	K_Q
0	0	0	0	0	0	x
0	0	1	0	1	0	x
0	1	0	0	1	0	x
0	1	1	1	0	1	x
1	0	0	0	1	x	1
1	0	1	1	0	x	0
1	1	0	1	0	x	0
1	1	1	1	1	x	0

New Serial Adder

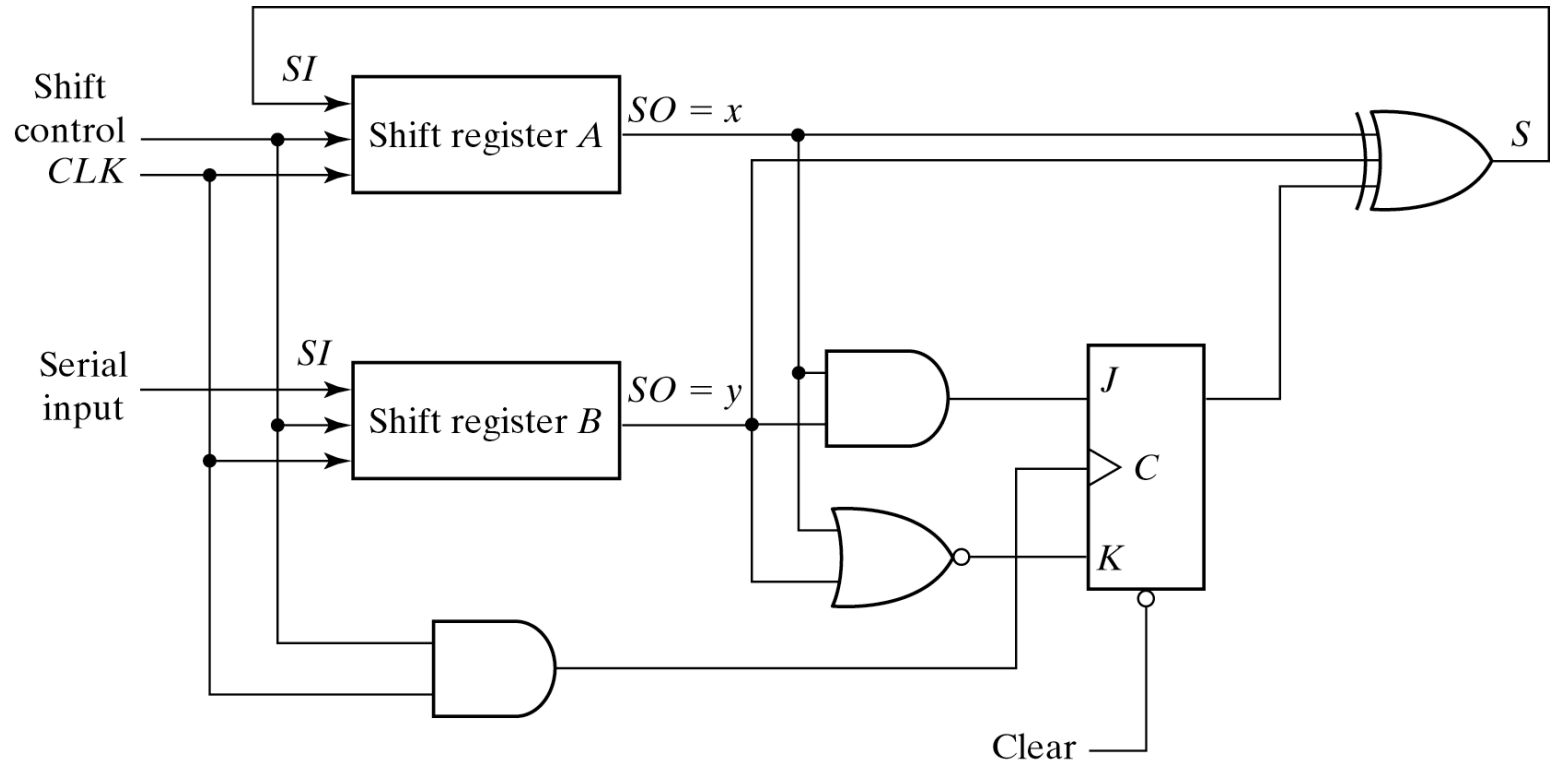


Fig. 6-6 Second form of Serial Adder

Counters

- **Counter**: A register that goes through a prescribed series of states
- **Two main types of counters**
 - 1- **asynchronous counters**: also known as Ripple counter
 - 2- **Synchronous counters**
 - *Ripple counters*
 - Flip flop output serves as a clock for triggering connected flip flops
 - *Synchronous counters*
 - All flip flops are triggered by a **clock signal at the same time**
- **Synchronous counters are more widely used**

Asynchronous Counters

- Each Flip flop output controls the CLK input of the next Flip flop.
- Flip flop do not change states in exact synchronism with the applied clock pulses.
- *Ripple counter* due to the way the flip flops respond one after another in a kind of rippling effect.

A ₃	A ₂	A ₁	A ₀
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

Binary Ripple Counter

- Reset signal sets all outputs to 0
- Count signal toggles output of low-order flip flop
- Low-order flip flop provides trigger for adjacent flip flop
- Not all flops change value simultaneously
 - Lower-order flops change first



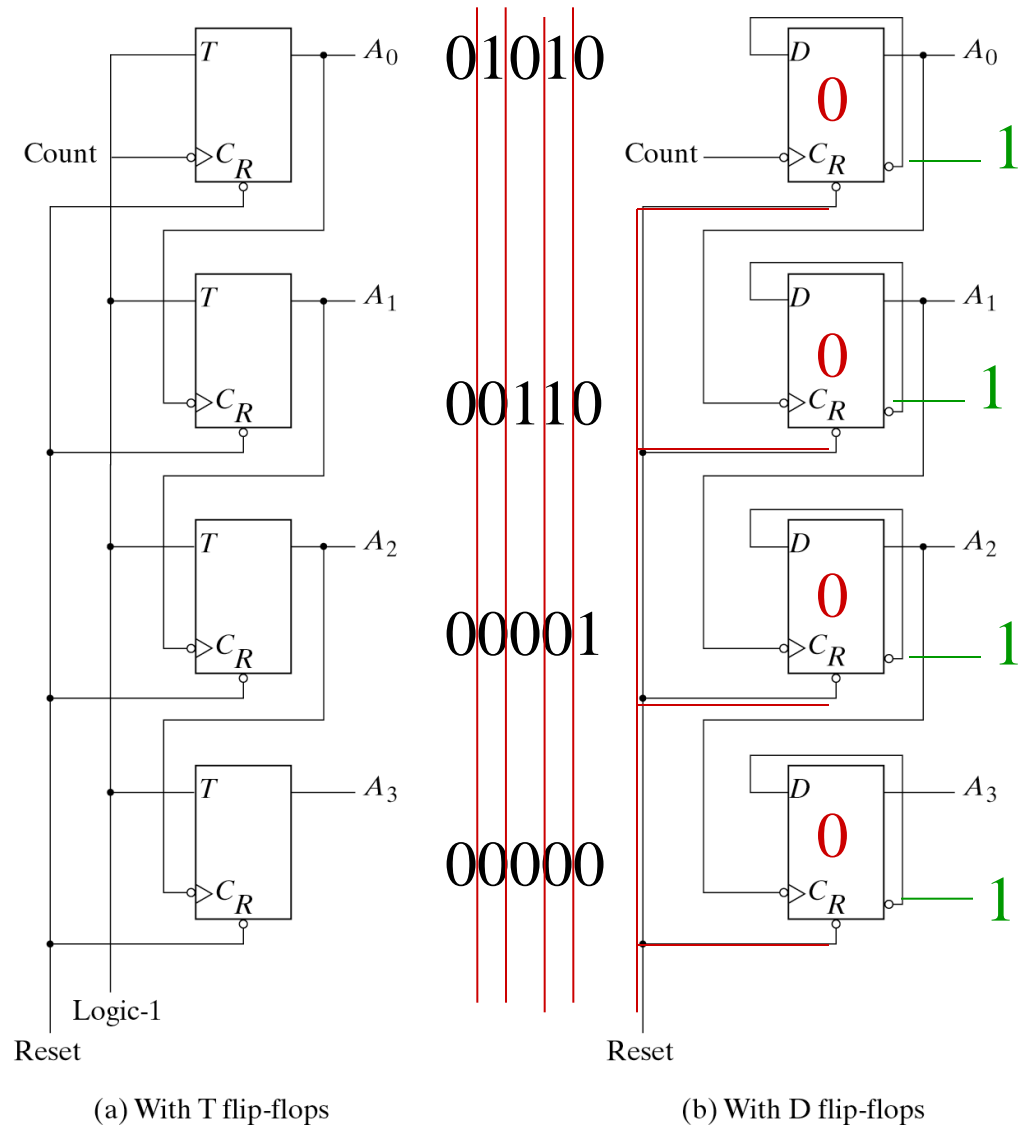


Fig. 6-8 4-Bit Binary Ripple Counter

Another Asynchronous Ripple Counter

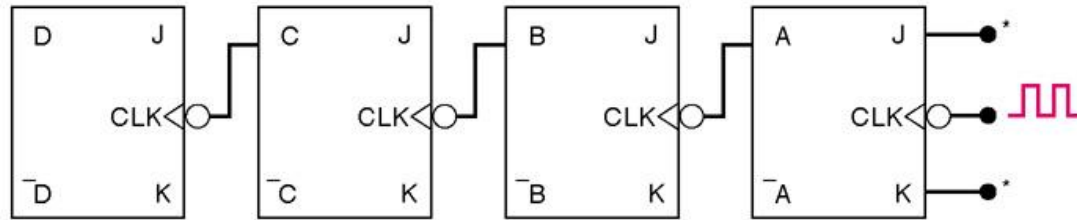

*All J and K inputs assumed to be 1.

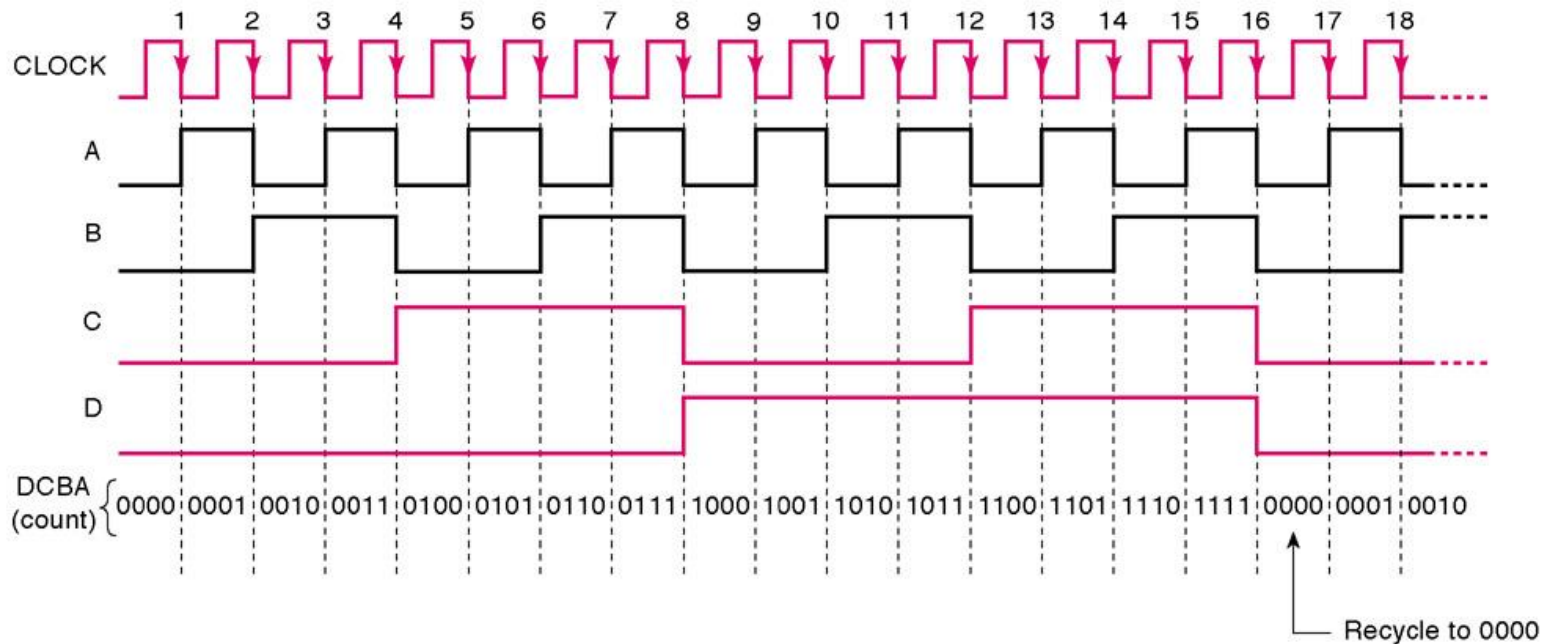


- Similar to T flop example on previous slide

Binary Counters

Counters produce a fixed sequence of binary digits, or states.


Counters are normally designed to recycle or restart the sequence.

Example:

 

Binary Counters: Modulus

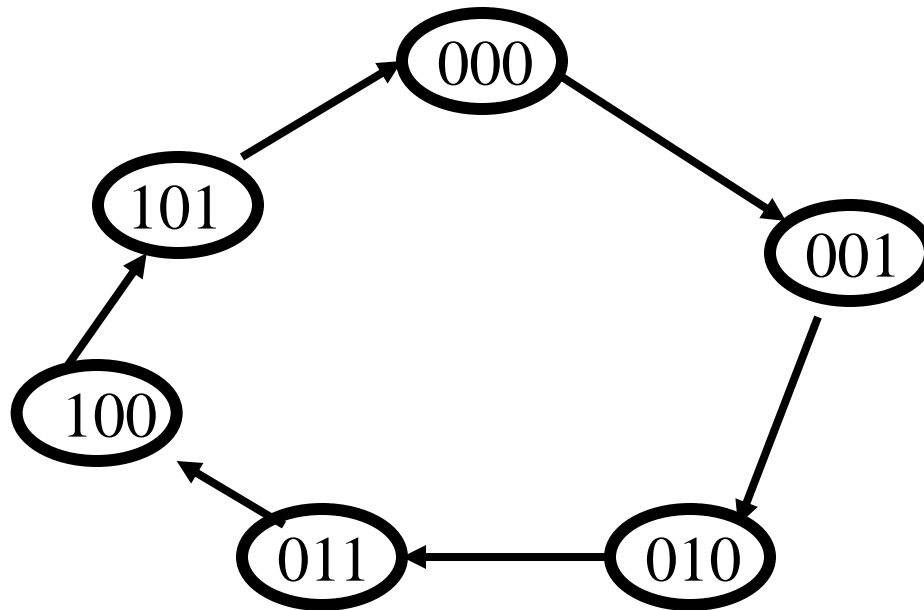- The number of output states is called the MODULUS, or MOD.
 - For example, a mod-6 counter has 6 unique output states → what's the max MOD ?



Counter Sequences

→ *Full Sequence Count*



refers to a natural count that includes all possible binary numbers. It's modulus is the same as its maximum modulus.

→ *A Truncated Sequence Count*

when the modulus is less than its maximum, or where less than all possible binary numbers are used.


Binary Counters: Up/Down

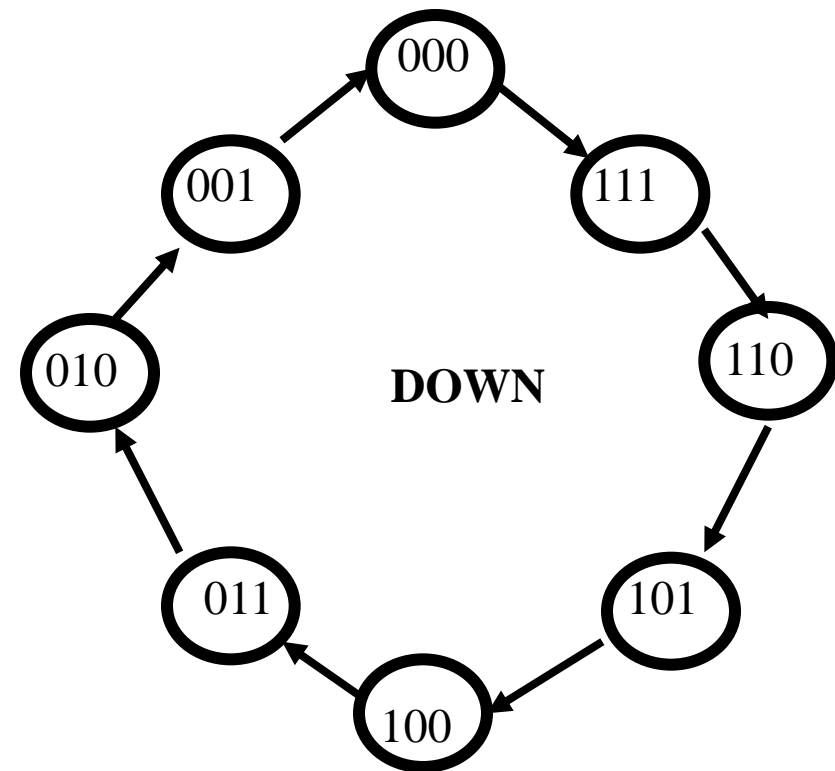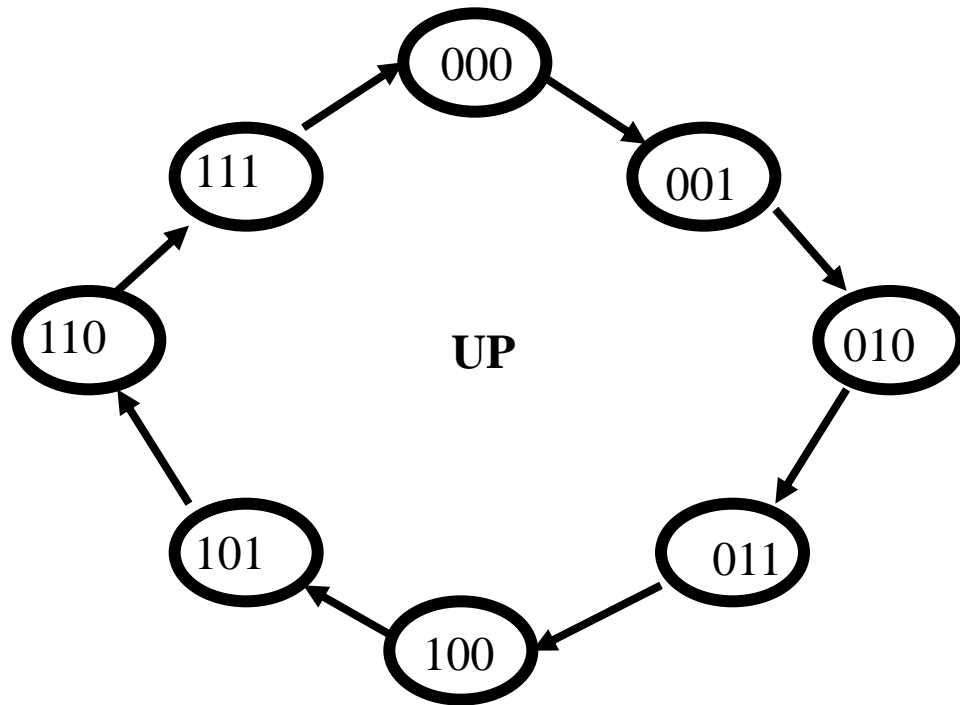A sequential count refers to a natural numerical count. The sequence can be Up or Down:



Counter State Diagram

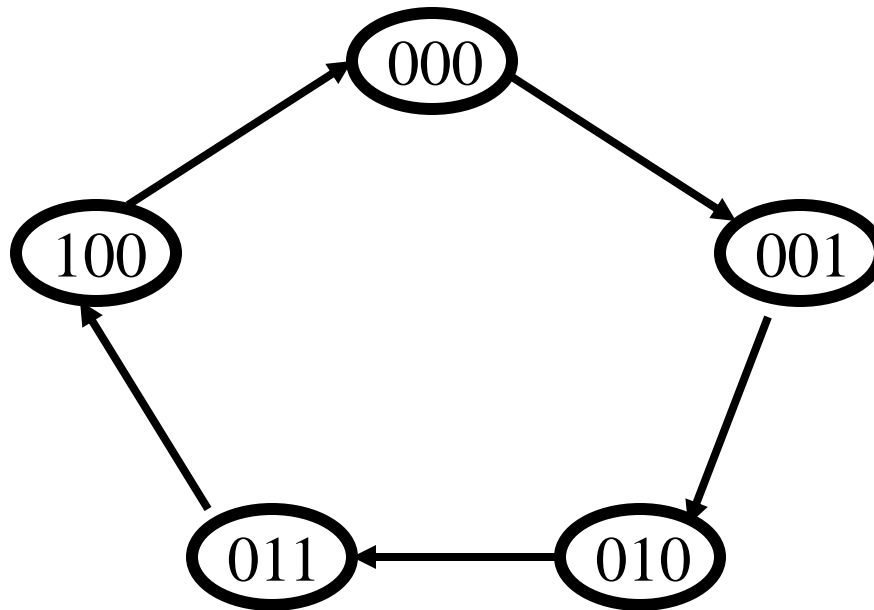- Counter states are sequential, where an output state will follow another in a sequence.
- State Diagrams are used to present the sequence of these states.



State Diagram

Counter State Table

- A State Table is another means of presenting state sequences.
- As with the state diagram, the state table will help determine the next output based on the present output state.

State Table

Current			Next		
Q_c	Q_b	Q_a	Q_c	Q_b	Q_a
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0

Design Procedure

- 1- Obtain from a (given) state table,
 - (i) the state diagram and
 - (ii) transition table
- 2- Provide the required input to each of the flip-flops by **utilizing the outputs of any of the other flip-flops.**
- 3- Use external gates, to detect specific, usable sequences of flip-flop outputs to create the necessary next input levels. (How to create inputs from outputs)
- 4- Use K-Maps to record and simplify the available outputs to create the inputs.
- 5- Implement the Circuit (i.e. Diagram)

Transition Tables


- By using K-Maps, we no longer need to utilize the toggling mode of a flip-flop (as in asynchronous). This allows us to use any edge triggered flip-flop to create the non-sequential counter.
- We need to know how the different flip-flops respond to various input states, based on their **current state**.

Building a Transition Table

- Building a Transition Table is done using the Function Tables of the Flip-Flops.
- Where the Function Table indicates “Q”, “Q’” or “No Change”, we indicate the binary value.

D Flip flop

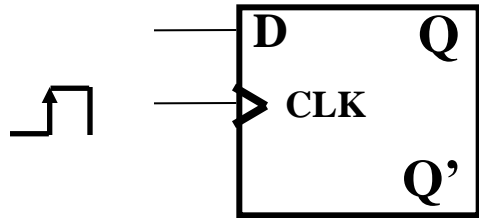
- Output changes only on the clock transition



Symbol

D	Q_{n+1}
0	0
1	1

D	CLK	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q_0	Q_0'

 

D Flip flop can be implemented using SR

$$S = D$$

$$R = D'$$


Transition Table: Example with D Flip Flop

D-FLIP-FLOP		
Present	Next	Input
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

- we indicate the present and the next states of the outputs.
- The input states indicates the required D input to produce the next state.

JK Flip flop

Symbol

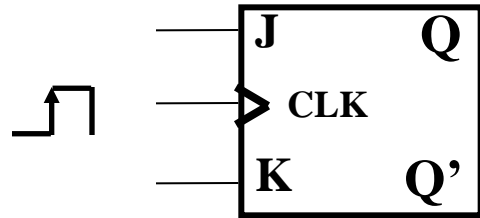

J	K	Q_{n+1}	Function
0	0	Q_n	No change
0	1	0	RESET
1	0	1	SET
1	1	Q'_n	complement (also Toggle)

Same as SR except for
 $K=J= 1$ the JK flip flop will
Output the opposite state of
 Q_n .

- Q_n = state *before* positive edge
- Q_{n+1} = state *after* positive edge

If $Q_n = 1$ then $Q_{n+1} = 0$

If $Q_n = 0$ then $Q_{n+1} = 1$

Transition Tables

J-K Flip-Flop Transition Table

- we indicate the present and next Q-output. If the flip-flop toggles or holds, we indicate that binary value.
- Also note that we need to determine both the J and K inputs.
- The “X” indicates “Don’t Care” states (can be ‘1’ or ‘0’ input).

J-K FLIP-FLOP		
Present	Next	Input J K
0	→ 0	0 X
0	→ 1	1 X
1	→ 0	X 1
1	→ 1	X 0

J-K Flip Flop Transition Table

J-K FLIP-FLOP		
Present	Next	Input J K
0	→ 0	0 X
0	→ 1	1 X
1	→ 0	X 1
1	→ 1	X 0

States

Hold or Reset

Toggle or Set


Toggle or Reset

Hold or Set

→ each output of the J-K Flip-Flop is the result of 2 possible states.

Building a K-Map with D Flip Flop

 - To build a K-Map, we first need:
 - 1- State Diagram of the output sequence
 - 2- State Table of the output sequence
 - 3- Transition Table for the Flip-Flop we intend to use (here D ff)
 - Present and Next outputs
 - Necessary inputs to create Next outputs




Present			Next		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A
0	0	0	0	1	0
0	1	0	1	1	0
1	1	0	0	0	1
0	0	1	0	0	0

D-FLIP-FLOP		
Present	Next	Input
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

Building a K-Map for D Flip Flop: **Step 1**

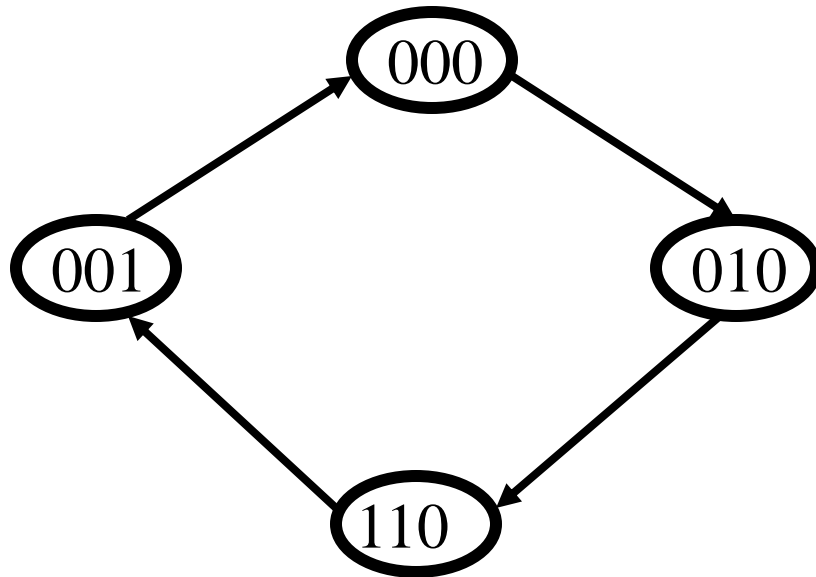- Draw the State Table and State Diagram of the output sequence.



State Diagram

Present	Next
$Q_C Q_B Q_A$	$Q_C Q_B Q_A$
0 0 0	0 1 0
0 1 0	1 1 0
1 1 0	0 0 1
0 0 1	0 0 0

State Table

Building the K-Map : Step 2

- Determine the type of Flip-Flop and its Transition Table. For our example, we use the D Flip-Flop:

D-FLIP-FLOP		
Present	Next	Input
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

Transition Table

Building the K-Map: Step 3

•Build the State Table with the inputs indicated:

D-FLIP-FLOP		
Present	Next	Input
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

Present			Next			Input		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	D_C	D_B	D_A
0	0	0	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

D-FLIP-FLOP

Present	Next	Input
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

Present			Next			Input		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	D_C	D_B	D_A
0	0	0	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

Animated

Building the K-Map: Step 4

Build a K-Map for each output:

Present			Next			Input		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	D_C	D_B	D_A
0	0	0	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

$Q_C Q_B$		Q_A	
		0	1
00	01	0	0
11	10	1	X
		0	X
		X	X

D_C

$Q_C Q_B$		Q_A	
		0	1
00	01	1	0
11	10	1	X
		0	X
		X	X

D_B

$Q_C Q_B$		Q_A	
		0	1
00	01	0	0
11	10	0	X
		1	X
		X	X

D_A

Present			Next			Input		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	D_C	D_B	D_A
0	0	0	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

000

010

	Q_A	0	1
$Q_C Q_B$	00	0	0
	01	1	X
	11	0	X
	10	X	X

D_C

	Q_A	0	1
$Q_C Q_B$	00	1	0
	01	1	X
	11	0	X
	10	X	X

D_B

	Q_A	0	1
$Q_C Q_B$	00	0	0
	01	0	X
	11	1	X
	10	X	X

D_A

A
N
I
M
A
T
E
D

Building the K-Map: Step 5

determine the simplified SOP for the inputs.

$Q_C Q_B \backslash Q_A$	0	1
00	0	0
01	1	X
11	0	X
10	X	X

D_C

$$D_C = Q'_C Q_B$$

$Q_C Q_B \backslash Q_A$	0	1
00	1	0
01	1	X
11	0	X
10	X	X

D_B

$$D_B = Q'_C Q'_A$$

$Q_C Q_B \backslash Q_A$	0	1
00	0	0
01	0	X
11	1	X
10	X	X

D_A

$$D_A = Q_C$$

Binary Counter Examples (will NOT be on the website)

- Examples of binary counter with JK flip Flop

1- Without missing States

2- With missing States

Binary counter with JK flip flop

Transition Table for JK FF

(a) JK flip-flop truth table

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


(b) Transition table for JK flip-flops

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Binary counter with JK flip flop

- Build state diagram
 - Build the state table that consists of
 - * Current state output
 - * Next state output
 - * JK inputs for each flip-flop
 - Use K-maps to simplify expressions for JK inputs
 - Build the circuit for the counter
-

Binary counter with JK flip flop

 

- 3-bit binary counter
 - 3 JK flip-flops are needed
 - Current state and next state outputs are 3 bits each
 - 3 pairs of JK inputs
-

Binary counter with JK flip flop

State table for the binary counter example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

Binary counter with JK flip flop

Use K-maps to simplify expressions for JK inputs

		BC			
A		00	01	11	10
0	0	0	0	1	0
1	d	d	d	d	d

$$J_A = B C$$

		BC			
A		00	01	11	10
0	d	d	d	d	d
1	0	0	1	0	0

$$K_A = B C$$

		BC			
A		00	01	11	10
0	0	1	d	d	d
1	0	1	d	d	d

$$J_B = C$$

		BC			
A		00	01	11	10
0	d	d	1	0	0
1	d	d	1	0	0

$$K_B = C$$

		BC			
A		00	01	11	10
0	1	d	d	1	
1	1	d	d	1	

$$J_C = 1$$


		BC			
A		00	01	11	10
0	d	1	1	d	
1	d	1	1	d	

$$K_C = 1$$

$X = d$

Binary counter with JK flip flop

- Final circuit for the binary counter

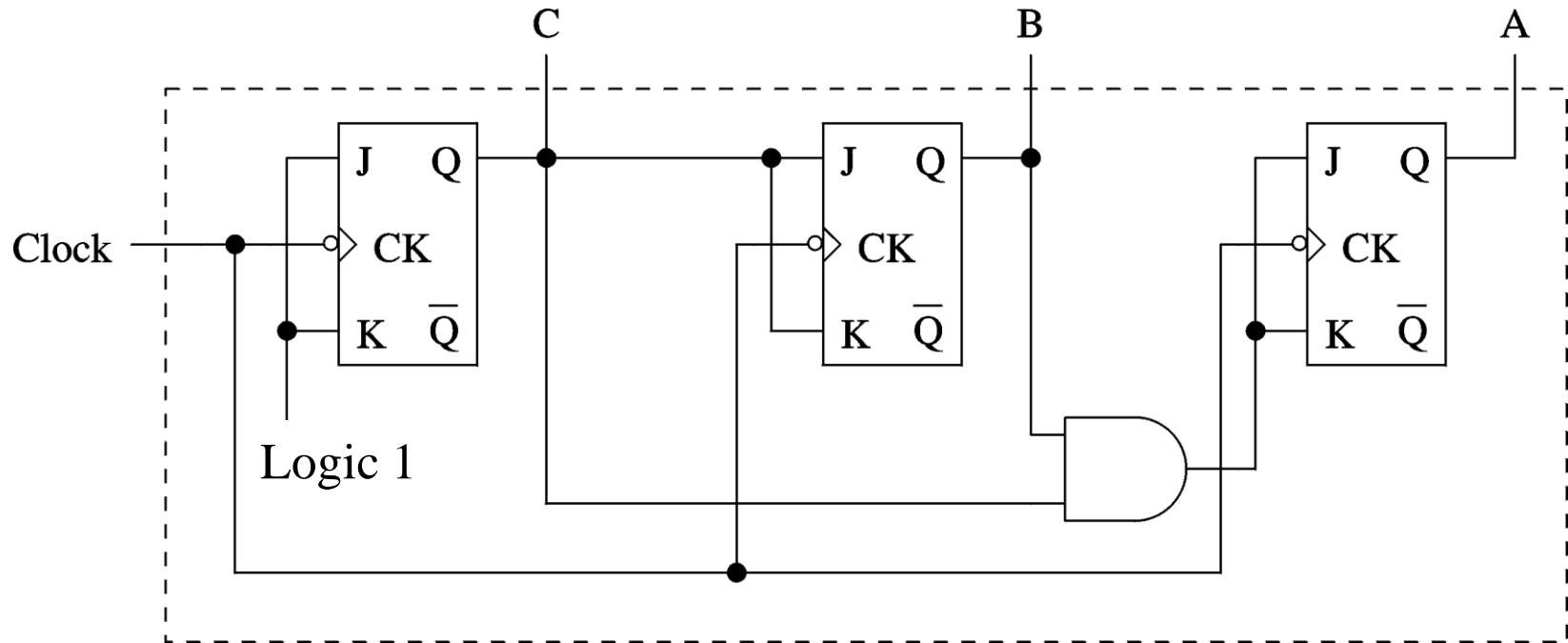


Binary counter with JK flip flop (missing states)

→ Example with missing states

0 → 3 → 5 → 7 → 6 → 0

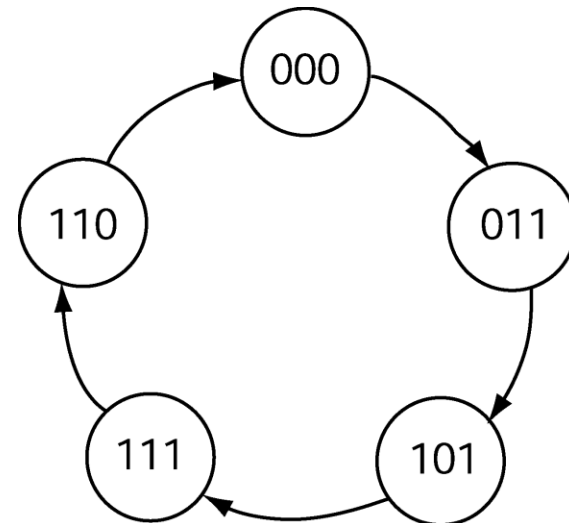- Same design process as before
- One significant change
 - * **Missing states**
 - » 1, 2, and 4
 - » Use don't cares for these states



Binary counter with JK flip flop (missing states)

State table
for the
counter
example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	1	1	0	X	1	X	1	X
0	0	1	X	X	X	X	X	X	X	X	X
0	1	0	X	X	X	X	X	d	X	X	X
0	1	1	1	0	1	1	X	X	1	X	0
1	0	0	X	X	X	X	X	X	X	X	X
1	0	1	1	1	1	X	0	1	X	X	0
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	1	1	0	X	0	X	0	X	1

Binary counter with JK flip flop (missing states)

K-maps to
simplify
JK input
expressions

X=d

		BC			
A		00	01	11	10
0		0	d	1	d
1		d	d	d	d

$$J_A = B$$

		BC			
A		00	01	11	10
0		d	d	d	d
1		d	0	0	1

$$K_A = \bar{C}$$

		BC			
A		00	01	11	10
0		1	d	d	d
1		d	1	d	d

$$J_B = 1$$

		BC			
A		00	01	11	10
0		d	d	1	d
1		d	d	0	1

$$K_B = \bar{A} + \bar{C}$$

		BC			
A		00	01	11	10
0		1	d	d	d
1		d	d	d	0


$$J_C = \bar{A}$$

		BC			
A		00	01	11	10
0		d	d	0	d
1		d	0	1	d


$$K_C = A B$$

Binary counter with JK flip flop (missing states)

Final circuit

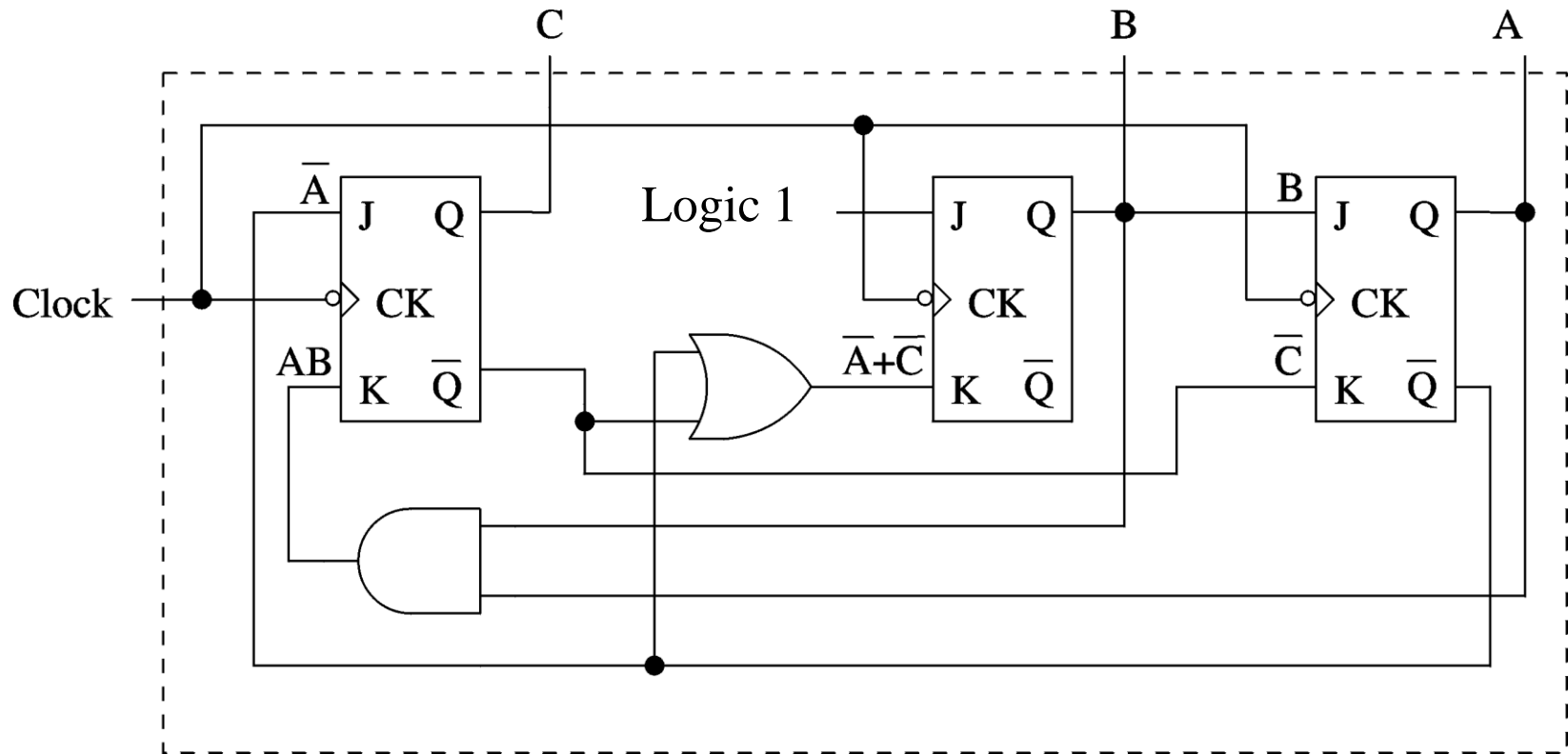

 Example: - Design a 3 - bit binary counter using T flip - flops






Example: - Design a 3 - bit binary counter using T flip - flops.

Present State	Next State	Flip - Flop Inputs		
A B C	A B C	T A	T B	T C
0 0 0	0 0 1	0	0	1
0 0 1	0 1 0	0	1	1
0 1 0	0 1 1	0	0	1
0 1 1	1 0 0	1	1	1
1 0 0	1 0 1	0	0	1
1 0 1	1 1 0	0	1	1
1 1 0	1 1 1	0	0	1
1 1 1	0 0 0	1	1	1


Example: - Design a 3 - bit binary counter using T flip - flops.

- Kmap

   

Design: Synchronous BCD

- Design a BCD counter using T Flip Flop

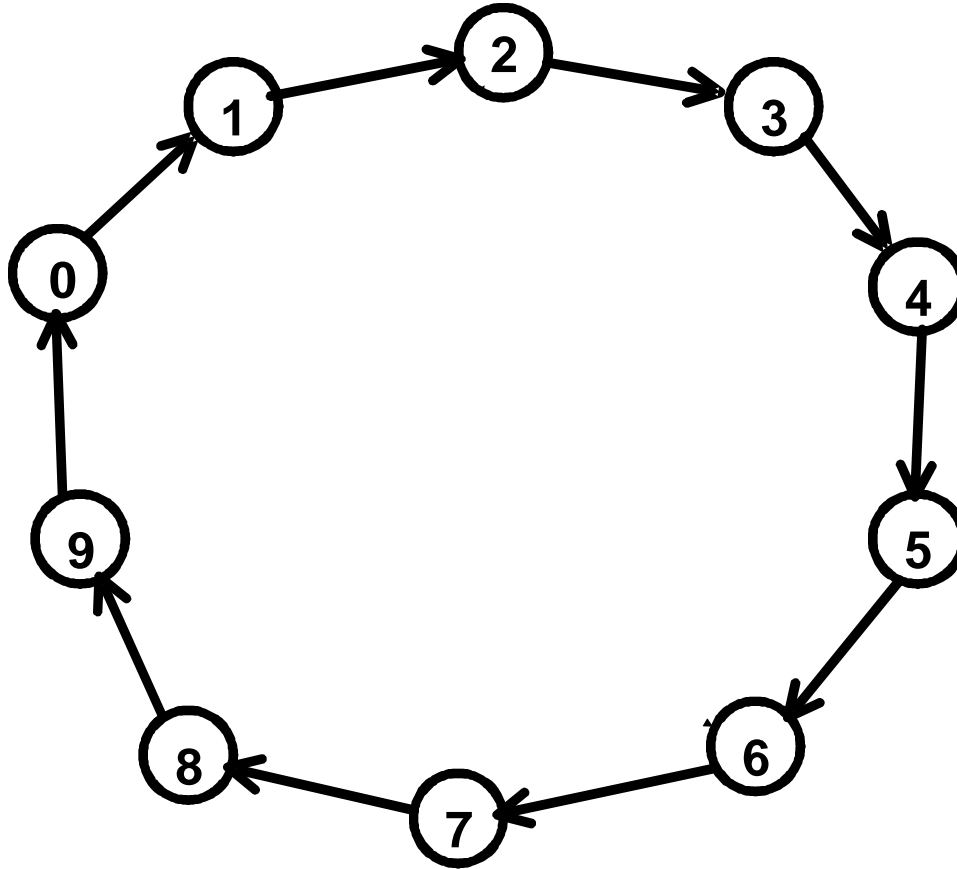

Design: Synchronous BCD

- State table

Current State				Next State				T-FF inputs			
Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	T ₈	T ₄	T ₂	T ₁
0	0	0	0	0	0	0	1				
0	0	0	1	0	0	1	0				
0	0	1	0	0	0	1	1				
0	0	1	1	0	1	0	0				
0	1	0	0	0	1	0	1				
0	1	0	1	0	1	1	0				
0	1	1	0	0	1	1	1				
0	1	1	1	1	0	0	0				
1	0	0	0	1	0	0	1				
1	0	0	1	0	0	0	0				

Design: Synchronous BCD

- We can use the sequential logic model to design a synchronous BCD counter with T flip-flops. Below is the State Table.

Current State				Next State				T-FF inputs			
Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	T ₈	T ₄	T ₂	T ₁
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1

- Don't care states have been left out here.
-

Synchronous BCD (Continued)

- Use K-Maps to minimize the next state function:





$$T_8 = Q_8 \bullet Q_1 + Q_4 \bullet Q_2 \bullet Q_1$$

$$T_4 = Q_2 \bullet Q_1$$

$$T_2 = Q_8' \bullet Q_1$$


$$T_1 = "1"$$

Note: Don't Cares are included here.

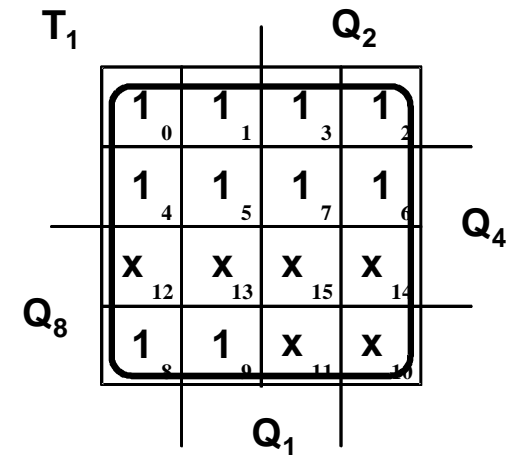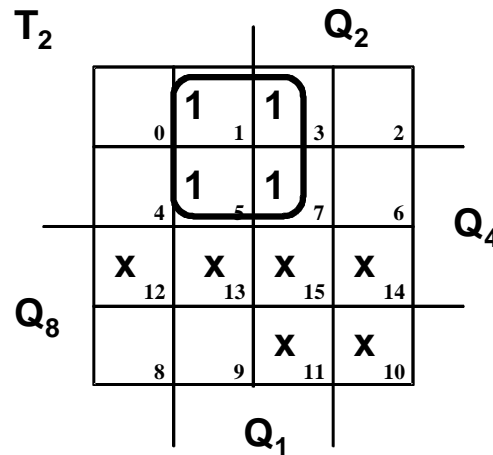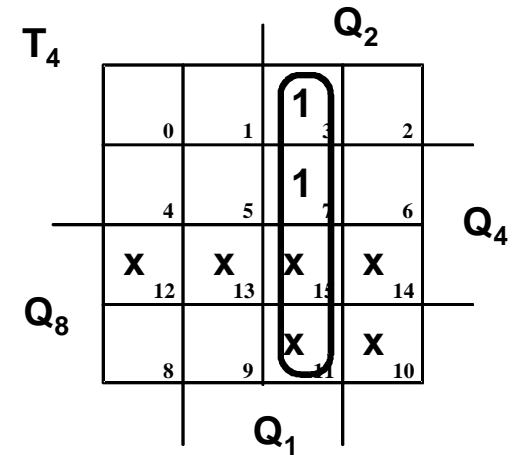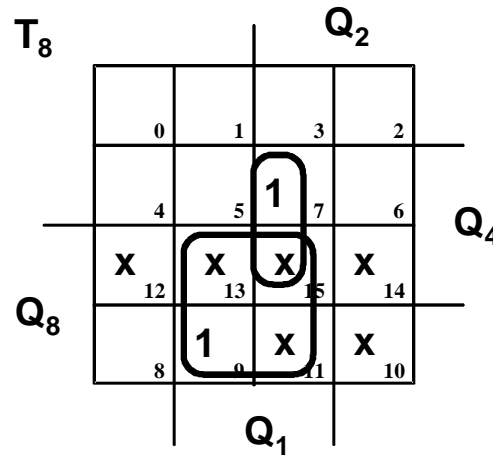

Synchronous BCD (Continued)

- The minimized circuit:

 

Designing a Synchronous BCD Counter

Present State				Next State				Output	Next State			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	1	0	0	1	1	0	0	0	0	1	1
0	1	0	1	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$TQ_1 = 1, \quad TQ_2 = Q_8'Q_1, \quad TQ_4 = Q_2Q_1, \quad TQ_8 = Q_8Q_1 + Q_4Q_2Q_1 \quad y = Q_8Q_1$$

Asynchrone, BCD Counter


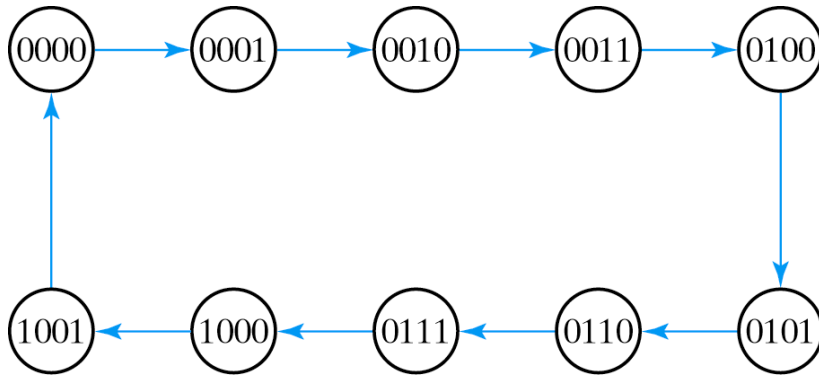


Fig. 6-9 State Diagram of a Decimal BCD-Counter

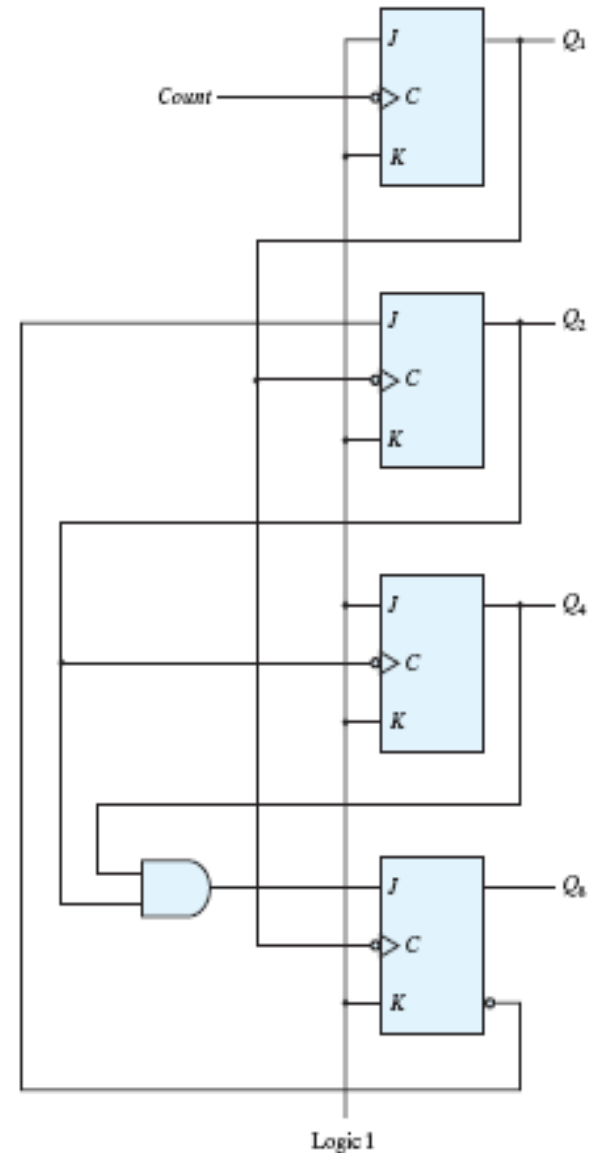

Decimal (BCD) Counter

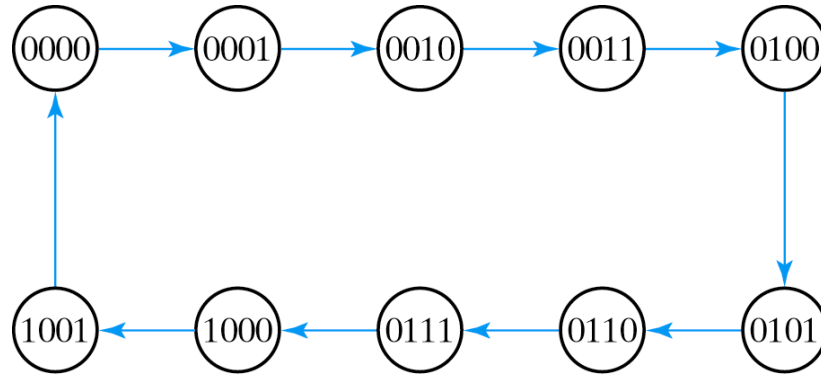


Fig. 6-9 State Diagram of a Decimal BCD-Counter


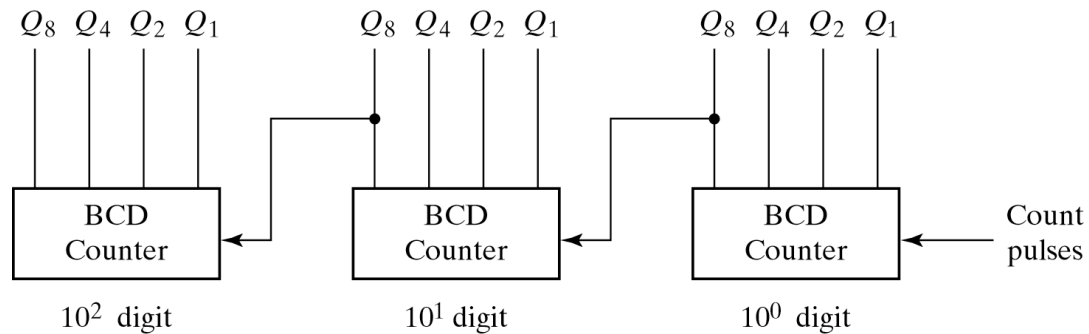


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

Counter with Parallel load

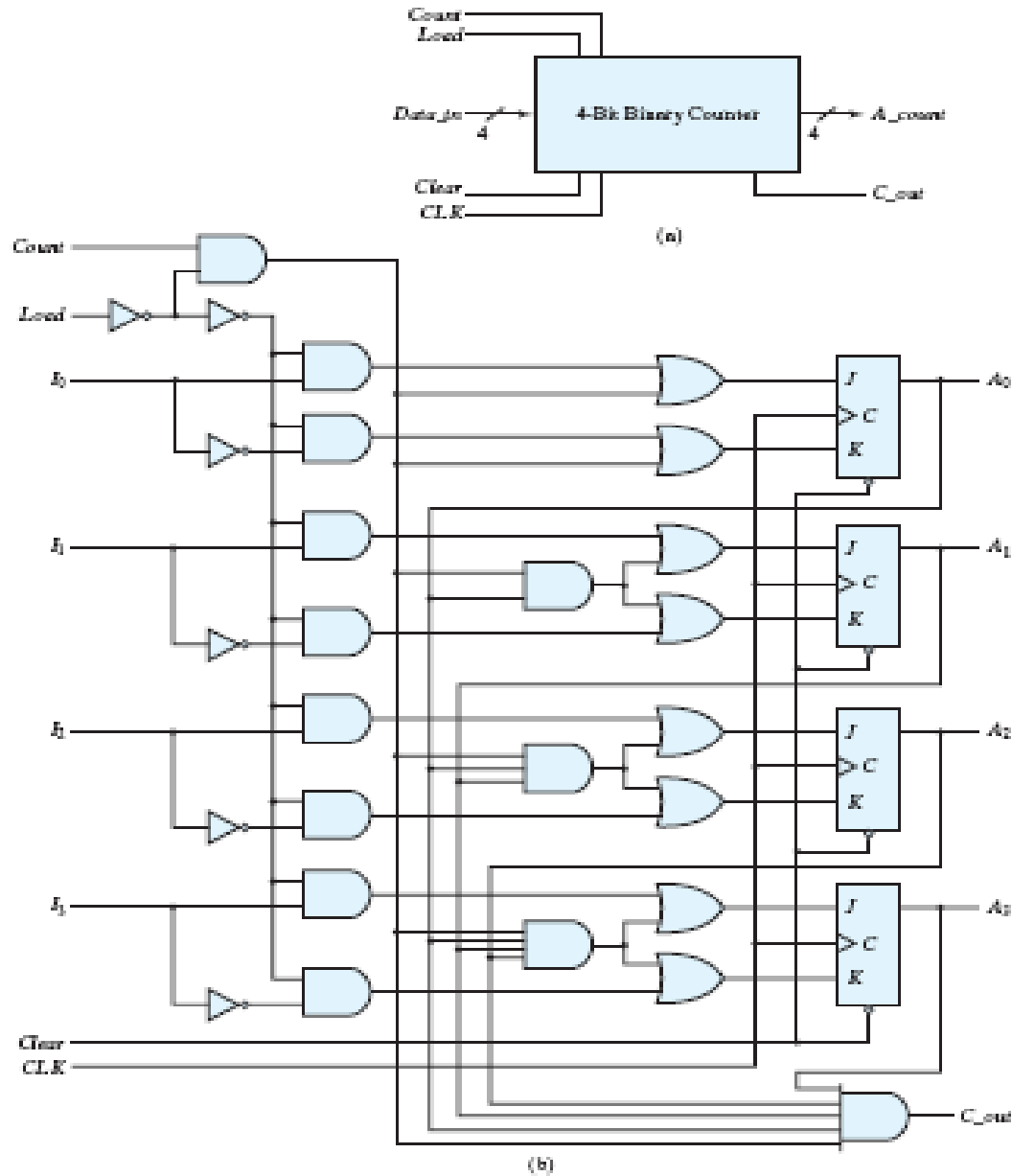

More BCD Counters (with Parallel Load)

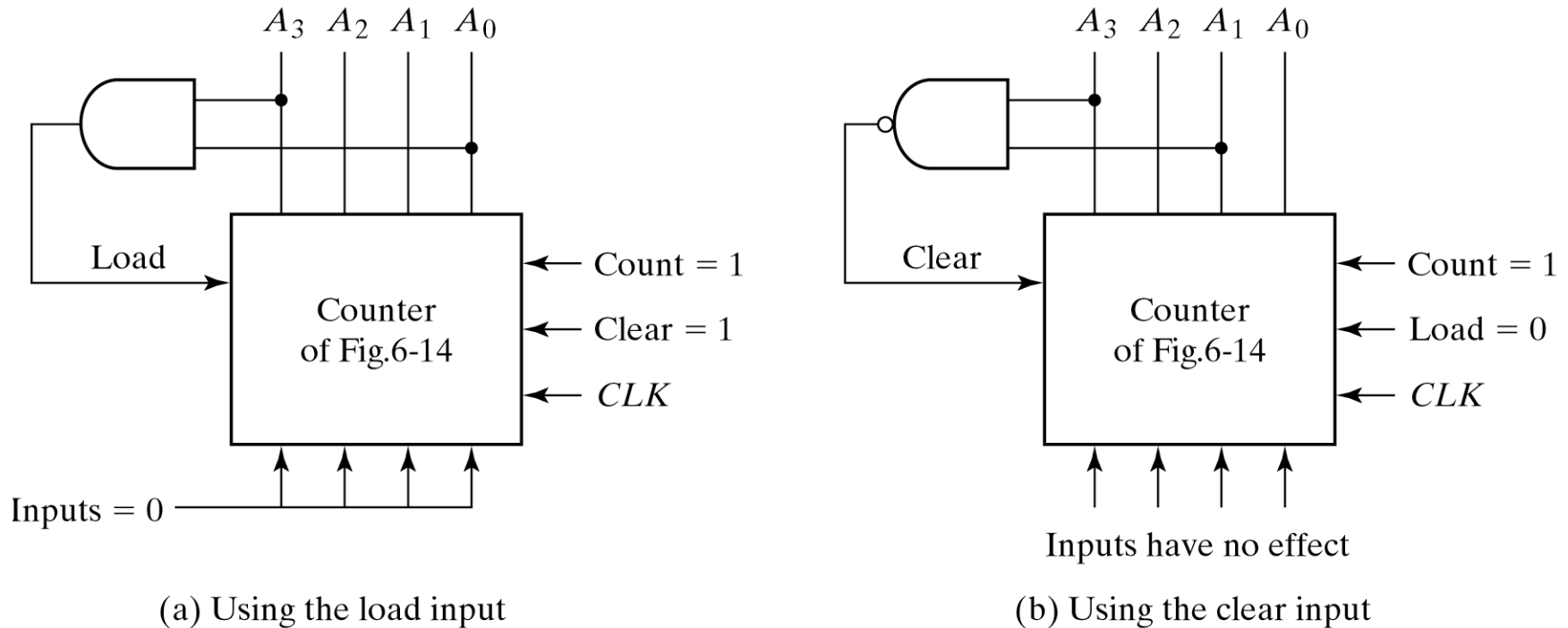


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

Sequential Logic Circuits: Examples

(**Note:** in addition to the examples presented here other examples were discussed in the class)

- Asynchronous counters (3 examples were discussed in the class)

- Synchronous counters (2 examples were discussed in the class)

- Steps for building synchronous counters (comprehensive examples with animation is used here to show the steps with the D flip Flops)



- Ring counter

- Johnson counter

Ring Counter


- A ring counter takes the serial output of the last Flip-Flop of a shift register and provides it to the serial input of the first Flip-Flop.
- This is also known as a re-circulating shift register.

Shift-Register Counters: Ring Counter

 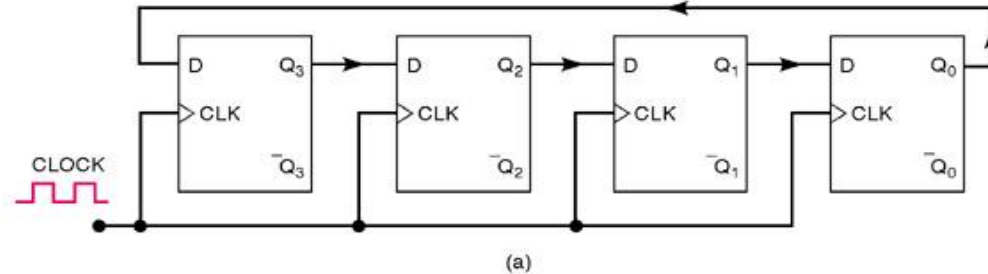

Q ₃	Q ₂	Q ₁	Q ₀	CLOCK pulse
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
.
.

(c)

 


Johnson Counter



- A Johnson Counter re-circulates the last flip-flop Q' (inverted) output back to the input of the first Flip-Flop.

000, 100, 110, 111, 011, 001, 000, 100, 110,

Initial state
↖

 


Johnson Counter

 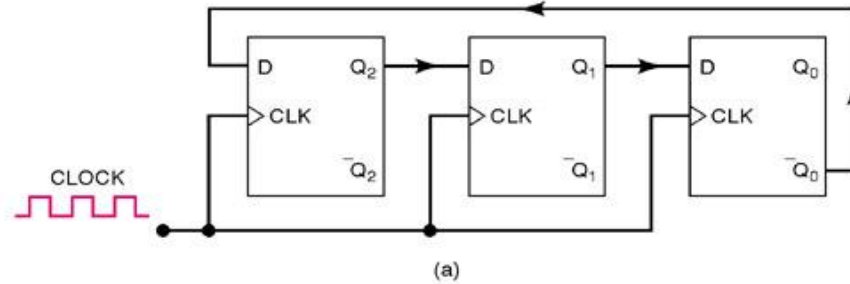

Q ₂	Q ₁	Q ₀	CLOCK pulse
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
·	·	·	·
·	·	·	·
·	·	·	·

(c)

 

(d)