

Lecture 2: Basic Quantities and Circuit Elements

ELEC2501 Circuits and Signals

- SI Units
- Basic quantities
 - Current
 - Voltage
- Voltage-current relationship
- Power
- Examples

- Circuit elements
- Sources
 - Independent
 - Dependent
- Examples

SI Units

Base Units

| unit | abbreviation | property |
|----------|--------------|---------------------|
| metre | m | length |
| kilogram | kg | mass |
| second | s | time |
| ampere | A | electric current |
| kelvin | K | temperature |
| candela | cd | luminous intensity |
| mole | mol | amount of substance |

Derived Units

Many exist. Some examples

| unit | abbreviation | property |
|--------|--------------|-----------------------|
| Watts | W | power |
| Volts | V | potential difference |
| Joules | J | energy |
| Ohms | Ω | electrical resistance |

Supplementary Units

| | | |
|-----------|-----|---------------------|
| radian | rad | unit of angle |
| steradian | sr | unit of solid angle |

Prefixes

| Prefix | T | G | M | k | m | μ | n | p |
|-----------|-----------|--------|--------|--------|-----------|-----------|-----------|------------|
| Magnitude | 10^{12} | 10^9 | 10^6 | 10^3 | 10^{-3} | 10^{-6} | 10^{-9} | 10^{-12} |

Basic Quantities.

Let us focus on some terms we will regularly use when analysing electrical circuits.

Current.


Rate of change of charge

$$i(t) = \frac{dq(t)}{dt} \quad \text{or} \quad q(t) = \int_{-\infty}^t i(x) dx$$


i - current (ampere)

q - charge (coulomb)

t - time

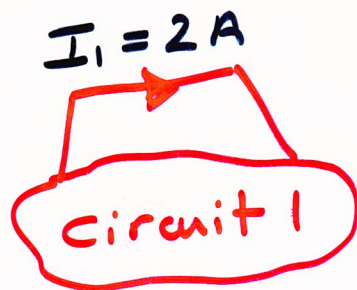

2C flowing L to R
in 1s.

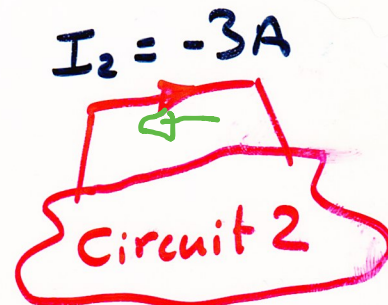

3C flowing R to L
in 1s.


Voltage, electromotive force (EMF) or potential difference.

Charges in motion yield an energy transfer. Voltage between two points is defined as the difference in energy level of a unit charge located at each of the two points.


$$V = \frac{W}{q}$$

V - potential difference (V)
 W - energy change or work done (J)
 q - charge (C).

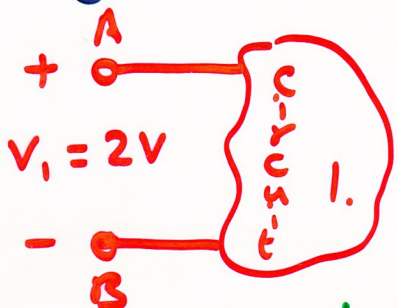By implication from this definition one point has a higher potential w.r.t. the other. Represented by sign convention.




A has higher potential

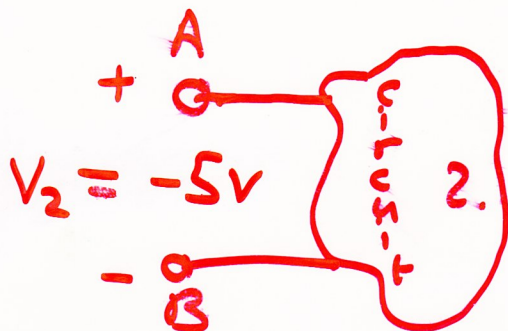


B has higher potential

Voltage - Current relationships.

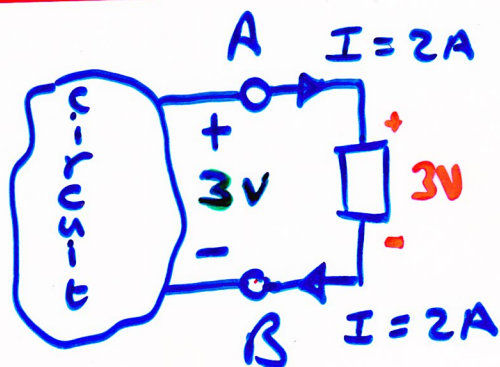


Energy absorbed.

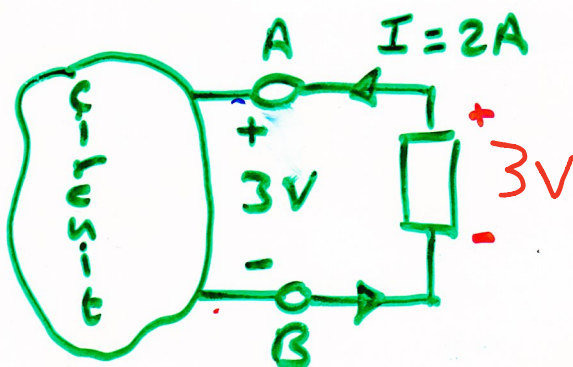

Energy supplied

Note the current flow convention

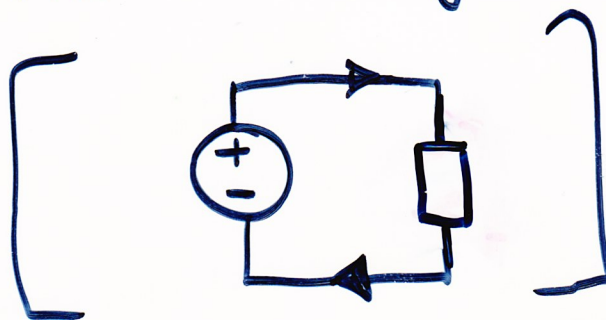

Current direction is $+$ \rightarrow $-$.
Opposite of actual electron flow.

4
Considering the potential difference in terms of energy and charge changes.

$$V = \frac{dW}{dq}$$

V - potential diff.

dW - energy change with charge change, dq .

But $i = dq/dt$

$$\text{So } \underbrace{V i}_{\text{~~~~~}} = \frac{dW}{dq} \frac{dq}{dt} = \frac{dW}{dt} = \underbrace{P}_{\text{~~~~~}}$$

P is power.


$$\text{Alternatively } \Delta W = \int_{t_1}^{t_2} v i dt$$

$$\underline{P = i v}$$

Examples

(1)

(Irwin E. 1 a)

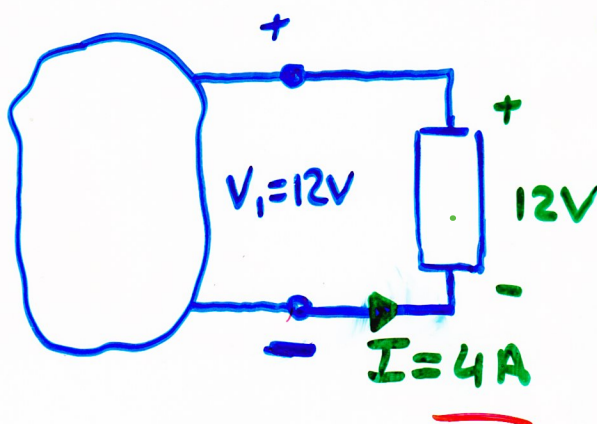

Determine the amount of power absorbed or supplied by the element.

$$V = 12V$$


$$I = \underline{-4A}$$

$$\therefore P = -48W$$

48W supplied.

(2)

(Irwin 1.36)

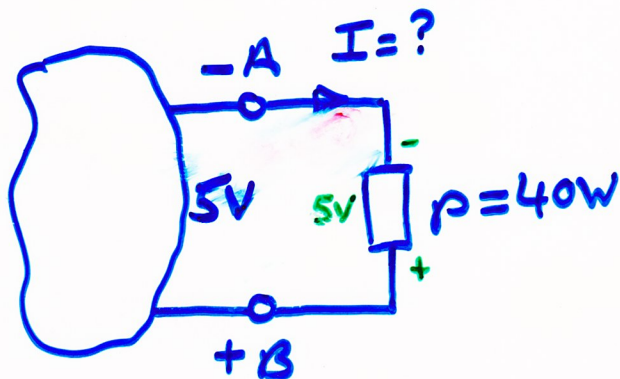

Determine the current

$$P = 40W \quad \underline{\underline{(absorbing)}}$$

$$V_{AB} = -5V$$

$$\text{Now } P = IV$$

$$I = \frac{P}{V}$$

$$I = \frac{40}{-5} = -8A$$

Circuit Elements

Circuit elements classified by the current through it and the voltage (or p.d.) across it.

Two types: **active** and **passive**

ACTIVE - generates energy e.g. batteries, transistor devices.



PASSIVE - no energy generation e.g. resistors, capacitors & inductors.

Deal with passive components later.
Consider **ACTIVE** elements now.

4 active sources

1. Independent voltage source
2. " current "
3. Dependent voltage source
4. " current "



Independent Sources.

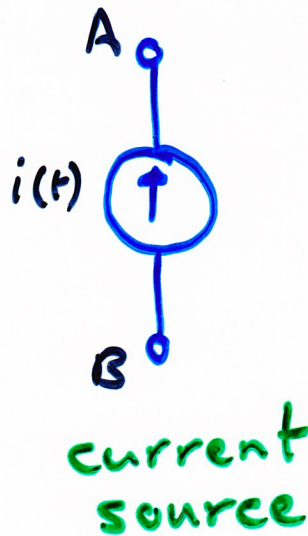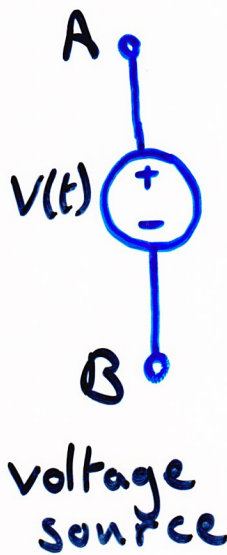

voltage source - voltage maintained independent of current through it.



current source - current maintained independent of voltage across it.

Dependent Sources.

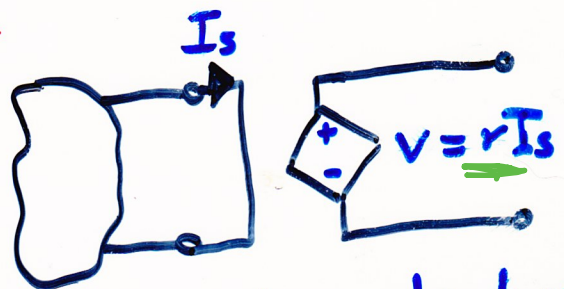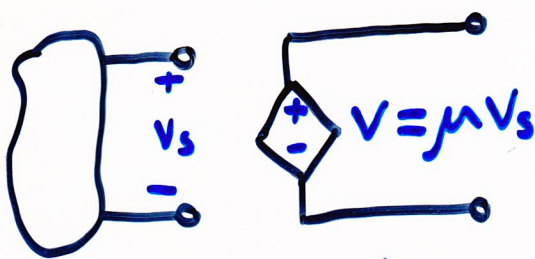

voltage dependent voltage source

current dependent voltage source

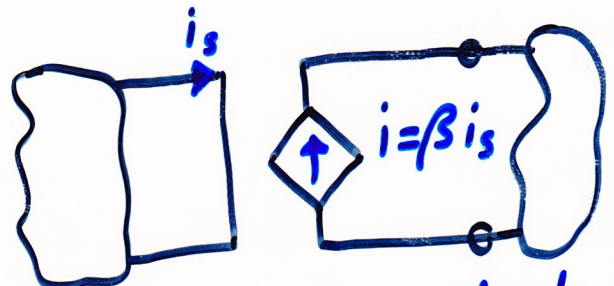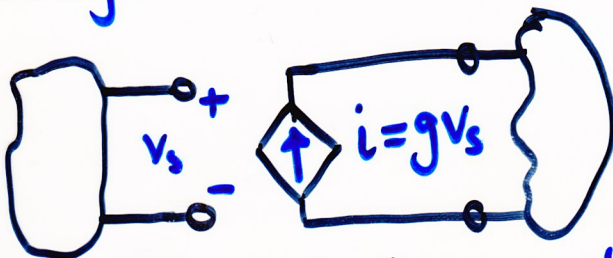


voltage dependent current source

current dependent current source.

Examples

(1)

(Irwin
Ext. 1.4b)

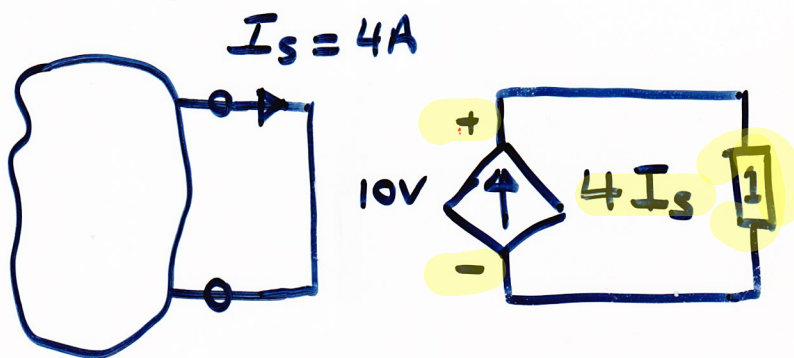

Power supplied to element 1?


$$I_s = 4A$$

$$\begin{aligned} \therefore \text{Current source produces, } I &= 4I_s \\ &= 4 \times 4 \\ &= \underline{16A} \end{aligned}$$

Potential across the element is 10V.

$$\begin{aligned} \text{So, power} &= I \times V \\ &= 16 \times 10 \\ &= \underline{160W} \end{aligned}$$

(2)
(Irwin
#1.3)

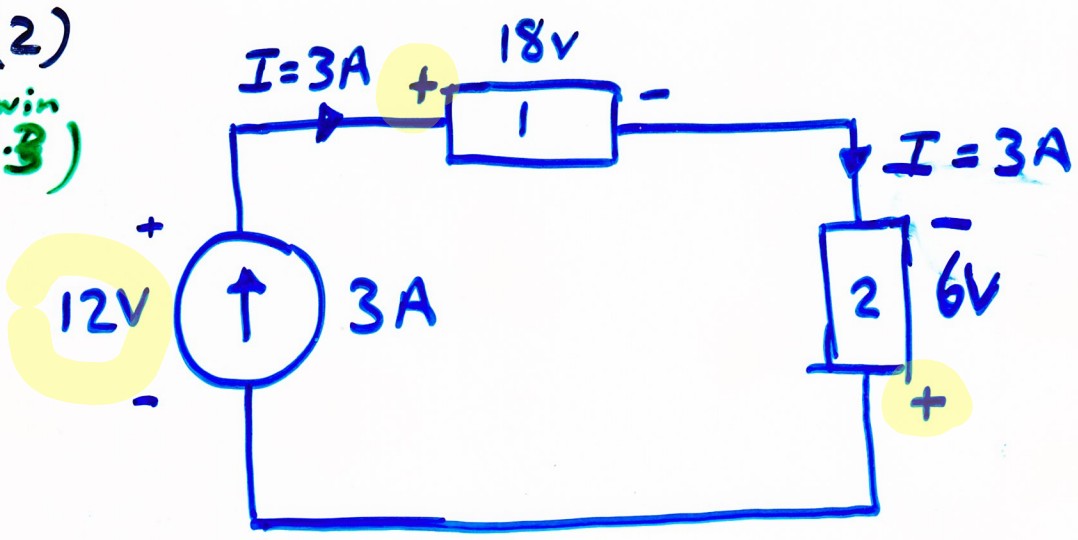


What are the power levels absorbed or supplied by elements 1 & 2?

Current source, $P_{\text{source}} = 12 \times 3 = -36W$
SUPPLIED!

Element 1, $P_1 = 3 \times 18 = 54W$
ABSORBED

Element 2, $P_2 = 3 \times -6 = -18W$
18W SUPPLIED.

(3) Problem 1.39 from Irwin.

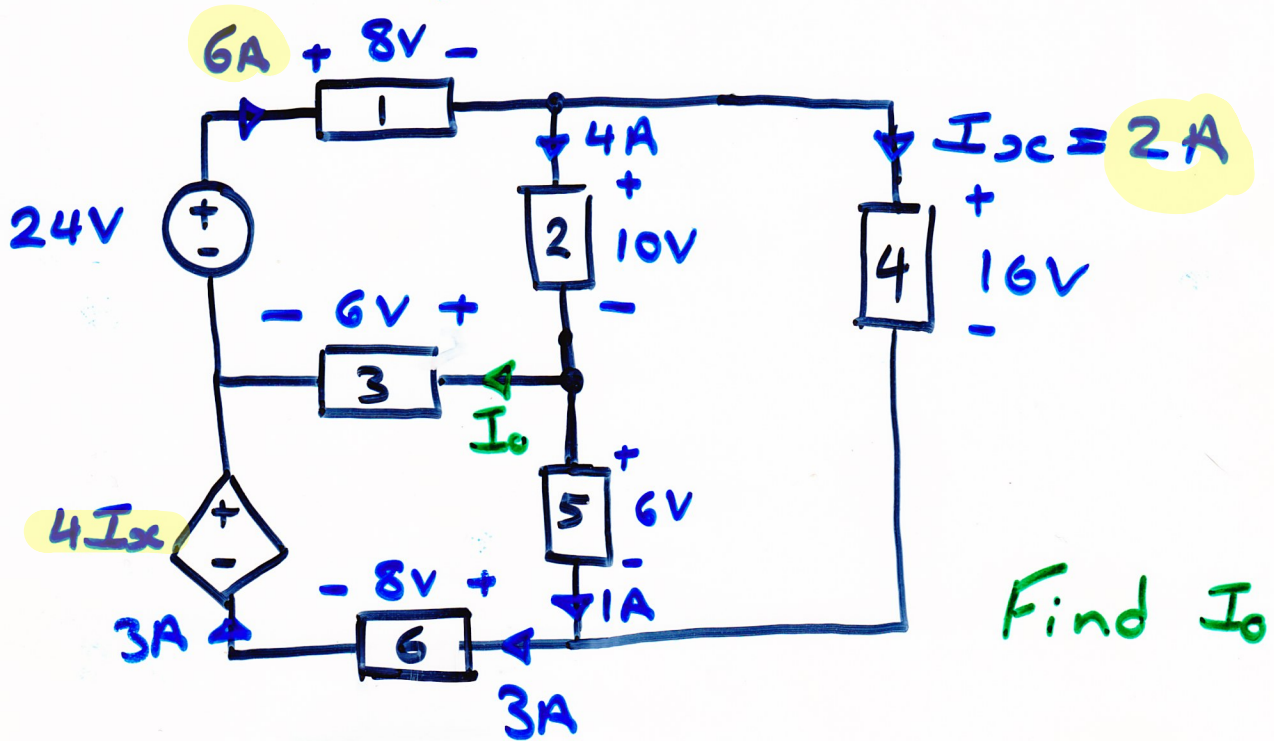

Voltage of dependent source, $V_{os} = 4 \times 2 = 8V$.

$$P_{os} = 8 \times 3 = -24W$$

$$P_{24V} = 24 \times 6 = -144W$$

$$P_1 = 8 \times (6) = 48W$$

$$P_2 = 10 \times (4) = 40W$$

$$P_4 = 16 \times (2) = 32W$$

$$P_5 = 6 \times (1) = 6W$$

$$P_6 = 8 \times (3) = 24W$$

$$\text{Total} = 18W$$

So element 3 must absorb 18W. Potential diff across is 6V so current is $18/6 = 3A$