

SYSC 3600 – Assignment #1 Solution

$$1/. \quad \dot{p} + kp = 0$$

fits general form $iy + 1/r y = 0$

$$\therefore p(t) = p_0 e^{-kt} = 100 e^{-kt} \text{ grams}$$

taking t in years (for convenience)

$$100 e^{-k(24100)} = 50 \quad \leftarrow \text{half of original 100 grams}$$

$$e^{-k(24100)} = 0.5$$

$$k = -\ln(0.5)/24100 = 2.876 \times 10^{-5} \text{ 1/years}$$

$$\text{time constant} = \tau = 1/k = 34,769 \text{ years}$$

It makes sense that the time constant is longer than the half life, as at one time constant only about 37% of the original amount will remain.

2/.

$$\text{area of can} = 2\left(\frac{\pi d^2}{4}\right) + \pi dh \quad \text{volume of can} = \frac{\pi d^2 h}{4}$$

$$\text{mass of beer} = \text{volume times density} = \frac{\pi d^2 h \rho}{4}$$

$$\text{heat transfer rate} = \dot{Q} = (T_R - T_B) * U * \text{area}$$

$$\text{rate of temperature change} = \dot{T}_B = \dot{Q} / (\text{mass} * c_p)$$

putting everything together:


$$\dot{T}_B = \left[(T_R - T_B) U \left(\frac{\pi d^2}{2} + \pi dh \right) \right] / \left(\frac{\pi d^2 h \rho c_p}{4} \right)$$
$$\dot{T}_B + \frac{4U \left(\frac{d}{2} + h \right)}{dh \rho c_p} T_B = \frac{4U \left(\frac{d}{2} + h \right)}{dh \rho c_p} T_R$$

The system is analogous to the charging capacitor example.

Note that the units work out (as they must).

$$\frac{4U \left(\frac{d}{2} + h \right)}{dh \rho c_p} \text{ has units of } 1/\text{sec}$$

3/.

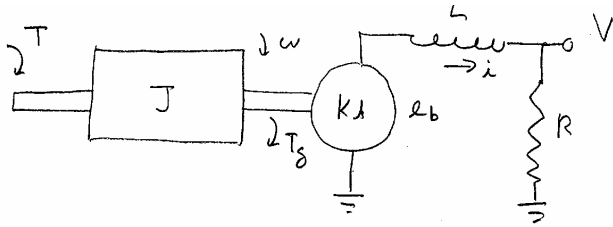

mechanical: $\dot{\omega} = \frac{T - T_g}{J}$ (1)

electrical: $-e_b + L\dot{i} + Ri = 0$ (2)

generator: $e_b = k_t \omega$ (3)

$T_g = k_t i$ (4)

output: $V = Ri$, $i = V/R$ (5)

$\dot{i} = \dot{V}/R$ (6)

start with (2)

use (5), (6) $-e_b + L(\dot{V}/R) + R(V/R) = 0$

use (3) $-k_t \omega + \frac{L}{R} \dot{V} + V = 0$

differentiate $-k_t \dot{\omega} + \frac{L}{R} \ddot{V} + \dot{V} = 0$

use (1) $-k_t \left(\frac{T - T_g}{J} \right) + \frac{L}{R} \ddot{V} + \dot{V} = 0$

use (4) $-k_t \left(\frac{T - k_t i}{J} \right) + \frac{L}{R} \ddot{V} + \dot{V} = 0$

use (5) $-k_t \left(\frac{T - k_t (V/R)}{J} \right) + \frac{L}{R} \ddot{V} + \dot{V} = 0$

simplify: $\frac{L}{R} \ddot{V} + \dot{V} + \frac{k_t^2}{RJ} V = \frac{k_t}{J} T$

check units: all terms are in $\frac{\text{kg m}^2}{\text{coulomb s}^2}$ ✓

in the steady state \ddot{V} and \dot{V} are zero


$$\circ \circ \frac{k_t^2}{R J} = \frac{k_t}{J} T \quad \text{from our equation.}$$

$$\frac{k_t}{R} V = T$$

we also know that in the steady state T_g must equal T and e_b must equal V

$$\circ \circ T = T_g = k_t i = k_t \left(\frac{V}{R} \right) = \frac{k_t}{R} V \quad \text{from eqn (4)}$$

this agrees with our derived equation. ✓

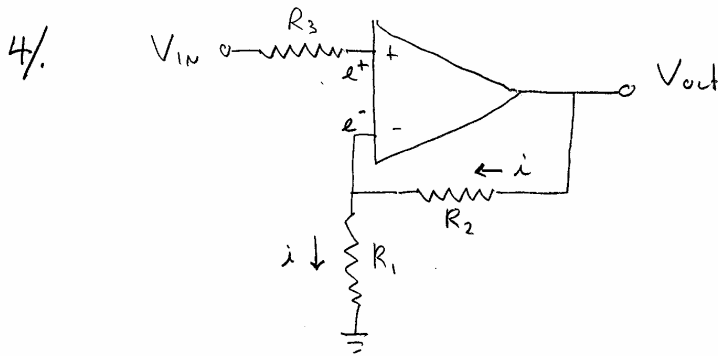

no current through R_3 , $\therefore e^+ = V_{in}$
inputs tend to same voltage $\therefore e^- = e^+ = V_{in}$

$$i = \frac{V_{out}}{R_1 + R_2} = \frac{e^-}{R_1} = \frac{V_{in}}{R_1}$$

$$\circ \circ V_{out} = V_{in} \left(\frac{R_1 + R_2}{R_1} \right)$$

non-inverting amplifier