

2.1

(a)

$x y z$	$x + y + z$	$(x + y + z)'$	x'	y'	z'	$x' y' z'$	$x y z$	$(x y z)$	$(x y z)'$	x'	y'	z'	$x' + y' + z'$
000	0	1	1	1	1	1	000	0	1	1	1	1	1
001	1	0	1	1	0	0	001	0	1	1	1	0	1
010	1	0	1	0	1	0	010	0	1	1	0	1	1
011	1	0	1	0	0	0	011	0	1	1	0	0	1
100	1	0	0	1	1	0	100	0	1	0	1	1	1
101	1	0	0	1	0	0	101	0	1	0	1	0	1
110	1	0	0	0	1	0	110	0	1	0	0	1	1
111	1	0	0	0	0	0	111	1	0	0	0	0	0

(b)

$x y z$	$x + y z$	$(x + y)$	$\{x + z\}$	$\{x + y\}(x + z)$
000	0	0	0	0
001	0	0	1	0
010	0	1	0	0
011	1	1	1	1
100	1	1	1	1
101	1	1	1	1
110	1	1	1	1
111	1	1	1	1

(c)

$x y z$	$x(y + z)$	$x y$	$x z$	$x y + x z$
000	0	0	0	0
001	0	0	0	0
010	0	0	0	0
011	0	0	0	0
100	0	0	0	0
101	1	0	1	1
110	1	1	0	1
111	1	1	1	1

(d)

$x y z$	x	$y + z$	$x + (y + z)$	$\{x + y\}$	$(x + y) + z$
000	0	0	0	0	0
001	0	1	1	0	1
010	0	1	1	1	1
011	0	1	1	1	1
100	1	0	1	1	1
101	1	1	1	1	1
110	1	1	1	1	1
111	1	1	1	1	1

(e)

$x y z$	$y z$	$x(y z)$	$x y$	$(x y) z$
000	0	0	0	0
001	0	0	0	0
010	0	0	0	0
011	1	0	0	0
100	0	0	0	0
101	0	0	0	0
110	0	0	1	0
111	1	1	1	1

2.4

$$(a) \quad A'C' + ABC + AC' = C' + ABC = (C + C')(C' + AB) = AB + C'$$

$$(b) \quad (xy' + z)' + z + xy + wz = (xy')'z' + z + xy + wz = [(x + y)z' + z] + xy + wz = \\ = (z + z')(z + x + y) + xy + wz = z + wz + x + xy + y = z(J + w) + x(J + y) + y = x + y + z$$

$$(c) \quad A'B(D' + C'D) + B(A + A'CD) = B(A'D' + A'C'D + A + A'CD) \\ = B(A'D' + A + A'D(C + C')) = B(A + A'(D' + D)) = B(A + A') = B$$

$$(d) \quad (A' + C)(A' + C')(A + B + C'D) = (A' + CC')(A + B + C'D) = A'(A + B + C'D) \\ = AA' + A'B + A'C'D = A'(B + C'D)$$

$$(e) \quad ABCD + A'BD + ABC'D = ABD + A'BD = BD$$

2.11 **(a)** $F(x, y, z) = (1,$

(b) $F(a, b, c) = (0,$


$$F = xy + xy' + yz$$

$$F = a'c' + bc$$


$x y z$	F
000	0
001	1
010	0
011	0
100	1
101	1
110	1
111	1

$a b c$	F
000	1
001	0
010	1
011	1
100	0
101	0
110	0
111	1


2.14 (a)

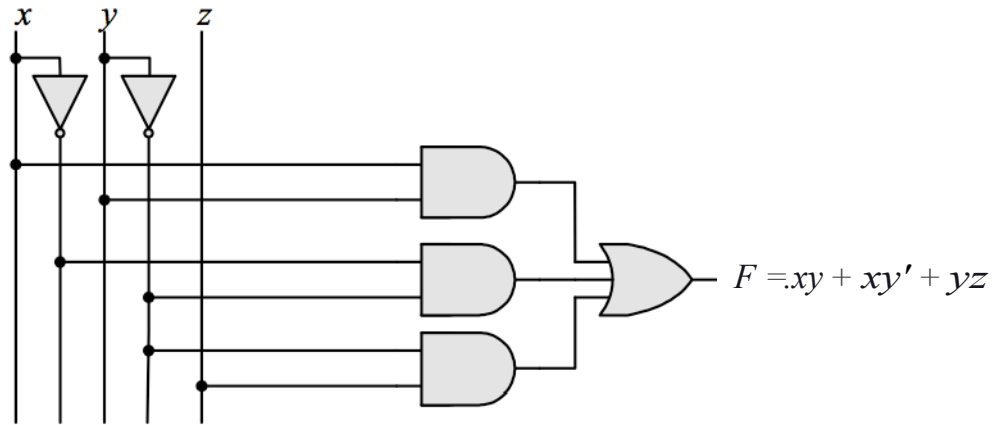


(b)

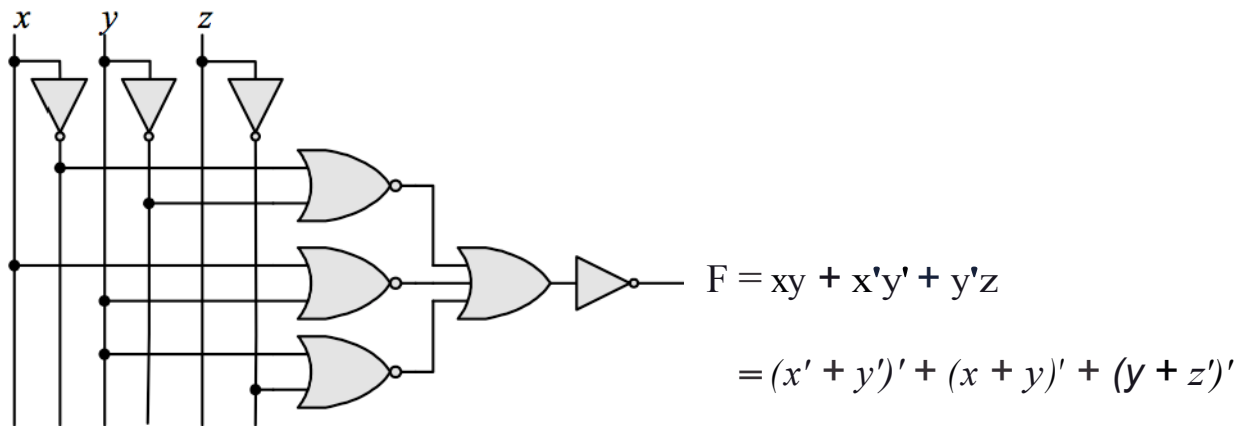

(c)

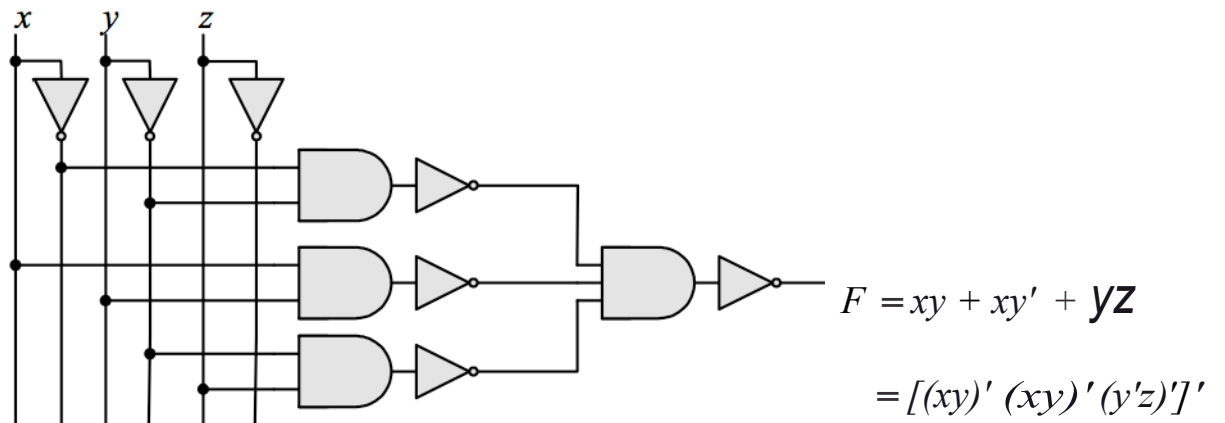


(d)

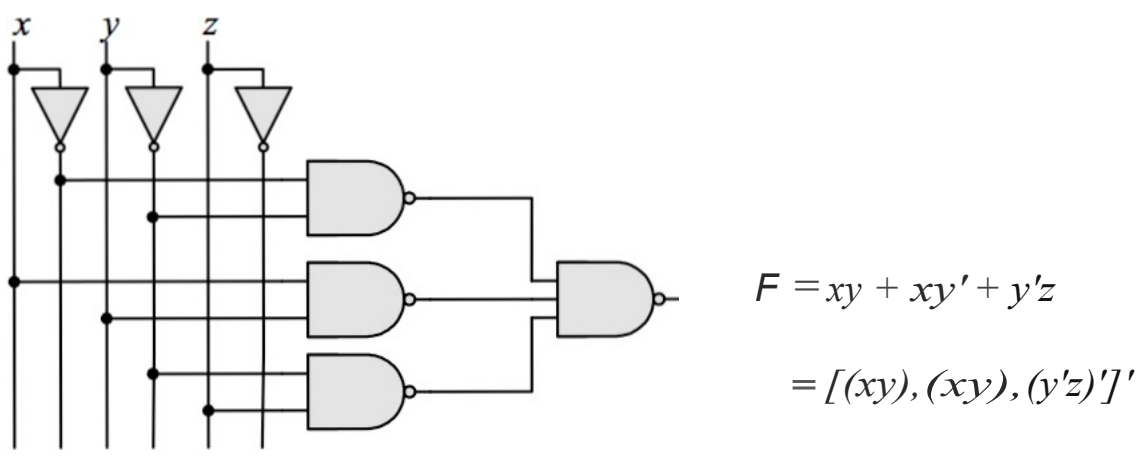

(c) $F = xy'z + xy'z + wX\}' + wxy + wxy = y'z + xy + 11.y = \mathbf{yZ} + y(w + x)$

(d) $F = y'z + yw + yx) = \mathbf{L(1, 5, 9, 13, 10, 11, 13, 15, 6, 7, 14, 15)}$
 $= \mathbf{L(1, 5, 6, 7, 9, 10, 11, 13, 14, 15)}$

(e)

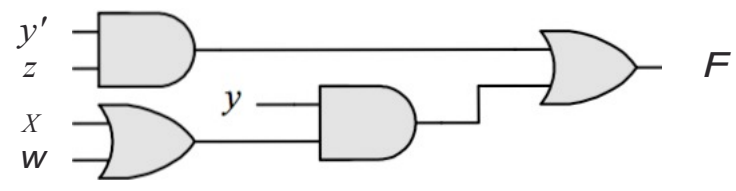

1 – Inverter, 2 – Two-input AND gates, 2 – Two-input OR gates


2.18 (a)

wxyz	F
000 0	0
00 0 1	1
0010	0
00 1 1	0
010 0	0
01 0 1	1
01 1 0	1
01 1 1	1
1000	0
10 0 1	1
10 1 0	1
10 1 1	1
1100	0
11 0 1	1
11 1 0	1
11 1 1	1

$$F = xyz + xyz + wXji + wxy + wxy$$


$$F = L(1, 5, 6, 7, 9, 10, 11, 13, 14, 15)$$

(b)

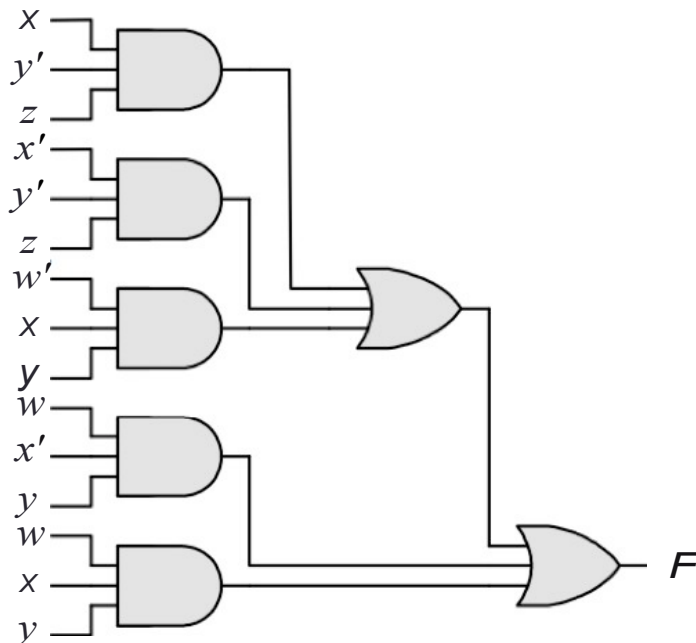


2.7


(a)

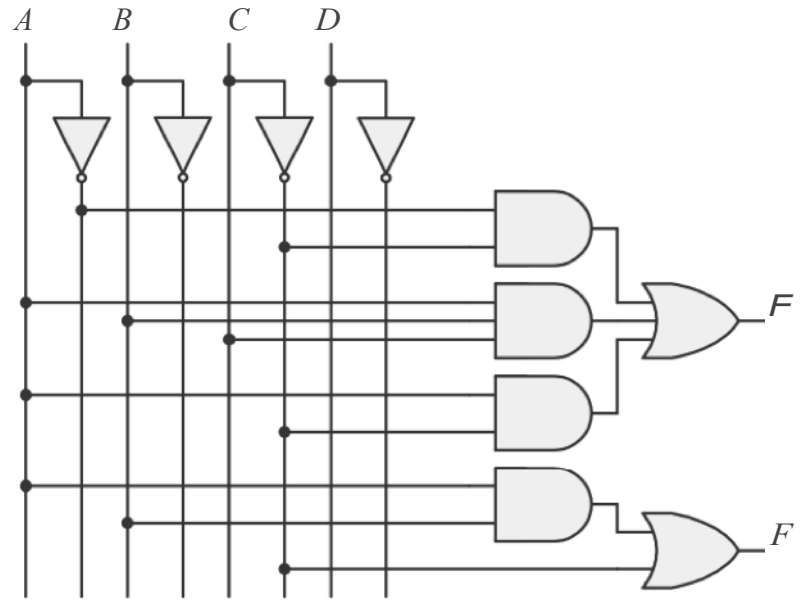


(b)

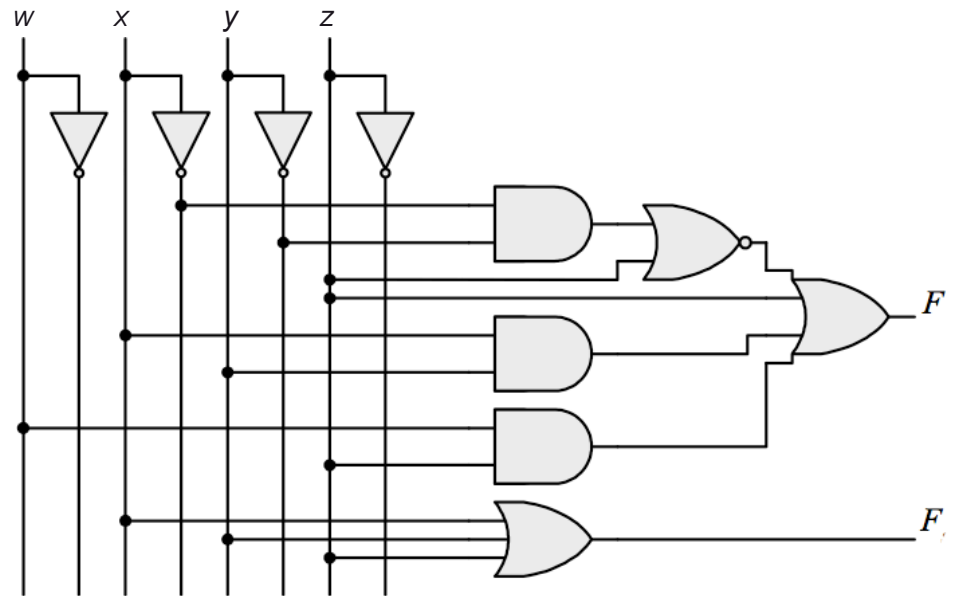

(c)

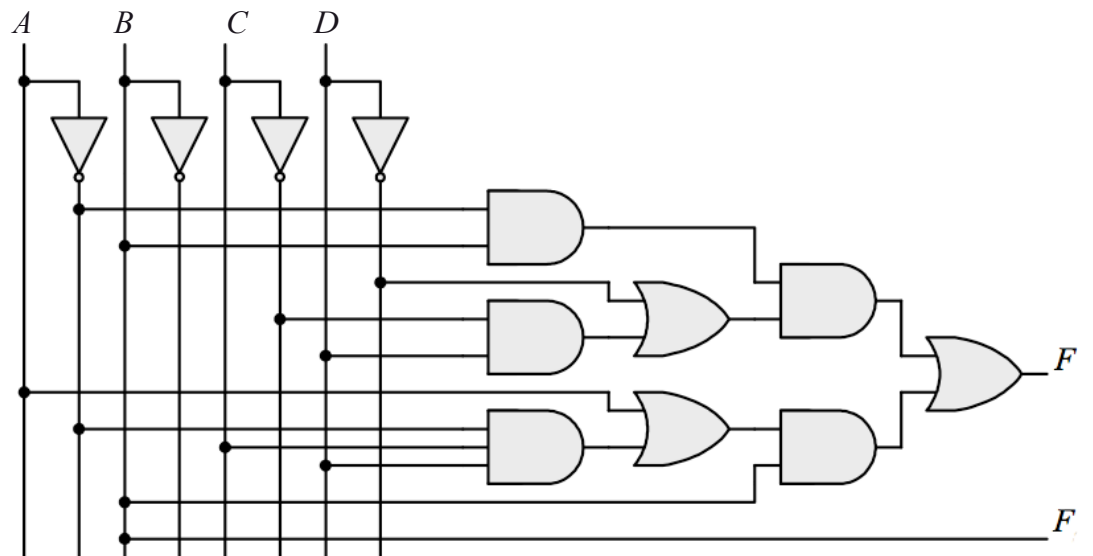

(d)

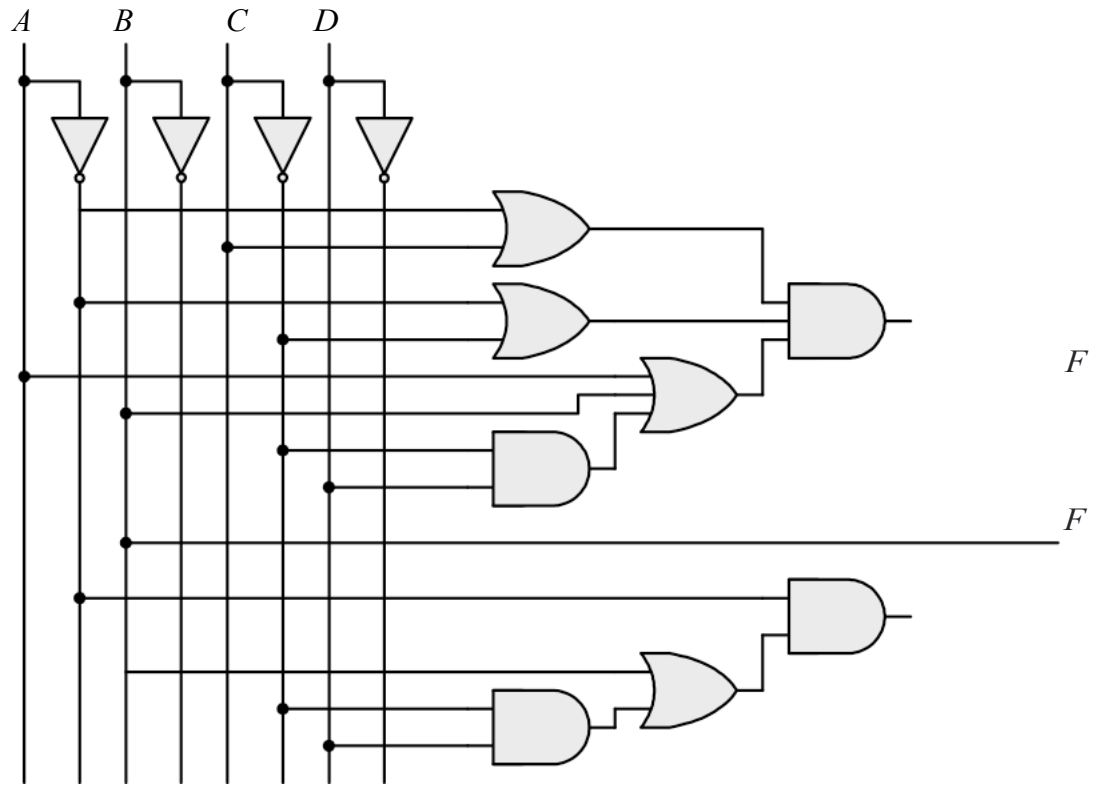

(e)

