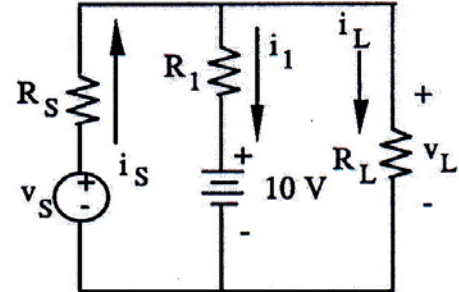


PROBLEM #1

Three cases need to be considered:

- (a) When $V_L > 10 \text{ V}$, D_1 will conduct
- (b) When $V_L < -5 \text{ V}$, D_4 will conduct
- (c) When $-5 \text{ V} < V_L < 10 \text{ V}$, all 4 diodes will be cut off.

For case (a), the circuit is shown on the right.




By KCL, $i_S = i_1 + i_L$, and

$$\frac{V_S - V_L}{10} = \frac{V_L - 10}{1} + \frac{V_L}{40}$$

Therefore, $V_L = \frac{4V_S + 400}{45} \text{ V}$

$$V_S > 12.5 \text{ V}$$

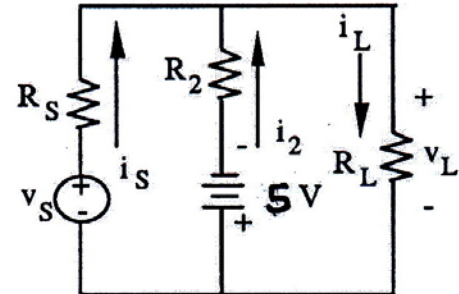For case (b), the circuit is shown on the right.



By KCL, $i_S + i_2 = i_L$, and

$$\frac{V_S - V_L}{10} + \frac{-5 - V_L}{10} = \frac{V_L}{40}$$


Therefore, $V_L = \frac{4V_S - 20}{9} \text{ V}$

$$V_S < -6.25 \text{ V}$$


For case (c), we have $V_L = \frac{4}{5}V_S$ and

$$-6.25 \text{ V} < V_S < 12.5 \text{ V}$$

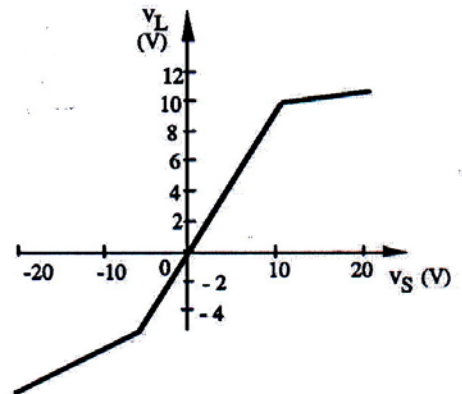The v_L - v_S curve is shown on the right:



PROBLEM #2

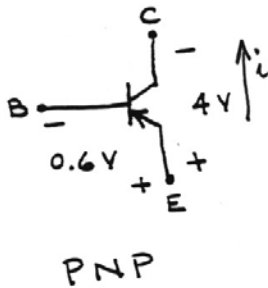

a) $V_{BE} = -0.6V$
the EB junction is forward biased.




$$V_{CE} = V_{BE} + V_{CB}$$


$$-4 = -0.6 + V_{CB}$$

$$\therefore V_{CB} = -3.4V$$

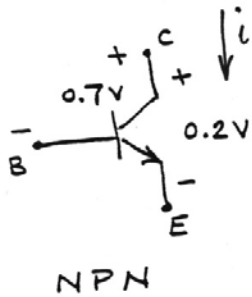
The CB junction is reverse biased.
 \therefore the transistor is in the active region



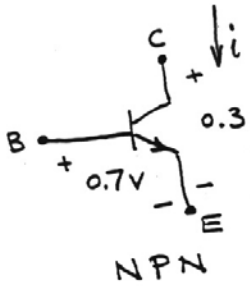b) $V_{CB} = 0.7V$
the BC junction is reverse biased.
 $V_{CE} = V_{BE} + V_{CB}$
 $0.2 = V_{BE} + 0.7 \therefore V_{BE} = -0.5V$
 \therefore the BE junction is reverse biased.
 \therefore the transistor is in the cut-off region



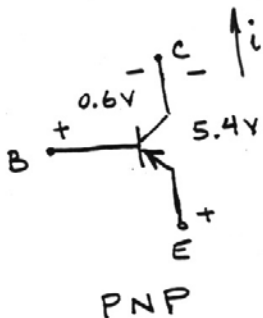c) $V_{BE} = 0.7V$
the BE junction is forward biased.
 $V_{CE} = V_{BE} + V_{CB}$
 $0.3 = 0.7 + V_{CB} \therefore V_{CB} = -0.4V$
 \therefore the BC junction is forward biased.
 \therefore the transistor is in the saturation region



d) $V_{CB} = -0.6V$
the CB junction is reverse biased.
 $V_{CE} = V_{BE} + V_{CB}$
 $-5.4 = V_{BE} - 0.6 \therefore V_{BE} = -4.8V$
 \therefore the EB junction is forward biased.
 \therefore the transistor is in the active region.

PROBLEM #3

a) If all the input voltages are high at 5V, no current can flow from the base of Q_1 to the emitter of Q_1 .

But the current from the base of Q_1 can flow through the collector of Q_1 , which is the same as the base current of Q_2 .

If Q_2 is assumed saturated ON, then the base plus collector current (equal to emitter current) of Q_2 flows through the $1k\Omega$ resistor. If Q_3 is assumed saturated ON, then some of this current flows through the base of Q_3 to the emitter of Q_3 .

Also, since Q_2 is saturated ON, all the collector current from the 5V source through the $1.6k\Omega$ resistor flows through the CE of Q_2 and there is insufficient current to turn ON Q_4 , which is therefore OFF.

Thus, $Q_2 =$ saturated ON
 $Q_3 =$ saturated ON
 $Q_4 =$ cut-off OFF

$$V_{B3} = 0.6V$$

$$V_{B2} = V_{BE2} + V_{B3} = 0.6 + 0.6 = 1.2V$$

$$V_{B1} = V_{BC1} + V_{BE2} + V_{B3} = 0.6 + 0.6 + 0.6 = 1.8V$$

$$V_{C2} = V_{CE2} + V_{B3} = 0.2 + 0.6 = 0.8V$$

$$V_{out} = V_{CE3} = 0.2V$$

b) If $V_B = 0V$ then current from the 5V source flows through the $4k\Omega$ resistor, through the base of Q_1 to the emitter of Q_1 , and therefore Q_1 is saturated ON.

$$\begin{aligned}\text{Thus, } Q_1 &= \text{saturated ON} \\ V_{B1} &= V_{BE1} = 0.6V \\ V_{B2} &= V_{CE1} = 0.2V\end{aligned}$$

There is insufficient current from Q_1 to the base of Q_2 , and therefore Q_2 is OFF. Since there is no Q_2 emitter current, therefore Q_3 is OFF.

$$\begin{aligned}Q_2 &= \text{cut-off OFF} \\ Q_3 &= \text{cut-off OFF} \\ V_{B3} &\approx 0V \text{ (small voltage due to leakage } I_{CEO}\text{)}\end{aligned}$$

If Q_2 is OFF, then the current from the 5V source through the $1.6k\Omega$ resistor turns Q_4 ON.

Thus, since Q_4 is ON,

$$5 - i_{c4} (150 \times 10^3) - V_{CE4} - V_{D1} = V_{out}$$

$$5 - i_{B4} (1.6 \times 10^3) - V_{BE4} - V_{D1} = V_{out}$$

$$5 - i_{c4} (150 \times 10^3) - 0.2 - 0.6 = V_{out}$$

$$5 - i_{B4} (1.6 \times 10^3) - 0.6 - 0.6 = V_{out}$$

$$i_{c4} = \beta i_{B4} = 5 i_{B4} \quad (\text{assume saturated } \beta = 5)$$

$$4.2 - i_{B4} (750 \times 10^3) = V_{out}$$

$$3.8 - i_{B4} (1.6 \times 10^3) = V_{out}$$

$$0.4 = i_{B4} (748.4 \times 10^3)$$

$$\therefore i_{B4} = 0.534 \mu A$$

$$i_{c4} = 2.67 \mu A$$

$$V_{out} = 3.8 V$$

$$V_{c2} \approx V_{BE4} + V_{D1} + V_{out}$$

$$= 0.6 + 0.6 + 3.8$$

$$\approx 5.0 V$$