

MECH 368 – ELECTRONICS FOR MECHANICAL ENGINEERS

ASSIGNMENT #1

(3.42, 3.43, 3.46, 3.67, 3.68, 3.69) - F

**Problem 3.42**

**Solution:**

Known quantities:

The values of the voltage sources and of the resistors in the circuit of Figure P3.42:

$$V_{S1} = V_{S2} = 12 \text{ V}$$

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

Find:

The voltage across  $R_2$ .

Analysis:

Specify the polarity of the voltage across  $R_2$ . Suppress the voltage source  $V_{S1}$  by replacing it with a short circuit. Redraw the circuit.

$$R_{eq} = R_1 \parallel R_3 = \frac{1}{2} \text{ k}\Omega = 0.5 \text{ k}\Omega$$


$$V_{R2-2} = V_{S2} \frac{R_2}{R_2 + R_{eq}} = \frac{(12)(1000)}{1000 + 500} = 8 \text{ V}$$

Suppress the voltage source  $V_{S2}$  by replacing it with a short circuit. Redraw the circuit.

$$R_{eq} = R_2 \parallel R_3 = \frac{1}{2} \text{ k}\Omega = 0.5 \text{ k}\Omega$$

$$V_{R2-1} = -V_{S1} \frac{R_{eq}}{R_1 + R_{eq}} = \frac{(12 \text{ V})(0.5 \text{ k}\Omega)}{1 \text{ k}\Omega + 0.5 \text{ k}\Omega} = -4 \text{ V}$$
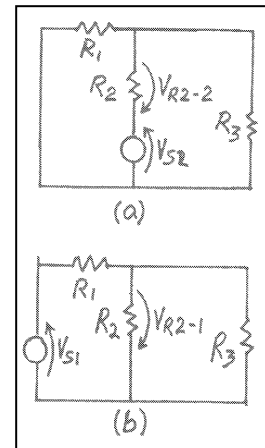
$$V_{R2} = V_{R2-1} + V_{R2-2} = -4 \text{ V} + 8 \text{ V} = 4 \text{ V}$$



**Note: Superposition must be used when the sources in a circuit are AC sources with different frequencies, or where some sources are DC and others are AC.**

### Problem 3.43

#### **Solution:**

Known quantities:

The values of the voltage sources and of the resistors in the circuit of Figure P3.43:

$$V_{S1} = V_{S2} = 450 \text{ V}$$

$$R_1 = 7 \Omega \quad R_2 = 5 \Omega \quad R_3 = 10 \Omega \quad R_4 = R_5 = 1 \Omega$$

Find:

The component of the current through  $R_3$  that is due to  $V_{S2}$ , using superposition.

Analysis:

Suppress  $V_{S1}$  by replacing it with a short circuit. Redraw the circuit.

$R_1$  and  $R_4$  are in parallel:

$$R_{14} = \frac{R_1 R_4}{R_1 + R_4} = \frac{(7)(1)}{7+1} = 0.875 \Omega$$

$R_{14}$  is in series with  $R_3$ :

$$R_{143} = R_{14} + R_3 = 0.875 + 10 = 10.875 \Omega$$

$$R_{eq} = R_5 + (R_2 \parallel R_{143}) = R_5 + \frac{R_2 R_{143}}{R_2 + R_{143}} = 1 + \frac{(5)(10.875)}{5+10.875} = 4.425 \Omega$$

$$OL: \quad I_S = \frac{V_{S2}}{R_{eq}} = \frac{450}{4.425} = 101.695 \text{ A}$$

$$CD: \quad I_{R3-2} = \frac{I_S R_2}{R_2 + R_{143}} = \frac{(101.695)(5)}{5+10.875} = 32.03 \text{ A}$$

### Problem 3.46

**Solution:**

**Known quantities:**

The values of the resistors, of the voltage source and of the current source in the circuit

**Find:**

The current through the voltage source using superposition.

**Analysis:**

(1) Suppress voltage source  $V$ . Redraw the circuit.

For mesh (a):  $i_a = 0$

For mesh (b):  $i_b(200 + 75 + 25) + i_c(-25) - 40 = 0$

For mesh (c):  $i_b(-25) + i_c(25 + 100) = 0$

Solving,

$i_b = 136 \text{ mA}$  and  $i_c = 27 \text{ mA}$ .

Therefore,  $i_1 = i_c = 27 \text{ mA}$ .

(2) Suppress current source  $I$ . Redraw the circuit.

For mesh (a):  $i_a(50) - 10 = 0$

For mesh (b):  $i_b(200 + 75 + 25) + i_c(-25) = 0$

For mesh (c):  $i_b(-25) + i_c(25 + 100) = -10$



Solving,

$i_a = 200 \text{ mA}$ ,  $i_b = -6.8 \text{ mA}$  and  $i_c = -81 \text{ mA}$ .

Therefore,

$i_2 = i_c - i_a = -281 \text{ mA}$ .

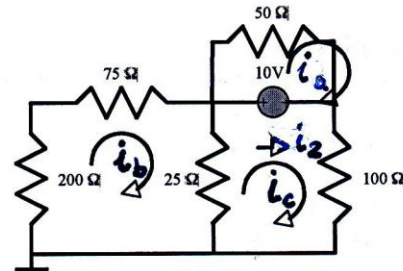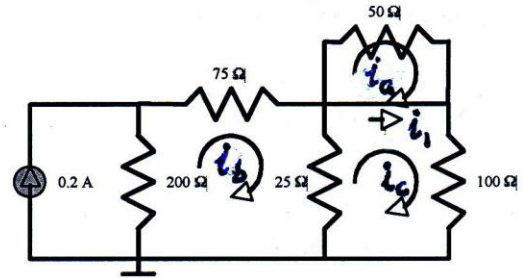Using the principle of superposition,  $i = i_1 + i_2 = -254 \text{ mA}$



### Problem 3.67


#### Solution:

##### Known quantities:

The schematic of the circuit (see Figure P3.26).
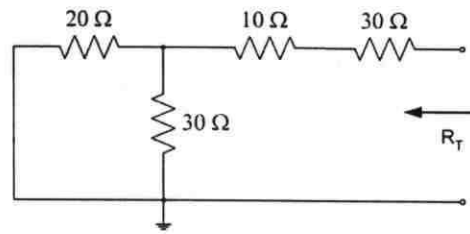
##### Find:

The Thévenin equivalent resistance seen by resistor  $R_s$ , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when  $R_s$  is the load.



##### Analysis:

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = 30 \Omega + 10 \Omega + (20 \Omega \parallel 30 \Omega) = 52 \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

For node #1:

$$\frac{v_1 - 3}{20} + \frac{v_1}{30} + \frac{v_1 - v_2}{10} = 0$$

For node #2:

$$\frac{v_2 - v_1}{10} = 0.5$$

Solving the system,

$$v_1 = 7.8 \text{ V and } v_2 = 12.8 \text{ V .}$$

Therefore,

$$v_{OC} = v_2 = 12.8 \text{ V .}$$

(3) Replace the load with a short circuit. Redraw the circuit.

For mesh (a):

$$i_a(20 + 30) - i_b(30) = 3$$

For meshes (b) and (c):

$$-i_a(30) + i_b(30 + 10) + i_c(30) = 0$$

For the current source:



$$i_c - i_b = 0.5$$

Solving the system,

$$i_a = -92 \text{ mA , } i_b = -254 \text{ mA and } i_c = 246 \text{ mA .}$$

Therefore,

$$i_{SC} = i_c = 246 \text{ mA .}$$

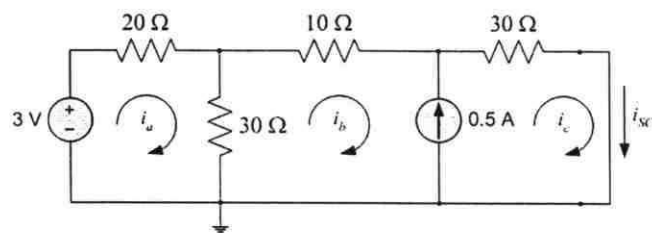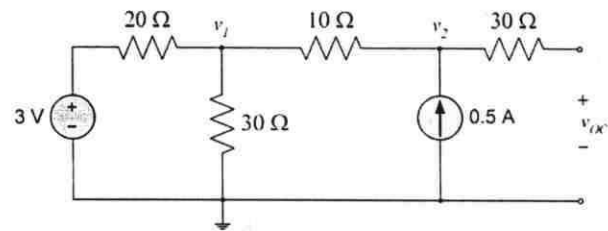

## Problem 3.68

### Solution:

#### Known quantities:

The schematic of the circuit (see Figure P3.41).

#### Find:

The Thévenin equivalent resistance seen by resistor  $R$ , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when  $R$  is the load.

#### Analysis:

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = 1 \Omega \parallel 0.3 \Omega = 0.23 \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

$$\text{For node \#1: } \frac{v_1}{1} + \frac{v_1 - 12}{0.3} = 12$$

Solving,

$$v_1 = 12 \text{ V.}$$

Therefore,

$$v_{OC} = v_1 = 12 \text{ V.}$$

(3) Replace the load with a short circuit. Redraw the circuit.

$$\text{For mesh (a): } i_a(1 + 0.3) - i_b(0.3) - 12(1) + 12 = 0$$




$$\text{For mesh (b): } -i_a(0.3) + i_b(0.3) = 12$$

Solving the system,

$$i_a = 12 \text{ A and } i_b = 52 \text{ A.}$$

Therefore,

$$i_{SC} = i_b = 52 \text{ A.}$$

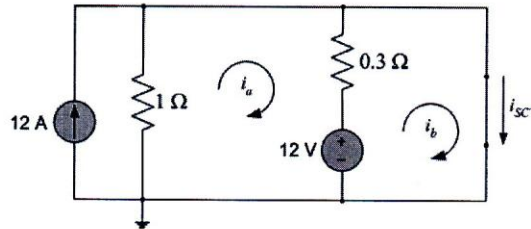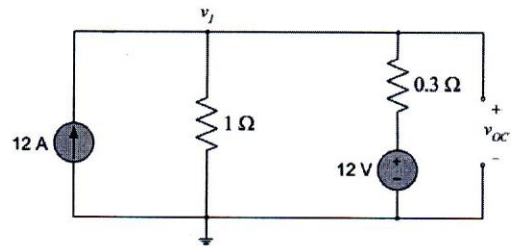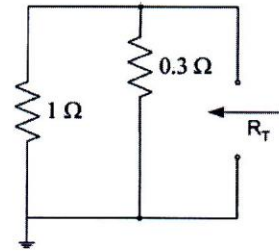

### Problem 3.69


**Solution:**

**Known quantities:**

The schematic of the circuit (see Figure P3.43).

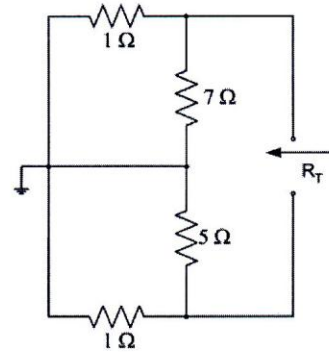**Find:**

The Thévenin equivalent resistance seen by resistor  $R_3$ , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when  $R_3$  is the load.



**Analysis:**

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = 1 \Omega \parallel 7 \Omega + 1 \Omega \parallel 5 \Omega = 1.71 \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

For node #1:  $\frac{v_1 - 450}{1} + \frac{v_1}{7} = 0$

For node #2:  $\frac{v_2 + 450}{1} + \frac{v_2}{5} = 0$

Solving the system,

$$v_1 = 393.75 \text{ V and } v_2 = -375 \text{ V.}$$

Therefore,

$$v_{OC} = v_1 - v_2 = 768.75 \text{ V.}$$

(3) Replace the load with a short circuit. Redraw the circuit.

For mesh (a):

$$i_a(1 + 7) - i_c(7) = 450$$

For mesh (b):

$$i_b(5 + 1) - i_c(5) = 450$$

For mesh (c):

$$-i_a(7) - i_b(5) + i_c(7 + 5) = 0$$

Solving the system,

$$i_a = 450 \text{ A, } i_b = 450 \text{ A and } i_c = 450 \text{ A.}$$

Therefore,

$$i_{SC} = i_c = 450 \text{ A.}$$

