

MECH 368 – ELECTRONICS FOR MECHANICAL ENGINEERS

ASSIGNMENT #4 (10.2, 10.3, 10.5, 10.6, 10.32)

Problem 10.2

Solution:

Known quantities:

Transistor type and operating characteristics:

- (a) npn, $V_{BE} = 0.8 \text{ V}$ and $V_{CE} = 0.4 \text{ V}$
- (b) npn, $V_{CB} = 1.4 \text{ V}$ and $V_{CE} = 2.1 \text{ V}$
- (c) pnp, $V_{CB} = 0.9 \text{ V}$ and $V_{CE} = 0.4 \text{ V}$
- (d) npn, $V_{BE} = -1.2 \text{ V}$ and $V_{CB} = 0.6 \text{ V}$

Find: The region of operation for each transistor.

Analysis:

- (a) Since $V_{BE} = 0.8 \text{ V}$, the BE junction is forward-biased. $V_{CB} = V_{CE} + V_{EB} = -0.4 \text{ V}$. Thus, the CB junction is forward-biased. Therefore, the transistor is in the saturation region.
- (b) $V_{BE} = V_{BC} + V_{CE} = 0.7 \text{ V}$. The BE junction is forward-biased. $V_{CB} = 1.4 \text{ V}$. The CB junction is reverse-biased. Therefore, the transistor is in the active region.
- (c) $V_{CB} = 0.9 \text{ V}$ for a pnp transistor implies that the CB junction is forward-biased. $V_{BE} = V_{BC} - V_{CE} = -1.3 \text{ V}$. The BE junction is forward-biased. Therefore, the transistor is in the saturation region.
- (d) With $V_{BE} = -1.2 \text{ V}$, the BE junction is reverse-biased. $V_{CB} = -0.6 \text{ V}$. The CB junction is reverse-biased. Therefore, the transistor is in the cutoff region.

Problem 10.3

Solution:

Known quantities: The circuit of Figure P10.3. $\beta = \frac{I_C}{I_B} = 100$.

Find:

The operating point and the state of the transistor.

Analysis:

$V_{BE} = 0.6 \text{ V}$ and the BE junction is forward biased.

$$I_B = \frac{V_{CC} - V_{BE}}{R_1 + (\beta + 1)R_E} = \frac{12 - 0.6}{820 + (101)(0.910)} = 12.5 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 1.25 \text{ mA}$$

Writing KVL around the right-hand side of the circuit:

$$\begin{aligned} -V_{CC} + I_C R_C + V_{CE} + I_E R_E &= 0 & \Rightarrow & \quad V_{CE} = V_{CC} - I_C R_C - (I_B + I_C) R_E \\ & & & \quad = 12 - (1.25)(2.2) - (0.0125 + 1.25)(0.910) \\ & & & \quad = 8.10 \text{ V} \end{aligned}$$

$$V_{CB} = V_{CE} - V_{BE} = 8.10 - 0.6 = 7.50 \text{ V}$$

Since the BE junction is forward biased and the BC junction is reverse biased, and also (extra information)

$V_{CE} > V_{BE} \Rightarrow$ The transistor is in the active region.

Problem 10.5

Solution:

Known quantities:

The circuit of Figure P10.5, assuming the BJT has $V_\gamma = 0.6\text{ V}$.

Find:

The emitter current and the collector-base voltage.

Analysis: **NOTE: The voltage source on the right of the circuit should be of opposite polarity.**

Applying KVL to the right-hand side of the circuit, $I_E = \left(\frac{15 - V_{BE}}{30000} \right) = \frac{15 - 0.6}{30000} = 520\ \mu\text{A}$

Then, on the left-hand side, assuming $\beta \gg 1$:

$$\begin{aligned} V_{CB} &= 10 - I_C \cdot R_C \\ -10 + I_C R_C + V_{CB} &= 0 \quad \Rightarrow \quad = 10 - (-520) \cdot (15) \cdot 10^{-3} \\ &= 17.8\text{ V} \end{aligned}$$

Problem 10.6

Solution:

Known quantities:

The circuit of Figure P10.6, assuming the BJT has $V_\gamma = 0.6\text{ V}$ and $\beta = \frac{I_C}{I_B} = 150$.

Find:

The operating point and the state of the transistor.

Analysis:

First, determine the Thévenin equivalent of the circuit connected to the base:

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{15}{62 + 15} \cdot 18 = 3.506\text{ V}$$

$$R_{BB} = R_1 \parallel R_2 = \frac{62 \cdot 15}{62 + 15} = 12.08\text{ k}\Omega$$

Then, applying KVL to the left-hand side of the circuit, we have: $-V_{BB} + I_B R_{BB} + V_{BE} + I_E R_E = 0$

But $I_E = (\beta + 1) \cdot I_B$, so the last equation becomes:

$$V_{BB} = I_B R_{BB} + V_{BE} + (\beta + 1) I_B R_E \quad \Rightarrow \quad V_{BB} - V_{BE} = I_B [R_{BB} + (\beta + 1) R_E]$$

$$I_B = \frac{V_{BB} - V_{BE}}{[R_{BB} + (\beta + 1) \cdot R_E]} = \frac{3.506 - 0.600}{12080 + 151 \cdot 1200} = 15.04\ \mu\text{A}$$

$$I_C = \beta \cdot I_B = 2.256\text{ mA}$$

Applying KVL to the right-hand side,

$$V_{CE} = V_{CC} - \beta \cdot I_B R_C - (\beta + 1) \cdot I_B R_E$$

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0 \quad \Rightarrow \quad = 18 - 150 \cdot 15.04 \cdot 3.3 \cdot 10^{-3} - 151 \cdot 15.04 \cdot 1.2 \cdot 10^{-3}$$

$$= 7.83 \text{ V}$$

Therefore, $I_{BQ} = 15.04 \mu\text{A}$, $I_{CQ} = 2.256 \text{ mA}$ and $V_{CEQ} = 7.83 \text{ V}$.

The transistor is in the active linear region.

Problem 10.32

Solution:

Known quantities: For the circuit shown in Figure P10.32:

$$V_{CC} = 12 \text{ V} \quad \beta = 130 \quad R_1 = 82 \text{ k}\Omega \quad R_2 = 22 \text{ k}\Omega \quad R_E = 0.5 \text{ k}\Omega \quad R_L = 16 \Omega.$$

Find:

V_{CEQ} at the DC operating point.

Analysis:

Simplify the circuit by obtaining the Thévenin equivalent of the biasing network (R_1 , R_2 , V_{CC}) in the base circuit:

$$V_D: V_{BB} = V_{TH} = V_{OC} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{12 \cdot 22}{82 + 22} = 2.538 \text{ V}$$

$$\text{Suppress } V_{CC}: R_B = R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{82 \cdot 22}{82 + 22} = 17.35 \text{ k}\Omega$$

Redraw the circuit using the Thévenin equivalent. The "DC blocking" or "AC coupling" capacitors act as open circuits for DC; therefore, the signal source and load can be neglected since this is a DC problem. Specify directions of current and polarities of voltages.

Assume the transistor is operating in its active region. Then, the base-emitter junction is forward biased.

$$V_{BEQ} \approx 700 \text{ mV [Si]} \quad I_{EQ} = [\beta + 1] I_{BQ}$$

$$\text{KVL: } -V_{BB} + I_{BQ} R_B + V_{BEQ} + I_{EQ} R_E = 0$$

$$-V_{BB} + I_{BQ} R_B + V_{BEQ} + [\beta + 1] I_{BQ} R_E = 0$$

$$I_{BQ} = \frac{V_{BB} - V_{BEQ}}{R_B + (\beta + 1) R_E} = \frac{2.538 - 0.7}{17350 + (130 + 1) \cdot 500} = 22.18 \mu\text{A}$$

$$I_{EQ} = (\beta + 1) I_{BQ} = (130 + 1) \cdot 22.18 \cdot 10^{-6} = 2.906 \text{ mA}$$

$$\text{KVL: } -I_{EQ} R_E - V_{CEQ} + V_{CC} = 0$$

$$V_{CEQ} = V_{CC} - I_{EQ} R_E = 12 - 2.906 \cdot 0.5 = 10.55 \text{ V}$$

The collector-emitter voltage is greater than its saturation value (0.3 V for Silicon). Therefore the initial assumption (operation in the active region) was correct and the solution is valid.

