




Digital Logic Design: Principles and Practices
ELG5195 (EACJ5705), Carleton CRN: 18371
Assignment #2


Q1. Implement $f(A,B,C,D) = \Sigma(1,4,5,7,9,12,13)$ using a MUX(8x1) where A, C, and D are connected to the multiplexor's select inputs.

	A	B	C	D	f
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

	A	C	D	B	f	
0	0	0	0	0	0	B
1	0	0	1	0	1	1
2	0	1	0	0	0	0
3	0	1	1	1	1	B
4	1	0	0	0	0	B
5	1	0	1	0	1	1
6	1	1	0	0	0	0
7	1	1	1	0	0	0

 

 Q2. A sequential circuit has two JK flip-flops A and B, one input X and one output Z. The circuit logic diagram is shown below. Derive the circuit State Table as well as the State diagram.



$$JA = B, KA = B'$$

$$JB = KB = (A \oplus X)' = AX + A'X'$$

$$Y = (A \oplus X) \oplus B$$

A_{t+1} and B_{t+1} can be derived using the JK characteristic equations.

$$\text{Ex., } A_{t+1} = A_t K_A' + A_t' J_A = A_t (B')' + A_t' (B) = A_t (B) + A_t' (B) = (A_t + A_t') B = B$$

You can also use the characteristic table instead of the equation:


J	K	Q_{t+1}
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

A	B	X	JA	KA	A_{t+1}	JB	KB	B_{t+1}
0	0	0	0	1	0	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	1	0	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	0	1	1	1
1	1	0	1	0	1	0	0	1
1	1	1	1	0	1	1	1	0

State Table:


Present State	In	Next State	Out
A B	X	$A_{t+1} B_{t+1}$	Y
0 0	0	0 1	0
0 0	1	0 0	1
0 1	0	1 0	1
0 1	1	1 1	0
1 0	0	0 0	1
1 0	1	0 1	0
1 1	0	1 1	0
1 1	1	1 0	1

State Diagram

 

Q3. Using *D flip-flops*, design and implement (devise the logic diagram) the sequential circuit specified by the following state table:

Present State	In	Next State	Out
A B	X	$A^{n+1} B^{n+1}$	Z
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 0	0
0 1	1	1 1	0
1 0	0	0 0	0
1 0	1	0 1	1
1 1	0	1 0	0
1 1	1	1 1	0

 

Q4. Using *JK flip-flops*, design and implement (devise the logic diagram) the sequential circuit specified by the following transition table:

Present State		Input	Next State		FF's Inputs (Excitations)			
A	B	X	A ⁺	B ⁺	JA	KA	JB	KB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

JA

BX	00	01	11	10
A				
0	0	0	0	1
1	X	X	X	X

JA = BX'

KA

BX	00	01	11	10
A				
0	X	X	X	X
1	0	0	1	0

KA = BX

JB


BX	00	01	11	10
A				
0	0	1	X	X
1	0	1	X	X

JB = X

KB

BX	00	01	11	10
A				
0	X	X	0	1
1	X	X	1	0

KB = A'B + AX

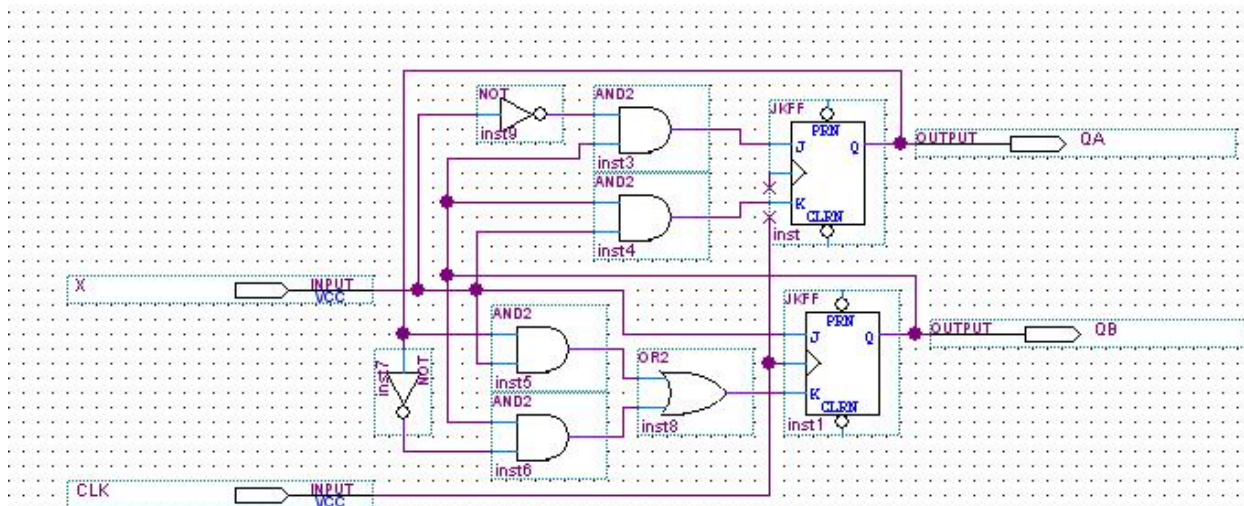

Q5. Design of a vending machine


Design and draw the logical diagram of a vending machine for pop drinks. Each can cost 15 cents. Only coins of 5 cents and of 10 cents are accepted. The circuit has two inputs X_1X_0 , and two outputs Y_1Y_0 . The behaviour of the circuit is described below:

X_1X_0 Description

- 0 0 No money is deposited in the machine
- 0 1 1 nickel is deposited in the machine
- 1 0 1 dime is deposited in the machine

- $Y_1 = 1 \Rightarrow$ Dispense a can
- $Y_0 = 1 \Rightarrow$ Give change a nickel

 1. Assuming that the machine starts from state 00, complete the state diagram of the sequential circuit given in the following figure:



2. Derive the state table ...

Next state S^{n+1} / Output = $Q_1^+ Q_0^+ / Y_1 Y_0$

$X_1 X_0$	0 0	0 1	1 1	1 0
$Q_1 Q_0$	0 0 / 0 0	0 1 / 0 0	x x / x x	1 0 / 0 0
0 1	0 1 / 0 0	1 0 / 0 0	x x / x x	0 0 / 1 0
1 1	x x / x x	x x / x x	x x / x x	x x / x x
1 0	1 0 / 0 0	0 0 / 1 0	x x / x x	0 0 / 1 1

Present state S^n				Next state S^{n+1} / Output			
Q_1	Q_0	X_1	X_0	Q_1^+	Q_0^+	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0
0	0	1	0	1	0	0	0
0	0	1	1	x	x	x	x
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	0	0	1	0
0	1	1	1	x	x	x	x
1	0	0	0	1	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	1	1
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

... and then the excitation table, given that JK flip-flops are used for the state register of this sequential circuit.

Present state S^n				Next state S^{n+1} / Output				Q_1 input		Q_0 input	
Q_1	Q_0	X_1	X_0	Q_1^+	Q_0^+	Y_1	Y_0	J_1	K_1	J_0	K_0
0	0	0	0	0	0	0	0	0	x	0	x
0	0	0	1	0	1	0	0	0	x	1	x
0	0	1	0	1	0	0	0	1	x	0	x
0	0	1	1	x	x	x	x	x	x	x	x
0	1	0	0	0	1	0	0	0	x	x	0
0	1	0	1	1	0	0	0	1	x	x	1
0	1	1	0	0	0	1	0	0	x	x	1
0	1	1	1	x	x	x	x	x	x	x	x
1	0	0	0	1	0	0	0	x	0	0	x
1	0	0	1	0	0	1	0	x	<u>1</u>	0	x
1	0	1	0	0	0	1	1	x	<u>1</u>	0	x
1	0	1	1	x	x	x	x	x	<u>x</u>	x	x
1	1	0	0	x	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x	x

3. Derive the simplified excitation equations of the JK flip-flops ...

$$Q_1^+ = Q_0 X_0 + Q_1' Q_0' X_1 + Q_1 X_1' X_0'$$

$X_1 X_0$	00	01	11	10
00	0	0	x	1
01	0	1	x	0
11	x	x	x	x
10	1	0	x	0

$$J_1 = Q_0 X_0 + Q_0' X_1$$

$X_1 X_0$	00	01	11	10
00	0	0	x	1
01	0	1	x	0
11	x	x	x	x
10	x	x	x	x

$$K_1 = X_1 + X_0$$

$X_1 X_0$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	1	x	1

$$Q_0^+ = Q_1' Q_0' X_0 + Q_0 X_1' X_0'$$

$X_1 X_0$	00	01	11	10
00	0	1	x	0
01	1	0	x	0
11	x	x	x	x
10	0	0	x	0

$$J_0 = Q_0' X_0$$

$X_1 X_0$	00	01	11	10
00	0	1	x	0
01	x	x	x	x
11	x	x	x	x
10	0	0	x	0

$$K_0 = X_1 + X_0$$

$X_1 X_0$	00	01	11	10
00	x	x	x	x
01	0	1	x	1
11	x	x	x	x
10	x	x	x	x

4. Draw the logic diagram of the circuit, using only NAND gates and JK flip flops.


... and the output equations.

$$Y_1 = Q_0 X_1 + Q_1 X_0 + Q_1 X_1$$


$X_1 X_0$	00	01	11	10
00	0	0	x	0
01	0	0	x	1
11	x	x	x	x
10	0	1	x	1

$$Y_0 = Q_1 X_1$$

$X_1 X_0$	00	01	11	10
00	0	0	x	0
01	0	0	x	0
11	x	x	x	x
10	0	0	x	1

 

 2. Represent the compatible state pairs on a merger diagram and find all classes of maximal compatibility. Find all minimal closed sets of compatible classes that cover the original FSM.



3. Use these set(s) to devise a reduced table that is compatible with the original FSM.

Pr. St.	Next state/output	Next state/output			
		00	01	10	11
P	A	D/-	C/0	A/-	-/1
	D	-/-	-/-	H/0	G/1
	H	I/0	E/0	I/0	-/-
	I	H/0	-/-	-/-	G/1
Q	B	G/OH/0	-/-	D/1	
	K	-/-	D/0	F/0	H/1
R	C	K/-	J/1	-/-	A/0
	E	B/1	F/1	-/-	D/0
S	F	D/1	B/0	-/-	I/1
	J	I/1	-/-	K/0	H/1
G	G	K/1	D/1	G/-	C/-

Pr. St.	Next state/output xy			
	00	01	10	11
P	P/0	R/0	P/0	G/1
Q	G/0	P/0	S/0	P/1
R	Q/1	S/1	-/-	P/0
S	P/1	Q/0	Q/0	P/1
G	Q/1	P/1	G/-	R/-

or a different table layout:

Pr. St.	Next state				Output			
	xy				xy			
	00	01	10	11	00	01	01	11
P	P	R	P	G	0	0	0	1
Q	G	P	S	P	0	0	0	1
R	Q	S	-	P	1	1	-	0
S	P	Q	Q	P	1	0	0	1
G	Q	P	G	R	1	1	-	-

Draw the state diagram of the reduced FSM.

4. Create the adjacency groups for the reduced state table.

Pr. St	Next state/output xy				Common successor for the same inputs (Rule 1)	Common ancestor for adjacent inputs (Rule 2)	Same output (e.g., "1" to minimize SoP) for the same input
	00	01	11	10			
P	P/0	R/0	G/1	P/0	P-S	P-R, G-P,G-R	P-Q, P-S
Q	G/0	P/0	P/1	S/0	Q-R, Q-S, Q-G	G-P, P-S, G-S	Q-S
R	Q/1	S/1	P/0	-/-	R-S,G-R	Q-S, P-S	R-S, 2xG-R
S	P/1	Q/0	P/1	Q/0		4xP-Q	G-S
G	Q/1	P/1	R/-	G/-		P-Q, P-R, G-R, G-Q	

	Rule 1	Rule 2	Rule 3
P-S	1	2	1
G-R	1	2	2
G-Q	1	1	
Q-R	1		
Q-S	1	1	1
R-S	1		1
P-R		2	
G-P		2	
P-Q		5	1
G-S		1	1

Ordered:

	Rule 1	Rule 2	Rule 3
G-R	1	2	2
P-S	1	2	1
Q-S	1	1	1
G-Q	1	1	
R-S	1		1
Q-R	1		
P-Q		5	1
P-R		2	
G-P		2	
G-S		1	1

5. Plot the state assignment map for the reduced state table if binary encoding of the states is employed.

Variant 1

Q ₁ Q ₀	00	01	11	10
Q ₂	P			
0	S	Q	G	R
1				

Variant 2

Q ₁ Q ₀	00	01	11	10
Q ₂	P	S	Q	
0	G	R		
1				

Variant 3

Q ₁ Q ₀	00	01	11	10
Q ₂	P	S	Q	R
0			G	
1				

Variant 4

Q ₁ Q ₀	00	01	11	10
Q ₂		P		
0	S	Q	G	R
1				

Rules observed

Rule 1	Rule 2	Rule 3
5	6	5
4	6	5
4	6	2
4	9	5

Derive the transition table.

Pr. St	Next state/output xy			
	00	01	10	11
P	P/0	R/0	P/0	G/1
Q	G/0	P/0	S/0	P/1
R	R/1	S/1	-/-	P/0
S	P/1	Q/0	Q/0	P/1
G	Q/1	P/1	G/-	R/-

Pr. St	Next state/output xy			
	00	01	10	11
P=000	000/0	010/0	000/0	111/1
Q=011	111/0	000/0	001/0	000/1
R=010	010/1	001/1	-/-	000/0
S=001	000/1	011/0	011/0	000/1
G=111	011/1	000/1	111/-	010/-

Pr. St	Next state/output xy			
	00	01	10	11
P=000	000/0	010/0	000/0	111/1
S=001	000/1	011/0	011/0	000/1
R=010	010/1	001/1	-/-	000/0
Q=011	111/0	000/0	001/0	000/1
100	-/-	-/-	-/-	-/-
101	-/-	-/-	-/-	-/-
110	-/-	-/-	-/-	-/-
G=111	011/1	000/1	111/-	010/-

6. Implement the state machine using J-K flip-flops.

Q_2

Pr. St	Next state/output xy			
	00	01	11	10
P=000	0	0	1	0
S=001	0	0	0	0
R=010	0	0	0	-
Q=011	1	0	0	0
100	-	-	-	-
101	-	-	-	-
110	-	-	-	-
G=111	0	0	0	1

J_2

Pr. St	Next state/output xy			
	00	01	11	10
P=000	0	0	1	0
S=001	0	0	0	0
R=010	0	0	0	-
Q=011	1	0	0	0
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	d	d	d	d

K_2

Pr. St	Next state/output xy			
	00	01	11	10
P=000	d	d	d	d
S=001	d	d	d	d
R=010	d	d	d	d
Q=011	d	d	d	d
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	1	1	1	0

$J_2 = xy Q_1' Q_0' + x'y' Q_1 Q_0$

$Q_1 Q_0$	00	01	11	10
0	xy	0	$x'y'$	0
1	d	d	d	d

$K_2 = x' + y$

$Q_1 Q_0$	00	01	11	10
0	d	d	d	d
1	d	d	$(xy)'$	d

Q_1

Pr. St	Next state/output xy			
	00	01	10	11
P=000	0	1	0	1
S=001	0	1	1	0
R=010	1	0	-	0
Q=011	1	0	0	0
100	-	-	-	-
101	-	-	-	-
110	-	-	-	-
G=111	1	0	1	1

J_1

Pr. St	Next state/output xy			
	00	01	10	11
P=000	0	1	0	1
S=001	0	1	1	0
R=010	d	d	d	d
Q=011	d	d	d	d
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	d	d	d	d

K_1

Pr. St	Next state/output xy			
	00	01	10	11
P=000	d	d	d	d
S=001	d	d	d	d
R=010	1	0	d	0
Q=011	1	0	0	0
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	1	0	1	1

$$J_1 = y Q_0' + (x \oplus y) Q_0 Q_0$$

$$K_1 = (x + y') Q_2 + x'y' Q_2' \text{ or, since } x'y'=1 \rightarrow y'=1 \rightarrow (x+y')=1, \rightarrow K_1 = (x + y')Q_2 + x'y$$

	$Q_1 Q_0$	00	01	11	10
Q_2					
0		y	$x \oplus y$	d	d
1		d	d	d	d

	$Q_1 Q_0$	00	01	11	10
Q_2					
0		d	d	$x'y'$	$x'y'$
1		d	d	$x+y'$	d

Q_0

Pr. St	Next state/output xy			
	00	01	10	11
P=000	0	0	0	1
S=001	0	1	1	0
R=010	0	1	-/-	0
Q=011	1	0	1	0
100	-	-	-	-
101	-	-	-	-
110	-	-	-	-
G=111	1	0	1	0

J_0

Pr. St	Next state/output xy			
	00	01	10	11
P=000	0	0	0	1
S=001	d	d	d	d
R=010	0	1	-/-	0
Q=011	d	d	d	d
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	d	d	d	d

K_0

Pr. St	Next state/output xy			
	00	01	10	11
P=000	d	d	d	d
S=001	1	0	0	1
R=010	d	d	d	d
Q=011	1	0	1	0
100	d	d	d	d
101	d	d	d	d
110	d	d	d	d
G=111	0	1	0	1

$$J_0 = xy Q_1' + x'y Q_1$$

$$K_0 = (x \oplus y)' Q_1' Q_0 + y' Q_2' Q_1 + y Q_2$$

	$Q_1 Q_0$	00	01	11	10
Q_2					
0		xy	d	d	$x'y$
1		d	d	d	d

	$Q_1 Q_0$	00	01	11	10
Q_2					
0		d	$(x \oplus y)'$	y'	d
1		d	d	y	d

Z

Pr. St	Next state/output xy			
	00	01	10	11
P=000	0	0	0	1
S=001	1	0	0	1
R=010	1	1	-	0
Q=011	0	0	0	1
100	-	-	-	-
101	-	-	-	-
110	-	-	-	-
G=111	1	1	-	-

$$Z = Q_2 + (x \oplus y)' Q_1' Q_0 + xy (Q_1 \oplus Q_0) + x' Q_1 Q_0'$$

	$Q_1 Q_0$	00	01	11	10
Q_2					
0		xy	$(x \oplus y)'$	xy	x'
1		d	d	1	d

OR:

Q ₂	Q ₁	Q ₀	x	y	Q ₂ ⁺	Q ₁ ⁺	Q ₀ ⁺	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
0	0	0	0	0	0	0	0	0	d	0	d	0	d
0	0	0	0	1	0	1	0	0	d	1	d	0	d
0	0	0	1	0	0	1	0	0	d	1	d	0	d
0	0	0	1	1	1	0	1	1	d	0	d	1	d
0	0	1	0	0	0	0	0	0	d	0	d	d	0
0	0	1	0	1	0	1	1	0	d	1	d	d	1
0	0	1	1	0	0	0	1	0	d	0	d	d	1
0	0	1	1	1	0	1	0	0	d	1	d	d	0
0	1	0	0	0	0	1	0	0	d	d	0	0	d
0	1	0	0	1	0	0	1	0	d	d	1	1	d
0	1	0	1	0	d	0	d	d	d	d	1	d	d
0	1	0	1	1	0	d	0	0	d	d	d	0	d
0	1	1	0	0	1	1	1	1	d	d	0	d	1
0	1	1	0	1	0	0	0	0	d	d	1	d	0
0	1	1	1	0	0	0	1	0	d	d	1	d	1
0	1	1	1	1	0	0	0	0	d	d	1	d	0
1	0	0	0	0	d	d	d	d	d	d	d	d	d
1	0	0	0	1	d	d	d	d	d	d	d	d	d
1	0	0	1	0	d	d	d	d	d	d	d	d	d
1	0	0	1	1	d	d	d	d	d	d	d	d	d
1	0	1	0	0	d	d	d	d	d	d	d	d	d
1	0	1	0	1	d	d	d	d	d	d	d	d	d
1	0	1	1	0	d	d	d	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d	d	d	d
1	1	0	0	0	d	d	d	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d	d	d	d
1	1	0	1	0	d	d	d	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d	d	d	d
1	1	1	0	0	0	1	1	d	1	d	0	d	1
1	1	1	0	1	0	0	0	d	1	d	1	d	0
1	1	1	1	0	1	1	1	d	0	d	0	d	1
1	1	1	1	1	0	1	0	d	1	d	0	d	0

$$J_2 = xy Q_1' Q_0' + x'y' Q_1 Q_0$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	0	0	1	0
001	0	0	0	0
011	1	0	0	0
010	0	0	0	d
100	d	d	d	d
101	d	d	d	d
111	d	d	d	d
110	d	d	d	d

$$K_2 = x' + y$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	d	d	d	d
001	d	d	d	d
011	d	d	d	d
010	d	d	d	d
100	d	d	d	d
101	d	d	d	d
111	1	1	1	0
110	d	d	d	d

$$J_1 = y Q_0' + (x \oplus y) Q_0$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	0	1	1	0
001	0	1	0	1
011	d	d	d	d
010	d	d	d	d
100	d	d	d	d
101	d	d	d	d
111	d	d	d	d
110	d	d	d	d

$$K_1 = (x + y') Q_2 + x'y'$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	d	d	d	d
001	d	d	d	d
011	1	0	0	0
010	1	0	0	d
100	d	d	d	d
101	d	d	d	d
111	1	0	1	1
110	d	d	d	d

$$J_0 = xy Q_1' + x'y Q_1$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	0	0	1	0
001	d	d	d	d
011	d	d	d	d
010	0	1	0	d
100	d	d	d	d
101	d	d	d	d
111	d	d	d	d
110	d	d	d	d

$$K_0 = (x \oplus y)' Q_1' Q_0' + y' Q_2' Q_1 + y Q_2$$

xy	00	01	11	10
Q ₂ Q ₁ Q ₀				
000	d	d	d	d
001	1	0	1	0
011	1	0	0	1
010	d	d	d	d
100	d	d	d	d
101	d	d	d	d
111	0	1	1	0
110	d	d	d	d

or : $K_0 = x'y' Q_2' + xy Q_1 + y' Q_2' Q_1 + y Q_2$

Schematics of the logic circuits