

CHAPTER - 9

TRANSMISSION LINES

CHAPTER 9

TRANSMISSION LINES

Exercise 9.1

$$r_i = 3 \text{ mm} , \quad r_o = 6 \text{ mm} , \quad \epsilon = 2.5 \epsilon_0$$

$$C_L = \frac{2\pi \times 2.5 \epsilon_0}{\ln \frac{6}{3}} = 2 \times 10^{-10} \text{ F/m} \quad C_L = 0.2 \text{ nF/m}$$

$$L_L = \frac{\mu_0}{2\pi} \ln \frac{6}{3} = 1.386 \times 10^{-7} \text{ H/m} \quad L_L = 0.1386 \text{ } \mu\text{H/m}$$

Exercise 9.2

$$l = 600 \text{ m} , \quad L_L = 0.4 \text{ } \mu\text{H/m} , \quad C_L = 85 \text{ pF/m} , \quad f = 100 \text{ kHz}$$

$$a) \quad u_p = \frac{1}{\sqrt{0.4 \times 10^{-6} \times 85 \times 10^{-12}}} = 1.715 \times 10^8 \text{ m/s}$$

$$\beta = \frac{\omega}{u_p} = \frac{2\pi \times 100 \times 10^3}{1.715 \times 10^8} = 3.664 \times 10^{-3} \text{ rad/m}$$

$$b) \quad \hat{Z}_c = \sqrt{\frac{L_L}{C_L}} = \sqrt{\frac{0.4 \times 10^{-6}}{85 \times 10^{-12}}} = 68.6 \text{ } \Omega$$

Exercise 9.3

$$t_d = 100 \text{ ns} , \quad L_\ell = 0.2 \mu\text{H/m} , \quad C_\ell = 60 \text{ pF/m}$$

$$u_p = \frac{1}{\sqrt{0.20 \times 10^{-6} \times 60 \times 10^{-12}}} = 2.8867 \times 10^8 \text{ m/s}$$

$$l = u_p t_d = 2.8867 \times 10^8 \times 100 \times 10^{-9} = 28.87 \text{ m}$$

Exercise 9.4

$$l = 20 \text{ m} , \quad L_\ell = 0.35 \mu\text{H/m} , \quad C_\ell = 45 \text{ pF/m}$$

$$P_R = 20 \text{ W} , \quad V_R = 50 \text{ V} , \quad f = 1 \text{ MHz}$$

$$a) \quad Z_c = \sqrt{\frac{0.35 \times 10^{-6}}{45 \times 10^{-12}}} = 88.19 \Omega$$

$$\beta = 2\pi \times 10^6 \sqrt{0.35 \times 10^{-6} \times 45 \times 10^{-12}}$$

$$\beta = 2.49 \times 10^{-2} \text{ rad/m}$$

$$b) \quad I_R = \frac{20}{50} = 0.4 \text{ A} , \quad \tilde{V}_R = 50 \angle 0^\circ \text{ V} , \quad \tilde{I}_R = 0.4 \angle 0^\circ \text{ A}$$

$$\tilde{I}_S = j \frac{1}{88.19} \sin(2.49 \times 10^{-2} \times 20) \times 50 \angle 0^\circ + \cos(2.49 \times 10^{-2} \times 20) \times 0.4 \angle 0^\circ$$

$$\tilde{I}_S = 0.444 \angle 37.62^\circ \text{ A}$$

$$\tilde{V}_S = \cos(2.49 \times 10^{-2} \times 20) \times 50 \angle 0^\circ + j 88.19 \times \sin(2.49 \times 10^{-2} \times 20) \times 0.4 \angle 0^\circ$$

$$\tilde{V}_S = 47.048 \angle 20.99^\circ \text{ V}$$

$$c) \quad \hat{S}_S = \tilde{V}_S \tilde{I}_S^* = 20 - j 5.975 \text{ VA} \Rightarrow P_S = 20 \text{ W} , \quad Q_S = -5.975 \text{ VAR}$$

Exercise 9.5

$$l = 50 \text{ m}, L_\ell = 0.3 \mu\text{H/m}, C_\ell = 40 \text{ pF/m}, \hat{S}_R = 10 + j2 \text{ VA}$$

$$V_R = 20 \text{ V}, f = 100 \text{ kHz}$$

$$\tilde{I}_R^* = \frac{\hat{S}_R}{\tilde{V}_R} = \frac{10 + j2}{20 \angle 0^\circ} = 0.5 + j0.1 \Rightarrow \tilde{I}_R = 0.5 - j0.1 \text{ A} = 0.51 \angle -11.31^\circ \text{ A}$$

$$\hat{Z}_L = \frac{20 \angle 0^\circ}{0.51 \angle -11.31^\circ} = 39.22 \angle 11.31^\circ \Omega$$

$$\beta = 2\pi \times 100 \times 10^3 \sqrt{0.3 \times 10^{-6} \times 40 \times 10^{-12}} = 2.18 \times 10^{-3} \text{ rad/m}$$

$$\hat{Z}_C = \sqrt{\frac{0.3 \times 10^{-6}}{40 \times 10^{-12}}} = 86.6 \Omega$$

$$\hat{Z}_{in}(0) = 86.6 \frac{39.22 \angle 11.31^\circ + j86.6 \tan(2.18 \times 10^{-3} \times 50)}{86.6 + j39.22 \angle 11.31^\circ \tan(2.18 \times 10^{-3} \times 50)}$$

$$\hat{Z}_{in}(0) = 39.592 + j15.383 \Omega = 42.475 \angle 21.23^\circ \Omega$$

Exercise 9.6

$$l = 2 \text{ m}, f = 10 \text{ MHz}, L_\ell = 0.251 \mu\text{H/m}, C_\ell = 48.28 \text{ pF/m}$$

$$\hat{Z}_{in}(0) = 50 + j25 \Omega$$

$$\beta = 2\pi \times 10 \times 10^6 \sqrt{0.251 \times 10^{-6} \times 48.28 \times 10^{-12}} = 0.219 \text{ rad/m}$$

$$\hat{Z}_C = \sqrt{\frac{0.251 \times 10^{-6}}{48.28 \times 10^{-12}}} = 72.103 \Omega$$

$$\hat{Z}_L = \hat{Z}_c \frac{\hat{Z}_{in} - j \hat{Z}_c \tan \beta l}{\hat{Z}_c - j \hat{Z}_{in} \tan \beta l}$$

$$\hat{Z}_L = 72.103 \frac{(50 + j25) - j72.103 \tan(0.219 \times 2)}{72.103 - j(50 + j25) \tan(0.219 \times 2)}$$

$$\hat{Z}_L = 41.858 + j4.177 \Omega$$

Exercise 9.7

$$l = 3\text{m}, \quad v_s = 20 \cos(3.14 \times 10^8 t) \text{ V}, \quad \hat{Z}_L = 100 + j20 \Omega$$

$$L_l = 0.2 \mu\text{H/m}, \quad C_l = 40 \text{ pF/m}$$

$$\hat{Z}_c = \sqrt{\frac{0.2 \times 10^{-6}}{40 \times 10^{-12}}} = 70.71 \Omega$$

$$\beta = 3.14 \times 10^8 \sqrt{0.2 \times 10^{-6} \times 40 \times 10^{-12}} = 0.605 \text{ rad/m}$$

$$\hat{Z}_{in}(0) = 70.71 \frac{(100 + j20) + j70.71 \tan(0.605 \times 3)}{70.71 + j(100 + j20) \tan(0.605 \times 3)} = 46.521 + j0.153 \Omega$$

$$\tilde{I}_s = \frac{20 \angle 0^\circ}{46.521 + j0.153} = 0.43 \angle -0.188^\circ \text{ A}$$

$$i_s = 0.43 \cos(3.14 \times 10^8 t - 0.188^\circ)$$

$$\hat{S}_s = \frac{1}{2} \tilde{V}_s \tilde{I}_s^* = 4.299 + j0.014 \text{ VA}$$

$$P_s = 4.299 \text{ W}$$

Exercise 9.8

$$l = 10 \text{ m} , \hat{Z}_c = 75 \Omega , \hat{Z}_L = 35 + j10 \Omega , v_R = \sqrt{2} \times 50 \cos 10^8 t \text{ V}$$

$$v_s = \sqrt{2} \times 66 \cos(10^8 t + 31^\circ) \text{ V}$$

$$\tilde{V}_R = \sqrt{2} \times 50 \angle 0^\circ \text{ V} , \hat{Z}_L = 36.4 \angle 15.95^\circ \Omega$$

$$\tilde{I}_R = \frac{\tilde{V}_R}{\hat{Z}_L} = \sqrt{2} \times 1.374 \angle -15.95^\circ \text{ A} = \sqrt{2} (1.321 - j0.3776) \text{ A}$$

In terms of "rms" voltages and currents, we can write,

$$66 \angle 31^\circ = 50 \cos(10\beta) + j(1.321 \times 75 - j0.3776 \times 75) \sin(10\beta)$$

$$50 \cos(10\beta) + 0.3776 \times 75 \sin(10\beta) = 56.57$$

$$1.321 \times 75 \sin(10\beta) = 33.99$$

$$\beta = 0.035$$

$$C_l = \frac{\beta}{\omega Z_c} = \frac{0.035}{10^8 \times 75} = 4.67 \times 10^{-12} \text{ F/m}$$

$$C_l = 4.67 \text{ pF/m}$$

$$L_l = C_l Z_c^2$$

$$L_l = 4.67 \times 10^{-12} \times 75^2 = 2.63 \times 10^{-8} \text{ H/m}$$

$$L_l = 0.0263 \text{ } \mu\text{H/m}$$

Exercise 9.9

$$l = 50 \text{ m} , \hat{\tau}_R = 0.75 \angle 9^\circ , V_R = 20 \text{ V} , P_R = 10 \text{ W} , C_\ell = 75 \text{ pF/m}$$

$$\cos \theta = 0.97 \text{ (inductive)} , f = 1 \text{ kHz}$$

$$I_R = \frac{10/0.97}{20} = 0.515 \text{ A} , \tilde{I}_R = 0.515 \angle -14.07^\circ \text{ A}$$

$$\hat{Z}_L = \frac{20}{0.515 \angle -14.07^\circ} = 38.8 \angle 14.07^\circ \Omega$$

$$a) \hat{\tau}_R = 1 + \hat{\rho}_R \Rightarrow \hat{\rho}_R = \hat{\tau}_R - 1 = 0.75 \angle 9^\circ - 1 = 0.285 \angle 155.65^\circ$$

$$b) \hat{Z}_c = \hat{Z}_L \frac{1 - \hat{\rho}_R}{1 + \hat{\rho}_R} = \frac{1 - 0.285 \angle 155.65^\circ}{1 + 0.285 \angle 155.65^\circ} \times 38.8 \angle 14.07^\circ =$$

$$\hat{Z}_c = 65.426 - j0.289 \Omega \quad \hat{Z}_c \approx 65.4 \Omega$$

$$c) L_\ell = 65.4^2 C_\ell \Rightarrow L_\ell = 3.208 \times 10^{-7} \text{ H/m}$$

$$\beta = 2\pi \times 10^3 \sqrt{3.208 \times 10^{-7} \times 75 \times 10^{-12}} = 3.082 \times 10^{-5} \text{ rad/m}$$

$$\tilde{V}_s = \tilde{V}_R \cos \beta l + j \hat{Z}_c \tilde{I}_R \sin \beta l \quad \tilde{V}_s = 20 + j0.052 \text{ V}$$

$$\tilde{I}_s = \frac{j}{\hat{Z}_c} \sin \beta l \cdot \tilde{V}_R + \cos \beta l \cdot \tilde{I}_R \quad \tilde{I}_s = 0.515 + j4.71 \times 10^{-4} \text{ A}$$

$$\hat{S}_s = \tilde{V}_s \tilde{I}_s^* = 10.3 + j0.017 \text{ VA} \quad P_s \approx 10 \text{ W}$$

Exercise 9.10

$$\hat{Z}_c = 75 \Omega, \text{ VSWR} = 1.3$$

$$\text{VSWR} = \frac{1 + |\rho_R|}{1 - |\rho_R|} = 1.3 \Rightarrow |\rho_R| = 0.13$$

$$\rho_R = \frac{R_L - 75}{R_L + 75} = 0.13 \Rightarrow R_L = 97.41 \Omega$$

$$\rho_{R_m} = \frac{R_L // R_m - 75}{R_L // R_m + 75} = 0 \Rightarrow R_L // R_m = 75 \Omega$$

$$\frac{R_L R_m}{R_L + R_m} = 75 \Rightarrow R_m = 326 \Omega$$

Exercise 9.11

$$\hat{Z}_c = 50 \Omega, \quad f = 1 \text{ MHz}, \quad R_L = 100 \Omega, \quad L_L = 10 \mu\text{H}$$

$$\hat{Z}_L = 100 + j 2\pi \times 10^6 \times 10 \times 10^{-6} = 100 + j 62.83 \Omega$$

$$\hat{\rho}_R = \frac{100 + j 62.83 - 50}{100 + j 62.83 + 50} = 0.494 \angle 28.76^\circ \quad |\hat{\rho}_R| = 0.494$$

$$\text{VSWR} = \frac{1 + 0.494}{1 - 0.494}$$

$$\text{VSWR} = 2.95$$

Exercise 9.12

$$\hat{Z}_c = 75 \Omega, \quad l = 10 \text{ m}, \quad f = 150 \text{ MHz}, \quad \hat{Z}_L = 150 + j225 \Omega$$

$$u_p = 2.95 \times 10^8 \text{ m/s}$$

$$\beta = \frac{2\pi \times 150 \times 10^6}{2.95 \times 10^8} = 3.195 \text{ rad/m}$$

$$\frac{1}{75} \frac{75 + j(150 + j225) \tan(3.195d)}{(150 + j225) + j75 \tan(3.195d)} = \frac{1}{75} + j \frac{1}{75 \tan(3.195l_s)}$$

Solving the above equation yields

$$d = 0.449 \text{ m} \quad \text{and} \quad l_s = 0.21 \text{ m}$$

Exercise 9.13

$$\hat{Z}_c = 50 \Omega, \quad l = 2 \text{ m}, \quad f = 60 \text{ MHz}, \quad l_s = 0.5 \text{ m}, \quad d = 0.6 \text{ m}, \quad t_f = 7 \text{ ns}$$

$$u_p = \frac{2}{7 \times 10^{-9}} = 2.86 \times 10^8 \text{ m/s}$$

$$\beta = \frac{2\pi \times 60 \times 10^6}{2.86 \times 10^8} = 1.32 \text{ rad/m}$$

$$\frac{1}{50} \frac{50 + j(R_L + jX_L) \tan(1.32 \times 0.6)}{(R_L + jX_L) + j50 \tan(1.32 \times 0.6)} = \frac{1}{50} + j \frac{1}{50 \tan(1.32 \times 0.5)}$$

$$\text{where } \hat{Z}_L = R_L + jX_L$$

Solving the above equation yields

$$R_L = 93.76 \Omega \quad \text{and} \quad X_L = -25.78 \Omega$$

Exercise 9.14

$$i_s = 2 \sin(314 \times 10^3 t) \text{ A}, \quad l = 10 \text{ m}, \quad v_s = 50 \cos(314 \times 10^3 t) \text{ V}$$

$$R = 0.25 \Omega, \quad L = 6.5 \mu\text{H}, \quad G = 0, \quad C = 320 \text{ pF}$$

$$R_L = \frac{0.25}{10} = 0.025 \Omega/\text{m}, \quad L_L = \frac{6.5}{10} = 0.65 \mu\text{H}/\text{m}, \quad C_L = \frac{320}{10} = 32 \text{ pF}/\text{m}$$

$$\hat{Z}_L = 0.025 + j 314 \times 10^3 \times 0.65 \times 10^{-6} = 0.025 + j 0.204 \Omega/\text{m}$$

$$\hat{Y}_L = j 314 \times 10^3 \times 32 \times 10^{-12} = j 1.005 \times 10^{-5} \text{ S}/\text{m}$$

$$\hat{Z}_C = \sqrt{\frac{\hat{Z}_L}{\hat{Y}_L}} = \sqrt{\frac{0.025 + j 0.204}{j 1.005 \times 10^{-5}}} = 142.79 - j 8.71 \Omega$$

$$\hat{\gamma} = \sqrt{\hat{Z}_L \hat{Y}_L} = \sqrt{(0.025 + j 0.204)(j 1.005 \times 10^{-5})} = 8.75 \times 10^{-5} + j 0.001435$$

$$\hat{Z}_{in}(0) = \frac{\tilde{V}_s}{\tilde{I}_s} = \frac{50 \angle 0^\circ}{2 \angle 0^\circ} = 25 \angle 0^\circ \Omega$$

$$\hat{Z}_L = \frac{\hat{Z}_C \tanh \hat{\gamma} l - \hat{Z}_{in}(0)}{\frac{\hat{Z}_{in}(0)}{\hat{Z}_C} \tanh \hat{\gamma} l - 1} = 24.76 - j 1.98 \Omega$$

$$P_{in} = (50 \times 2) \frac{1}{2} = 50 \text{ W}$$

$$\tilde{V}_R = \cosh \hat{\gamma} l \cdot \tilde{V}_s - \hat{Z}_C \tilde{I}_s \sinh \hat{\gamma} l = 49.66 \angle -4.714^\circ \text{ V}$$

$$\tilde{I}_R = -\frac{1}{\hat{Z}_C} \sinh \hat{\gamma} l \cdot \tilde{V}_s + \cosh \hat{\gamma} l \cdot \tilde{I}_s = 2 \angle -0.143^\circ \text{ A}$$

$$\hat{S}_R = (\tilde{V}_R \tilde{I}_R^*) \frac{1}{2} = 49.5 - j 3.96 \text{ VA} \quad P_R = 49.5 \text{ W}$$

$$\eta = \frac{P_R}{P_s} = \frac{49.5}{50} = 0.99 \quad \text{or} \quad \eta = 99\%$$

Exercise 9.15

$$l = 40 \text{ m}, \quad \hat{Z}_c = 75 \angle -4^\circ \Omega, \quad \alpha_{dB} = 0.001 \text{ dB/m}, \quad f = 2 \text{ MHz},$$

$$u_p = 2.5 \times 10^8 \text{ m/s}, \quad \tilde{V}_s = 60 \angle 0^\circ \text{ V}, \quad \tilde{I}_R = 0$$

$$\alpha = \frac{\alpha_{dB}}{8.69} = \frac{0.001}{8.69} = 1.151 \times 10^{-4} \text{ Np/m}, \quad \beta = \frac{2\pi \times 2 \times 10^6}{2.5 \times 10^8} = 0.05 \frac{\text{rad}}{\text{m}}$$

$$\hat{\gamma} = 1.151 \times 10^{-4} + j0.05 \quad \cosh \hat{\gamma} l = 0.426 \angle 179.44^\circ, \quad \sinh \hat{\gamma} l = 0.905 \angle 90.12^\circ$$

$$a) \quad \tilde{V}_R = \frac{\tilde{V}_s}{\cosh \hat{\gamma} l} = \frac{60 \angle 0^\circ}{0.426 \angle 179.44^\circ} = 140.91 \angle -179.44^\circ \text{ V}$$

$$b) \quad \tilde{I}_s = \frac{1}{\hat{Z}_c} \sinh \hat{\gamma} l \cdot \tilde{V}_R = \frac{60 \angle 0^\circ}{75 \angle -4^\circ} (0.905 \angle 90.12^\circ) = 1.7 \angle -85.32^\circ \text{ A}$$

Assuming V_s and I_s as the "rms" values yields the power

$$\hat{S}_s = \tilde{V}_s \tilde{I}_s^* = 8.33 + j101.66 \text{ VA}$$

$$P_s = 8.33 \text{ W}, \quad Q_s = 101.66 \text{ VAR}$$

Exercise 9.16

$$V_s = 5V, \quad l = 10\text{m}, \quad R_c = 50\Omega, \quad R_L = 100\Omega, \quad R_s = 0$$

$$u_p = 2.85 \times 10^8 \text{ m/s} \quad t = 5t_t$$

$$\rho_R = \frac{100 - 50}{100 + 50} = \frac{1}{3}, \quad \rho_s = \frac{0 - 50}{0 + 50} = -1$$

$$t_t = \frac{l}{2.85 \times 10^8} = 3.5 \times 10^{-8} \text{ s} = 35 \text{ ns}$$

$$V_s(0) = 5V, \quad I_s(0) = \frac{5}{50} = 0.1 \text{ A}$$

$$V_R(35 \text{ ns}) = 5 + \frac{5}{3} = \frac{20}{3} \text{ V}, \quad I_R(35 \text{ ns}) = 0.1 - \frac{0.1}{3} = \frac{0.2}{3} \text{ A}$$



$$P_R(35 \text{ ns}) = V_R(35 \text{ ns}) I_R(35 \text{ ns}) = \frac{20}{3} \times \frac{0.2}{3} = \frac{4}{9} \text{ W}$$

$$V_R(105 \text{ ns}) = -\frac{5}{3} - \frac{5}{9} = -\frac{20}{9} \text{ V}, \quad I_R(105 \text{ ns}) = -\frac{0.1}{3} + \frac{0.1}{9} = -\frac{0.2}{9} \text{ A}$$

$$P_R(105 \text{ ns}) = \left(-\frac{20}{9}\right) \left(-\frac{0.2}{9}\right) = \frac{4}{81} \text{ W}$$

$$V_R(175 \text{ ns}) = \frac{5}{9} + \frac{5}{27} = \frac{20}{27} \text{ V}, \quad I_R(175 \text{ ns}) = \frac{0.1}{9} - \frac{0.1}{27} = \frac{0.2}{27} \text{ A}$$

$$P_R(175 \text{ ns}) = \left(\frac{20}{27}\right) \left(\frac{0.2}{27}\right) = \frac{4}{729} \text{ W}$$

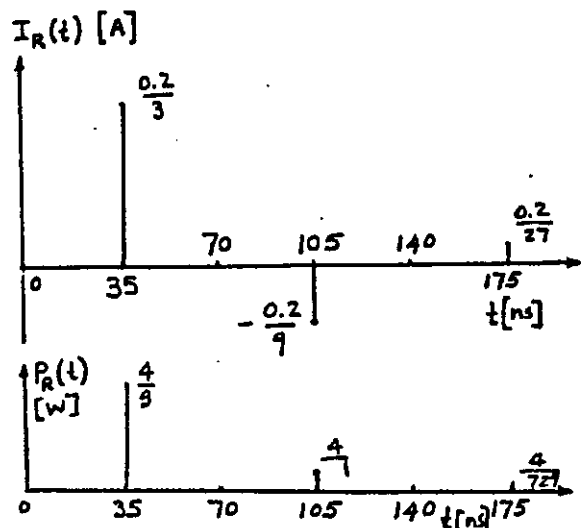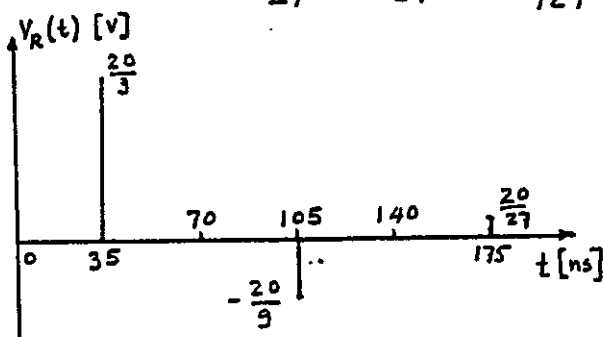


Exercise 9.17

$$V_G = 10V, \quad l = 20m, \quad R_c = 75\Omega, \quad R_G = 5\Omega, \quad R_L = 100\Omega$$


$$u_p = 3 \times 10^8 \text{ m/s}, \quad z = 5m$$

$$\beta_R = \frac{100 - 75}{100 + 75} = 0.143, \quad \beta_S = \frac{5 - 75}{5 + 75} = -0.875$$
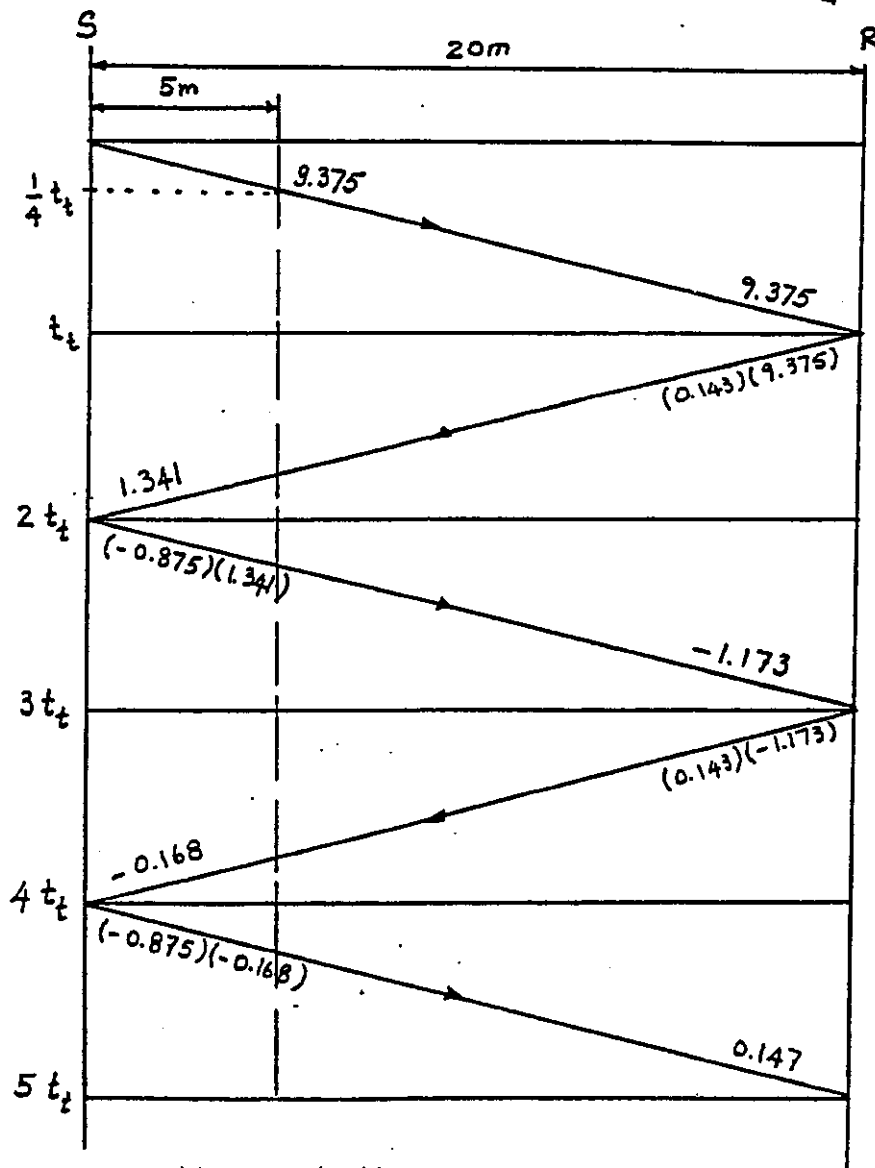
$$t_t = \frac{20}{3 \times 10^8} = 6.67 \times 10^{-8} \text{ s}, \quad V_S = \frac{V_G}{R_G + R_c} R_c = \frac{10 \times 75}{5 + 75} = 9.375V$$





Voltage Lattice Diagram.

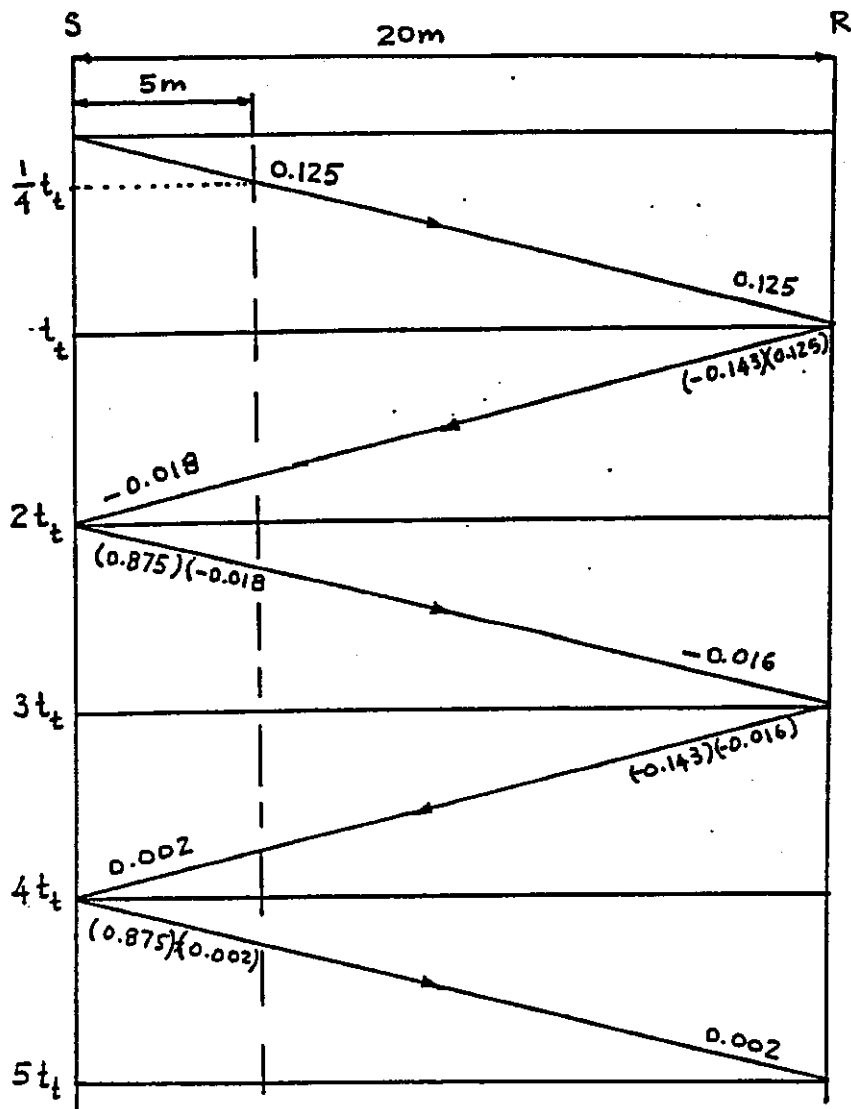

$$I_s = \frac{V_G}{R_G + R_c}$$

$$I_s = \frac{10}{5 + 75} = 0.125 \text{ A}$$

Current lattice diagram.

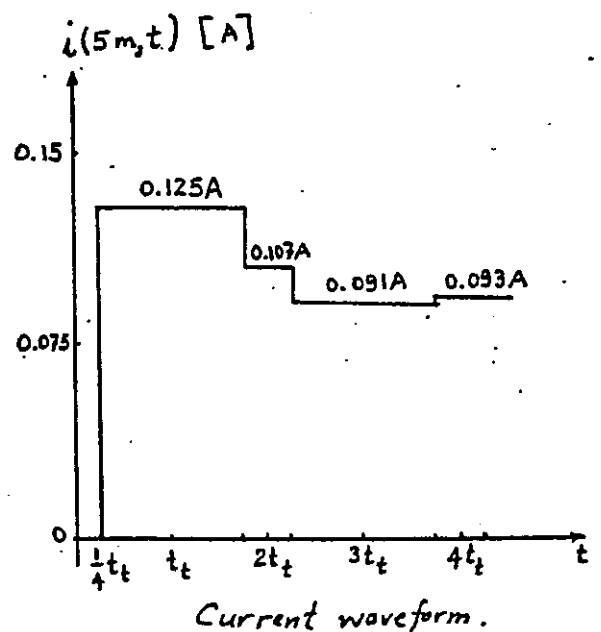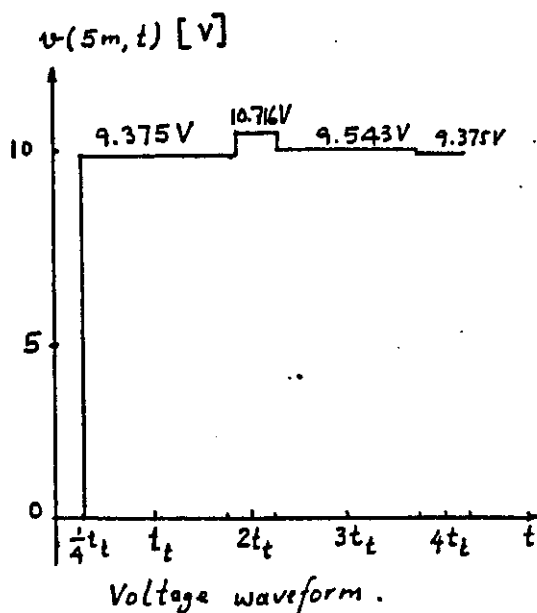

Exercise 9.18

$$R_{c1} = 75 \Omega, R_{c2} = 50 \Omega, R_L = 30 \Omega, V_G = 10V, R_G = 25 \Omega$$


$$t_{t1} = 3 \mu s, t_{t2} = 2 \mu s$$


$$\rho_s = \frac{25 - 75}{25 + 75} = -0.5, \quad \rho_R = \frac{30 - 50}{30 + 50} = -0.25,$$

$$\rho_1 = \frac{50 - 75}{50 + 75} = -0.2, \quad \tau_1 = 1 - 0.2 = 0.8 \text{ Towards the second cable.}$$

$$\rho_2 = \frac{75 - 50}{50 + 75} = 0.2, \quad \tau_2 = 1 + 0.2 = 1.2 \text{ Towards the first cable.}$$

$$V_s = \frac{10}{25 + 75} 75 = 7.5V$$

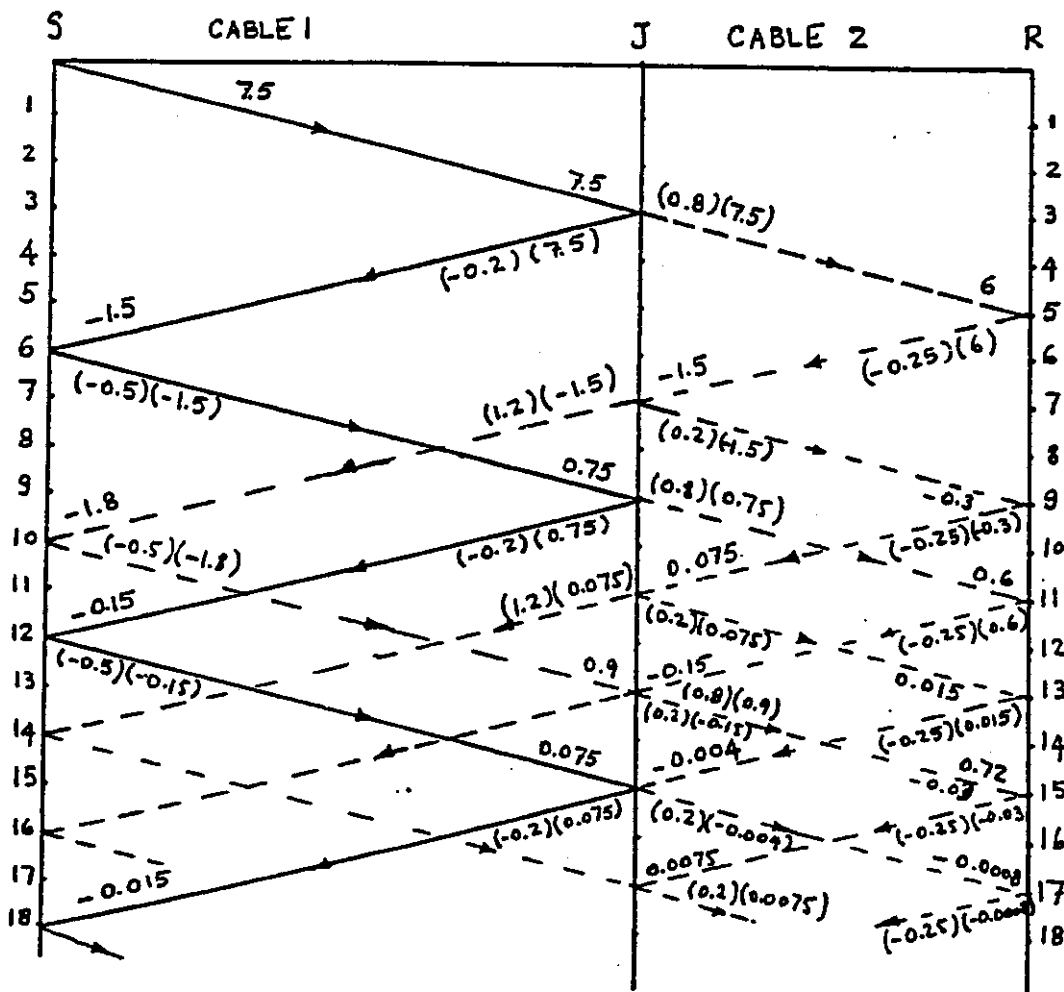

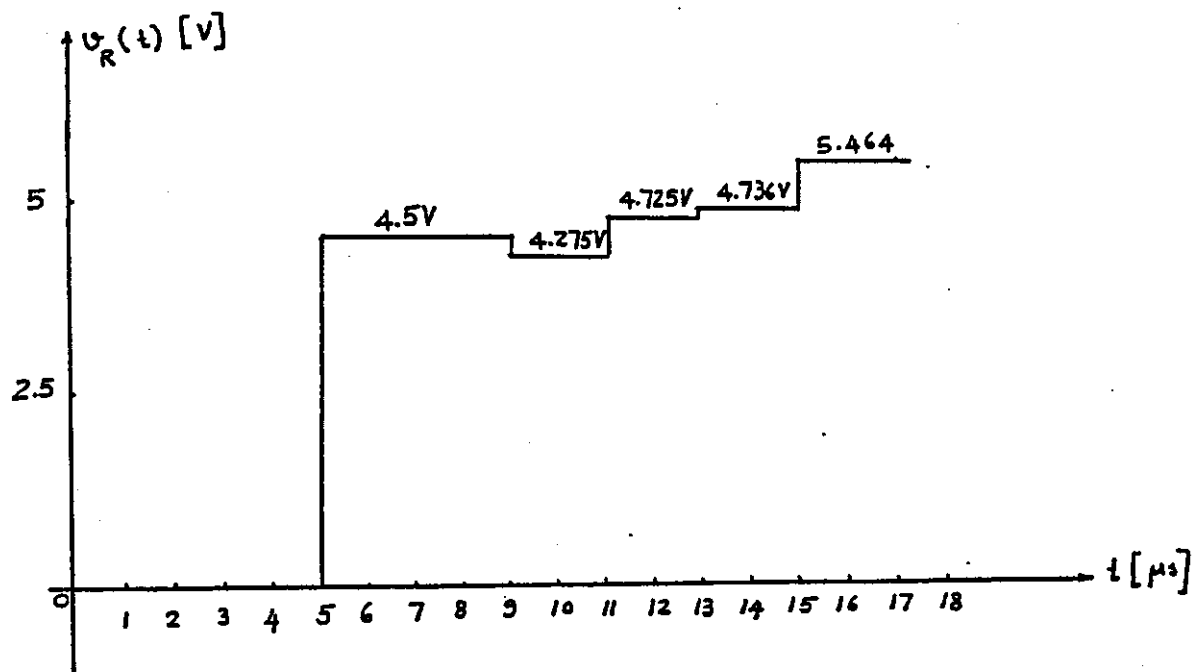

Voltage waveform at the receiving end.

Exercise 9.19

$$r = 2 \text{ mm}, \quad f = 60 \text{ Hz}, \quad f = 1000 \text{ Hz}, \quad f = 1 \text{ MHz}, \quad \sigma = 3.55 \times 10^7 \text{ S/m}$$

$$\text{At } f = 60 \text{ Hz} \quad \delta_c = \sqrt{\frac{2}{2\pi \cdot 60 \times 4\pi \times 10^{-7} \times 3.55 \times 10^7}} = 1.09 \times 10^{-2} \text{ m}$$

$$\delta_c = 1.09 \text{ cm}$$

$$\text{At } f = 1000 \text{ Hz} \quad \delta_c = \sqrt{\frac{2}{2\pi \cdot 10^3 \times 4\pi \times 10^{-7} \times 3.55 \times 10^7}} = 2.67 \times 10^{-3} \text{ m}$$

$$\delta_c = 2.67 \text{ mm}$$

$$\text{At } f = 1 \text{ MHz} \quad \delta_c = \sqrt{\frac{2}{2\pi \cdot 10^6 \times 4\pi \times 10^{-7} \times 3.55 \times 10^7}} = 8.45 \times 10^{-5} \text{ m}$$

$$\delta_c = 0.0845 \text{ mm}$$

Exercise 9.20

$$a = \frac{10}{2} = 5 \text{ mm} \quad f = 1 \text{ kHz}, \quad f = 1 \text{ MHz}, \quad \sigma = 3.55 \times 10^7 \text{ S/m}$$

At $f = 1 \text{ kHz}$

$$\delta_c = \sqrt{\frac{2}{2\pi \times 10^3 \times 3.55 \times 10^7 \times 4\pi \times 10^{-7}}} = 1.09 \times 10^{-2} \text{ m}$$

The internal resistance:

$$R_{li} = \frac{1}{2\pi a \sigma \delta_c} = \frac{1}{2\pi \times 5 \times 10^{-3} \times 3.55 \times 10^7 \times 1.09 \times 10^{-2}} = 82.26 \times 10^{-6} \Omega/\text{m}$$

The internal inductance:

$$L_{li} = \frac{82.26 \times 10^{-6}}{2\pi \times 10^3} = 1.309 \times 10^{-8} \text{ H/m}$$

At $f = 1 \text{ MHz}$

$$\delta_c = \sqrt{\frac{2}{2\pi \times 10^6 \times 3.55 \times 10^7 \times 4\pi \times 10^{-7}}} = 8.45 \times 10^{-5} \text{ m}$$

The internal resistance:

$$R_{li} = \frac{1}{2\pi \times 5 \times 10^{-3} \times 3.55 \times 10^7 \times 8.45 \times 10^{-5}} = 1.06 \times 10^{-2} \Omega/\text{m}$$

The internal inductance:

$$L_{li} = \frac{1.06 \times 10^{-2}}{2\pi \times 10^6} = 1.69 \times 10^{-9} \text{ H/m}$$

Problem 9.2

$$l = 20 \text{ km} \quad \hat{Z}_c = 150 \Omega \quad u_p = 0.9c$$

$$u_p = \frac{1}{\sqrt{L_l C_l}} = 0.9 \times 3 \times 10^8, \quad \hat{Z}_c = \sqrt{\frac{L_l}{C_l}} = 150 \Omega$$

$$\frac{L_l}{C_l} = 150^2 \quad (1) \quad , \quad \frac{1}{L_l C_l} = (2.7 \times 10^8)^2 \quad (2)$$


Solving (1) and (2) simultaneously yields,

$$L_l = 5.56 \times 10^{-7} \text{ H/m}, \quad C_l = 2.47 \times 10^{-11} \text{ F/m}$$

$$\text{Total inductance } L = 20 \times 10^3 \times 5.56 \times 10^{-7} = 11.12 \times 10^{-3} \text{ H or } 11.12 \text{ mH}$$

$$\text{Total capacitance } C = 20 \times 10^3 \times 2.47 \times 10^{-11} = 4.94 \times 10^{-7} \text{ F or } 0.494 \mu\text{F}$$

Problem 9.3

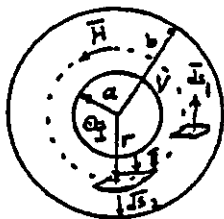

Inductance:

$$\vec{H} = \frac{I}{2\pi r} \vec{a}_\phi \quad [\text{A/m}], \quad \vec{B} = \mu_0 \frac{I}{2\pi r} \vec{a}_\phi \quad [\text{T}]$$

$$d\vec{S}_l = dr dz \vec{a}_\phi$$

$$\Phi = \int_0^l \int_a^b \mu_0 \frac{I}{2\pi r} \vec{a}_\phi \cdot dr dz \vec{a}_\phi = \mu_0 \frac{I}{2\pi} \ln \frac{b}{a} \quad [\text{Wb/m}]$$

$$\lambda = N \Phi \quad N=1 \quad \lambda = \Phi = \mu_0 \frac{I}{2\pi} \ln \frac{b}{a} \quad \left[\frac{\text{Wb}}{\text{m}} \right]$$

$$L = \frac{d\Phi}{dI} = \frac{\mu_0}{2\pi} \ln \frac{b}{a} \quad [\text{H/m}]$$

Capacitance:

$$\vec{E} = \frac{V}{r \ln \frac{b}{a}} \vec{a}_r \quad \left[\frac{V}{m} \right], \quad \vec{D} = \epsilon \vec{E} = \epsilon \frac{V \vec{a}_r}{r \ln \frac{b}{a}} \quad [C/m^2]$$

$$d\vec{s}_2 = r d\phi dz \vec{a}_r$$

$$Q = \int_0^l \int_0^{2\pi} \epsilon \frac{V}{r \ln \frac{b}{a}} \vec{a}_r \cdot r d\phi dz \vec{a}_r = \frac{2\pi \epsilon V}{\ln \frac{b}{a}} \quad \left[\frac{C}{m} \right]$$

$$C = \frac{dQ}{dV} = \frac{2\pi \epsilon}{\ln \frac{b}{a}} \quad \left[\frac{F}{m} \right]$$

Problem 9.4

$$t_d = 14 \text{ ns} \quad \text{at} \quad f = 1 \text{ MHz} \quad l = 2 \text{ m} \quad \mu = \mu_0 \quad \epsilon_r = ?$$

$$t_d = \frac{l}{u_p} = l \sqrt{L_l C_l}$$

$$\text{From Problem 9.3} \quad L_l = \frac{\mu_0}{2\pi} \ln \frac{b}{a}, \quad C_l = 2\pi \epsilon_0 / \ln \frac{b}{a}$$

$$t_d = l \sqrt{\left(\frac{\mu_0}{2\pi} \ln \frac{b}{a} \right) \left(\frac{2\pi \epsilon_r \epsilon_0}{\ln \frac{b}{a}} \right)} = l \sqrt{\mu_0 \epsilon_0 \epsilon_r}$$

$$\epsilon_r = \frac{\left(\frac{14 \times 10^{-9}}{2} \right)^2}{4\pi \times 10^{-7} \times 8.85 \times 10^{-12}} = 4.4$$

Problem 9.5

$$l = 300 \text{ m}, \hat{Z}_c = 75 \Omega, \mu_p = 220,000 \text{ km/s}, f = 3 \text{ MHz}$$

$$\hat{Z}_L = 150 + j400 \Omega, \tilde{V}_R = 50 \angle 0^\circ \text{ V (rms)}$$

$$\tilde{I}_R = \frac{\tilde{V}_R}{\hat{Z}_L} = \frac{50 \angle 0^\circ}{150 + j400} = 0.117 \angle -69.44^\circ \text{ A}$$

$$\beta = \frac{\omega}{\mu_p} = \frac{2\pi \times 3 \times 10^6}{220,000 \times 10^3} = 8.57 \times 10^{-2} \text{ rad/m}$$

$$\tilde{V}_s = (50 \angle 0^\circ) \cos(8.57 \times 10^{-2} \times 300) + j75 \times (0.117 \angle -69.44^\circ) \sin(8.57 \times 10^{-2} \times 300)$$

$$\tilde{V}_s = 46.412 \angle 2.077^\circ \text{ V}$$

Problem 9.6

$$l = 2 \text{ m}, f = 15 \text{ MHz}, \beta = 369.6 \times 10^3 \text{ rad/m}, \hat{Z}_c = Z_c \angle 0^\circ, \hat{S}_R = 3.5 - j1.5 \text{ VA},$$

$$\tilde{V}_R = 50 \angle 0^\circ \text{ V}, V_s = 34 \text{ V}$$

$$\tilde{I}_R^* = \frac{3.5 - j1.5}{50} = 0.07 - j0.03 \Rightarrow \tilde{I}_R = 0.0762 \angle 23.2^\circ \text{ A}$$

$$34 \angle \phi = 50 \cos(369.6 \times 10^3 \times 2) + jZ_c 0.0762 \angle 23.2^\circ \sin(369.6 \times 10^3 \times 2)$$

$$34 \cos \phi + j34 \sin \phi = 36.95 - 0.02 Z_c + j0.047 Z_c$$

$$34 \cos \phi + 0.02 Z_c = 36.95 \quad (1), \quad 34 \sin \phi = 0.047 Z_c \quad (2)$$

Solving (1) and (2) simultaneously yields,

$$Z_c = 283.24 \Omega, \phi = 23.05^\circ$$

Problem 9.7

$$\hat{S}_R = 100 + j30 \text{ MVA}, \quad l = 100 \text{ km}, \quad f = 60 \text{ Hz}, \quad V_R = 110 \text{ kV}$$

$$L_l = 0.372 \mu\text{H/m}, \quad C_l = 76 \text{ pF/m}$$

$$a) \quad \hat{Z}_c = \sqrt{\frac{0.372 \times 10^{-6}}{76 \times 10^{-12}}} = 69.96 \Omega$$

$$b) \quad u_p = \frac{1}{\sqrt{0.372 \times 10^{-6} \times 76 \times 10^{-12}}} = 188,071 \text{ km/s}$$

$$\beta = \frac{2\pi \times 60}{188,071 \times 10^3} = 2 \times 10^{-6} \text{ rad/m}$$

$$c) \quad \tilde{I}_R^* = \frac{(100 + j30) \times 10^6}{110 \times 10^3} = 909.1 + j272.73$$

$$\tilde{I}_R = 949.13 \angle -16.7^\circ \text{ A}$$


$$\tilde{V}_s = (110 \times 10^3 \angle 0^\circ) \cos(2 \times 10^{-6} \times 100 \times 10^3) + j(69.96 \angle 0^\circ)(949.13 \angle -16.7^\circ) \sin(2 \times 10^{-6} \times 10^3)$$

$$\tilde{V}_s = 112.31 \angle 6.46^\circ \text{ kV}$$

$$d) \quad \Delta V = V_s - V_R$$

$$\Delta V = 112.31 - 110 = 2.31 \text{ kV}$$

Problem 9.8

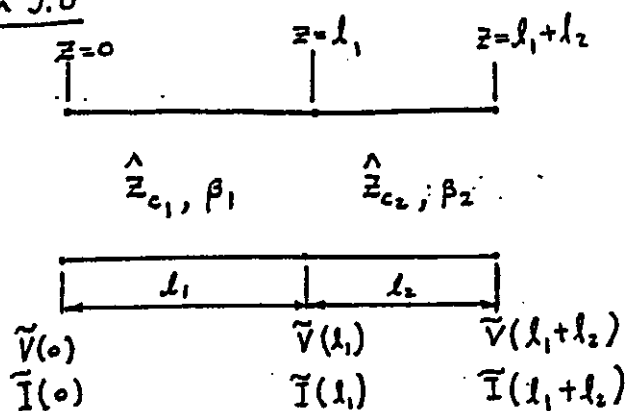

$$\begin{bmatrix} \tilde{V}(l_1) \\ \tilde{I}(l_1) \end{bmatrix} = \begin{bmatrix} \cos \beta_2 l_2 & j \hat{Z}_{c2} \sin \beta_2 l_2 \\ j \frac{1}{\hat{Z}_{c2}} \sin \beta_2 l_2 & \cos \beta_2 l_2 \end{bmatrix} \begin{bmatrix} \tilde{V}(l_1 + l_2) \\ \tilde{I}(l_1 + l_2) \end{bmatrix}$$

$$\begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} = \begin{bmatrix} \cos \beta_1 l_1 & j \hat{Z}_{c1} \sin \beta_1 l_1 \\ j \frac{1}{\hat{Z}_{c1}} \sin \beta_1 l_1 & \cos \beta_1 l_1 \end{bmatrix} \begin{bmatrix} \tilde{V}(l_1) \\ \tilde{I}(l_1) \end{bmatrix}$$

$$\begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} = \begin{bmatrix} \cos \beta_1 l_1 & j \sin \beta_1 l_1 \\ j \frac{1}{\hat{Z}_{c1}} \sin \beta_1 l_1 & \cos \beta_1 l_1 \end{bmatrix} \begin{bmatrix} \cos \beta_2 l_2 & j \sin \beta_2 l_2 \\ j \frac{1}{\hat{Z}_{c2}} \sin \beta_2 l_2 & \cos \beta_2 l_2 \end{bmatrix} \begin{bmatrix} \tilde{V}(l_1 + l_2) \\ \tilde{I}(l_1 + l_2) \end{bmatrix}$$

$$\hat{A} = \begin{bmatrix} \cos \beta_1 l_1 \cos \beta_2 l_2 - \frac{\hat{Z}_{c1}}{\hat{Z}_{c2}} \sin \beta_1 l_1 \sin \beta_2 l_2 & j \hat{Z}_{c2} \sin \beta_2 l_2 \cos \beta_1 l_1 + j \hat{Z}_{c1} \sin \beta_1 l_1 \cos \beta_2 l_2 \\ j \frac{1}{\hat{Z}_{c1}} \sin \beta_1 l_1 \cos \beta_2 l_2 + j \frac{1}{\hat{Z}_{c2}} \sin \beta_2 l_2 \cos \beta_1 l_1 & -\frac{\hat{Z}_{c2}}{\hat{Z}_{c1}} \sin \beta_1 l_1 \sin \beta_2 l_2 + \cos \beta_1 l_1 \cos \beta_2 l_2 \end{bmatrix}$$

Problem 9.9

$$l = 20 \text{ m}, f = 10 \text{ MHz}, \hat{Z}_L = 100 + j60 \Omega, L_x = 3 \times 10^{-7} \text{ H/m}, C_x = 40 \times 10^{-12} \text{ F/m}$$

$$\hat{Z}_c = \sqrt{\frac{3 \times 10^{-7}}{40 \times 10^{-12}}} = 86.6 \Omega$$

$$\beta = 2\pi \times 10 \times 10^6 \sqrt{3 \times 10^{-7} \times 40 \times 10^{-12}} = 0.218 \text{ rad/m}$$

$$\frac{l}{2} = \frac{20}{2} = 10 \text{ m}$$

$$\hat{Z}_{in}(0) = 86.6 \frac{100 + j60 + j86.6 \tan[0.218(20-10)]}{86.6 + j(100 + j60) \tan[0.218(20-10)]} = 45.81 \angle 6.77^\circ \Omega$$

$$\hat{Z}_{in}(0) = 45.49 + j5.40 \Omega$$

Problem 9.10

$$l = 90 \text{ m}, \hat{Z}_c = 50 \Omega, f = 500 \text{ kHz}, v_p = 2.8 \times 10^8 \text{ m/s}$$

$$\hat{Z}_{in}(0) = 60 - j20 \Omega,$$

$$\beta = \frac{2\pi \times 500 \times 10^3}{2.8 \times 10^8} = 1.122 \times 10^{-2} \text{ rad/m}$$

$$\hat{Z}_L = \hat{Z}_c \frac{\hat{Z}_{in}(0) - j\hat{Z}_c \tan \beta l}{\hat{Z}_c - j\hat{Z}_{in}(0) \tan \beta l}$$

$$\hat{Z}_L = 50 \frac{(60 - j20) - j50 \tan(1.122 \times 10^{-2} \times 90)}{50 - j(60 - j20) \tan(1.122 \times 10^{-2} \times 90)}$$

$$\hat{Z}_L = 56.09 + j20.75 \Omega$$

Problem 9.11

$$l = 2 \text{ m}, \quad \hat{Z}_c = 75 \, \Omega, \quad \mu_p = 2.6 \times 10^8 \text{ m/s}, \quad \hat{Z}_L = 120 + j90 \, \Omega$$

$$V_R(t) = 150 \cos(1.26 \times 10^8 t) \quad \omega = 1.26 \times 10^8 \text{ rad/s}$$

$$\beta = \frac{1.26 \times 10^8}{2.6 \times 10^8} = 4.85 \times 10^{-1} \text{ rad/m}$$

$$a) \quad \hat{\rho}_R = \frac{120 + j90 - 75}{120 + j90 + 75} = 0.469 \angle 38.68^\circ = 0.366 + j0.293$$

$$\hat{\rho}(z) = (0.469 \angle 38.68^\circ) (e^{-j2 \times 0.485(z-z)})$$

$$\hat{\rho}(z) = 0.469 e^{-j(1.265 - 0.97z)}$$

$$b) \quad 150 \angle 0^\circ = \hat{V}^+ e^{-j0.485 \times 2} (1 + 0.469 e^{j0.675})$$

$$\hat{V}^+ = 107.36 \angle 43.47^\circ \text{ V}$$

$$\tilde{V}_f = (107.36 \angle 43.47^\circ) (1 \angle -0.485 \times 2 \text{ rad}) = 107.36 \angle -12.08^\circ \text{ V}$$

$$\tilde{V}_b = \hat{\rho}_R \tilde{V}_f = (0.469 \angle 38.68^\circ) (107.36 \angle -12.08^\circ) = 50.35 \angle 26.60^\circ \text{ V}$$

$$c) \quad V_{SWR} = \frac{1 + \rho_R}{1 - \rho_R} = \frac{1 + 0.469}{1 - 0.469} = 2.766$$

$$d) \quad \hat{\rho}(0) = 0.469 e^{-j1.265} = 0.469 \angle -72.48^\circ$$

$$\tilde{V}(0) = 107.36 \angle 43.67^\circ \left[1 + 0.469 \angle -72.48^\circ \right]$$

$$\tilde{V}(0) = 131.59 \angle 22.09^\circ \text{ V}$$

$$\Delta V = V(0) - V(l) = 131.59 - 150 = -18.41 \text{ V}$$

$$e) \quad P_f(z) = \operatorname{Re} \left[\left(\hat{V}^+ e^{-j\beta z} \right) \left(\frac{\hat{V}^{+*}}{\hat{Z}_c} e^{j\beta z} \right) \right]$$

$$= \frac{V^{+2}}{Z_c} = \frac{107.36^2}{75} = 153.68 \text{ W}$$

$$P_f(z) = 153.68 \text{ W}$$

$$P_b(z) = \operatorname{Re} \left\{ \left[\hat{V}^+ e^{-j\beta z} \hat{\rho}_R e^{-j2\beta(1-z)} \right] \left[-\frac{\hat{V}^{+*}}{\hat{Z}_c} e^{j\beta z} \hat{\rho}_R^* e^{j2\beta(1-z)} \right] \right\}$$

$$= -\frac{V^{+2}}{Z_c} \rho_R^2 = -\frac{107.36^2}{75} 0.469^2 = -33.80 \text{ W}$$

$$P_b(z) = -33.80 \text{ W}$$

$$f) \quad P(0) = P_f(0) + P_b(0) = 153.68 - 33.80 = 119.88 \text{ W}$$

$$P(l) = P_f(l) + P_b(l) = 153.68 - 33.80 = 119.88 \text{ W}$$

$$\eta = \frac{P(l)}{P(0)} = \frac{119.88}{119.88} = 100\%$$

Problem 9.12

$$l = 50 \text{ m}, \quad L_l = 0.5 \mu\text{H/m}, \quad C_l = 50 \text{ pF/m}, \quad v_s(t) = 280 \cos(6.28 \times 10^7 t)$$

$$\hat{Z}_L = 250 \angle 0^\circ \Omega$$

$$a) \quad \hat{Z}_c = \sqrt{\frac{0.5 \times 10^{-6}}{50 \times 10^{-12}}} = 100 \Omega \quad \rho_R = \frac{250 - 100}{250 + 100} = 0.43$$

$$b) \quad \beta = 6.28 \times 10^7 \sqrt{0.5 \times 10^{-6} \times 50 \times 10^{-12}} = 0.314 \text{ rad/m}$$

$$\hat{\rho}(0) = \hat{\rho}_R e^{-j2\beta l} = 0.43 e^{-j2 \times 0.314 \times 50} = 0.43 e^{-j31.4}$$

$$\hat{V}^+ = \frac{280 \angle 0^\circ}{1 + 0.43 e^{-j31.4}} = 195.81 \angle -0.274^\circ \text{ V}$$

$$\tilde{V}_f(z) = \hat{V}^+ e^{-j\beta z} = (195.81 \angle -0.274^\circ) e^{-j0.314z} \quad [V]$$

$$\tilde{V}_b(z) = \hat{p}(z) \hat{V}^+ e^{-j\beta z} = (195.81 \angle -0.274^\circ e^{-j0.314z}) (0.43 e^{-j2 \times 0.314(50-z)})$$

$$\tilde{V}_b(z) = (84.2 \angle -0.274^\circ) e^{j(0.314z - 31.4)} \quad [V]$$

$$\tilde{I}_f(z) = \frac{195.81 \angle -0.274^\circ e^{-j0.314z}}{100} = 1.96 \angle -0.274^\circ e^{-j0.314z} \quad [A]$$

$$\tilde{I}_b(z) = - \frac{84.2 \angle -0.274^\circ e^{j(0.314z - 31.4)}}{100}$$

$$\tilde{I}_b(z) = -0.842 \angle -0.274^\circ e^{j(0.314z - 31.4)} \quad [A]$$

$$\begin{aligned} c) \quad P_f(z) &= \text{Re} [\tilde{V}_f \tilde{I}_f^*] \\ &= \text{Re} [(195.81 \angle -0.274^\circ e^{-j0.314z}) (1.96 \angle 0.274^\circ e^{j0.314z})] \end{aligned}$$

$$P_f(z) = 383.79 \text{ W}$$

$$\begin{aligned} P_b(z) &= \text{Re} [\tilde{V}_b \tilde{I}_b^*] \\ &= \text{Re} [(84.2 \angle -0.274^\circ e^{j(0.314z - 31.4)}) (-0.842 \angle 0.274^\circ e^{-j(0.314z - 31.4)})] \end{aligned}$$

$$P_b(z) = -70.9 \text{ W}$$

Problem 9.13

$$l = 0.42 \text{ m}, \quad l = \frac{\lambda}{4}, \quad \hat{Z}_L = 20 - j10 \, \Omega, \quad C = 50.78 \text{ pF}$$

$$i_s(t) = \sqrt{2} \cos(6 \times 10^8 t) \text{ A}$$

$$\omega = 6 \times 10^8 \text{ rad/s}, \quad \frac{\lambda}{4} = 0.42 \Rightarrow \lambda = 1.68 \text{ m}, \quad \beta = \frac{2\pi}{1.68} = 3.74 \text{ rad/m}$$

$$C_L = \frac{50.78 \times 10^{-12}}{0.42} = 1.209 \times 10^{-10} \text{ F/m}, \quad L_L = \frac{\beta^2}{\omega^2 C_L} = \frac{3.74^2}{(6 \times 10^8)^2 \times 1.209 \times 10^{-10}}$$

$$L_L = 3.214 \times 10^{-7} \text{ H/m}$$

$$\hat{Z}_c = \sqrt{\frac{3.214 \times 10^{-7}}{1.209 \times 10^{-10}}} = 51.56 \, \Omega$$

$$\hat{Z}_{in}(0) = \frac{51.56^2}{20 - j10} = 118.87 \angle 26.57^\circ \, \Omega$$

$$I_{s,rms} = \frac{\sqrt{2}}{\sqrt{2}} = 1 \text{ A} \quad \tilde{I}_s = 1 \angle 0^\circ \text{ A}$$

$$\tilde{V}_s = (1 \angle 0^\circ)(118.87 \angle 26.57^\circ) = 118.87 \angle 26.57^\circ \text{ V}$$

Problem 9.14

$$l = 7 \text{ m}, \quad \hat{Z}_G = 28 \angle -20^\circ \, \Omega, \quad \tilde{V}_R = 50 \angle 0^\circ \text{ V}, \quad \tilde{I}_R = 2 \angle 0^\circ \text{ A (rms)}$$

$$\hat{Z}_L = \frac{50 \angle 0^\circ}{2 \angle 0^\circ} = 25 \angle 0^\circ \, \Omega \quad \text{For the maximum power transfer,}$$

$$\hat{Z}_{in}(0) = \hat{Z}_G^*$$

$$\therefore \hat{Z}_{in}(0) = 28 \angle 20^\circ \, \Omega$$

$$28 \angle 20^\circ = Z_c \frac{25 + j Z_c \tan 7\beta}{Z_c + j 25 \tan 7\beta}$$

$$(26.31 + j 9.58)(Z_c + j 25 \tan 7\beta) = Z_c (25 + j Z_c \tan 7\beta)$$

$$26.31 Z_c - 23.95 \tan 7\beta = 25 Z_c \quad (1)$$

$$657.75 \tan 7\beta + 9.58 Z_c = Z_c^2 \tan 7\beta \quad (2)$$

Solving (1) and (2) simultaneously yields

$$Z_c = 28.86 \Omega \quad \text{and} \quad \beta = 0.144 \text{ rad/m}$$

Problem 9.15

$$\hat{Z}_c = 75 \Omega, \quad \hat{Z}_L = 10 - j40 \Omega$$

$$\text{Voltage reflection coefficient: } \hat{\rho}_{RV} = \frac{10 - j40 - 75}{10 - j40 + 75} = 0.813 \angle -123.2^\circ$$

$$\text{Current reflection coefficient: } \hat{\rho}_{RI} = -\hat{\rho}_{RV} = 0.813 \angle 56.8^\circ$$

Problem 9.16

$$\hat{Z}_c = 50 \Omega, \quad f = 1 \text{ MHz}, \quad \hat{Z}_{osc} = 1 \text{ M}\Omega$$

$$\hat{Z}_L = \hat{Z}_m // \hat{Z}_{osc} = \frac{\hat{Z}_m \hat{Z}_{osc}}{\hat{Z}_m + \hat{Z}_{osc}}$$

No reflection at R yields $\hat{\rho}_R = 0$,

$$\hat{\rho}_R = \frac{\hat{Z}_L - \hat{Z}_c}{\hat{Z}_L + \hat{Z}_c} = \frac{\frac{\hat{Z}_m \hat{Z}_{osc}}{\hat{Z}_m + \hat{Z}_{osc}} - \hat{Z}_c}{\frac{\hat{Z}_m \hat{Z}_{osc}}{\hat{Z}_m + \hat{Z}_{osc}} + \hat{Z}_c} = 0$$

$$\hat{Z}_m 10^6 - 50(\hat{Z}_m + 10^6) = 0 \quad \hat{Z}_m = \frac{50 \times 10^6}{10^6 - 50} \approx 50 \Omega$$

Problem 9.17

$$l = 1.2 \text{ m}, \quad \hat{Z}_{in}(0) = 120 - j80 \, \Omega, \quad \lambda = 2 \text{ m}, \quad f = 50 \text{ MHz}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{2} = \pi \text{ rad/m}$$

$$120 - j80 = Z_c \frac{Z_L + jZ_c \tan(1.2\pi)}{Z_c + jZ_L \tan(1.2\pi)}$$

$$120 Z_c + 58.08 Z_L = Z_c Z_L \quad (1)$$

$$87.12 Z_L - 80 Z_c = Z_c^2 0.726 \quad (2)$$


Solving (1) and (2) simultaneously yields,

$$Z_c = 120.51 \, \Omega$$

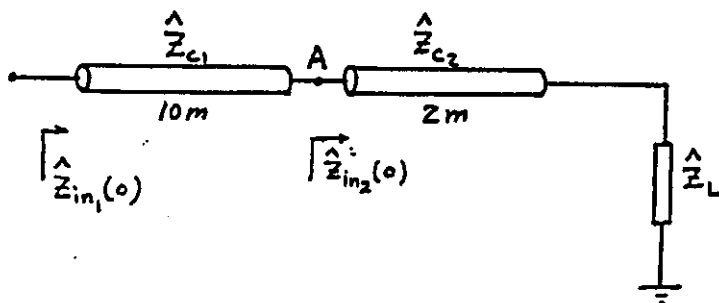Problem 9.18

$$\hat{Z}_{c1} = 50 \, \Omega, \quad l = 10 \text{ m}, \quad f = 200 \text{ kHz}, \quad \tilde{V} = 50 \angle 0^\circ \text{ V (rms)}$$

$$\hat{Z}_{c2} = 75 \, \Omega, \quad l = 2 \text{ m}, \quad \hat{Z}_L = 120 - j200 \, \Omega$$



$$a) \quad \rho_A = \frac{75 - 50}{75 + 50} = 0.2$$


$$\tau_A = 1 + \rho_A = 1 + 0.2 = 1.2$$

$$b) \quad \omega = 2\pi \times 200 \times 10^3 = 4\pi \times 10^5 \text{ rad/s}$$

$$u_{p1} = \frac{10}{36 \times 10^{-9}} = 2.78 \times 10^8 \text{ m/s}, \quad \beta_1 = \frac{4\pi \times 10^5}{2.78 \times 10^8} = 4.52 \times 10^{-3} \text{ rad/m}$$

$$u_{p2} = \frac{2}{8 \times 10^{-9}} = 2.5 \times 10^8 \text{ m/s}, \quad \beta_2 = \frac{4\pi \times 10^5}{2.5 \times 10^8} = 5.03 \times 10^{-3} \text{ rad/m}$$
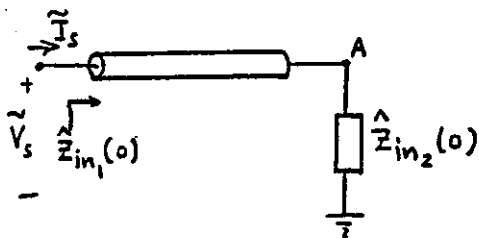
$$\hat{Z}_{in2}(0) = 75 \frac{(120 - j200) + j75 \tan(5.03 \times 10^{-3} \times 2)}{75 + j(120 - j200) \tan(5.03 \times 10^{-3} \times 2)} = 226.49 \angle -59.84^\circ \Omega$$



$$\hat{Z}_{in1}(0) = \frac{226.49 \angle -59.84^\circ + j50 \tan(4.52 \times 10^{-3} \times 10)}{50 + j(226.49 \angle -59.84^\circ) \tan(4.52 \times 10^{-3} \times 10)} = 190.02 \angle -64.55^\circ \Omega$$

$$\tilde{I}_s = \frac{50 \angle 0^\circ}{190.02 \angle -64.55^\circ} = 0.263 \angle 64.55^\circ \text{ A}$$

$$\tilde{V}_A = (50 \angle 0^\circ) \cos(4.52 \times 10^{-3} \times 10) - j(0.263 \angle 64.55^\circ) \times 50 \times \sin(4.52 \times 10^{-3} \times 10)$$

$$\tilde{V}_A = 50.48 \angle -0.29^\circ \text{ V}$$

$$\tilde{I}_A = -j \frac{1}{50} (50 \angle 0^\circ) \sin(4.52 \times 10^{-3} \times 10) + (0.263 \angle 64.55^\circ) \cos(4.52 \times 10^{-3} \times 10)$$

$$\tilde{I}_A = 0.223 \angle 59.52^\circ \text{ A}$$

Problem 9.19

$$Z_c = 50 \Omega \quad VSWR = 1.5$$

$$VSWR = \frac{1 + \rho_R}{1 - \rho_R} \quad 1.5 = \frac{1 + \rho_R}{1 - \rho_R} \Rightarrow \rho_R = 0.2$$

$$\rho_R = \frac{Z_L - 50}{Z_L + 50} = 0.2 \Rightarrow Z_L = 75 \Omega$$

With no standing waves $VSWR = 1$ or $\rho_R = 0$.

$$\text{For } \rho_R = 0 \quad Z'_L = Z_c = 50 \Omega$$

$$Z'_L = Z_L // Z_M = 50 \Rightarrow \frac{1}{75} + \frac{1}{Z_M} = \frac{1}{50} \Rightarrow Z_M = 150 \Omega$$

Problem 9.20

$$l = 10 \text{ m}, \quad f = 50 \text{ MHz}, \quad \hat{Z}_c = 80 \Omega, \quad \beta = 1.18 \text{ rad/m}, \quad Z_L = 1500 \Omega, \quad V_R = 100 \text{ V}$$

$$\tilde{I}_R = \frac{100 \angle 0^\circ}{1500} = 0.067 \angle 0^\circ \text{ A}$$

$$\tilde{V}_S = (100 \angle 0^\circ) \cos(1.18 \times 10) + j(80 \times 0.067 \angle 0^\circ) \sin(1.18 \times 10)$$

$$\tilde{V}_S = 72.14 \angle -2.94^\circ \text{ V}$$

$$V_S = 72.14 \text{ V (rms)}$$

Problem 9.21

$$\rho_R = \frac{1500 - 80}{1500 + 80} = 0.899 \angle 0^\circ$$

$$\sqrt{2} \ 72.14 \angle -2.94^\circ = \hat{V}^+ (1 + 0.899 e^{-j2 \times 1.18 \times 10})$$

$$\hat{V}^+ = 57.91 \angle -23.67^\circ \text{ V}$$

$$V(z) = 57.91 \sqrt{1 + 0.899^2 + 2 \times 0.899 \cos[2 \times 1.18(10 - z)]}$$

$$V(z) = 57.91 \sqrt{1.808 + 1.798 \cos(23.6 - 2.36z)}$$

To determine the voltage peak

$$23.6 - 2.36z = 0 \Rightarrow z = 10 \text{ m}$$

or

$$23.6 - 2.36z = 2\pi \Rightarrow z = 7.34 \text{ m}$$

$$V_{\max} = V(10 \text{ m}) = 57.91 \sqrt{1.808 + 1.798} = 109.97 \text{ V}$$

This maximum occurs at every $\lambda/2 = \frac{\pi}{1.18} = 2.66 \text{ m}$

$$I(z) = \frac{57.91}{50} \sqrt{1 + 0.899^2 - 2 \times 0.899 \cos[2 \times 1.18(10 - z)]}$$

$$I(z) = 1.16 \sqrt{1.808 - 1.798 \cos(23.6 - 2.36z)}$$

To determine the current peak

$$23.6 - 2.36z = \pi \Rightarrow z = 8.67 \text{ m}$$

or

$$23.6 - 2.36z = 3\pi \Rightarrow z = 6.0 \text{ m}$$

$$I_{\max} = I(8.67 \text{ m}) = 1.16 \sqrt{1.808 + 1.798} = 2.2 \text{ A}$$

This maximum current occurs at every half wavelength,

i.e. $\frac{\lambda}{2} = \frac{\pi}{1.18} = 2.66 \text{ m}$

Problem 9.22

$$Z_c = 75 \Omega, \text{ VSWR} = 2$$

$$2 = \frac{1 + \rho_R}{1 - \rho_R} \Rightarrow \rho_R = \frac{1}{3}$$

$$Z_{\max} = \frac{V_{\max}}{I_{\max}} = \frac{V^+ (1 + \rho_R)}{\frac{V^+ (1 - \rho_R)}{Z_c}} = Z_c \frac{1 + \rho_R}{1 - \rho_R} = 75 \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 150 \Omega$$

$$Z_{\min} = \frac{V_{\min}}{I_{\min}} = \frac{V^+ (1 - \rho_R)}{\frac{V^+ (1 + \rho_R)}{Z_c}} = Z_c \frac{1 - \rho_R}{1 + \rho_R} = 75 \frac{1 - \frac{1}{3}}{1 + \frac{1}{3}} = 37.5 \Omega$$

Problem 9.23

$$f = 10 \text{ MHz}, \quad Z_c = 55 \Omega, \quad Z_L = (R_L = 20 \Omega // C_L = 100 \text{ pF})$$

$$\hat{Z}_L = \frac{1}{\frac{1}{Z_0} + j 2\pi \times 10^7 \times 10^{-10}} = 19.69 - j 2.47 \Omega$$

$$\hat{\rho}_R = \frac{19.69 - j 2.47 - 55}{19.69 - j 2.47 + 55} = -0.471 - j 0.049 \Rightarrow \rho_R = 0.474 \angle -3.039 \text{ rad}$$

$\phi = -3.039 \text{ rad}$

$$\text{VSWR} = \frac{1 + 0.474}{1 - 0.474} = 2.8$$

$$2\beta(l - z) - \phi = 2\pi n \quad n = 0, 1, 2, 3, \dots$$

$$\text{For } n = 0: 2 \times 0.22(l - z) + 3.039 = 0 \Rightarrow l - z = -6.9 \text{ m}$$

$n = 0$ is infeasible because $l - z < 0$

$$n = 1: 2 \times 0.22(l - z) + 3.039 = 2\pi$$

$$l - z = 7.37 \text{ m}$$

Problem 9.24

$$\hat{Z}_C = 50 \Omega, \quad l = 12 \text{ m}, \quad u_p = 2.7 \times 10^8 \text{ m/s}, \quad \hat{Z}_L = 150 \Omega$$

$$v_G(t) = 25 \cos(8 \times 10^5 t) \text{ V}, \quad \hat{Z}_G = 10 - j5 \Omega$$

$$\omega = 8 \times 10^5 \text{ rad/s}, \quad \beta = \frac{8 \times 10^5}{2.7 \times 10^8} = 2.96 \times 10^{-3} \text{ rad/m}$$

$$a) \quad \hat{Z}_{in}(0) = 50 \frac{150 + j50 \tan(2.96 \times 10^{-3} \times 12)}{50 + j150 \tan(2.96 \times 10^{-3} \times 12)} = 148.5 - j14.05 \Omega$$

$$\tilde{I}_s = \frac{25 \angle 0^\circ}{10 - j5 + 148.5 - j14.05} = 0.157 \angle 6.86^\circ \text{ A}$$

$$\tilde{V}_s = \hat{Z}_{in}(0) \tilde{I}_s = 23.359 \angle 1.449^\circ \text{ V}$$

$$\hat{S}_s = \tilde{V}_s \tilde{I}_s^* = 3.642 - j0.345 \text{ VA}$$

$$P_s = 3.642 \text{ W}, \quad Q_s = -0.345 \text{ VAR}$$

$$b) \quad \hat{Z}_{in}(12 \text{ m}) = \hat{Z}_L = 150 \Omega$$

$$\tilde{V}_R = (23.359 \angle 1.449^\circ) \cos(2.96 \times 10^{-3} \times 12) - j50 \times (0.157 \angle 6.86^\circ) \sin(2.96 \times 10^{-3} \times 12)$$

$$\tilde{V}_R = 23.37 \angle 0.77^\circ \text{ V}$$

$$\tilde{I}_R = \frac{V_R}{\hat{Z}_L} = \frac{23.37 \angle 0.77^\circ}{150} = 0.156 \angle 0.77^\circ \text{ A}$$

$$\hat{S}_R = \tilde{V}_R \tilde{I}_R^* = 3.642 \text{ W}$$

$$P_R = 3.642 \text{ W}, \quad Q_R = 0$$

$$c) \hat{Z}_{in}(3m) = 50 \frac{150 + j50 \tan[2.96 \times 10^{-3}(12-3)]}{50 + j150 \tan[2.96 \times 10^{-3}(12-3)]} = 149.153 - j10.591 \Omega$$

$$\tilde{V}(3m) = (23.359 / 1.449^\circ) \cos[2.96 \times 10^{-3}(12-3)] - j50 \times 0.157 / 6.855^\circ \sin(2.96 \times 10^{-3} \times 9)$$

$$\tilde{V}(3m) = 23.368 + j0.383 \text{ V}$$

$$\begin{aligned} \tilde{I}(3m) &= 23.35 / 1.449^\circ (-j \frac{1}{50}) \sin[2.96 \times 10^{-3}(12-3)] \\ &\quad + 0.157 / 6.855^\circ \cos[2.96 \times 10^{-3}(12-3)] \end{aligned}$$

$$\tilde{I}(3m) = 0.156 + j0.006 \text{ A}$$

$$\hat{S}(3m) = \tilde{V}(3m) \tilde{I}^*(3m) = 3.642 - j0.086 \text{ VA}$$

$$P(3m) = 3.642 \text{ W}, \quad Q(3m) = -0.086 \text{ VAR}$$

$$d) \hat{Z}_{in}(9m) = 50 \frac{150 + j50 \tan[2.96 \times 10^{-3}(12-9)]}{50 + j150 \tan[2.96 \times 10^{-3}(12-9)]} = 149.905 - j3.55 \Omega$$

$$\tilde{V}(9m) = 23.359 + j0.521 \text{ V}$$

$$\tilde{I}(9m) = 0.156 + j0.015 \text{ A}$$


$$\hat{S}(9m) = \tilde{V}(9m) \tilde{I}^*(9m) = 3.642 - j0.259 \text{ VA}$$

$$P(9m) = 3.642 \text{ VA}, \quad Q = -0.259 \text{ VAR}$$

$$e) V_{drop} = V_S - V_R = 23.359 - 23.37 = -0.011 \text{ V}$$

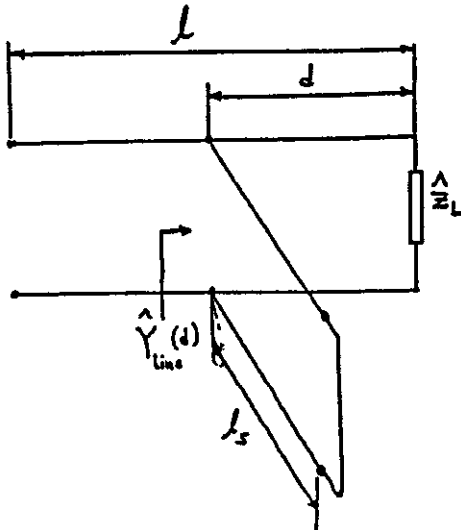Problem 9.25

$$R_c = 50\Omega, \quad l = 100\text{m}, \quad \hat{Z}_L = 40 - j100\Omega, \quad t_d = 0.5\mu\text{s}, \quad f = 20\text{MHz}$$



$$u_p = \frac{100}{0.5 \times 10^{-6}} = 20 \times 10^7 \text{ m/s}, \quad \beta = \frac{\omega}{u_p} = \frac{2\pi \times 20 \times 10^6}{2 \times 10^8} = 20\pi \times 10^{-2} \text{ rad/m}$$

$$\beta = 0.2\pi \text{ rad/m}$$

$$\hat{Y}_{line}(d) = \frac{1}{50} \frac{50 + j(40 - j100) \tan(0.2\pi d)}{(40 - j100) + j50 \tan(0.2\pi d)} = \frac{1}{50} + j \frac{1}{50 \tan(0.2\pi l_s)}$$

Solving the above equation yields,

$$d = 2.42\text{m} \quad \text{or} \quad d = 0.931\text{m} \quad \text{and} \quad l_s = 0.5\text{m}$$

Usually the shortest distance " d " to the load is preferred.

Problem 9.26

$$l = 15 \text{ m}, \quad f = 125 \text{ MHz}, \quad \hat{Z}_L = 150 + j225 \Omega, \quad d_i = 2.5 \text{ mm}, \quad d_o = 6 \text{ mm}$$


$$\epsilon_r = 2.5$$

$$L_1 = \frac{4\pi \times 10^{-7}}{2\pi} \ln \frac{3}{1.25} = 1.75 \times 10^{-7} \text{ H/m}$$

$$C_1 = \frac{2\pi \times 2.5 \times 8.85 \times 10^{-12}}{\ln \frac{3}{1.25}} = 1.59 \times 10^{-10} \text{ F/m}$$

$$Z_c = \sqrt{\frac{L_1}{C_1}} = \sqrt{\frac{1.75 \times 10^{-7}}{1.59 \times 10^{-10}}} = 33.18 \Omega$$
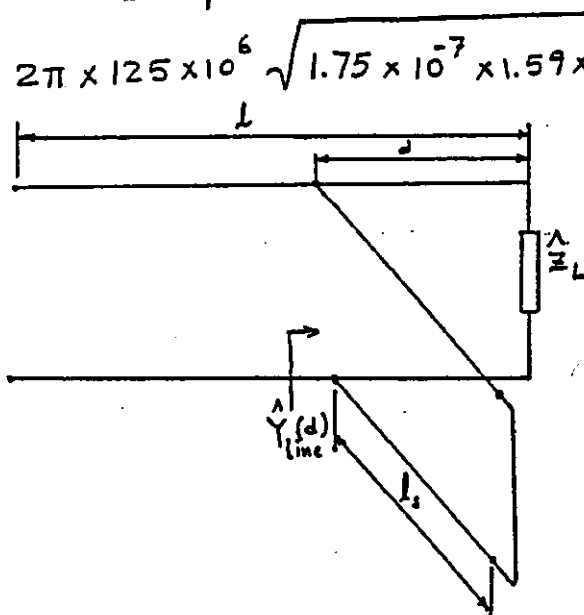
$$\beta = 2\pi \times 125 \times 10^6 \sqrt{1.75 \times 10^{-7} \times 1.59 \times 10^{-10}} = 4.14 \text{ rad/m}$$



$$\hat{Y}_{line}(d) = \frac{1}{33.18} \frac{33.18 + j(150 + j225) \tan(4.14d)}{(150 + j225) + j33.18 \tan(4.14d)} = \frac{1}{33.18} + j \frac{1}{33.18 \tan(4.14l_s)}$$

Solving the above equation yields,

$$d = 34.28 \text{ cm} \quad \text{and} \quad l_s = 6.56 \text{ cm}$$

Problem 9.27

$$l = 100 \text{ m}, r = 5 \text{ mm}, L = 150 \mu\text{H}, G = 0, C = 2000 \text{ pF}$$

$$L_l = \frac{150}{100} = 1.5 \mu\text{H/m}, C_l = \frac{2000}{100} = 20 \text{ pF/m}, R_l(f) = \frac{1}{r} \sqrt{\frac{f\mu}{\pi\sigma}}$$

$$\hat{Z}_l(f) = R_l(f) + j\omega L_l, \hat{Y}_l(f) = j\omega C_l$$

$$\hat{Z}_c = \sqrt{\frac{\hat{Z}_l(f)}{\hat{Y}_l(f)}}, \hat{\gamma} = \sqrt{\hat{Z}_l(f) \hat{Y}_l(f)} = \alpha(f) + j\beta(f)$$

$$u_p = \frac{\omega}{\beta(f)}$$

f [kHz]	R_l [Ω]	\hat{Z}_c [Ω]	$\hat{\gamma}$	α [Np/m]	β [rad/m]	u_p [m/s]
10	0.002	273.872 - j 2.413	$3.032 \times 10^{-6} + j 3.442 \times 10^{-4}$	3.032×10^{-6}	3.442×10^{-4}	1.83×10^8
10^2	0.005	273.862 - j 0.763	$9.589 \times 10^{-6} + j 0.003$	9.589×10^{-6}	0.003	1.83×10^8
10^3	0.017	273.861 - j 0.241	$3.032 \times 10^{-5} + j 0.034$	3.032×10^{-5}	0.034	1.83×10^8
10^4	0.053	273.861 - j 0.076	$9.589 \times 10^{-5} + j 0.344$	9.589×10^{-5}	0.344	1.83×10^8
10^5	0.166	273.861 - j 0.024	$3.032 \times 10^{-4} + j 3.44$	3.032×10^{-4}	3.44	1.83×10^8
10^6	0.525	273.861 - j 0.008	$9.589 \times 10^{-4} + j 34.414$	9.589×10^{-4}	34.414	1.83×10^8

Problem 9.28

$$l = 100 \text{ km}, \quad R_l = 34.63 \times 10^{-6} \Omega/\text{m}, \quad L_l = 1500 \times 10^{-9} \text{ H/m}, \quad G = 0, \quad f = 60 \text{ Hz}$$

$$C_l = 55 \times 10^{-12} \text{ F/m}, \quad P_R = 100 \text{ MW}, \quad \cos \theta = 0.9 \text{ (lagging)}, \quad V_R = 100,000 \text{ V}$$

$$a) \quad I_R = \frac{100 \times 10^6}{10^5 \times 0.9} = 1111.11 \text{ A}$$

$$\hat{Z}_l = 34.63 \times 10^{-6} + j 2\pi \times 60 \times 1.5 \times 10^{-6} = 5.665 \times 10^{-4} \angle 86.5^\circ \Omega/\text{m}$$

$$\hat{Y}_l = j 2\pi \times 55 \times 10^{-12} = 2.073 \times 10^{-8} \angle 90^\circ \text{ S/m}$$

$$\hat{Z}_c = \sqrt{\frac{\hat{Z}_l}{\hat{Y}_l}} = 165.3 \angle -1.752^\circ \Omega, \quad \hat{\gamma} = \sqrt{\hat{Z}_l \hat{Y}_l} = 1.048 \times 10^{-7} + j 3.426 \times 10^{-6}$$

$$\tilde{V}_S = 100000 \cosh[(1.048 \times 10^{-7} + j 3.426 \times 10^{-6}) \times 100 \times 10^3] - 165.$$

$$-(165 \angle -1.752^\circ) \times (1111.11 \angle -25.84^\circ) \sinh[(1.048 \times 10^{-7} + j 3.426 \times 10^{-6}) \times 100 \times 10^3]$$

$$\tilde{V}_S = 1.093 \times 10^5 \angle -34.097^\circ \text{ V} \quad \text{or} \quad \tilde{V}_S = 109.3 \angle -34.097^\circ \text{ kV}$$

$$\tilde{I}_S = -\frac{1}{165 \angle -1.752^\circ} \sinh(\hat{\gamma} l) \times 100000 + (1111.11 \angle -25.84^\circ) \cosh(\hat{\gamma} l)$$

$$\tilde{I}_S = 1066 \angle -10.785^\circ \text{ A}$$

$$\hat{S}_S = \tilde{V}_S \tilde{I}_S^* = 1.07 \times 10^8 - j 4.609 \times 10^7 \text{ VA} \quad \left| \begin{array}{l} \text{Efficiency: } \eta = \frac{P_R}{P_S} = \frac{100}{107} \\ \eta = 93.5\% \end{array} \right.$$

$$P_S = 107 \text{ MW} \quad Q_S = -46.09 \text{ MVAR}$$

$$\hat{S}_R = \tilde{V}_R \tilde{I}_R^* = 10^8 + j 4.843 \times 10^7 \text{ VA}$$

$$P_R = 100 \text{ MW}, \quad Q_R = 48.43 \text{ MVAR}$$

Voltage regulation:

$$\Delta V = \frac{|\tilde{V}_S| - |\tilde{V}_R|}{|\tilde{V}_R|} = \frac{109.3 - 100}{100}$$

$$\Delta V = 9.3\%$$

Problem 9.29

$$l = 200 \text{ m}, \quad \hat{Z}_L = \hat{Z}_{in}^{\text{dipole}} = 74 + j42.5 \, \Omega, \quad f = 90 \text{ MHz}$$

$$R_l = 1.4 \times 10^{-3} \, \Omega/\text{m}, \quad L_l = 220 \times 10^{-9} \text{ H/m}, \quad C_l = 177 \times 10^{-12} \text{ F/m}$$

$$G_l = 0.1 \, \mu\text{S/m}$$

a)

$$\omega = 2\pi f = 2\pi \times 90 \times 10^6 = 180\pi \times 10^6 \text{ rad/s}$$

$$\hat{Z}_c = \sqrt{\frac{1.4 \times 10^{-3} + j180\pi \times 10^6 \times 220 \times 10^{-9}}{0.1 \times 10^{-6} + j180\pi \times 10^6 \times 177 \times 10^{-12}}} = 35.255 - j1.808 \times 10^{-4} \, \Omega$$

$$\hat{\gamma} = \sqrt{(1.4 \times 10^{-3} + j180\pi \times 10^6 \times 220 \times 10^{-9})(0.1 \times 10^{-6} + j180\pi \times 10^6 \times 177 \times 10^{-12})}$$

$$\hat{\gamma} = 2.162 \times 10^{-5} + j3.529$$

$$\hat{Z}_{in}(0) = \hat{Z}_c \frac{\hat{Z}_L + \hat{Z}_c \tanh(\hat{\gamma}l)}{\hat{Z}_c + \hat{Z}_L \tanh(\hat{\gamma}l)} = 12.775 + j7.262 \, \Omega$$

b) $\tilde{I}_s = 10 \angle 0^\circ \text{ A}$

$$\tilde{V}_s = \hat{Z}_{in}(0) \tilde{I}_s = (12.775 + j7.262)(10 \angle 0^\circ) = 127.75 + j72.62 \text{ V}$$

$$\tilde{V}_s = 146.946 \angle 29.619^\circ \text{ V}$$

$$\tilde{V}_R = \cosh(\hat{\gamma}l) \cdot \tilde{V}_s - \hat{Z}_c \tilde{I}_s \sinh(\hat{\gamma}l) \quad \tilde{V}_R = 352.074 \angle -99.234^\circ \text{ V}$$

$$\tilde{I}_R = \frac{\tilde{V}_R}{\hat{Z}_L} = \frac{352.074 \angle -99.234^\circ}{74 + j42.5} = -2.602 - j3.202 \text{ A} = 4.126 \angle -129.10^\circ \text{ A}$$

Power delivered to the cable: $\hat{S}_s = \tilde{V}_s \tilde{I}_s^* = 1277 + j726.239 \text{ VA}$
 $P_s = 1277 \text{ W}, \quad Q_s = 726.239 \text{ VAR}$

Power transmitted by the antenna: $\hat{S}_R = \tilde{V}_R \tilde{I}_R^* = 1260 + j723.423 \text{ VA}$
 $P_R = 1260 \text{ W}, \quad Q_R = 723.423 \text{ VAR}$

Problem 9.30

$$l = 500 \text{ m}, \quad \hat{Z}_C = 50 \angle -5^\circ \Omega, \quad \alpha = 50 \times 10^{-3} \text{ dB/m}, \quad f = 2.5 \text{ MHz}$$

$$u_p = 2.3 \times 10^8 \text{ km/s}, \quad \hat{Z}_L = 200 - j300 \Omega, \quad \tilde{V}_s = 20 \angle 0^\circ \text{ V}$$

$$\alpha = \frac{50 \times 10^{-3}}{8.69} = 0.0058 \text{ Np/m}, \quad \beta = \frac{2\pi \times 2.5 \times 10^6}{2.3 \times 10^8} = 0.0683 \text{ rad/m}$$

$$\hat{\gamma} = \alpha + j\beta = 0.0058 + j0.0683 = 0.0685 \angle 85.15^\circ$$

$$\hat{Z}_{in}(0) = (50 \angle -5^\circ) \frac{(200 - j300) + (50 \angle -5^\circ) \tanh[(0.0685 \angle 85.15^\circ) \times 500]}{(50 \angle -5^\circ) + (200 - j300) \tanh[(0.0685 \angle 85.15^\circ) \times 500]}$$

$$\hat{Z}_{in}(0) = 50.211 \angle -4.834^\circ \Omega$$

$$\tilde{I}_s = \frac{\tilde{V}_s}{\hat{Z}_{in}(0)} = \frac{20 \angle 0^\circ}{50.211 \angle -4.834^\circ} = 0.398 \angle 0^\circ \text{ A}$$

$$\tilde{I}_R = -\frac{1}{50 \angle -5^\circ} (20 \angle 0^\circ) \sinh[(0.0685 \angle 85.15^\circ) \times 500]$$

$$+ (0.398 \angle 0^\circ) \cosh[(0.0685 \angle 85.15^\circ) \times 500]$$

$$\tilde{I}_R = 0.006 \angle -105.983^\circ \text{ A}$$

$$\tilde{V}_R = \hat{Z}_L \tilde{I}_R = 2.011 \angle -162.293^\circ \text{ V}$$

Power delivered to the load:

$$\hat{S}_R = \tilde{V}_R \tilde{I}_R^* = 0.006 - j0.009 \text{ VA}$$

$$P_R = 6 \text{ mW}, \quad Q_R = 9 \text{ mVAR}$$

Problem 9.32

$$l = 50 \text{ m}, \quad \hat{Z}_C = 40 \angle -5^\circ \Omega, \quad \hat{Z}_L = 280 \Omega, \quad v_g(t) = 20 \cos(6 \times 10^6 t) \text{ V}$$

$$v_s(t) = 18 \cos(6 \times 10^6 t - 12^\circ) \text{ V}, \quad \hat{Z}_G = 30 + j40 \Omega$$

a) $\tilde{V}_S = 18 \angle -12^\circ \text{ V}, \quad \tilde{V}_G = 20 \angle 0^\circ \text{ V}$

$$\tilde{V}_S = \frac{\tilde{V}_G}{\hat{Z}_G + \hat{Z}_{in}(0)} \hat{Z}_{in}(0) \Rightarrow \hat{Z}_{in}(0) = 194.485 - j56.76 \Omega$$

b) The propagation constant:

From the input-impedance, at $z=0$,

$$\tanh(\hat{\gamma}l) = \frac{\hat{Z}_C [\hat{Z}_L - \hat{Z}_{in}(0)]}{\hat{Z}_{in}(0) \hat{Z}_L - \hat{Z}_C^2} = \frac{(40 \angle -5^\circ) [280 - (194.485 - j56.76)]}{(194.485 - j56.76)(280) - 40^2}$$

$$\tanh(\hat{\gamma}l) = 0.053 + j0.053 \Rightarrow \hat{\gamma}l = 0.053 + j0.053$$

$$\hat{\gamma} = \frac{\hat{\gamma}l}{l} = 1.06 \times 10^{-3} + j1.06 \times 10^{-3}$$

c) Reflection coefficient:

$$\hat{\rho}_R = \frac{\hat{Z}_L - \hat{Z}_C}{\hat{Z}_L + \hat{Z}_C} = \frac{280 - 40 \angle -5^\circ}{280 + 40 \angle -5^\circ} = 0.751 \angle 11.456^\circ$$

$$\tilde{I}_S = \frac{\tilde{V}_S}{\hat{Z}_{in}(0)} = \frac{18 \angle -12^\circ}{194.485 - j56.76} = 0.089 \angle 4.27^\circ \text{ A}$$

$$\tilde{V}_R = \cosh(\hat{\gamma}l) \cdot \tilde{V}_S - \hat{Z}_C \tilde{I}_S \sinh(\hat{\gamma}l) \Rightarrow \tilde{V}_R = 17.854 \angle -12.548^\circ \text{ V}$$

$$\tilde{I}_R = \frac{\tilde{V}_R}{\hat{Z}_L} = \frac{17.854 \angle -12.548^\circ}{280} = 0.064 \angle -12.548^\circ \text{ A}$$

$$v_R(t) = 17.854 \cos(6 \times 10^6 t - 12.548^\circ) \text{ V}$$

$$i_R(t) = 0.064 \cos(6 \times 10^6 t - 12.548^\circ) \text{ A}$$

d.) Average power due to forward wave:

$$\hat{V}^+ = \frac{\tilde{V}_S + \hat{Z}_C \tilde{I}_S}{2} = 10.748 \angle -10.148^\circ \text{ V}$$

$$P^+(z) = \frac{1}{2} \frac{(V^+)^2}{Z_C} e^{-2\alpha z} \cos \theta_{Z_C}$$

$$P^+(z) = \frac{1}{2} \frac{(10.748)^2}{40} e^{-2 \times 1.05 \times 10^{-3} z} \cos 5^\circ$$

$$P^+(z) = 1.438 e^{-2.10 \times 10^{-3} z} \text{ W}$$

Average power due to backward wave:

$$\hat{V}^- = \tilde{V}_S - \hat{V}^+ = 7.266 \angle -14.74^\circ \text{ V}$$

$$P^-(z) = -\frac{1}{2} \frac{(V^-)^2}{Z_C} e^{2\alpha z} \cos \theta_{Z_C}$$

$$P^-(z) = -\frac{1}{2} \frac{(7.266)^2}{40} e^{2 \times 1.05 \times 10^{-3} z} \cos 5^\circ$$

$$P^-(z) = -0.657 e^{2.10 \times 10^{-3} z} \text{ W}$$

$$e) \quad P_S = P^+(0) + P^-(0) = 1.438 - 0.657 = 0.781 \text{ W}$$

$$P_R = P^+(50\text{m}) + P^-(50) = 1.295 - 0.729 = 0.566 \text{ W}$$

$$\eta = \frac{P_R}{P_S} = \frac{0.566}{0.781} = 0.7247 \Rightarrow \eta = 72.47\%$$

Problem 9.33

$$l = 25 \text{ m}, \quad L_x = 0.4 \mu\text{H/m}, \quad C_x = 45 \text{ pF/m}, \quad R_x = 8 \Omega/\text{m}, \quad G_x = 0$$

$$v_s(t) = 60 \cos(7 \times 10^6 t) \text{ V}, \quad \hat{Z}_L = 160 \Omega$$

$$\hat{Z}_c = \sqrt{\frac{8 + j 7 \times 10^6 \times 0.4 \times 10^{-6}}{j 7 \times 10^6 \times 45 \times 10^{-12}}} = 164.035 \angle -21.81^\circ \Omega$$

$$\hat{\gamma} = \sqrt{(8 + j 7 \times 10^6 \times 0.4 \times 10^{-6})(j 7 \times 10^6 \times 45 \times 10^{-12})} = 0.03 + j 0.042$$

$$a) \quad \hat{\rho}_R = \frac{\hat{Z}_L - \hat{Z}_c}{\hat{Z}_L + \hat{Z}_c} = \frac{160 - 164.035 \angle -21.81^\circ}{160 + 164.035 \angle -21.81^\circ} = 0.319 \angle 92.48^\circ \xrightarrow{1.614 \text{ rad}}$$

$$\hat{\rho}(z) = \rho_R e^{-[2\hat{\gamma}(l-z) - j\phi_R]}$$

$$\hat{\rho}(z) = 0.319 e^{-[2(0.03 + j 0.042)(l-z) - j 1.614]}$$

$$\hat{\rho}(z) = 0.319 e^{-0.06(25-z)} e^{-j[0.084(25-z) - 1.614]}$$

$$b) \quad \hat{Z}_{in}(0) = (164.035 \angle -21.81^\circ) \frac{160 + (164.035 \angle -21.81^\circ) \tanh[0.03 + j 0.042 \times 25]}{(164.035 \angle -21.81^\circ) + 160 \tanh[0.03 + j 0.042 \times 25]}$$

$$\hat{Z}_{in}(0) = 144.09 - j 117.73 \Omega$$

$$\tilde{I}_s = \frac{\tilde{V}_s}{\hat{Z}_{in}(0)} = \frac{60 \angle 0^\circ}{144.09 - j 117.73} = 0.322 \angle 39.25^\circ \text{ A}$$

$$\left. \begin{aligned} \tilde{V}_s &= \hat{V}^+ + \hat{V}^- \\ \tilde{I}_s &= \frac{\hat{V}^+}{\hat{Z}_c} - \frac{\hat{V}^-}{\hat{Z}_c} \end{aligned} \right\} \Rightarrow \begin{aligned} \hat{V}^+ &= 56.415 \angle 1.83^\circ \text{ V} \\ \hat{V}^- &= 4.035 \angle -26.438^\circ \text{ V} \end{aligned}$$

0.032 rad
-0.461 rad

Forward voltage wave:

$$\tilde{V}_f(z) = 56.415 e^{-(0.03 + j0.042)z} \cdot e^{j0.032} = 56.415 e^{-0.03z} \cdot e^{-j(0.042z - 0.032)}$$

Backward voltage wave:

$$\tilde{V}_b(z) = 4.035 e^{(0.03 + j0.042)z} \cdot e^{-j0.461} = 4.035 e^{0.03z} \cdot e^{j(0.042z - 0.461)}$$

Forward current wave:

$$\tilde{I}_f(z) = 0.344 e^{j0.032} \cdot e^{j0.617} \cdot e^{-(0.03 + j0.042)z} = 0.344 e^{-0.03z} \cdot e^{j(0.649 - 0.042z)}$$

Backward current wave:

$$\tilde{I}_b(z) = -0.0246 e^{0.03z} \cdot e^{j(0.649 + 0.042z)}$$

c) Average power due to forward wave:

$$P^+(z) = \frac{1}{2} \frac{(V^+)^2}{Z_c} e^{-2\alpha z} \cos \theta_{z_c}$$

$$P^+(z) = \frac{1}{2} \frac{56.415^2}{164.035} e^{-2 \times 0.03z} \cos 35.35^\circ$$

$$P^+(z) = 7.912 e^{-0.06z}$$

Average power due to backward wave:

$$P^-(z) = -\frac{1}{2} \frac{(V^-)^2}{Z_c} e^{2\alpha z} \cos \theta_{z_c}$$

$$\bar{P}(z) = -\frac{1}{2} \frac{4.035^2}{164.035} e^{2 \times 0.03z} \cos 35.35^\circ$$

$$\bar{P}(z) = -0.0405 e^{0.06z}$$

$$d) P_s = 7.912 - 0.0405 = 7.87 \text{ W}$$

$$P_R = 7.912 e^{-0.06 \times 2.5} - 0.0405 e^{0.06 \times 2.5} = 1.58 \text{ W}$$

$$\eta = \frac{1.58}{7.87} = 0.201 \quad \eta = 20.1\%$$

$$e) \tilde{V}_R = 56.415 e^{-0.03 \times 25} e^{-j(0.042 \times 25 - 0.032)} + 4.035 e^{0.03 \times 25} e^{j(0.042 \times 25 - 0.461)}$$

$$\tilde{V}_R = 27.688 \angle -40.39^\circ \text{ V}$$

Voltage drop : $\Delta V = 60 - 27.688 = 32.31 \text{ V}$

Problem 9.34



$$\epsilon = 3.5 \epsilon_0 \quad \mu = \mu_0 \quad \sigma_{cu} = 5.8 \times 10^7 \text{ S/m}$$

$$R_l = \frac{2}{a} \sqrt{\frac{\mu f \pi}{\sigma}} = \frac{2}{5 \times 10^{-3}} \sqrt{\frac{4\pi \times 10^{-7} \times 100 \times 10^6 \pi}{5.8 \times 10^7}} = 1.044 \text{ } \Omega/\text{m}$$

$$L_l = \frac{\mu d}{a} = \frac{4\pi \times 10^{-7} \times 0.2 \times 10^{-3}}{5 \times 10^{-3}} = 5.0265 \times 10^{-8} \text{ H/m}$$

$$C_l = \frac{\epsilon a}{d} = \frac{3.5 \times 8.85 \times 10^{-12} \times 5 \times 10^{-3}}{0.2 \times 10^{-3}} = 7.744 \times 10^{-10} \text{ F/m}$$

$$a) \hat{Z}_c = \sqrt{\frac{1.044 + j2\pi \times 10^8 \times 5.0265 \times 10^{-8}}{j2\pi \times 10^8 \times 7.744 \times 10^{-10}}} = 8.059 \angle -0.947^\circ \text{ } \Omega$$

$$b) \hat{Y} = \sqrt{(1.044 + j2\pi \times 10^8 \times 5.0265 \times 10^{-8})(j2\pi \times 10^8 \times 7.744 \times 10^{-10})}$$

$$\hat{Y} = 0.065 + j3.921 \text{ } 1/\text{m}$$

$$c) \beta = \frac{\omega}{u_p} \Rightarrow u_p = \frac{\omega}{\beta} = \frac{2\pi \times 10^8}{3.921} = 1.602 \times 10^8 \text{ m/s}$$

Problem 9.35

$$v_s = 5 \cos(6.28 \times 10^8 t) \quad , \quad \tilde{I}_R = 5 \times 10^{-3} \angle 0^\circ \text{ A}$$

$$\tilde{V}_s = 5 \angle 0^\circ \text{ V}$$

$$\tilde{I}_s = \frac{1}{\hat{Z}_c} \sinh \hat{\gamma} l \cdot \tilde{V}_R + \cosh \hat{\gamma} l \cdot \tilde{I}_R \quad (1)$$

$$\tilde{V}_R = \cosh \hat{\gamma} l \cdot \tilde{V}_s - \hat{Z}_c \sinh \hat{\gamma} l \cdot \tilde{I}_s \quad (2)$$

Substituting (2) in (1) yields

$$\tilde{I}_s = \frac{\frac{1}{\hat{Z}_c} \sinh \hat{\gamma} l \cosh \hat{\gamma} l \cdot \tilde{V}_s + \cosh \hat{\gamma} l \cdot \tilde{I}_R}{1 + \sinh^2 \hat{\gamma} l} \quad (3)$$

$$\tilde{I}_s = 0.604 \angle 5.328^\circ \text{ A}$$

$$\hat{S}_s = \frac{1}{2} \tilde{V}_s \tilde{I}_s^* = 1.503 - j 0.14 \text{ VA}$$

$$P_s = 1.503 \text{ W} \quad , \quad Q_s = -0.14 \text{ VAR}$$

Problem 9.36

$$l = 2 \text{ m} \quad , \quad r_i = 1 \text{ mm} \quad , \quad r_o = 5 \text{ mm} \quad , \quad v_s(t) = 10 \cos(5 \times 10^{10} t) \text{ V}$$

$$i_R(t) = 0.5 \cos(5 \times 10^{10} t - 10^\circ) \text{ mA}$$

$$\sigma = 5.8 \times 10^7 \text{ S/m} \quad , \quad \epsilon = 2.5 \epsilon_0 \quad , \quad \mu = \mu_0$$

$$R_l = \frac{1}{2} \sqrt{\frac{f \mu}{\pi \sigma}} \left(\frac{1}{r_i} + \frac{1}{r_o} \right) = 4.445 \Omega$$

$$L_l = \frac{\mu}{2\pi} \ln \frac{r_o}{r_i} = 3.219 \times 10^{-7} \text{ H/m} \quad , \quad C_l = \frac{2\pi \epsilon}{\ln \frac{r_o}{r_i}} = 8.638 \times 10^{-11} \text{ F/m}$$

$$\hat{Z}_C = \sqrt{\frac{4.445 + j 5 \times 10^{10} \times 3.219 \times 10^{-7}}{j 8.638 \times 10^{11} \times 5 \times 10^{10}}} = 61.046 \angle -0.0075^\circ \Omega$$

$$\hat{\gamma} = \sqrt{(4.445 + j 5 \times 10^{10} \times 3.219 \times 10^{-7})(j 8.638 \times 10^{11} \times 5 \times 10^{10})}$$

$$\hat{\gamma} = 0.036 + j 263.643 \text{ 1/m}$$

From (3) of Problem 9.35,

$$\tilde{I}_S = 0.091 \angle -79.812^\circ \text{ A}$$

$$\hat{S}_S = \frac{1}{2} \tilde{V}_S \tilde{I}_S^* = 0.08 + j 0.446 \text{ VA}$$

$$P_S = 0.08 \text{ W}$$

$$\tilde{V}_R = \cosh(\hat{\gamma} l) \cdot \tilde{V}_S - \hat{Z}_C \sinh \hat{\gamma} l \cdot \tilde{I}_S$$

$$\tilde{V}_R = 11.364 \angle 2.365^\circ \text{ V}$$

$$\hat{S}_R = \frac{1}{2} \tilde{V}_R \tilde{I}_R^* = 0.003 + j 6.084 \times 10^{-4} \text{ VA}$$

$$P_R = 0.003 \text{ W}, \quad Q_R = 6.084 \times 10^{-4} \text{ VAR}$$

$$P_{\text{loss}} = P_S - P_R = 0.077 \text{ W}$$

Problem 9.37

$$l = 350 \text{ km}, P_R = 150 \text{ MW}, V_R = 300 \text{ kV}, \cos \theta = 1, f = 60 \text{ Hz}$$

$$R_l = 0.1 \Omega/\text{km}, L_l = 1.5 \text{ mH}/\text{km}, C_l = 7.9 \text{ nF}/\text{km}, G_l = 0$$

$$a) \hat{Z}_l = \sqrt{\frac{0.1 + j 2\pi \times 60 \times 1.5 \times 10^{-3}}{j 2\pi \times 60 \times 7.9 \times 10^{-9}}} = 439.11 \angle -5.01^\circ \Omega$$

$$b) \hat{\gamma} = \sqrt{(0.1 + j 2\pi \times 60 \times 1.5 \times 10^{-3})(j 2\pi \times 60 \times 7.9 \times 10^{-9})}$$

$$\hat{\gamma} = 1.143 \times 10^{-4} + j 1.303 \times 10^{-3} \text{ 1/km}$$

$$c) \alpha_p = \frac{\omega}{\beta} = \frac{2\pi \times 60}{1.303 \times 10^{-3}} = 2.893 \times 10^5 \text{ km/s}$$

$$d) \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{1.303 \times 10^{-3}} = 4822.09 \text{ km}$$

$$e) \text{ At } l = 350 \text{ km}, V_R = 300,000 \text{ V}, I_R = \frac{150 \times 10^6}{300 \times 10^3} = 500 \text{ A}$$

$$300 \times 10^3 \angle 0^\circ = \hat{V}^+ e^{-\hat{\gamma} 350} + \hat{V}^- e^{\hat{\gamma} 350} \quad (1)$$

$$500 \angle 0^\circ = \frac{\hat{V}^+ e^{-\hat{\gamma} 350}}{439.11 \angle -5.01^\circ} - \frac{\hat{V}^- e^{\hat{\gamma} 350}}{439.11 \angle -5.01^\circ} \quad (2)$$

Solving (1) and (2) simultaneously yields

$$\hat{V}^+ = 2.701 \times 10^5 \angle 24.007^\circ \text{ V}, \quad \hat{V}^- = 4.012 \times 10^4 \angle -12.893^\circ \text{ V}$$

$$\tilde{V}_f = 2.701 \times 10^5 e^{j0.419} e^{-(1.143 \times 10^{-4} + j1.303 \times 10^{-3})z}$$

$$\tilde{V}_f = 2.701 \times 10^5 e^{-1.143 \times 10^{-4}z} e^{-j(1.303 \times 10^{-3}z - 0.419)} \text{ V}$$

where z is in km.

$$\tilde{V}_b = 4.012 \times 10^4 e^{j0.224z} (1.143 \times 10^{-4} + j1.303 \times 10^{-3})z$$

$$\tilde{V}_b = 4.012 \times 10^4 e^{1.143 \times 10^{-4}z} e^{j(1.303 \times 10^{-3}z - 0.224)} \quad V$$

where z is in km.

$$f) \quad \tilde{V}_s = \tilde{V}_f(0) + \tilde{V}_b(0)$$

$$\tilde{V}_s = 2.701 \times 10^5 \angle 24.007^\circ + 4.012 \angle -12.843^\circ$$

$$\tilde{V}_s = 3.032 \times 10^5 \angle 19.455^\circ \quad V \quad \Rightarrow \quad 303.2 \angle 19.455^\circ \text{ kV}$$

$$g) \quad \tilde{I}_s = \frac{\tilde{V}_f(0)}{\hat{z}_c} - \frac{\tilde{V}_b(0)}{\hat{z}_c}$$

$$\tilde{I}_s = 544.818 \angle 34.794^\circ \text{ A}$$

$$\hat{S}_s = \tilde{V}_s \tilde{I}_s^*$$

$$\hat{S}_s = 1.593 \times 10^8 - j4.369 \times 10^7 \text{ VA}$$

$$P_s = 159.3 \text{ MW}, \quad Q_s = -43.69 \text{ MVAR}$$

$$h) \quad \eta = \frac{P_R}{P_s}$$

$$\eta = \frac{150}{159.3} = 0.942$$

$$\eta = 94.2\%$$

Problem 9.38

For a distortionless line $R_L C_L = L_L G_L$ (1).

$$\hat{Z}_c = \sqrt{\frac{R_L + j\omega L_L}{G_L + j\omega C_L}} = \sqrt{\left(\frac{L_L}{C_L}\right) \left(\frac{\frac{R_L}{L_L} + j\omega}{\frac{G_L}{C_L} + j\omega}\right)}$$

For a distortionless line using (1) yields

$$\hat{Z}_c = \sqrt{\frac{L_L}{C_L}}$$

$$\hat{\gamma} = \sqrt{(R_L + j\omega L_L)(G_L + j\omega C_L)} = \sqrt{\left(\sqrt{R_L^2 + \omega^2 L_L^2} \left[\tan^{-1} \frac{\omega L_L}{R_L}\right]\right) \left(\sqrt{G_L^2 + \omega^2 C_L^2} \left[\tan^{-1} \frac{\omega C_L}{G_L}\right]\right)}$$

$$\hat{\gamma} = \sqrt{(R_L^2 + \omega^2 L_L^2)(G_L^2 + \omega^2 C_L^2)} \left[\tan^{-1} \frac{\omega L_L}{R_L}\right] \text{ for a distortionless line.}$$

$$\alpha = \sqrt{\sqrt{(R_L^2 + \omega^2 L_L^2)(G_L^2 + \omega^2 C_L^2)} \frac{R_L^4}{(R_L^2 + \omega^2 L_L^2)^2}} = \sqrt{\frac{R_L^4 G_L^2}{R_L^2} \frac{1 + \omega^2 \frac{C_L^2}{G_L^2}}{1 + \omega^2 \frac{L_L^2}{R_L^2}}}$$

For a distortionless line using (1) yields, $\alpha = \sqrt{R_L G_L}$

$$\beta = \sqrt{\sqrt{(R_L^2 + \omega^2 L_L^2)(G_L^2 + \omega^2 C_L^2)} \frac{\omega^4 L_L^4}{(R_L^2 + \omega^2 L_L^2)^2}} = \sqrt{\frac{\omega^4 L_L^4 \omega^2 C_L^2}{\omega^2 L_L^2} \frac{\frac{G_L^2}{\omega^2 C_L^2} + 1}{\frac{R_L^2}{\omega^2 L_L^2} + 1}}$$

For a distortionless line using (1) yields,

$$\beta = \omega \sqrt{L_L C_L}$$

Problem 9.39

$$L_\ell = 0.4 \mu\text{H/m}, \quad C_\ell = 86 \text{ pF/m}, \quad R_\ell = 11 \text{ m}\Omega/\text{m}, \quad f = 95 \text{ MHz}$$

$$\hat{Z}_c = \sqrt{\frac{L_\ell}{C_\ell}} = \sqrt{\frac{0.4 \times 10^{-6}}{86 \times 10^{-12}}} = 68.2 \Omega$$

$$\alpha = \sqrt{R_\ell G_\ell} \quad G_\ell = \frac{R_\ell C_\ell}{L_\ell} = \frac{11 \times 10^{-3} \times 86 \times 10^{-12}}{0.4 \times 10^{-6}} = 2.365 \times 10^{-6} \text{ S/m}$$

$$\alpha = \sqrt{11 \times 10^{-3} \times 2.365 \times 10^{-6}} = 2 \times 10^{-4} \text{ Np/m}$$

$$\beta = 2\pi \times 95 \times 10^6 \sqrt{0.4 \times 10^{-6} \times 86 \times 10^{-12}} = 3.5 \text{ rad/m}$$

$$\hat{\gamma} = 2 \times 10^{-4} + j 3.5$$

$$u_p = \frac{2\pi \times 95 \times 10^6}{3.5} = 1.705 \times 10^8 \text{ m/s}$$

Problem 9.40

$$l = 20 \text{ m}, \quad \hat{Z}_c = 75 \Omega, \quad t_d = 90 \text{ ns}, \quad (\alpha l)_{\text{dB}} = 0.1 \text{ dB}$$

$$\alpha l = \frac{0.1}{8.69} = 0.0115 \text{ Np}, \quad \alpha = \frac{0.0115}{20} = 5.75 \times 10^{-4} \text{ Np/m}$$

$$t_d = 90 \text{ ns}, \quad u_p = \frac{20}{90 \times 10^{-9}} = 2.22 \times 10^8 \text{ m/s}$$

$$\frac{1}{\sqrt{L_\ell C_\ell}} = 2.22 \times 10^8, \quad 75 = \sqrt{\frac{L_\ell}{C_\ell}} \Rightarrow \begin{aligned} L_\ell &= 3.378 \times 10^{-7} \text{ H/m} \\ C_\ell &= 6 \times 10^{-11} \text{ F/m} \end{aligned}$$

$$R_\ell C_\ell = G_\ell L_\ell \Rightarrow G_\ell = \frac{R_\ell C_\ell}{L_\ell}, \quad \alpha^2 = R_\ell G_\ell, \quad R_\ell = \sqrt{\frac{\alpha^2 L_\ell}{C_\ell}} = \alpha \hat{Z}_c$$

$$R_\ell = 5.75 \times 10^{-4} \times 75 = 0.0432 \Omega/\text{m}, \quad G_\ell = \frac{0.0432 \times 6 \times 10^{-11}}{3.378 \times 10^{-7}} = 7.67 \times 10^{-6} \text{ S/m}$$

Problem 9.41

$$f = 100 \text{ kHz}, \quad r_i = 1.5 \text{ mm}, \quad r_o = 3 \text{ mm}, \quad \sigma = 5.8 \times 10^7 \text{ S/m}, \quad \epsilon = 2.2 \epsilon_0$$

$$L_l = \frac{4\pi \times 10^{-7}}{2\pi} \ln \frac{3}{1.5} = 1.39 \times 10^{-7} \text{ H/m}$$

$$C_l = \frac{2\pi \times 2.2 \times 8.85 \times 10^{-12}}{\ln \frac{3}{1.5}} = 8.82 \times 10^{-11} \text{ F/m}$$

$$R_l = \frac{1}{2} \sqrt{\frac{100 \times 10^3 \times 4\pi \times 10^{-7}}{\pi \times 5.8 \times 10^7} \left(\frac{1}{1.5 \times 10^{-3}} + \frac{1}{3 \times 10^{-3}} \right)} = 1.313 \times 10^{-2} \Omega/\text{m}$$

$$G_l = \frac{1.313 \times 10^{-2} \times 8.82 \times 10^{-11}}{1.39 \times 10^{-7}} = 8.33 \times 10^{-6} \text{ S/m}$$

$$\hat{Z}_c = \sqrt{\frac{1.39 \times 10^{-7}}{8.02 \times 10^{-11}}} = 41.63 \Omega$$

$$\alpha = \sqrt{R_l G_l} = \sqrt{1.313 \times 10^{-2} \times 8.33 \times 10^{-6}} = 331 \times 10^{-4} \text{ Np/m}$$

$$\beta = 2\pi \times 100 \times 10^3 \sqrt{1.39 \times 10^{-7} \times 8.82 \times 10^{-11}} = 2.199 \times 10^{-3} \text{ rad/m}$$

$$u_p = \frac{100 \times 10^3 \times 2\pi}{2.199 \times 10^{-3}} = 2.856 \times 10^8 \text{ m/s}$$

Problem 9.42

$$l = 10\text{m}, L = 2\mu\text{H}, C = 2000\text{pF}, R_G = 10\Omega, R_L = 100\Omega$$

$$V_S = 10\text{V} \quad t_p = 1\text{ns}$$

$$a) \quad L_l = \frac{2}{10} = 0.2\mu\text{H/m}, \quad C_l = \frac{2000}{10} = 200\text{pF/m}$$

$$R_c = \sqrt{\frac{0.2 \times 10^{-6}}{200 \times 10^{-12}}} = 31.63\Omega$$



$$I_S = \frac{10}{10 + 31.63} = 0.24\text{A}$$







$$u_p = \frac{1}{\sqrt{0.2 \times 10^{-6} \times 200 \times 10^{-12}}} = 1.58 \times 10^8 \text{ m/s}$$

$$t_t = \frac{10}{1.58 \times 10^8} = 6.32 \times 10^{-8} \text{ s} \quad t_t = 63.2\text{ns}$$

$$\rho_R = \frac{100 - 31.63}{100 + 31.63} = 0.52$$

$$\rho_S = \frac{10 - 100}{10 + 100} = -0.82$$

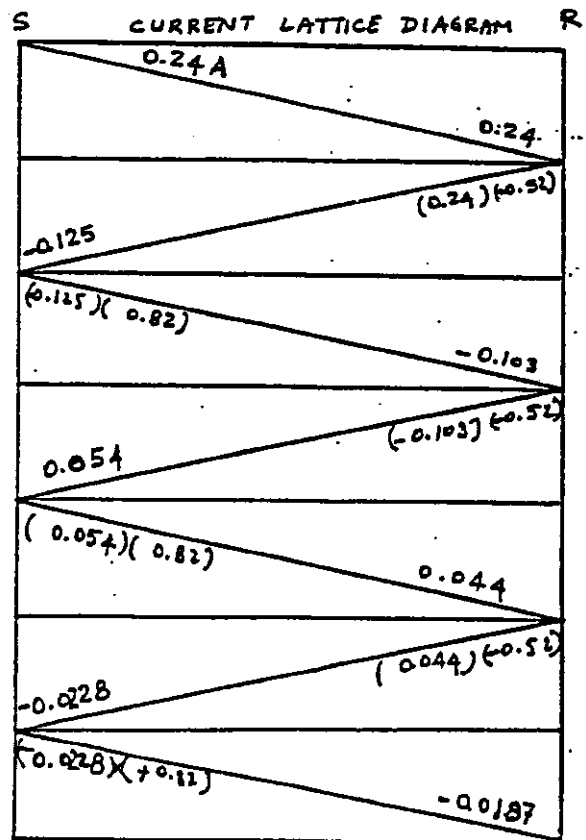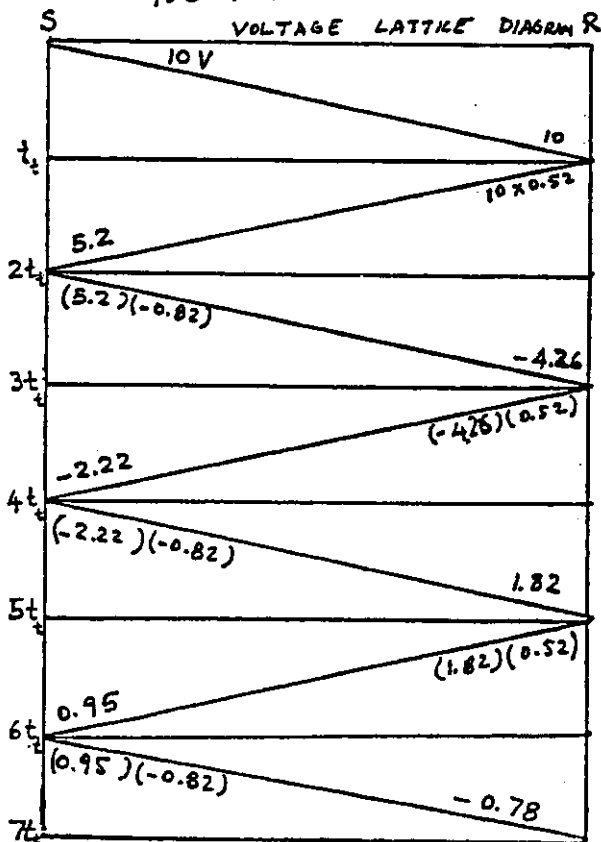

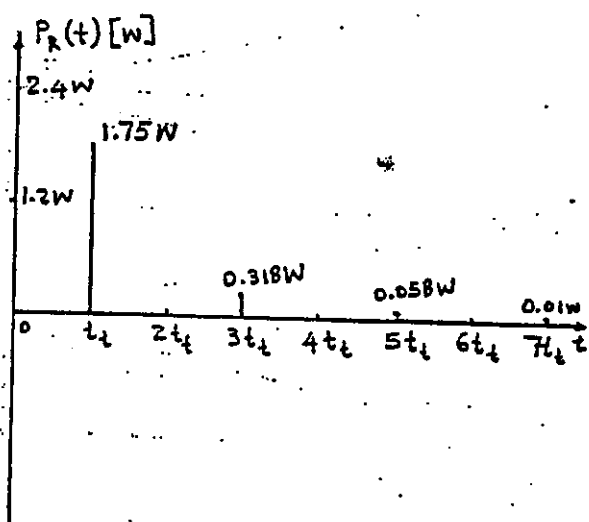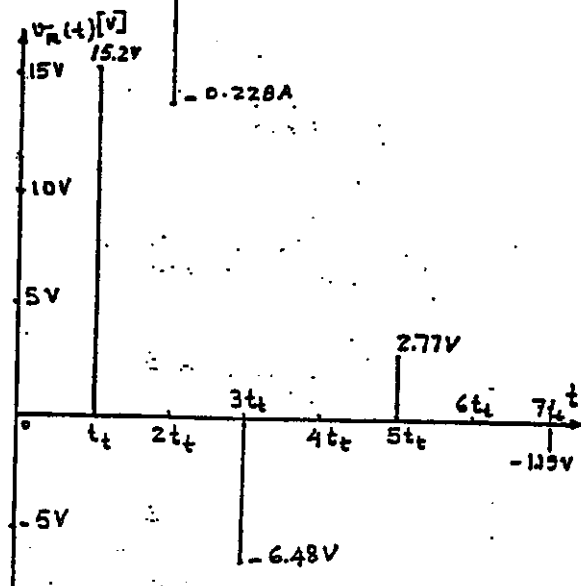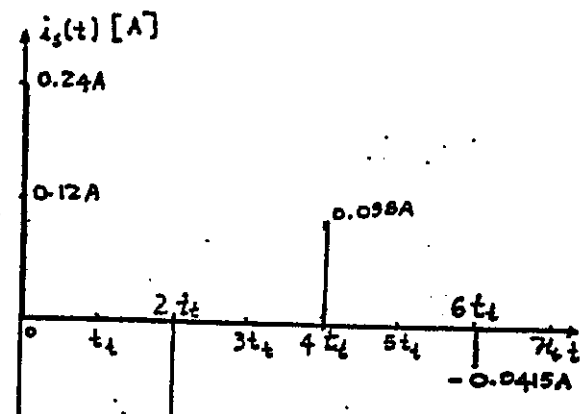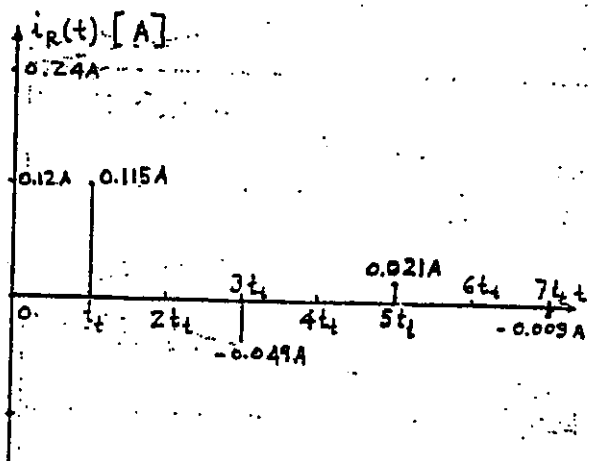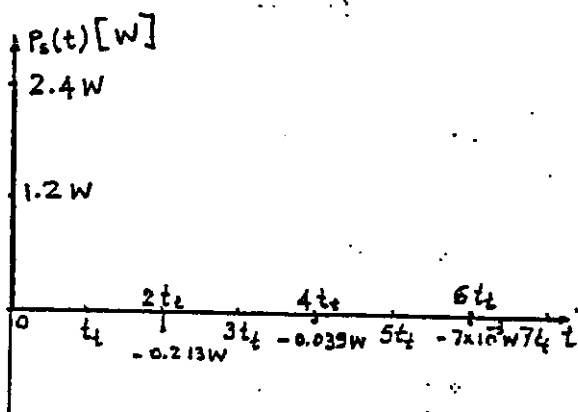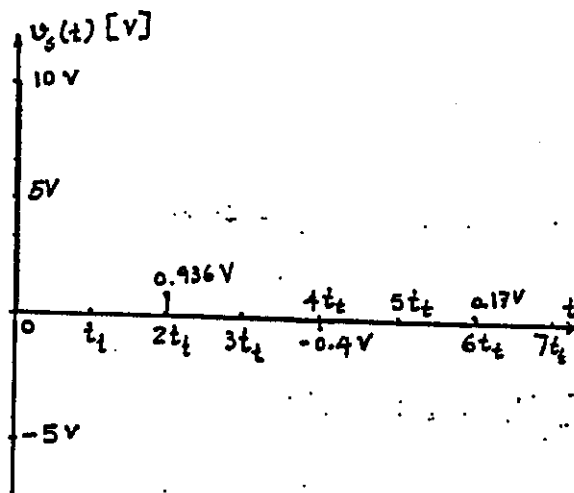

Problem 9.43



$$V_s = 100\text{V}, l = 100\text{m}, R_c = 90\Omega, R_g = 50\Omega, R_L = 250\Omega$$




$$\mu_p = 250000\text{ km/s}$$




$$I_s = \frac{100}{90} = 1.11\text{A}$$

$$t_t = \frac{100}{2.5 \times 10^8} = 4 \times 10^{-7}\text{ s} = 0.4\mu\text{s}$$

$$\rho_R = \frac{250 - 90}{250 + 90} = 0.47, \quad \rho_s = \frac{50 - 90}{50 + 90} = -0.29$$

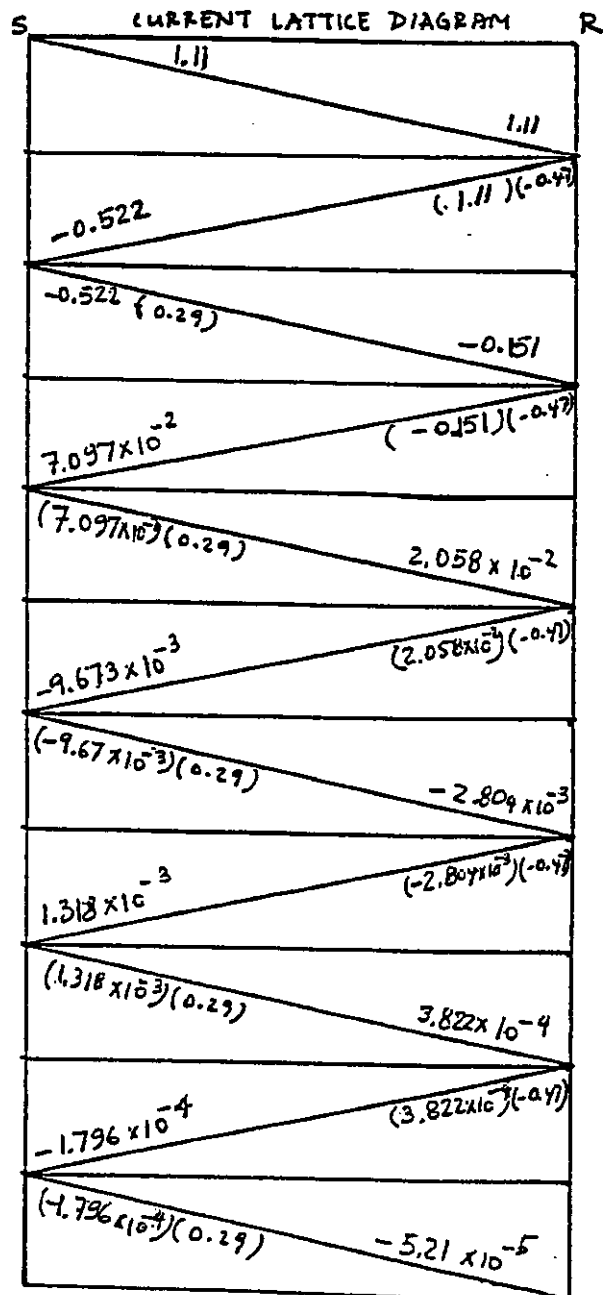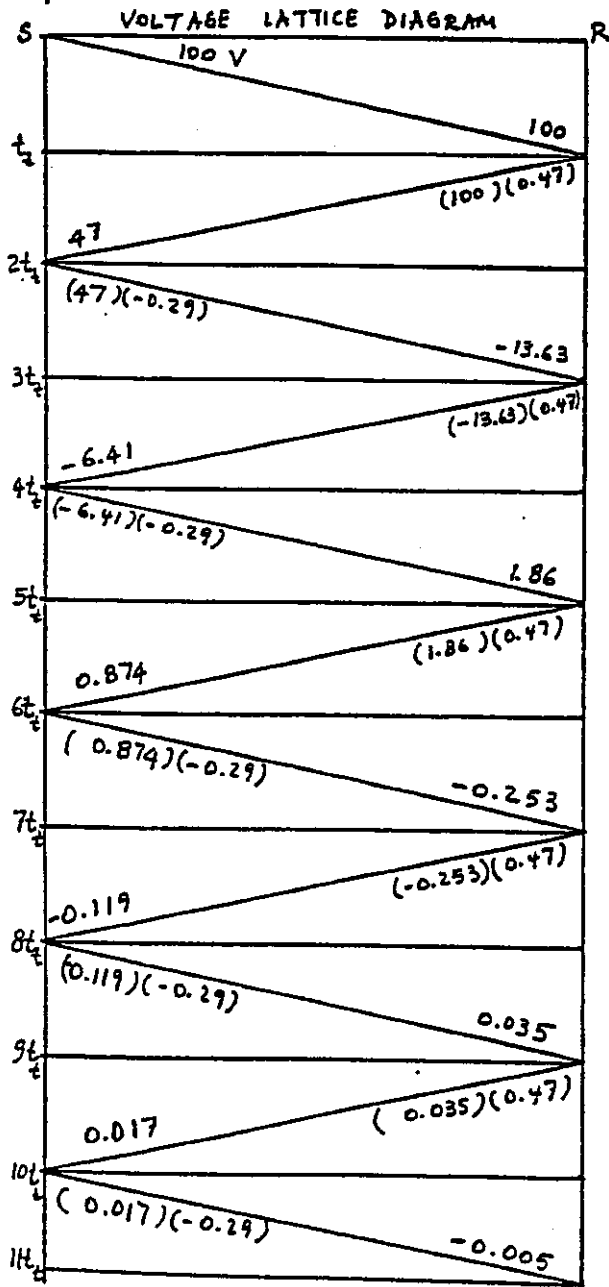

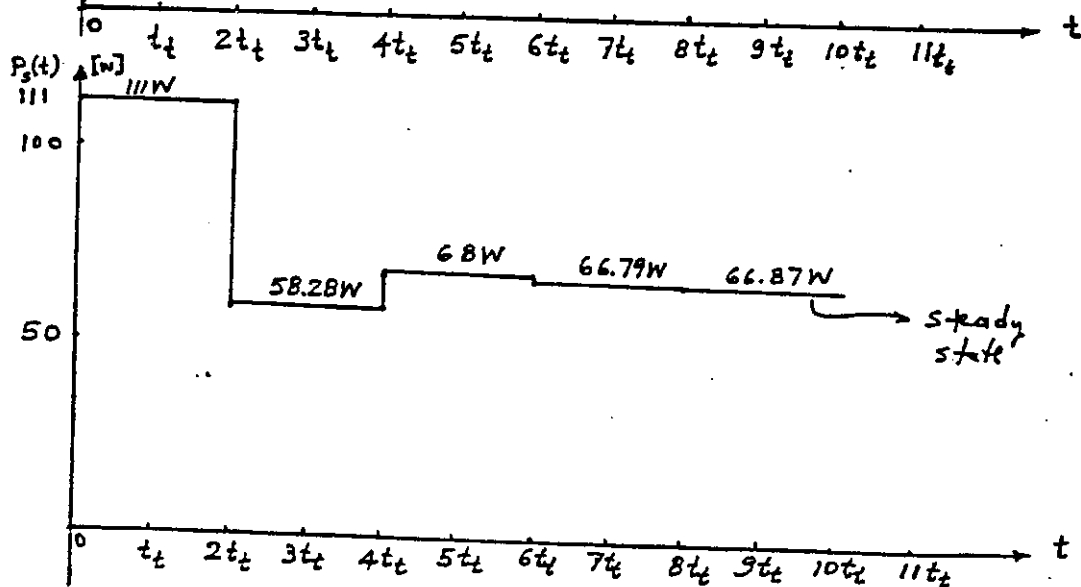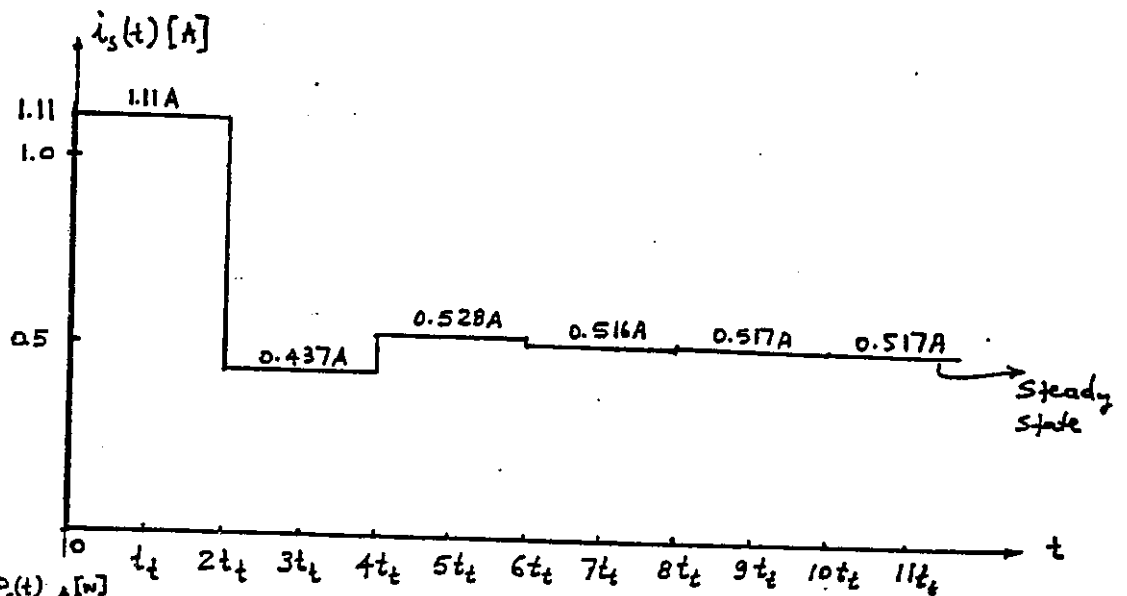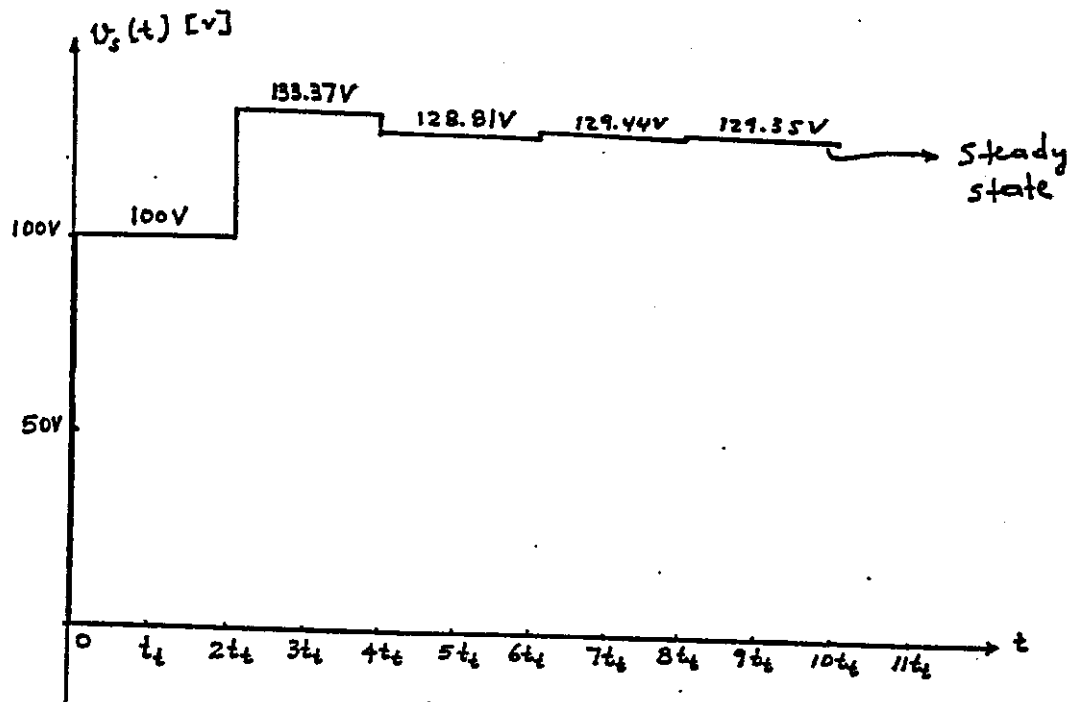

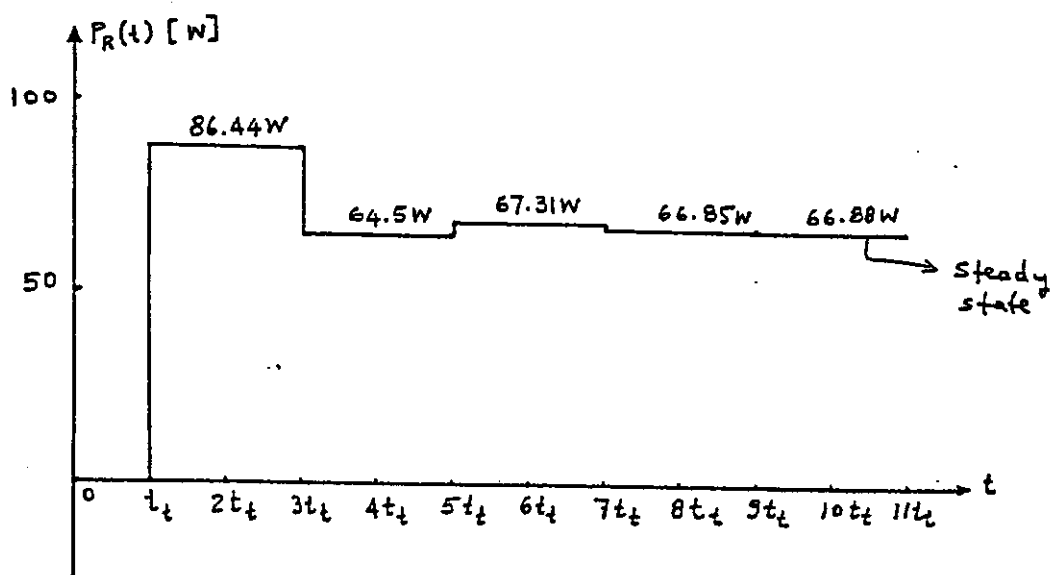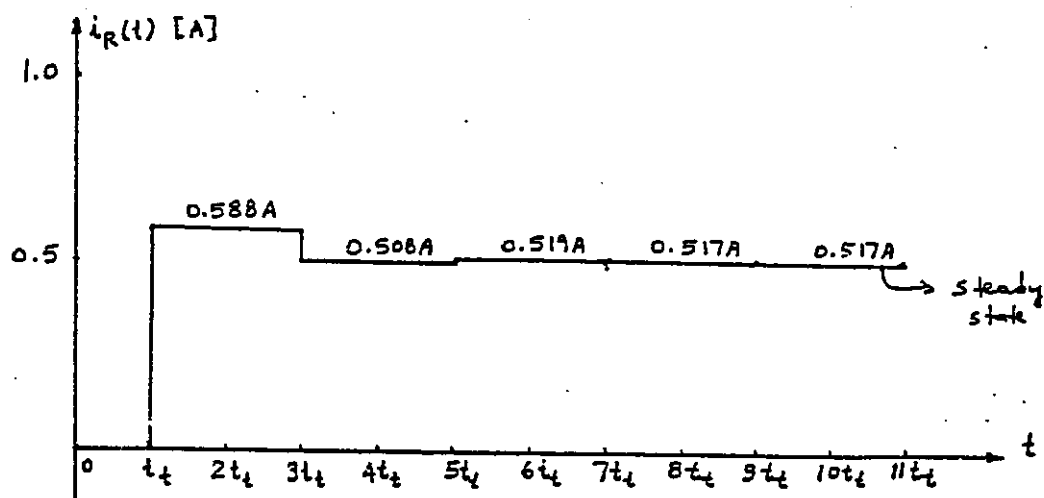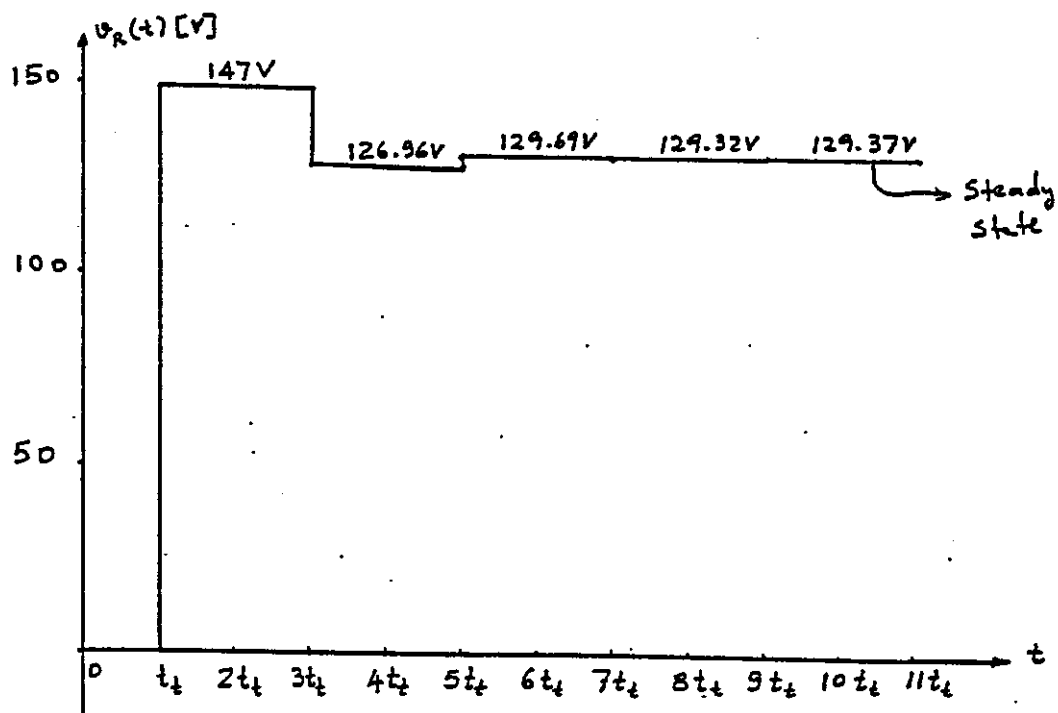

Problem 9.44


$P_L = 1 \text{ kW}$, $V_L = 120 \text{ V (dc)}$ $l = 500 \text{ m}$, $R_c = 90 \Omega$

$$V_s = 130 \text{ V} \quad , \quad R_G = 50 \, \Omega \quad \quad u_p = 210000 \text{ km/s}$$

$$t_t = \frac{500}{210000 \times 10^3} = 2.38 \times 10^{-6} \text{ s} \quad , \quad R_L = \frac{V_L^2}{P_L} = \frac{120}{1000} = 14.4 \Omega$$

$$\rho_R = \frac{4.4 - 90}{14.4 + 90} = -0.724$$

$$\rho_s = \frac{50 - 90}{50 + 90} = -0.29$$

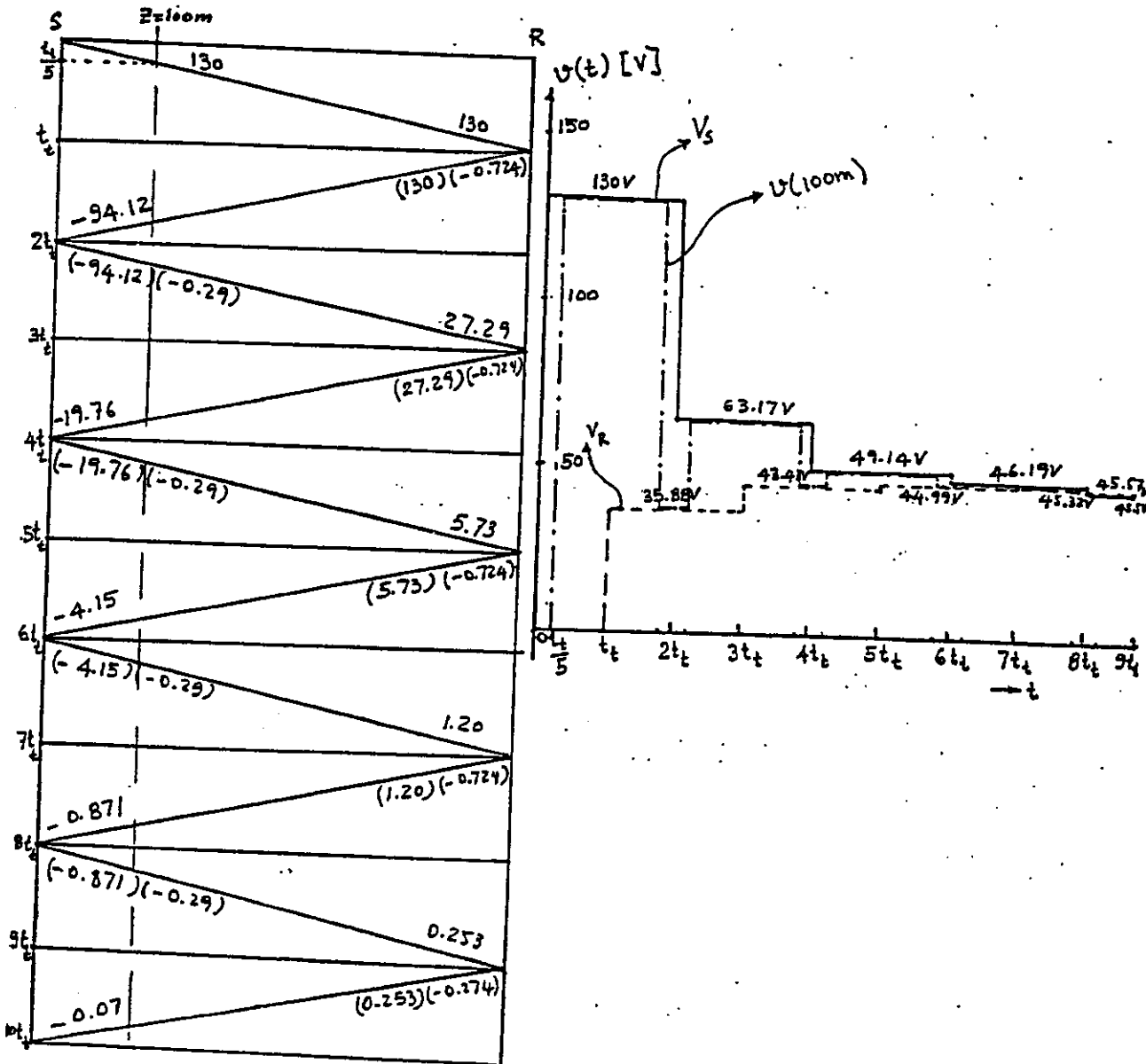


Problem 9.45



$$R_{C1} = 100\Omega, t_{t1} = 4\mu s, R_{C2} = 50\Omega, t_{t2} = 2\mu s, R_G = 50\Omega, R_L = 50\Omega$$

$$V_S = 24V \quad \rho_R = \frac{50-50}{50+50} = 0, \quad \rho_S = \frac{50-100}{50+100} = -\frac{1}{3},$$

$$\rho_1 = \frac{50-100}{50+100} = -\frac{1}{3}, \quad \tau_1 = 1 - \frac{1}{3} = \frac{2}{3} \quad \text{Towards the } 50\text{-}\Omega \text{ line.}$$

$$\rho_2 = \frac{100-50}{100+50} = \frac{1}{3}, \quad \tau_2 = 1 + \frac{1}{3} = \frac{4}{3} \quad \text{Towards the } 100\text{-}\Omega \text{ line.}$$

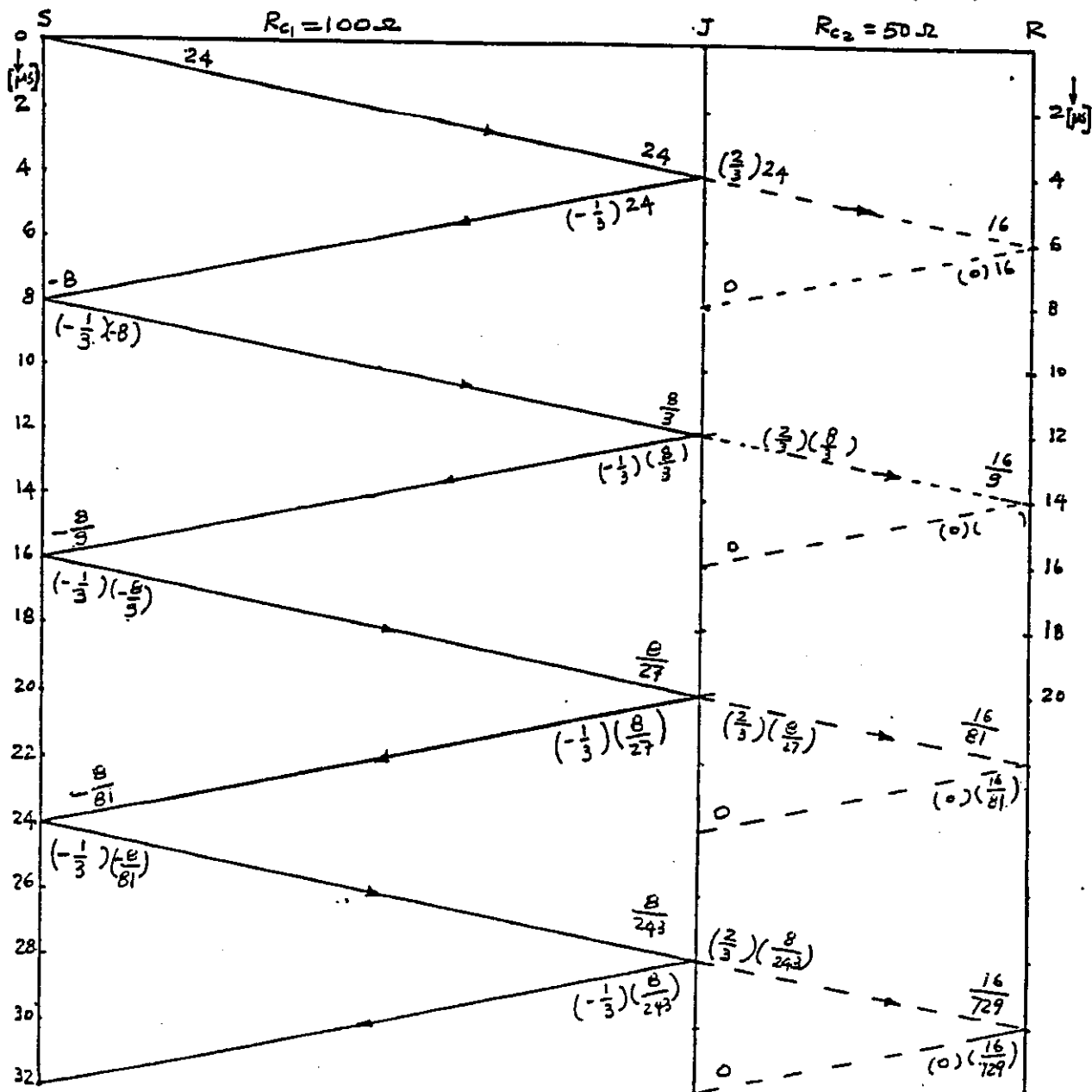

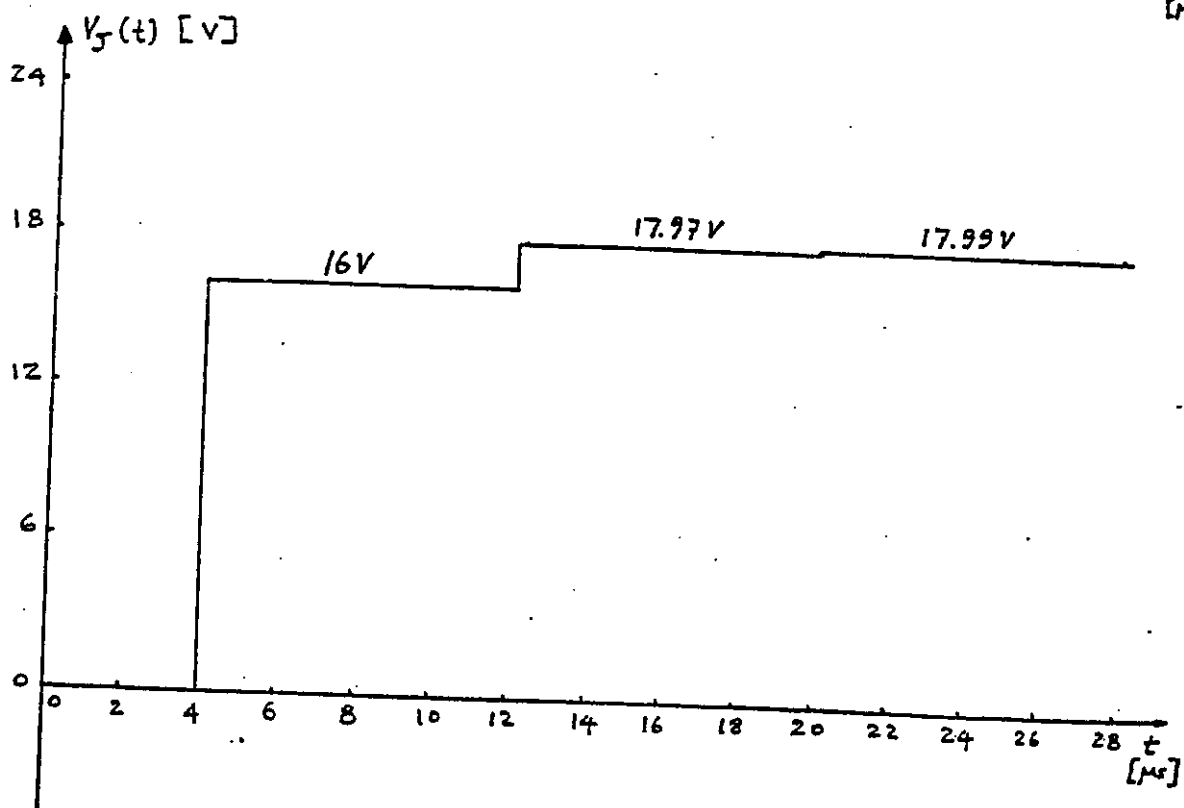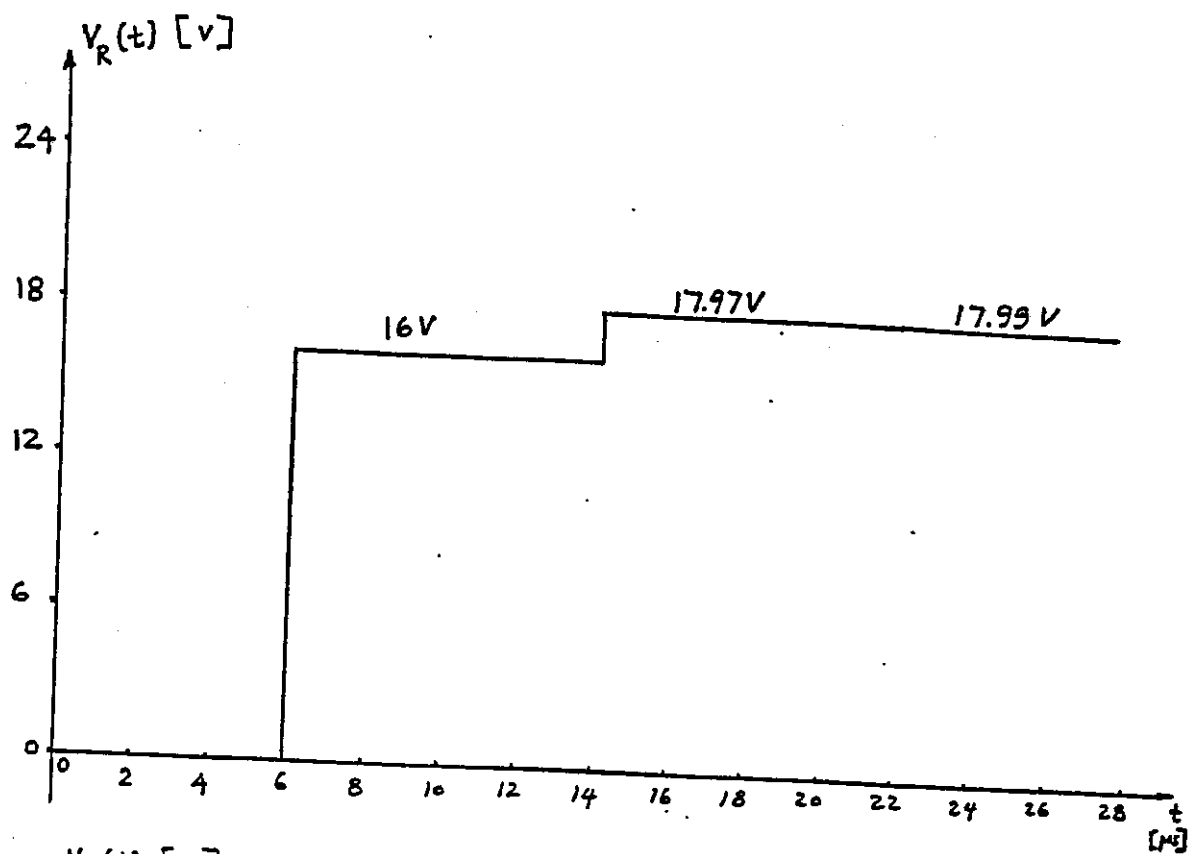

Problem 9.46

$d = 4 \text{ mm}$, $f = 100 \text{ Hz}$, 1 kHz , 10 kHz , 100 kHz , 1 MHz , 10 MHz , 100 MHz , 1 GHz , $\mu = 4\pi \times 10^{-7} \text{ H/m}$, $\sigma = 5.8 \times 10^7 \text{ S/m}$

$$a = \frac{d}{2} = 2 \text{ mm}$$

$$R_{ci} = \frac{1}{2 \times 10^{-3}} \sqrt{\frac{4\pi \times 10^{-7} f}{4\pi \times 5.8 \times 10^7}} = 2.076 \times 10^{-5} \sqrt{f}$$

$$R_{ci} = 2.076 \times 10^{-5} \sqrt{f}$$

$$L_{ci} = \frac{R_{ci}}{2\pi f} = \frac{2.076 \times 10^{-5} \sqrt{f}}{2\pi f} = 3.304 \times 10^{-6} \frac{1}{\sqrt{f}}$$

$f [\text{Hz}]$	$R_{ci} [\frac{\Omega}{\text{m}}]$	$L_{ci} [\text{H/m}]$
100	2.076×10^{-4}	3.304×10^{-7}
10^3	6.565×10^{-4}	1.045×10^{-7}
10^4	2.076×10^{-3}	3.304×10^{-8}
10^5	6.565×10^{-3}	1.045×10^{-8}
10^6	2.076×10^{-2}	3.304×10^{-9}
10^7	6.565×10^{-2}	1.045×10^{-9}
10^8	2.076×10^{-1}	3.304×10^{-10}
10^9	6.565×10^{-1}	1.045×10^{-10}