 




# Asynchronous Circuits

## Races, Cycles and Effect of Hazards



*"All circuits have problems, but asynchronous circuits have more problems"*



## Feedback in Digital Circuits

### The Difference Between Asynchronous and Synchronous Feedback

- Synchronous feedback must wait for for the clock.
- Input signals must not change when the clock does.
- Always behave like the state table says
  
- Asynchronous feedback comes immediately with only gate delays.
- Inputs can come at any time.
- Circuits may not behave as the state table says.


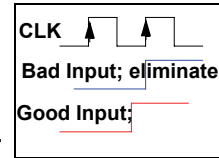



FIG. 2-1 Illustrates synchronous and asynchronous feedback

 



**The 3 Forms of Asynchronous Feedback**

**FIG. 2-2** The three ( one is fake ) forms of asynchronous feedback circuits

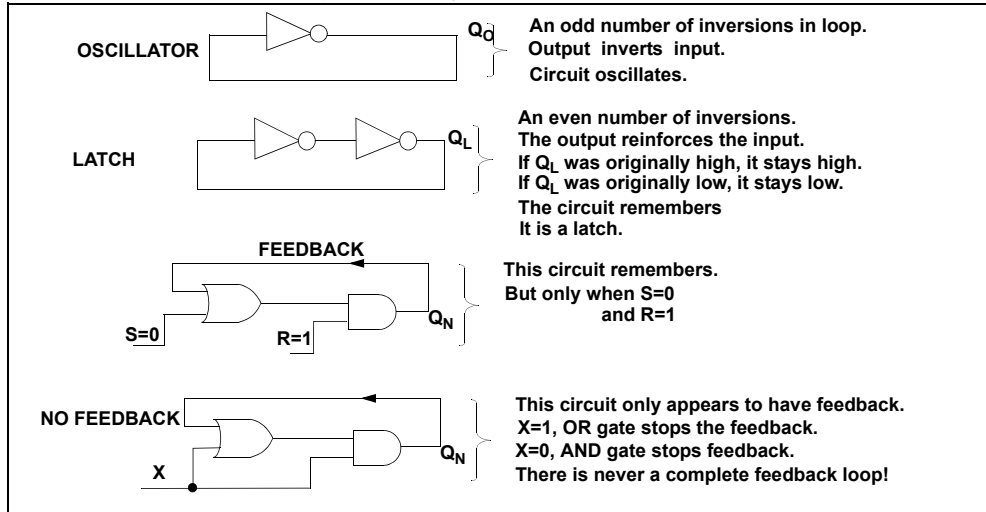

Asynchronous feedback circuits *oscillate* or *remember*.

They *oscillate* if the feedback loop has an odd number of inversions.


They *remember* if the feedback loop has an even number of inversions.



**Sensitized Paths**

A signal path is *sensitized* if a change in its input changes its output.


**FIG. 2-3** Sensitized and unsensitized paths

 

A feedback path must be sensitized for the circuit to remember/oscillate

In practical circuits, the feedback is only *sensitized* part of the time.

**FIG. 2-4** Apparent feedback path is never *sensitized*

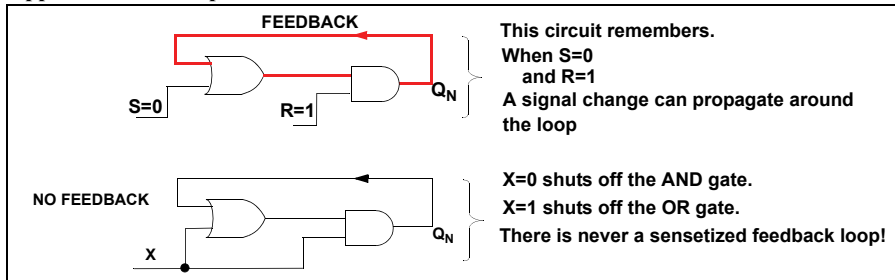




## Analysis of Asynchronous Circuits

### Review of Synchronous State Machines


The state is the collective output of all flip-flops and latches.  
 The next state is the state after the clock edge.

FIG. 2-5 A state machine using D flip-flops.

 

A state machine is defined by its *next state table*.

FIG. 2-6 State Graph and Next State Table for a Mythological Circuit.

 


### State Variables For Asynchronous Circuits

**In synchronous circuits (with D flip-flops)**  
 Each flip-flop remembers one bit.  
 Each flip-flop holds a state variable.  
 The present state is the flip-flop output(s) "A"  
 The next state is the the D input(s), "a<sup>+</sup>"

**In asynchronous circuits**  
 Each feedback loop latches one bit  
 Each feedback loop holds a state variable.  
 The state is the value fed back to the input.  
 The next state is value out of the gate.

In Asynchronous circuits the state is value on the feedback lead.  
 Mark an **X** on the wire where you want to read the state.  
 Write "A", the present state on the output side.  
 Write "a<sup>+</sup>", the next state, on the input side.

FIG. 2-7 Synchronous and asynchronous state variables

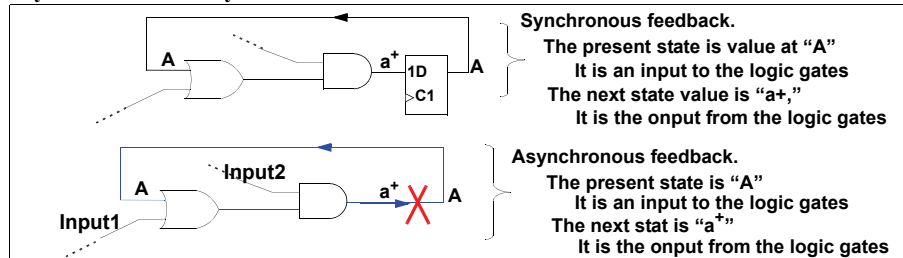

In steady state, the asynchronous present state = next state,  $A = a^+$   
 On an input change,  $a^+$  may change.  
 This will immediately change A and give a new state.



**Relation Between "A" and "a<sup>+</sup>"**

**FIG. 2-8 Delay separates a<sup>+</sup> and A**

Very small delay in wire

Very small delay in wire

Very small delay in wire

**Asynchronous feedback model.**

a<sup>+</sup> comes out of circuit.  
After a short delay it reenters the circuit as A  
A travels through the sensitized path and emerges as a<sup>+</sup>.

The state A is continuously regenerated by a<sup>+</sup>  
a<sup>+</sup> is continuously recalculated from A and inputs

An input change may change a<sup>+</sup>.  
After the wire delay this will change A.  
A will stay in this new state until an input changes a<sup>+</sup> again.

We usually put an X on the schematic to show where a<sup>+</sup> changes to A.  
Should the X be at X<sub>1</sub> or X<sub>2</sub>?\*

\* The X is thinking point where a<sup>+</sup> changes to A. It can be anywhere in the feedback path



**Where To Put The Loop Breaks**

**FIG. 2-9 Break each independent feedback loop with an X (push button).**  
An independent feedback loop can store one bit.

two loops both broken.

**FIG. 2-10 Sometimes two independent loops are really one**  
Then cut them with one X.

One independent feedback loop which looks like two.

**FIG. 2-11 Extra breaks:**  
Analysis will still work with several breaks in one loop.  
Adds unnecessary states, make more work.  
When in doubt, use extra breaks.

One feedback loop.  
An unnecessary extra break.



## Analysis of an Asynchronous Circuit

### Tracing the Signals

A typical analysis:

1. Break the feedback loops at the appropriate places, A and B in FIG. 2-12.
2. Write equations relating the values on the input side of the break ( $a^+$  and  $b^+$ ) with values on the output side (A, B) and the inputs (s).

That is  $a^+ = f(A,B,s)$ ,  
 $b^+ = g(A,B,s)$ .

3. Make a state table.

FIG. 2-12 A Sample Circuit For Analysis.

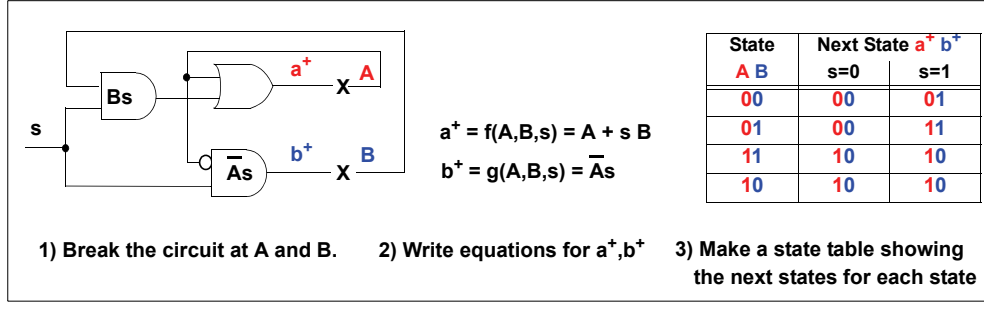


FIG. 2-13 Tracing State Changes on the Sample Circuit.

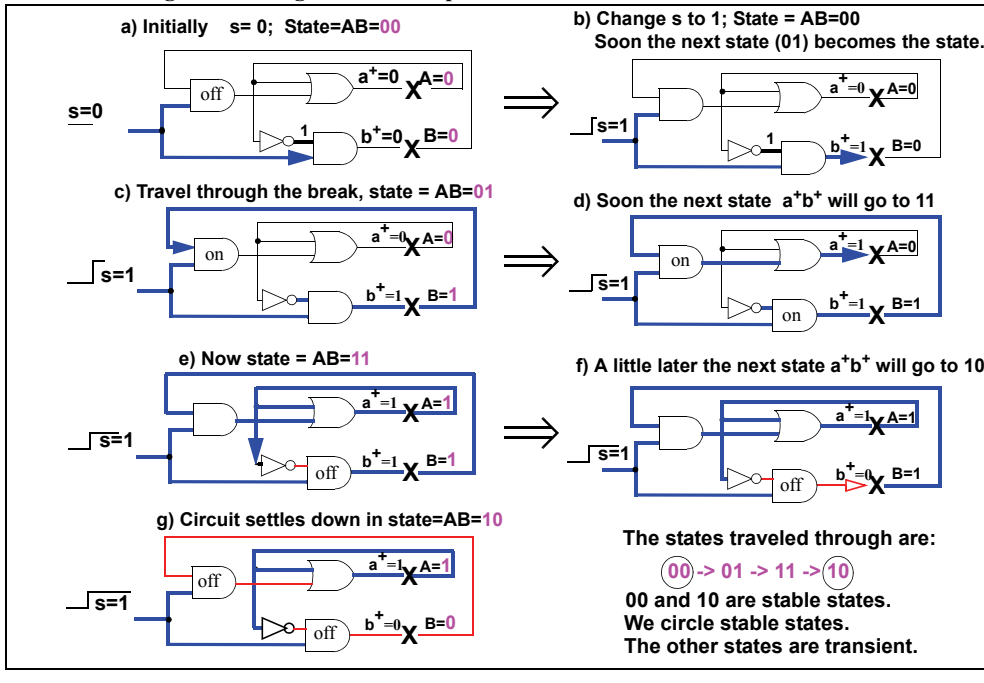




FIG. 2-14 Tracing State Changes on the Next State Table.

State A B	Next State a <sup>+</sup> b <sup>+</sup>	
	s=0	s=1
00	00	01
01	00	11
11	10	10
10	10	10

Stable states:  
where next state = present state.  
are circled

Transient intermediate states:  
all other states

**Analysis**  
Start and end on stable states.  
Travel on the next state side of table.  
Path through next states is the same as  
the path through the present states.  
States traveled through when s rises 0 → 1.

00 → 01 → 11 → 10

### Delays and the Sample Circuit

- The sequence of state changes is independent of the circuit delays.
- With random delays on all gates and all wires, the states would still change 00 → 01 → 11 → 10
- Be sure s does not change again until the final stable state is reached.
- This circuit is *delay Independent*.


Not all circuits are this well behaved.




## Circuits Where Delays Matter

### Circuits with Races

FIG. 2-15 Circuit where state changes depend on delays

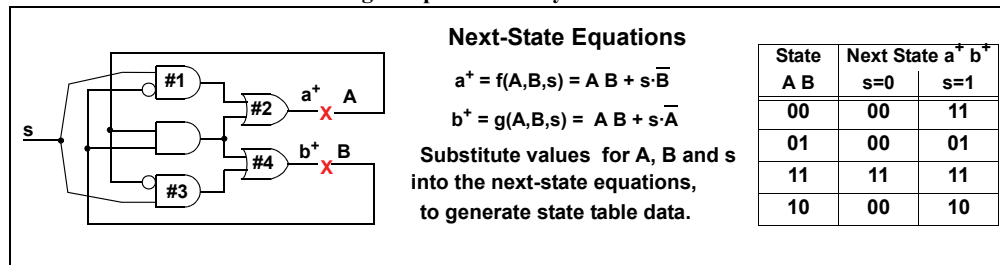


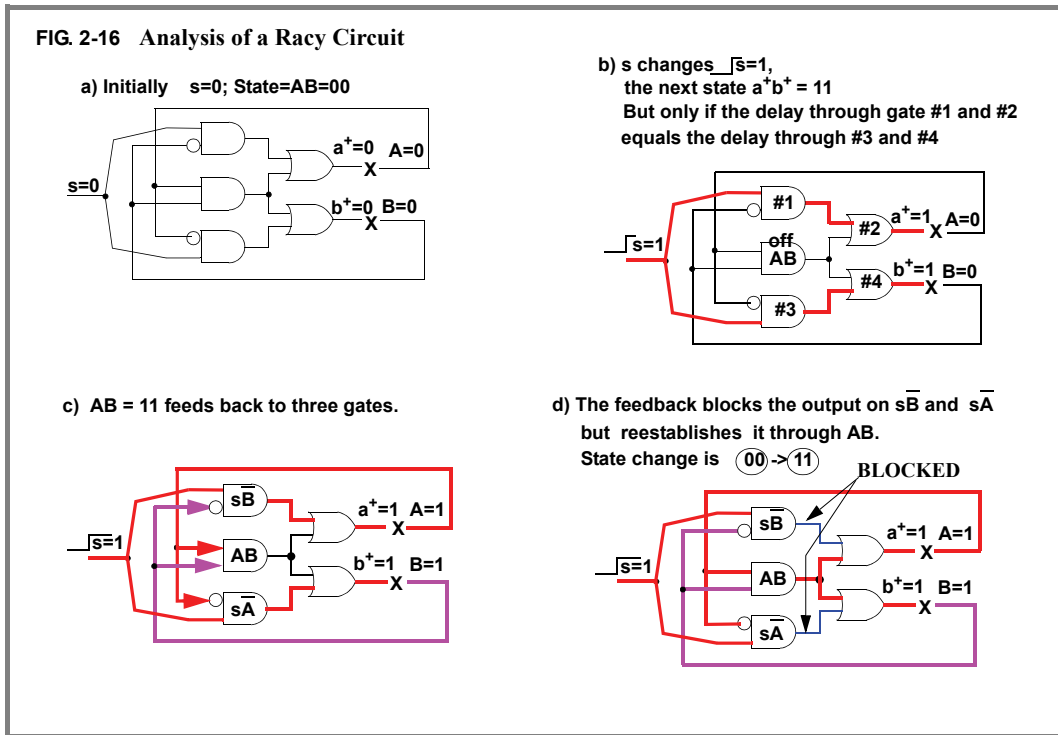
- This circuit does not always behave like the state table
- The sequence of states passed through depends on delays
- We will see:
  - if #1 and #2 are faster, ends in state 10
  - if #3 and #4 are faster, end in state 01,
  - if they are equal, end in state 11.
- The circuit has a *race*.



© John Knight

Electronics Department, Carleton University

March 26, 2009

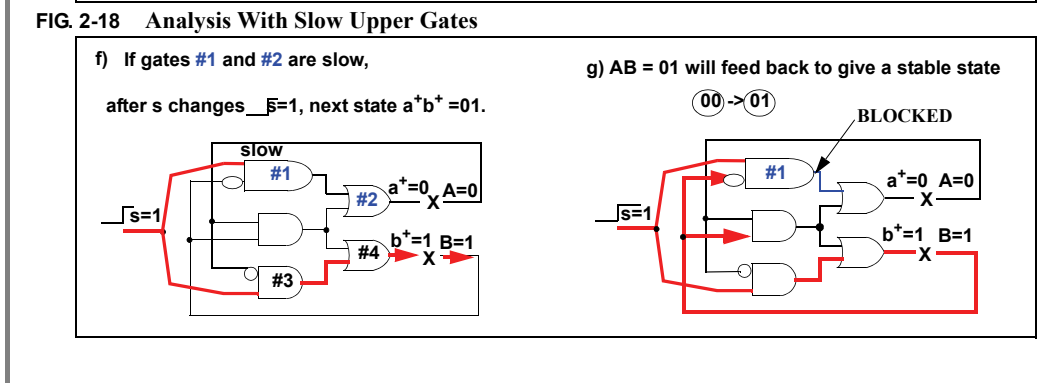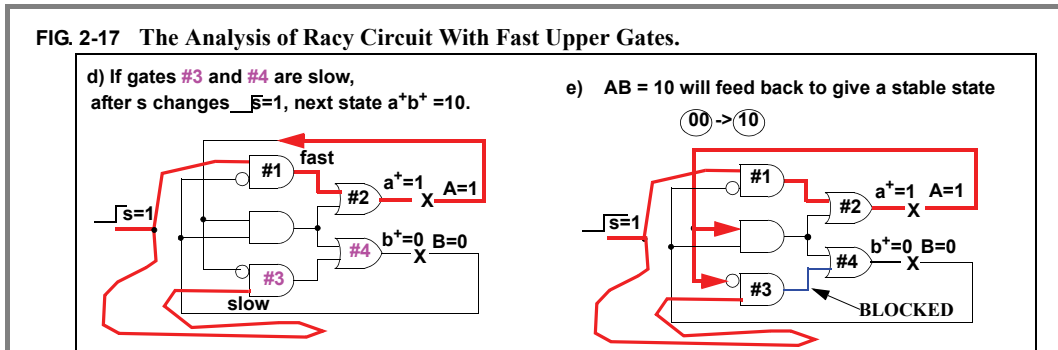

© John Knight

Electronics Department, Carleton University

March 26, 2009



**Analysis of A Racy Circuit Using A State Table**

Get next-state equations from the circuit.  
Use them to build a state table.

Note any two-bit change in the state.  
when in state 00,  
s goes 0 1  
next state is 11

Identify races by:  
A two-bit (or more) change in a state variable.

The possible results from the double-bit change is shown in FIG. 2-20.

FIG. 2-19 State-Table and Equations for the Racy Circuit in FIG. 2-17.


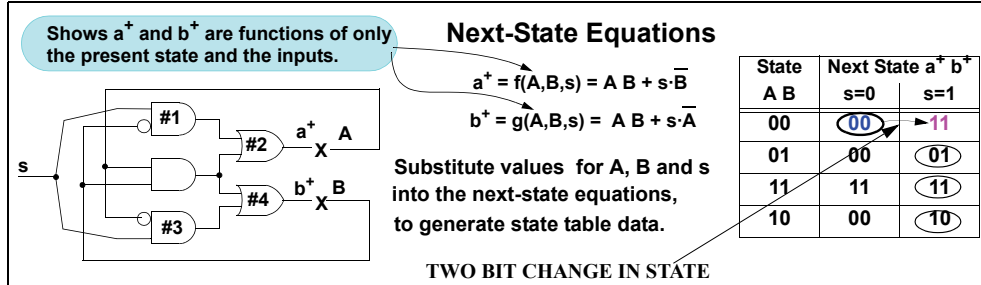


FIG. 2-20 The Three Possible Outcomes of the Race in the Racy Circuit.

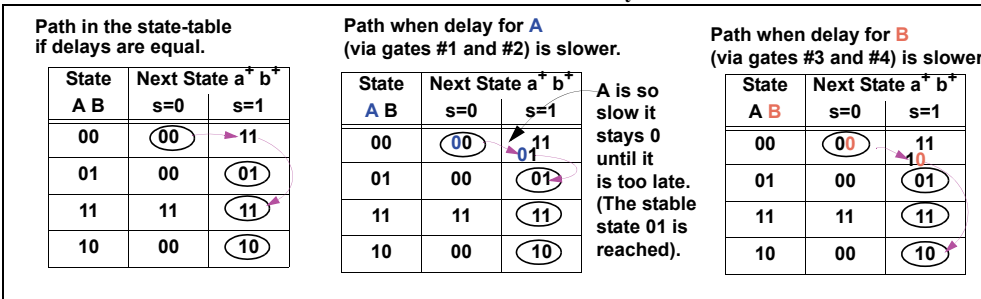

If gates #1 and #2 are fastest, the stable next state will be AB=10.

If gates #3 and #4 are fastest, the stable next state will be AB=01.

With equal delays, the stable next state will be AB=11.

**Races Have a Simultaneous Two-Bit Change in the State Variables**

Look for double-bit change in a state variables, and you will find the races.



**Noncritical, and Other Non-important Races.**

Not all races are a problem:

**Noncritical Races**  
 Some races take different paths but end in the same final stable state.  
 These are called *noncritical races*. FIG. 2-21 and FIG. 2-22

**Unused Races ("Who Cares" Races)**  
 Some races are in a part of the state table which is never used. FIG. 2-23

**Races To Equivalent States (States that could be merged)**  
 The final states of the race might be equivalent.  
 The machine would externally behave the same no matter how the race came out.



**FIG. 2-21 A Noncritical Race With Three Paths.**

**Next-State Equations**  
 $a^+ = f(A,B,s) = B + s\bar{A}$   
 $b^+ = g(A,B,s) = s + B\bar{A}$

State A B	Next State a <sup>+</sup> b <sup>+</sup>	
	s=0	s=1
00	00	11
01	11	11
11	10	11
10	00	01

A slow B slow

**FIG. 2-22 The Three Possible Paths Individually Shown.**

Path for equal delays.

State A B	Next State a <sup>+</sup> b <sup>+</sup>	
	s=0	s=1
00	00	11
01	11	11
11	10	11
10	00	01

Gates #1 and #2 are slower.  
Then A is slower than B

State A B	Next State a <sup>+</sup> b <sup>+</sup>	
	s=0	s=1
00	00	11
01	11	11
11	10	11
10	00	01

A is slow so next state becomes 01

Gates #3 and #4 are slower.  
Then B is slower than A

State A B	Next State a <sup>+</sup> b <sup>+</sup>	
	s=0	s=1
00	00	11
01	11	11
11	10	11
10	00	01


**The race is noncritical.  
All paths lead to state 11**



**A “Who Cares” Race.**

This Race is in state 01 as  $s$  changes  $\rightarrow$ .  
 The stable states and all the transitions between them are shown.  
 The “Who Cares” race is between unstable states.  
 Further, no useful transition goes through it.  
 The circuit does not use the transition.  
 No one cares if it has a race.

FIG. 2-23 A Circuit With a “Who Cares” Race.

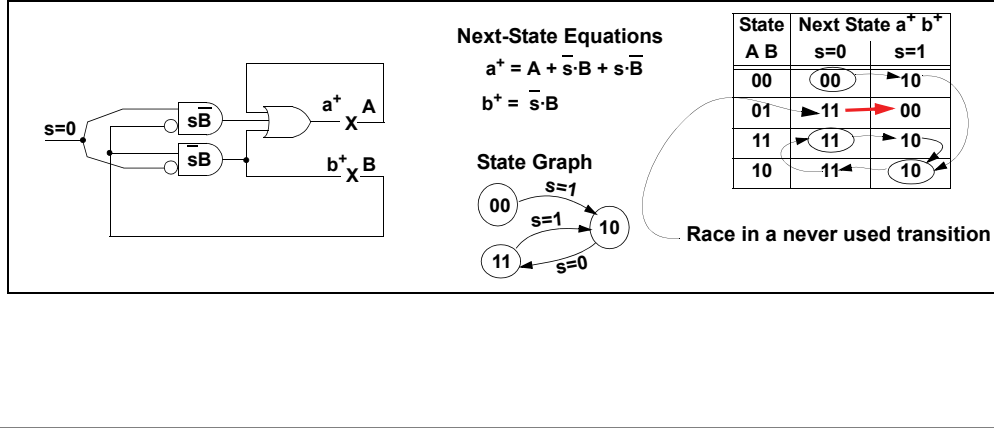


**Races Between Transient States Where One Cares!**

**A Race Between Transient States, But On a Path Between Stable States.**


FIG. 2-23 showed a “who cares race” between unused transient states.  
 This race is between transient states, but should not be ignored.

 It is an intermediate transition in the path between two stable states.-



The second transition from 01  $\rightarrow$  10 has a double bit change.  
 The circuit may end up in the stable state 11.

FIG. 2-24 Ra

 



### Oscillations (Cycles) In State Tables.

Cycles are oscillations  
They are transitions that once entered, never reach a stable state.

#### The Two Types of Cycles:

1. The oscillation continue forever or until turned off.  
These have:  
no stable state in the path of the cycle  
no races in the path that can reach a stable state.
2. It oscillates a few cycles before falling into a stable state.  
These have:  
a stable state in the column,  
a race in the path.<sup>1</sup>  
Not covered in these short form notes.

1. For three or more state variables, also check the race can reach a stable state.



FIG. 2-25 A Cycle Which Will Continue Oscillating Forever.

**Electronic Coin Tosser**

**No Stable States In s=1 Column**

When s=1, It will oscillate forever.

There are two feedback paths  
The one through gate #2 oscillates (odd number of inverters).  
The one through gate #1 is a latch. (even number of inverters).

The circuit will:  
oscillate when s=1, and  
latch the last output value when s -> 0.

State	Next State a <sup>+</sup>	
A	s=0	s=1
0	0	1
1	1	0

FIG. 2-26 A Cycle, With Stable States In Column, But No Races, Will Continue Forever.

**Stable States In the s=1 Column Without a Race**

From the state table; there is a cycle.  
From the circuit; the A loop oscillates.  
The B loop stays fixed at B=0.  
The A loop oscillating cannot make B=1  
The A loop oscillating cannot reach a stable state.

State	Next State a <sup>+</sup> b <sup>+</sup>	
A B	s=0	s=1
00	00	10
01	00	01
11	00	01
10	00	00



### Asynchronous State-Machines With Several Input Variables.

With only one external input. →

Single input asynchronous circuits have two types of races

1. Races between the state bits.
2. Races between a state variable and an input.  
These are called *essential hazards* and will not be discussed.

With two or more inputs. →


In addition, with multiple inputs, one can have-

3. Races between the two inputs
 
#### Multiple Asynchronous Inputs are Miserable

Two inputs races cannot be handled by this theory.

Theoreticians usually state-  
Nearly simultaneous input changes are *not allowed*.



Practical designers must force rational behavior for double changes.  
One might:

- Design the machine to work properly for all states a race might enter.
  - Interlock the signals so they cannot change at the same time.
  - Feed the multiple input signals separately into a synchronous circuit.
- See next course.



### A Two-input State-Table With Races

Double input changes are *not allowed*.

The State-Table has 4 other races.

1. Start at (11) with  $sx=10 \rightarrow sx=11$ .  
This race leads into a cycle
2. Start at (01) with  $sx=00 \rightarrow sx=10$ .  
This wraps around the table.  
The final state must be stable.  
It may be any of (00), (11) or (10).

FIG. 2-27 Two input async. circuit

State A B	Next State $a^+ b^+$			
	$sx=00$	$sx=01$	$sx=11$	$sx=10$
00	00	01	10	00
01	01	01	00	10
11	00	00	00	11
10	00	10	11	10

No means we don't allow two inputs to change at once.

FIG. 2-28

1)

AB	$a^+ b^+$			
	00	01	11	10
00	00	01	10	00
01	01	01	00	10
11	00	00	00	
10	00	10	11	10

2)

AB	$a^+ b^+$			
	00	01	11	10
00	00	01	10	00
01	01	01	00	10
11	00	00	00	11
10	00	10	11	10



**A Two-input State-Table With Races (Cont)**

Double input changes are *not allowed*.  
The races continued:

- Start at (10) with  $sx=10 \rightarrow sx=11$ .  
No race on first hop  
2nd hop has a race, and leads into the same cycle as 1)
- Start at (11) with  $sx=10 \rightarrow sx=00$ .  
This may end in either states (00) or (01)

**FIG. 2-29 Two input async. circuit**

State		Next State $a^+ b^+$			
A	B	$sx=00$	$sx=01$	$sx=11$	$sx=10$
00	00	00	01	10	00
01	01	01	00	00	10
11	00	00	00	00	11
10	00	10	11	10	10

**FIG. 2-30**

3)

AB	$a^+ b^+$			
	00	01	11	10
00	00	01	10	00
01	01	01	00	10
11	00	00	00	11
10	00	10	11	10

4)

AB	$a^+ b^+$			
	00	01	11	10
00	00	01	10	00
01	01	01	00	10
11	00	00	00	11
10	00	10	11	10

5. State variable races with double input variable changes.  
State marked (01)  $\xrightarrow{NO}$  (10)  $\xrightarrow{NO}$  (10) AB=01  
The double input change will make a mess of the circuit function.  
We take steps to make sure it will never happen (*not allowed*).  
Or (*next year*) follow all possibilities



**Removal of Races**

Race-free designs are done by careful state assignment.  
Races are double-bit state-variable change.

Thus states connected to another state must differ in value by one-and-only-one bit

Adjacent Karnaugh map squares differ by one bit.  
Assign states on a Karnaugh map.

**Short summary**  
States joined by arrows should cuddle on a K-map.

**FIG. 2-31 Assigning Bit-Patterns to States Using a Karnaugh Map.**

Adjacent Karnaugh map squares differ by one bit.

	0	1
00	000	001
01	010	011
11	110	111
10	100	101

Print the state names on map  
place connected states  
in adjacent squares.

	0	1
00	A	D
01	B	E
11	C	
10	F	E

Read the state assignment off the map

A = 000  
B = 010  
C = 110  
F = 100  
D = 001  
E = 101

Connected states must differ by only one bit



FIG. 2-32 Assigning Bit-Patterns to Difficult State Graphs By Adding States.


 


FIG. 2-33 Assigning Bit-Patterns to States Using Flow-Through States.

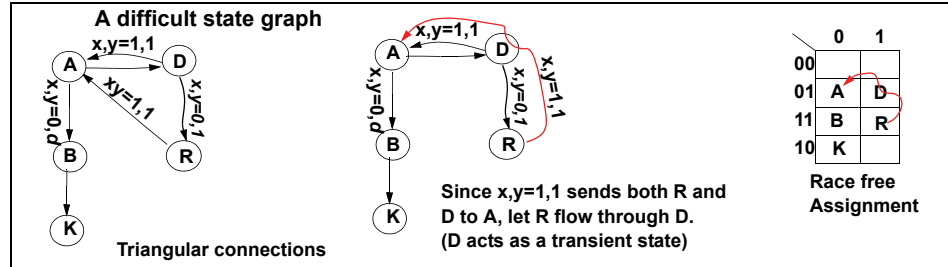

Adding extra state variables will eventually solve the race problem. However it may make the circuit larger and slightly slower.



Find A Race Free Assignment for the State Table

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	D	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

(1) Circle stable states.

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	D	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

(2) Fill in the allowed (single input change) transitions from A to other stable states.

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	D	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

(3) Fill in the other transitions between stable states, for single column input changes.

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	D	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D



### Finding A Race Free Assignment

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	D	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

Revise some next states to be flow-through states (two hops) to avoid races.

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	R
A	A	A	R	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

(3) Sketch transitions on a state table. Try to make transitions horizontal or vertical.

(4) Get rid of angles and jumps  
Can get rid of some angles

(5) Get rid of 3 sided loops.  
3 sided loops are bad

(6) Move state locations to map

	0	1
00	D	
01	R	
11	A	B
10	C	

(7) Rotate map to place R in 000

	0	1
00	R	
01	A	B
11	C	
10	D	



### Race Free Assignments

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R	R	A	R	B
A	A	A	R	B
B	A	--	--	B
C	A	C	R	--
D	D	C	R	D

(9) Fill in new transient states and race-free assignment.

State	Next State			
	Input XY=00	Input XY=01	Input XY=11	Input XY=10
R=000	R=000	A=001	R=000	A=001
A=001	A=001	A=001	R=000	B=101
B=101	A=001	--	--	B=101
C=011	A=001	C=011	D=010	--
D=010	D=010	C=011	R=000	D=010

(8) Get race-free state assignment off map

R=000  
A=001  
B=101  
C=011  
D=010




## Hazards Can Poison Asynchronous Machines

### Example: The Hazard in the Transparent D-Latch

The simple form of D-latch (transparent latch) is just a MUX.  
 The latch has a static-1 hazard when  $D, Q = 1, 1$ .  
 This glitch can feed back and latch itself.

FIG. 2-34

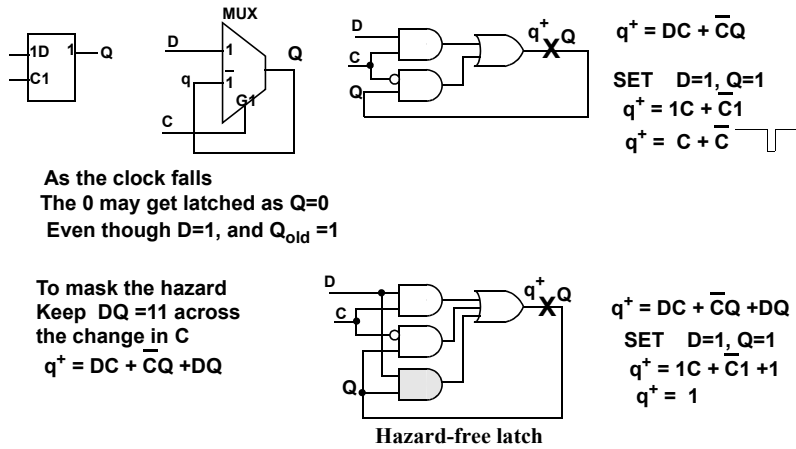

As the clock falls  
 The 0 may get latched as  $Q=0$   
 Even though  $D=1$ , and  $Q_{old}=1$

To mask the hazard  
 Keep  $DQ=11$  across  
 the change in C  
 $q^+ = DC + \bar{C}Q + DQ$

Hazard-free latch




## Common Hazard-Free D-Latch Circuit

### Explanatory note

This D-latch circuit is often used and is hazard free.  
 Analysis of the transistor circuits will show this is about 30% larger than the latch with the hazard, and smaller than the last circuit with the masking gate.

FIG. 2-35

 



### Problems

#### 1. Undesirable Properties Detectable From State Tables

Table 1: State Tables for despicable machines

Present State $Q_1Q_2$	Next State $Q_1^+Q_2^+$		Output Z	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	1
01	01	00	0	0
11	00	11	0	0
10	11	10	1	0


Present State $F_1F_2$	Next State $F_1^+F_2^+$			
	ab = 00	ab = 01	ab = 11	ab = 10
00	11	01	00	00
01	11	10	01	01
11	11	11	11	01
10	10	11	00	10

These state tables have several problems.

The left table has a race, a cycle and a second race. The second race may be hard to find because it is in a two-hop state change.

The right table has three races.

 - a) Circle the stable states.
- b) Use arrows on the state table to show the races
- c) Draw a partial state graph to show each problem transitions. See example ->t
- d) Indicate which graph you are using
- e) State whether each race is critical or noncritical.



#### 2. Supernatural Problem

The following problem was posed in the sequential circuits lab in the University of Massachusetts at Amherst. It is allegedly based on a letter sent to Sherlock Holmes by Lamont Cranston.



January 18, 1892

My dear Mr. Holmes:

Some time ago I purchased an old house in which I am presently living. Unfortunately I found it to be haunted by two ghostly noises - a Ribald Singing and a Sardonic Laughter. As a result it is hardly habitable. There is hope however, for by actual testing I have found their behavior is subject to certain laws, obscure but infallible, and that they can be affected by my playing the organ or burning incense.

In each ten minute period, each noise is either sounding or silent - on or off. What each will do during the ensuing period depends only on what has happened during the immediately preceding period, in the following exact way.

The singing in the succeeding period will continue as before (sounding or silent) unless there was organ playing and no laughter. If there was organ playing and no laughter, then the singing will reverse (silent will become sounding, sounding will become silent).

As for the laughter, if there was incense burning, then the laughter will follow the singing of the previous period. Thus with incense burning, the laughter sounds if the singing sounded for the previous ten minutes. If however, there is no incense burning, the laughter will do the opposite of what the previous singing did.

At this minute of writing, the laughter and the singing are both sounding and I indeed fear for my sanity. Please tell me what manipulations of organ and incense I should make in order to make the house quiet and keep it so.

With kindest regards to Dr. Watson, I remain,

Your admiring friend,

Lamont Cranston

February 3, 1892

Dear Mr. Cranston:

Your problem is a most interesting one. Dr. Watson and myself spent an evening pondering your puzzle, and we believe we have a methodology which will offer you relief.

Following the work of the late Mr. George Boole in his book, "The Laws of Thought," we will use the symbol S for the state variable "singing." S will be 1 for the presence of singing or 0 for its absence. S+ will represent this state variable S during the forthcoming ten minute interval. In a similar way we will use L as a state variable for the laughter. Let the inputs to this ghastly system, the burning incense and the organ music, be represented by the symbols B (burning) and M (organ music). We use M, not O so it will not be confused with the digit zero. This will avoid a common error amongst students of the philosophy of logic.

Unfortunately the reply is torn at this point, presumably by a disapproving supernatural singer. Can you complete the solution for the good Mr. Cranston? He cannot reset the ghosts, so you will need a solution that works from any starting point. Also Mr. Cranston - really it is the marker - expects a state table with the states in K-map order. He will also need a sequence to follow for any starting point.