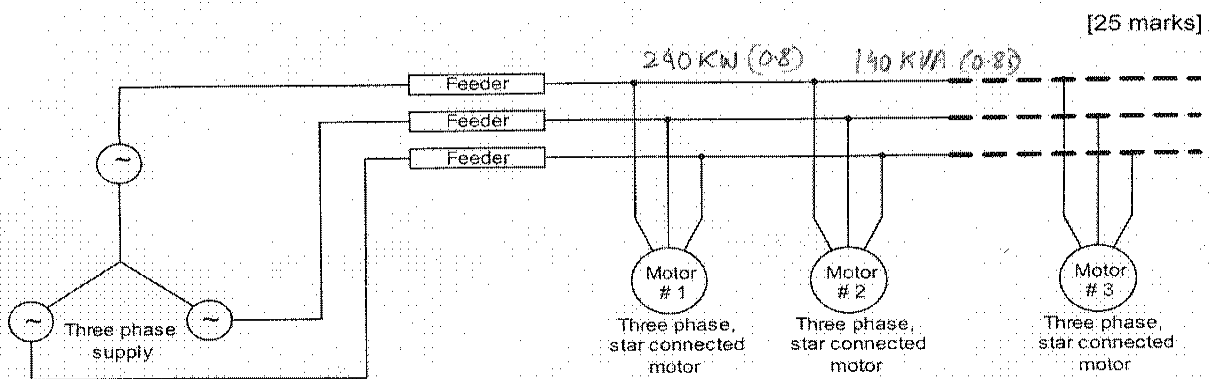


*YRCE, ENAB EL
SADANEY*

Question 1:


The industrial plant shown in Figure 1 consists of two three-phase, star connected motors connected in parallel and fed from a feeder of capacity 250 A per phase and a negligible impedance. The first motor absorbs 240 KW at a lagging power factor of 0.8; the second motor absorbs 140 KVA at a lagging power factor of 0.85. The supply voltage is $680\sqrt{3}$ volt (line to line, RMS).

- Determine the value of the system power factor, active, reactive and apparent powers.
- If the plant is to expand by adding a new three-phase, star connected motor that absorbs 100 KVA at a lagging power factor of 0.8. Can this load be added without exceeding the feeder capacity?
- What will be the capacitor cost for adding the new motor if the cost of the capacitor banks is \$150/KVAR?



[25 marks]

Figure (1)

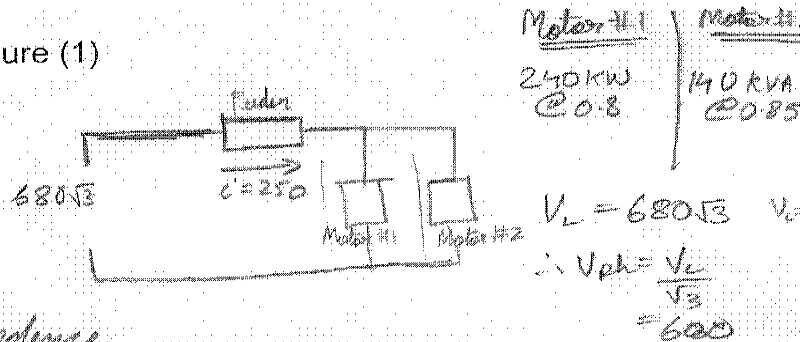

a) $P.F = \cos(\theta_1 - \theta_2)$
 $P = \sqrt{3} V_L I_L \cos(\theta_1 - \theta_2)$
 $Q = \sqrt{3} V_L I_L \sin(\theta_1 - \theta_2)$
 $S = \sqrt{3} V_L I_L$

Since feeder has negligible impedance

For motor #1

$P = 240 \text{ kW}$ $\cos \theta = 0.8 \Rightarrow \theta = 36.86^\circ$

$Q \Rightarrow \tan 36.86 = \frac{Q}{P} \Rightarrow 0.75 \times 240 \text{ kW} = 179,935.29$

$\therefore S \Rightarrow \sqrt{P^2 + Q^2} = 300 \text{ kVA} \approx 299,961.14 \text{ VA}$

P.F. = 0.8

For motor #2

$S = 140 \text{ kVA @ } 0.85$

$\cos \theta = P.F. = 0.85 \Rightarrow \theta = 31.7^\circ$

$P = \cos 31.7 \times 140 \text{ kVA} = 119 \text{ kW} = 119,113.5 \text{ W}$

$Q = \sin 31.7 \times 140 \text{ kVA} = 73.56 \text{ kVAR} = 73,560 \text{ VAR}$

∴ The system uses —

$$P_T = P_{\text{motor}_1} + P_{\text{motor}_2} = \del{544} 240 + 119 = \underline{359 \text{ kW}}$$

$$Q_T = Q_{\text{motor}_1} + Q_{\text{motor}_2} = 186 + 73.56 = \underline{253.56 \text{ kVAR}}$$

$$\therefore S_{\text{total}} = \sqrt{P_T^2 + Q_T^2} = \underline{439.5 \text{ kVA}}$$

$$\therefore \text{P.F.} \Rightarrow \cos \theta = \frac{P}{S} = 0.82 = \underline{35.2^\circ}$$

adding new motor \rightarrow 100 kVA @ P.F. 0.8

Current drawn by

$$\text{Motor \# 1} \Rightarrow P = 3 V_{\text{ph}} I_{\text{ph}} \cos \theta = 53 V_{\text{ph}} I_{\text{ph}} \cos \theta$$

$$240 \text{ kW} = \frac{680 \sqrt{3}}{\sqrt{3}} \times I \times 0.8$$

$$I = \underline{147.0 \text{ A}}$$

Current drawn by

$$\text{Motor \# 2} \Rightarrow S = 3 V_{\text{ph}} I_{\text{ph}}$$

$$\frac{140000}{680 \times 3} = I_{\text{ph}} = \underline{68.6 \text{ A}}$$

Current drawn by motor \# 3

$$S = 100 \text{ kVA}$$

$$S = 3 V_{\text{ph}} I_{\text{ph}}$$

$$\therefore \frac{100000}{3 \times 680} = I_{\text{ph}} = \underline{49 \text{ A}}$$

Total current absorbed by all motors = 264 Amp which is $>$ Supplied 250A ∴ No new motor can be added

Exam ID#001062-03

Course: ECE 261 Term: F03 Type: M Solutions: S

ECE261 Midterm

Capacitor Bank
\$150/KVAR

$\therefore \text{Total cost} = Q \times 150 \text{ dollars}$


Flux in each section

Flux \Rightarrow equivalent of I in that

$$\phi \text{ in I} = \frac{NI}{R_T}$$

$$\phi \text{ in II} = \frac{NI}{R_T}$$

I

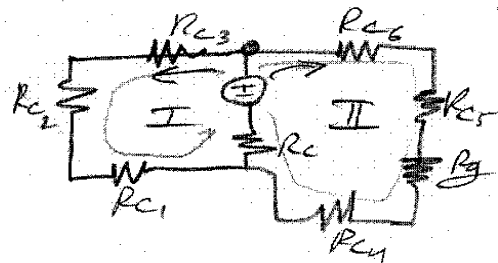

$$R_C = \frac{l}{\mu_0 \mu_r N^2 A}$$

$R_{C1} = R_{C2}$
 $R_{C3} = R_{C4}$
 $R_{C5} = R_{C6}$
 $R_g = \text{calculated in i}$

$$R_{C1} = \frac{.4}{10000 \times 0.04 \times 0.02}$$

$$R_{C2} = \frac{.5}{10000 \times 0.04 \times 0.02}$$

$$R_{C3} = \frac{.48}{10000 \times 0.04 \times 0.02}$$

self inductance of coil 1 is

$$L_{11} = \frac{N \phi}{I_1}$$

$$= \frac{N^2}{I_1}$$



=

$$b) \quad I_2 \Rightarrow \quad mmf = NI_2$$

Using

$$B = \frac{\Phi}{A}$$

$$\text{where } \Phi = \frac{NI}{R_T}$$

$$\textcircled{1}$$


$$\text{If } R_T = R_g = 0$$

$$BA = \frac{NI \cdot 0}{R_g = 0}$$

$\therefore I_2$ should be 0

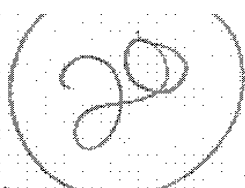Question 3:

A 50 KVA, 600/2400 V, 60 Hz, single-phase transformer has open circuit and short circuit test data as follows:



	Volt [V]	Current [A]	Power [W]
Open circuit test	600	3.34	484
Short circuit test	76.4	15.0	392.0


- Determine:
- The approximate equivalent circuit referred to the primary and referred to the secondary.
 - Draw the transformer phasor diagram referred to the primary (use the approximate equivalent circuit)
 - The efficiency and voltage regulation at half load and 84% power factor leading.
 - The necessary load to be added in parallel to the original load to obtain maximum efficiency while making the system power factor equals to 0.9 lagging.

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = 0.25 = \frac{600}{2400}$$

[12+6+10+12=40 marks]

a)

O.C.

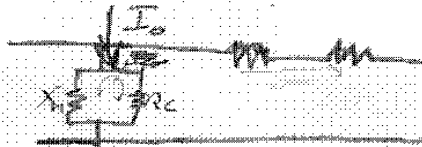

$$P = VI \cos \theta$$

$$484 = 600 \times 3.34 \times \cos \theta$$

$$\cos \theta = 0.24$$

$$\theta = 76^\circ$$

$$R_c = \frac{V}{I_0 \cos \theta}$$

$$= \frac{600}{3.34 \times 0.24} = 742.5 \Omega$$

$$X_m = \frac{V}{I_0 \sin \theta}$$

$$= \frac{600}{3.34 \times 0.97} = 185.14 \Omega$$

to primary

Ref to secondary $\Rightarrow \div a^2$

$$R_c' = R_c / a^2 = 11,880 \Omega$$

$$X_m' = X_m / a^2 = 2962.24 \Omega$$

S.C.

$$I = 15 A$$

$$I_{rated} = \frac{S}{V}$$

$$= \frac{50000}{2400} = 20.8 A$$

$$P = 392 \text{ Using } P_{copper} = I^2 R$$


$$R_{eq} = \frac{V^2}{P} = \frac{76.4^2}{392} = 14.8 \Omega$$

$$Z = \frac{V}{I} = \frac{76.4}{15} = 5.09 \Omega$$

$$X_{eq} = \sqrt{Z^2 - R_{eq}^2} = \sqrt{5.09^2 - 14.8^2} = 13.85 \Omega$$

$$R_{eq}' = R_{eq} \times a^2 = 11.88 \Omega$$
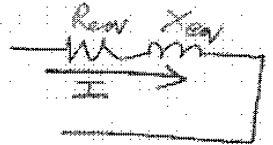
$$X_{eq}' = X_{eq} \times a^2 = 2962.24 \Omega$$



$$X_c = \frac{I_0 \sin \theta}{I_{rated}}$$

$$= \frac{3.34 \times 0.97}{20.8} = 0.155$$

Ref to primary

$$R_{eq}' = R_{eq} \times a^2$$


$$X_{eq}' = X_{eq} \times a^2$$

$$R_{eq}' = 11.88 \Omega$$

$$X_{eq}' = 2962.24 \Omega$$

$$Z_{eq}' = \sqrt{R_{eq}'^2 + X_{eq}'^2} = \sqrt{11.88^2 + 2962.24^2} = 2962.24 \Omega$$
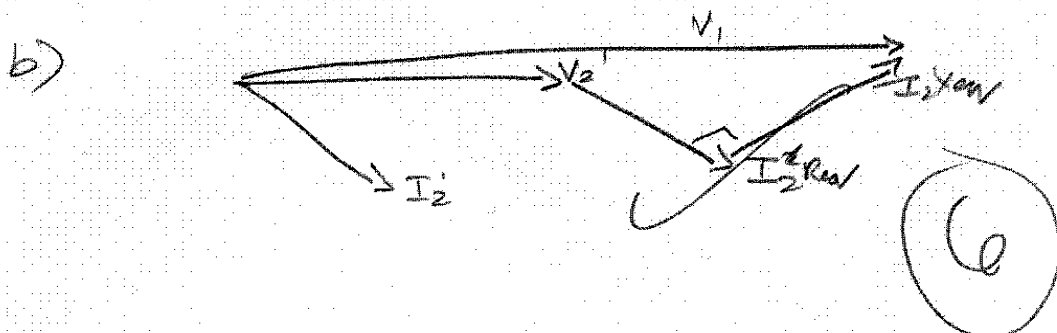
$$Z_{eq}' = \sqrt{R_{eq}'^2 + X_{eq}'^2} = \sqrt{11.88^2 + 2962.24^2} = 2962.24 \Omega$$



c)
$$\epsilon = \frac{|V_1| - |V_2'|}{|V_2'|}$$
 Ref to primary

m)

half load $\rightarrow x = 0.5$

$$\eta = \frac{x S_{core}}{x S_{core} + P_{core} + x^2 P_{copper, Full load}}$$

$S \rightarrow$ half load

$S_{min} = 50$
half load = 25

$$x = \frac{I_{min}}{I_{rated}} = \frac{15}{20.8} = 0.72$$

$P_{copper} = x^2 P_{copper, FL}$

$\eta = \frac{0.72 \times 25 \times 0.84}{0.72 \times 25 \times 0.84 + 484 + (0.72)^2 \times P_{copper, FL}} \times 100\%$

$= \frac{1512}{1512 + 484 + 392} \times 100\%$

$= 0.94 \times 100 = 94\%$

this is NOT $P_{copper, FL}$

$V_1 = V_2' + I_2' (R_{eq} + X_{eq})$ $I_2' = I_2$ $I_2, rated = 20.8A$

$V_2' = V_2 \times a$
 $= 2400 \times \frac{1}{4}$
 $= 600$

$V_1 = 600 + I_2' (R_{eq} + X_{eq})$
 $= 613 + 34$

$\epsilon = \frac{613 - 600}{600}$
 $= 0.0216$

Question 4:

Chose the correct answer:

[1] Two three-phase circuits connected in delta and star, respectively are connected to the same supply. They will consume the same power if:

a. $Z_{\Delta} = \sqrt{3}Z_y$

b. $Z_{\Delta} = 3Z_y$

c. $Z_{\Delta} = \frac{1}{3}Z_y$

d. $Z_{\Delta} = Z_y$

[2] Three-wattmeter method can be used for measuring the power in:

a. Only star balance loads.

b. Only delta balanced loads.

c. Balanced star or delta loads.

d. Balanced or unbalanced loads.

[3] Eddy current losses are reduced by:

a. Reducing the magnetic circuit resistance

b. Reducing the magnetic circuit reluctance.

c. Laminating the iron core.

d. Reducing the transformer voltage

[4] The leakage flux in transformers is reduced by:

a. Increasing the core reluctance.

b. Utilizing soft magnetic material.

c. Primary and secondary windings being coaxial

d. Reducing the separation between the primary and secondary windings.

[5] The voltage per turn in the transformer windings:

a. Is the same in both primary and secondary.

b. Is dependant on the windings voltage ratings.

c. Is larger in the primary than the secondary.

d. Is larger in the secondary than the primary.

[6] The transformer output voltage might be higher than the input voltage if:

a. The load is highly inductive

b. The load is pure resistance

c. The secondary is open circuit

d. The load is highly capacitive

[7] The short circuit test in transformers should be conducted:

a. In high voltage side while low voltage is shorted.

b. In high voltage side while low voltage is loaded.



c. In low voltage side while high voltage is shorted.

d. In low voltage side while high voltage is loaded.

$$\chi = \frac{N^2}{l}$$

$$\delta = \frac{N^2 I^2}{R}$$

[14 marks]

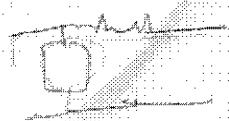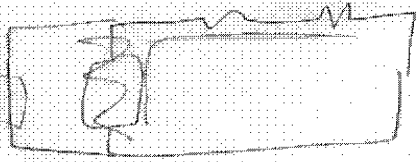

10