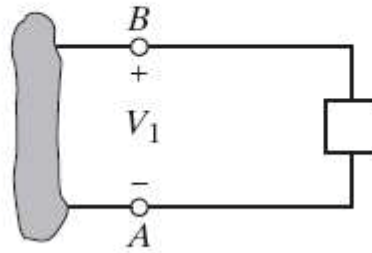


- 1.8** Five coulombs of charge pass through the element in Fig. P1.8 from point *A* to point *B*. If the energy absorbed by the element is 120 J, determine the voltage across the element.



**Figure P1.8**

---

**SOLUTION:**

$$W = -V_1 Q$$

$$V_1 = -\frac{W}{Q}$$

$$V_1 = -\frac{120}{5}$$

$$V_1 = -24\text{V}$$

- 1.16 The charge that enters the BOX in Fig. P1.16 is shown in the graph below. Calculate and sketch the current flowing into and the power absorbed by the BOX between 0 and 10 milliseconds.

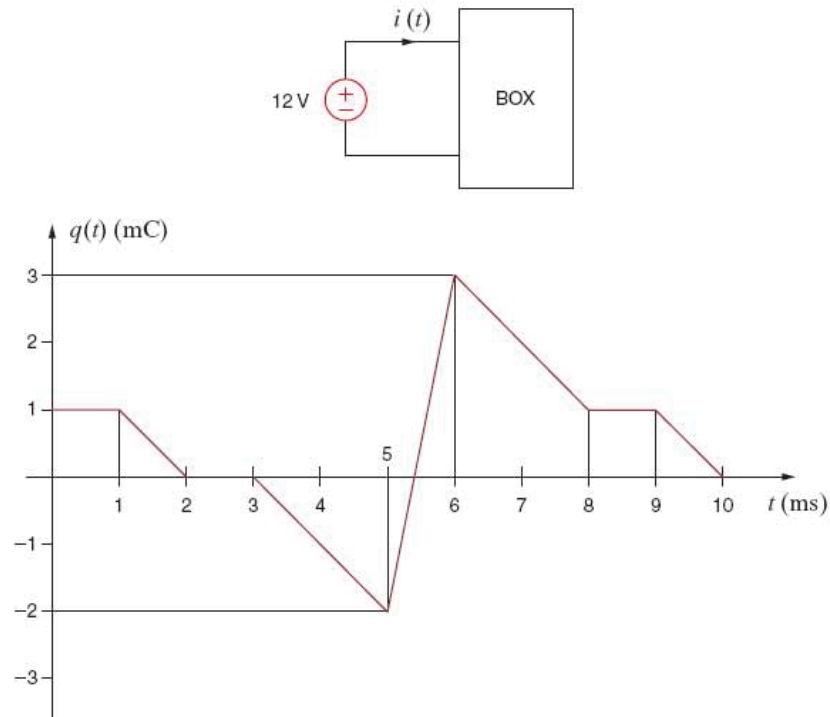


Figure P1.16

**SOLUTION:**

$$i(t) = \frac{dq}{dt} \text{ (slope of the curve)}$$

$$P = -vi = 12i$$

$$\underline{0 \leq t \leq 1 \text{ ms} :}$$

$$i(t) = \frac{1-1}{1-0} = 0 \quad P = 12(0) = 0$$

$$\underline{1 \leq t \leq 2 \text{ ms} :}$$

$$i(t) = \frac{0-1}{2-1} = -1 \text{ A} \quad P = (12)(-1) = -12 \text{ W}$$

$$\underline{2 \leq t \leq 3 \text{ ms} :}$$

$$i(t) = \frac{0-0}{3-2} = 0 \quad P = 0$$

$$\underline{3 \leq t \leq 5 \text{ ms:}}$$

$$i(t) = \frac{-2-0}{5-3} = -1 \text{ A} \quad P = (12)(-1) = -12 \text{ W}$$

$$\underline{5 \leq t \leq 6 \text{ ms:}}$$

$$i(t) = \frac{3-(-2)}{6-5} = 5 \text{ A} \quad P = (12)(5) = 60 \text{ W}$$

$$\underline{6 \leq t \leq 8 \text{ ms:}}$$

$$i(t) = \frac{1-3}{8-6} = -1 \text{ A} \quad P = (12)(-1) = -12 \text{ W}$$

$$\underline{8 \leq t \leq 9 \text{ ms:}}$$


$$i(t) = \frac{1-1}{9-8} = 0 \quad P = (12)(0) = 0$$


$$\underline{9 \leq t \leq 10 \text{ ms:}}$$

$$i(t) = \frac{0-1}{10-9} = -1 \text{ A} \quad P = (12)(-1) = -12 \text{ W}$$

$$\underline{t > 10 \text{ ms:}}$$

$$i(t) = 0 \quad P = 0$$

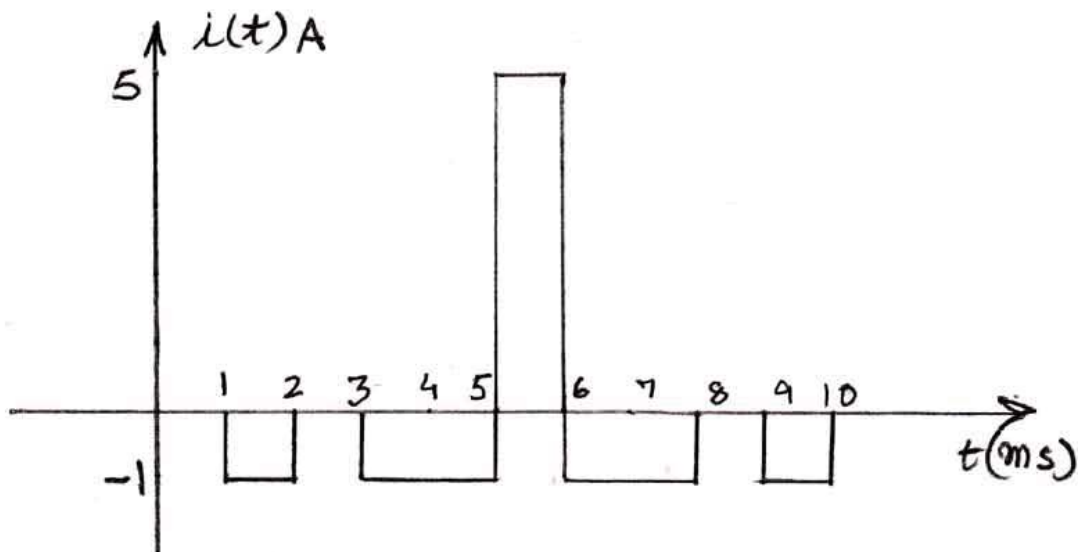

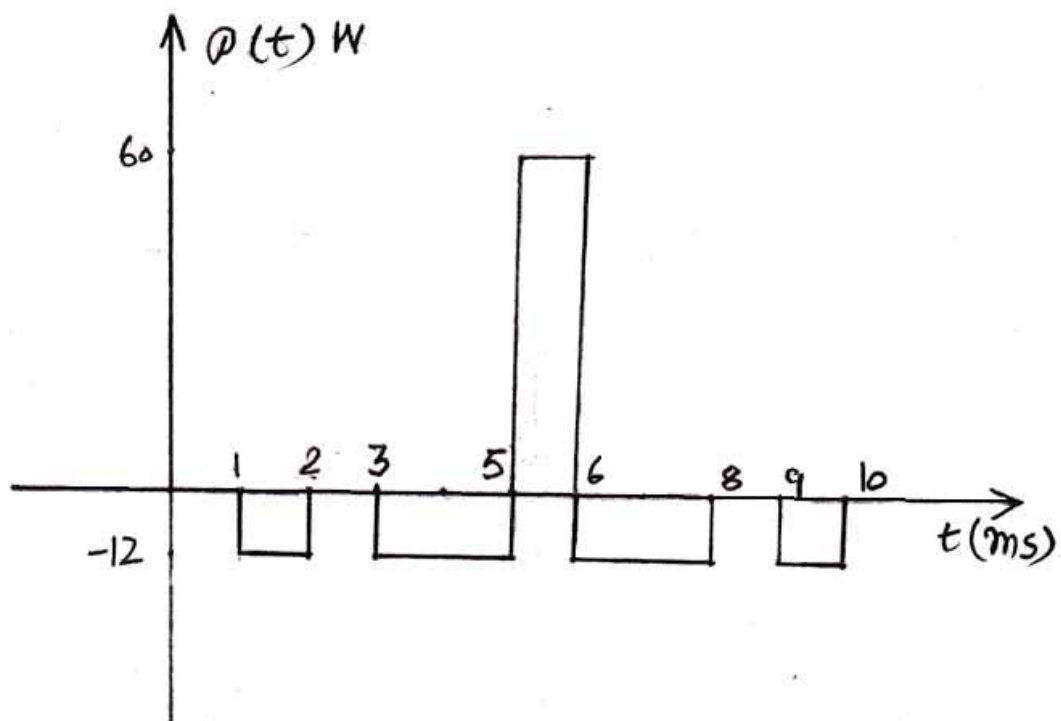

- 1.21** Calculate the power absorbed by element A in Fig. P1.21.


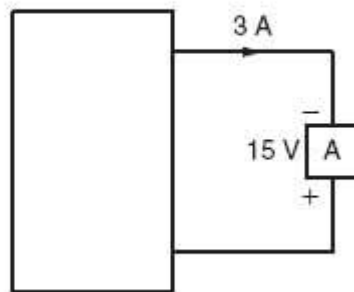


Figure P1.21

**SOLUTION:**

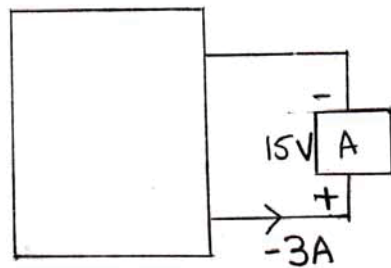

$$p = (15)(-3) = -45\text{W}$$

- 1.27 (a)** In Fig. P1.27 (a),  $P_1 = 36$  W. Is element 2 absorbing or supplying power, and how much?
- (b)** In Fig. P1.27 (b),  $P_2 = -48$  W. Is element 1 absorbing or supplying power, and how much?

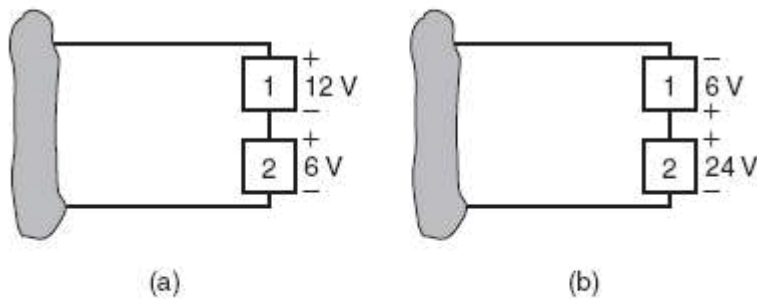


Figure P1.27

**SOLUTION:**

$$a) P_1 = 36 \text{ W}$$

$$I = \frac{P_1}{V}$$

$$I = \frac{36}{12}$$

$$I = 3 \text{ A}$$

$$P_2 = V_2 I$$

$$P_2 = 6(3)$$

$$P_2 = 18 \text{ W absorbed}$$

$$b) P_2 = -48 \text{ W}$$

$$I = \frac{P_2}{-V_2}$$

$$I = \frac{-48}{-24}$$

$$I = 2 \text{ A}$$

$$P_1 = V_1 I$$

$$P_1 = 6(2)$$

$$P_1 = 12 \text{ W absorbed}$$

- 1.30 Choose  $I_s$  such that the power absorbed by element 2 in Fig. P1.30 is 7 W.

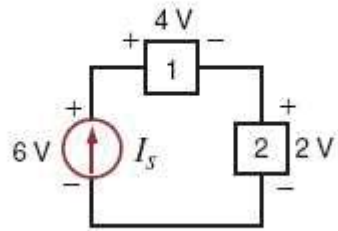


Figure P1.30

SOLUTION:

$$P_2 = 7 \text{ W absorbed}$$

$$P_2 = V_2 I_s$$

$$I_s = \frac{P_2}{V_2} = \frac{7}{2}$$

$$I_s = 3.5 \text{ A}$$

1.36 Determine the power absorbed by element 1 in Fig. P1.36.

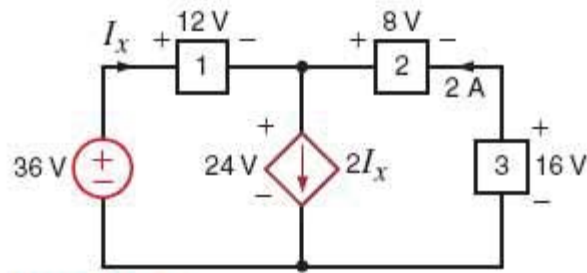


Figure P1.36

**SOLUTION:**

$$P_{36V} = -36I_x \text{ W}$$

$$P_1 = 12I_x \text{ W}$$

$$P_{2I_x} = 48I_x \text{ W}$$

$$P_2 = -16 \text{ W}$$

$$P_3 = -32 \text{ W}$$

$$36I_x + 16 + 32 = 12I_x + 48I_x$$

$$48 = 24I_x$$

$$I_x = 2 \text{ A}$$

$$P_1 = 24 \text{ W}$$

**2.2** Determine the current and power dissipated in the resistors in Fig. P2.2.

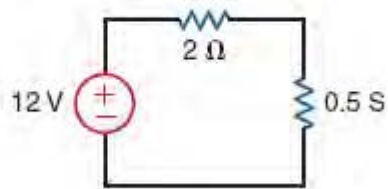


Figure P2.2

**SOLUTION:**

$$R_2 = \frac{1}{0.5} = 2 \Omega$$

$$I = \frac{12}{2+2}$$

$$I = 3A$$

$$P_{R_1} = I^2 R_1 = (3)^2 (2)$$

$$P_{R_1} = 18 W$$

$$P_{R_2} = I^2 R_2 = (3)^2 (2)$$

$$P_{R_2} = 18 W$$

- 2.8** An automobile uses two halogen headlights connected as shown in Fig. P2.8. Determine the power supplied by the battery if each headlight draws 3 A of current.

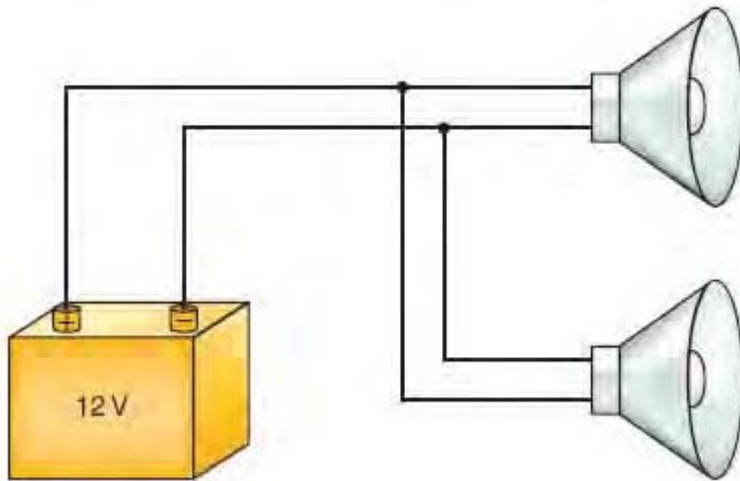


Figure P2.8

---

**SOLUTION:**

$$I_1 = I_2 = 3\text{ A}$$

$$I = I_1 + I_2 = 6\text{ A}$$

$$P_{12\text{V}} = VI = 12(6)$$

$$P_{12\text{V}} = 72\text{ W}$$

**2.10** Find  $I_1$  in the network in Fig. P2.10.

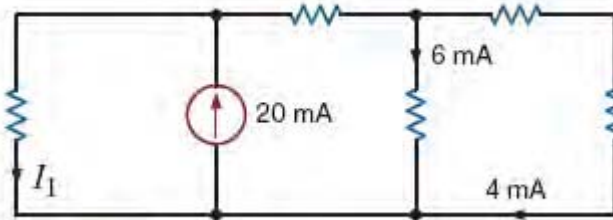


Figure P2.10

**SOLUTION:**

$$\begin{aligned} \text{KCL at node B: } I_2 &= 6\text{m} + 4\text{m} \\ I_2 &= 10\text{mA} \end{aligned}$$

$$\begin{aligned} \text{KCL at node A: } I_1 + I_2 &= 20\text{m} \\ I_1 &= 20\text{m} - 10\text{m} \\ I_1 &= 10\text{mA} \end{aligned}$$

2.13 Find  $I_1$  in the circuit in Fig. P2.13.


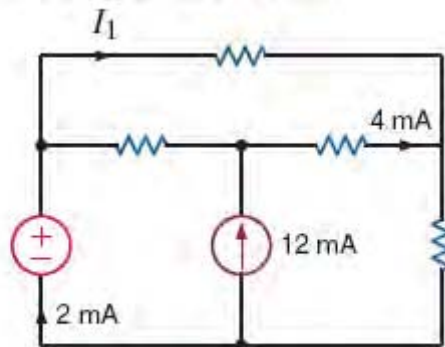


Figure P2.13

SOLUTION:

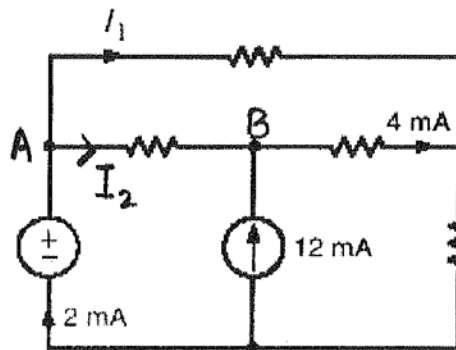

$$\text{KCL at node B: } I_2 + 12\text{m} = 4\text{m}$$

$$I_2 = -8\text{mA}$$

$$\text{KCL at node A: } 2\text{m} = I_1 + I_2$$

$$I_1 = 10\text{mA}$$

2.15 Determine  $I_L$  in the circuit in Fig. P2.15.

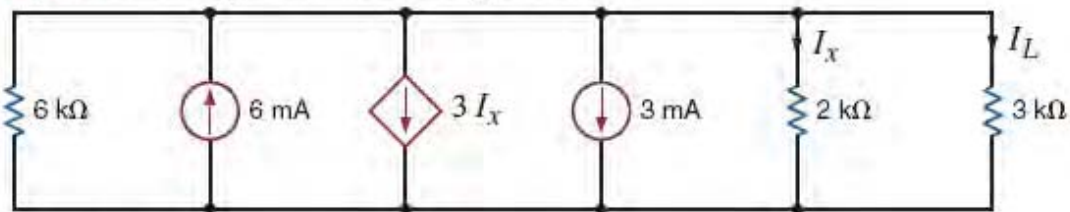


Figure P2.15

**SOLUTION:**

$$6\text{ m} = \frac{V}{6\text{ k}} + 3I_x + 3\text{ m} + I_x + I_L$$

$$\frac{V}{6\text{ k}} + 4I_x + I_L = 3\text{ m}$$

$$I_x = \frac{V}{2\text{ k}} \quad \text{and} \quad I_L = \frac{V}{3\text{ k}}$$

$$\frac{V}{6\text{ k}} + 4\left(\frac{V}{2\text{ k}}\right) + \frac{V}{3\text{ k}} = 3\text{ m}$$

$$V + 12V + 2V = 18$$

$$15V = 18$$

$$V = \frac{18}{15} \text{ V}$$

$$I_L = \frac{18}{15(3\text{ k})}$$

$$I_L = 0.4\text{ mA}$$

2.17 Find  $I_1$  in the network in Fig. P2.17.

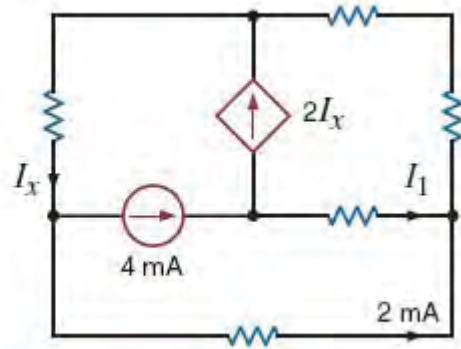


Figure P2.17

**SOLUTION:**

$$I_x = 4 \text{ mA} + 2 \text{ mA} = 6 \text{ mA}$$

$$4 \text{ mA} = 2I_x + I_1$$

$$= 12 \text{ mA} + I_1$$

$$I_1 = -8 \text{ mA}$$

2.25 Find  $V_{fb}$  and  $V_{ec}$  in the circuit in Fig. P2.25.

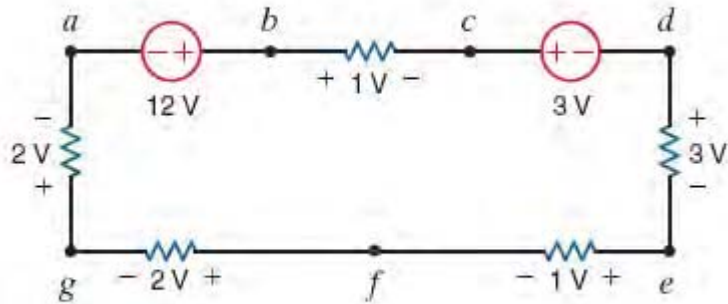


Figure P2.25

**SOLUTION:**

KVL around fbcdef:

$$V_{fb} + 1 + 3 + 3 + 1 = 0$$

$$V_{fb} = -8V$$

KVL around ecde:

$$V_{ec} + 3 + 3 = 0$$

$$V_{ec} = -6V$$

2.31 Find  $V_o$  in the network in Fig. P2.31.

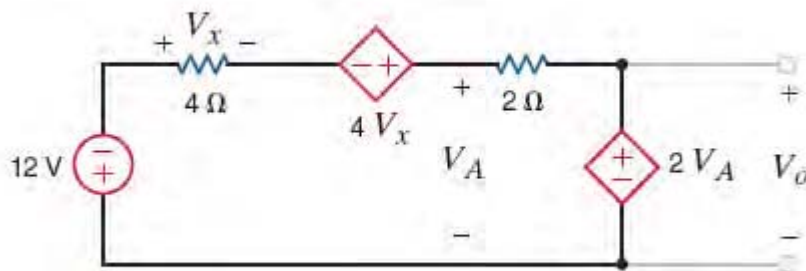


Figure P2.31

**SOLUTION:**

$$\text{KVL: } 4V_x = 12 + 4I + 2I + 2V_A$$

$$V_x = 4I$$

$$4(4I) = 12 + 6I + 2V_A$$

$$2V_A = 10I - 12$$

$$V_A = 5I - 6$$

$$\text{KVL: } 4V_x = 12 + V_x + V_A$$

$$4(4I) = 12 + 4I + V_A$$

$$V_A = 12I - 12$$

$$I = \frac{V_A + 12}{12}$$

$$V_A = 5\left(\frac{V_A + 12}{12}\right) - 6$$

$$12V_A = 5V_A + 60 - 72$$

$$7V_A = -12$$

$$V_A = -\frac{12}{7} \text{ V}$$

$$V_o = 2V_A = 2\left(-\frac{12}{7}\right) = -\frac{24}{7} \text{ V}$$

**2.40** Find  $V_x$  and the power supplied by the 15-V source in the circuit in Fig. P2.40.

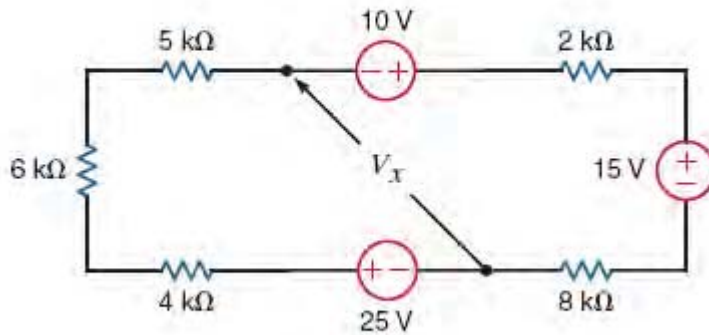


Figure P2.40

**SOLUTION:**

$$\begin{aligned} \text{KVL : } 25 + 10 &= 4\text{KI} + 6\text{KI} + 5\text{KI} + 2\text{KI} + 15 + 8\text{KI} \\ 25\text{KI} &= 20 \\ I &= 0.8\text{mA} \end{aligned}$$

$$\begin{aligned} \text{KVL : } V_x + 10 &= 2\text{KI} + 15 + 8\text{KI} \\ V_x &= 5 + 10\text{K}(0.8\text{m}) \\ V_x &= 13\text{V} \end{aligned}$$

$$\begin{aligned} P_{15\text{V}} &= VI = 15(0.8\text{m}) \\ P_{15\text{V}} &= 12\text{mW (absorbed)} \end{aligned}$$