

2.110 Determine the value of V_o in the network in Fig. P2.110.


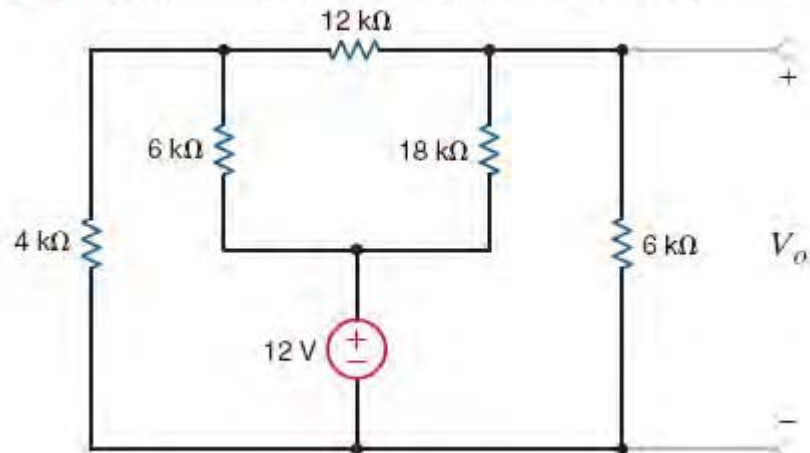


Figure P2.110

SOLUTION:

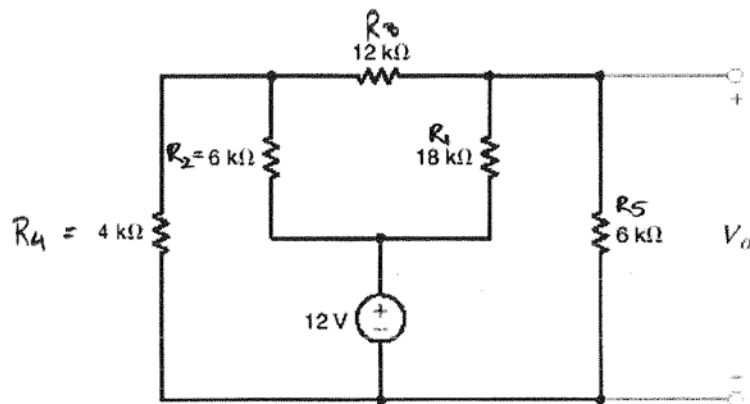


Using a delta to wye transformation:

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3} = \frac{18k(6k)}{18k + 6k + 12k} = 3k\Omega$$



$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3} = \frac{6k(12k)}{18k + 6k + 12k} = 2k\Omega$$
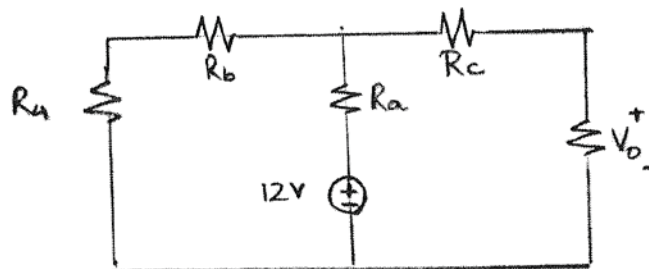
$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{18k(12k)}{18k + 6k + 12k} = 6k\Omega$$



$$R' = R_4 + R_b = 4K + 2K$$

$$R' = 6K \Omega$$

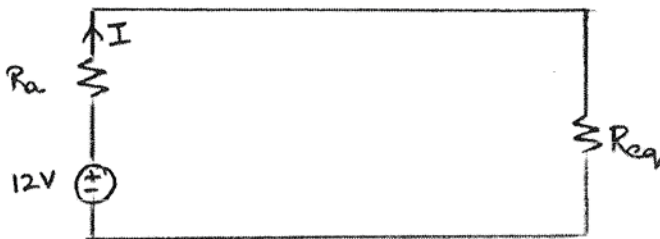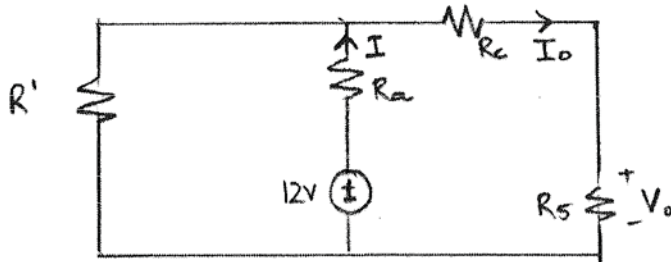

$$R_{eq} = R' \parallel (R_c + R_5) = 6K \parallel (6K + 6K)$$

$$R_{eq} = 6K \parallel 12K = \frac{6K(12K)}{6K + 12K} = 4K \Omega$$

$$I = \frac{12}{R_a + R_{eq}} = \frac{12}{3K + 4K}$$

$$I = 1.714 \text{ mA}$$

Using current division:

$$I_o = \left(\frac{R'}{R' + R_c + R_5} \right) (I)$$

$$I_o = \left(\frac{6k}{6k+6k+6k} \right) (1.714m)$$

$$I_o = 0.571mA$$

$$V_o = I_o R_5 = (0.571m)(6k)$$

$$V_o = 3.43V$$

2.112 Find V_o in the network in Fig. P2.112.

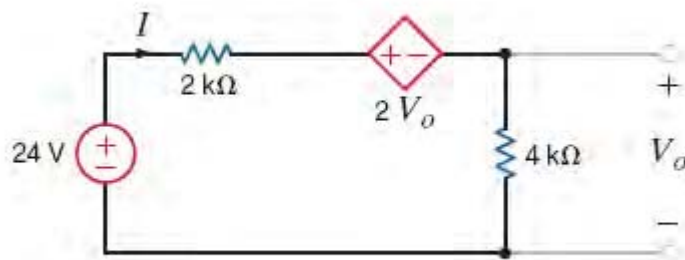


Figure P2.112

SOLUTION:

KVL:

$$24 = 2kI + 2V_o + V_o$$

$$I = \frac{24 - 3V_o}{2k}$$

$$V_o = I(4k) = \left(\frac{24 - 3V_o}{2k} \right) (4k)$$

$$V_o = 48 - 6V_o$$

$$7V_o = 48 - 6V_o$$

$$7V_o = 48$$

$$V_o = 6.86V$$

2.120 A typical transistor amplifier is shown in Fig. P2.120. Find the amplifier gain G (i.e., the ratio of the output voltage to the input voltage).


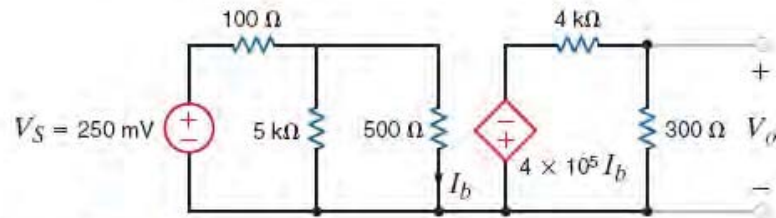


Figure P2.120

SOLUTION:

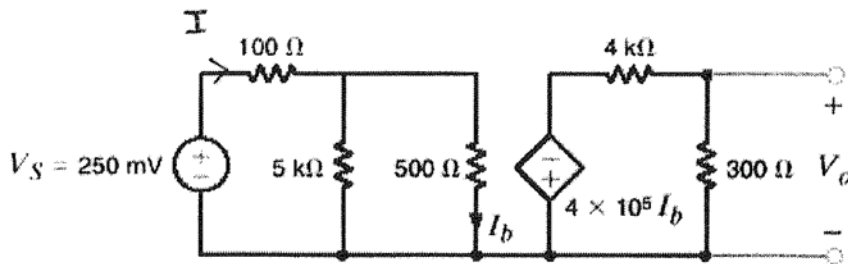

$$I = \frac{V_S}{(500 \parallel 5k) + 100} = \frac{250 \text{ m}}{454.55 + 100}$$

$$I = 0.451 \text{ mA}$$

$$I_b = \left(\frac{5k}{5k + 500} \right) (0.451 \text{ m})$$

$$I_b = 0.41 \text{ mA}$$

$$V_o = \left(\frac{300}{4k + 300} \right) (-4 \times 10^5) (0.41 \text{ mA})$$

$$V_o = -11.44 \text{ V}$$

$$G = \frac{V_o}{V_S} = \frac{-11.44}{250 \text{ m}}$$

$$G = -45.76$$

2.56 Find R_{AB} in the network in Fig. P2.56.


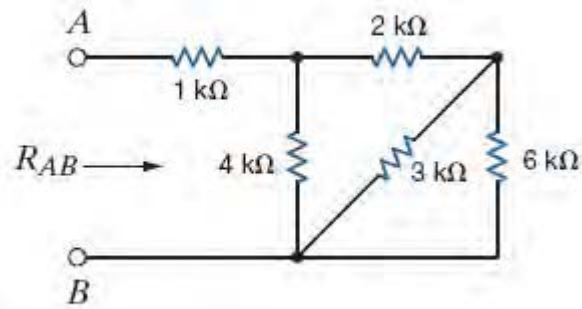


Figure P2.56

SOLUTION:
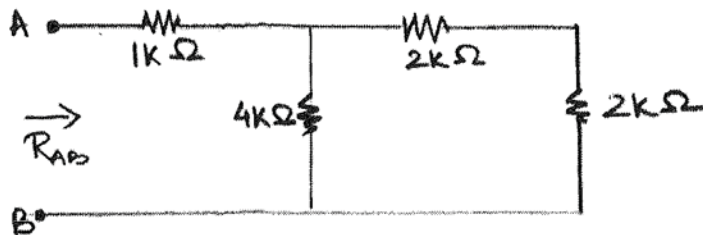
$$3\text{k} \parallel 6\text{k} = 2\text{k}\Omega$$



$$R_{AB} = (4\text{k} \parallel 2\text{k}) + 1\text{k}$$

$$R_{AB} = 3\text{k}\Omega$$

2.63 Find the equivalent resistance R_{eq} in the network in Fig. P2.63.



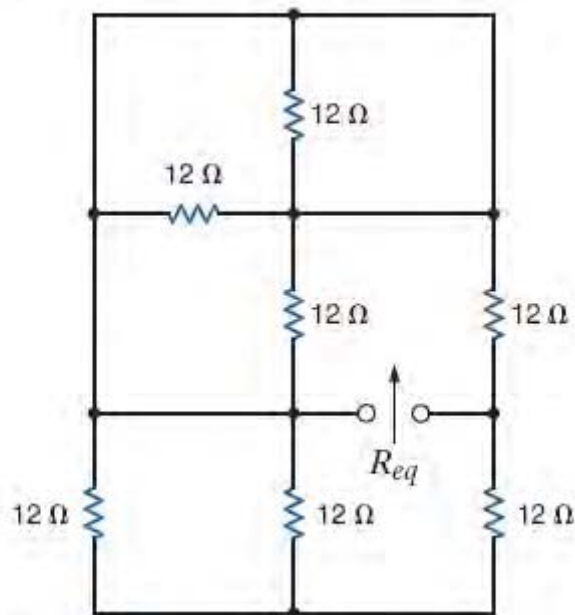
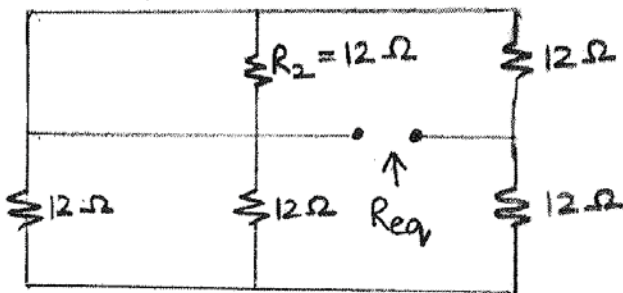


Figure P2.63

SOLUTION:

$$R_A = R_1 \parallel R_3 = 6 \Omega$$

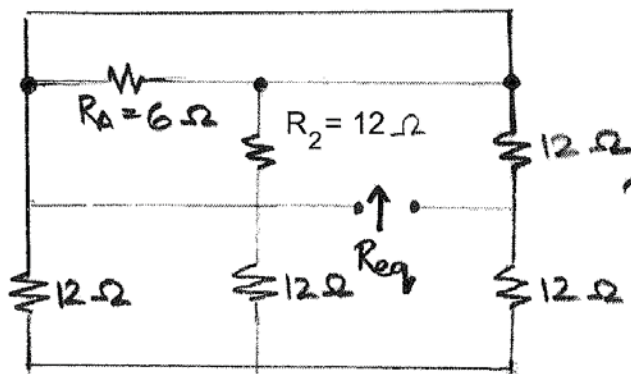

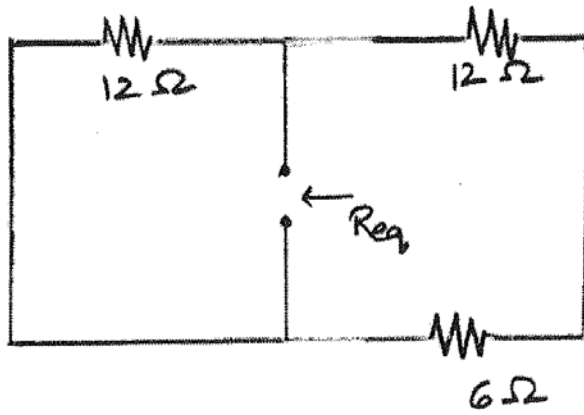

$$R_{eq} = 12 \parallel 18$$

$$R_{eq} = 7.2\ \Omega$$

2.83 If $I_o = 2 \text{ mA}$ in the circuit in Fig. P2.83, find V_s .


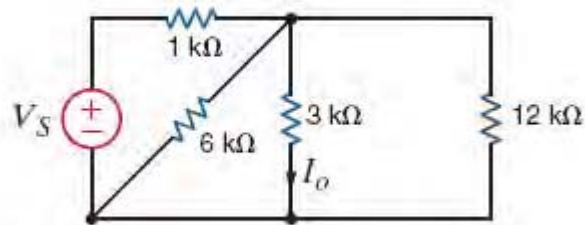


Figure P2.83

SOLUTION:

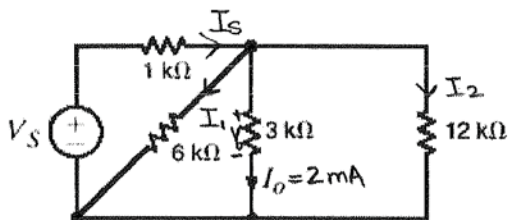

$$V_o = I_o (3\text{k}) = 2\text{m}(3\text{k}) = 6\text{V}$$

$$I_1 = \frac{6}{6\text{k}} = 1\text{mA}$$

$$I_2 = \frac{6}{12\text{k}} = 0.5\text{mA}$$

KCL:

$$I_s = I_1 + I_o + I_2 = 1\text{m} + 2\text{m} + 0.5\text{m}$$

$$I_s = 3.5\text{mA}$$

KVL:

$$V_s = 1\text{k}I_s + V_o$$

$$V_s = 1\text{k}(3.5) + 6$$

$$V_s = 9.5\text{V}$$

2.87 If $V_1 = 5\text{ V}$ in the circuit in Fig. P2.87, find I_S .



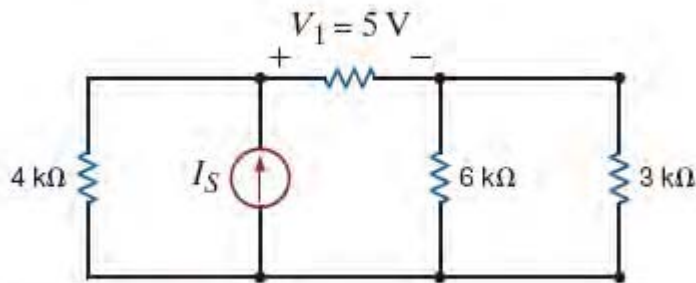


Figure P2.87

SOLUTION:

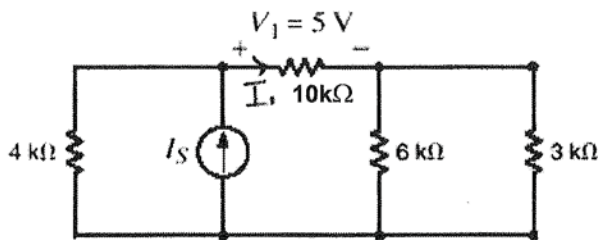
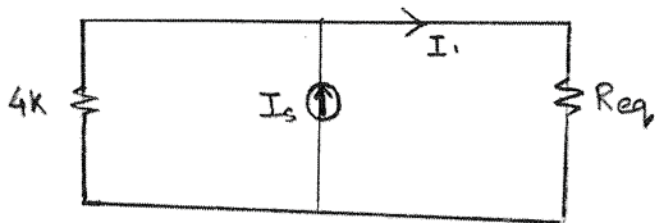
$$I_1 = \frac{V_1}{10\text{k}} = \frac{5}{10\text{k}} = \frac{1}{2} \text{ mA}$$



$$R_{eq} = (6\text{k} \parallel 3\text{k}) + 10\text{k}$$

$$R_{eq} = 12\text{k} \Omega$$

$$I_1 = \left(\frac{4\text{k}}{4\text{k} + 12\text{k}} \right) I_S$$

$$I_S = \left(\frac{I_1}{\frac{4\text{k}}{4\text{k} + 12\text{k}}} \right) = \left(\frac{\frac{1}{2} \text{ mA}}{\frac{4\text{k}}{4\text{k} + 12\text{k}}} \right)$$

$$I_S = 2 \text{ mA}$$

2.92 Find the value of I_A in the network in Fig. P2.92.


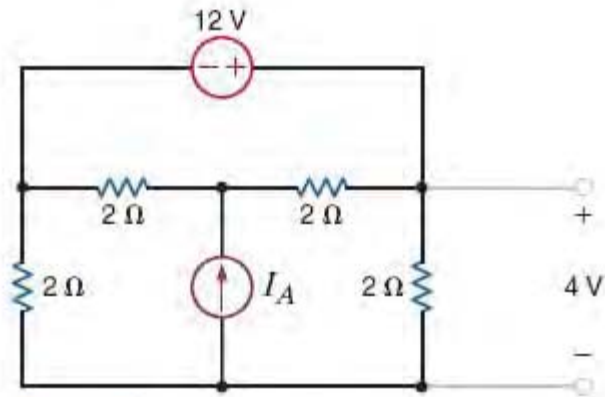


Figure P2.92

SOLUTION:

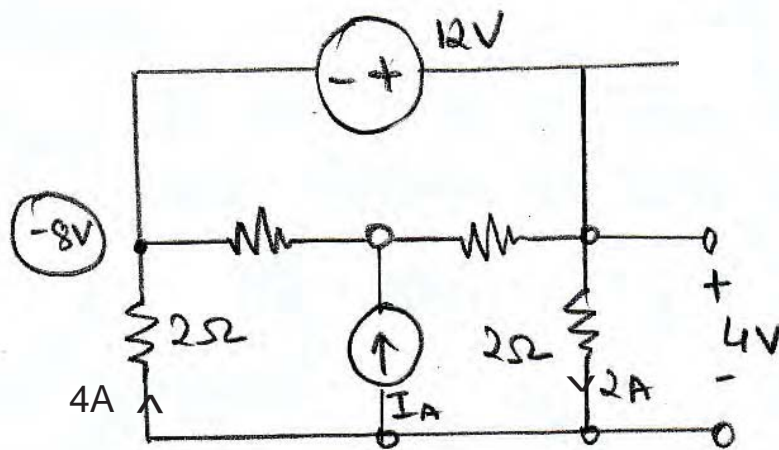

$$I_A = -2A$$

3.1 Find I_1 in the circuit in Fig. P3.1.

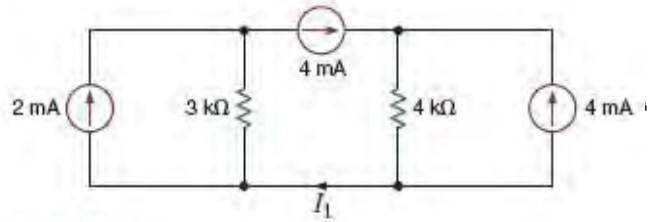


Figure P3.1

SOLUTION:

$$I_1 = 4 \text{ mA}$$

3.7 Find I_o in the circuit in Fig. P3.7 using nodal analysis.

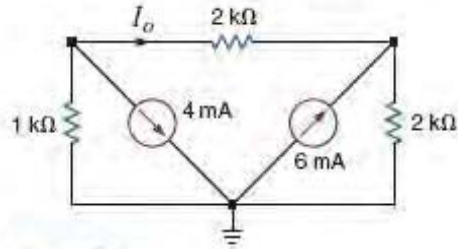


Figure P3.7


SOLUTION:

$$\begin{bmatrix} \frac{1}{k} + \frac{1}{2k} & -\frac{1}{2k} \\ -\frac{1}{2k} & \frac{1}{2k} + \frac{1}{2k} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{4}{k} \\ \frac{6}{k} \end{bmatrix}$$

$$\begin{aligned} \Delta &= \left(\frac{3}{2k}\right)\left(\frac{1}{k}\right) - \left(\frac{1}{4k^2}\right) = \frac{3}{2k^2} - \frac{1}{4k^2} \\ &= \frac{6}{4k^2} - \frac{1}{4k^2} = \frac{5}{4k^2} \end{aligned}$$

$$\begin{aligned} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \frac{4k^2}{5} \begin{bmatrix} \frac{1}{k} & \frac{1}{2k} \\ \frac{1}{2k} & \frac{3}{2k} \end{bmatrix} \begin{bmatrix} -4/k \\ 6/k \end{bmatrix} \\ &= \frac{4k^2}{5} \begin{bmatrix} -\frac{4}{k^2} & +\frac{3}{k^2} \\ -\frac{2}{k^2} & +\frac{9}{k^2} \end{bmatrix} = \frac{4}{5} \begin{bmatrix} -1 \\ 7 \end{bmatrix} = \begin{bmatrix} -\frac{4}{5} \\ \frac{28}{5} \end{bmatrix} \end{aligned}$$
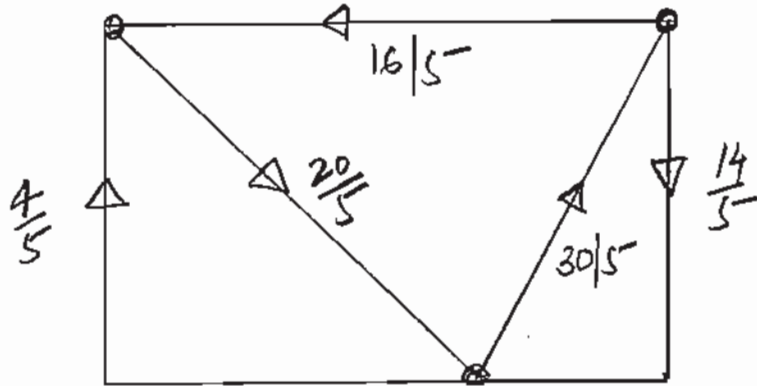
$$I_D = \frac{1}{2k} \left(-\frac{4}{5} - \frac{28}{5} \right) = \frac{1}{2k} \left(\frac{-32}{5} \right) = \frac{-16}{5} \text{ mA}$$



3.12 Find V_o in the network in Fig. P3.12 using nodal analysis.


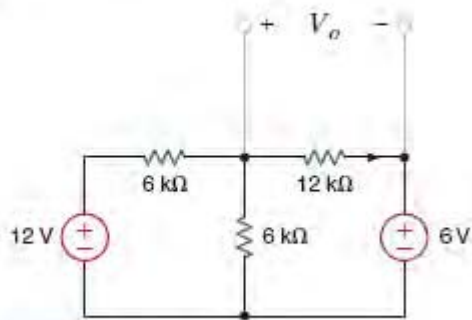


Figure P3.12

SOLUTION:

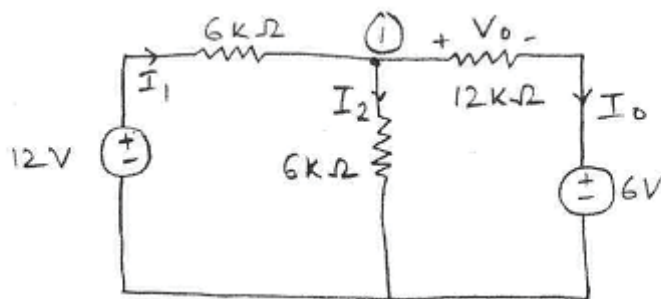

$$\text{KCL at } \textcircled{1}: I_1 = I_2 + I_o$$

$$\frac{12 - V_1}{6\text{K}} = \frac{V_1}{6\text{K}} + \frac{V_1 - 6}{12\text{K}}$$

$$24 - 2V_1 = 2V_1 + V_1 - 6$$

$$5V_1 = 30$$

$$V_1 = 6\text{V}$$

$$V_o = V_1 - 6$$

$$= 6 - 6$$

$$V_o = 0\text{V}$$

3.18 Find V_o in the circuit in Fig. P3.18 using nodal analysis.


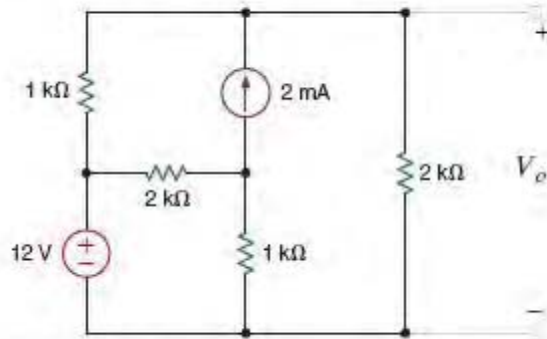


Figure P3.18

SOLUTION:

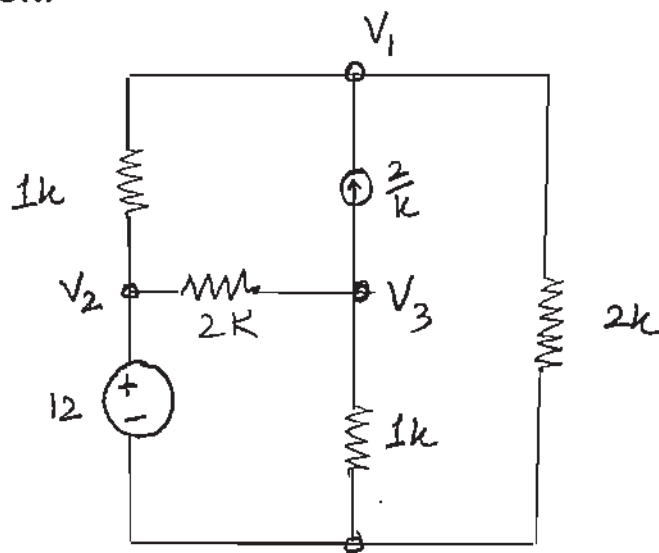


$$\frac{V_1 - 12}{1k} + \frac{V_1}{2k} = \frac{2}{k}$$

$$\frac{V_3 - 12}{2k} + \frac{V_3}{1k} = -\frac{2}{k}$$

$$\frac{V_1}{k} + \frac{V_1}{2k} = \frac{14}{k} \Rightarrow \frac{3}{2} V_1 = 14 \quad V_1 = \frac{28}{3} V$$
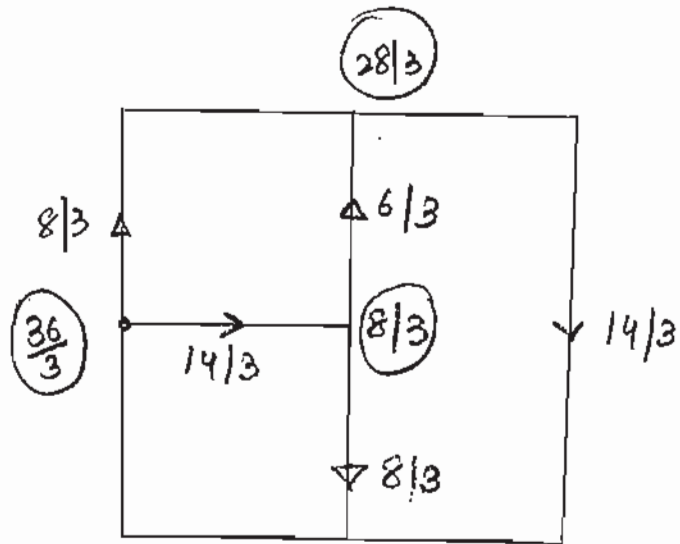
$$\frac{V_3}{2k} + \frac{V_3}{1k} = \frac{4}{k} \Rightarrow \frac{3}{2} V_3 = 4 \quad V_3 = \frac{8}{3} V$$



3-22 Find V_o in the network in Fig. P3.22 using nodal analysis.

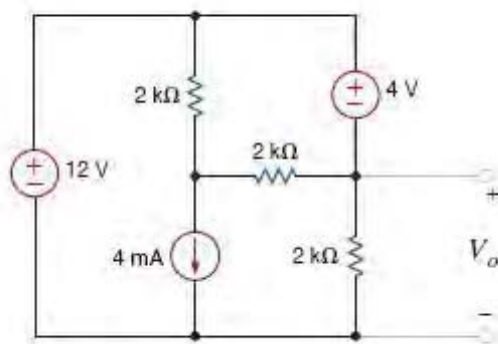


Figure P3.22

SOLUTION:

$$V_o = 12 - 4 = 8V$$

3.35 Find V_o in the circuit in Fig. P3.35 using nodal analysis.

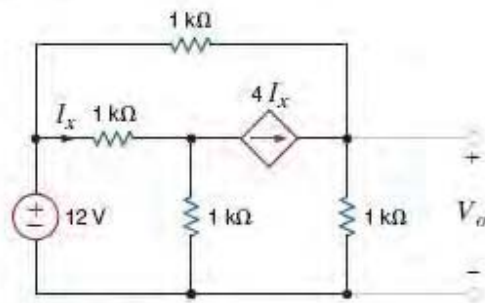


Figure P3.35

SOLUTION:

$$\frac{V_1 - 12}{k} + \frac{V_1}{k} + 4I_X = 0$$

$$\frac{V_o - 12}{k} + \frac{V_o}{k} = 4I_X \quad I_X = \frac{12 - V_1}{k}$$

$$V_1 - 12 + V_1 + 48 - 4V_1 = 0$$

$$V_o - 12 + V_o = 48 - 4V_1$$


$$-2V_1 + 36 = 0$$

$$2V_o + 4V_1 = 60$$

$$V_1 = 18V$$

$$2V_o = 60 - 72 = -12$$

$$V_o = -6V$$

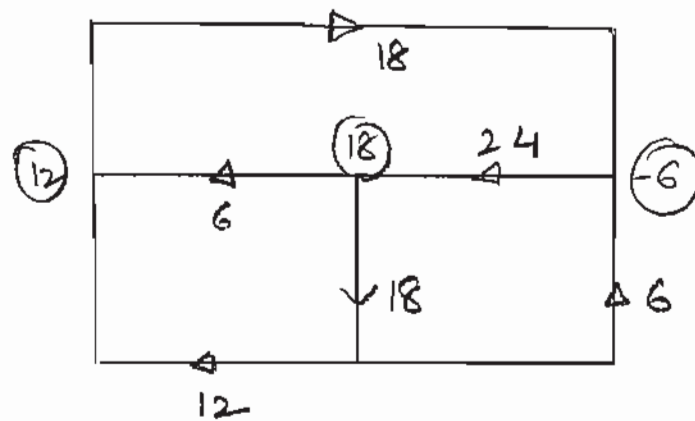

3.53 Find I_o in the network in Fig. P3.53 using mesh analysis.


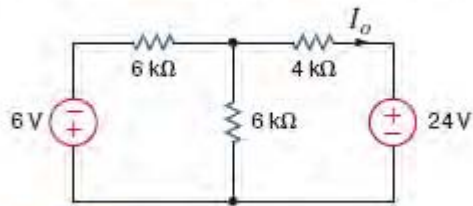


Figure P3.53

SOLUTION:

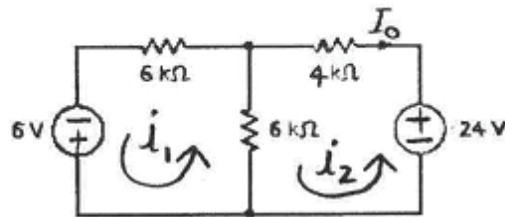

Let the loop current be I_1 & I_2 mA as indicated in the figure

KVL for loop 1 :

$$6 = 6I_1 + 6(I_1 - I_2)$$

$$\Rightarrow 6 = 12I_1 - 6I_2 \quad \text{--- (1)}$$

KVL for the loop 2 :

$$24 = 4I_2 + 6(I_2 - I_1)$$

$$\Rightarrow 24 = -6I_1 + 10I_2 \quad \text{--- (2)}$$

Solving equation ① & ② gives

$$I_2 = \frac{27}{7} \text{ mA}$$

$$\therefore I_o = -I_2$$

$$I_o = -\frac{27}{7} \text{ mA} = -3.857 \text{ mA}$$

$$\boxed{I_o = -3.857 \text{ mA}}$$

3.58 Find V_o in the circuit in Fig. P3.58 using mesh analysis.


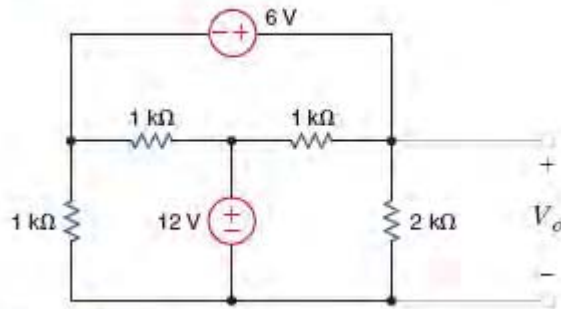


Figure P3.58

SOLUTION:

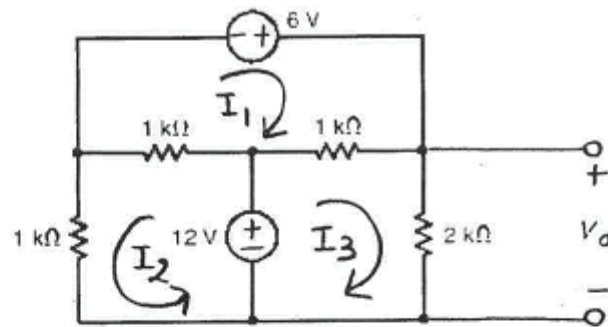

Let the mesh/loop currents be I_1 , I_2 & I_3 as shown in the diagram

KVL in loop 1 :

$$6 = (I_1)1 - I_3 + 1(I_1 + I_2)$$

$$\Rightarrow 6 = 2I_1 + I_2 - I_3 \quad \text{--- ①}$$

KVL in the loop 2 :

$$12 = 2I_2 + I_1 \quad \text{--- ②}$$

3.70 Using loop analysis, find V_o in the network in Fig. P3.70.


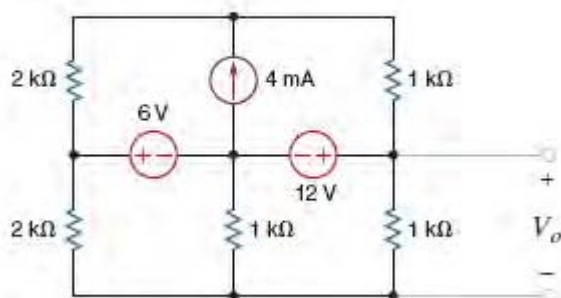


Figure P3.70

SOLUTION:

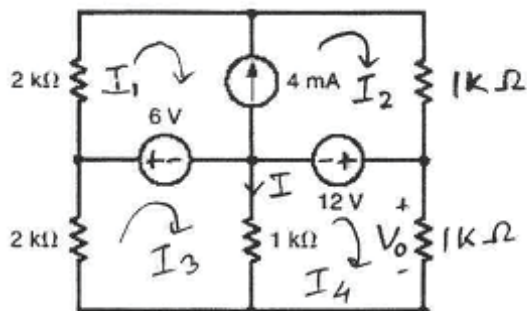

$$\text{KCL: } I + I_4 = I_3$$

$$I = I_3 - I_4$$

$$\text{KVL: } 6 = 2\text{K}I_1 + 1\text{K}I_2 + 12$$

$$\boxed{2\text{K}I_1 + 1\text{K}I_2 = -6}$$

$$\text{KVL: } 12 = 6 + 2\text{K}I_3 + 1\text{K}I_4$$

$$\boxed{2\text{K}I_3 + 1\text{K}I_4 = 6}$$

$$\text{KVL: } 2\text{K}I_3 + 6 + \text{K}I = 0$$

$$2\text{K}I_3 + 1\text{K}(I_3 - I_4) = -6$$

$$\boxed{3\text{K}I_3 - 1\text{K}I_4 = -6}$$

$$2\text{K}I_3 + 1\text{K}I_4 = 6$$

$$3\text{K}I_3 - 1\text{K}I_4 = -6$$

$$I_3 = 0\text{A}$$

$$I_4 = 6\text{mA}$$

$$V_o = 1\text{K}(I_4) = 6\text{V}$$

3.78 Use loop analysis to find V_o in the network in Fig. P3.78.


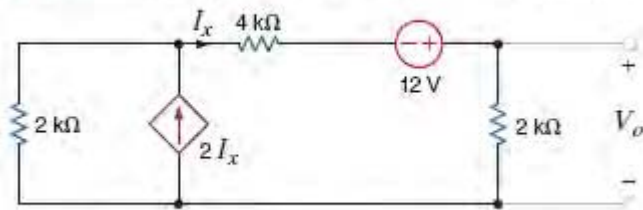


Figure P3.78

SOLUTION:

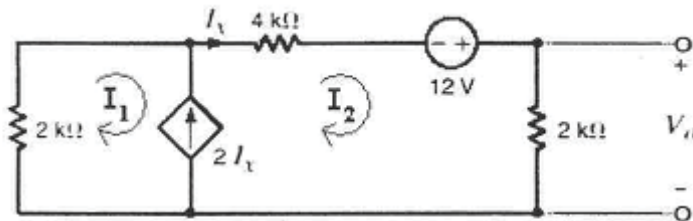

$$\text{KCL: } I_1 + 2I_x = I_x$$

$$I_1 = -I_x \text{ and } I_2 = I_x$$

$$\text{KVL: } 12 = 2kI_1 + 4kI_2 + 2kI_2$$

$$2kI_1 + 6kI_2 = 12$$

$$2k(-I_x) + 6k(I_x) = 12$$

$$4kI_x = 12$$

$$I_x = 3\text{mA}$$

$$V_o = 2kI_x = 2k(3\text{m})$$

$$V_o = 6\text{V}$$

- 3.86. Use mesh analysis to find V_o in the circuit in Fig. P3.86.


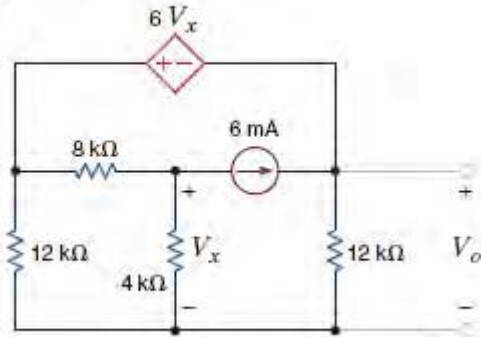


Figure P3.86

SOLUTION:

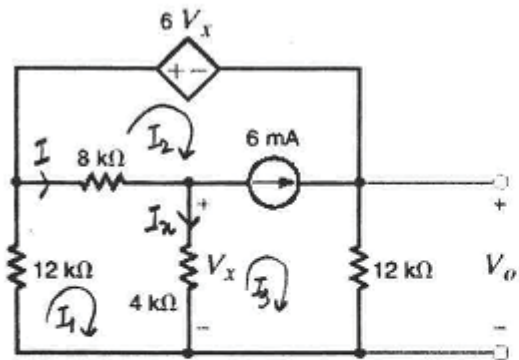

$$\text{KCL: } I_1 = I + I_2$$

$$I = I_1 - I_2$$

$$\text{KCL: } I = 6\text{m} + I_x$$

$$I_x = I_1 - I_2 - 6\text{m}$$

KVL lower left loop:

$$12\text{k} I_1 + 8\text{k} I + 4\text{k} I_x = 0$$

$$12\text{k} I_1 + 8\text{k}(I_1 - I_2) + 4\text{k}(I_1 - I_2 - 6\text{m}) = 0$$

$$\boxed{24\text{k} I_1 - 12\text{k} I_2 = 24}$$

$$\text{KVL outer loop: } 12kI_1 + 6V_x + 12kI_3 = 0$$

$$V_x = 4kI_x = 4k(I_1 - I_2 - 6m)$$

$$V_x = 4kI_1 - 4kI_2 - 24$$

$$12kI_1 + 6[4kI_1 - 4kI_2 - 24] + 12kI_3 = 0$$

$$36kI_1 - 24kI_2 + 12kI_3 = 144$$

$$\text{KCL: } I_x + I_3 = I_1$$

$$I_3 = I_1 - [I_1 - I_2 - 6m]$$

$$I_3 = I_2 + 6m$$

$$36kI_1 - 24kI_2 + 12k(I_2 + 6m) = 144$$

$$\boxed{36kI_1 - 12kI_2 = 72}$$

$$24kI_1 - 12kI_2 = 24$$

$$36kI_1 - 12kI_2 = 72$$

$$I_1 = 4mA$$

$$I_2 = 6mA$$

$$I_3 = 6m + 6m$$

$$I_3 = 12mA$$

$$V_o = 12k(I_3) = 12k(12m)$$

$$V_o = 144V$$