

- 5.1 Use linearity and the assumption that $V_o = 1\text{ V}$ to find the actual value of V_o in Fig. P5.1.


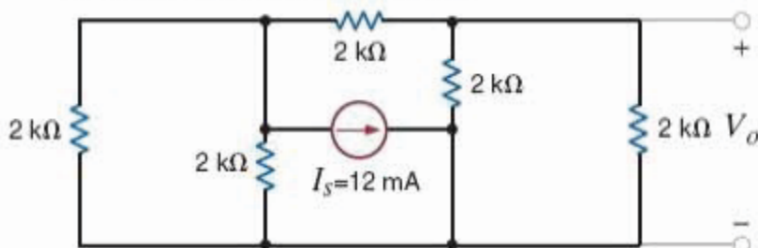


Figure P5.1

SOLUTION:

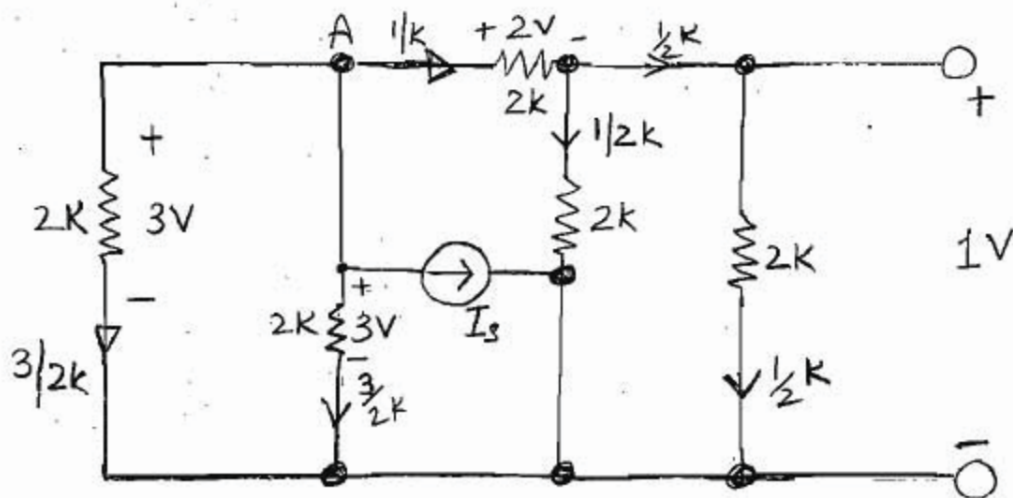

KCL at node

$$\frac{3}{2K} + \frac{3}{2K} + I_s + \frac{1}{K} = 0$$

$$I_s = -\frac{4}{K} \text{ A}$$

$$\frac{V_o}{I_s} = \frac{1}{-\frac{4}{K} \text{ A}} = \frac{V_o}{\frac{12}{K} \text{ A}} \Rightarrow V_o = -3\text{ V}$$

5.13 Find V_o in the circuit in Fig. P5.13 using superposition.


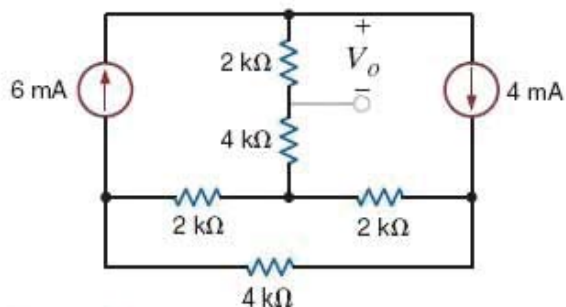
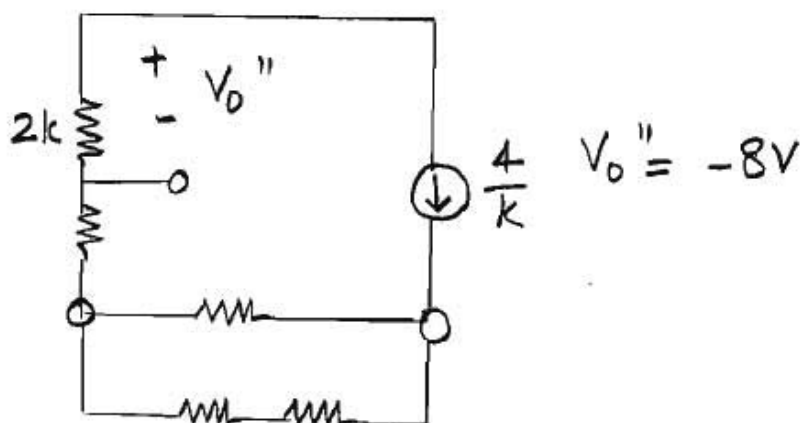


Figure P5.13

SOLUTION:

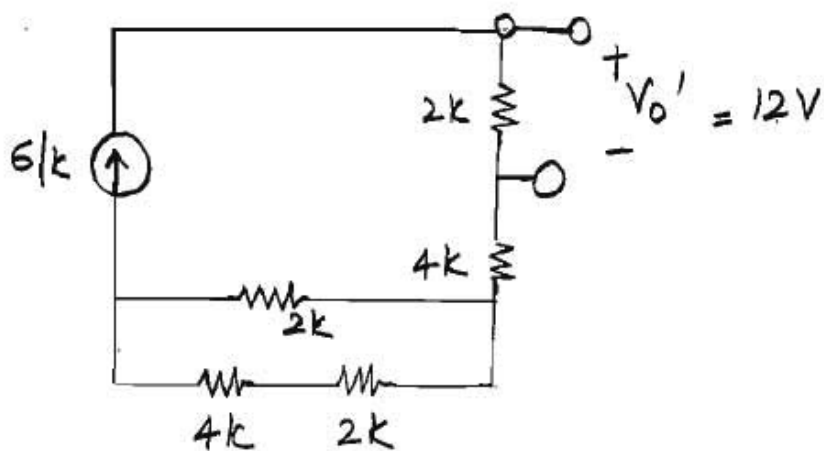

$$V_o = V_o' + V_o'' = 12 - 8 = 4V$$

5.21 Use superposition to find I_o in the circuit in Fig. P5.21.


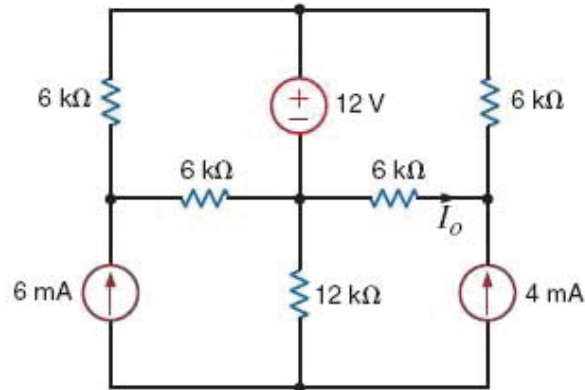
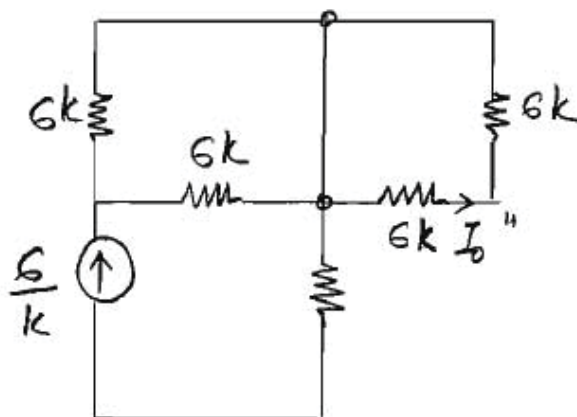
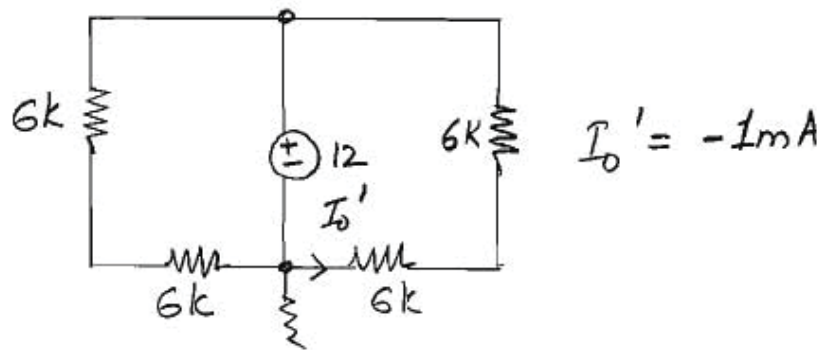



Figure P5.21

SOLUTION:

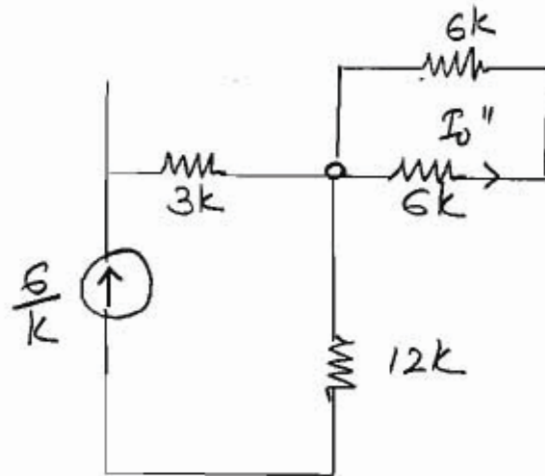

$I_0'' \Rightarrow$


$$I_0'' = 0$$

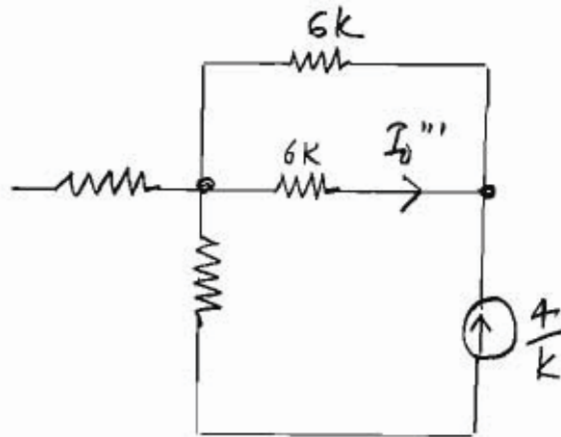

$$I_0''' = -2\text{mA}$$

$$I_0 = I_0' + I_0'' + I_0'''$$

$$= -1 + 0 - 2$$

$$= -3\text{mA}$$

- 5.4 Find I_o in the circuit in Fig. P5.4 using linearity and the assumption that $I_o = 1$ mA.


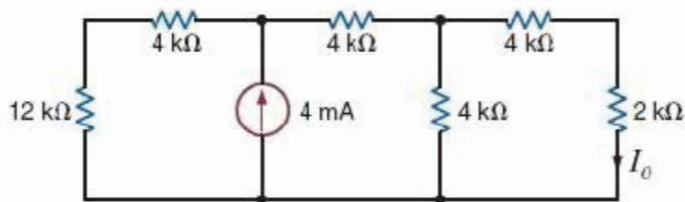


Figure P5.4

SOLUTION:

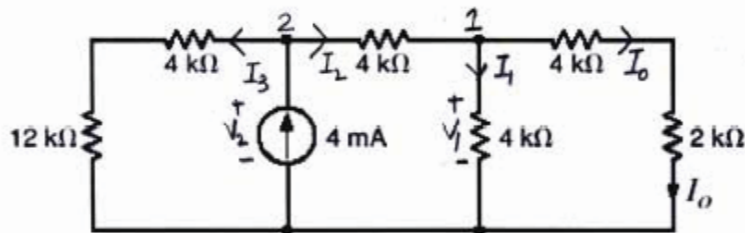

Assume $I_o = 1$ mA

$$V_1 = I_o (2k + 4k) = 1m (6k) = 6V$$

$$\text{KCL at 1: } I_2 = I_1 + I_o$$

$$I_2 = \frac{V_1}{4k} + I_o = \frac{6}{4k} + 1m = 2.5mA$$

KVL around middle loop:

$$V_2 = I_2 (4k) + V_1 = 2.5m (4k) + 6 = 16V$$

$$\text{KCL at 2: } I_3 = I_2 + I_o$$

$$I_3 = \frac{V_2}{16k} + 2.5m = \frac{16}{16k} + 2.5m = 3.5mA$$

Actually, $I_3 = 4mA$

$$I_o = 1m \left(\frac{4m}{3.5m} \right) = 1.14mA$$

5.40 Find I_o in the circuit in Fig. P5.40 using Thévenin's theorem.


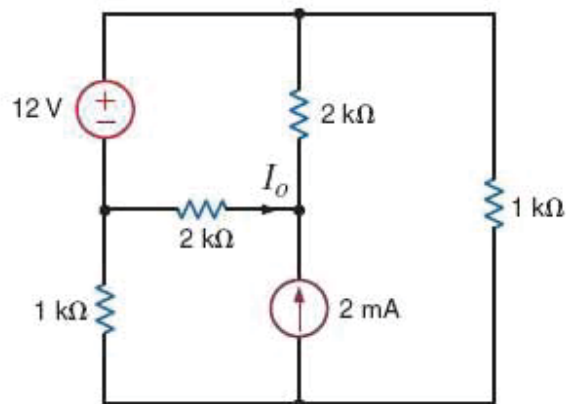




Figure P5.40

SOLUTION:

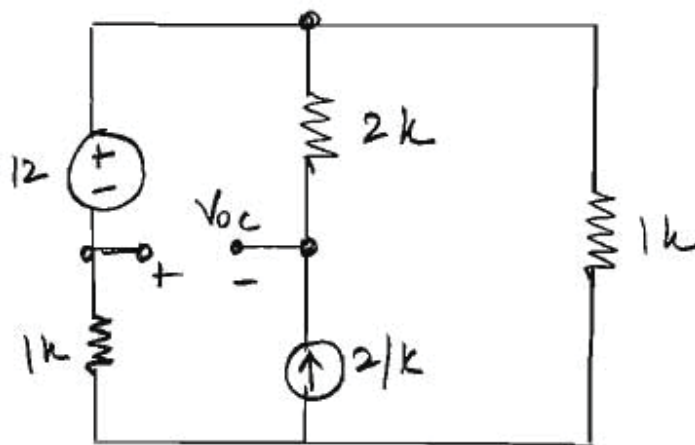

$$-V_{oc} - 12 - 2k \left(\frac{2}{k} \right) = 0$$

$$V_{oc} = -16V$$

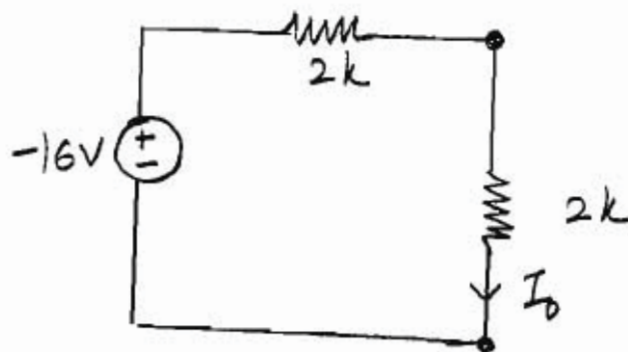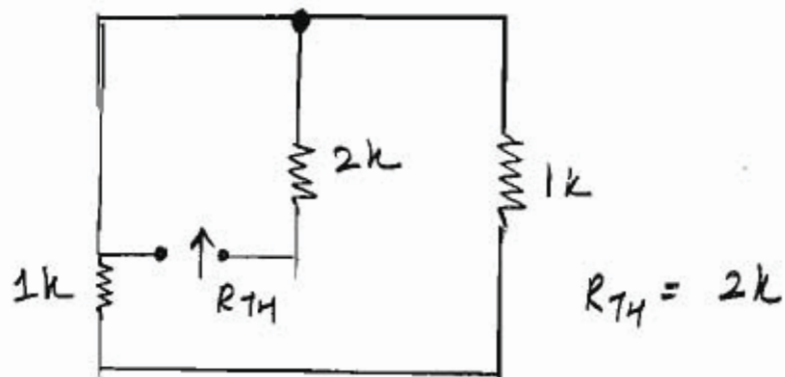

$$I_0 = \frac{-16}{4k} \\ = -4mA$$

5.53 Find I_o in the network in Fig. P5.53 using Norton's theorem.


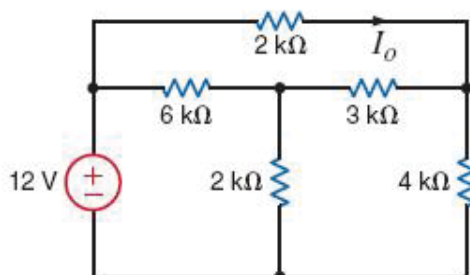


Figure P5.53

SOLUTION:

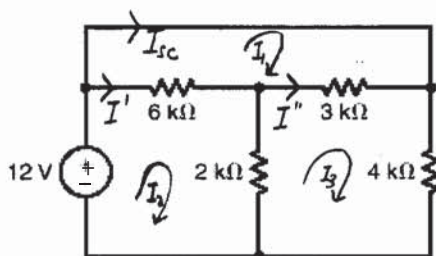

$$\begin{aligned} I_1 &= I_{sc} \\ I_2 &= I' + I_{sc} \\ I' &= I_2 - I_1 \\ I'' + I_1 &= I_3 \\ I'' &= I_3 - I_1 \\ I &= I_2 - I_3 \end{aligned}$$

$$\text{KVL left loop: } 12 = 6kI' + 2kI$$

$$12 = 6k(I_2 - I_1) + 2k(I_2 - I_3)$$

$$\text{KVL right loop: } 3kI'' + 4kI_3 - I(2k) = 0$$

$$3k(I_3 - I_1) + 4kI_3 - (I_2 - I_3)(2k) = 0$$

$$-3kI_1 - 2kI_2 + 9kI_3 = 0$$

$$\text{KVL outer loop: } 12 = 4kI_3$$

$$I_3 = 3\text{mA}$$

$$-3kI_1 - 2kI_2 = -27$$

$$12 = -6kI_1 + 8kI_2 - 2k(3\text{mA})$$


$$-6kI_1 + 8kI_2 = 18$$

$$-3kI_1 - 2kI_2 = -27$$


$$I_1 = 5\text{mA}$$

$$I_2 = 6\text{mA}$$

$$I_{sc} = 5\text{mA}$$

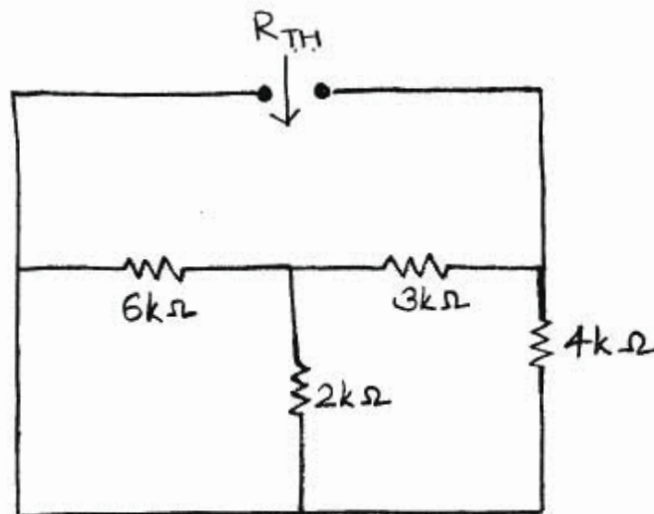
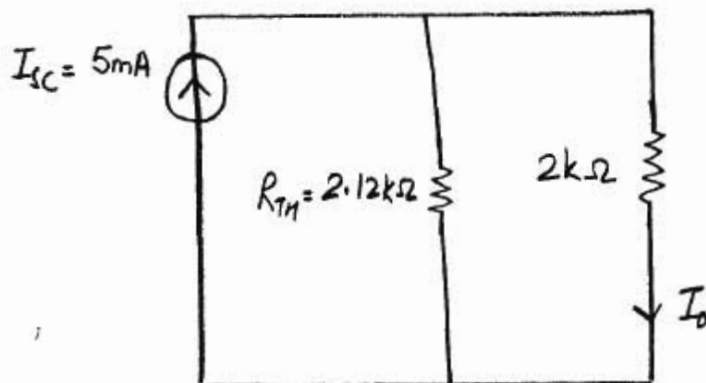
$$R_{TH} = [(6k \parallel 2k) + 3k] \parallel 4k = 2.12k\Omega$$



$$I_0 = \left(\frac{2.12k}{2.12k + 2k} \right) (5m) = 2.57mA$$

5.6 Find I_o in the network in Fig. P5.6 using superposition.



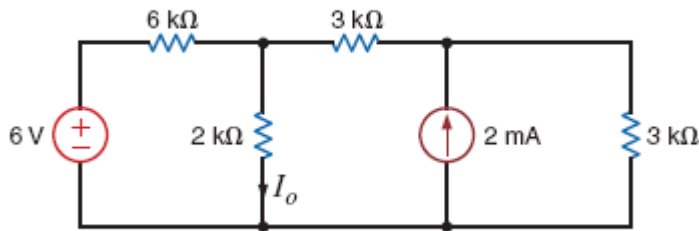


Figure P5.6

SOLUTION:

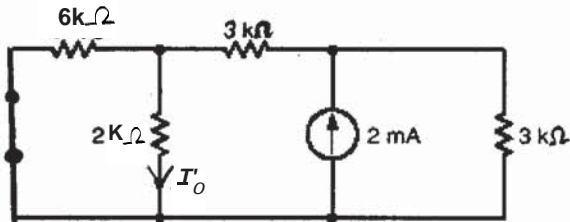


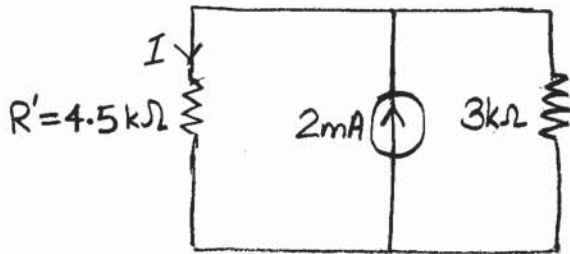
$$R' = (6k \parallel 2k) + 3k = 4.5k \Omega$$



$$I = \frac{3k}{3k + 4.5k} (2m) = 0.8mA$$
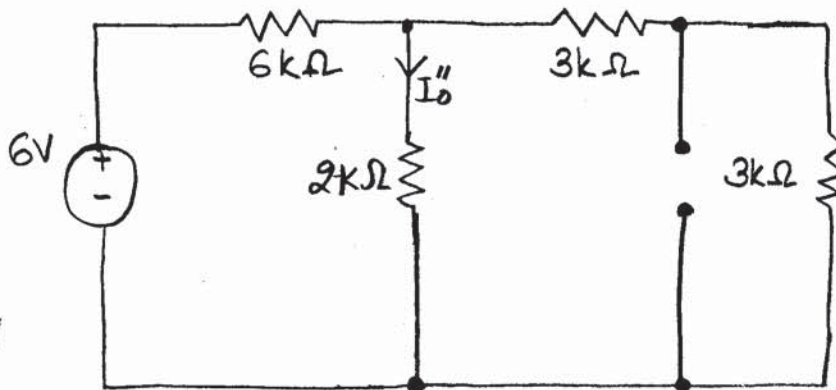
$$I_o' = \frac{6k}{6k + 2k} (0.8m) = 0.6mA$$



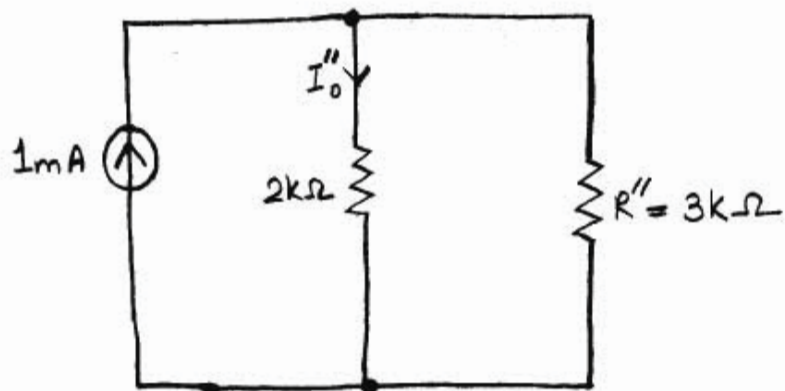

$$R'' = (6k \parallel (3k + 3k)) = 3k\Omega$$

$$I''_0 = \left(\frac{3k}{2k + 3k} \right) (1m) = 0.6mA$$

$$I_0 = 0.6m + 0.6m = 1.2mA$$

5.66 Find V_o in the circuit in Fig. P5.66 using Thévenin's theorem.


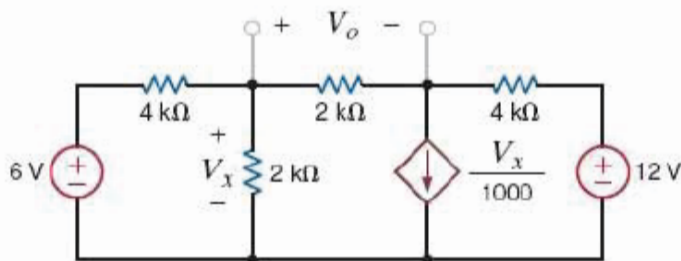


Figure P5.66

SOLUTION:

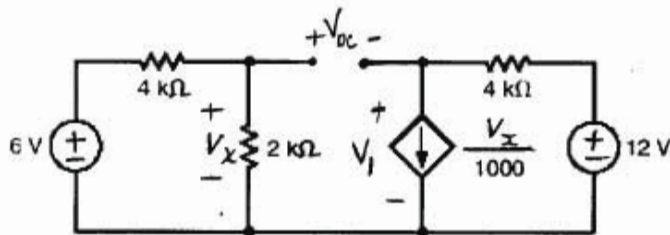


$$V_x = \left(\frac{2k}{2k + 4k} \right) (6) = 2V$$

$$V_1 + \frac{V_x}{1000} (4k) = 12$$

$$V_1 = 4V$$

$$V_{oc} = V_x - V_1$$

$$V_{oc} = 2 - 4 = -2V$$

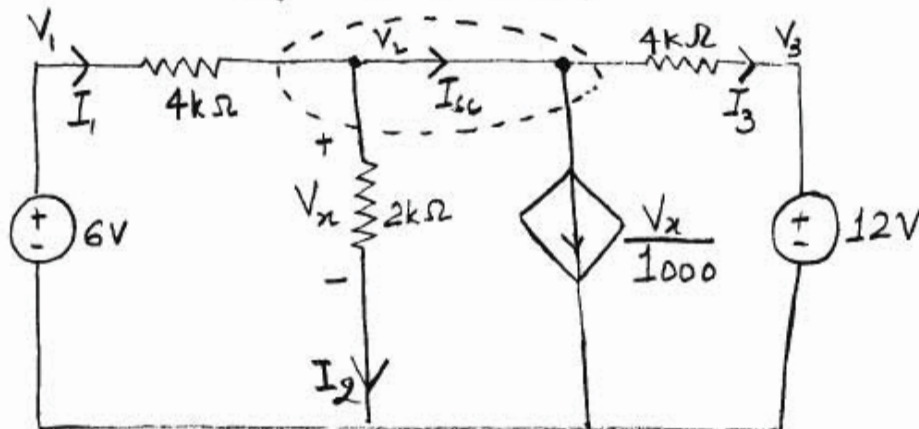

$$V_x = V_2$$

$$V_1 = 6V$$

$$V_3 = 12V$$

$$\frac{V_1 - V_2}{4k} = \frac{V_2}{2k} + \frac{V_x}{1000} + \frac{V_2 - V_3}{4k}$$

$$\frac{6 - V_2}{4k} = \frac{V_2}{2k} + \frac{V_2}{1000} + \frac{V_2 - 12}{4k}$$

$$V_2 = 2.25V$$


$$\frac{V_1 - V_2}{4k} = \frac{V_2}{2k} + I_{sc}$$

$$I_{sc} = \frac{6 - 2.25}{4k} - \frac{2.25}{2k}$$

$$= -0.1875 \text{ mA}$$

$$R_{TH} = \frac{-2}{-0.1875 \text{ mA}}$$

$$= 10.67 \text{ k}\Omega$$

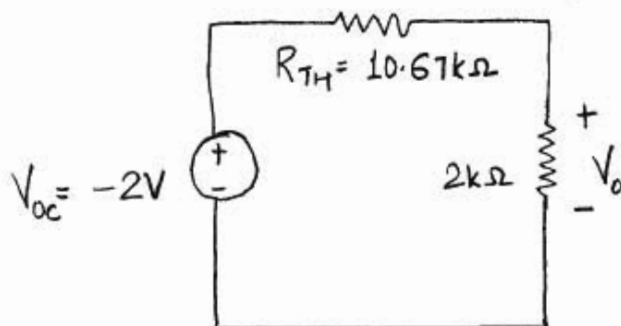

$$V_o = \left(\frac{2k}{2k + 10.67k} \right) (-2) = -0.316V$$

5.85 Use source transformation to find V_o in the network in Fig. P5.85.



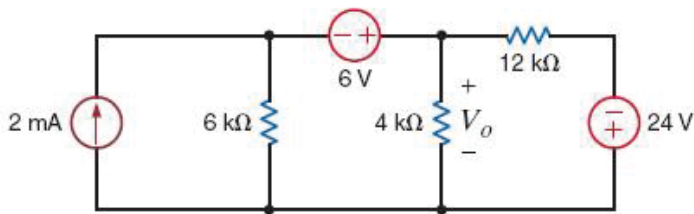
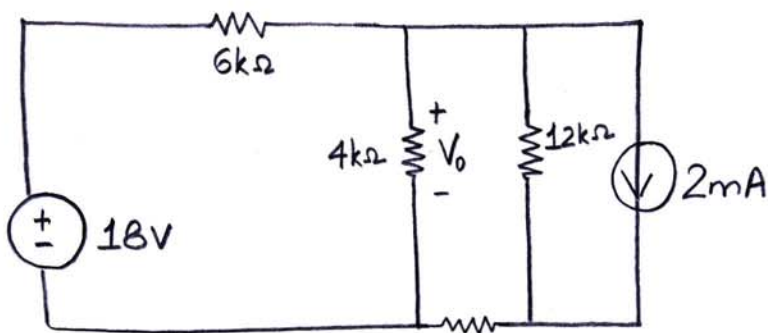
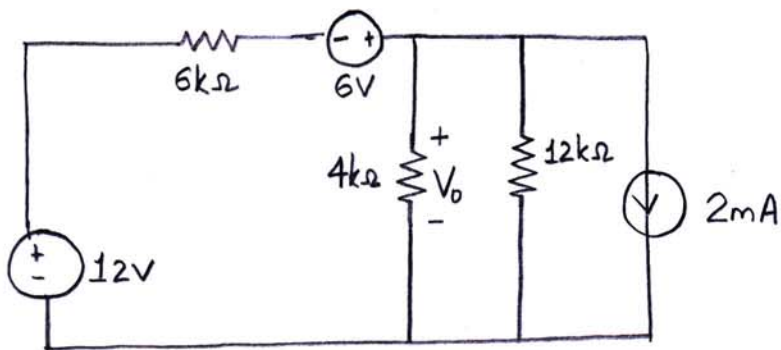


Figure P5.85

SOLUTION:

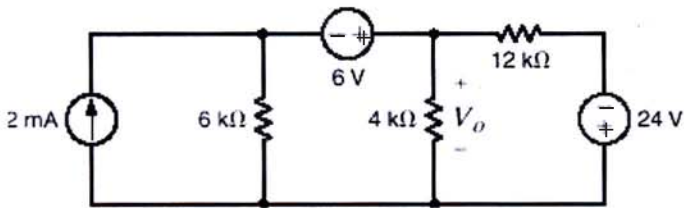

$$R = 4k \parallel 12k$$

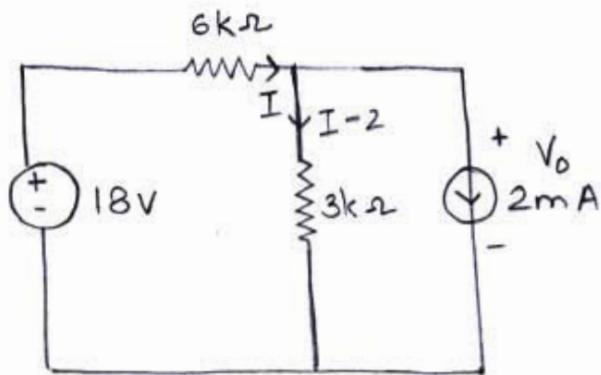

$$18 - 6kI - 3k(I-2) = 0$$

$$\frac{24}{9k} = I$$

$$2.66\text{mA} = I$$

$$\therefore 3k(I-2) = 2\text{V} = V_0$$

5.91 Find I_o in the circuit in Fig. P5.91 using source transformation.



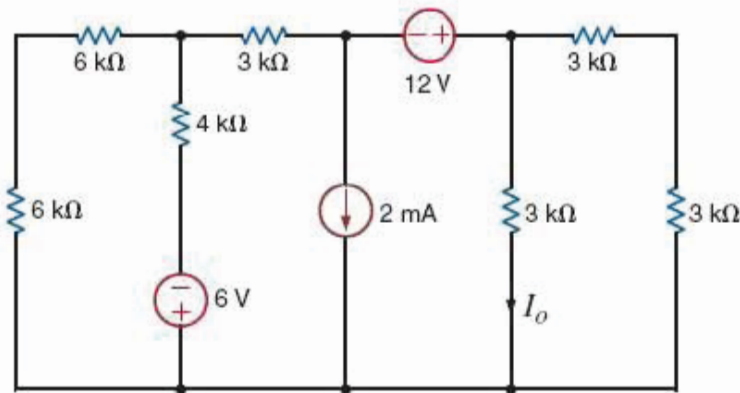





Figure P5.91

SOLUTION:

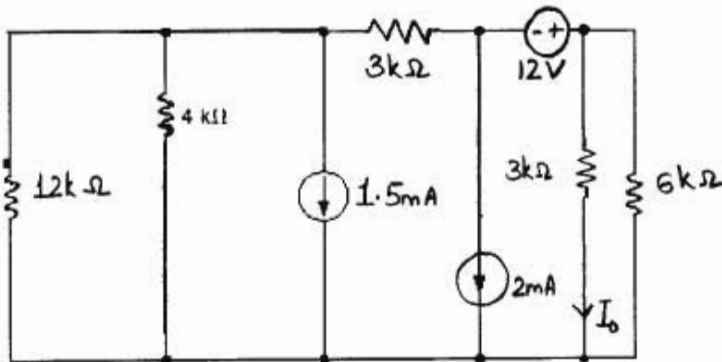


$$R' = 12k \parallel 4k = 3k\Omega$$

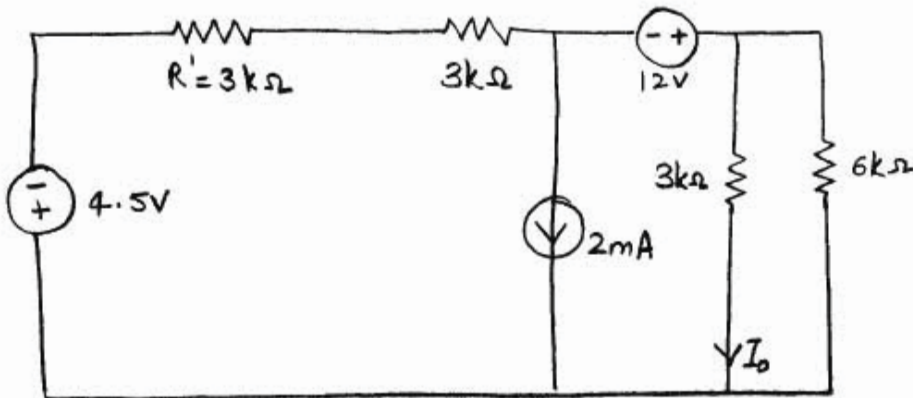

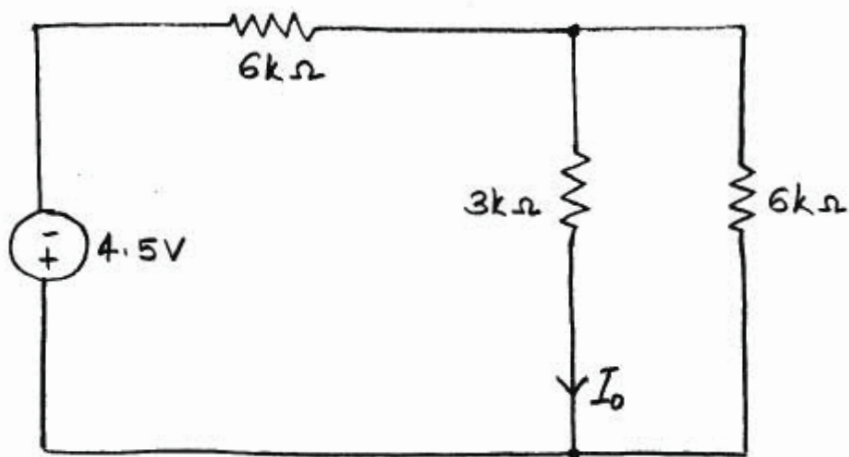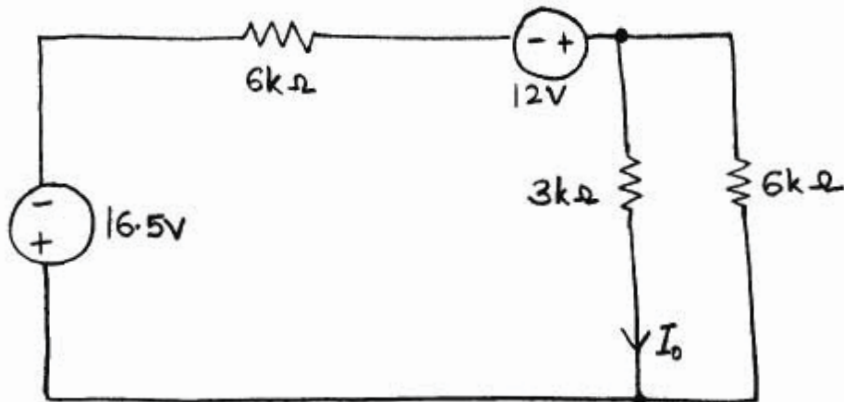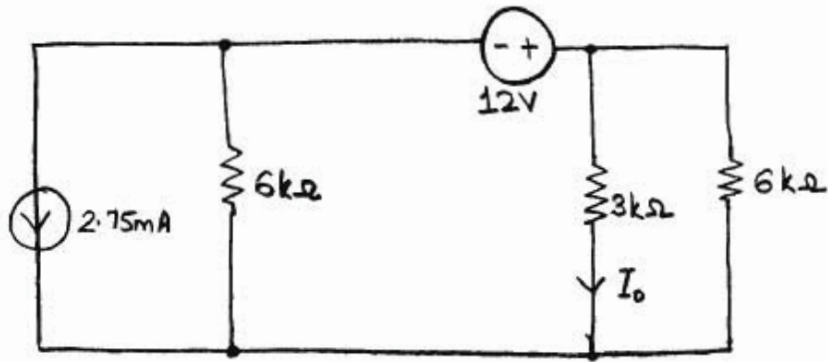
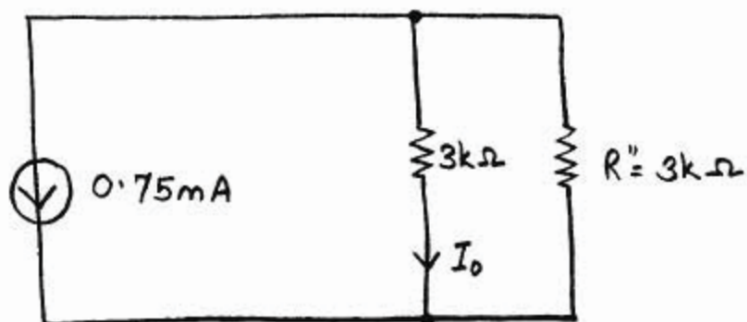
$$R'' = 6\text{k} \parallel 6\text{k} = 3\text{k}\Omega$$



$$\begin{aligned} I_0 &= \left(\frac{3\text{ k}}{3\text{ k} + 3\text{ k}} \right) (-0.75\text{ mA}) \\ &= -0.375\text{ mA} \end{aligned}$$

- 6.1** An uncharged 100- μF capacitor is charged by a constant current of 1 mA. Find the voltage across the capacitor after 4 s.

SOLUTION:

$$V(t) = \frac{1}{C} \int_0^T i(t) dt$$

$$V(t) = \frac{1}{100\mu} \int_0^4 1 \text{ m} dt$$

$$V(t) = \frac{1}{100\mu} [1 \text{ m}(4) - 0]$$

$$V(t) = 40\text{V}$$

or

$$V = 40\text{V}$$

6.20 The waveform for the current in a $50\text{-}\mu\text{F}$ initially uncharged capacitor is shown in Fig. P6.20. Determine the waveform for the capacitor's voltage.

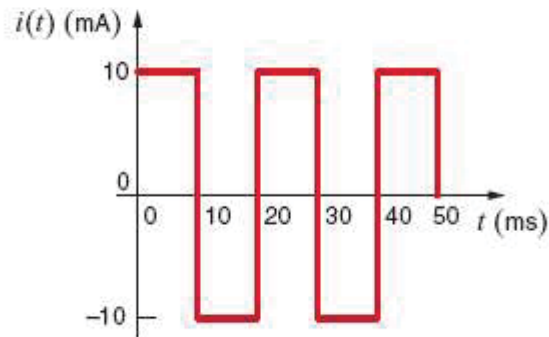


Figure P6.20

SOLUTION:

$$v_C(t) = \frac{1}{C} \int i_C(t) dt + v_0$$

$$\text{for } i(t) = 10 \text{ mA}$$

$$v_C(t) = \frac{1}{50\mu} \int 10 \text{ m} dt + v_0$$

$$v_C(t) = 200t + v_0$$

$$\text{for } i(t) = -10 \text{ mA}$$

$$v_C(t) = \frac{1}{50} \int -10 \text{ m} dt + v_0$$

$$v_C(t) = -200t + v_0$$

$$\text{for } t < 0$$

$$v_C(t) = 0$$

$$\text{for } 0 \leq t \leq 10 \text{ ms}$$

$$v_C(t) = 200t \text{ V}$$

$$\text{for } 10\text{ms} \leq t \leq 20\text{ms}$$

$$v_C(t) = -200t + 4 \text{ V}$$

$$\text{for } 20\text{ms} \leq t \leq 30\text{ms}$$

$$v_C(t) = 200t - 4 \text{ V}$$

$$\text{for } 30\text{ms} \leq t \leq 40\text{ms}$$

$$v_C(t) = -200t + 8 \text{ V}$$

$$\text{for } 40\text{ms} \leq t \leq 50\text{ms}$$

$$v_C(t) = 200t - 8 \text{ V}$$

$$\text{for } t \geq 50\text{ms}$$

$$v_C(t) = 0 \text{ V}$$

$$v_C(t) = \begin{cases} 0 & t < 0 \\ 200t \text{ V} & 0 \leq t \leq 10\text{ms} \\ 4 - 200t \text{ V} & 10\text{ms} \leq t \leq 20\text{ms} \\ -4 + 200t \text{ V} & 20\text{ms} \leq t \leq 30\text{ms} \\ 8 - 200t \text{ V} & 30\text{ms} \leq t \leq 40\text{ms} \\ -8 + 200t \text{ V} & 40\text{ms} \leq t \leq 50\text{ms} \\ 0 & 50\text{ms} \leq t \leq 60\text{ms} \end{cases}$$

6.22 The current in an inductor changed from 0 to 200 mA in 4 ms and induces a voltage of 100 mV. What is the value of the inductor?

SOLUTION:

$$V(t) = L \frac{di(t)}{dt}$$

$$V = L \frac{\Delta I}{\Delta t}$$

$$\Delta I = 200 \text{ mA}$$

$$\Delta t = 4 \text{ ms}$$

$$L = V \left(\frac{\Delta t}{\Delta I} \right)$$

$$L = 100 \text{ m} \left(\frac{4 \text{ m}}{200 \text{ m}} \right)$$

$$L = 2 \text{ mH}$$

- 6.37** Draw the waveform for the voltage across a 24-mH inductor when the inductor current is given by the waveform shown in Fig. P6.37.

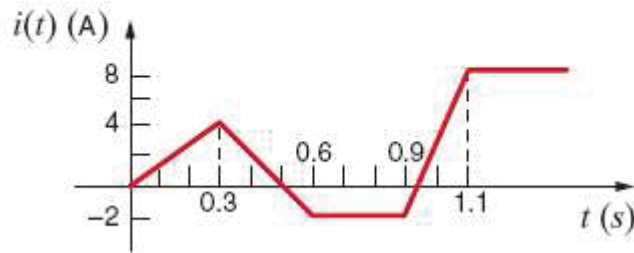


Figure P6.37

SOLUTION:

$$v(t) = L \frac{di(t)}{dt}$$

$$\text{for } t \leq 0, \quad v(t) = 0$$

$$\text{for } 0 \leq t \leq 0.3 \text{ s}$$

$$v(t) = 24 \text{ m} \left[\frac{40}{3} \right]$$

$$v(t) = 320 \text{ mV}$$

$$\text{for } 0.3 \text{ s} < t \leq 0.6 \text{ s}$$

$$v(t) = 24 \text{ m} [-20]$$

$$v(t) = -480 \text{ mV}$$

$$\text{for } 0.6 \text{ s} < t \leq 0.9 \text{ s}$$

$$v(t) = 0$$

$$\text{for } 0.9 \text{ s} < t \leq 1.1 \text{ s}$$


$$V(t) = 24 \text{ m} [50]$$

$$V(t) = 1200 \text{ mV}$$

$$\text{for } t > 1.15$$

$$V(t) = 0$$
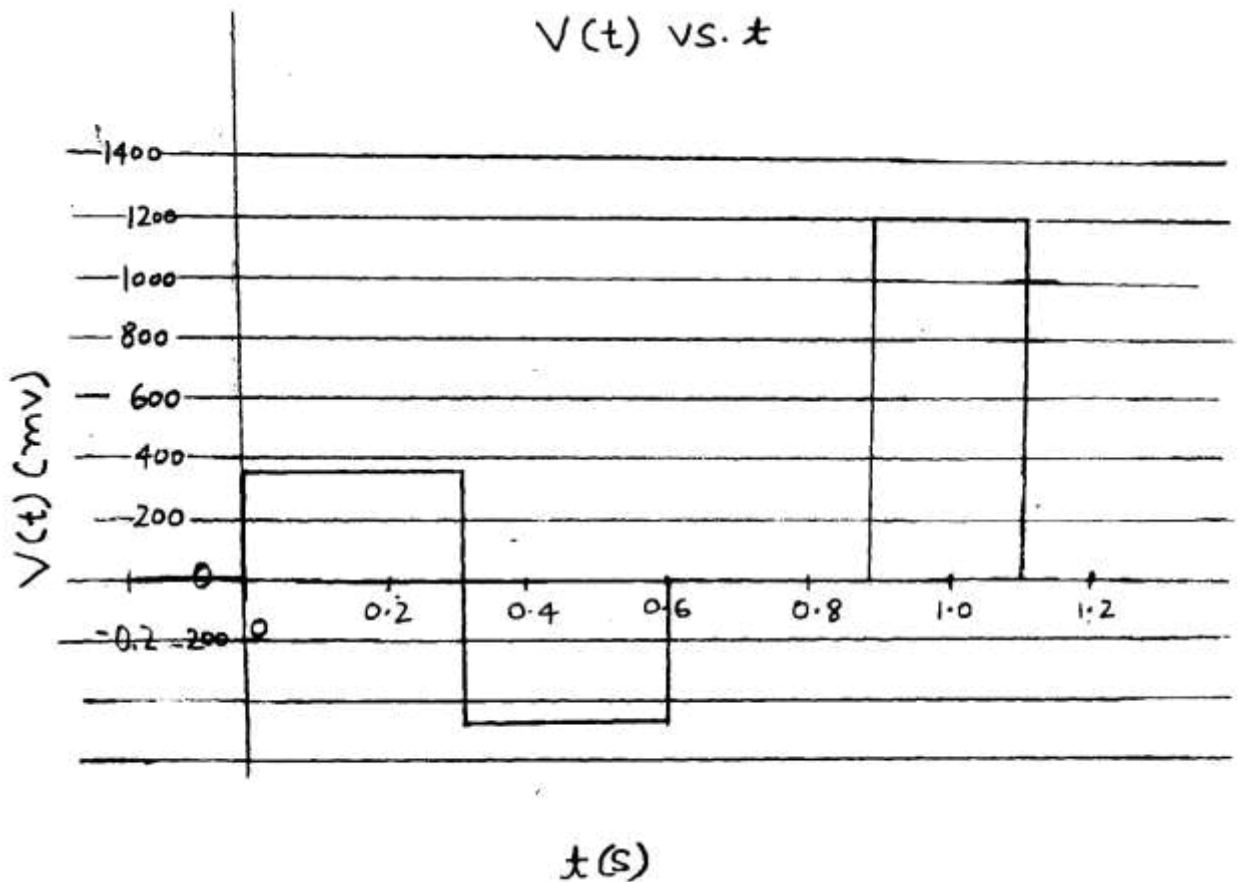
$$V(t) = \begin{cases} 0 & t \leq 0 \\ 320 \text{ mV} & 0 < t \leq 0.3 \text{ s} \\ -480 \text{ mV} & 0.3 \text{ s} < t \leq 0.6 \text{ s} \\ 0 & 0.6 \text{ s} < t \leq 0.9 \text{ s} \\ 1200 \text{ mV} & 0.9 \text{ s} < t \leq 1.1 \text{ s} \\ 0 & t > 1.1 \text{ s} \end{cases}$$



6.50 Find the total capacitance C_T of the network in Fig. P6.50.


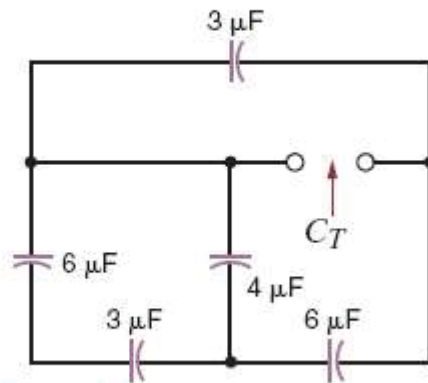


Figure P6.50

SOLUTION:

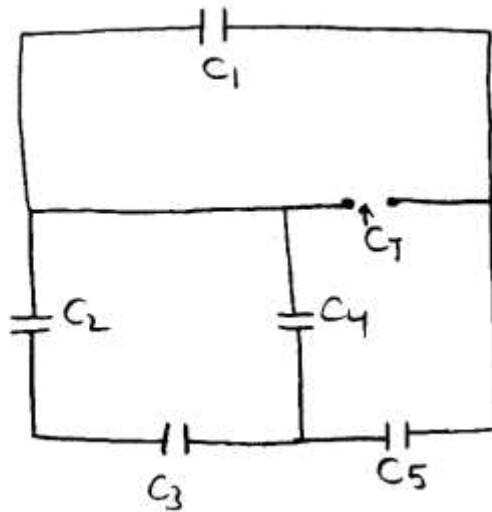


$$C_1 = 3\mu\text{F}, C_2 = 6\mu\text{F}, C_3 = 3\mu\text{F}, \\ C_4 = 4\mu\text{F}, C_5 = 6\mu\text{F}$$

$$C' = 4\mu + \frac{6\mu(C_3)}{6\mu + C_3}$$

$$C' = 4\mu + \frac{6\mu(3\mu)}{6\mu + 3\mu}$$

$$C' = 6\mu\text{F}$$

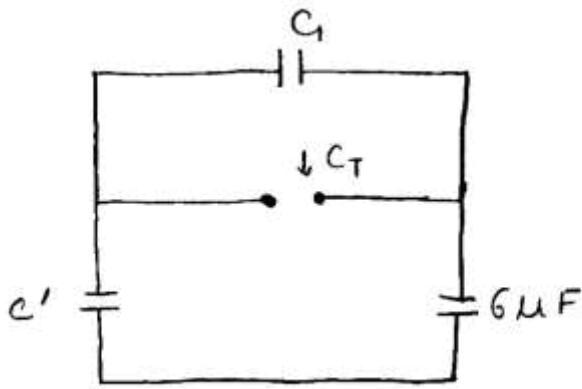

$$C_T = \frac{C'(6\mu)}{C' + 6\mu} + C_1$$

$$C_T = \frac{6\mu(6\mu)}{6\mu + 6\mu} + 3\mu$$

$$C_T = 6\mu F$$

6.56 Find C_T in the circuit in Fig. P6.56 if all capacitors are $6 \mu\text{F}$.


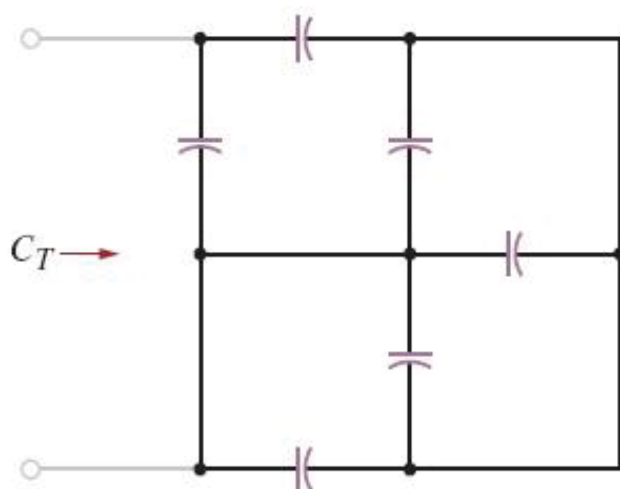
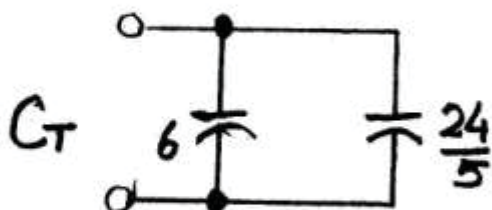
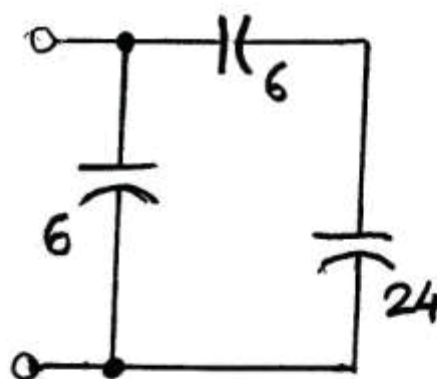


Figure P6.56

SOLUTION:

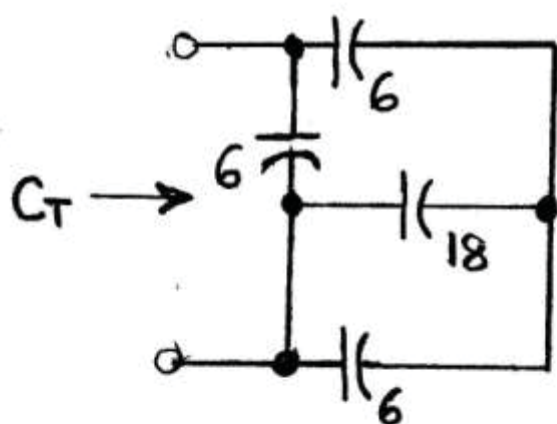

$$\frac{24}{5} + 6 = \frac{24}{5} + \frac{30}{5} = \frac{54}{5} \mu\text{F} = C_T$$

6.69 Determine the inductance at terminals A-B in the network in Fig. P6.69.


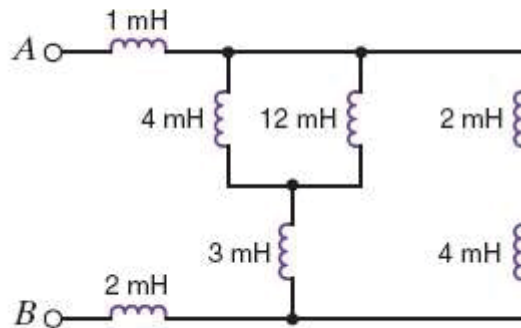


Figure P6.69

SOLUTION:

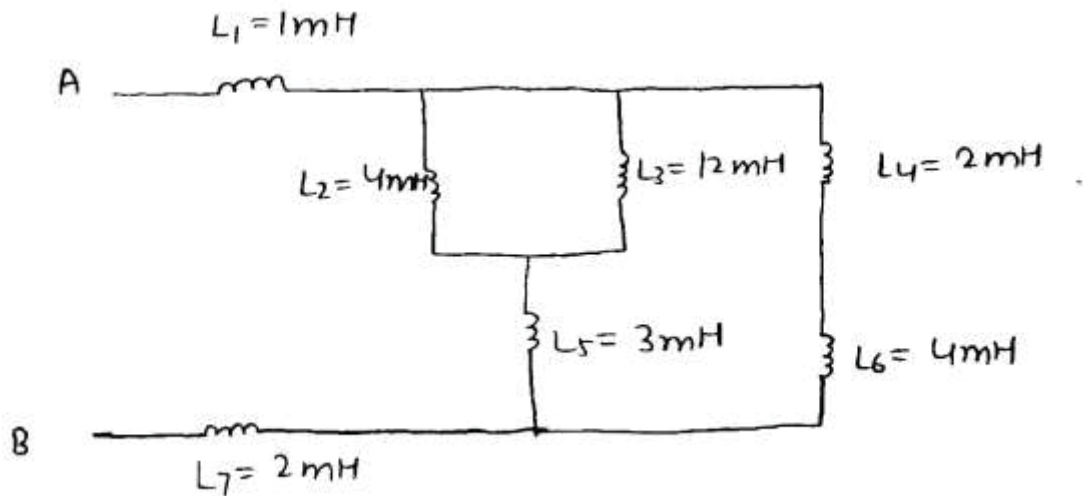

$$L_{AB} = [(L_4 + L_6)] \parallel [(L_2 \parallel L_3) + L_5] + L_1 + L_7$$

$$L_{AB} = [6\text{m}] \parallel \left[\frac{4\text{m}(12\text{m})}{4\text{m} + 12\text{m}} + 3\text{m} \right] + 1\text{m} + 2\text{m}$$

$$L_{AB} = [6\text{m}] \parallel [3\text{m} + 3\text{m}] + 3\text{m}$$

$$L_{AB} = 3\text{m} + 3\text{m}$$

$$L_{AB} = 6\text{mH}$$

6.72 Find L_T in the circuit in Fig. P6.72.


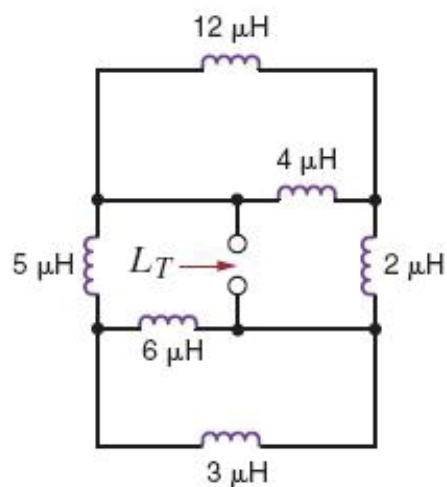


Figure P6.72

SOLUTION:

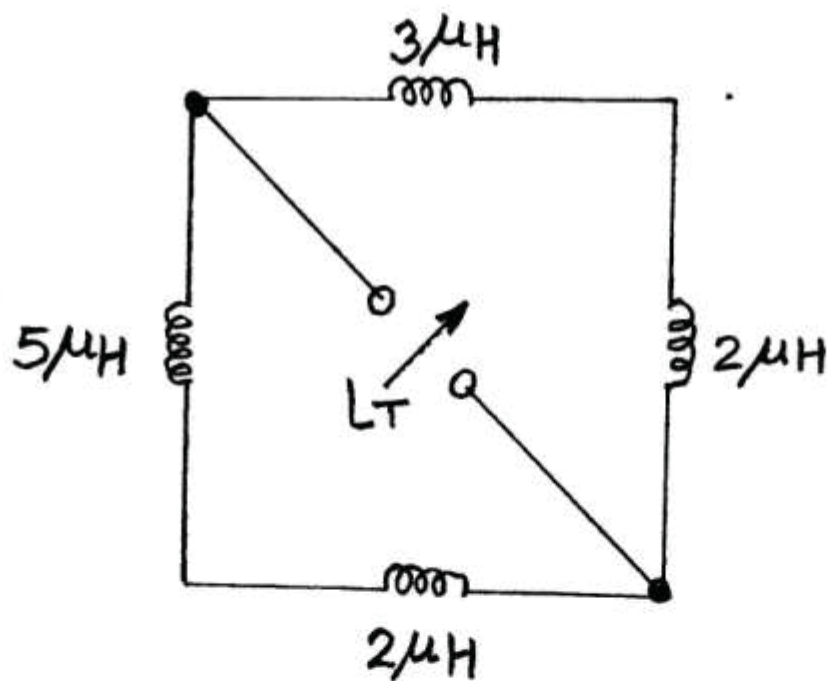

$$L_T = 7 \mu\text{H} // 5 \mu\text{H}$$

$$= \frac{35}{12} \mu\text{H}$$

- 6.9 The voltage across a 20- μF capacitor is shown in Fig. P6.9. Determine the waveform for the current in the capacitor.

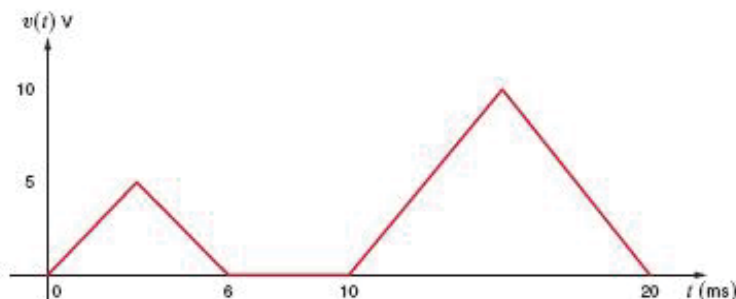


Figure P6.9

SOLUTION:

$$i(t) = \frac{cdv}{dt} = 20 \times 10^{-6} \frac{dv}{dt}$$

$$v(t) = \frac{5}{3 \times 10^{-3}} t \quad 0 \leq t \leq 3 \text{ ms}$$

$$= \frac{-5}{3 \times 10^{-3}} t + 6 \quad 3 \text{ ms} \leq t \leq 6 \text{ ms}$$

$$= 0 \quad 6 \text{ ms} \leq t \leq 10 \text{ ms}$$

$$= \frac{10}{5 \times 10^{-3}} t - 20 \quad 10 \text{ ms} \leq t \leq 15 \text{ ms}$$

$$= \frac{-10}{5 \times 10^{-3}} t + 20 \quad 15 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$i(t) = 20 \times 10^{-6} \left(\frac{5}{3} \times 10^3 \right) = \frac{1}{3} \times 10^{-1} = 33.3 \text{ mA} \quad 0-3 \text{ ms}$$

$$= -33.3 \text{ mA} \quad 3-6 \text{ ms}$$

$$= 0 \quad 6-10 \text{ ms}$$

$$= (20 \times 10^{-6})(2 \times 10^3) = 40 \text{ mA} \quad 10-15 \text{ ms}$$

$$= -40 \text{ mA} \quad 15-20 \text{ ms}$$

