

- 7.5 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.5.


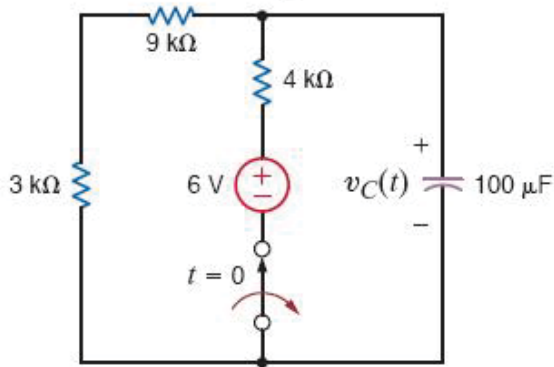


Figure P7.5

SOLUTION:


for $t = 0^-$:

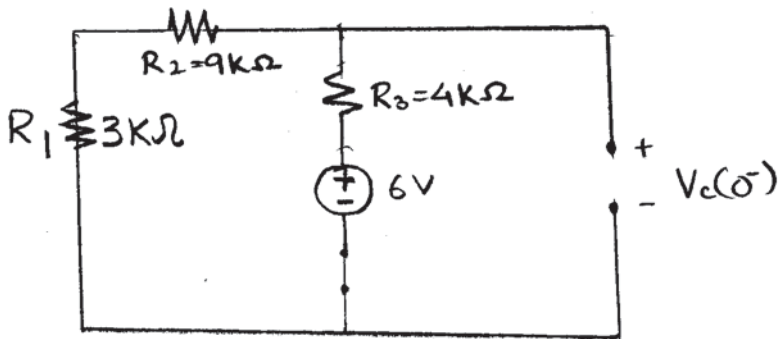

$$V_C(0^-) = \left(\frac{R_1 + R_2}{R_1 + R_2 + R_3} \right) (6)$$

$$V_C(0^-) = 4.5 \text{ V}$$

for $t > 0$:

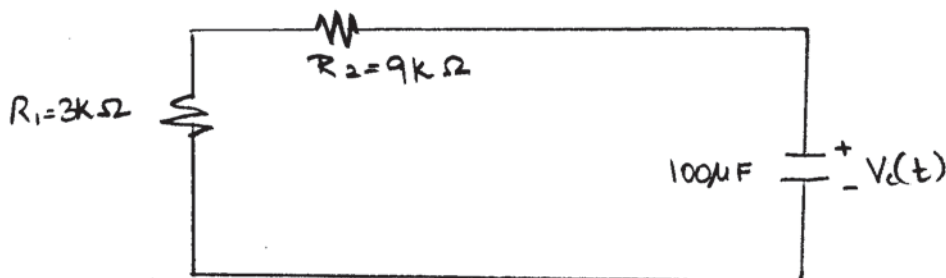

$$C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R_1 + R_2} = 0$$

$$\frac{dV_c(t)}{dt} + \frac{V_c(t)}{(R_1 + R_2)C} = 0$$

$$r + \frac{1}{(R_1 + R_2)C} = 0$$

$$r = \frac{-1}{(R_1 + R_2)C}$$

$$V_c(t) = A e^{\gamma t}$$

$$V_c(t) = A e^{-\frac{t}{(R_1 + R_2)C}}$$

$$V_c(0^-) = 4.5 \text{ V} = V_c(0^+)$$

$$A = 4.5$$

$$V_c(t) = 4.5 e^{-\frac{t}{10.2}} \text{ V}, t > 0$$

- 7.7 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.7 and plot the response including the time interval just prior to opening the switch.


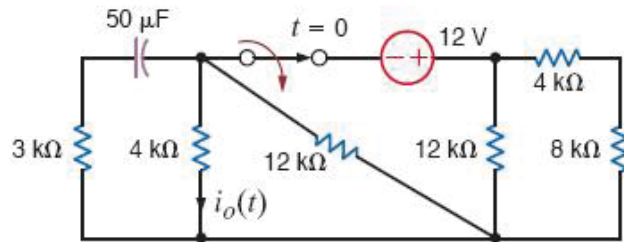


Figure P7.7

SOLUTION:

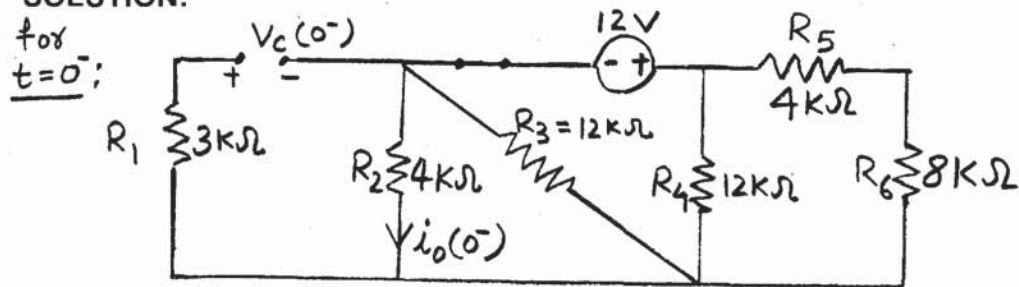

$$R_x = R_4 \parallel (R_5 + R_6) = 6 \text{ k}\Omega$$

$$R_y = R_2 \parallel R_3 = 3 \text{ k}\Omega$$



$$V_C(0^-) = \left(\frac{R_y}{R_x + R_y} \right) (12)$$

$$V_C(0^-) = 4 \text{ V}$$

$$i_o(0^-) = -\frac{V_C(0^-)}{R_2}$$

$$= -\frac{4}{4\text{K}}$$

$$i_o(0^-) = -1 \text{ mA}$$

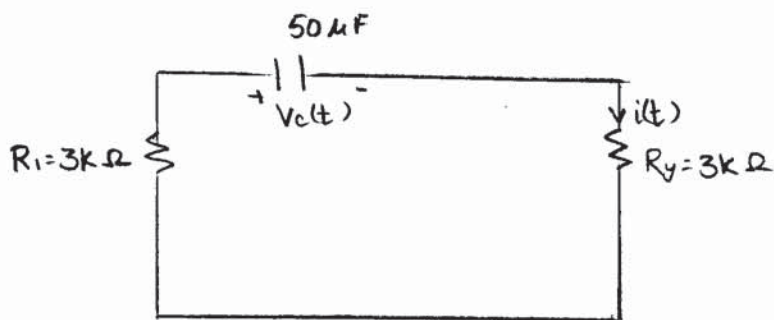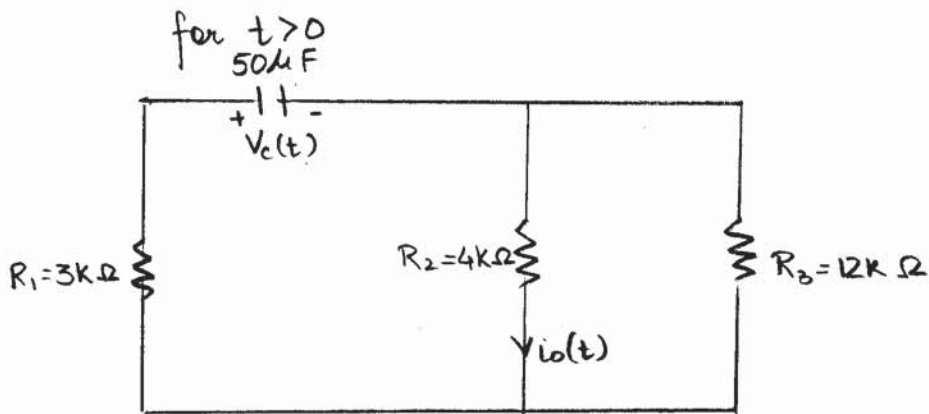

KVL:

$$V_c(t) + R_y i(t) + R_1 i(t) = 0$$

$$i(t) = C \frac{dV_c(t)}{dt}$$

$$R_y C \frac{dV_c(t)}{dt} + R_1 C \frac{dV_c(t)}{dt} + V_c(t) = 0$$

$$\frac{dV_c(t)}{dt} + \frac{V_c(t)}{(R_1 + R_y)C} = 0$$

$$\gamma + \frac{1}{(R_1 + R_y)C} = 0$$

$$\gamma = -\frac{1}{(R_1 + R_y)C}$$

$$V_c(t) = A e^{\gamma t}$$

$$V_c(t) = A e^{\frac{-t}{(R_1 + R_2)C}}$$

$$V_c(t) = A e^{\frac{-t}{0.3}}$$

$$V_c(0^-) = 4V = V_c(0^+)$$

$$A = 4$$

$$V_c(t) = 4 e^{\frac{-t}{0.3}} \text{ V, } t > 0$$

KVL:

$$R_2 i_o(t) + R_1 C \frac{dV_c(t)}{dt} + V_c(t) = 0$$

$$i_o(t) = \frac{-V_c(t) - R_1 C \frac{dV_c(t)}{dt}}{R_2}$$


$$\frac{dV_c(t)}{dt} = -13.333 e^{-t/0.3}$$

$$i_o(t) = \frac{-4 e^{-\frac{t}{0.3}} - (3 \times 10^3)(50 \times 10^{-6})(-13.333 e^{-\frac{t}{0.3}})}{4 \times 10^3}$$

$$i_o(t) = \frac{-2 e^{-\frac{t}{0.3}}}{4 \times 10^3}$$

$$i_o(t) = -0.5 e^{-\frac{t}{0.3}} \text{ mA, } t > 0$$

$$i_o(0^-) = -1\text{mA}$$

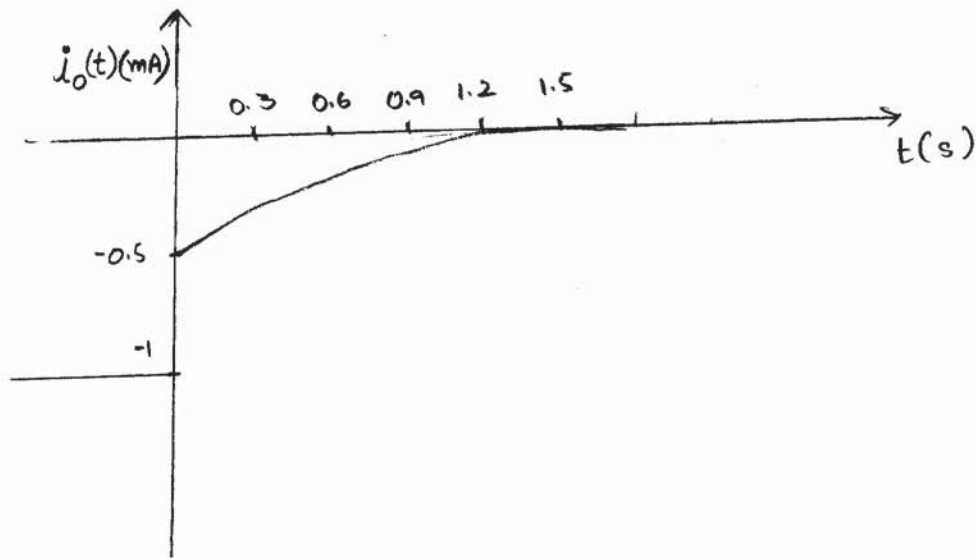

7.10 In the network in Fig. P7.10, find $i_o(t)$ for $t > 0$ using the differential equation approach.


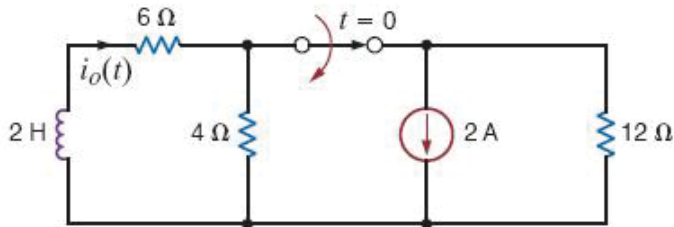


Figure P7.10

SOLUTION: for $t = 0^-$:

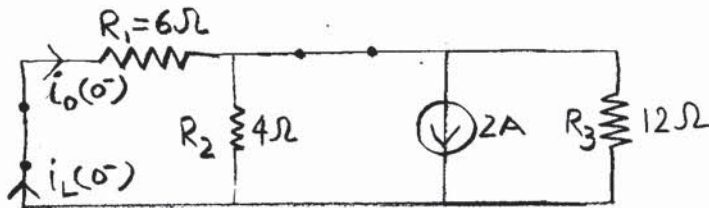


$$R' = R_2 \parallel R_3 = 3\Omega$$

$$i_L(0^-) = \left(\frac{R'}{R_1 + R'} \right) (2)$$

$$i_L(0^-) = \frac{2}{3} \text{ A}$$

$$i_o(0^+) = i_L(0^+) = \frac{2}{3} \text{ A}$$

for $t > 0$

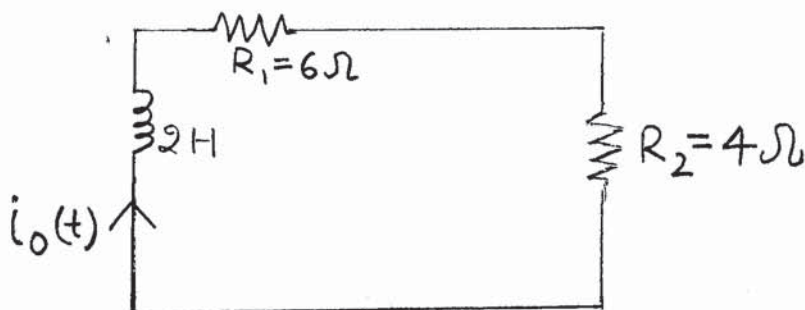

$$i_L(t) = i_o(t)$$

$$\text{KVL: } L \frac{di_o(t)}{dt} + R_1 i_o(t) + R_2 i_o(t) = 0$$

$$\frac{di_o(t)}{dt} + \frac{R_1 + R_2}{L} i_o(t) = 0$$

$$r + \frac{R_1 + R_2}{L} = 0$$

$$r = \frac{-(R_1 + R_2)}{L}$$

$$i_o(t) = A e^{rt}$$

$$i_o(t) = A e^{-\frac{(R_1 + R_2)}{L} t}$$

$$i_o(t) = A e^{-5t}$$

$$i_o(0^-) = \frac{2}{3} A = i_o(0^+)$$

$$A = \frac{2}{3}$$

$$i_o(t) = \frac{2}{3} e^{-5t} A, \quad t > 0$$

7.13 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.13 and plot the response, including the time interval just prior to opening the switch.


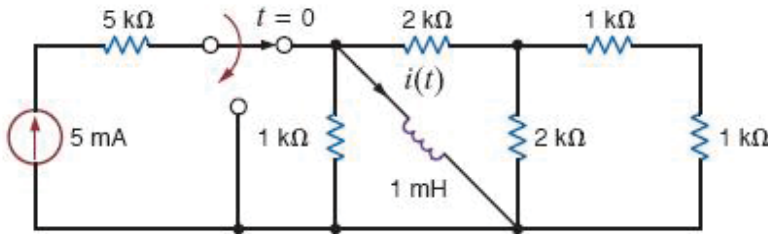


Figure P7.13


SOLUTION:

for $t = 0^-$

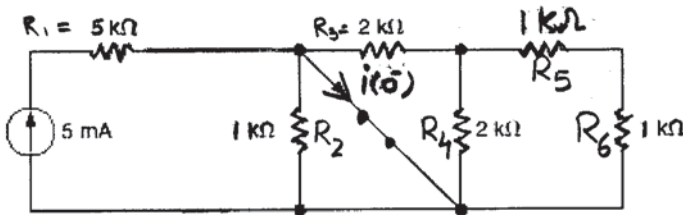

$i(0^-) = 5 \text{ mA}$, all of the current will flow through the short circuit.

for $t > 0$

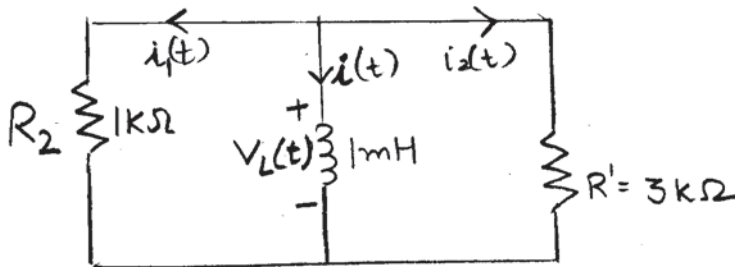

$$R' = [(R_5 + R_6) \parallel R_4] + R_3$$

$$R' = 3 \text{ k}\Omega$$

KCL:

$$i_1(t) + i(t) + i_2(t) = 0$$

$$\frac{V_L(t)}{R_2} + i(t) + \frac{V_L(t)}{R'} = 0$$

$$V_L(t) = L \frac{di(t)}{dt}$$

$$\left(\frac{1}{R_2} + \frac{1}{R'}\right) L \frac{di(t)}{dt} + i(t) = 0$$

$$\frac{di(t)}{dt} + \left(\frac{R_2 R'}{R_2 + R'}\right) \frac{i(t)}{L} = 0$$

$$\gamma + \frac{R_2 R'}{(R_2 + R')L} = 0$$

$$\gamma = \frac{-R_2 R'}{(R_2 + R')L}$$

$$i(t) = Ae^{\gamma t}$$


$$i(t) = Ae^{-\frac{R_2 R'}{(R_2 + R')L} t}$$

$$i(t) = Ae^{-7.5 \times 10^5 t}$$

$$i(0^-) = 5 \text{ mA} = i(0^+)$$

$$A = 5 \times 10^{-3}$$
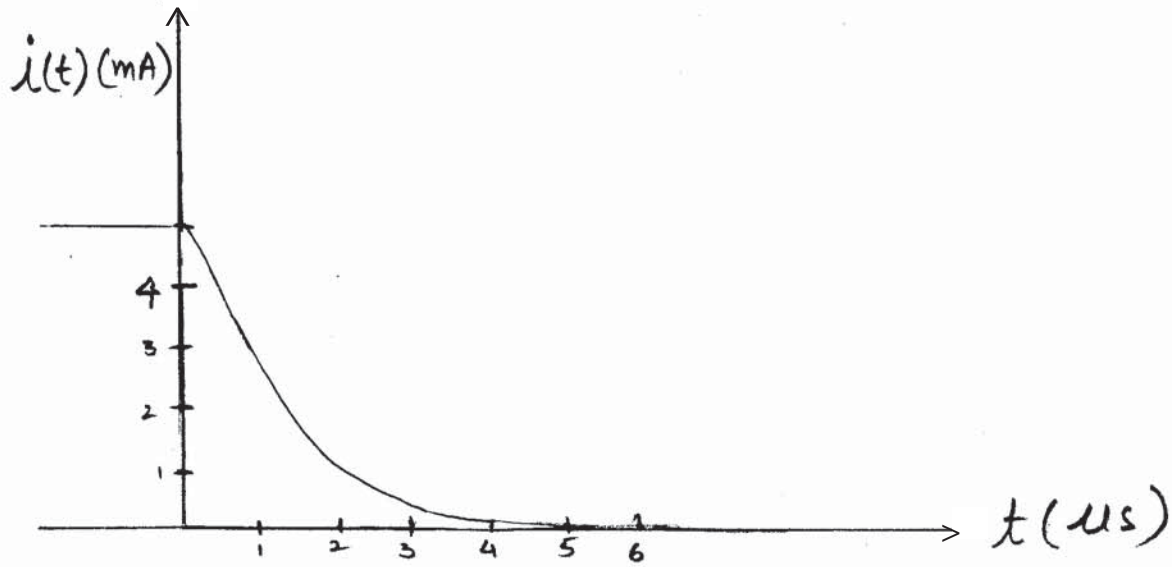
$$i(t) = 5e^{-7.5 \times 10^5 t} \text{ mA}, \quad t > 0$$



7.20 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.20.


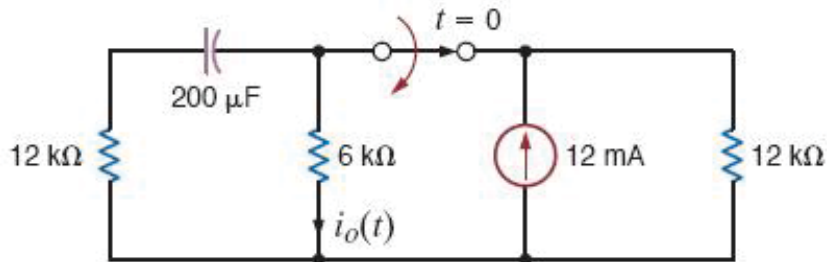


Figure P7.20

SOLUTION:

$$t = 0^- :$$

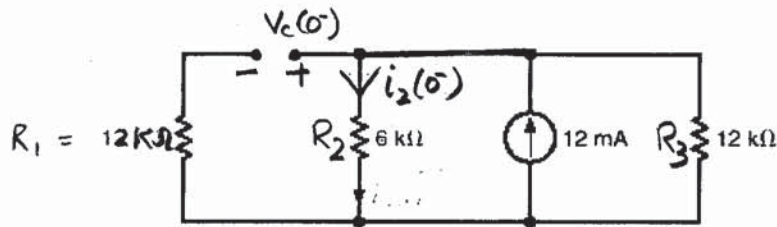


$$i_2(0^-) = \left(\frac{R_3}{R_2 + R_3} \right) (12 \times 10^{-3})$$

$$i_2(0^-) = 8 \text{ mA}$$

$$V_C(0^-) = i_2(0^-) (R_2)$$

$$V_C(0^-) = (8 \times 10^{-3}) (6 \times 10^3)$$

$$V_C(0^-) = 48 \text{ V}$$

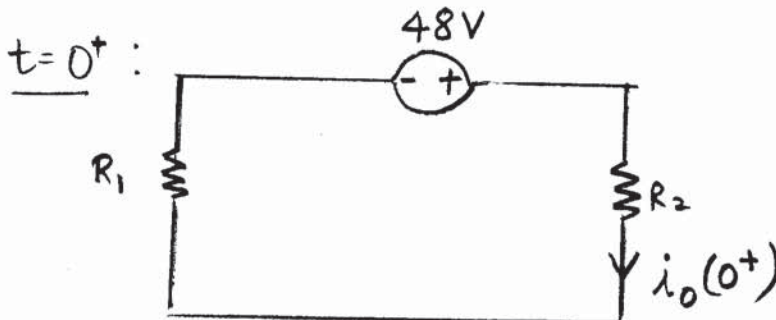


$$i_o(0^+) = \frac{48}{R_1 + R_2}$$

$$i_o(0^+) = 2.67 \text{ mA}$$

$$K_1 + K_2 = 2.67 \times 10^{-3}$$


$t = \infty$;

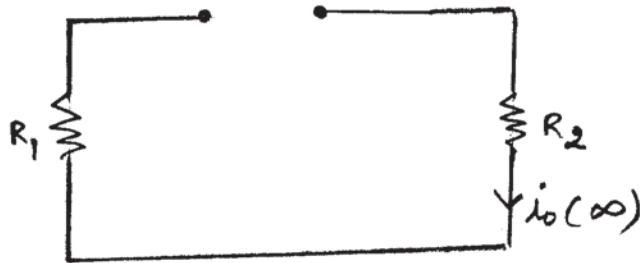

$$i_o(\infty) = 0 \text{ A}$$

$$K_1 = 0$$

$$K_2 = 2.67 \times 10^{-3}$$

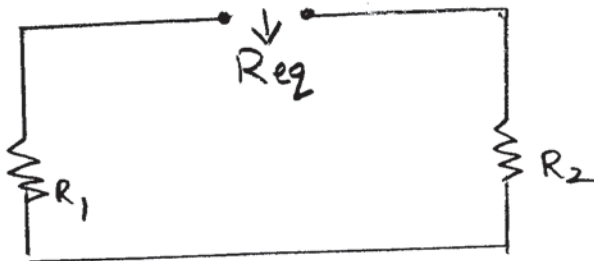

$$R_{eq} = R_1 + R_2$$

$$R_{eq} = 18 \text{ k}\Omega$$

$$\tau = R_{eq}C = (18 \times 10^3) (200 \times 10^{-6})$$

$$\tau = 3.6 \text{ s}$$

$$i_o(t) = k_1 + k_2 e^{-t/\tau}$$

$$i_o(t) = 2.67 e^{-t/3.6} \text{ mA}$$

7.32 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.32.


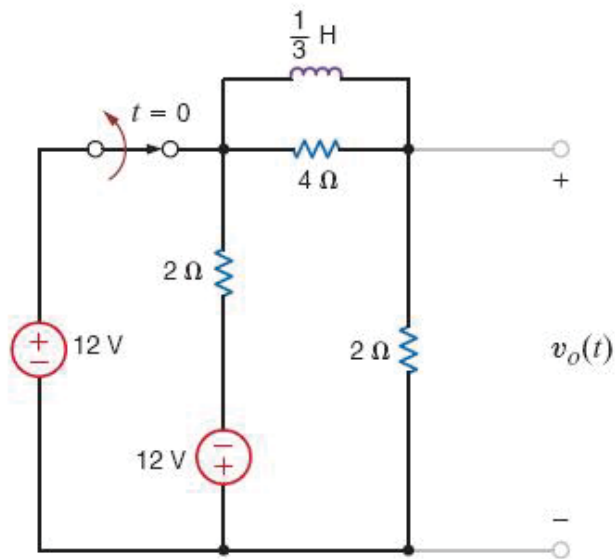


Figure P7.32

SOLUTION:



$t = 0^-$:

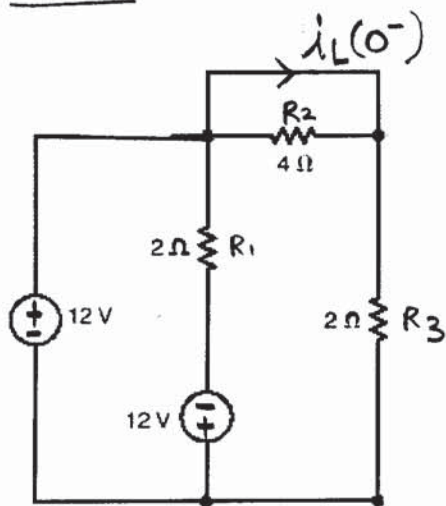

$$i_L(0^-) = \frac{12}{R_3} = \frac{12}{2}$$

$$i_L(0^-) = 6\text{ A}$$

$t = 0^+$:

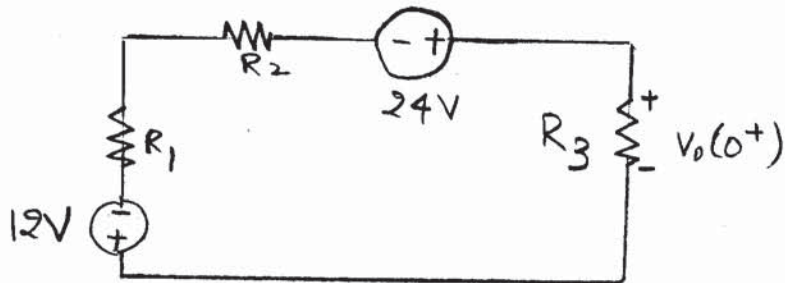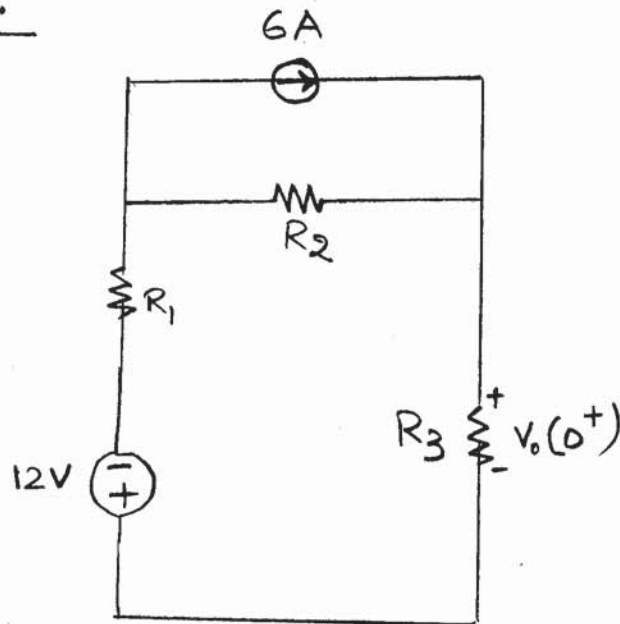


$$V_o(0^+) = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) (24 - 12)$$

$$V_o(0^+) = 3V$$

$$K_1 + K_2 = 3$$

$t = \infty$:

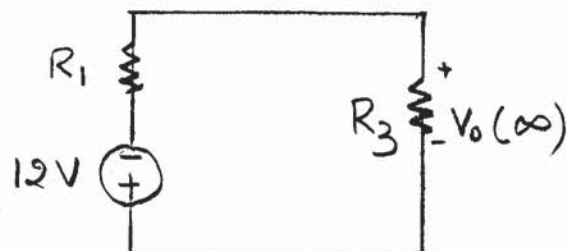


$$V_o(\infty) = \left(\frac{R_3}{R_1 + R_3} \right) (-12)$$

$$V_o(\infty) = -6V$$

$$K_1 = -6$$

$$-6 + K_2 = 3$$

$$K_2 = 9$$

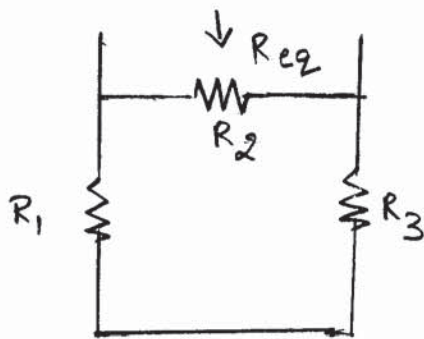

$$R_{eq} = R_2 \parallel (R_1 + R_3)$$

$$R_{eq} = 2 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1/3}{2} = \frac{1}{6} \text{ s}$$

$$V_o(t) = K_1 + K_2 e^{-t/\tau}$$

$$V_o(t) = -6 + 9e^{-6t} \text{ V}, \quad t > 0$$

7.42 The switch in the circuit in Fig. P7.42 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$.


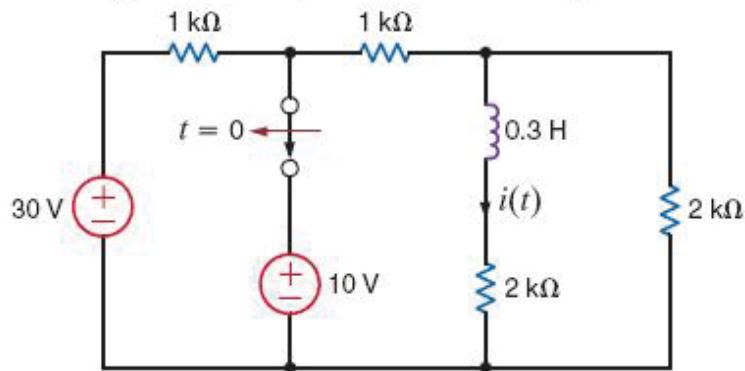


Figure P7.42

SOLUTION:

Step 1. $i(t) = k_1 + k_2 e^{-t/\tau}$

Step 2. $t = 0^-$

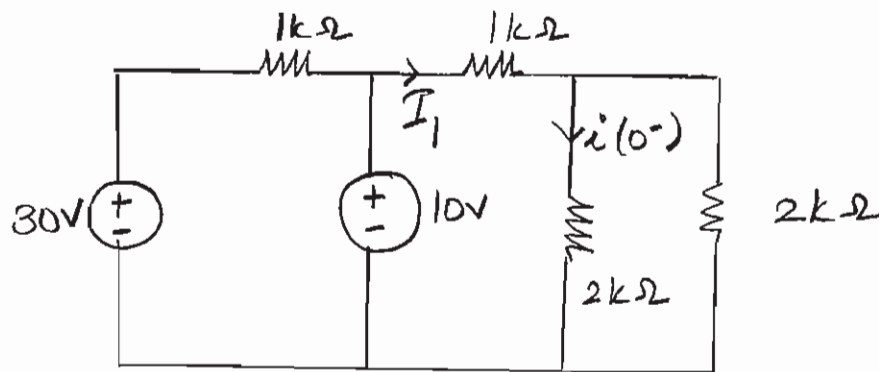



$$I_1 = \frac{10}{\frac{1k + (2k)(2k)}{2k + 2k}} = 5\text{mA}$$

$$i(0^-) = 5\text{m} \left(\frac{2k}{2k + 2k} \right) = 2.5\text{mA}$$

Step 3. $t = 0^+$

$$i(0^-) = i(0^+) = 2.5\text{mA}$$


Step 4. $t = \infty$

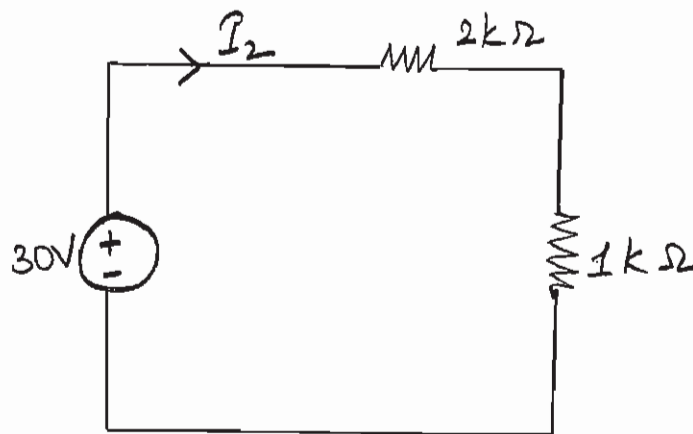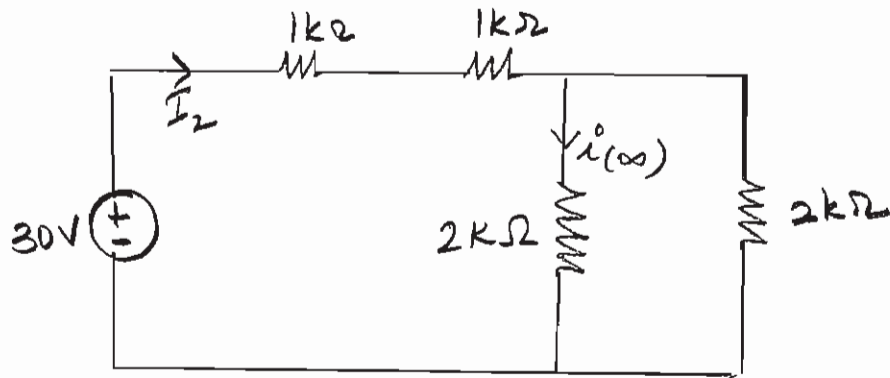


$$I_2 = \frac{30}{2k + 1k} = 10 \text{ mA}$$

$$i(\infty) = 10 \text{ m} \left(\frac{2k}{2k + 2k} \right) \\ = 5 \text{ mA}$$

Step 5. find τ

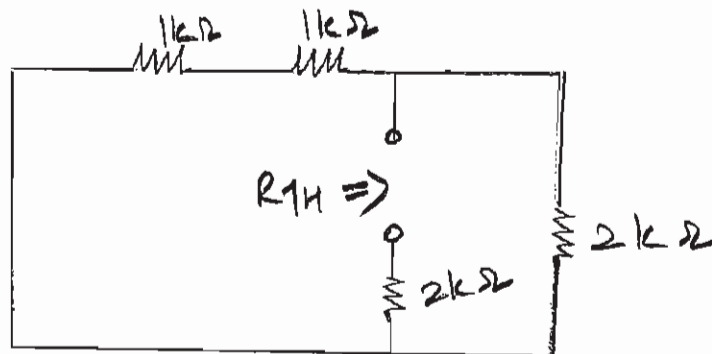

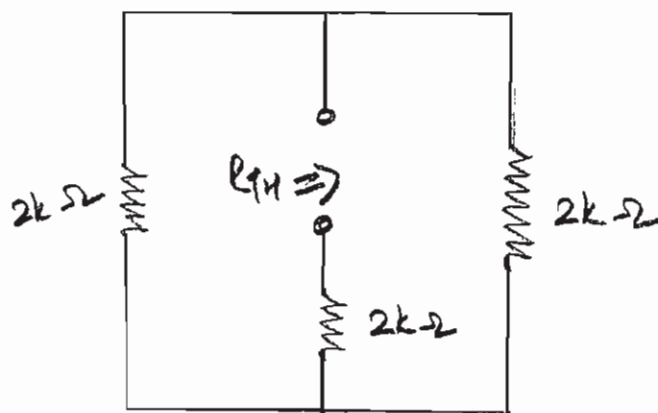

$$R_{TH} = 2k + \frac{(2k)(2k)}{2k + 2k}$$

$$R_{TH} = 3k\Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{0.3}{3 \times 10^3} = 10^{-4} \text{ s}$$

step 6. $i(t) = k_1 + k_2 e^{-t/\tau}$

$$i(\infty) = 5 \text{ mA} = k_1$$

$$i(0^+) = 2.5 \text{ mA} = k_1 + k_2 \quad k_2 = -2.5 \text{ mA}$$

$$i(t) = 5 - 2.5 e^{-t/10^{-4}} \text{ mA}, \quad t > 0$$