

**8.95** Use source exchange to determine  $V_o$  in the network in Fig. P8.95.



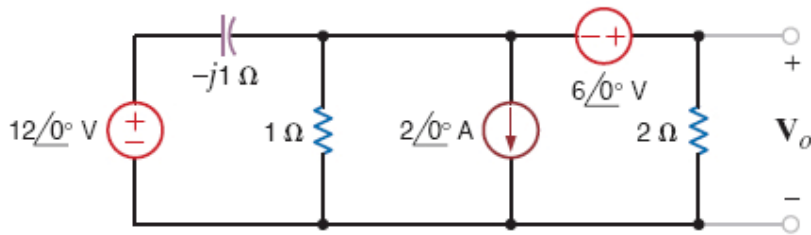
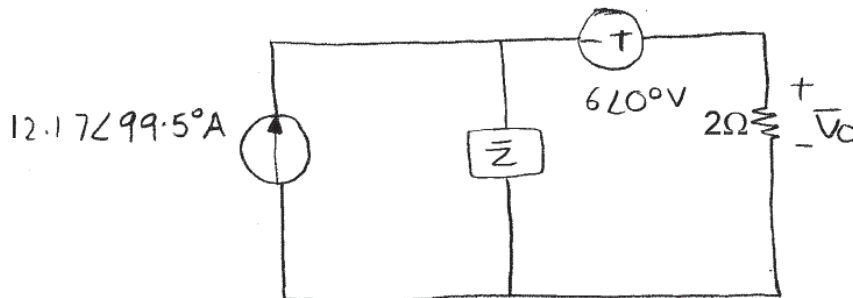


Figure P8.95

**SOLUTION:**

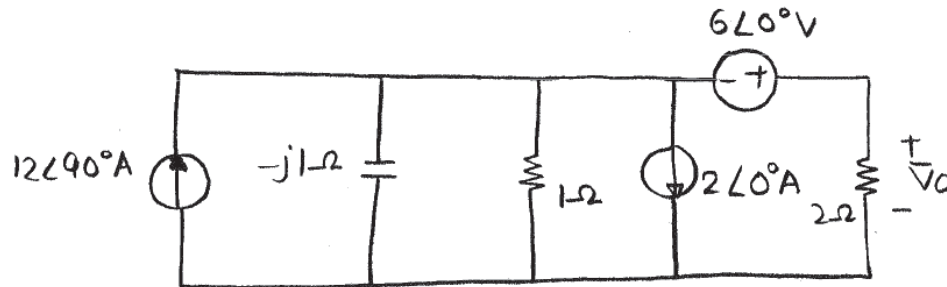
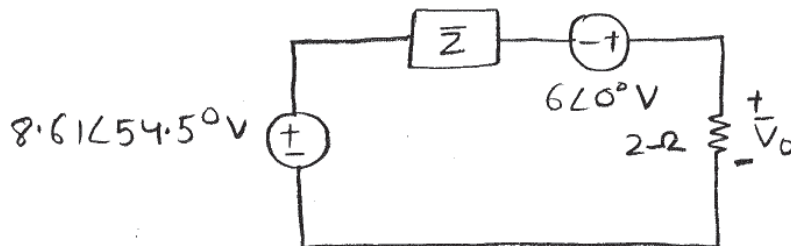
$$\bar{Z} = 1 \parallel -j1 = \frac{1(-j1)}{1-j1} = 0.707 \angle -45^\circ \Omega$$



$$\bar{v}_0 = \left( \frac{2}{2 + 0.707 \angle -45^\circ} \right) (6 \angle 0^\circ + 8.61 \angle 54.5^\circ)$$

$$\bar{v}_0 = 10.23 \angle 43.82^\circ \text{ V}$$

**8.113** Find  $V_x$  in the circuit in Fig. P8.113 using Norton's theorem.



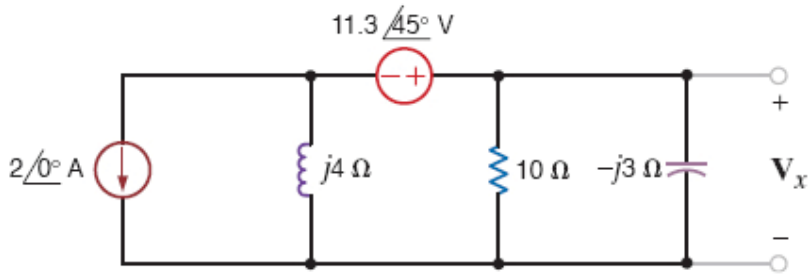
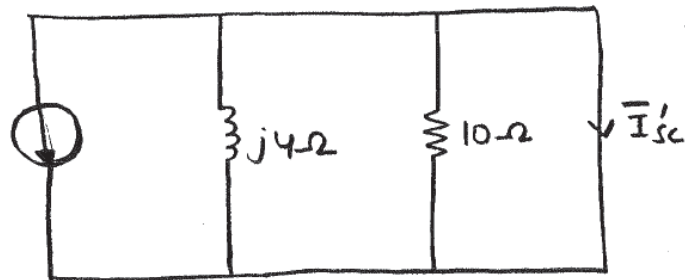


Figure P8.113

**SOLUTION:**

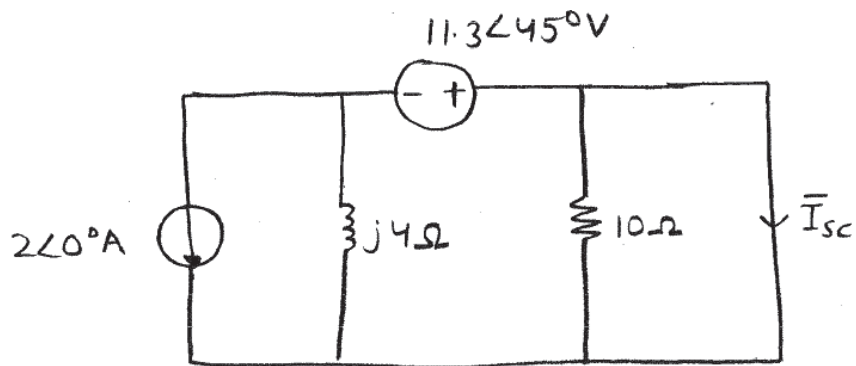

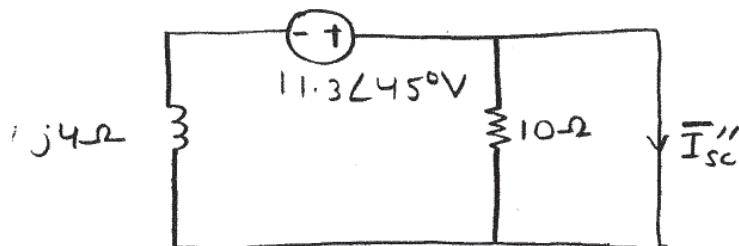
$$\bar{I}'_{sc} = -2\angle 0^\circ \text{ A}$$



$$\bar{I}_{sc}'' = \frac{11.3 \angle 45^\circ}{j4} = 2.83 \angle -45^\circ \text{ A}$$

$$\bar{I}_{sc} = \bar{I}_{sc}' + \bar{I}_{sc}'' = -2 \angle 0^\circ + 2.83 \angle -45^\circ$$

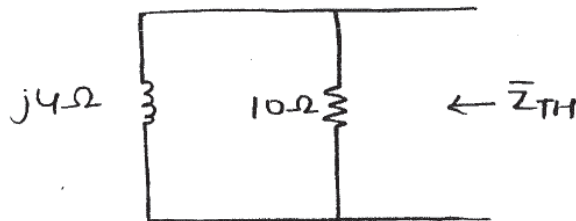
$$\bar{I}_{sc} = 2 \angle -90^\circ \text{ A}$$



$$\bar{Z}_{TH} = 10 \parallel j4$$

$$\bar{Z}_{TH} = \frac{10(j4)}{10 + j4}$$
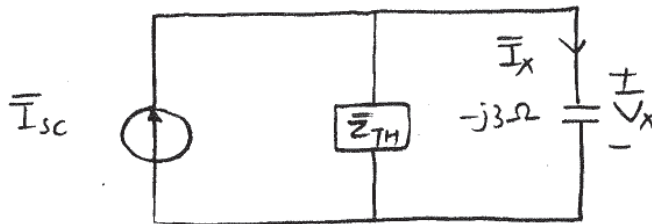
$$\bar{Z}_{TH} = 3.7 \angle 68.2^\circ \Omega$$



$$\bar{I}_x = \left( \frac{3.7 \angle 68.2^\circ}{3.7 \angle 68.2^\circ - j3} \right) (2 \angle -90^\circ)$$

$$\bar{I}_x = 5.13 \angle -39.38^\circ \text{ A}$$

$$\bar{V}_x = -j3 (5.13 \angle -39.38^\circ)$$

$$\bar{V}_x = 15.4 \angle 129.4^\circ \text{ V}$$

**8.125** Calculate the Thévenin equivalent impedance  $Z_{Th}$  in the circuit shown in Fig. P8.125.


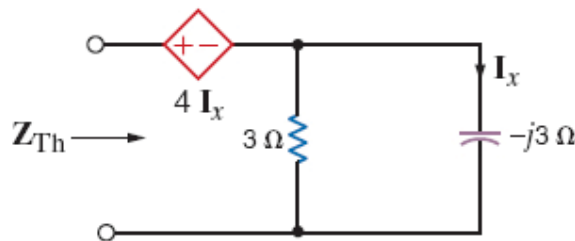


Figure P8.125

**SOLUTION:**

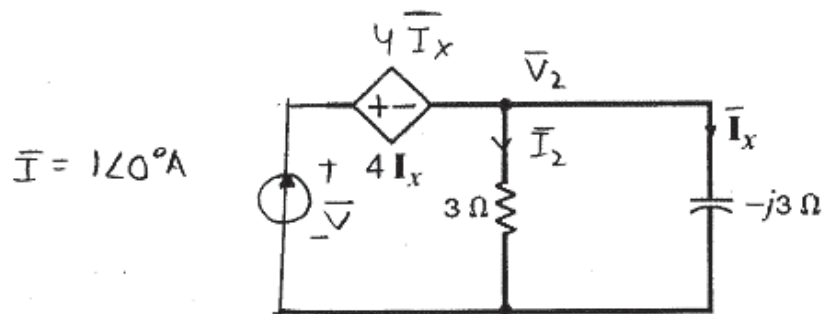

$$\text{KCL at } \textcircled{2} : 120^\circ = I_2 + \bar{I}_x$$

$$\frac{\bar{V}_2}{3} + \frac{\bar{V}_2}{-j3} = 120^\circ$$

$$-j1\bar{V}_2 + \bar{V}_2 = -j3(120^\circ)$$

$$\bar{V}_2(1-j1) = 3\angle-90^\circ$$

$$\bar{V}_2 = 2.12\angle-45^\circ \text{ V}$$

$$\bar{I}_2 = \frac{\bar{V}_2}{3} = \frac{2.12\angle-45^\circ}{3} = 0.707\angle-45^\circ \text{ A}$$

$$\bar{I}_x = \frac{\bar{V}_2}{-j3} = \frac{2.12\angle-45^\circ}{-j3} = 0.707\angle45^\circ \text{ A}$$

$$\text{KVL: } \bar{V} = 4\bar{I}_x + 3\bar{I}_2$$

$$\bar{V} = 4(0.707 \angle 45^\circ) + 3(7.07 \angle -45^\circ)$$

$$\bar{V} = 3.54 \angle 8.13^\circ \text{ V}$$

$$\bar{Z}_{TH} = \frac{\bar{V}}{\bar{I}} = \frac{3.54 \angle 8.13^\circ}{1 \angle 0^\circ}$$

$$\bar{Z}_{TH} = 3.54 \angle 8.13^\circ \Omega$$

- 12.1** Determine the driving point impedance at the input terminals of the network shown in Fig. P12.1 as a function of  $s$ .


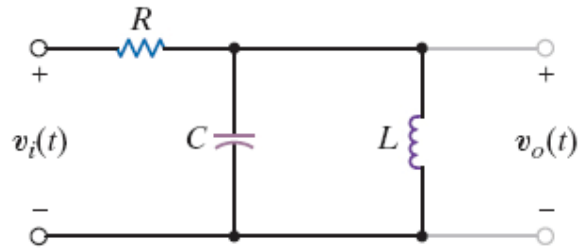


Figure P12.1

**SOLUTION:**

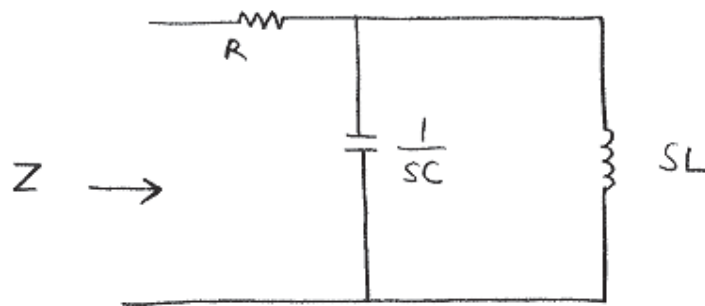

$$Z = R + \left( \frac{1}{sC} \parallel sL \right)$$

$$Z = R + \frac{\frac{1}{sC} (sL)}{\frac{1}{sC} + sL}$$

$$Z = R + \frac{\frac{L}{C}}{\frac{s^2 LC + 1}{sC}}$$

$$Z = R + \frac{sL}{s^2 LC + 1}$$

$$Z = \frac{R(S^2LC + 1) + SL}{S^2LC + 1}$$

$$Z = R \left[ \frac{S^2 + \frac{S}{RC} + \frac{1}{LC}}{S^2 + \frac{1}{LC}} \right]$$

- 12.8** Find the transfer impedance  $V_o(s)/I_s(s)$  for the network shown in Fig. P12.8.


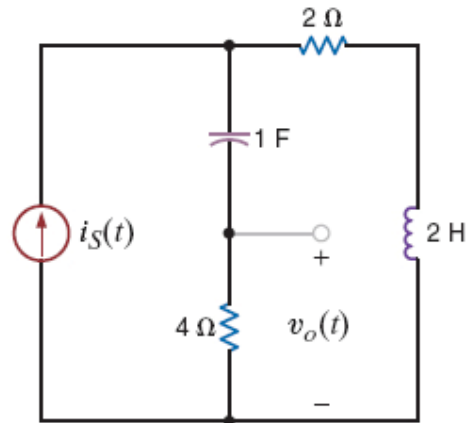


Figure P12.8

**SOLUTION:**

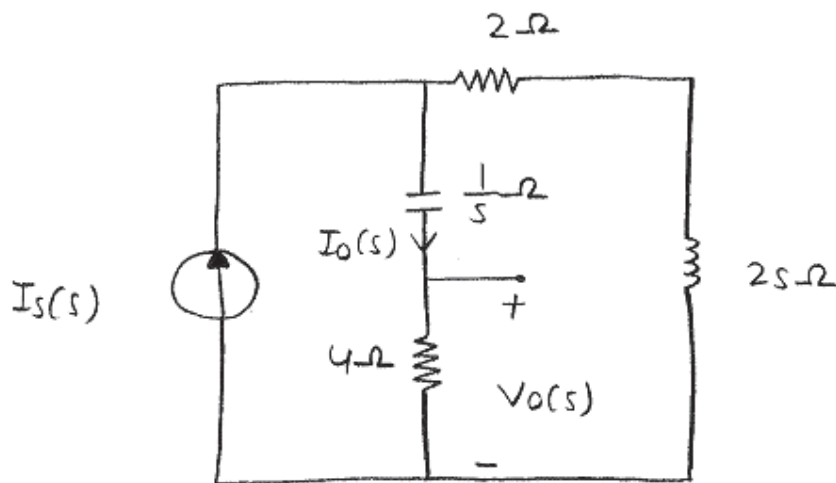

$$I_o = \left( \frac{2 + 2s}{2 + 2s + \frac{1}{s} + 4} \right) I_s$$

$$I_o = \frac{2s + 2}{2s^2 + 2s + 4s + 1} I_s$$

$$I_o = \frac{2s(s+1)}{2s^2 + 6s + 1} I_s$$

$$\frac{I_o}{I_s} = \frac{2s(s+1)}{2s^2 + 6s + 1}$$

$$\frac{V_o}{I_s} = \frac{4I_o}{I_s} = 4 \left[ \frac{2s(s+1)}{2s^2 + 6s + 1} \right]$$

$$\frac{V_o}{I_s} = \frac{8s(s+1)}{2s^2 + 6s + 1}$$

**12.9** Draw the Bode plot for the network function

$$H(j\omega) = \frac{j\omega 4 + 1}{j\omega 20 + 1}$$


**SOLUTION:**

$$H(j\omega) = \frac{j\omega 4 + 1}{j\omega 20 + 1}$$

$$H(\omega) = \frac{1}{5} \frac{j\omega + 1/4}{j\omega + 1/20}$$

$$\text{Mag}(\omega) = 20 \times \log \left[ \sqrt{\frac{(1+16\omega^2)}{(1+400\omega^2)}} \right]$$
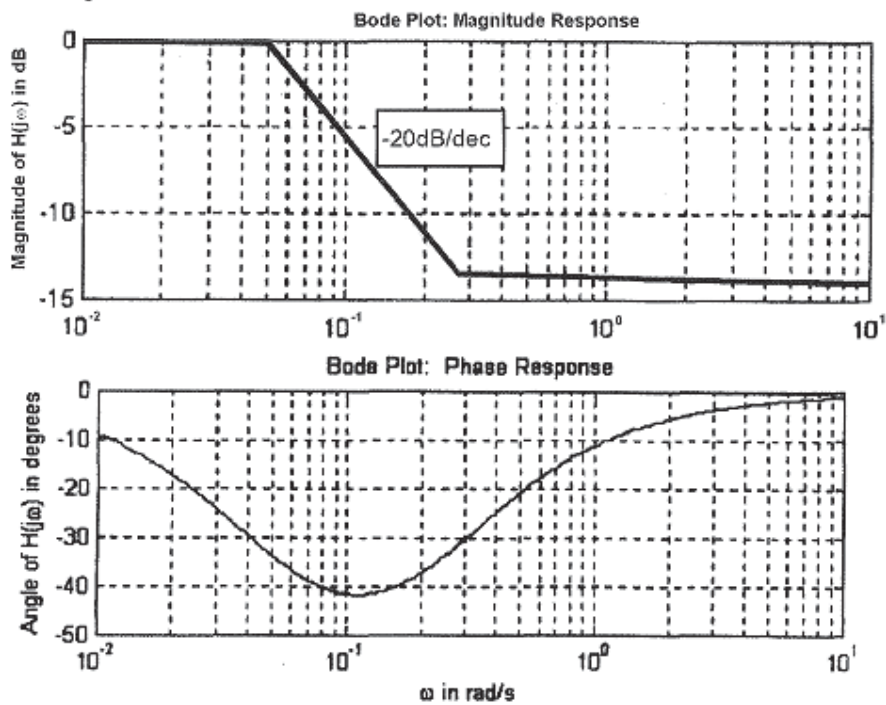
$$\text{angle}(\omega) = \tan^{-1}(4\omega) - \tan^{-1}(20\omega)$$



**12.10** Draw the Bode plot for the network function

$$H(j\omega) = \frac{j\omega}{(j\omega + 1)(0.1j\omega + 1)}$$


**SOLUTION:**

$$H(j\omega) = \frac{j\omega}{(j\omega + 1)(0.1j\omega + 1)}$$

$$H(j\omega) = \frac{10j\omega}{(j\omega + 1)(j\omega + 10)}$$

$$\text{Mag}(\omega) = 20 \times \log \left( \sqrt{\frac{100\omega^2}{(1+\omega^2)(\omega^2+100)}} \right)$$
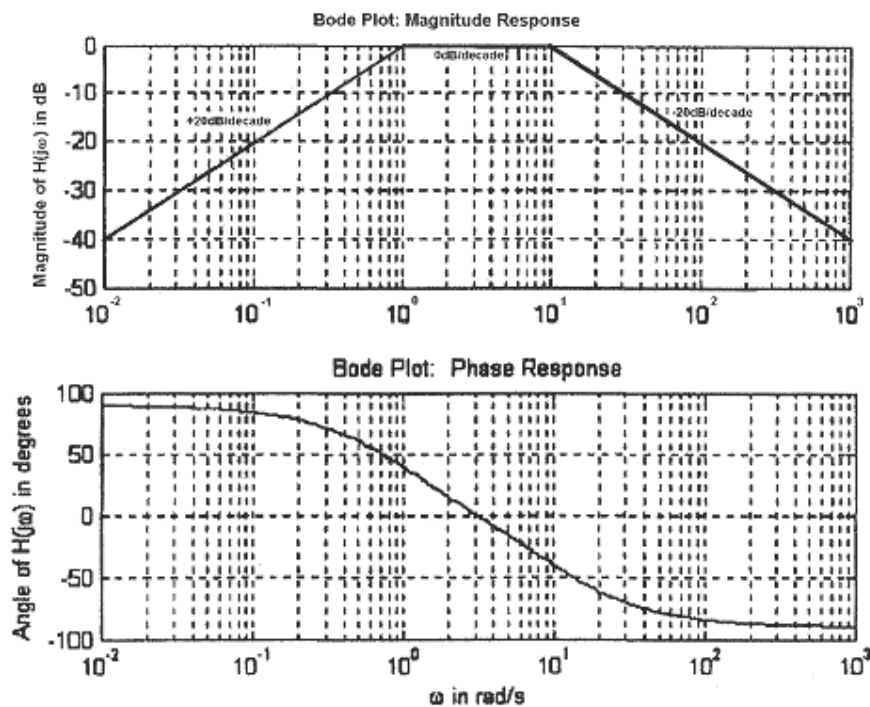
$$\text{angle}(\omega) = +90^\circ - \tan^{-1}(\omega) - \tan^{-1}\left(\frac{\omega}{10}\right)$$



**12.13** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$H(j\omega) = \frac{20(0.1j\omega + 1)}{j\omega(j\omega + 1)(0.01j\omega + 1)}$$

**SOLUTION:**

$$H(j\omega) = \frac{20(0.1j\omega + 1)}{j\omega(j\omega + 1)(0.01j\omega + 1)}$$

$$H(j\omega) = \frac{20(0.1)(j\omega + 10)}{j\omega(j\omega + 1)(0.01)(j\omega + 100)}$$

$$H(j\omega) = \frac{200(j\omega + 10)}{j\omega(j\omega + 1)(j\omega + 100)}$$


$$\text{as } \omega \rightarrow 0$$

$$|H(j\omega)| \rightarrow \frac{20}{\omega}$$

$$|H|_{\omega=0.1} = \frac{200(10)}{(0.1)(1)(100)}$$

$$= 200$$

$$= 46 \text{ dB}$$

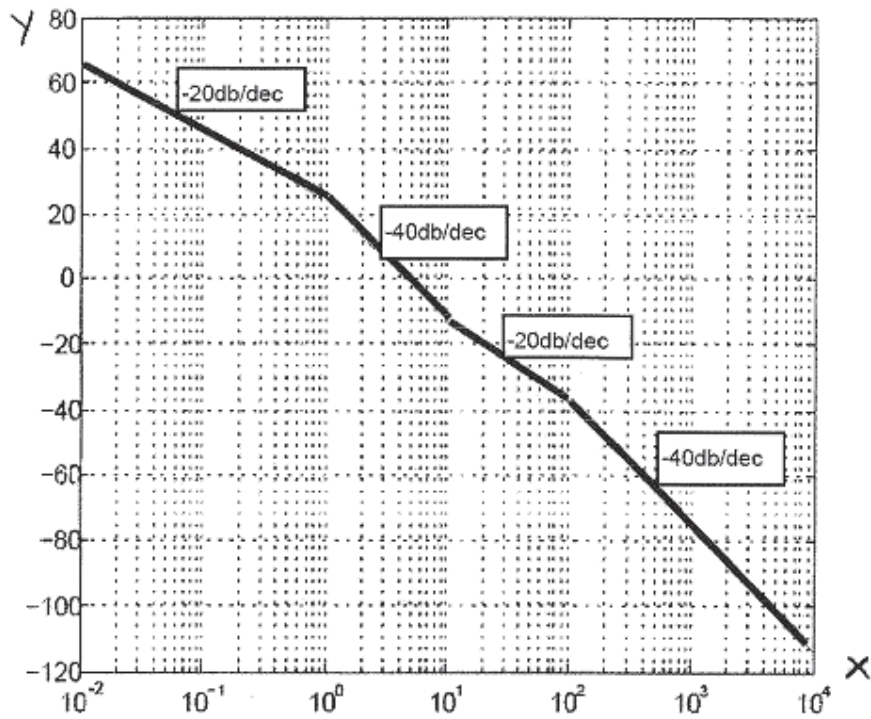


x axis:  $\omega$  in radian/sec  
y axis:  $\text{Mag} |H(j\omega)|$  in dB

**12.21** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$H(j\omega) = \frac{10(5j\omega + 1)}{(100j\omega + 1)(0.02j\omega + 1)}$$

**SOLUTION:**

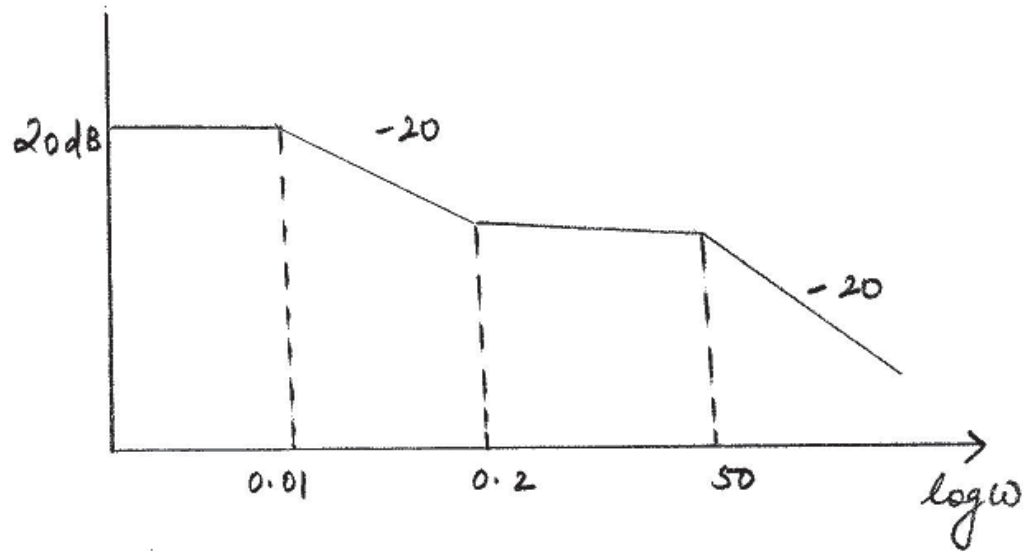

**12.27** Find  $H(j\omega)$  if its magnitude characteristic is shown in Fig. P12.27.

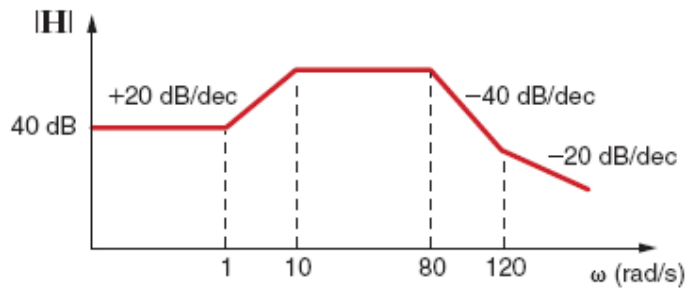


Figure P12.27

**SOLUTION:**

poles exist at :

$$10 \text{ rad/s}$$

double pole at  $80 \text{ rad/s}$

zeros exist at :

$$1 \text{ rad/s}$$

$$120 \text{ rad/s}$$

$$H(j\omega) = \frac{K(j\omega+1)(j\omega+120)}{(j\omega+10)(j\omega+80)^2}$$

for  $\omega \ll 1$

$$|H(j\omega)| = 40 \text{ dB} = 100$$

$$100 = \frac{K(1)(120)}{10(80)^2}$$

$$K = 5.33 \times 10^4$$

$$H(j\omega) = \frac{5.33 \times 10^4 (j\omega + 1) (j\omega + 120)}{(j\omega + 10) (j\omega + 80)^2}$$