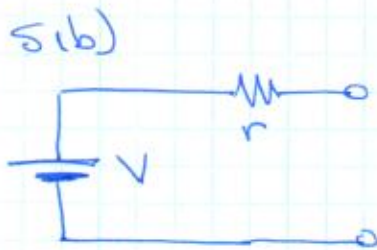


Midterm exam answer key

1/4

Version 1

S1a) Electric current: directed flow of charge through a conductor




V: source of voltage: it creates the difference of potential (voltage) at the source output

r: internal resistance: models the drop in output voltage when the current increases (or dependence of output voltage of current)

S1c) True power represents the power dissipated as heat by the resistor

S1d) Volt-Ampere-reactive (VAR)

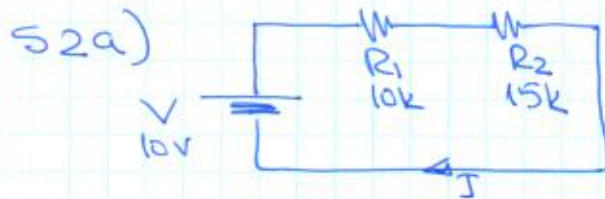S1e) $G = \frac{I}{V}$; G = conductance, I = current, V = voltage



S2b) We need to determine the current I first

$$I = \frac{V}{R_1 + R_2} \quad I = \frac{10V}{10 \cdot 10^3 + 15 \cdot 10^3} \quad I = 0.4 \text{ mA}$$

$$V_{R_1} = I \cdot R_1 \quad \Rightarrow \quad V_{R_1} = 0.4 \times 10^{-3} \times 10 \cdot 10^3 \quad V_{R_1} = 4V$$

$$V_{R_2} = I \cdot R_2 \quad \Rightarrow \quad V_{R_2} = 0.4 \times 10^{-3} \times 15 \cdot 10^3 \quad V_{R_2} = 6V$$


OR OR

$$V_{R_2} = V - V_{R_1} \quad V_{R_2} = 10 - 4$$

S2c) Since the resistors are connected in series,

$$I_{R_1} = I_{R_2} = I \quad I_{R_1} = 0.4 \text{ mA} \quad I_{R_2} = 0.4 \text{ mA}$$

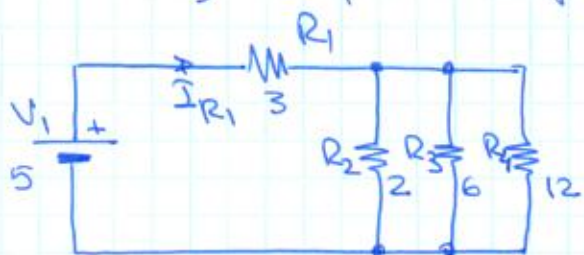S3ab) Upon inspecting the schematic, R_2 , R_3 and R_4 are connected in parallel.



Let $R_p = R_2 \parallel R_3 \parallel R_4$

$$R_p = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$I_{R_1} = \frac{V_1}{R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}}$$

$$I_{R_1} = \frac{5}{3 + \frac{1}{\frac{1}{2} + \frac{1}{6} + \frac{1}{12}}} =$$

$$= \frac{5}{3 + \frac{1}{\frac{6}{12} + \frac{2}{12} + \frac{1}{12}}} = \frac{5}{3 + \frac{12}{9}} = \frac{5}{\frac{13}{3}} = \frac{15}{13} \text{ A} \quad I_{R_1} = \underline{1.154 \text{ A}}$$

$$V_{R_1} = R_1 \cdot I_{R_1} \quad V_{R_1} = 3 \cdot \frac{15}{13} \quad V_{R_1} = \frac{45}{13} \text{ V} = \underline{3.46 \text{ V}}$$

$$V_{R_2} = V_{R_3} = V_{R_4} = V_1 - V_{R_1} \Rightarrow V_{R_2} = V_{R_3} = V_{R_4} = \underline{1.54 \text{ V}}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} \quad I_{R_2} = \underline{0.77 \text{ A}}$$

$$I_{R_3} = \frac{V_{R_3}}{R_3} \quad I_{R_3} = \underline{0.257 \text{ A}}$$

$$I_{R_4} = \frac{V_{R_4}}{R_4} \text{ or } I_{R_4} = I_{R_1} - I_{R_2} - I_{R_3} \quad I_{R_4} = \underline{0.128 \text{ A}}$$

S3c) Let R_2 resistance be x . The text tells us that the resistance is $x \Omega$ and the conductance is x (Siemens). Thus

$$x = \frac{1}{x} \quad (\text{because } G = \frac{1}{R} \text{ or } R = \frac{1}{G}) \Rightarrow$$

$\Rightarrow x^2 = 1 \Rightarrow x = \pm 1$. We only retain the positive value (resistance can't be negative in this context), so $R_2 = \underline{1 \Omega}$

We need to recalculate the current through R_1 :

$$I_{R_1} = \frac{V_1}{R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}}$$

$$I_{R_1} = \frac{5}{3 + \frac{1}{\frac{1}{1} + \frac{1}{6} + \frac{1}{12}}}$$

$$= \frac{5}{3 + \frac{1}{\frac{12}{12} + \frac{2}{12} + \frac{1}{12}}} = \frac{5}{3 + \frac{12}{15}} = \frac{5}{\frac{57}{15}} = \frac{75}{57} \text{ A}$$

$$I_{R_1} = \underline{\underline{1.3596 \text{ A}}}$$

$$\left. \begin{aligned} V_{R_1} &= R_1 \cdot I_{R_1} \\ V_{R_3} &= V_1 - V_{R_1} \end{aligned} \right\} \Rightarrow \left. \begin{aligned} V_{R_3} &= V_1 - R_1 \cdot I_{R_1} \\ P_{R_3} &= \frac{V_{R_3}^2}{R_3} \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow P_{R_3} = \frac{(V_1 - R_1 \cdot I_{R_1})^2}{R_3} \quad P_{R_3} = \frac{(5 - 3 \times 1.3596)^2}{6}$$

$$P_{R_3} = \underline{\underline{141.4 \text{ mW}}}$$

54)

$$L_i = \text{initial inductance} \quad L_i = \frac{\mu_m N^2 A}{l_i}$$

4/4

$$L_f = \text{final inductance} \quad L_f = \frac{\mu_m N^2 A}{l_f}$$

We're told that $L_f = 1.2 \times L_i$
 \uparrow 20% increase

$$\frac{L_f}{L_i} = 1.2 \quad \Leftrightarrow \quad \frac{\mu_m N^2 A}{l_f} \cdot \frac{l_i}{\mu_m N^2 A} = 1.2 \quad \Rightarrow$$

$$\Rightarrow l_f = \frac{l_i}{1.2} \quad \left| - l_i \Rightarrow l_f - l_i = l_i \left(\frac{1}{1.2} - 1 \right) \right.$$

$$l_i = 6 \times \overset{\text{radius}}{r} \quad \text{given.} \quad r = \frac{d}{2} \quad \leftarrow \text{diameter} \quad d = 10 \cdot 10^{-2} \text{ m} \quad \left. \right\}$$

$$\Rightarrow l_f - l_i = 6 \times \frac{10 \cdot 10^{-2}}{2} \cdot \left(\frac{10}{12} - \frac{12}{12} \right)$$

$$l_f - l_i = 6 \cdot \frac{0.1}{2} \cdot \left(-\frac{2}{12} \right) = -0.05 \text{ m}$$

So the coil needs to be compressed with 5 cm to achieve a 20% increase in inductance.