


Midterm exam answer key

1/4
v2

Version 2

S1a) Electrical resistance: opposition exerted by a conductor to an electric current flowing through it.

S1b)

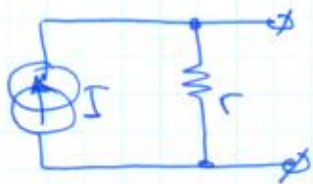

I : source of current: it determines the electric current flowing through the external circuit

r : internal resistance: models the dependency of the output current of the load

S1c) Reactive power in the power reversibly stored in the magnetic field of the inductor.

S1d) Volt-Ampere (VA)

S1e) $G = \frac{I}{V}$; $G =$ conductance, $I =$ current, $V =$ voltage



S2b) $V_1 = V_2 = V$ $V_1 = 15V$, $V_2 = 15V$

S2c) We need to determine the current I first.

$$I = \frac{V}{R_1 \parallel R_2} \quad I = \frac{V}{\frac{R_1 R_2}{R_1 + R_2}} = V \cdot \frac{R_1 + R_2}{R_1 R_2}$$


$$I = 15 \cdot \frac{50 \cdot 10^3}{20 \cdot 10^3 \cdot 30 \cdot 10^3} \quad I = 1.25 \text{ mA}$$

$$I_1 = \frac{V}{R_1} ; I_1 = \frac{15}{20 \cdot 10^3} \quad I_1 = 0.75 \text{ mA}$$

$$I_2 = \frac{V}{R_2} \text{ or } I_2 = I - I_1 ; \text{ either give } I_2 = 0.5 \text{ mA}$$

Note: Computing I is optional, but helpful to confirm values obtained for I_1 and I_2

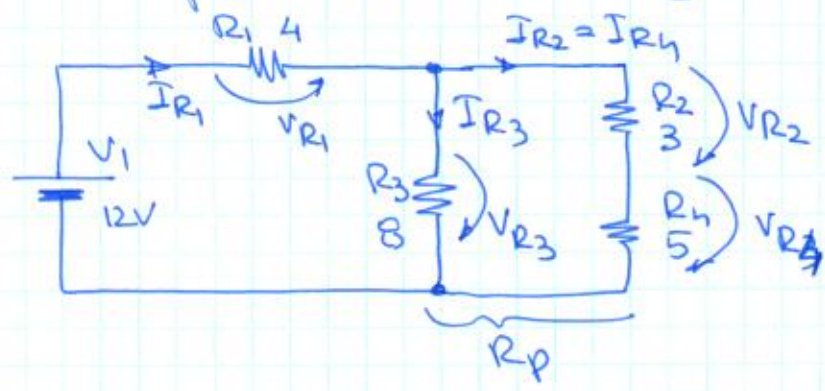S3 ab) Upon inspecting the schematic, R_2 and R_4 are connected in series, and their group is in parallel with R_3



Let $R_p = R_3 \parallel (R_2 + R_4)$
 $R_p = \frac{R_3 (R_2 + R_4)}{R_3 + R_2 + R_4}$

$$I_{R_1} = \frac{V_1}{R_1 + R_p} \Rightarrow I_{R_1} = \frac{V_1}{R_1 + \frac{R_3 (R_2 + R_4)}{R_3 + R_2 + R_4}}$$

$$I_{R_1} = \frac{12}{4 + \frac{8(3+5)}{8+3+5}} = \frac{12}{4 + \frac{48 \cdot 8}{16}} = \frac{12}{8} = 1.5 \text{ A}$$

$$V_{R_1} = R_1 \cdot I_{R_1} \Rightarrow V_{R_1} = 4 \times 1.5 \quad V_{R_1} = 6 \text{ V}$$

$$V_{R_3} = V_{R_2} + V_{R_4} = V_1 - V_{R_1} \Rightarrow V_{R_3} = 12 - 6 = 6 \text{ V}$$

↑ parallel ↓

$$I_{R_3} = \frac{V_{R_3}}{R_3} \quad I_{R_3} = \frac{6}{8} \quad I_{R_3} = 0.75 \text{ A}$$

$$I_{R_2} = I_{R_1} - I_{R_3} \text{ (KCL)} \Rightarrow I_{R_2} = 0.75 \text{ A}$$

$$I_{R_4} = I_{R_2} \text{ (series)} \Rightarrow I_{R_4} = 0.75 \text{ A}$$

$$V_{R_2} = R_2 \cdot I_{R_2} \Rightarrow V_{R_2} = 3 \cdot \frac{3}{4} \quad V_{R_2} = 2.25 \text{ V}$$

$$V_{R_4} = R_4 \cdot I_{R_4} \Rightarrow V_{R_4} = 5 \cdot \frac{3}{4} \quad V_{R_4} = 3.75 \text{ V}$$

Check: (optional) $V_{R_1} + V_{R_3} = V_1 \quad 12 = 12 \text{ V}$

$$V_{R_2} + V_{R_4} = V_{R_3} \quad 2.25 + 3.75 = 6 \text{ V}$$

53c) let R_2 resistance be x . The text ^{3/4} tells us that the resistance is x Ohms, and the conductance is x Siemens. Thus,

$$x = \frac{1}{x} \quad (\text{because } G = \frac{1}{R} \text{ or } R = \frac{1}{G}) \quad (\Rightarrow)$$

(\Rightarrow) $x^2 = 1 \Rightarrow x = \pm 1$. We only retain the positive value (resistance can't be negative in this context), so $R_2 = 1 \Omega$.

We need to recalculate the currents/voltages:

$$I_{R_1} = \frac{V_1}{R_1 + \frac{R_3(R_2+R_4)}{R_3+R_2+R_4}} \quad I_{R_1} = \frac{12}{4 + \frac{8 \cdot (1+5)}{8+1+5}} = \frac{12}{4 + \frac{8 \cdot 6}{14}}$$

$$I_{R_1} = \frac{12 \cdot 14}{4 \cdot 14 + 48} = \frac{168}{104} \quad I_{R_1} = 1.615 \text{ A}$$

$$\left. \begin{aligned} V_{R_1} &= R_1 \cdot I_{R_1} \\ V_{R_3} &= V_{R_2} + V_{R_4} = V_1 - V_{R_1} \quad (\text{KVL}) \end{aligned} \right] \Rightarrow$$

$$\Rightarrow V_{R_2} + V_{R_4} = V_1 - R_1 \cdot I_{R_1}$$

$V_{R_2} + V_{R_4}$ = voltage across the series group

$$I_{R_2} = I_{R_4} = \frac{V_{R_2} + V_{R_4}}{R_2 + R_4} \quad \Rightarrow$$

$$\left. \begin{aligned} \Rightarrow I_{R_4} &= \frac{V_1 - R_1 \cdot I_{R_1}}{R_2 + R_4} \\ P_{R_4} &= R_4 \cdot I_{R_4}^2 \end{aligned} \right] \Rightarrow P_{R_4} = R_4 \left[\frac{V_1 - R_1 I_{R_1}}{R_2 + R_4} \right]^2$$

$$\text{So } P_{R_h} = 5 \cdot \left(\frac{12 - 4 \times 1.615}{1 + 5} \right)^2 \quad P_{R_h} = 4.26 \text{ W} \quad \sqrt{4/4}$$

54) $L_i = \text{initial inductance} \quad L_i = \frac{\mu_m N^2 A}{l_i}$

$L_f = \text{final inductance} \quad L_f = \frac{\mu_m N^2 A}{l_f}$

We're told that $L_f = 0.9 \times L_i$
 \uparrow 10% decrease

$$\frac{L_f}{L_i} = \frac{9}{10} \quad (\Rightarrow) \quad \frac{\cancel{\mu_m N^2 A}}{l_f} \cdot \frac{l_i}{\cancel{\mu_m N^2 A}} = \frac{9}{10} \Rightarrow$$

$$\Rightarrow l_f = \frac{10}{9} \cdot l_i \quad | - l_i \Rightarrow l_f - l_i = l_i \left(\frac{10}{9} - 1 \right)$$

$$l_f - l_i = \frac{l_i}{9} \quad ; \quad l_i = 9 \times r \quad r = \frac{d}{2} \cdot d = 6 \cdot 10^{-2} \text{ m}$$

$$l_f - l_i = \frac{1}{9} \cdot \cancel{9} \cdot \frac{d}{2} \quad l_f - l_i = \frac{6 \cdot 10^{-2}}{2}$$

$$l_f - l_i = 3 \text{ cm} = 0.03 \text{ m}$$

So the coil needs to be extended with 3 cm to achieve a 10% decrease in inductance.

Note : the formula $L = \frac{\mu_m N^2 A}{l}$ is valid for $l > 10 \cdot d$ — however, in the context of this problem we assume that the L formula is valid regardless of the coil length / diameter ratio.