

CEG2136: Computer Architecture I CEG2536: Architecture des Ordinateurs I

Duration: 1 hour and 30 minutes

- Closed book exam. All electronic devices including calculators are not allowed.
- If in doubt how to interpret a question, make an assumption and elaborate your solution based on this hypothesis. Explain all your assumptions and well define the symbols used.
- If you finish 10 minutes or less before the due time, remain seated until the end of the exam.

Question 1

1.1 (12 x 1.5 point)

Fill out each row of the following table with the corresponding representation in other bases of the number given in that row; show the details of your calculations.

decimal	binary	hexadecimal	octal
25.5			
	1010.01		
		1A	
			32

1.2 (4 points)

In the 8-bit signed 2's complement representation, the number of distinct numbers is:

- (a) 256
- (b) 128
- (c) 255
- (d) None of these

1.3 (6+6+8 = 20 points)

7-bit registers are used in this question to store numbers expressed in 2's complement representation.

(a) Convert the following two signed numbers to binary observing the above assumption:

$$A = (-31)_{10}$$

$$B = (+63)_{10}$$

(b) Find the 2's complement of the signed binary numbers A and B, and give your results in decimal, too:

(c) Perform the following arithmetic operations in signed-2's complement representation, using a 7-bit ALU; show operations and results (including intermediary steps), both in binary and in decimal. Are there any overflows? How can a computer detect overflow?

$$(+63)_{10} + (-31)_{10}$$

$$(-63)_{10} - (-31)_{10}$$

Are there any overflows? How can a computer detect overflow?

Question 2

2.1 (4x1.5 point)

You have a SRAM memory chip with a capacity of 8k x 4

a) How many input-output data lines does it have?

Answer a)

b) How many address lines does it have?

Answer b)

c) What is its capacity expressed in "bits"?

Answer c)

2.2 (2x6 = 12 points)

What is wrong with the following transfer statements (RTL)?

a) xT: $AR \leftarrow AR'$, $AR \leftarrow 0$

b) yT: $PC \leftarrow AR$, $PC \leftarrow PC + 1$


Question 3 (20 points)

Design a 3-bit multi-function register A ($A_2A_1A_0$) whose operation is described in the following table, where C_1 and C_0 are two control bits.

Use in your design JK flip flops, logic gates and any digital components (encoders, decoders, multiplexers, etc.); draw a detailed diagram of the logic circuit of the multi-function register.

Function table of 3-bit register A.

Clock	C_1	C_0	Operation
↑	0	0	No change
↑	0	1	Increment by 3
↑	1	0	Decrement by 3
↑	1	1	Loading external inputs, say $I_2 I_1 I_0$

 

Question 4 (20 points)

Design a 4-bit arithmetic circuit, with two selection variables x and y ; the 1-bit variable z is an input of full adder. The circuit generates the following eight arithmetic operations under control of x , y and z :

(Note: X' is the 1's complement of X)

$x y$	$z = 0$	$z = 1$
0 0	$F = A+B$ (add)	$F = A+B+1$
0 1	$F = A$ (transfer)	$F = A+1$ (increment)
1 0	$F = B'$ (complement)	$F = B'+1$ (negate)
1 1	$F = A+B'$	$F = A-B$ (subtract)

Draw the logic diagram of the two least significant bits of your arithmetic circuit, *only*. Use full adders and other logic circuits (multiplexer, gates) as required.