

**Variables**

- P = Power [W]
- V = Voltage [V]
- I = Current [A]
- W = Energy [J]
- R = Resistance [ $\Omega$ ]
- $\rho$  = resistivity
- G = Conductance [ $\Omega^{-1}$ ]
- $\sigma$  = conductivity
- $\lambda$  = flux linkage [Wb-turn]
- L = Inductance [H]
- C = Capacitance [F]
- $\epsilon_i$  = permittivity of i [ $F m^{-1}$ ]
- E = Electro Motive Force [V]

- P = Real Power [W]
- Q = Reactive Power [var]
  - ↳ only imaginary
- S = Complex Power [VA]
- |S| = Apparent Power

- H = Magnetic Field Intensity [ $A m^{-1}$ ]
- J = Electric Current Density [ $A m^{-2}$ ]
- B = Magnetic Flux Density [ $J = Wb m^{-2}$ ]
- F = Magneto Motive Force [A-turn]
- $\Phi$  = Magnetic Flux [Wb]
- $\mu_i$  = Permeability of i [ $H m^{-1}$ ]
- $\mathcal{P}$  = Permeance [ $Wb A^{-1}$ ]
- R = Reluctance [ $A^{-1} Wb$ ]

- e = induced voltage in coil terminals [V]
- Z = Impedance [ $\Omega$ ]
- X = Reactance [ $\Omega$ ]

$P = VI = RI^2$   
 $W = \int RI^2 dt = \int P dt$   
 $R = \frac{\rho l}{S} \rightarrow l = \text{length}, S = \text{Cross Section}$   
 $G = \frac{1}{R} \rightarrow \sigma = \frac{1}{\rho}$

**Inductor**

$\lambda = \int V dt$   
 $V = L \frac{di}{dt} \rightarrow i = \frac{1}{L} \int v dt + I_0$   
 $W = \frac{L(I_0)^2}{2}$   
 $X_L = \omega L = 2\pi f L$

**Capacitor:**

$q = VC$   
 $i = C \frac{dv}{dt}$   
 $v = \frac{1}{C} \int_0^T i dt + V_0$   
 $W = \frac{CV^2}{2}$   
 $C = \frac{\epsilon_0 \epsilon_r S}{d} \rightarrow S = \text{area}, d = \text{gap}$   
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

- Kirchoff's laws**
- Electric
    - Voltage = 0 in a loop
    - Current = 0 at a node
  - Magnetic
    - MMF = 0 in a loop
    - Flux = 0 at a node
- ↳ Summing R  
 - Series:  $R_{tot} = R_1 + R_2$   
 - Parallel:  $1/R_{tot} = 1/R_1 + 1/R_2$

**Phasors**

$I = I_{max} (\cos(\omega t) + j \sin(\omega t))$   
 ↳ Resistor:  $V = IR$   
 ↳ Inductor:  $V = -\omega L I_{max} (\sin(\omega t) + j \cos(\omega t))$   
 ↳ Capacitor:  $V = \frac{I_{max}}{\omega C} (\sin(\omega t) - j \cos(\omega t))$

$A e^{j\omega t} = A (\cos(\omega t) + j \sin(\omega t))$   
 $A e^{j(\omega t + \theta)} = A (e^{j\theta}) (e^{j\omega t})$   
 ↳ At  $t=0$ , angle =  $\theta$

Resistor: In Phase, Real power  
 Inductor: V leads I, Reactive Power  
 Capacitor: V lags I, Reactive Power

$S = P + jQ = v \cdot i$   
 Power factor:  $\frac{P}{S} = \cos \phi$   
 where  $\phi$  is the phase angle

$I_{RMS} \sqrt{2} = I_{max}$   
 $V_{RMS} \sqrt{2} = V_{max}$

- Fourier and Laplace**
1. Take Periodic Input
  2. Convert into Sinusoidal functions
  3. Find the output signal for each
  4. Combine all output signals
- Fourier:  $\int_{-\infty}^{\infty} f(x) e^{-j\omega x} dx$  | Laplace:  $\int_0^{\infty} f(t) e^{-st} dt$

**Magnetic Circuits**

$\mathcal{F} = Ni = H_c l_c = \frac{L_c B_c}{\mu_c} + \frac{g B_g}{\mu_0}$   
 $\rightarrow l_c = \text{core length}$   
 $g = \text{gap length}$   
 $\Phi = BA \rightarrow A = \text{area}$   
 $B = \mu H$   
 $\mu_0 = 4\pi \times 10^{-7} H m^{-1}$   
 $R = \frac{l}{\mu A} \rightarrow R_g = \frac{g}{\mu_0 A}$   
 $\Phi = \frac{\mathcal{F}}{R_c + R_g}$

On a Conductor  
In a Magnetic Field:  
 $F_m = i(\text{length} \times B)$   
 $E = l(\text{velocity} \times B)$

**Flux Linkage**

$\lambda = \int e dt = N \Phi$   
 $L = \frac{\lambda}{i} = \frac{N^2}{R_{tot}}$

**Multicoil**

$\mathcal{F} = N_1 i_1 + N_2 i_2$   
 $\Phi = \frac{N_1 i_1 + N_2 i_2}{R_{tot}} \approx \frac{N_1 i_1 + N_2 i_2}{R_g}$   
 $\lambda_1 = L_{11} i_1 + L_{12} i_2$   
 $\lambda_2 = \left(\frac{N_1^2}{R_g}\right) i_1 + \left(\frac{N_1 N_2}{R_g}\right) i_2$   
 $P = ie = i \frac{d\lambda}{dt}$   
 stored energy  $W = \frac{\lambda^2}{2L} = \frac{Li^2}{2}$

**Transformers**

↳ 2 type: Core and Shell

In No-load conditions, an EMF is induced in the primary coil.

$V = R_1 i_p + e$   
 ↳ induced EMF

In no load  $R \approx 0$

$\hookrightarrow V_1 = e_1 = \omega N_1 \Phi_{max} \cos(\omega t)$   
 $V_{RMS} = E_{RMS} = \sqrt{2} f N_1 \Phi_{max}$     f = frequency  
 $\rightarrow \Phi_{max} = \frac{V_1}{\sqrt{2} \pi f N_1}$

Exciting Current:  $i_p \rightarrow$  waveform is different

In phase component supplies power for core losses

Out of phase current lags  $90^\circ$  behind

Core loss =  $P_c = E_1 I_p \cos \theta_c \rightarrow I_c = \frac{P_c}{E_1}$

**Ideal Transformer:**

$\frac{V_1}{V_2} = \frac{N_1}{N_2}$      $\frac{I_1}{I_2} = \frac{N_2}{N_1}$      $P = V_1 I_1 = V_2 I_2$      $Z_1 = \frac{V_1}{I_1} = \left(\frac{N_1}{N_2}\right)^2 Z_2$

Secondary leakage Flux

$\frac{E_2}{E_1} = \frac{N_2}{N_1}$