 


Non-ideal Behavior of Wires

Set # 2

- ❑ Interference problems are typically occurred at high frequencies where circuit components such as R, L, C, and wires can have highly non-ideal behavior.
- ❑ In circuit theory (@ low frequencies), a wire is theoretically considered as a short circuit. Wire and other circuit components dimensions are not taken into consideration. However, at high frequencies a wire can exhibit significant resistance, inductance, and capacitance that depend on its physical and material properties.
- ❑ To Design an EMC device, you need to be aware of such non-ideal behavior of these components to eliminate potential EMI problems




1

Non-ideal Behavior of Wires


1. Most real wires have resistance:



2. Real wires have capacitance

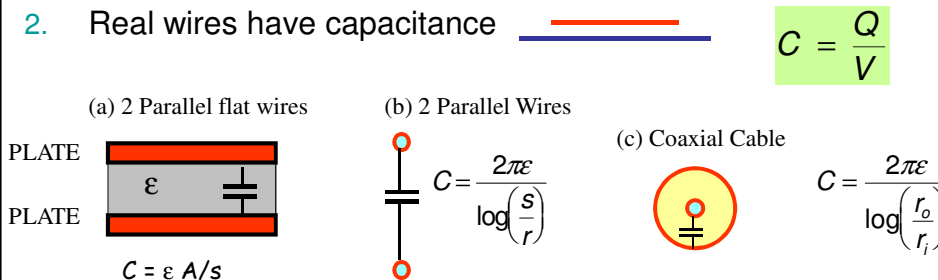


3. Real wires have inductance

 

• They cause time delay and loss

 Lumped Versus Distributed Circuits: Lumped Circuits




- Lumped circuit elements:
 - Resistor, capacitor, inductor
- Lumped circuit elements are defined by


$$v = Ri, \quad v = L di/dt$$
- Use KVL and/or KCL and involve only **one variable, time**.
- The travel time of the electric signal is negligible.

3

Distributed Circuits

 

- Travel time cannot be neglected.
- The **voltages** and currents in such a circuit are **functions of position as well as time**.
- Lumped circuit analysis is substantially simpler than distributed circuit analysis.
- Points for determining whether a circuit should be considered “lumped” or “distributed”
 - Component size versus wavelength (Freq. D.)
 - Pulse rise time versus round propagation trip time (Time domain)

 


4

Non-ideal Behavior of Wires

Resistance of Wires


Most *real* wires have resistance:

 

- R depends on material (σ : conductivity, S/m), length: **L**, cross section: **A**

- R causes time delay and loss
- A dc approximation is given by:

$$R = \frac{L}{\sigma A}$$

 


- At high frequencies, a better approximation is given by:

$$R_{HF} \cong \frac{L}{2r} \sqrt{\frac{f\mu_o}{\pi\sigma}}$$


Examples: (s = spacing, r = radius, A = area of plate)

(a) 2 Parallel flat wires

 


$$C = \epsilon A/s$$

(b) 2 Parallel Wires

 


(c) Wire above Ground Plane

 


$$C = 2 \pi \epsilon / \log (2s/r)$$

(d) Coaxial Cable

 


Interconnects

Front View

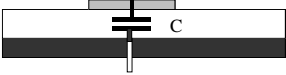


$$C = \epsilon A_c / s$$

$$= \epsilon l w / s, \quad w > s$$

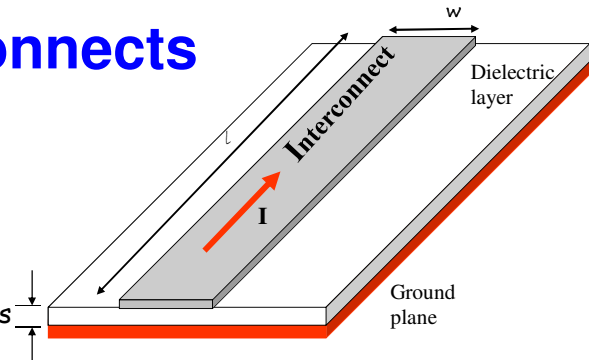

Side View

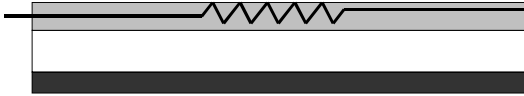

$$R = \rho l / A_R$$

$$= \rho l / wd$$

- **IDEAL MODEL:**
 - We treat wires as entities along which the voltage is constant and signals (EM waves) as infinitely fast
 - No voltage drop & No time delay


7

Interconnect Models


- **DISTRIBUTED MODEL:**

We treat wires as entities along which the voltage can be different and signals (EM waves) as having a finite speed


voltage drop & time delay




(a) Ideal wire

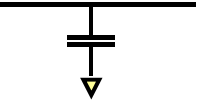


(b) Lumped C

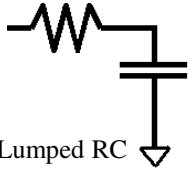

(c) Lumped RC

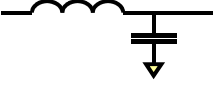

(d) Lumped LC

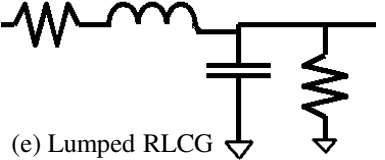

(e) Lumped RLCG

8

Interconnected Inverters

EXAMPLE

interconnect: 2 mm long, 1 μm thick, and 1.5 μm wide,
 $\rho = 2.8 \mu\Omega\text{-cm}$

Substrate: $\epsilon = 3.8 \epsilon_0 = 3.365 \times 10^{-11} \text{ F/cm}$, 100 nm thick

Use: $C = \epsilon A_c/s = \epsilon (lw)/s$, & $R = \rho l/A_R = \rho l/(wd)$

Calculate: $R_{\text{int}} = 37.3 \Omega$ & $C_{\text{int}} = 1.1 \times 10^{-10} \text{ F}$

(1) Ideal circuit model for interconnected gates.

(2) circuit model including interconnect RC-lump model.

Interconnect RC-lump model. 9

Transmission Lines Equations: Review Summary
Textbook Section 4.5

For forward(+) traveling wave (direction of power flow from generator to load)

$V(z) = V_o e^{-\gamma z} = V_o e^{-\alpha z} e^{-j\beta z}$

where $\gamma = \sqrt{(G + j\omega C)(R + j\omega L)} = \alpha + j\beta$

$v = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}}$


$V(z,t) = \text{Re}[V(z)e^{j\omega t}] = V_o e^{-\alpha z} \cos(\omega t - \beta z)$ With $V_o = \text{real \#}$

$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$ $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$


For lossless lines:

$Z_{\text{in}} = Z_o \frac{Z_L + j Z_o \tan(\beta l)}{Z_o + j Z_L \tan(\beta l)}$ $\alpha = 0, \beta = \omega\sqrt{LC} \text{ \& } Z_o = \sqrt{\frac{L}{C}}$ 10

Transmission lines & Digital devices

 


Trapezoid-shaped pulse signal

 

Line connecting 2 digital gates

Equivalent problem

 


$$Z_0 = \sqrt{\frac{L}{C}}$$

$$v = \frac{1}{\sqrt{LC}}$$




$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Transmission lines model in PSPICE



Trapezoid-shaped pulse

 

   It is defined in terms of: amplitude, pulse time delay, pulse rise-time, pulse fall-time, pulse width and period.





Typical equivalent circuit

  

Load voltage (Pspice simulation)

  Per unit length parameters (pul) - Sec 4.2 (L, C, R & G)



Note: For lossless system, $R=0$ and $G=0$

PUL parameters: Wire-Type Structures


The per-unit-length external inductance is defined as the ratio of the flux penetrating a unit length surface between the wires:

$$l = \frac{\psi_m}{I}$$

Flux due to a current-carrying wire:

$$\psi_m = \int_S \vec{B}_T \cdot \vec{ds} \quad \text{where} \quad \vec{B}_T = \mu_0 \vec{H}_T$$
 
$$\oint_C \vec{H}_T \cdot d\vec{l} = I_{\text{enclosed}} \implies H_T = \frac{I}{2\pi r}$$



∴ Flux per unit wire length

$$\psi_m = \int_{r=R_1}^{R_2} \frac{\mu_0 I}{2\pi r} dr = \frac{\mu_0 I}{2\pi} \ln\left(\frac{R_2}{R_1}\right)$$

Per unit length parameters (Cont.)

- For TEM wave (E_z and $H_z = 0$), we can compute the per-unit-length inductance l using dc field computations even though the fields will be varying with time.
- If the medium surrounding the two conductors is homogeneous, then c and l are related as

$$lc = \mu\epsilon$$


- Hence we only need to determine c or l
- For the case of an inhomogeneous medium as is the case for the microstrip and the PCB, this relations does not apply.

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.¹⁵

PUL parameters: Two parallel wires

 
A) The per-unit-length inductance

One wire carries a current I directed into the page and the other wire carries a current of the same magnitude but directed out of the page.



$$\begin{aligned}\psi_m &= \frac{\mu_0 I}{2\pi} \ln\left(\frac{s - r_{w2}}{r_{w1}}\right) + \frac{\mu_0 I}{2\pi} \ln\left(\frac{s - r_{w1}}{r_{w2}}\right) \\ &= \frac{\mu_0 I}{2\pi} \ln\left[\frac{(s - r_{w2})(s - r_{w1})}{r_{w2} r_{w1}}\right]\end{aligned}$$

PUL parameters: Two parallel wires

 

For widely separated wires ($s \gg r_{w1}, r_{w2}$)

$$l = \frac{\mu_0}{2\pi} \ln\left(\frac{s^2}{r_{w2}r_{w1}}\right) \quad (\text{in H/m})$$

Special case ($r_{w1} = r_{w2} = r_w$):

$$l = \frac{\mu_0}{\pi} \ln\left(\frac{s}{r_w}\right)$$


B) The per-unit-length capacitance

$$c = \frac{\mu_0 \epsilon_0}{l} \Rightarrow c = \frac{\pi \epsilon_0}{\ln(s/r_w)}$$

PUL Parameters: one wire above a ground plane

$$c \cong \frac{2\pi\epsilon_0}{\ln(2h/r_w)} \quad h \gg r_w$$
 
$$l \cong \frac{\mu_0}{2\pi} \ln\left(\frac{2h}{r_w}\right) \quad h \gg r_w$$




PUL parameters: coaxial cable

- Assume the current I flows along the inner wire surface and returns along the interior surface of the shield.

$$l = \frac{\mu_0}{2\pi} \ln\left(\frac{r_s}{r_w}\right)$$


$$c = \frac{\mu_0 \epsilon_0}{l}$$

 

Cross section

PUL parameters: Printed Circuit Board (PCB) Structures (I)


 
- The inductance and capacitance per unit length can be determined in terms of the characteristic impedance Z_c and velocity of propagation v as



$$c = \frac{1}{v Z_C}$$

$$l = \frac{Z_C}{v}$$

$$v = \frac{v_o}{\sqrt{\epsilon_r'}}$$

  

v_o is the speed of light

ϵ_r' is the effective dielectric constant (?)

- Generally, the exact per-unit-length parameters cannot be determined in closed form but can be obtained as approximate relations.

19


PUL parameters: PCB Structures (II)

Case 1:

A strip-line in a homogeneous medium,

$$\epsilon_r' = \epsilon_r$$
 
$$Z_C = \frac{30\pi}{\sqrt{\epsilon_r}} \left[\frac{1}{\frac{w_e}{s} + 0.441} \right]$$



Cross section

$$v = \frac{v_o}{\sqrt{\epsilon_r'}}$$

$$c = \frac{1}{v Z_C}$$

$$l = \frac{Z_C}{v}$$


$$\frac{w_e}{s} = \begin{cases} \frac{w}{s} & \frac{w}{s} \geq 0.35 \\ \frac{w}{s} - \left(0.35 - \frac{w}{s}\right)^2 & \frac{w}{s} \leq 0.35 \end{cases}$$

20

PUL parameters: PCB Structures (III)

Case 2:

The microstrip structure,

 

$$\epsilon_r' = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 10h/w}}$$

$$Z_C = \begin{cases} \frac{60}{\sqrt{\epsilon_r'}} \ln \left[\frac{8h}{w} + \frac{w}{4h} \right] & \frac{w}{h} \leq 1 \\ \frac{120\pi}{\sqrt{\epsilon_r'}} \left[\frac{w}{h} + 1.393 + 0.667 \ln \left(\frac{w}{h} + 1.444 \right) \right]^{-1} & \frac{w}{h} \geq 1 \end{cases}$$

$$v = \frac{v_o}{\sqrt{\epsilon_r'}}$$

$$c = \frac{1}{v Z_C}$$


$$l = \frac{Z_C}{v}$$

21

PUL parameters: PCB Structures (IV)

Case 3:

Two lands of width w placed on one side,

 

$$k = \frac{s}{s + 2w}$$

$$\epsilon_r' = \frac{\epsilon_r + 1}{2} \left\{ \tanh \left[0.775 \ln \left(\frac{h}{w} \right) + 1.75 \right] + \frac{kw}{h} [0.04 - 0.7k + 0.01(1 - 0.1\epsilon_r)(0.25 + k)] \right\}$$

$$v = \frac{v_o}{\sqrt{\epsilon_r'}}$$

$$c = \frac{1}{v Z_C}$$

$$Z_C = \begin{cases} \frac{120}{\sqrt{\epsilon_r'}} \ln \left(2 \frac{1 + \sqrt{k}}{1 - \sqrt{k}} \right) & \frac{1}{\sqrt{2}} \leq k \leq 1 \\ \frac{377\pi}{\sqrt{\epsilon_r'} \ln \left(2 \frac{1 + \sqrt{k'}}{1 - \sqrt{k'}} \right)} & 0 \leq k \leq \frac{1}{\sqrt{2}} \end{cases}$$

$$l = \frac{Z_C}{v}$$


22

High-Speed Digital Interconnects and Signal Integrity: Section 4.4


Illustration of “clock skew” caused by unequal propagation paths

 (a) unequal propagation paths

$$\begin{aligned} \text{Path \#1} &= \text{TD1} + \text{TD2} \\ \text{Path \#2} &= \text{TD1} + \text{TD3} + \text{TD2} \\ \text{Path \#2} - \text{Path \#1} &= \Delta\text{TD} = \text{TD3} \end{aligned}$$


 
$$\begin{aligned} \text{Path \#1} &= \text{TD1} + \text{TD3} + \text{TD2} \\ \text{Path \#2} &= \text{TD1} + \text{TD3} + \text{TD2} \\ \text{Path \#2} - \text{Path \#1} &= \Delta\text{TD} = 0 \end{aligned}$$






(b) equal propagation paths


Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 23

High-Speed Digital Interconnects and Signal Integrity

   A typical signal integrity problem:
a transmission line
interconnecting two CMOS gates;



Simulate, using PSpice:



 


The voltage at the line output (the input to the load CMOS gate) showing the ringing that may cause logic errors.

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 24

High-Speed Digital Interconnects and Signal Integrity

   PSPICE prediction of the voltage at the input to the line; ➔



Measured voltage at the input to the line.




25

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

High-Speed Digital Interconnects and Signal Integrity: Termination and Matching Effects



A) Effect of Capacitive

Termination

  
 


B) Effect of Inductive

Termination

  



C) Effect of Series match

  


Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

High-Speed Digital Interconnects and Signal Integrity: Effectiveness of Matching Scheme


Problem specification

  

↓

 


**Pspice Results:
no series matching**

 


Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons, 27

 
High-Speed Digital Interconnects and Signal Integrity: A) Effectiveness of Series Matching Scheme



 Add 30 Ω resistor in series with the source, i.e., matching at the source




 **PSpice Results:
Applying the series match scheme shows that the ringing is eliminated.**




Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons, 28

 
High-Speed Digital Interconnects and Signal Integrity: B) Effectiveness of Parallel Matching Scheme



 Add 50 Ω resistor in parallel with C, i.e., matching at the load



 - For the parallel match,
- The line is not completely matched at the load. At high frequencies, the line is not matched.
 - The steady-state level the load voltage falls significantly below the desired 5-V level, and logic errors may occur.









PSpice Results

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 29

High-Speed Digital Interconnects and Signal Integrity:

C) Line Length effect

      

- The distributed parameter effects of the line is negligible if L is electrically short at the highest significant frequency: $L < v/(10F_{max})$, with $F_{max} = 1/\tau_r$


Hence the line and any mismatches should not significantly degrade the output waveform if the pulse rise time is greater than 10 one-way time delays of the line:

$$\tau_r > 10 T_D$$

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 30

Effects of Component Leads: Sections 5.3-5.6

 
- A component is connected to the circuit via leads (bare wires)
- The high-frequency behavior of components is affected by the length of the leads.
- The length and separation of the leads cause the component to have, in addition to the ideal behavior, an inductive element and a capacitive element.



Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 31

Effects of Component Leads: Equivalent Cct.

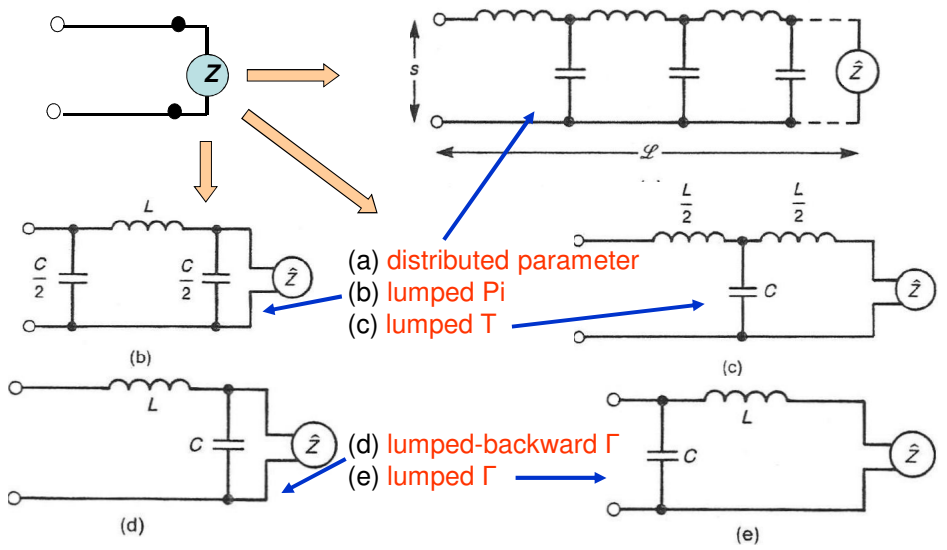
Lumped-circuit models are used when the lead length L and separation s are electrically short at the required frequency.




Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 32

Effects of Component Leads: Resistors (5.4)

 Frequency behavior of the impedance of an ideal resistor:



Non-ideal resistor:

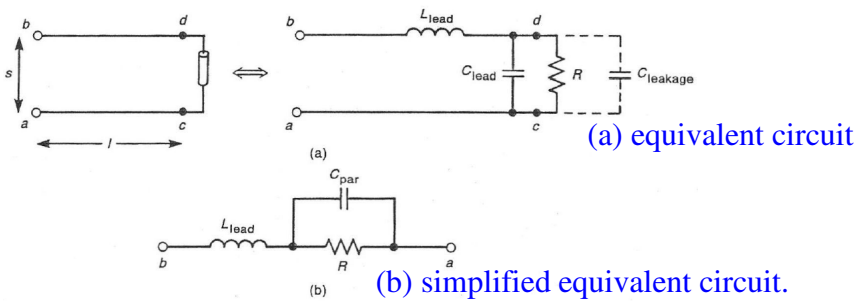

The non-ideal resistor including the effects of the leads:

$$\hat{Z}(j\omega) = L_{\text{lead}} \frac{1/L_{\text{lead}}C_{\text{par}} - \omega^2 + j\omega/RC_{\text{par}}}{j\omega + 1/RC_{\text{par}}}$$



Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

Effects of Component Leads: Resistors

Bode Plot: is a plot of magnitude and phase of a function vs frequency and typically employs log scales.

The non-ideal resistor:


 
 
Bode plots of the impedance variation with frequency.



Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

Effects of Component Leads: Resistors

   
Equivalent circuit of a resistor for various frequencies:





Measured impedance of a 1000-Ω carbon resistor having ½ in. lead lengths:
 (a) magnitude (b) phase

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

 Effects of Component Leads: Capacitors (5.5)



 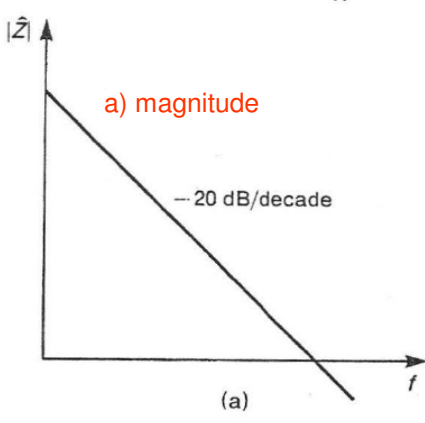
$$\hat{Z}(j\omega) = \frac{1}{j\omega C}$$



Frequency response of the impedance of an ideal capacitor:
 (a) magnitude; (b) phase.

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

Effects of Component Leads: Capacitors

 

The model depends on the physical construction of the capacitor


Typically R_{diel} is very large & $C \gg C_{lead}$

Modeling of a physical capacitor with an equivalent circuit.

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.


Effects of Component Leads: Capacitors

 A simplified equivalent circuit of a capacitor including the effects of lead length.



$$\hat{Z}(j\omega) = L_{lead} \frac{1/L_{lead}C - \omega^2 + j\omega R_s/L_{lead}}{j\omega}$$



 
Bode plots of the impedance:
(a) magnitude; (b) phase.



Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

Effects of Component Leads: Capacitors

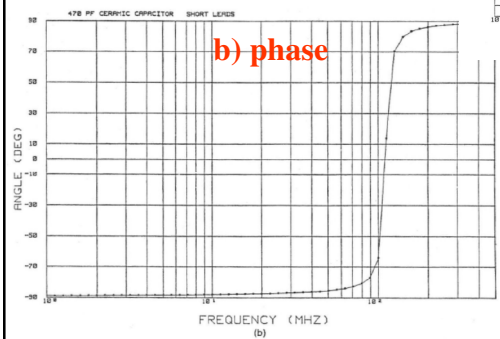  
Measured impedance of a 470-pF ceramic capacitor with short lead lengths:





Note the self resonant frequency (pure resistive impedance)

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 39

 Effects of Component Leads: Inductors (5.6)



$$\hat{Z}_L = j\omega L$$

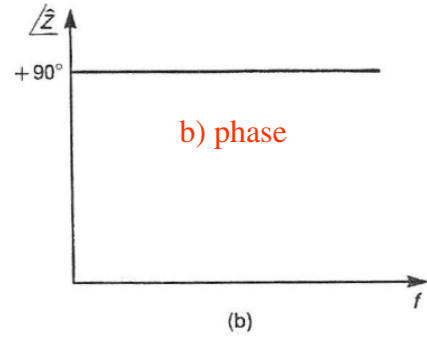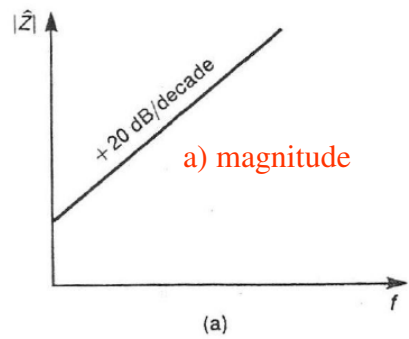


Frequency response of the impedance of an ideal inductor: (a) magnitude; (b) phase.

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons. 40

Effects of Component Leads: Inductors

 
A simplified equivalent circuit of an inductor including the effects of leads



The model depends on the physical construction of the inductor.

$$\hat{Z}_L(j\omega) = R_{par} \frac{1 + j\omega L/R_{par}}{1 - \omega^2 LC_{par} + j\omega R_{par} C_{par}}$$




Bode plots of the impedance:

 

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

Effects of Component Leads: Inductors

Measured impedance of a 1.2 μH inductor:

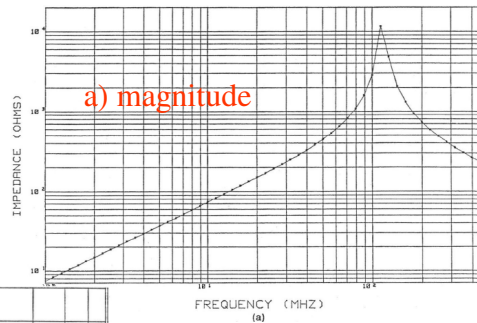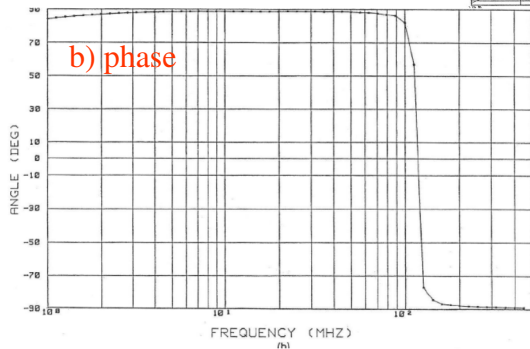 

Note the self resonant frequency (pure resistive impedance)

Source: P.R. Clayton: Introduction to Electromagnetic Compatibility, 2nd edition, 2006, John Wiley & Sons.

P5.4.1.

The magnitude of an impedance is sketched as a Bode plot

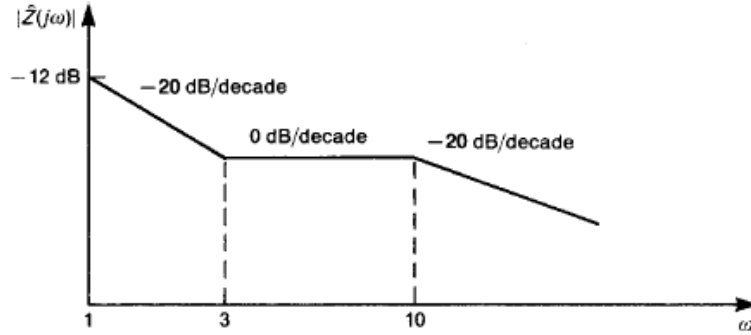


FIGURE P5.4.1

Determine one possible impedance expression for this.

 


FIGURE P5.4.1

From the Bode plot
Circuit has 2 Cs and 1 R

Three possible configurations:

