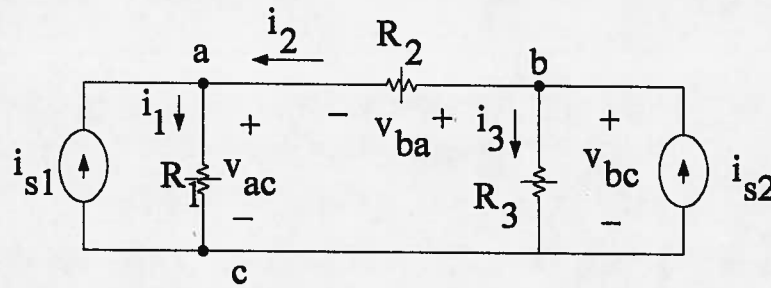


Elec275 – Principles of Electrical Engg
Fall 2014 – Quiz 1(b)

1. For the network shown below, (a) the various component values are given as: $i_{s1} = 2 \text{ mA}$, $R_1 = 6 \text{ k ohms}$, $R_2 = 10 \text{ k ohms}$, $R_3 = 8 \text{ k ohms}$. Determine the value of i_{s2} so that $v_{ba} = 10 \text{ volts}$. (Use only KCL, KVL and/or OL). (b) Also, determine the power dissipated in each of the resistances R_1 , R_2 and R_3 .

(5 marks)



a)

Solution:
$$i_2 = \frac{V_{ba}}{R_2} = \frac{10}{10^k} = 1 \text{ (mA)}$$

kcl @ node a:
$$i_{s1} + i_2 - i_1 = 0$$

$$i_1 = 2 + 1 = 3 \text{ (mA)}$$

kvl around bacb:
$$V_{ba} + V_{ac} = V_{bc}$$

$$i_2 R_2 + i_1 R_1 = i_3 R_3$$

$$V_{bc} = 28 \text{ (V)} \Rightarrow i_3 = \frac{28}{8} = 3.5 \text{ (mA)}$$

kcl @ node b:
$$i_2 + i_3 = i_{s2}$$

$$i_{s2} = 4.5 \text{ (mA)}$$

b)
$$P_{R_1} = i_1^2 R_1 = 54 \text{ (mW)}$$

$$P_{R_2} = i_2^2 R_2 = 10 \text{ (mW)}$$

$$P_{R_3} = i_3^2 R_3 = 98 \text{ (mW)}$$