

Lecture 8 – Gate-Level Minimization – Part II

Rami Abielmona
University of Ottawa
February 06, 2015
ITI 1100 B
Digital Systems I

Presentation Outline


- Implicants
- POS Form
- Seven-Segment Decoder
- Implementation using NAND/NOR
- Other Implementations
- Key terms

Implicants

Given a logic function $z = F(x_0, x_1, x_2, \dots)$

Implicant = product term that, if equal to 1, implies $f = 1$

 - whenever the implicant is $I \Rightarrow f = 1$
- f can be 1 other times, as well: may be implied by other implicants




- from the K-map point of view, an implicant is a rectangle of 1, 2, 4, 8, ... (any power of 2) 1's

Prime Implicant = cannot be totally covered by another implicant (e.g., **AC**, **BC**, **A'B**)

Each "1" which is covered by a single implicant is marked with a star (*)

Essential Prime Implicant = a prime implicant that contains at least one "1*"

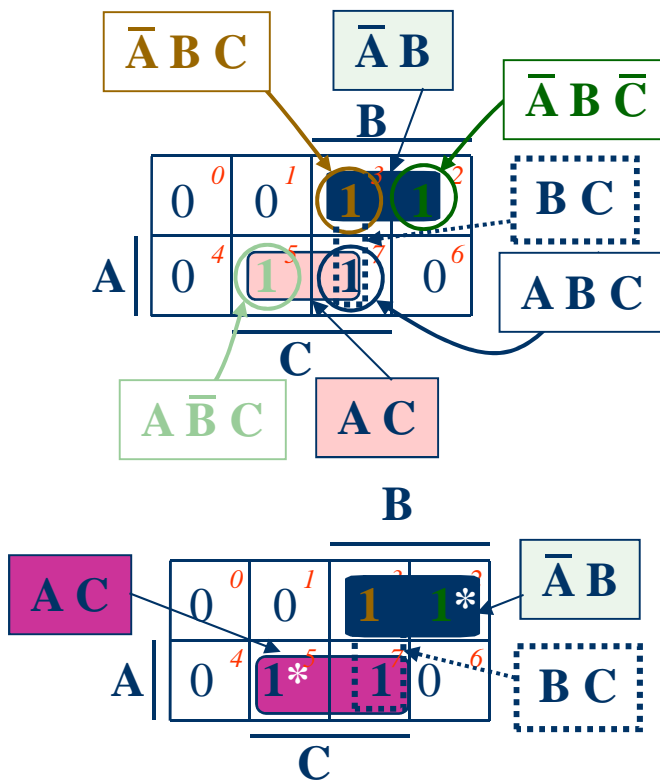A **minimum cover** of a logic function has to contain all its prime implicants



Prime implicants

When grouping square:

- a group should contain a maximum of adjacent squares

→ Known as *PRIME IMPLICANT*

- each group represents one term in the function
- a function should contain a minimum set of terms


when selecting groups :

- Select only those groups that have at least one square that is not covered by another group:

→ Known as *Essential Prime Implicant*

- Do not select a group that has all its squares covered by other groups: → Known as *Optional prime implicant*

b) Obtain Sum of Products for F

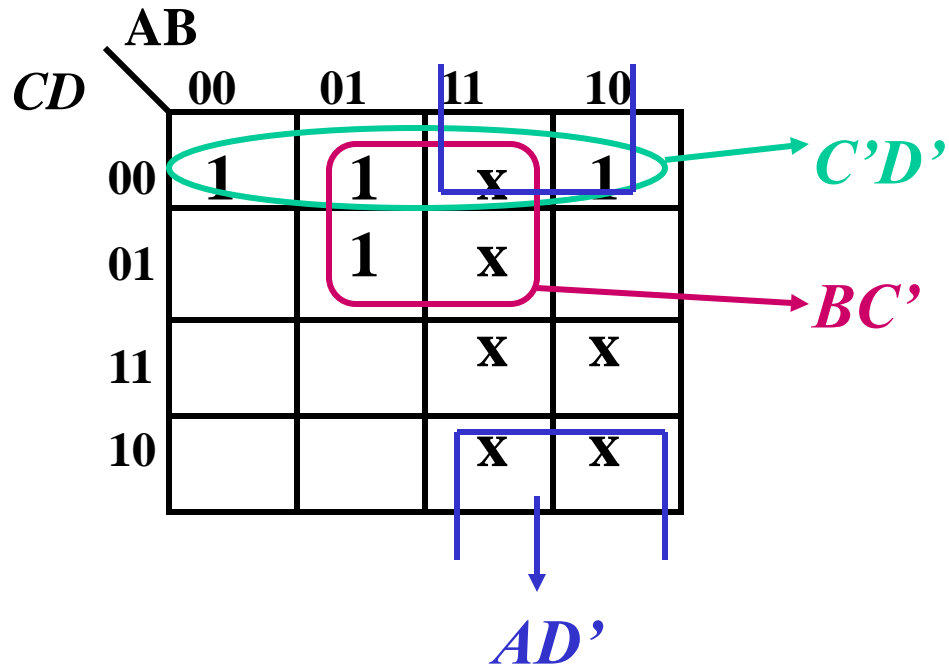

$$F = BC' + C'D'$$

c) Obtain product of Sums : 2 STEPS


1 - use Minterms to simplify and obtain F'

$$F' = B'D + C$$



2 - complement F' to get the Product of Sum form

$$F'' = (B'D + C)' = (B'' + D') \cdot C'$$

$$F = (B + D') \cdot C'$$

 


Two Level Implementations

 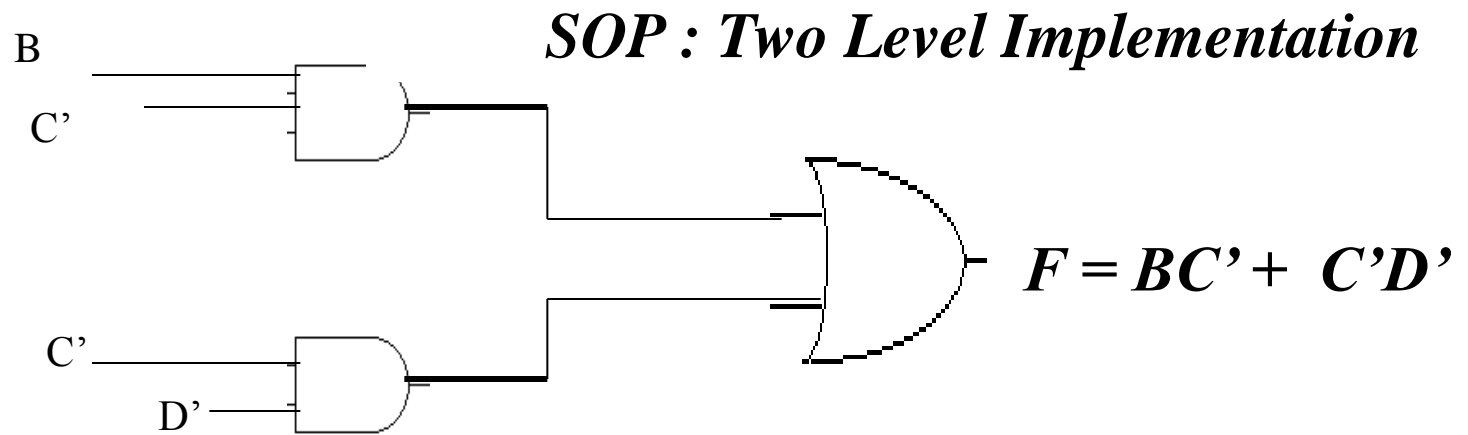

Seven Segment Decoder -Example

 a BCD to Seven Segment Decoder inputs data in BCD form and converts it to a seven segment output





(a) Segment designation


(b) Numerical designation for display

A- BCD to Seven Segment Decoder

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x

  

Don't care terms

 

Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

K-MAP

		CD			
		00	01	11	10
AB	00	1		1	1
	01		1	1	1
	11				
	10	1	1		

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1		1	
	11				
	10	1	1		

$a =$





		CD			
		00	01	11	10
AB	00	1	1	1	
	01	1	1	1	1
	11				
	10	1	1		

$b =$

		CD			
		00	01	11	10
AB	00	1		1	1
	01		1		1
	11				
	10	1	1		

$c =$

$d =$

    

g		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	1	1	0	1
	11	d	d	d	d
	10	1	1	d	d

$$g = BC' + B'C + CD' + A$$

Implementations using NAND & NOR Gates


- Digital circuits are frequently constructed with NAND or NOR gates rather with AND and OR gates.

→ Both NAND and NOR gates are very valuable as any design can be realized using either one.


- It is easier to build digital circuits using all NAND or NOR gates than to combine AND, OR, and NOT gates.

- NAND/NOR gates are typically faster and cheaper to produce.

Logic Operations with NAND Gates

 




(a) AND-invert

 

(b) Invert-OR

Two Graphic Symbols for NAND Gate


Logic Operations with NAND Gates

   


Logic Operations with NAND Gates

NAND gates Implementations



$$(AB)'' + (CD)'' = ((AB)'(CD)')'$$

 

a) Two level with AND-OR

 

b) Two level with NAND & Invert-OR

  




c) Two level with NAND gates
(use this in exam)

Three Ways to Implement $F = AB + CD$

NAND gates implementations -Examples


1: $(xy)'$ 2: $(x'y)'$ 4: $((xy)')' + ((x'y)')' + (z)'$ = $xy' + x'y + z$

   3: $((xy)')(x'y)(z)'$ = $(xy)'' + (x'y)'' + (z)'$ = $xy' + x'y + z$




Using NAND gates to implement SOP

Logic Operations with NOR Gates

 




(a) OR-invert

 

(a) Invert-AND

Two Graphic Symbols for NOR Gate


Logic Operations with NOR Gates

   

Logic Operations with NOR Gates

NOR gates Implementation -Examples

POS with NOR

 

Implementing $F = (A + B)(C + D)E$


Other implementation examples

		yz		y	
		00	01	11	10
x	0	1	0	0	0
x	1	0	0	0	1
		z			


$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

 (a) Map simplification in sum of products.




AND-NOR

 


NAND-AND

(b) $F = (x'y + xy' + z)'$

 

OR-NAND

 

NOR-OR

(c) $F = [(x + y + z)(x' + y' + z)]'$

Key Terms and Review Points

- Essential Prime Implicant
 - Implicant
 - Optional Prime Implicant
 - Prime Implicant
 - Minimum Cover
 - NAND/NOR Implementation
-
- References: Dr. Karmouch and Dr. Groza ITI 1100 Slides