

Lecture 10 – Combinational Logic – Part II

Rami Abielmona
University of Ottawa
February 10, 2015
ITI 1100 B
Digital Systems I

Presentation Outline

- Implementation Using Decoders
- Implementation Using NAND Gates
- Active-High/Active-Low Decoders
- Encoders
- Priority Encoders
- Multiplexers/Demultiplexers
- Key terms

Implementing Boolean Functions Using Decoders

- Any combinational circuit can be constructed using **decoders and OR gates!** Why?

→ **Here is an example:**

Implement a full adder circuit with a decoder and two OR gates.

Recall full adder equations, and let X, Y, and Z be the inputs:

$$S(X, Y, Z) = \Sigma m(1, 2, 4, 7)$$


$$C(X, Y, Z) = \Sigma m(3, 5, 6, 7).$$

- **Since there are 3 inputs and a total of 8 minterms, we need a 3-to-8 decoder.**

Implementing Boolean Functions Using Decoders


$$S(X,Y,Z) = \Sigma m(1,2,4,7)$$

$$C(X,Y,Z) = \Sigma m(3,5,6,7)$$

 


Implementing a decoder with NAND gates

 - The decoders studied so far are **active-high** decoders (i.e. implemented **with AND gates**)



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 
- Active-low decoders** are implemented **using NAND gates** (i.e. with an inverted EN input and inverted outputs).



EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1


Active-High and Active-Low decoders

 - Active-high decoders generate *minterms*, as we have already seen.



$$\begin{aligned}Q3 &= S1 S0 \\Q2 &= S1 S0' \\Q1 &= S1' S0 \\Q0 &= S1' S0'\end{aligned}$$

 - Active-low decoders generate *Maxterms*.



$$\begin{aligned}Q3' &= (S1 S0)' = S1' + S0' \\Q2' &= (S1 S0')' = S1' + S0 \\Q1' &= (S1' S0)' = S1 + S0' \\Q0' &= (S1' S0')' = S1 + S0\end{aligned}$$

Building a 3-to-8 decoder with two 2-to-4 decoders

- Another way to design a 3-to-8 decoder is to use two 2-to-4 decoders.
- from the truth table of 3-8 decoder we can notice some patterns:
 - When $S_2 = 0$, outputs Q_0 - Q_3 are generated as in a 2-to-4 decoder.
 - When $S_2 = 1$, outputs Q_4 - Q_7 are generated as in a 2-to-4 decoder.
- S_2 can be used as an **Enable input** that activates/deactivates the 2-to-4 decoders.

S_2	S_1	S_0	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q_0 = S_2' S_1' S_0' = m_0$$

$$Q_1 = S_2' S_1' S_0 = m_1$$

$$Q_2 = S_2' S_1 S_0' = m_2$$

$$Q_3 = S_2' S_1 S_0 = m_3$$

$$Q_4 = S_2 S_1' S_0' = m_4$$


$$Q_5 = S_2 S_1' S_0 = m_5$$

$$Q_6 = S_2 S_1 S_0' = m_6$$

$$Q_7 = S_2 S_1 S_0 = m_7$$

Building a 3-to-8 decoder with two 2-to-4 decoders

 
- We can use enable inputs to string decoders together. 3-to-8 decoder constructed from two 2-to-4 decoders:



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Active-low decoder example

 - We can use active-low decoders to implement arbitrary functions as a product of maxterms.
- For example, here is an implementation of the function $f(x,y,z) = \prod M(4,5,7)$, using an active-low decoder.



- The “ground” symbol connected to EN represents logical 0, so this decoder is always enabled.
- We need an AND gate for a product of sums.

Decoder Expansions

- Larger decoders can be constructed using a number of smaller ones.

→ HIERARCHICAL design

- *Example:*

A 6-to-64 decoder can be designed using **four 4-to-16** and **one 2-to-4** decoders. How? (tip: Use the 2-to-4 decoder to generate the enable signals to the four 4-to-16 decoders).

4-input tree decoder

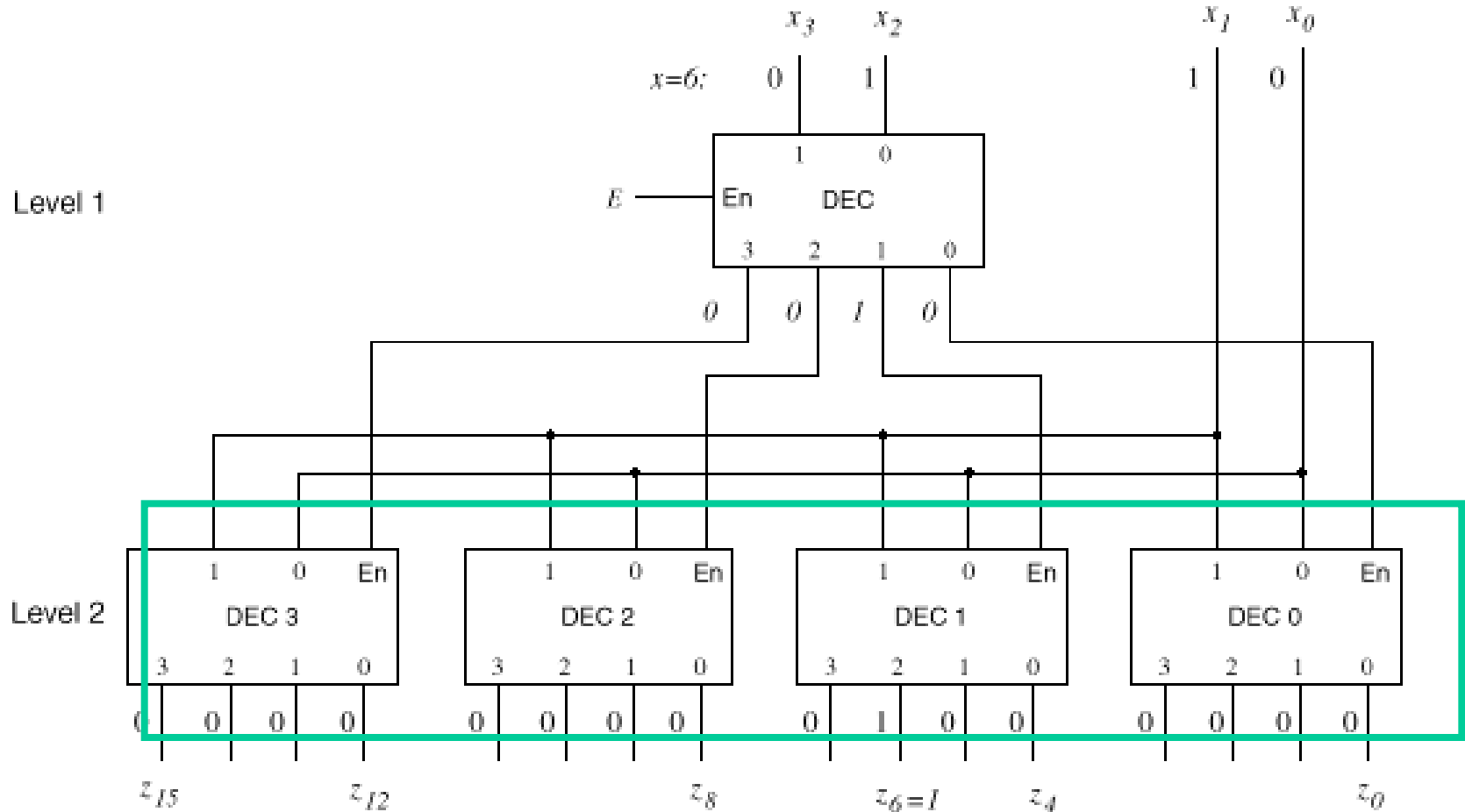


Figure 9.8: 4-input tree decoder

Encoder

- An encoder has a number of input lines, only one of which is activated at a given time.
- The opposite of the decoding process.

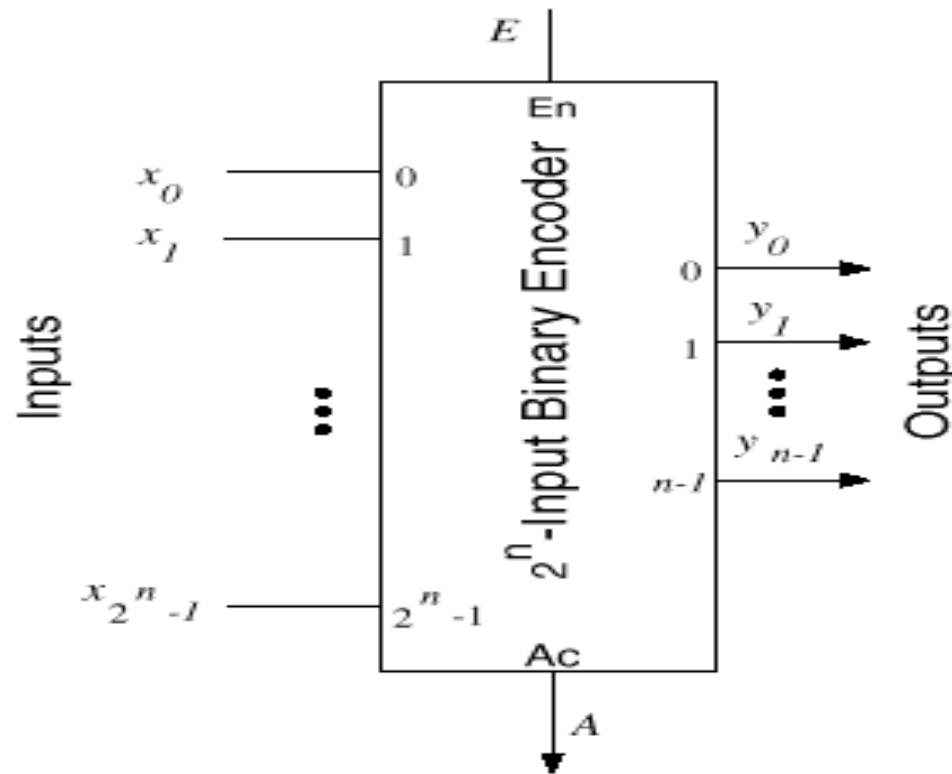


Figure 9.12: 2^n -input binary encoder.

Encoder

Example: 8-to-3 Encoder

x_7	x_6	x_5	x_4	x_3	x_2	x_1	x_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Encoder

 


Figure 9.13: Implementation of an 8-input binary encoder.

Encoder

- In the previous truth table each line selected 0 through 7 generates its own binary code such as a 1 is a 001, 5 is a 101 and so on.
- Boolean functions for Outputs

$$y_2 = x_4 + x_5 + x_6 + x_7$$

$$y_1 = x_2 + x_3 + x_6 + x_7$$

$$y_0 = x_1 + x_3 + x_5 + x_7$$

Simple Encoder Design Issues

- There are two ambiguities associated with the design of a simple encoder:
 - Only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination (for example, if x_3 and x_6 are 1 simultaneously, the output of the encoder will be 111. (100 and 011))
 - An output with all 0's can be generated when all the inputs are 0's, or when X_0 is equal to 1.

Encoder

Example: 8-to-3 Encoder

x_7	x_6	x_5	x_4	x_3	x_2	x_1	x_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Priority Encoders

- Solves the ambiguities multiple assigned inputs are allowed; **one has priority over all others.**
- Separate indication of **not assigned** inputs (all inputs are 0s).



Example: 4-to-2 Priority Encoder Truth Table

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


4-to-2 Priority Encoder (cont.)

- The operation of the priority encoder is such that:
 - If two or more inputs are equal to 1 at the same time, the input in the highest-numbered position will take precedence.
 - A *valid output indicator*, designated by V , is set to 1 only when one or more inputs are equal to 1. $V = D_3 + D_2 + D_1 + D_0$ by inspection.

4-to-2 Priority Encoder (cont.)

  


4-to-2 Priority Encoder (cont.)

 


Multiplexer (MUX): Data Selectors

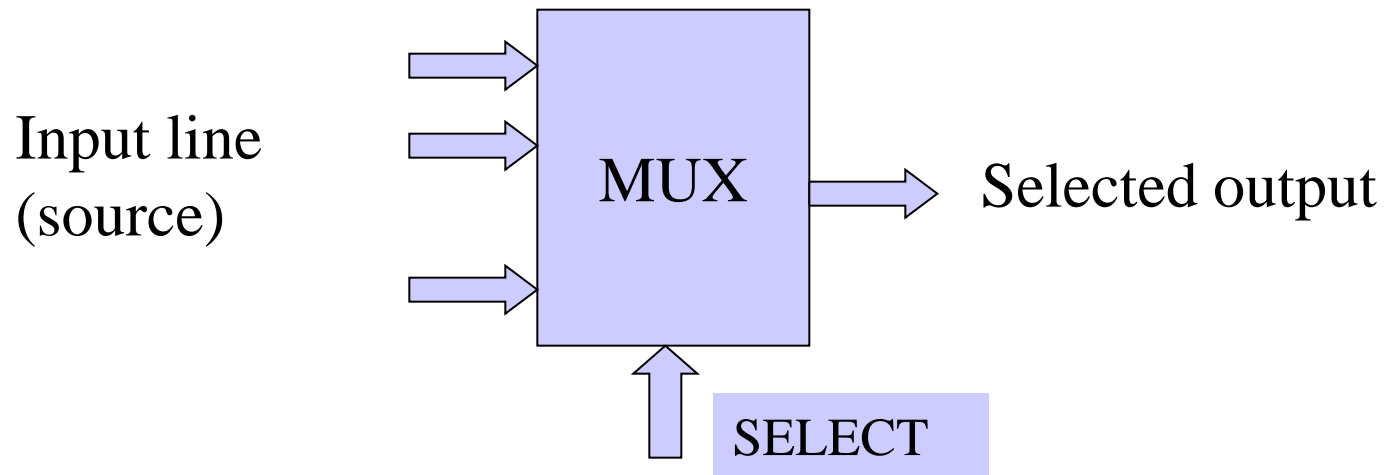- A multiplexer selects one of several input signals and passes it on to the output.
- Routing of selected data input to the output is controlled by SELECT inputs.



Multiplexer

 
- Multiplexers, or muxes, are used to choose between resources.
- A real-life example: in the old days before networking, several computers could share one printer through the use of a switch.



Multiplexer (MUX): Data Selectors [2]

- A combinational circuit with 2^n *data inputs*, 1 data output and a number of bit *control input* that select one of the data inputs

 C takes the value of A or B depending on the value of S



2-to-1 Multiplexer

S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


2-to-1 Multiplexer

When $S = 0 \rightarrow C = A$, when $S = 1 \rightarrow C = B$


$$C = \bar{S}.A.\bar{B} + \bar{S}.A.B + S.\bar{A}.B + S.A.B$$
$$= \bar{S}.A + S.B$$

Inputs			Output
S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Two level implementation

 

4 – 1 Multiplexer (MUX)

 

if $(S_1 S_0)_2 = 0$ Then $Y = I_0$

$$Q = \bar{S}_0 \cdot \bar{S}_1 \cdot I_0$$


if $(S_1 S_0)_2 = 1$ Then $Y = I_1$

$$Q = S_0 \cdot \bar{S}_1 \cdot I_1$$

and so on, thus we have

$$Y = \bar{S}_1 \cdot \bar{S}_0 \cdot I_0 + \bar{S}_1 \cdot S_0 \cdot I_1 + S_1 \cdot \bar{S}_0 \cdot I_2 + S_1 \cdot S_0 \cdot I_3$$

4-1 MUX- Two level Implementation

 

(a) Logic diagram


s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

FIG. 4.25 4-to-1 Data Multiplexer

Demultiplexer (DEMUX): Data Distributor

 
- Demultiplexer (DEMUX) takes a single input and distributes it over several outputs.



1-line-to-8-line Demultiplexer

SELECT code			OUTPUTS							
S_2	S_1	S_0	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

1-line-to-8-line Demultiplexer

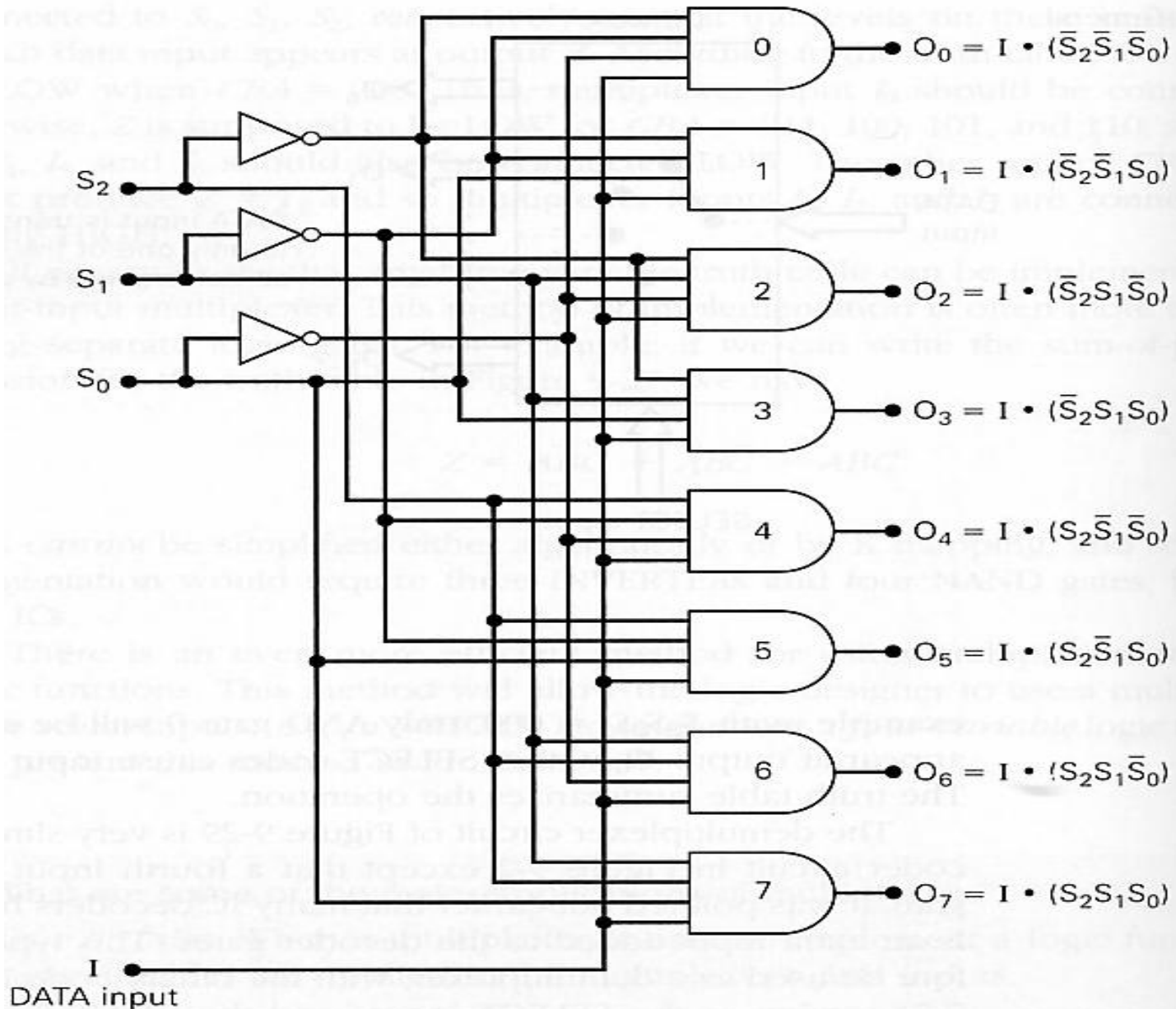

Key Terms and Review Points

- 1-to-8 Demultiplexer
 - 8-to-3 Encoder
 - 4-to-2 Priority Encoder
 - Active-High Decoders
 - Active-Low Decoders
 - Decoder Expansions
 - Demultiplexer
 - Encoders
 - Multiplexer
 - Priority Encoders
-
- References: Dr. Karmouch ITI 1100 Slides