




COURSE : Electrical power engineering	NUMBER: ELEC 331	SECTION: W
EXAMINATION : Midterm	DATE : 24-02-14	TIME : 13:15 - 14:30 # OF PAGES: 2
INSTRUCTOR: Luiz Lopes		
SPECIAL INSTRUCTIONS: - Answer all questions. No crib sheets. In cascaded questions, you can assume suitable values for parameters you are not able to calculate in previous sub-questions.		

1) A 220 V / 60 Hz three-phase  $\Delta$ -connected generator supplies two loads. Load 1 presents an impedance of  $2.5 \angle -36.87^\circ \Omega$  while Load 2 consists of a resistance of  $3 \Omega$  in series with an inductance of 4 mH. Compute:

- The rms value of the line voltage across the loads
- The (three-phase) reactive power consumed by Load 1.
- The rms value of the phase current in Load 2 ( $I_{\phi 2}$ ).


(30 marks)

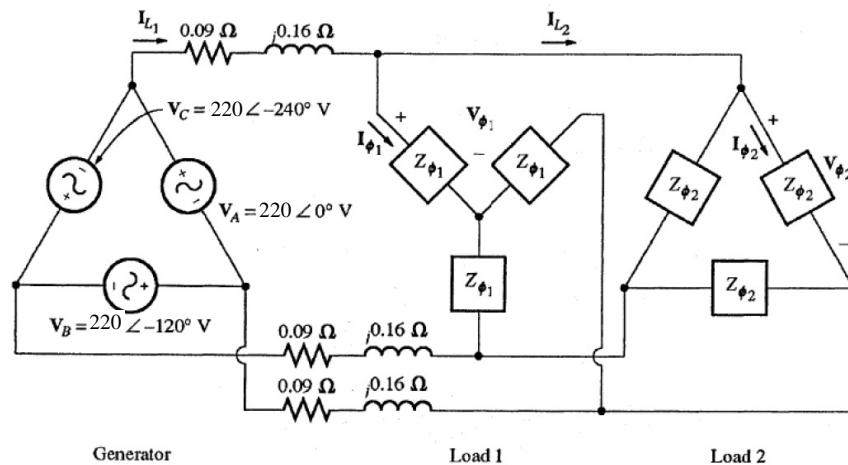

2) Consider the magnetic structure shown below. The DC current ( $i$ ) is equal to 8 A.

- Draw the analogous magnetic circuit, clearly showing the MMF, and its value, the flux (direction) and the reluctance(s).
- Determine the flux density ( $B$ ) in the (metal) core. Neglect the fringing effect of the air-gap. (ELEC-275 final 2012)


(20 marks)

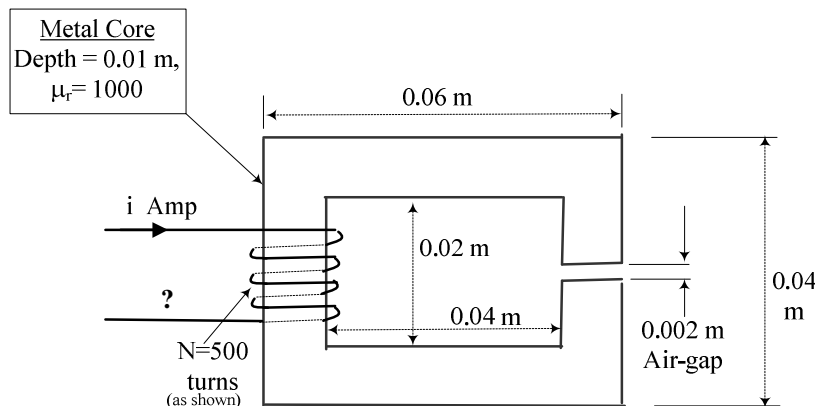

Drawing not exactly to scale

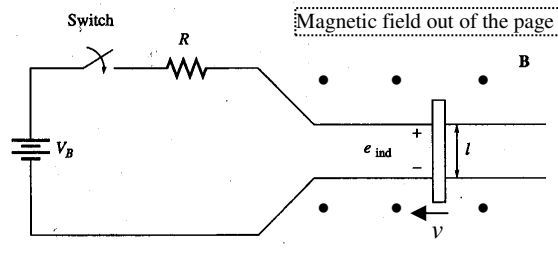3) The linear DC machine shown below presents the following parameters:  $V_B = 100\text{ V}$ ,  $R = 0.2\ \Omega$ ,  $l = 5\text{ m}$  and  $B = 0.5\text{ T}$ . Consider the steady-state condition when the switch is closed and the bar is moving with a speed of  $32\text{ m/s}$ . Compute:

- The power supplied by the battery to the DC machine
- The required external force (magnitude and direction, i.e. right-to-left or left-to-right) on the bar for this operating condition.




(20 marks)

4) A  $75\text{ kVA}$   $14.4\text{ kV}:240\text{ V}$  single-phase transformer has the following parameters:  $R_{eq} = 7.68\text{ m}\Omega$  and  $X_{eq} = 38.4\text{ m}\Omega$ , seen from the low voltage side and  $R_c = 100\text{ k}\Omega$  and  $X_M = 250\text{ k}\Omega$ , seen from the high voltage side.

- Draw the per-unit equivalent model showing all impedances and their magnitudes.
- Using the pu equivalent model, compute the voltage regulation of the transformer when supplying  $75\text{ kVA}$  to a resistive inductive load with power factor of  $0.85$  and at rated (load) voltage.
- How much power could this transformer supply to a load if connected as a step-up auto-transformer?


(30 marks)

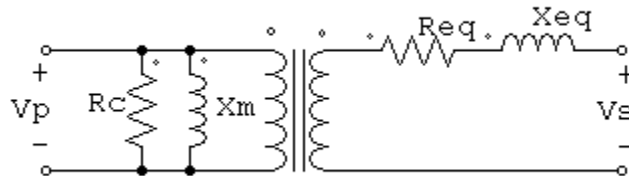

## Formula sheet

### Ac circuits:

$$\begin{aligned}\bar{S} &= \bar{V} \bar{I}^* = P + jQ = |\bar{V}| |\bar{I}| (\cos \phi + j \sin \phi) \\ S &= \sqrt{P^2 + Q^2} \quad PF = P/S = \cos \phi \\ P_{3\phi} &= \sqrt{3} V_L I_L \cos \theta = 3 I_L^2 Z \cos \theta \\ Q_{3\phi} &= \sqrt{3} V_L I_L \sin \theta = 3 I_L^2 Z \sin \theta \\ S_{3\phi} &= \sqrt{3} V_L I_L = 3 I_L^2 Z\end{aligned}$$

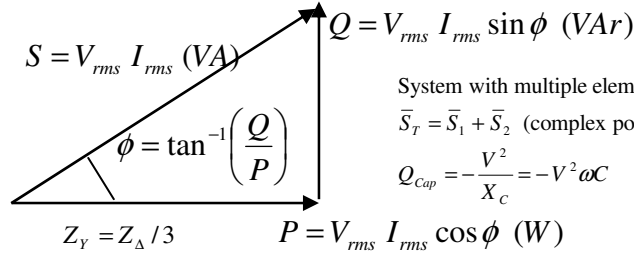

System with multiple elements

$$\bar{S}_T = \bar{S}_1 + \bar{S}_2 \text{ (complex power!), } Q_T = Q_{L1} + Q_{L2}, P_T = P_{L1} + P_{L2}$$

$$Q_{Cap} = -\frac{V^2}{X_C} = -V^2 \omega C$$

### Magnetic Circuits:

$$\oint \mathbf{H} \cdot d\mathbf{l} = I_{net}, H l_c = N i, H = \frac{N i}{l_c} \text{ (Ampere-turn/m)} \quad B = \mu H, \mu = \mu_r \mu_0, \mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$\phi = \int_A \mathbf{B} \cdot d\mathbf{A}, \phi = BA, \phi = \frac{\mu N i A}{l_c} \text{ (Weber - Wb)} \quad \mathfrak{S} = N i, \mathfrak{S} = \phi \mathfrak{R}, \mathfrak{R} = \frac{\mathfrak{S}}{\phi} = \frac{l_c}{\mu A} \quad e_{ind} = N \frac{d\phi}{dt}$$

$$e_{ind} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} \quad F = i(\mathbf{l} \times \mathbf{B})$$

### Transformers:

$$\text{(ideal)} \quad \frac{v_P(t)}{v_S(t)} = \frac{N_P}{N_S} = a, \quad \frac{i_P(t)}{i_S(t)} = \frac{N_S}{N_P} = \frac{1}{a}$$

$$P_{in} = P_{out}, Q_{in} = Q_{out}, S_{in} = S_{out}, Z_{in} = a^2 Z_L$$

$$Y_E = \frac{1}{R_C} - j \frac{1}{X_M} = |Y_E| \angle -\theta_{OC}, |Y_E| = \frac{I_{OC}}{V_{OC}}, \cos \theta_{OC} = \frac{P_{OC}}{I_{OC} V_{OC}}$$

$$Z_{SE} = R_{eq} + jX_{eq} = |Z_{SE}| \angle \theta_{SC}, |Z_{SE}| = \frac{V_{SC}}{I_{SC}}, \cos \theta_{SC} = \frac{P_{SC}}{I_{SC} V_{SC}}$$

$$VR = \frac{V_{S,nl} - V_{S,fl}}{V_{S,fl}} \times 100\% \quad \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{out}}{P_{out} + P_{core} + P_{Cu}} \times 100\%, \quad P_{Cu} = I_S^2 R_{eq}, \quad P_{core} = \frac{(V_p / a)^2}{R_C}$$

$$v(t) = V_M \sin \omega t \quad \phi(t) = \frac{1}{N_p} \int v(t) dt \quad \phi(t) = -\frac{V_M}{\omega N_p} \cos \omega t \quad \hat{\phi}_{ss} = -\frac{V_M}{\omega N_p}$$

$$\text{autotransformers: } \frac{V_C}{V_{SE}} = \frac{N_C}{N_{SE}} \quad N_C I_C = N_{SE} I_{SE} \quad \frac{V_L}{V_H} = \frac{N_C}{N_{SE} + N_C} \quad \frac{I_L}{I_H} = \frac{N_{SE} + N_C}{N_C} \quad \frac{S_{IO}}{S_{Wind}} = \frac{N_{SE} + N_C}{N_{SE}}$$

$$\text{pu system: } \text{Quantity (pu)} = \frac{\text{Actual Value}}{\text{Base value of quantity}}$$

