

**MCG 4136 / MCG 5184
MECHATRONICS**

Final Examination (60%)

Dec 11, 2012

Prof. D. Neculescu

Page 1 of 4

Duration: 3 h.

NOTE: Closed book exam. Calculators permitted. All **12** problems of equal value.

1. A strain gauge with nominal resistance $R = 0.2 \text{ k}\Omega$ is installed in a branch of a Wheatstone bridge having for unstrained strain gauge $R_1 = R_2 = R_3 = R_4 = R$ and $V_i = 12 \text{ V}$. The strain gauge is subject to a strain as a result of bending the beam on which it is cemented. A digital voltmeter with input resistance $R_m = 10 \text{ M}\Omega$ gives a reading of $V_o = 20 \text{ mV}$

Calculate the change of the resistance ΔR and the strain σ for gauge factor $G = 2.00$.

2. A weighted-resistor Digital-to-Analog Converter has $N = 8$ bit, the reference voltage $v_R = 10 \text{ V}$, the Most Significant Bit resistance $R = 1 \text{ k}\Omega$, and the feedback resistance of the operational amplifier $R_F = 5 \text{ k}\Omega$.

Calculate:

- The output voltage v_0 corresponding to the Least Significant Bit;
 - The output voltage v_0 corresponding to the Most Significant Bit;
 - The maximum value of the output voltage v_0 ;
 - The nominal full-scale output voltage v_0 ;
 - The resolution
 - The output voltage v_0 corresponding to the binary input 10110011.
-

3. An incremental encoder with 2° slots evenly distributed along the circumference of 10 cm radius is installed on a shaft rotating at 1000 rpm.

Calculate the frequency in of the pulse output (in pulses per second) of the encoder before sampling.

4. Assume a wire of diameter D , length L , cross section area A and resistivity ρ

a) Obtain the equation for the gauge factor G function of axial strain and Poisson ratio and resistivity ρ change with strain.

b) For a wire with 300Ω nominal resistance, a Poisson ratio $\mu = 0.5$ and an insignificantly low resistivity change with strain, calculate the change of the resistance of the wire when subject to an axial strain of 10^{-12} m/m.

5. An accelerometer based o a strain gauge consist in a cantilever beam of length $L = 5$ mm, width $w = 1.5$ mm and thickness $t = 0.2$ mm, fitted with a (seismic) mass $M = 0.001$ kg. The modulus of elasticity of the beam is $E = 200 \times 10^9$ N/m². The strain gauge cemented at $l = 5$ mm, from the free end of the beam and having $G = 2.0$ is connected to a bridge which is interfaced to an ADC through an inverting amplifier. Assume nominal resistance of the strain gauge of $R = 300 \Omega$ and the supply voltage of the bridge $V_i = 5$ V.

The output voltage of the inverting operational amplifier is $V_o = [V_i R_o G \epsilon / (2R)]$

a) Calculate the acceleration a which produces a voltage output $V_o = 0.1$ V when the resistance of the inverting amplifier is $R_o = 1$ M Ω .

b) In case the ADC has only the range 0 to 10 V available, calculate a value for R_o which will give 5 V for V_o , for an acceleration value and all other factors being kept the same.

6. The Gain – Bandwidth Product (GBP) of an operational amplifier is 10 MHz. The operational amplifier is an amplifier with a gain of 100 dB.

a) Calculate the bandwidth of the amplifier;

b) Can this amplifier be used for amplifying signals of 1000 Hz. If not, calculate the gain of the amplifier having the same GBP = 10 MHz


7. Assume a positioning measuring potentiometer (with total resistance $R = 35 \text{ k}\Omega$, total length $L=5 \text{ cm}$ and input voltage $V_i = 10 \text{ V}$) has the wiper at $x= 2.5 \text{ cm}$. The voltage V_o of the potentiometer is measured with an analog voltmeter with input resistance $R_o = 35 \text{ k}\Omega$ connected as load of a potentiometer.

- Calculate the voltage V_o measured by the analog voltmeter;
 - Calculate the error in analog voltmeter measurement of V_o with regard to the V_o measured by a digital voltmeter with $R_o = 2 \text{ M}\Omega$.
-

8. A tachometer has the tachometer constant $K = 6 \text{ V/krpm}$ (krpm= 1000 revolutions per minute) and is connected to a 8 bit ADC which has input voltage range from 0 to 10 V.

- Calculate the maximum acceptable velocity that can be measured by the tachometer in this configuration.
 - Calculate the velocity measurement resolution of the tachometer with ADC.
-

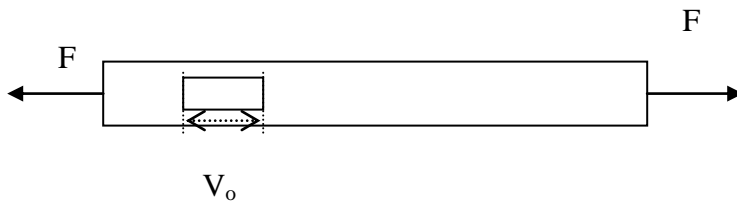9. A strain gauge can be installed on a steel bar to measure the applied axial force, as shown



The bar has the Young elastic modulus $200 * 10^6 \text{ kN/m}^2$ and a cross section area 2 cm^2 is subject to an axial force F . For measuring this force, a strain gauge with a nominal resistance $R = 300 \Omega$ is cemented to the bar and connected in a branch of bridge with all other branches with resistances equal to 300Ω and with the inverting amplifier output resistance of $1.5 \text{ M}\Omega$. The strain gauge factor is 2.0 and the voltage $V_i = 12 \text{ V}$.

Calculate the force F given a measured voltage output 6 V .

=====

10. A PC based data acquisition system is considered for a J type thermocouple, having a Seebeck coefficient of $51 \mu\text{V}/^\circ\text{C}$. Two limit designs will have to be evaluated.

Design A)

- a **8-bit A/D** converter which has input voltage ranges of 0 to 100 mV or 0 to 10 V selectable by software;
- a standard electronic reference junction block with a temperature uncertainty of $\pm 0.3^\circ\text{C}$ at 0°C ;
- a standard thermocouple with $\pm 0.75^\circ\text{C}$ error limit.

Design B)

- a **16-bit A/D** converter which has input voltage ranges of 0 to 10 V or 0 to 1 V selectable by software.
- a special electronic reference junction block with a temperature uncertainty of $\pm 0.02^\circ\text{C}$
- a special thermocouple with $\pm 0.025^\circ\text{C}$ error limit 0°C

Compare the two designs.

- a) calculate the resolution and determine the suitable input voltage range for the analog input voltage for A/D converter of **Design A and B**;
 - b) calculate the combined uncertainty (of A/D converter, Reference Junction and Thermocouple) regarding the temperature measurement. Which design is preferable?
-

11. For a weighted resistors 4 bit Digital to Analog Converter:

- a) Draw the equivalent circuit diagram
 - b) What is the ratio of the:
resistance for the Least Significant Bit / resistance for the Most Significant Bit.
-

12. Consider a Stepper Motor with 2 phase stator and 6 teeth rotor.

- a) Draw the diagram of the motor showing the stator phases and their electric Connections as well as the 6 teeth rotor.
 - b) Show the diagrams for four steps in full-stepping case.
- =====

HINTS

$$F = \frac{2RAE}{V_i R_0 G} V_0$$

axial stress = $6 \text{ Mal} / (w t^2)$.

$$v_0 = \{ 2 R_F v_R / R \} \{ b_1 / 2 + b_2 / (2^2) + \dots + b_N / (2^N) \}$$