

March/6/12PhysPylan FergusonRecap:

Faraday's law $\rightarrow \mathcal{E} = -\frac{d}{dt} (\overbrace{BA \cos \theta}^{\Phi_B})$

Lenz's law \rightarrow $A \cos \theta \frac{dB}{dt}$ $B \cos \theta \frac{dA}{dt}$ $BA \frac{d}{dt} (\cos \theta)$, $\theta = \omega t$

• Square loop pulled out of a magnitude field with velocity

$$\mathcal{E} = -\frac{d}{dt} (BLx) = -BLv_{\text{velocity}}$$

Current: $i = \frac{\mathcal{E}}{R_{\text{loop}}}$

Force: $F = iLB = \frac{B^2 L^2 v}{R_{\text{loop}}}$

Power: $P = Fv = \frac{B^2 L^2 v^2}{R_{\text{loop}}}$

• Square loop rotated in a magnitude field with freq "f"

$$\mathcal{E} = -NBA 2\pi f \sin[2\pi ft]$$

Inductors:

$$\mathcal{E} = -\left(\mu_0 \frac{N^2 A}{L}\right) \frac{di}{dt} = -L \frac{di}{dt}$$

Inductance [H]



RL circuits



$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$L \frac{di}{dt} + iR = \mathcal{E}$$

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-\left(\frac{R}{L}\right)t} \right)$$

if $t=0$, $i=0$

$t=\infty$, $i = \frac{\mathcal{E}}{R}$

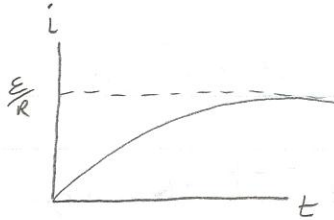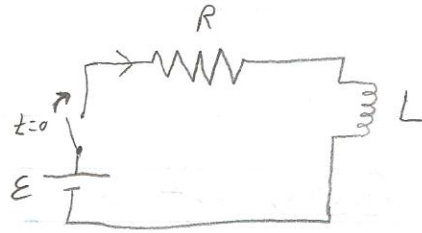

Energy storage

$$\mathcal{E} = L \frac{di}{dt} + iR$$

multiply by i ...

$$\mathcal{E}i = Li \frac{di}{dt} + i^2 R$$

↑ Power dissipated from battery ↑ Power dissipated in inductor ↑ Power dissipated in resistor

$$\frac{dU}{dt} = Li \frac{di}{dt}$$

$$U_B = \int Li \frac{di}{dt} = \frac{1}{2} Li^2$$

$$U_B = \frac{1}{2} Li^2 \quad \text{Energy in inductor}$$

March 6/12

Phys

Dylan Ferguson


LC Oscillations

E.M. Oscillations

L.C. circuits

$$U_B = \frac{1}{2} L i^2, \quad U_E = \frac{1}{2} \frac{q^2}{C}$$
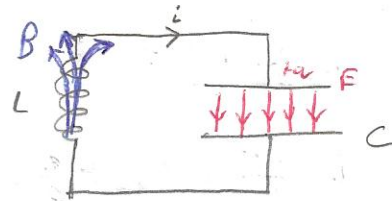
$$U_B + U_E = U = \text{constant} \\ (\text{no resistance})$$



$$\frac{dU}{dt} = 0 = \frac{dU_B}{dt} + \frac{dU_E}{dt}$$

$$\frac{d}{dt} \left(\frac{1}{2} L i^2 \right) + \frac{d}{dt} \left(\frac{1}{2} \frac{q^2}{C} \right) = 0$$


$$\frac{di}{dt} \cdot \frac{d}{di} \left(\frac{1}{2} L i^2 \right) + \frac{dq}{dt} \frac{d}{dq} \left(\frac{1}{2} \frac{q^2}{C} \right) = 0$$

$$\frac{di}{dt} L i + \frac{dq}{dt} \frac{q}{C} = 0$$

$$L \frac{di}{dt} + \frac{q}{C} = 0$$

$$\frac{di}{dt} = -\frac{1}{LC} q$$
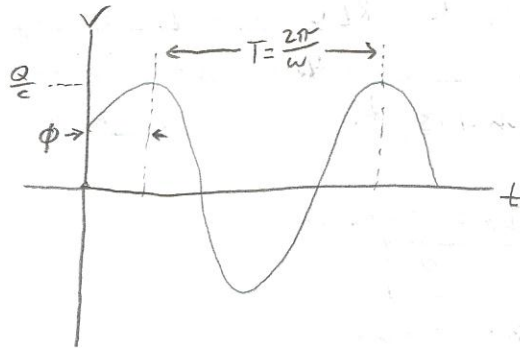
$$\boxed{\frac{d^2 q}{dt^2} = -\frac{1}{LC} q}$$



$$q = Q \cos(\omega t + \phi)$$

initial charge on capacitor \rightarrow Q
 angular frequency \rightarrow $\omega \rightarrow \frac{1}{\sqrt{LC}}$
 phase constant \rightarrow ϕ

Damped Oscillations

$$L \frac{di}{dt} + \frac{q}{C} = -iR \quad \frac{dq}{dt}$$

$$L = \frac{di}{dt} + \frac{q}{C} = -iR$$



$$L = \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

Solve for q:

$$q = Q e^{-\frac{Rt}{2L}} \cos(\omega' t + \phi)$$

$$\omega' = \sqrt{\omega^2 - \left(\frac{R}{2L}\right)^2}$$

$$\left(\frac{1}{LC}\right)$$

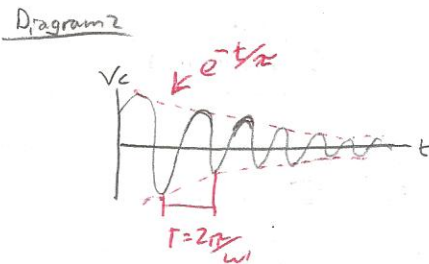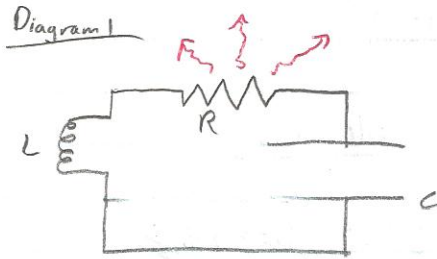

Q: In the RLC circuit displaying damped oscillations as shown (Diagram 2), when the voltage across the capacitor is a maximum, $V = \frac{Q}{C} e^{-\frac{t}{\tau}} \cos[\omega' t + \phi]$. What is the current through the resistor?

a) $I_R = +$ maximum

b) $I_R = 0$

c) $I_R = -$ minimum

March 6/12

Phys

3/12

Pylan Ferguson

AC power

- Driving currents with A.C.
- A.C. power \rightarrow most common form of power because you can easily step up or down with a transformer.



Resistive load

$$V(t) = V_0 \sin(\omega t)$$

(apply ohm's law for the current)

$$V_R = I_R R$$

$$I_R = \frac{V_R}{R} \sin(\omega t)$$

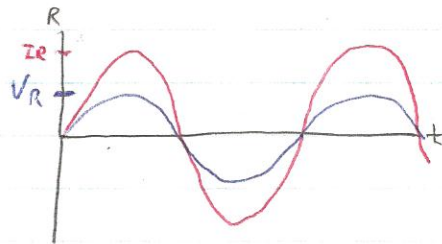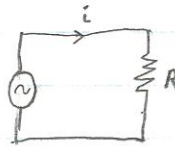


Capacitive load

$$V = V_0 \sin \omega t$$



$$q = CV_0 \sin \omega t$$

$$i = \frac{dq}{dt} = \omega C V_0 \cos \omega t$$

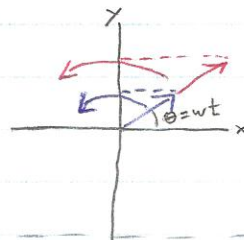Current leads the voltage
(i.e. ahead by 90°)



Capacitive load

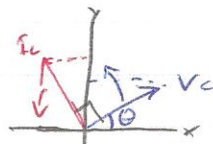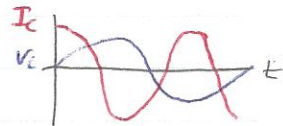

$$X_C = \frac{V}{i} = \frac{V_0 \sin \omega t}{\omega C V_0 \cos \omega t}$$

$$\text{Resistance } X_C = \left(\frac{1}{\omega C} \right) \frac{\sin \omega t}{\sin(\omega t + 90^\circ)}$$

$$|X_C| = \left| \frac{1}{\omega C} \right| \cdot \left| \frac{1}{2\pi f C} \right|$$

