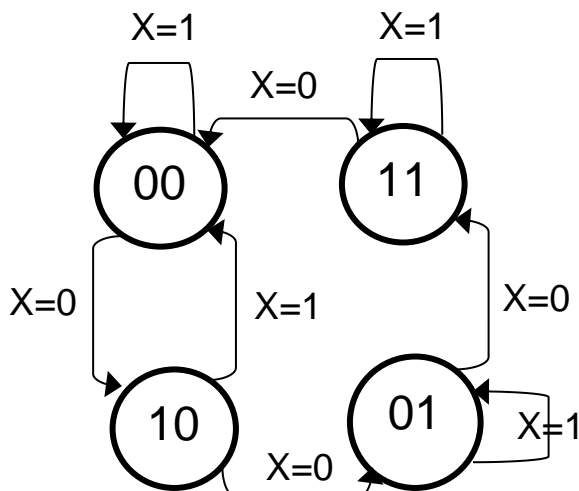


P1. The next figure shows the state diagram of a logic circuit which has a unique one-bit external input x .

- [12 points] Start off by deriving the state table of the circuit. Then, assuming that JK flip-flops are to be used in the implementation, extend the state table with the excitation table of the circuit.
- [12 points] Find simplified expressions for each flip-flop inputs.

2.



	A^n	B^n	X	A^{n+1}	B^{n+1}	J_A	K_A	J_B	K_B
(0)	0	0	0	1	0	1	x	0	x
(1)	0	0	1	1	1	1	x	1	x
(2)	0	1	0	1	1	1	x	x	0
(3)	0	1	1	0	1	0	x	x	0
(4)	1	0	0	0	1	x	1	1	x
(5)	1	0	1	0	0	x	1	0	x
(6)	1	1	0	0	0	x	1	x	1
(7)	1	1	1	1	1	x	0	x	0

SOLUTION:





Recall:

A) the “copy & paste recipe:”

... or B) The JK FF Excitation Table, i.e.:

- $J = \text{next state}$ if **present state is 0**
- $J = \text{don't care (x)}$ if **present state is 1**
- $K = \text{don't care (x)}$ if **present state is 0**
- $K = \text{complement of the next state}$ if **present state is 1**

	if $Q^n = 0$	if $Q^n = 1$
$J =$	[1] Q^{n+1}	[2] x
$K =$	[3] x	[4] $(Q^{n+1})'$

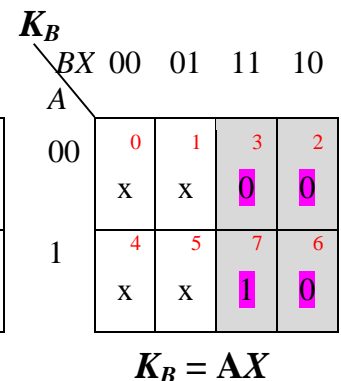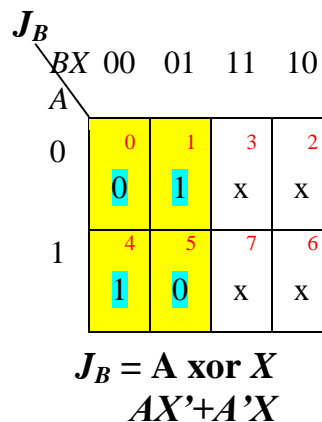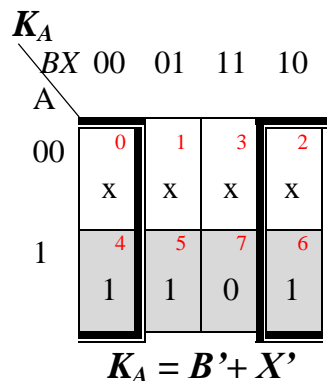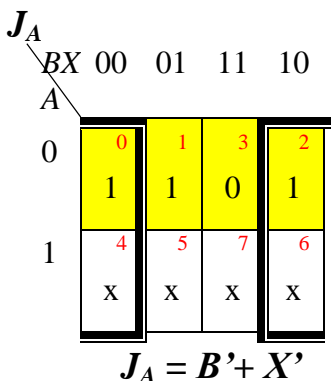

P2. [14 points] A sequential circuit has 3 data inputs DB_2, DB_1 and DB_0 and a control input “LD” (load data). The operation of the sequential circuit is described in the functional Table 1. Design the sequential circuit using three T flip-flops.

(P2.1.) Provide the *next state functions* of the T flip-flops $\{Q_i^{n+1}, i = [0, 1, 2]\}$, either by filling out column Q_i^{n+1} of Table 2, or by writing directly its logic expression $Q_i^{n+1} = \delta(LD, Q_i^n, D_i^n)$

(P2.2.) Find the excitation equations $\{T_i = f(LD, Q_i, D_i), i = [0, 1, 2]\}$ of the T flip-flops

(P2.3.) Draw the logic diagram of the circuit that you designed; explain your work.

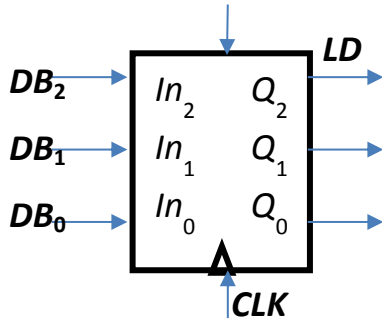


Table 1

LD	Q_i^{n+1} (next state)
0	Q_i^n (present state)
1	DB_i^n (data input)

(P2.1.)

$$Q_i^{n+1} = LD' Q_i^n + LD D_i^n$$

$$i = \{0, 1, 2\}$$

Table 2.

LD	Q_i^n	DB_i^n	Q_i^{n+1} P2.1	T_i P2.2
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	0	1
1	1	1	1	0

For (P2.2) Use the T FF's excitation table:

Q^n	Q^{n+1}	T^n
0	0	0
0	1	1
1	0	1
1	1	0

...
 or excitation equation:

$$T = \overline{Q^n} \cdot Q^{n+1} + Q^n \cdot \overline{Q^{n+1}}$$


$$T = Q^n \oplus Q^{n+1}$$

Then from Table 2:

$$T_i = LD \cdot \overline{Q_i} \cdot DB_i + LD \cdot Q_i \cdot \overline{DB_i}$$

$$T_i = LD \cdot (Q_i \oplus DB_i), i = \{0, 1, 2\}$$

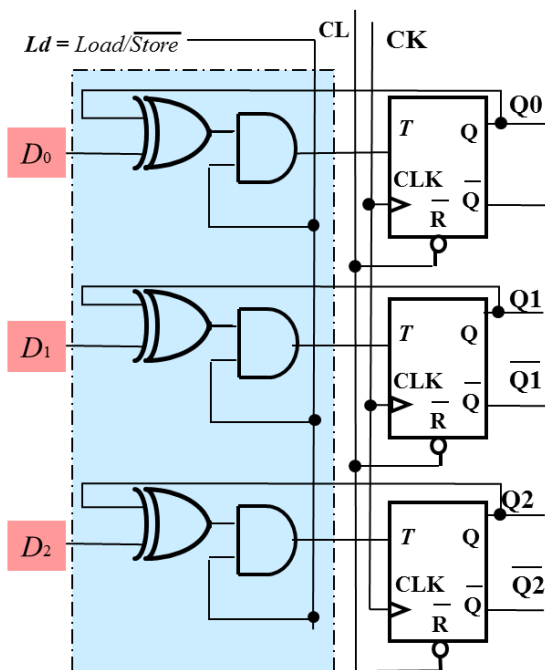The circuit can be implemented with gates only or using a 2-input multiplexor controlled by LD



OR

