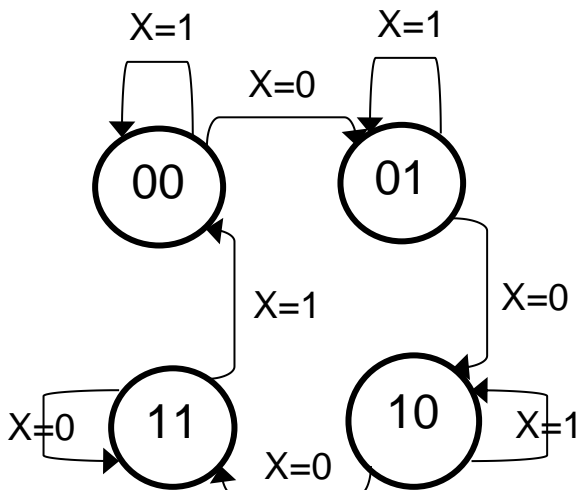


- P1. The next figure shows the state diagram of a logic circuit which has a unique one-bit external input  $x$ .
- [12 points] Start off by deriving the state table of the circuit. Then, assuming that JK flip-flops are to be used in the implementation, extend the state table with the excitation table of the circuit.
  - [12 points] Find simplified expressions for each flip-flop inputs.



$A^n$	$B^n$	$X$	$A^{n+1}$	$B^{n+1}$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	x	1	x
0	0	1	0	0	0	x	0	x
0	1	0	1	0	1	x	x	1
0	1	1	0	1	0	x	x	0
1	0	0	1	1	x	0	1	x
1	0	1	1	0	x	0	0	x
1	1	0	1	1	x	0	x	0
1	1	1	0	0	x	1	x	1

**SOLUTION**

Recall:

... or B) The JK FF Excitation Table

A) The "copy & paste recipe:"

- = next state if present state is 0
- J = don't care if present state is 1
- K = don't care if present state is 0
- K = complement of the next state if present state is

i.e.:

	if $Q^n = 0$	if $Q^n = 1$
J =	1. $Q^{n+1}$	2. x
K =	3. x	4. $(Q^{n+1})'$

$Q^n$	$Q^{n+1}$	$J^n$	$K^n$
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

2.

$J_A$	BX	00	01	11	10
0	0	0	1	3	2
0	1	0	0	0	1
1	0	4	5	7	6
1	1	x	x	x	x

$J_A = B X'$

$K_A$	BX	00	01	11	10
0	0	0	1	3	2
0	1	x	x	x	x
1	0	4	5	7	6
1	1	0	0	1	0

$K_A = BX$

$J_B$	BX	00	01	11	10
0	0	0	1	3	2
0	1	1	0	x	x
1	0	4	5	7	6
1	1	1	0	x	x

$J_B = X'$

$K_B$	BX	00	01	11	10
0	0	0	1	3	2
0	1	x	x	0	1
1	0	4	5	7	6
1	1	x	x	1	0

$K_B = (A \text{ xor } X)'$   
 $= A'X' + AX$

P2. [14 points] A sequential circuit has 3 data inputs  $DB_2, DB_1$  and  $DB_0$  and a control input “LD” (load data). The operation of the sequential circuit is described in the functional Table 1. Design the sequential circuit using three T flip-flops.

(P2.1.) Provide the next state functions of the T flip-flops  $\{Q_i^{n+1}, i = [0, 1, 2]\}$ , either by filling out column  $Q_i^{n+1}$  of Table 2, or by writing directly its logic expression  $Q_i^{n+1} = \delta(LD, Q_i^n, D_i^n)$

(P2.2.) Find the excitation equations  $\{T_i = f(LD, Q_i, D_i), i = [0, 1, 2]\}$  of the T flip-flops

(P2.3.) Draw the logic diagram of the circuit that you designed; explain your work.

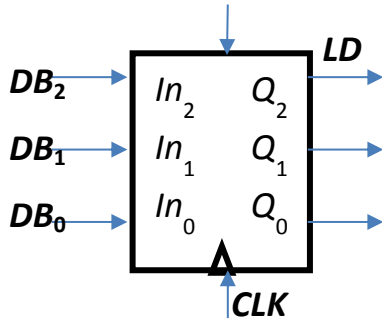


Table 1

LD	$Q_i^{n+1}$ (next state)
0	$DB_i^n$ (data input)
1	$Q_i^n$ (present state)

(P2.1.)  
 $Q_i^{n+1} = LD Q_i^n + LD' DB_i^n$   
 $i = \{0, 1, 2\}$

Table 2.

LD	$Q_i^n$	$DB_i^n$	$Q_i^{n+1}$ P2.1	$T_i$ P2.2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

For (P2.2) Use the T FF's excitation table to fill in  $T_i$  of

Table2:

$Q^n$	$Q^{n+1}$	$T^n$
0	0	0
0	1	1
1	0	1
1	1	0

...  
 or excitation equation:

$$T = \overline{Q^n} \cdot Q^{n+1} + Q^n \cdot \overline{Q^{n+1}}$$


$$T = Q^n \oplus Q^{n+1}$$

Then from Table 2:

$$T_i = LD \cdot \overline{Q_i} \cdot DB_i + LD \cdot Q_i \cdot \overline{DB_i}$$

$$T_i = LD \cdot (Q_i \oplus DB_i), i = \{0, 1, 2\}$$

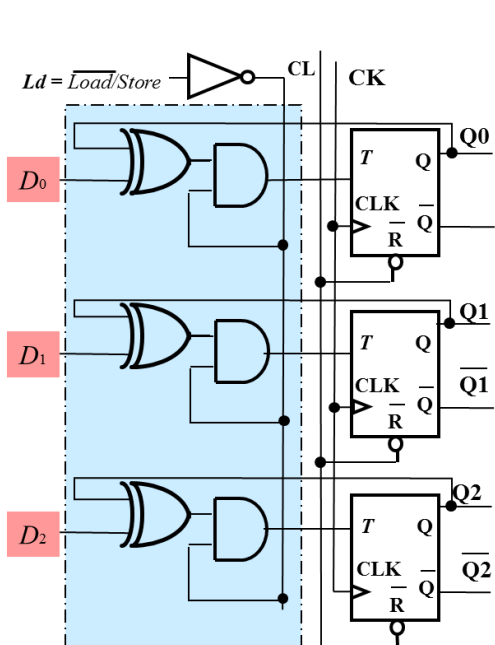(P2.3.) The circuit can be implemented with gates only or using a 2-input multiplexor controlled by LD



OR

