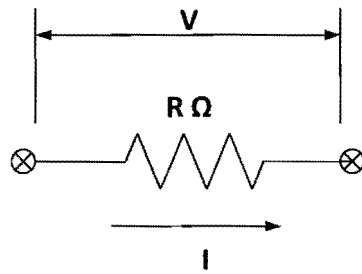


1. <8 Marks>




(a) Complete the following table.

V volts	I amps	R ohms	P watts
100	10	10	1000
60	20	3	1200
50	10	5	500
200	10	20	2000
75	2	37.5	150
50	10	5	500

$\frac{1}{2}$ MARK EACH

(b)

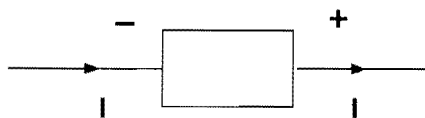


This component is: (Check one)

Consuming Power?


Supplying Power? ①

(c)

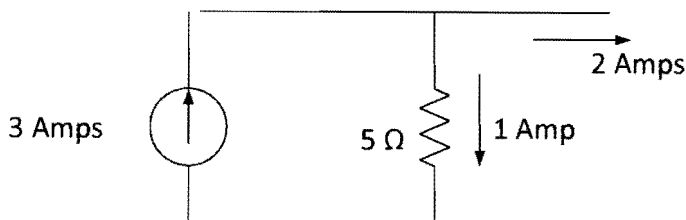

The constant current source is supplying? 15 watts ①

2. <12 Marks>

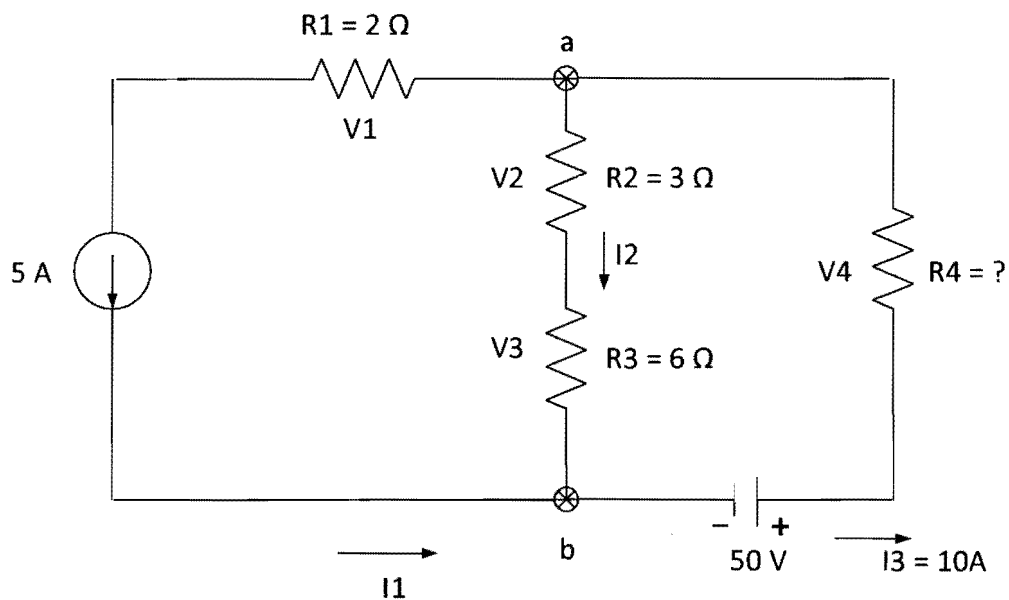

For the above circuit:

- Apply KCL to determine I_2
- Apply Ohms Law to determine V_{ab}
- Determine the value of R_4
- Determine the total power loss in all resistors
- Determine the power supplied / consumed by
 - The 50 volt battery
 - The constant current element.

(a) At node "b" $I_1 + I_2 - I_3 = 0$
 $5A + I_2 - 10 = 0$
 $\therefore \underline{I_2 = 5A}$ (2)

(b) $V_{ab} = V_2 + V_3 = I_2 (R_2 + R_3)$
 $= 5(3 + 6) = \underline{45V} = V_{ab}$ (2)

(c) $V_{R4} = +45 - 50 = -5V$
 $I_3 = 10A$
 $R = \frac{V}{I} = \frac{5}{10} = \underline{\underline{\frac{1}{2} \Omega}}$ (3)

(d)

$$R_1: 5^2 \times 2 = 50 \text{ W}$$

$$R_2: 5^2 \times 3 = 75 \text{ W}$$


$$R_3: 5^2 \times 6 = 150 \text{ W}$$

$$R_4: 10^2 \times \frac{1}{2} = 50 \text{ W}$$

$$\sum = \underline{\underline{325 \text{ W}}} \quad (2)$$

(e) 1) 50V BATTERY: $50 \times 10 = 500 \text{ W}$ (1)

2) CONSTANT CURRENT SOURCE

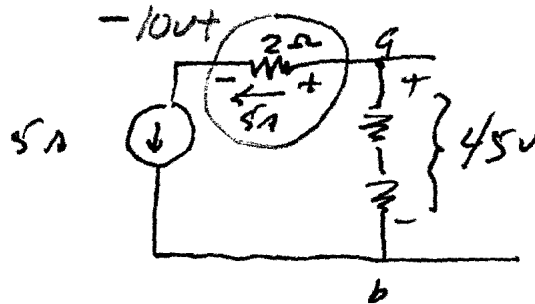

\therefore VOLTAGE ACROSS
5A SOURCE
 $-10 + 45 = 35 \text{ V}$


\therefore Power = $5 \times 35 = \underline{\underline{175 \text{ W}}} \quad (2)$

CHECK

$500 - 175 = 325 \text{ W} = \text{Power consumed by resistors.}$

TOTAL 12 MARKS

3. <10 Marks>

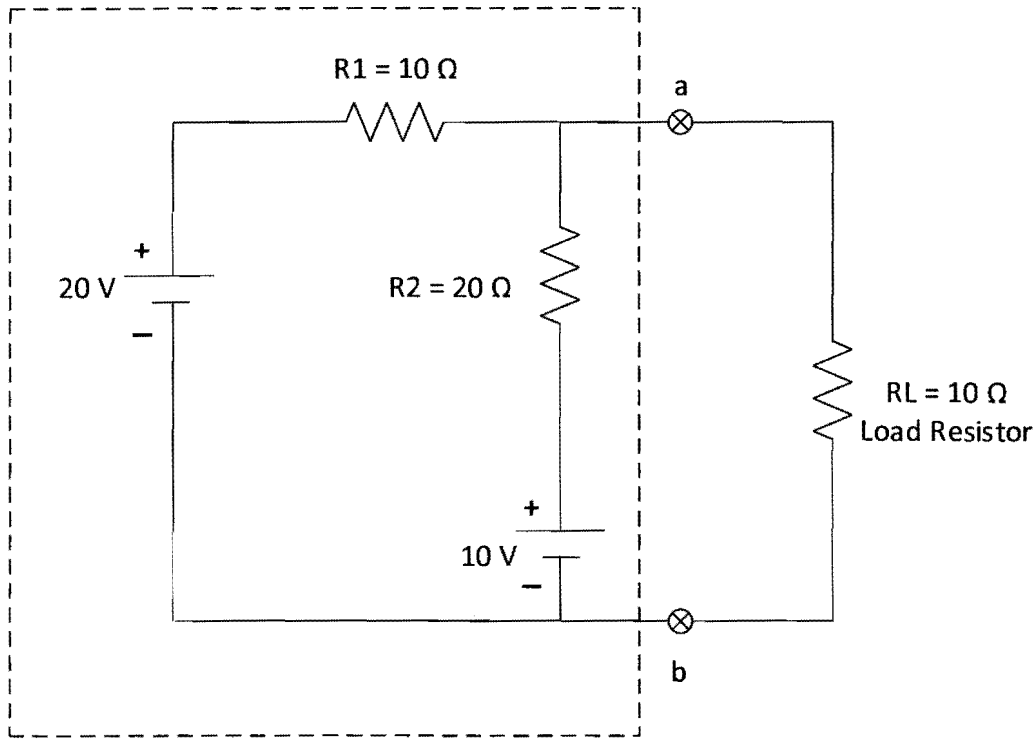

- Determine V_t and R_t , and draw the Thevenin equivalent for the circuit driving the load resistor R_L
- Convert a) to a Norton equivalent circuit
- Determine the power delivered to the load resistor R_L
- What value of R_L would result in maximum power dissipated in the load?
- Calculate the power for this new value of R_L .

(e) $V_t = V_{oc}$


$$I = \frac{(20 - 10)}{20 + 10} = \frac{10}{30}$$

$$\therefore V_{oc} = \frac{10}{30} \times 20 + 10 = \underline{\underline{16.667\text{V}}} \quad \textcircled{2}$$

R_{th}

$$R_{eq} = R_{th} = \frac{20 \times 10}{20 + 10} = \underline{\underline{6.667\ \Omega}} \quad \textcircled{1}$$


THEVENIN EQUIVALENT CIR.

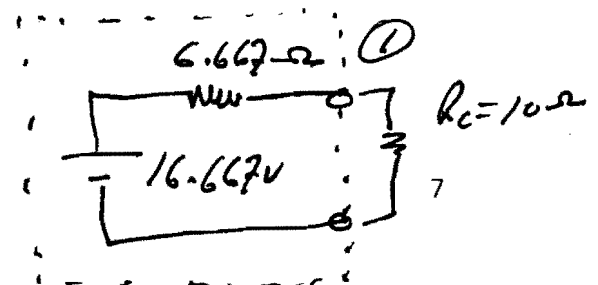

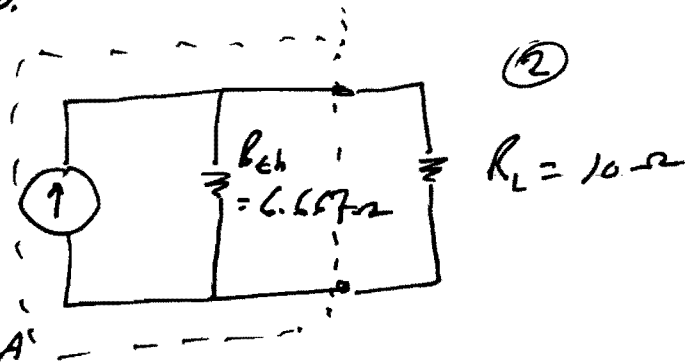(b) Norton.

$$I_N = \frac{V_{th}}{R_{th}}$$

$$= \frac{16.667}{6.667} = \underline{\underline{2.5 A}}$$



$$(c) P_L = I^2 R = \left(\frac{16.667}{6.667 + 10} \right)^2 \times 10 = \underline{\underline{10 \text{ W}}} \text{ (2)}$$

(d) For max power $R_L = R_{th}$

$$\therefore R_L = \underline{\underline{6.667 \Omega}} \text{ (1)}$$

$$(e) P_{max} = \left(\frac{16.667}{6.667 + 6.667} \right)^2 \times 6.667 = \underline{\underline{10.417 \text{ W}}} \text{ (1)}$$

TOTAL 10 MARKS