


Module 3

Methods of Analysis of Resistive Circuits

Chapter 4 of Dorf and Svoboda's
book


Analysis of general resistive circuits

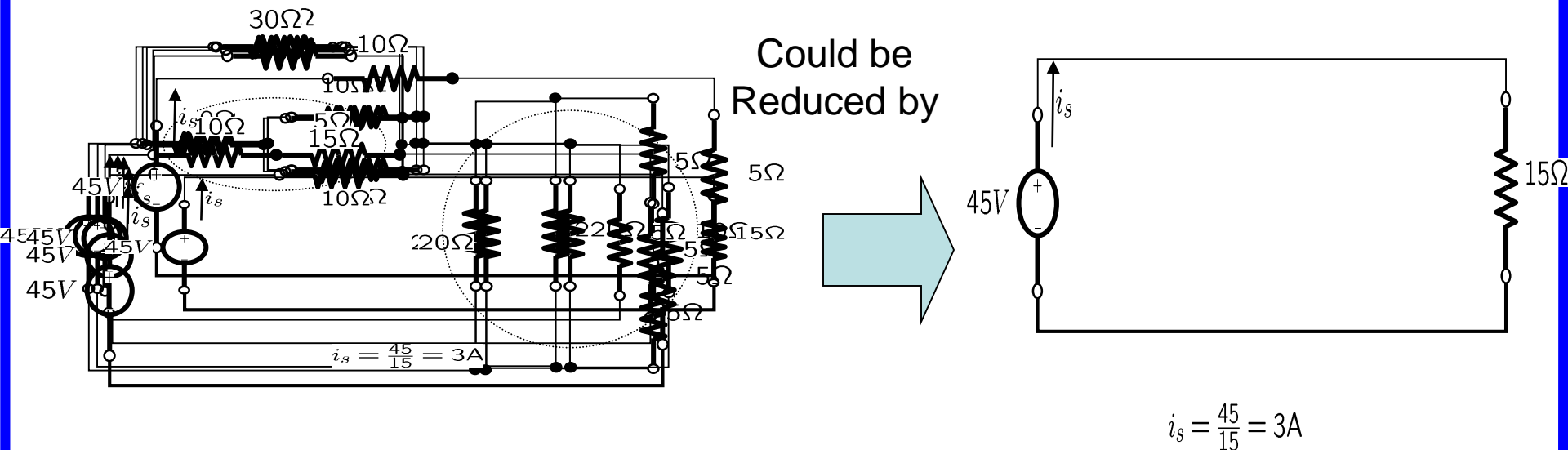In the examples we had seen so far, we were able to do our circuit analysis ONLY by simplifying the circuit, using the notion of parallel and series resistors. For example,




Not all the circuits can be treated likewise. See the following circuit as an example

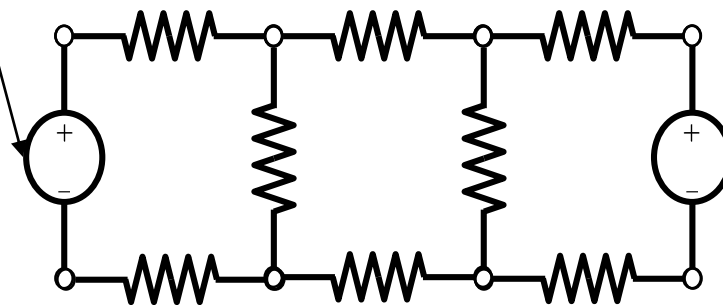This circuit does not have any two or more parallel or series resistors. Therefore, it does not allow any further simplification.



What we need for analysis is

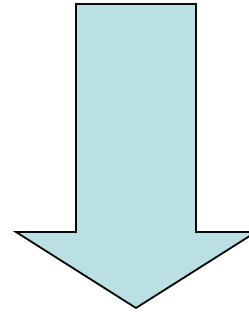

Systematic procedure to analyze general resistive circuits

In this module we will study two main approaches

**Node Voltage Analysis
Method**

**Mesh Current Analysis
Method**

Our plan in this module

4

(3)1/4

2

1

Node Voltage Analysis Method

Mesh Current Analysis Method

Systematic Analysis Steps for circuits

Systematic Analysis Steps for circuits

Independent Current Sources

Independent Current + Voltage Sources

Dependent Current + Voltage Sources

→→→→ Examples

Independent Voltage Sources

Independent Current + Voltage Sources

Dependent Current + Voltage Sources

→→→→ Examples

3

Comparison between the two methods

→ Which method would it be easier to use if we are given some circuit

Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express current in the circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

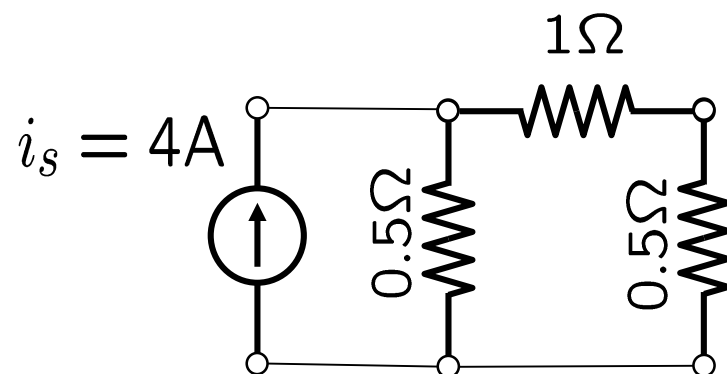We are going to use this Circuit as an example to illustrate the steps



Direct
Substitution

Matrix
Algebra

Node Voltage Analysis Method


Circuits with independent Current Sources - **Step (1/6)**

Identify the number
of nodes in the circuit

Easy

Assume the number of nodes is n

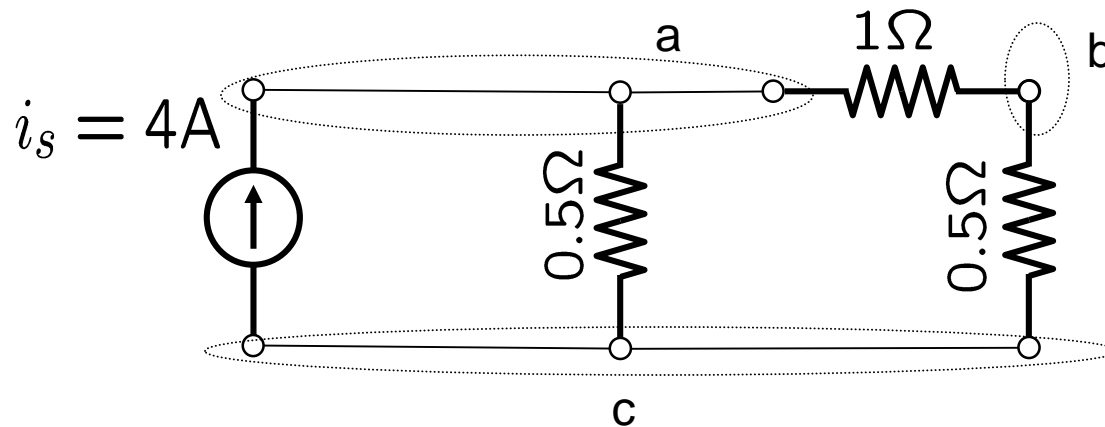In the example circuit we have 3 nodes. a, b and c.



Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express current in the circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

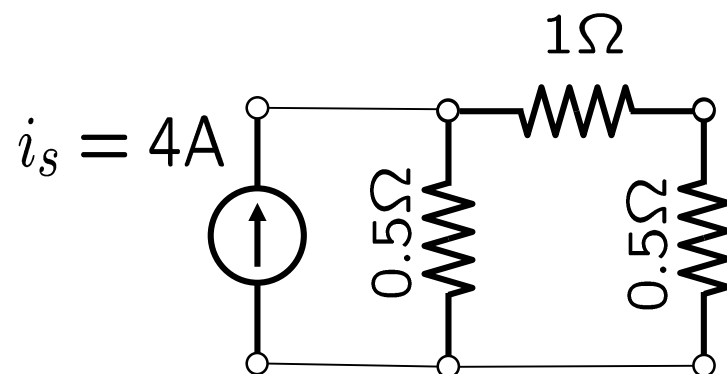We are going to use this Circuit as an example to illustrate the steps



Direct
Substitution

Matrix
Algebra

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

Step 2


Designate one node
as a reference node

What is the reference node?!

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

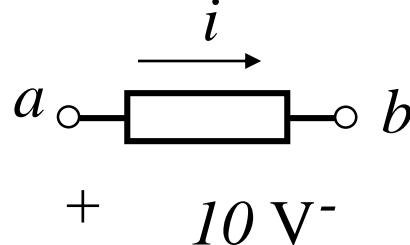

In case of a single element which has a voltage difference of 10 volts between its terminals as shown above, we can choose either point as a reference point. So if we choose point “**a**” as a reference point we indicate that by connecting it to the ground symbol.




Node Voltage Analysis Method


Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

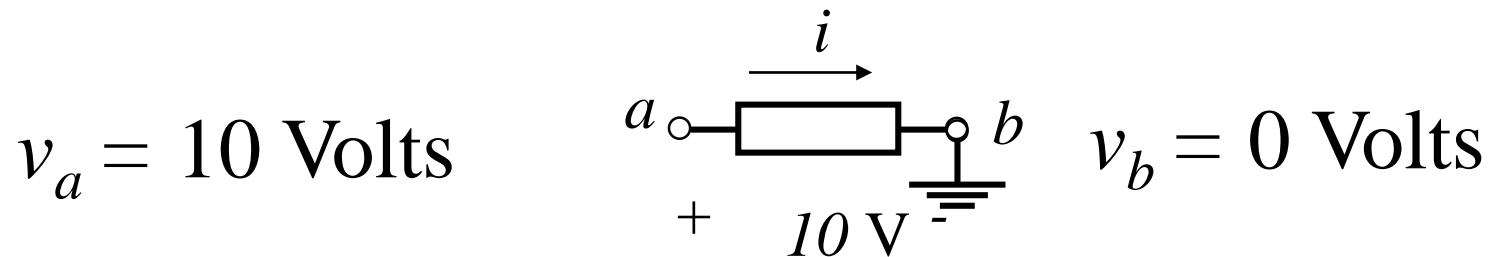If point b is chosen a reference node, then one can say that node a has an absolute voltage of 10 volts when referred to point b .



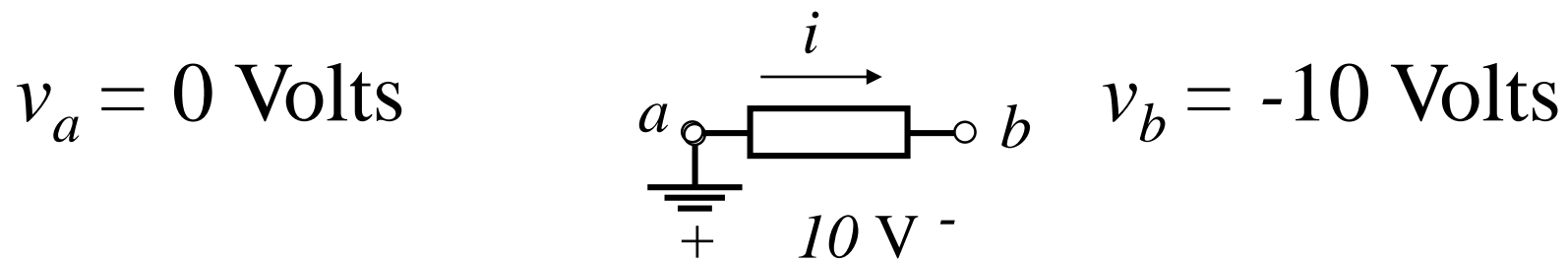If point a is chosen a reference node, then one can say that node b has an absolute voltage of -10 volts when referred to point a .



Node Voltage Analysis Method


Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

A reference node is: A node to which every other node voltage is referred to it.

An Example

For the circuit shown →→→

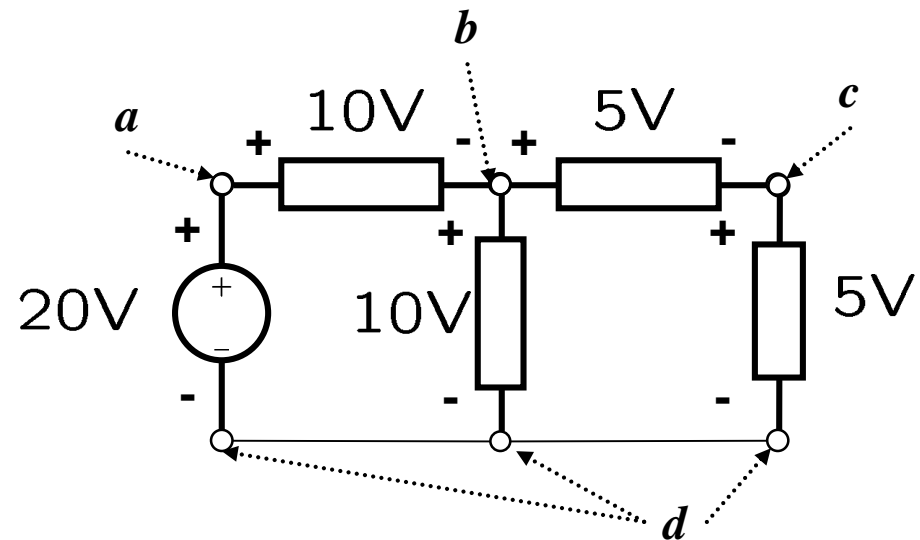

Find all the node voltages assuming that one node is a reference.


Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

Solution:

1. Assuming node d is the reference

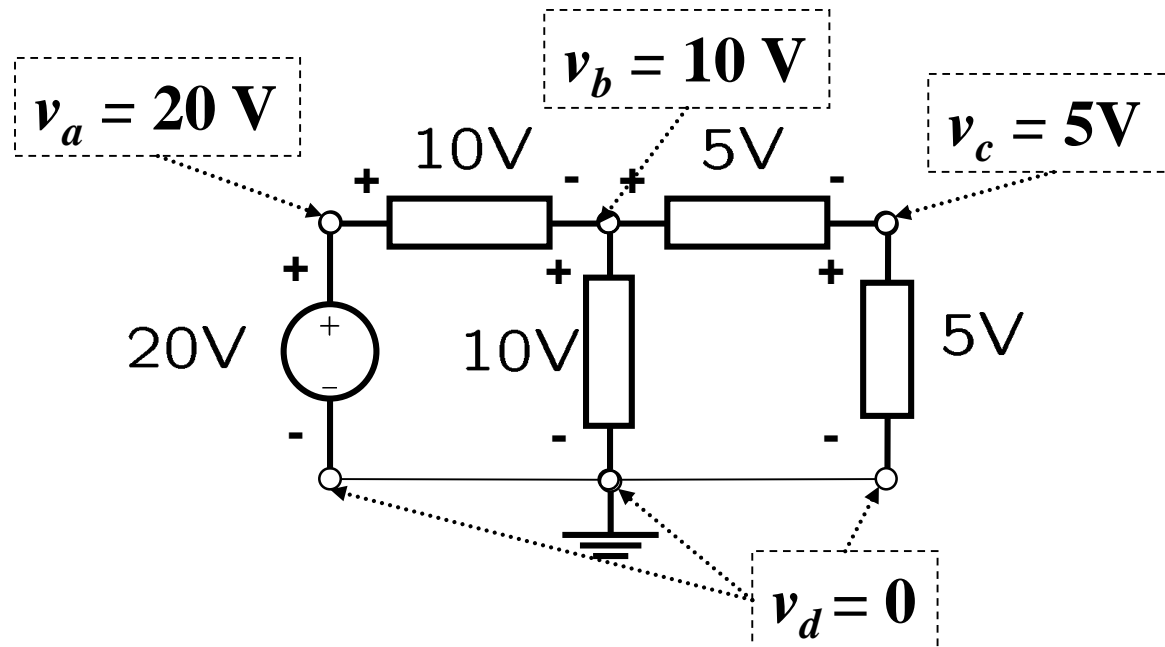


Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

Solution:

2. Assuming node c is the reference

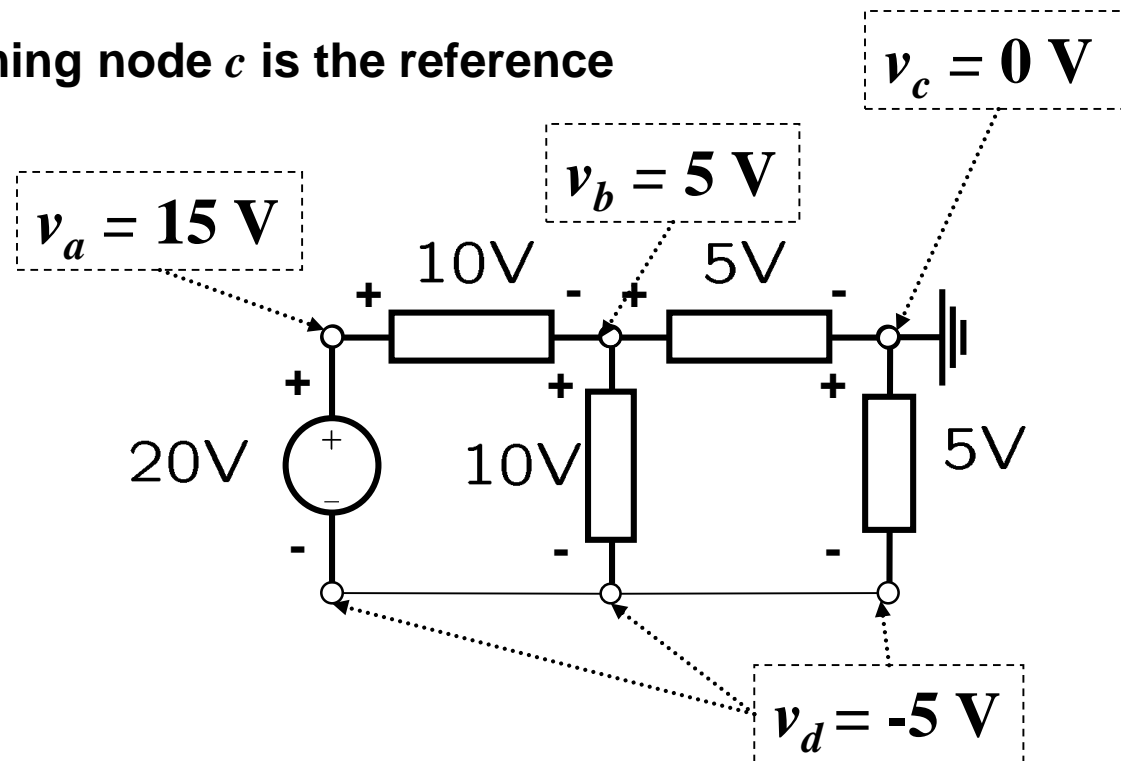


Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

Solution:

3. Assuming node *b* is the reference

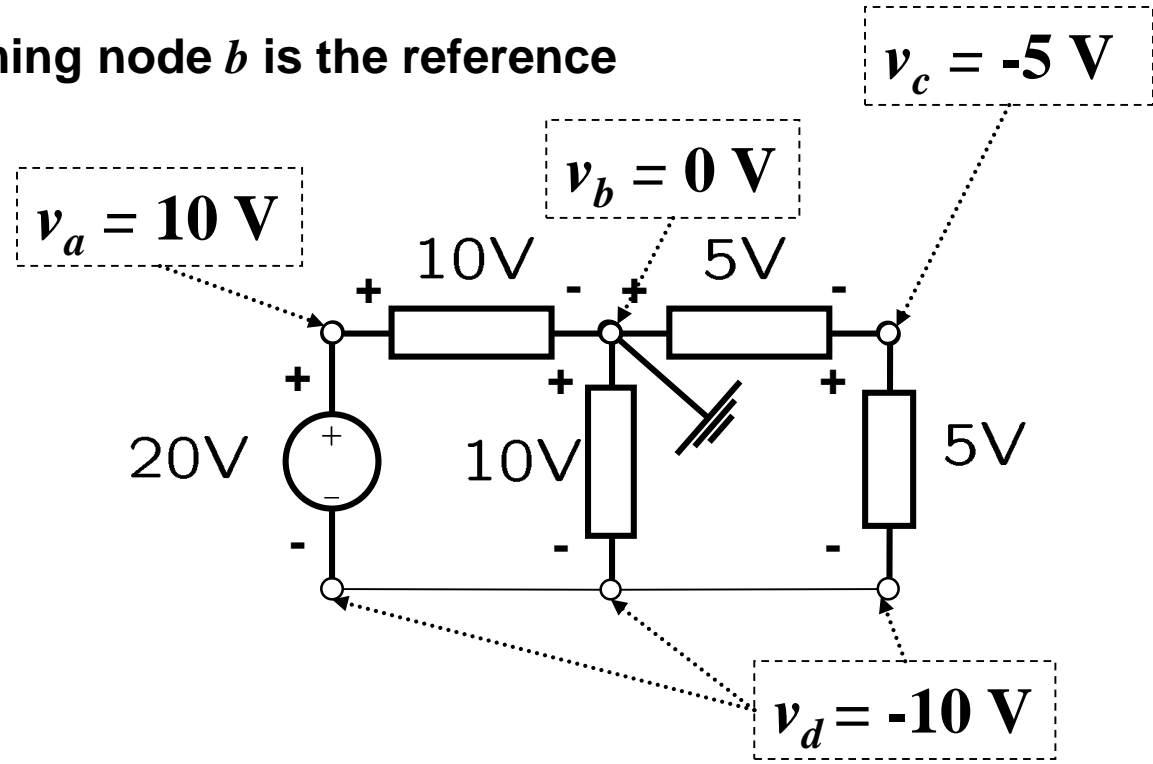

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (2/6)**

What is the reference node?!

A good practice is to use the reference node in the negative terminal of the independent voltage source or the ingoing terminal of the independent current source. This makes analyzing circuits more convenient.

Sometimes, the problem is given where a reference node has been indicated on the circuit schematic. In this case, we will have to use the reference node as indicated.

Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express unknown currents in circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

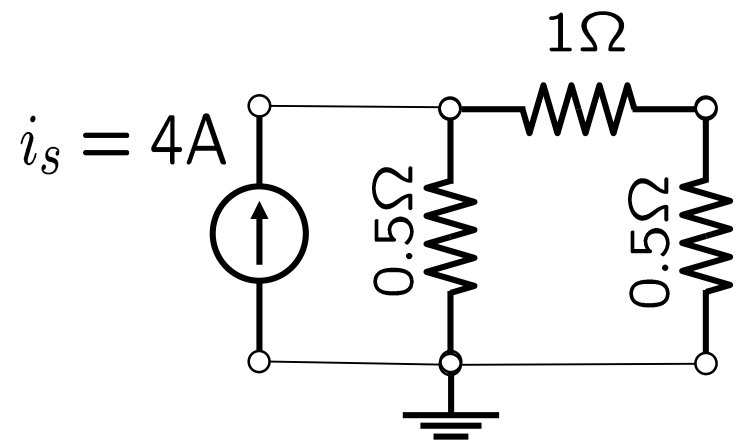We are going to use this Circuit as an example to illustrate the steps



Direct
Substitution

Matrix
Algebra

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (3/6)**Step 3

Express unknown currents in circuit elements in terms of node voltages

Unknown Currents

 $i_1 \ i_2 \ i_3$


Node Voltages

 $v_a \ v_b \ v_c$

$$i_1 = \frac{v_a - v_b}{1}$$

$$i_2 = \frac{v_a - v_c}{0.5} = \frac{v_a}{0.5}$$
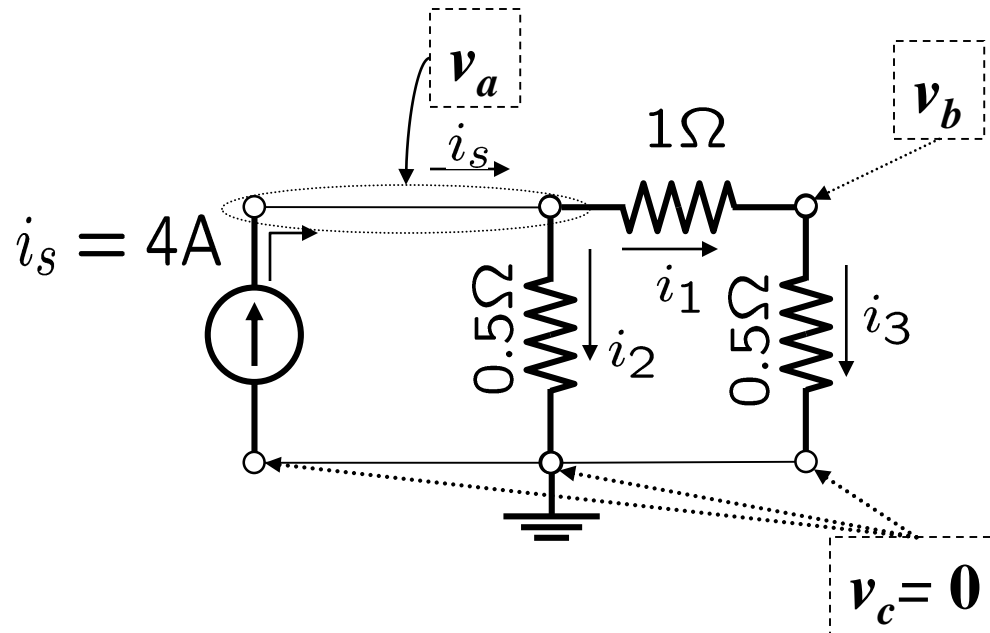
$$i_3 = \frac{v_b - v_c}{0.5} = \frac{v_b}{0.5}$$



Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express unknown currents in circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

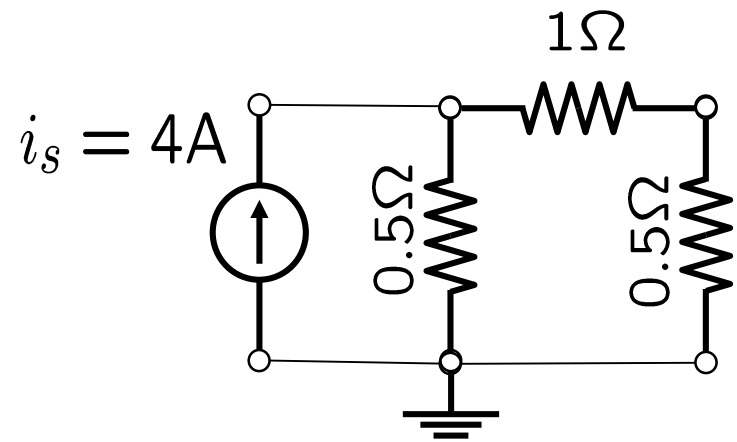We are going to use this Circuit as an example to illustrate the steps



Direct
Substitution

Matrix
Algebra

Node Voltage Analysis Method


Circuits with independent Current Sources - **Step (4/6)****Step 4**

Apply KCL Law at each node except the reference node


KCL at node a

Σ Currents entering a =

Σ Currents exiting from a

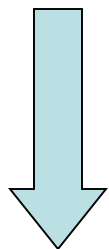

$$i_s = i_1 + i_2$$

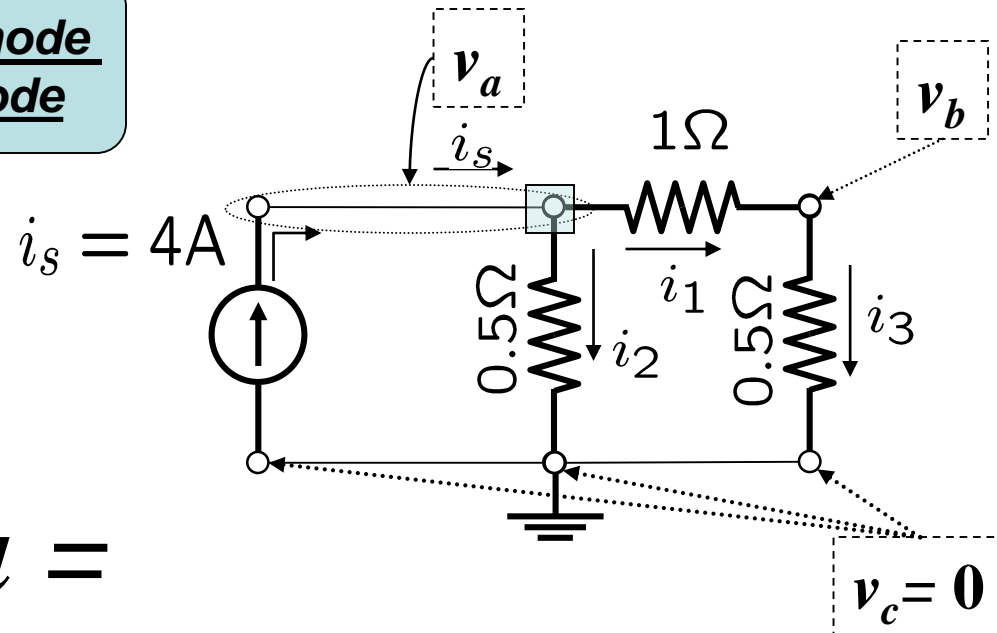


Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (4/6)****Step 4**

Apply KCL Law at each node except the reference node


KCL at node a

$$\Sigma \text{ Currents entering } b =$$
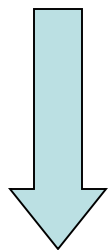
$$\Sigma \text{ Currents exiting from } b$$


$$i_1$$

$$=$$
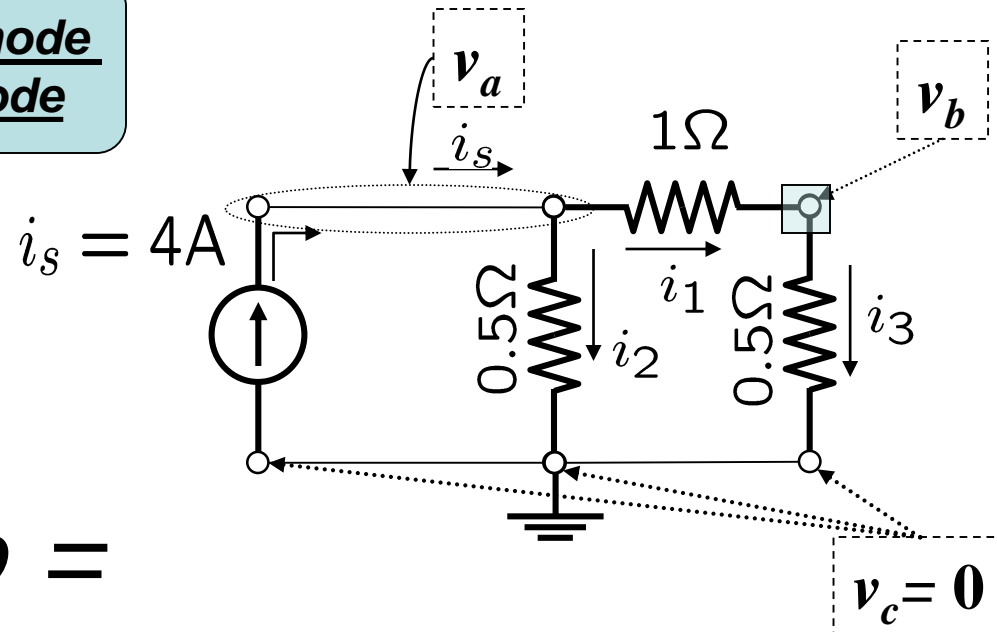
$$i_3$$


Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express unknown currents in circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

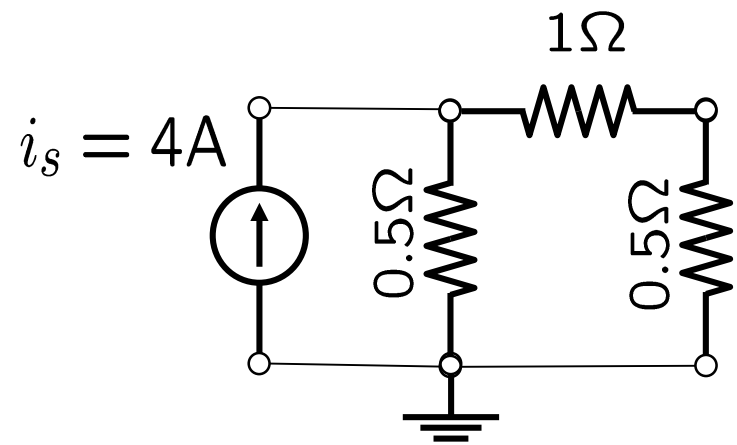We are going to use this Circuit as an example to illustrate the steps



Direct
Substitution

Matrix
Algebra

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (5/6)****Step 5**

Solve the equations resulting from KCL to get node voltages

Direct Substitution

$$i_s = i_1 + i_2$$

$$i_1 = i_3$$

$$4 = \frac{v_a - v_b}{1} + \frac{v_a}{0.5}$$

$$\frac{v_a - v_b}{1} = \frac{v_b}{0.5}$$

$$4 = 3v_a - v_b$$

$$v_a = 3v_b$$

From **Step 3, we have**

$$i_1 = \frac{v_a - v_b}{1}$$

$$i_2 = \frac{v_a - v_c}{0.5} = \frac{v_a}{0.5}$$

$$i_3 = \frac{v_b - v_c}{0.5} = \frac{v_b}{0.5}$$

$$i_s = 4A$$

Node Voltage Analysis Method

Circuits with independent Current Sources - **Step (5/6)****Step 5**

Solve the equations resulting from KCL to get node voltages

Direct Substitution

$$\begin{aligned} 4 &= 3v_a - v_b \\ v_a &= 3v_b \end{aligned}$$

$$4 = 3 \times 3v_b - v_b$$

$$v_b = \frac{1}{2} \text{ V} \quad \longrightarrow \quad v_a = \frac{3}{2} \text{ V}$$

Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express unknown currents in circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node


Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages
Find the currents in the elements

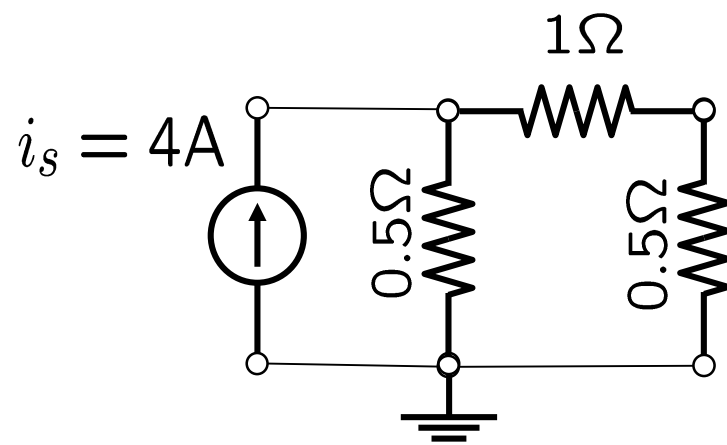We are going to use this Circuit as an example to illustrate the steps



Direct Substitution

Matrix Algebra

Node Voltage Analysis Method


Circuits with independent Current Sources - **Step (6/6)**

Step 6

Using the node voltages
Find the currents in the elements

From Step 3, we have
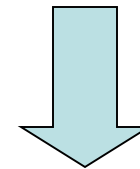
$$\begin{aligned}i_1 &= \frac{v_a - v_b}{1} \\i_2 &= \frac{v_a - v_c}{0.5} = \frac{v_a}{0.5} \\i_3 &= \frac{v_b - v_c}{0.5} = \frac{v_b}{0.5}\end{aligned}$$




$$\begin{aligned}i_1 &= 1\text{A} \\i_2 &= 3\text{A} \\i_3 &= 1\text{A}\end{aligned}$$

From Step 5, we have

$$\begin{aligned}v_a &= \frac{3}{2}\text{V} \\v_b &= \frac{1}{2}\text{V}\end{aligned}$$

Checking your answer

You can also

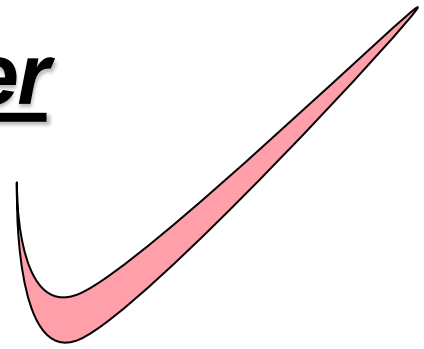

VERIFY

Your solution!!!

How to verify your solution??

The solution has to satisfy:




KCL at every node

KVL for every loop

How to verify your solution??

$$\begin{aligned} v_a &= \frac{3}{2} \text{V} \\ v_b &= \frac{1}{2} \text{V} \\ i_1 &= 1 \text{A} \\ i_2 &= 3 \text{A} \\ i_3 &= 1 \text{A} \end{aligned}$$

Solution of the previous example

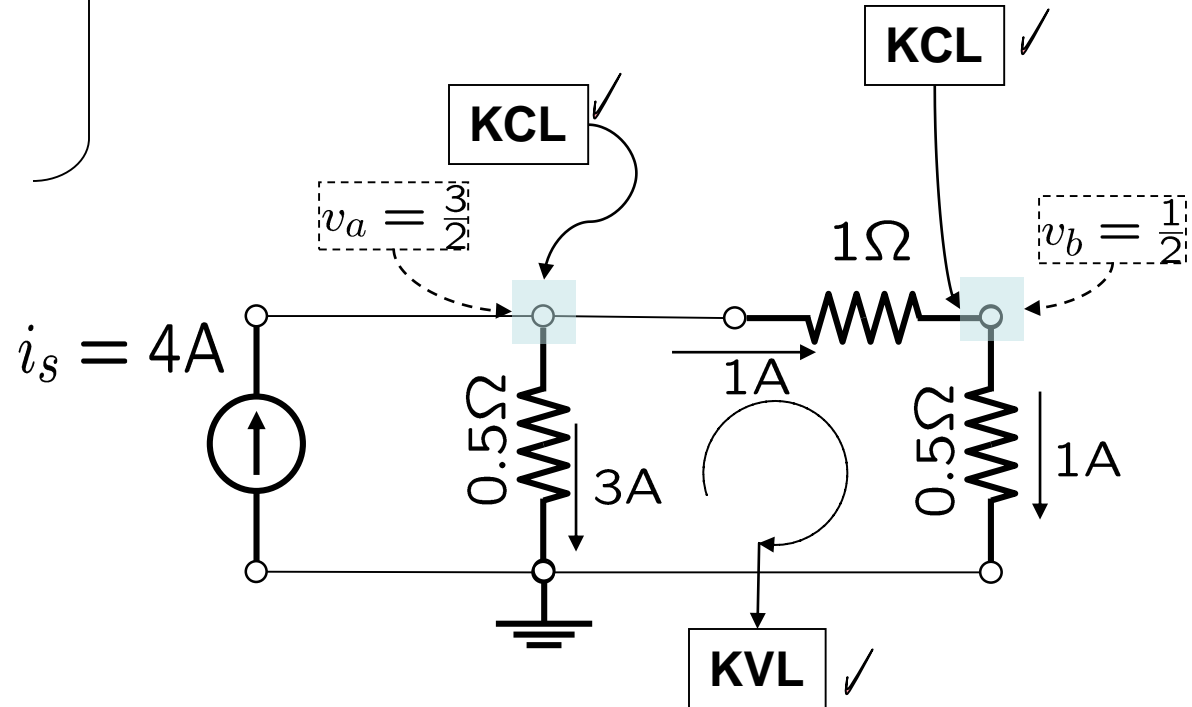

Node Voltage Analysis Method

**WHY and HOW
does it
work ??**

Node Voltage Analysis Method

WHY and HOW?

The basic strategy


Consider node voltages as unknowns except for the reference node

To solve for a number of unknowns we need the same number of equations

Generate the required equations by applying KCL at each node


Solve the resulting equations to obtain the unknown nodes voltages

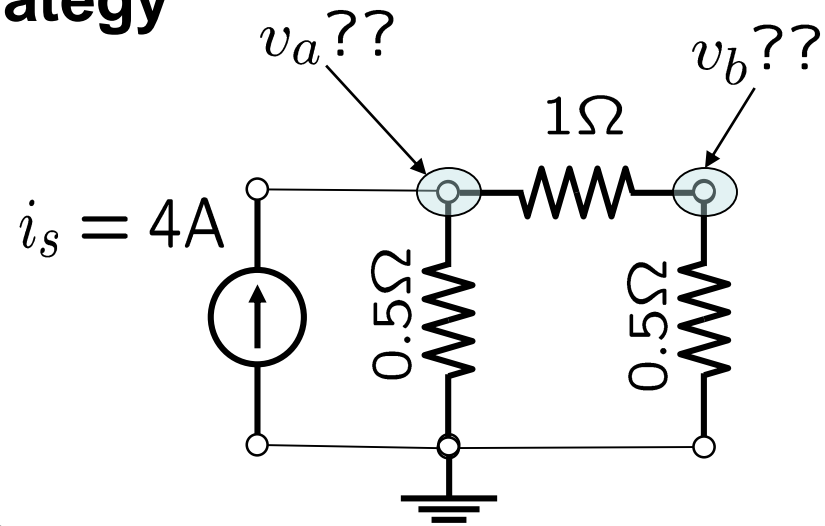Using Calculated Nodes voltages, calculate the currents



Another Example

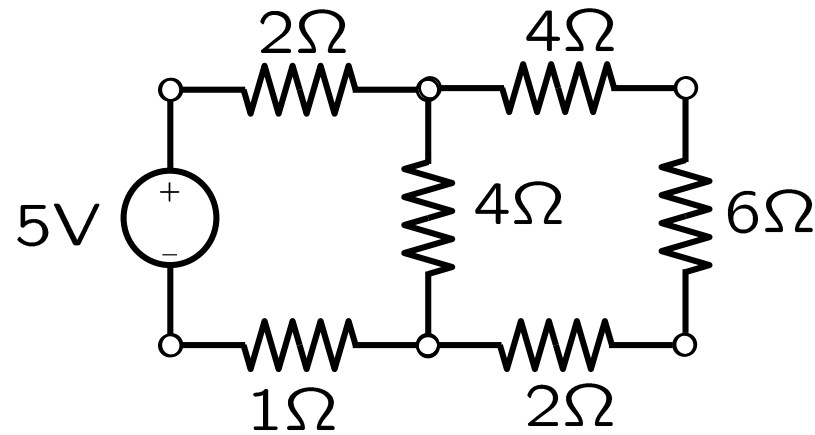Use the node voltage method to calculate all voltages and currents in the circuit shown below.



Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit



Step 2

Designate one node as a reference node

Step 3

Express current in the circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node

Step 5

Solve the equations resulting from KCL to get node voltages

Direct Substitution

Matrix Algebra

Step 6


Using the node voltages
Find the currents in the elements

Node Voltage Analysis Method

Step (1/6)

Step 1

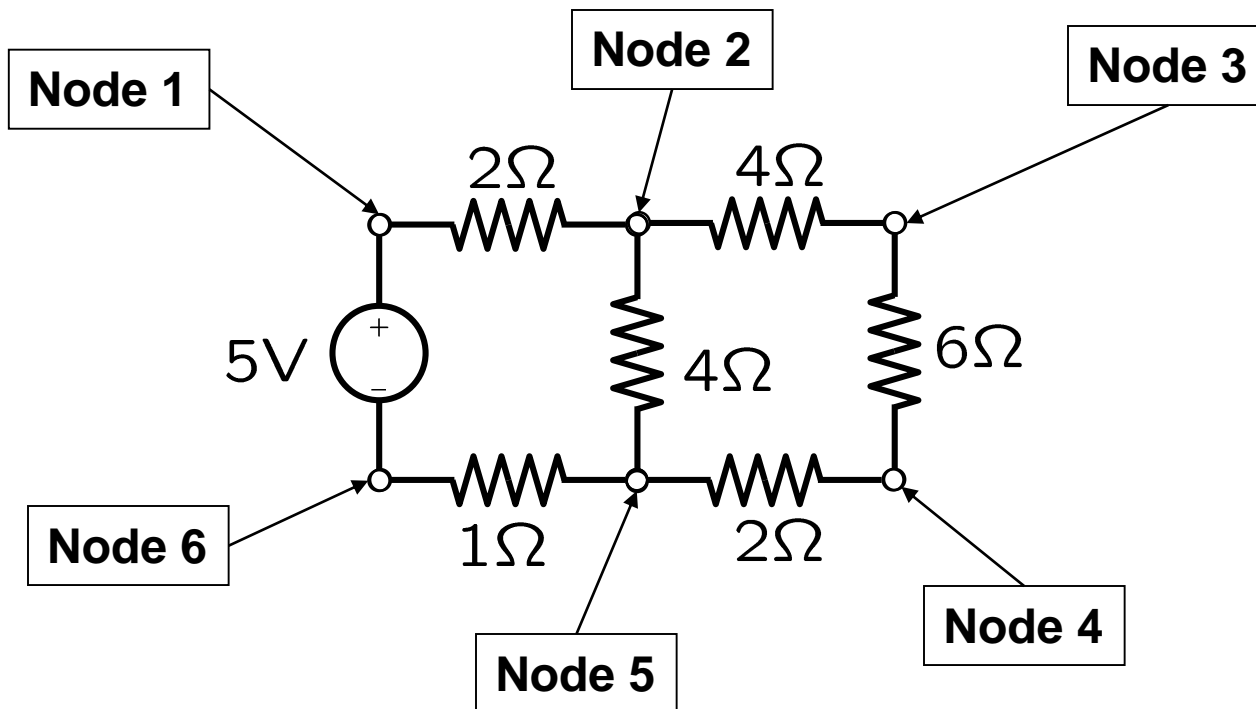Identify the number of nodes in the circuit



Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node



Step 3

Express current in the circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node

Step 5

Solve the equations resulting from KCL to get node voltages

Direct Substitution

Matrix Algebra

Step 6


Using the node voltages
Find the currents in the elements

Node Voltage Analysis Method

Step (2/6)

Step 2

Designate one node as a reference node

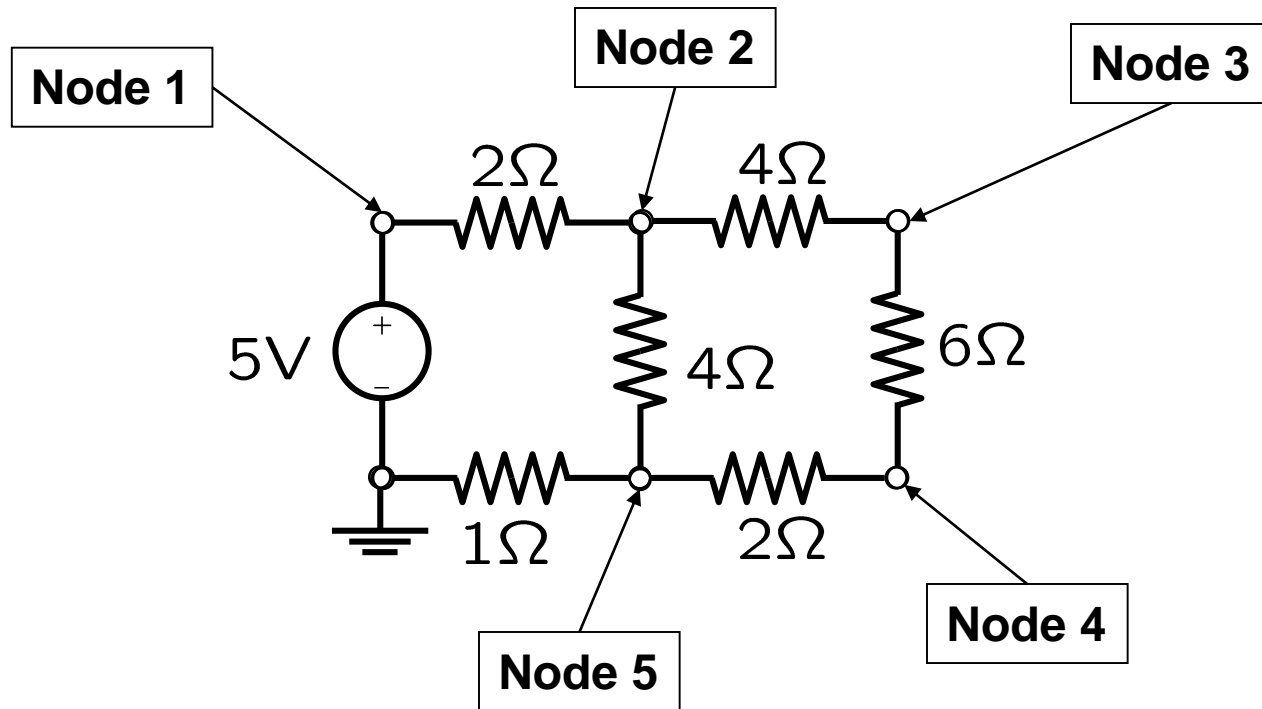

Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express current in the circuit elements in terms of node voltages



Step 4

Apply KCL Law at each node except the reference node

Step 5

Solve the equations resulting from KCL to get node voltages

Direct Substitution

Matrix Algebra

Step 6


Using the node voltages
Find the currents in the elements

Node Voltage Analysis Method

Step (3/6)

Step 3

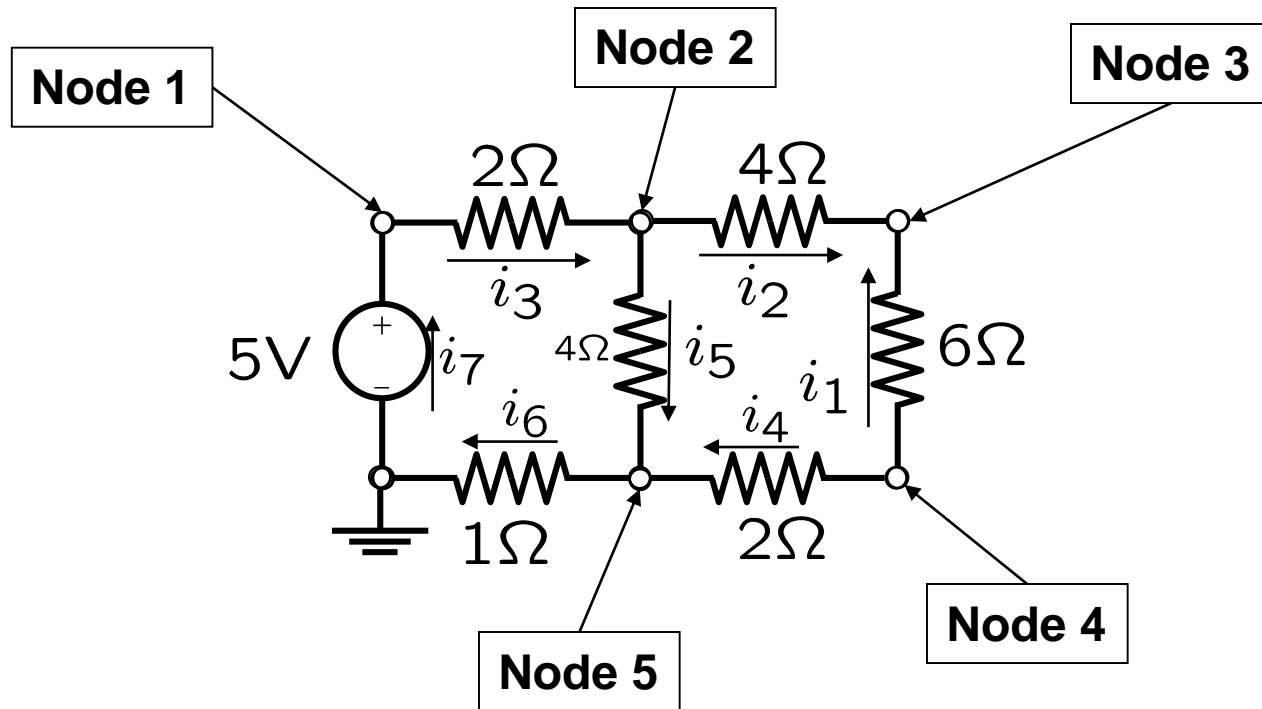Express current in the circuit elements in terms of node voltages



Node Voltage Analysis Method

Step (3/6)

Step 3

Express current in the circuit elements in terms of node voltages

$$i_1 = \frac{v_4 - v_3}{6}$$


$$i_2 = \frac{v_2 - v_3}{4}$$

$$i_3 = \frac{v_1 - v_2}{2}$$

$$i_4 = \frac{v_4 - v_5}{2}$$

$$i_5 = \frac{v_2 - v_5}{4}$$

$$i_6 = \frac{v_5 - 0}{1}$$

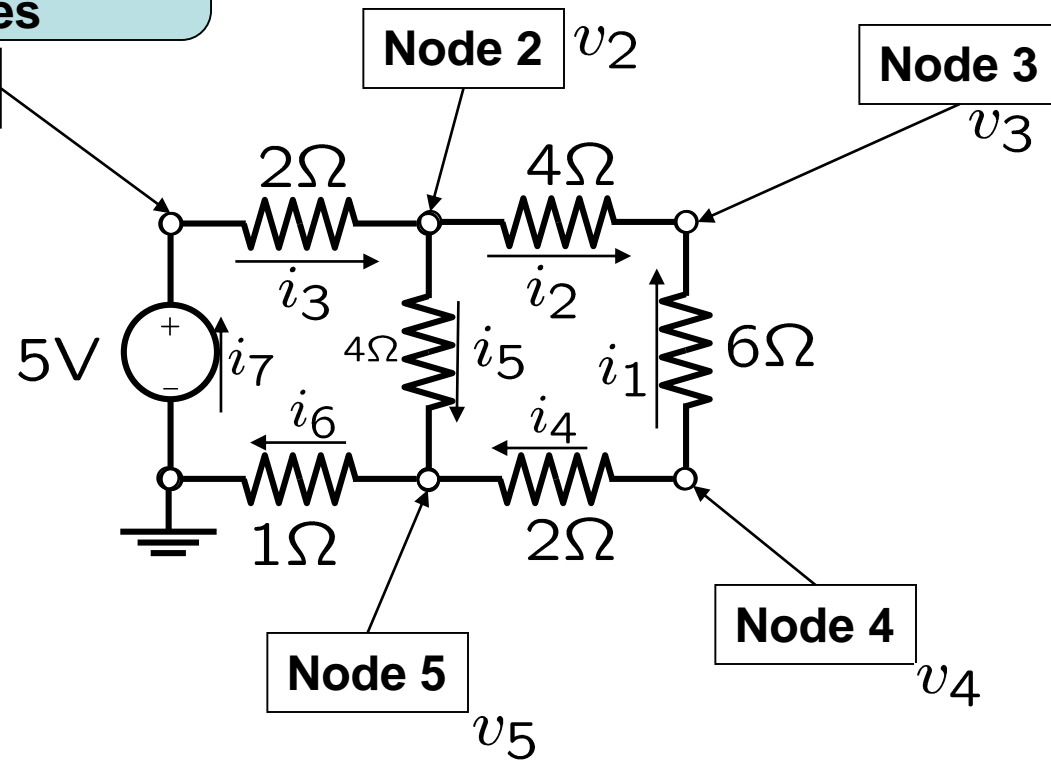

Node Voltage Analysis Method

Step (3/6)

Step 3

Express current in the circuit elements in terms of node voltages


Node 1

v_1


Node 2 v_2

Node 3 v_3

v_3

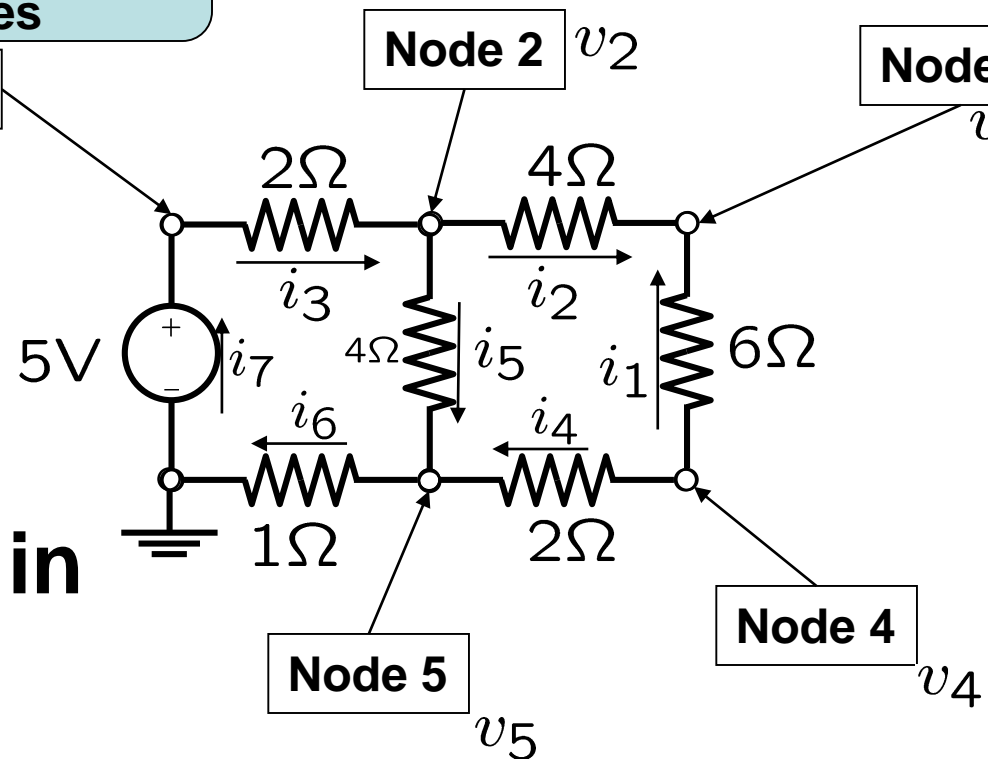

i_7

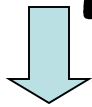

Can not be written in terms of node voltages

Node Voltage Analysis Method

Circuits with independent Current Sources

Step 1

Identify the number of nodes in the circuit

Step 2

Designate one node as a reference node

Step 3

Express current in the circuit elements in terms of node voltages

Step 4

Apply KCL Law at each node except the reference node

Step 5

Solve the equations resulting from KCL to get node voltages

Step 6

Using the node voltages Find the currents in the elements

These steps will

FAIL


if we have
independent
Voltage Source

Direct
Substitution

Matrix
Algebra



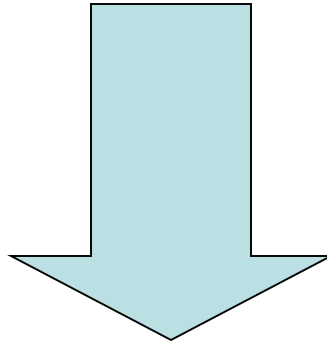Node Voltage Analysis Method
Circuits with independent Current Sources



**Should be modified
to handle
independent
Voltage Source**

Our plan in this module

1

**Node Voltage Analysis
Method**

**Systematic Analysis Steps
for circuits**

**Independent
Current
Sources**

**Independent
Current
+
Independent
Voltage
Sources**

**Dependent
Current
+
Voltage
Sources**

→→→→ Examples

2

**Mesh Current Analysis
Method**

**Systematic Analysis Steps
for circuits**

**Independent
Voltage
Sources**

**Independent
Current
+
Voltage
Sources**

**Dependent
Current
+
Voltage
Sources**

→→→→ Examples

3

Comparison between the two methods

→ Which method would it be easier if we are given some circuit