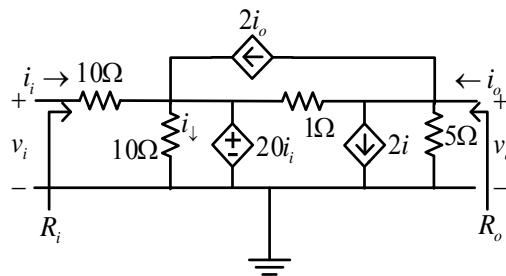


Course	Number		Section
Electronics I	ELEC 311		BB
Examination	Date	Time	# of pages
Final	August 12, 2005	Three hours	3
Instructor			
Dr. R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
Students are allowed to use silent, non-programmable electronic calculators without text display.			
Special Instructions:			
Attempt all questions. Show all steps clearly in neat and legible handwriting. Students are required to return question paper together with exam booklet(s).			

Q.1: For the equivalent circuit below, find the corresponding basic voltage amplifier model, i.e., find (a)  $A_{VO} = v_o/v_i$ , (ii)  $R_i$ , and (iii)  $R_o$ . Now find the corresponding transconductance model equivalent for the same circuit.




Q.2: A zener diode exhibits a constant voltage of 5.6 V for currents greater than five times than the knee current  $I_{ZK}=0.5$  mA. The zener is used to build a shunt regulator fed from a raw DC supply with nominal value of 15 V. The load current varies from 0 mA to 15 mA. Find a suitable value for the resistance R which is connected in series with the raw DC supply. The zener has an internal resistance of 5 ohms. What will be the load regulation of this regulator system?


Q.3: A semiconductor junction diode is used in an automatic gain control system as shown below. The ac resistance of the diode is dependent on the amplitude  $V_p$  of the input signal. Higher  $V_p$  is, lower is the diode ac resistance and more it tends to attenuate the input ac signal. That is how the gain control mechanism works.

The input signal is half-wave rectified to generate a DC voltage which drives the DC current through the diode. This DC voltage is given by  $V_p / \pi$ . The diode is a 1 mA diode. The voltage drop across the diode changes by 100 milli volts for a decade (10 times) change in current through it. You may use the relation:  $V_2 = V_1 + 2.303nV_T \log(I_2 / I_1)$ . The DC resistance of the diode can be neglected.

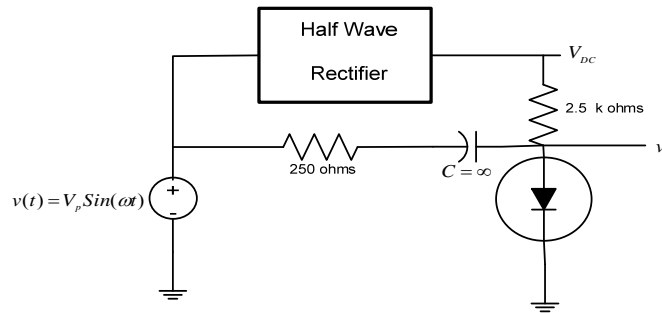
- (a) If the input ac signal has an amplitude of 15 volts, what will be the output signal magnitude  $v_o$ ?
- (b) If the input ac signal amplitude shoots up to 30 volts, how much (approximately) will  $v_o$  become?



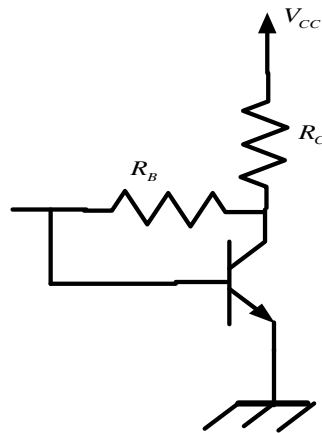Q.4: Design the following BJT circuit to obtain a dc current of 1 mA and to ensure a  $\pm 2 \text{ V}$  signal swing at the collector; that is design for  $V_{CE} = 2.3 \text{ V}$ . Given that  $V_{CC} = 10 \text{ V}$ , and  $\beta = 100$ .




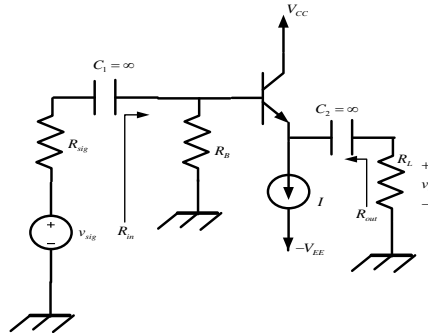Q.5: Consider the emitter-follower BJT amplifier circuit below. Find  $R_{in}$ ,  $R_{out}$  and the voltage gain  $v_o/v_{sig}$ . Given  $R_{sig} = 10\text{ k}\Omega$ ,  $R_B = 40\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $\beta=49$ , and  $V_A = 100\text{ V}$ . The bias current  $I = 5\text{ mA}$ . What is the largest peak amplitude of an output sine-wave signal that can be used without the transistor cutting off?




Q.6: (a) Consider the MOS circuit below. The transistor  $Q_1$  is biased for  $I_D = 80\text{ }\mu\text{A}$ . Both  $Q_1$  and  $Q_2$  have  $V_t=0.6\text{ V}$ . Design  $R$  and then find the drain current and drain voltage for  $Q_2$ . The channel modulation effect may be ignored and you may use the I-V equation:  $I = K_{ni}(V_{GS} - V_t)^2$ ,  $i=1,2$  for your work. Given  $K_{n1} = 500\text{ }\mu\text{A/V}^2$ ,  $K_{n2} = 750\text{ }\mu\text{A/V}^2$  for transistors  $Q_1$  and  $Q_2$  respectively.

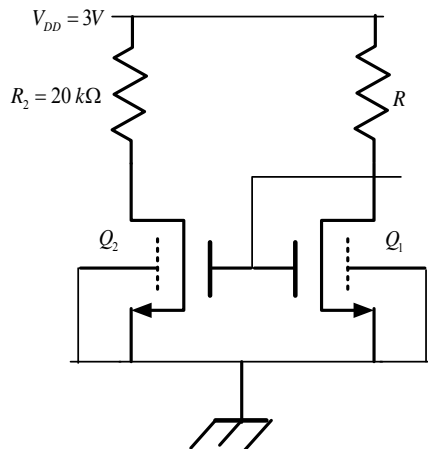(b) Assume now that the early voltage  $V_A = 40\text{ V}$  for both  $Q_1$  and  $Q_2$ . Draw the ac equivalent model for the circuit below.



Course	Number		Section
Electronics I	ELEC 311		BB
Final Examination	Date	Time	# of pages
	August 22, 2006	Three hours	4
Instructor			
Dr. R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
Students are allowed to use silent, non-programmable electronic calculators without text display.			
Special Instructions:			
Attempt all questions. Show all steps clearly in neat and legible handwriting. Students are required to return question paper together with exam booklet(s).			

**Q.1:** For the circuit shown below, find  $I_D$  and  $V_D$  for the case  $V_{DD}=5\text{ V}$ , and  $R=10\text{ k}\Omega$ . Assume that the diode has a voltage drop of  $0.7\text{ V}$  at  $1\text{-mA}$  current and that the voltage changes by  $0.1\text{ V/decade}$  of current change. Use (a) iteration method, and (b) the piecewise-linear model for the diode with  $V_{D0}=0.65\text{ V}$  and  $r_D=20\ \Omega$ .

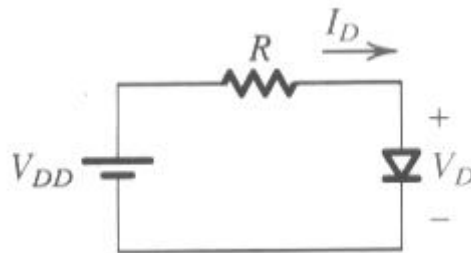

**Figure 1**


**Q.2:** A bridge-rectifier circuit with a filter capacitor has  $R=100\ \Omega$ . The secondary transformer delivers a sinusoid of  $12\text{ V (rms)}$  and has a frequency of  $60\text{ Hz}$ . The diodes have  $V_D=0.8\text{ V}$  each.

(a) What will be the value of the filter capacitor so that the ripple voltage is limited to below  $0.5\text{ V}$  peak-to-peak?

- (b) What is the DC voltage at the output of the system?
- (c) What is the conduction angle for the diode?

**Q.3:** For the transistor amplifier shown below, assume  $\alpha \cong 1$  and  $V_{BE} = 0.5 \text{ V}$  at the edge of conduction.


- (a) What are the values of  $V_E$  and  $V_C$  for  $V_B = 0 \text{ V}$ ?
- (b) For what value of  $V_B$  does the transistor cut off?, Saturate?
- (c) In each case, what values of  $V_E$  and  $V_C$  result?

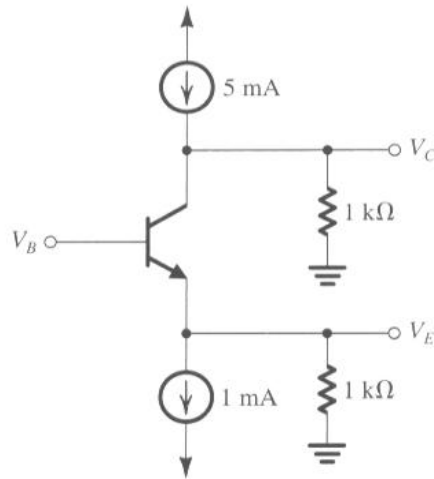

**Figure 3**


**Q.4:** For the BJT circuit below, the signal source generates ac signal with zero DC. The transistor has  $\beta = 100$ , and  $r_o = 200 \text{ k}\Omega$ .

- (a) Find  $R_E$  to establish a DC current of  $0.5 \text{ mA}$ . Assume  $V_{BE} = 0.7 \text{ V}$  for conduction.
- (b) Find  $R_C$  to obtain  $V_C = 5 \text{ V}$ .
- (c) With  $R_L = 10 \text{ k}\Omega$ , draw the ac equivalent circuit for the amplifier system, and
- (d) Determine the system voltage gain.

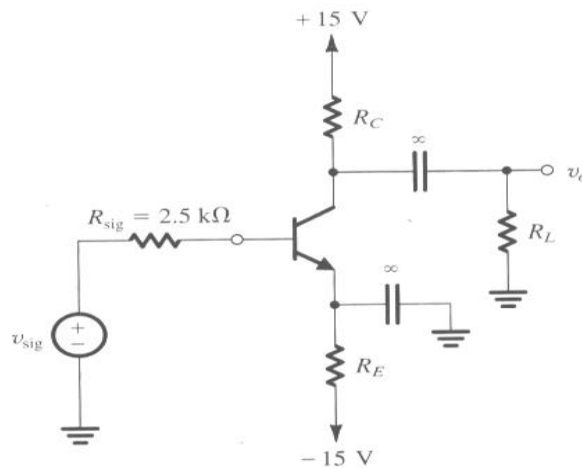


**Figure 4**

- Q.5:** For the circuit shown below, find
- the input resistance  $R_{in}$  , and
  - the voltage gain  $v_o/v_{sig}$  . Assume that the source provides a small signal  $v_{sig}$  and that  $\beta = 100$ .
  - What will be the maximum  $v_{sig}$  value for which the small signal approximation will remain valid?

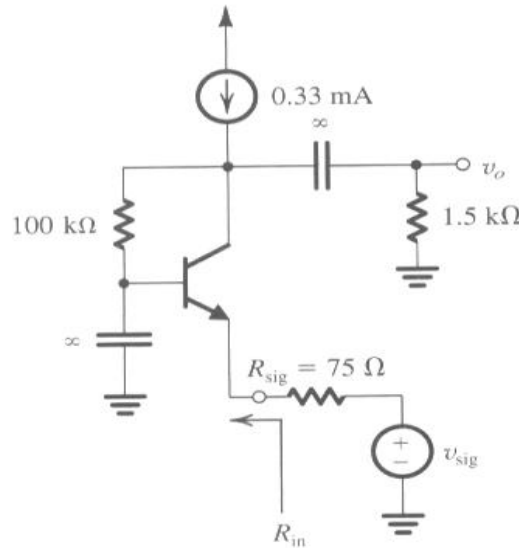

**Figure 5**

- Q.6:** Consider the MOSFET amplifier in the figure below. Given that  $V_G = 4V$ ,  $R_S = 1$  kΩ . The transistor has  $V_t = 1V$ , and  $k_n'(W/L) = 2$  mA/V<sup>2</sup> .
- Find the bias current  $I_D$ ?
  - What will be the voltage gain  $v_o/v_{sig}$ , if  $R_D = 20$  kΩ ,  $R_{G1} = 2$  MΩ ,  $R_{G2} = 1$  MΩ ,  $R_{sig} = 10$  kΩ , and  $V_{DD} = 12$  V?

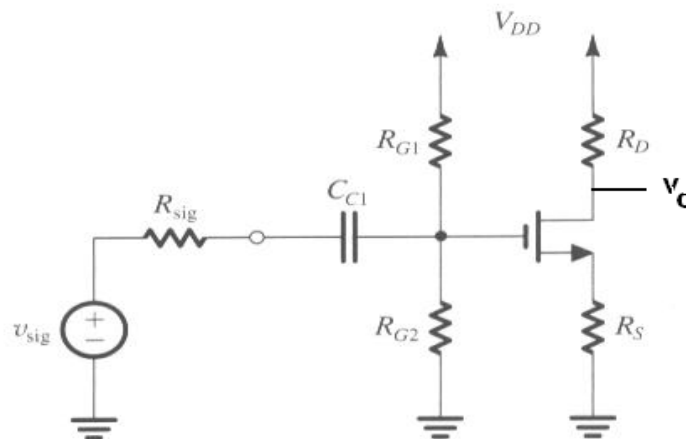

**Figure 6**

## Some important Formulas (BJT & MOSFET)

Model Parameters in Terms of DC Bias Currents			
$g_m = \frac{I_C}{V_T}$	$r_e = \frac{V_T}{I_E} = \alpha \left( \frac{V_T}{I_C} \right)$	$r_\pi = \frac{V_T}{I_B} = \beta \left( \frac{V_T}{I_C} \right)$	$r_o = \frac{ V_A }{I_C}$
In Terms of $g_m$			
$r_e = \frac{\alpha}{g_m}$	$r_\pi = \frac{\beta}{g_m}$		
In Terms of $r_e$			
$g_m = \frac{\alpha}{r_e}$	$r_\pi = (\beta + 1)r_e$	$g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$	
Relationships Between $\alpha$ and $\beta$			
$\beta = \frac{\alpha}{1 - \alpha}$	$\alpha = \frac{\beta}{\beta + 1}$	$\beta + 1 = \frac{1}{1 - \alpha}$	

### Overdrive voltage:

$$v_{OV} = v_{GS} - V_t$$

$$v_{GS} = V_t + v_{OV}$$

### Operation in the *triode* region:

#### ■ Conditions:

- (1)  $v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0$
- (2)  $v_{GD} \geq V_t \Leftrightarrow v_{DS} \leq v_{GS} - V_t \Leftrightarrow v_{DS} \leq v_{OV}$

#### ■ $i$ - $v$ Characteristics:

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

#### ■ For $v_{DS} \ll 2(v_{GS} - V_t) \Leftrightarrow v_{DS} \ll 2v_{OV}$

$$r_{DS} \equiv \frac{v_{DS}}{i_D} = 1 / \left[ \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t) \right]$$

### Operation in the *saturation* region:

#### ■ Conditions:

- (1)  $v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0$
- (2)  $v_{GD} \leq V_t \Leftrightarrow v_{DS} \geq v_{GS} - V_t \Leftrightarrow v_{DS} \geq v_{OV}$

#### ■ $i$ - $v$ Characteristics:

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

$$r_o = \left[ \lambda \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \right]^{-1} = \frac{V_A}{I_D}$$

where

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2$$

#### ■ Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} v_{OV} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{v_{OV}}$$

#### ■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

Course	Number		Section
Electronics I	ELEC 311		BB
Final Examination	Date	Time	# of pages
	August 15, 2007	Three hours	4
Instructor			
Dr. R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
Students are allowed to use silent, non-programmable electronic calculators without text display.			
Special Instructions:			
Attempt all questions.			
Show all steps clearly in neat and legible handwriting.			
Students are required to return question paper together with exam booklet(s).			

Q.1: For the equivalent circuit below, find the corresponding basic voltage amplifier model, i.e., find (a)  $A_{VO} = v_o/v_i$ , (ii)  $R_i$ , and (iii)  $R_o$ .


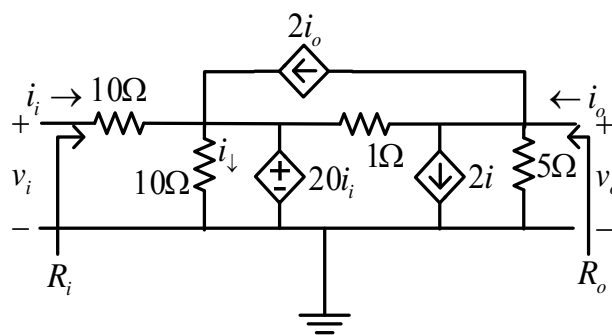


Figure 1

Q.2: A semiconductor junction diode is used in an automatic gain control system as shown below. The ac resistance of the diode is dependent on the amplitude  $V_p$  of the input signal. Higher  $V_p$  is, lower is the diode ac resistance and more it tends to attenuate the input ac signal. That is how the gain control mechanism works.

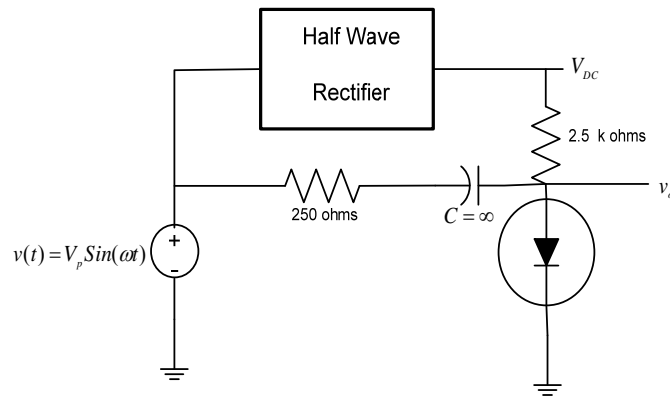

**Figure 2**

The input signal is half-wave rectified to generate a DC voltage which drives the DC current through the diode. This DC voltage  $V_{DC}$  is given by  $V_p / \pi$ , where  $V_p$  is the amplitude of the *ac* signal.

The diode is a 1 mA diode. The voltage drop across the diode changes by 100 milli volts for a decade (10 times) change in current through it. You may use the relation  $V_2 = V_1 + 2.303nV_T \log(I_2 / I_1)$ . The DC resistance of the diode can be neglected.

- If the input ac signal has an amplitude of 15 volts, what will be the amplitude of the output signal  $v_o$ ?
- If the input ac signal amplitude shoots up to 30 volts, how much will  $v_o$  become?

Q.3: For the transistor amplifier shown below, assume  $\alpha \cong 1$  and  $V_{BE} = 0.5$  V at the edge of conduction.

- What are the values of  $V_E$  and  $V_C$  for  $V_B = 0$  V?
- For what value of  $V_B$  does the transistor cut off?, Saturate?
- In each case, what values of  $V_E$  and  $V_C$  result?

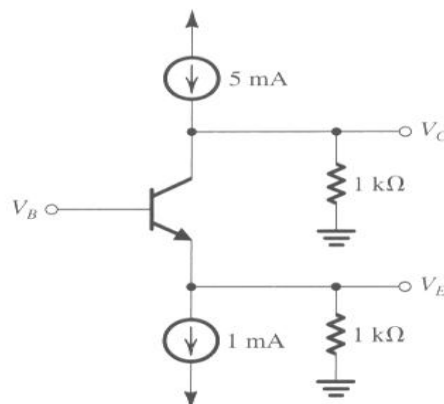


Figure 3

Q.4: For the circuit shown below, find

(a) the input resistance  $R_{in}$ , and

(b) the voltage gain  $v_o/v_{sig}$ . Assume that the source provides a small signal  $v_{sig}$  and that  $\beta = 100$ .

(c) What will be the maximum  $v_{sig}$  value for which the small signal approximation will remain valid?


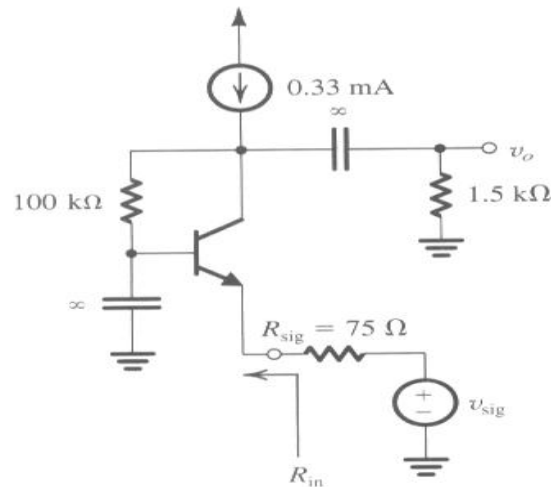


Figure 4

Q.5: Consider the MOSFET amplifier in the figure below. Given that  $V_G = 4V$ ,  $R_S = 1 k\Omega$ . The transistor has  $V_t = 1V$ , and  $k_n'(W/L) = 2 mA/V^2$ .

(a) Find the bias current  $I_D$ ?


(b) What will be the voltage gain  $v_o/v_{sig}$ , if  $R_D = 20 k\Omega$ ,  $R_{G1} = 2 M\Omega$ ,  $R_{G2} = 1 M\Omega$ ,  $R_{sig} = 10 k\Omega$ , and  $V_{DD} = 12 V$ ?

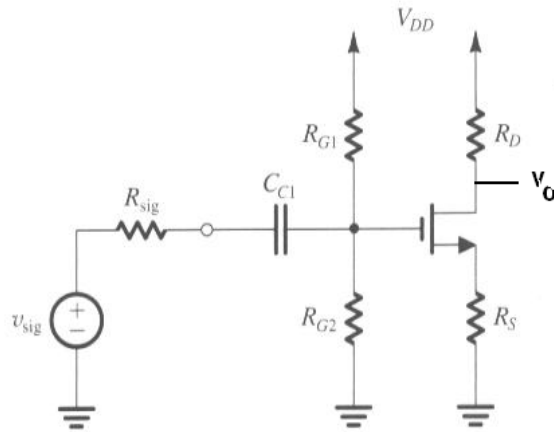

**Figure 5**

Q.6: (a) Consider the MOS circuit below. The transistor  $Q_1$  is biased for  $I_D = 80 \mu\text{A}$ . Both  $Q_1$  and  $Q_2$  have  $V_t = 0.6 \text{ V}$ . Design  $R$  and then find the drain current and drain voltage for  $Q_2$ . The channel modulation effect may be ignored and you may use the I-V equation:  
 $I_i = K_{n_i}(V_{GS} - V_t)^2$ ,  $i=1,2$  for your work. Given  
 $K_{n1} = 500 \mu\text{A}/\text{V}^2$ ,  $K_{n2} = 750 \mu\text{A}/\text{V}^2$  for transistors  $Q_1$  and  $Q_2$  respectively.

(a) Assume now that the early voltage  $V_A = 40 \text{ V}$  for both  $Q_1$  and  $Q_2$ . Draw the ac equivalent model for the circuit below.

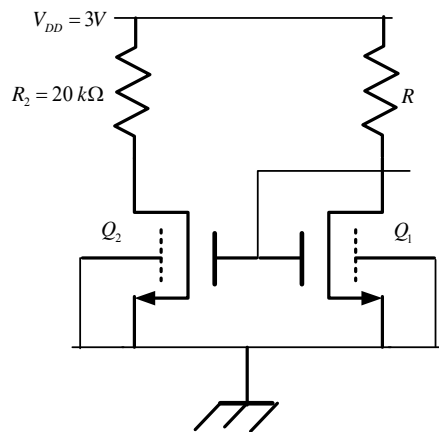

**Figure 6**

Course	Number	Section	
Electronics I	ELEC 311	BB	
Examination	Date	Time	# of pages
Final	August 20, 2008	3 hours	4
Instructor(s)			
R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
Students are allowed to use ENCS approved calculators only.			
Special Instructions:			
Attempt ALL questions. Show all steps clearly in neat and legible handwriting. Students are required to return question paper together with exam booklet(s).			

Q.1: A full wave bridge rectifier circuit with 1-k $\Omega$  load  $R_L$  operates from a 120-V (rms) 60-Hz supply through a 10:1 step-down transformer as shown in figure 1 below. Each of the diode is modeled as a battery with 0.7-V drop.

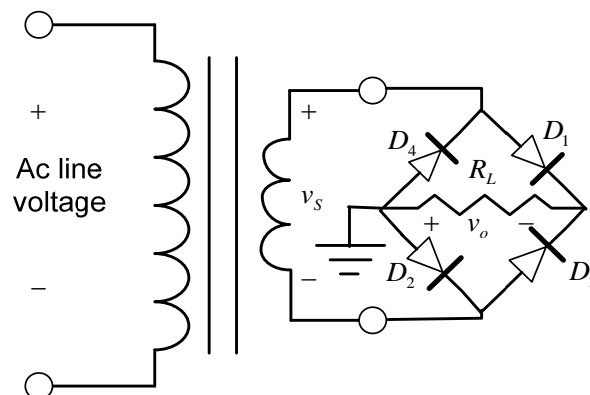


Figure 1

- (a) What is the peak value of the rectified voltage across the load?
- (b) For what fraction of a cycle does each diode conduct?
- (c) What is the average current through the load?

Q.2: For the circuit shown in figure 2, the voltage  $V_E$  was measured to be  $-0.7\text{ V}$ . If  $\beta=50$ , find  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$ .

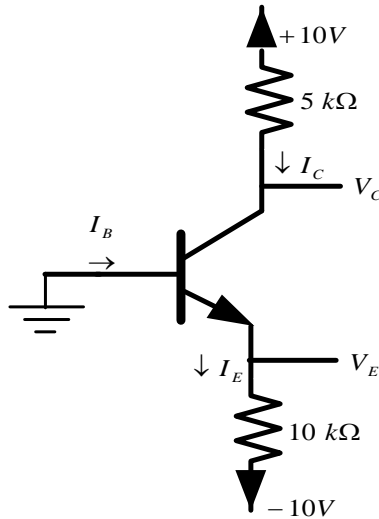


Figure 2

Q.3: In the circuit shown below (Fig.3), the transistor has  $\beta=199$ . Find

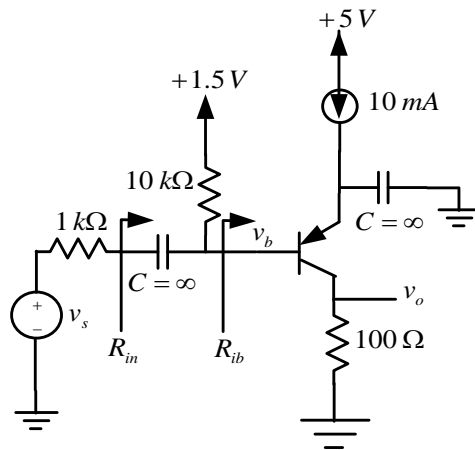


Figure 3

- (a) the DC voltage at the collector.
- (b) the DC voltage at the base
- (c) the input resistance  $R_{in}$  (use the small-signal ac equivalent circuit model for the BJT)

Q.4: In the BJT amplifier circuit of figure 4, the DC bias current  $I_C$  is 2.3 mA. The transistor has a  $\beta=100$  and Early voltage  $V_A = 100$  Volts.

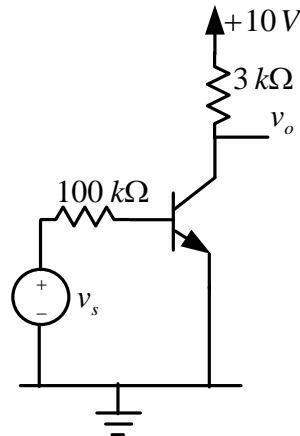


Figure 4

- Draw the small-signal ac equivalent model for the amplifier and show the values of the ac parameters  $g_m$ ,  $r_\pi$ ,  $r_o$ .
- Find the voltage gain  $v_o/v_s$ .
- Up to what value of  $v_s$  the amplifier will operate properly (i.e., the BJT shall remain in the active mode)?

Q.5: Consider the MOFET amplifier shown in figure 5. Design the resistances so that you can achieve  $V_D=3.4$  V,  $V_S = 1.6$  V, and  $I_D=0.3$  mA. The voltage divider resistances  $R_{G1}$ ,  $R_{G2}$  has a current of 1- $\mu$ A. The MOSFET has  $V_t=1$  V,  $k_n(w/L) = 1$  mA/V<sup>2</sup>.

Given  $V_{DD}=10V$

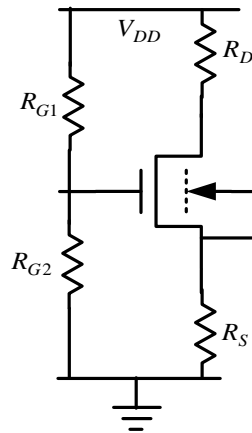


Figure 5

Q.6: For the NMOS amplifier shown in figure 6, replace the transistor with its T-equivalent model.

Derive

- the expression for the voltage gain  $v_s/v_i$ .
- the expression for the voltage gain  $v_d/v_i$ .

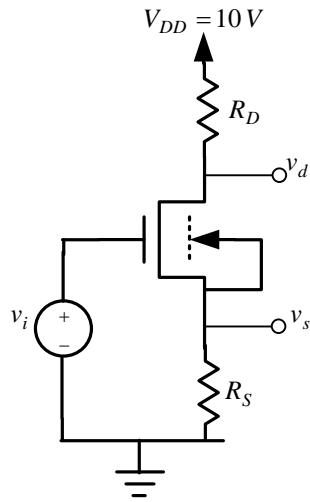


Figure 6

(Some formulae and equivalent circuits)

$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, \quad r_e = \frac{r_\pi}{\beta + 1},$ $I_C = I_S \exp(V_{BE} / V_T)$
$I_D = k \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ <p>(linear region)</p>	$I_D = k \left( \frac{W}{2L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$ <p>(saturation region)</p>	$g_m = k \left( \frac{W}{L} \right) (V_{GS} - V_t) = \sqrt{\frac{2kI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$
<p>BJT hybrid pi</p>	<p>BJT T</p>	
<p>MOS hybrid pi</p>	<p>MOS T</p>	



Course	Number	Section
Electronics I	ELEC 311/1	BB
Examination	Date	Time
Final	August 14, 2009	3 hours
Instructor(s)	# of pages	
Dr.R. Raut	6	
<p>Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)</p> <p>Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes</p> <p>Students are allowed to use ENCS faculty approved calculators</p> <p>Special Instructions:</p> <p>You <b>MUST</b> attempt <b>Q.1</b> (<i>soft skill</i> component) .</p> <p>For <b>Q.2-Q.7</b>, answer any <b>FOUR</b> questions.</p> <p><i>Before submitting your answer book, <b>fill in the Table below</b> indicating the answers you want to be graded.</i></p> <p>If you <b>do not fill in the Table</b>, the instructor will mark your answers <i>as they appear one after another in the answer book</i></p> <p>Show all steps clearly in neat and legible handwriting.</p> <p>Students are required to <i>return the question paper</i> together with exam booklet(s).</p>		

**Table**

Answers to be graded	<b>Q.1 (compulsory)</b>				
Marks					


**(Soft skill component- The student MUST answer this question)**

**Q.1:** Consider the MOS circuit below. Both  $Q_1$  and  $Q_2$  have  $V_t=0.7$  V. Ignore the channel modulation effect. You may use the I-V equation:  $I = K_m(V_{GS} - V_t)^2$ ,  $i=1,2$  for your work.

Given  $K_{n1} = 500 \mu A/V^2$ ,  $K_{n2} = 750 \mu A/V^2$  for transistors  $Q_1$  and  $Q_2$  respectively.

(a) Design  $R$  to establish  $I_D = 100 \mu A$  in the transistor  $Q_1$

(b) Find the drain current and drain voltage for  $Q_2$ .

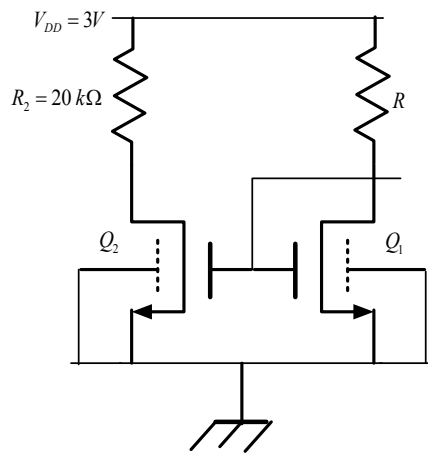


**Figure 1:**

(Answer any **FOUR** from the questions below)

**Q.2:** A zener diode exhibits a voltage of 6.5 V for  $I_Z = 5$  mA. The zener has  $I_{ZK} = 0.5$  mA, and a minimum of *five times*  $I_{ZK}$  must flow through the zener for reliable operation. The diode has an internal resistance of 15 ohms. The device is used to build a shunt regulator circuit as shown below.


The raw DC supply has a nominal value of 15 V, and can range between 12 V to 18 V. The load current varies from 0 mA to 15 mA.

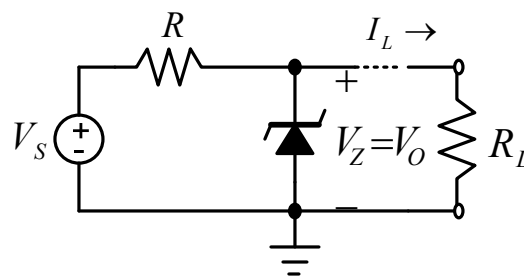

**Figure 2:**

- (a) Design a suitable value for the resistance  $R$  for reliable operation.
- (b) What will be the output voltage if  $R_L = 450 \Omega$  is connected across the output of the system and the raw DC is at its lowest value (12 V)?

**Q.3:** A bridge-rectifier circuit with a filter capacitor has  $R_L = 100$  ohms. The secondary transformer delivers a sinusoid of 15 V (rms) and has a frequency of 60 Hz. The diodes have  $V_{DO} = 0.7$  V each.

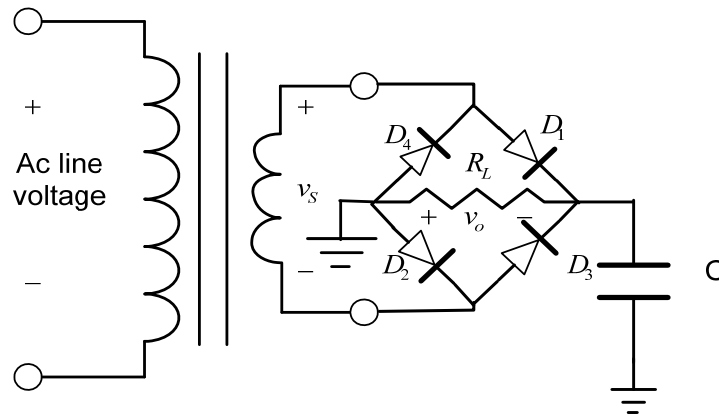


**Figure 3**

- (a) What will be the value of the filter capacitor  $C$  so that the ripple voltage is limited to below 500 mV peak-to-peak?
- (b) What is the DC voltage at the output of the system?
- (c) What is the conduction angle for each diode in the system? Explain with appropriate sketches.

**Q.4:** For the BJT circuit (Figure 4), the signal source generates ac signal with zero DC. The transistor has  $\beta = 100$ , and  $r_o = 20 \text{ k}\Omega$ .

- (a) Find  $R_E$  to establish a DC current of  $I_E = 0.5 \text{ mA}$ . Assume  $V_{BE} = 0.7 \text{ V}$  for conduction.
- (b) Find  $R_C$  to obtain  $V_C = 5 \text{ V}$ .
- (c) Determine the system voltage gain with  $R_L = 10 \text{ k}\Omega$ ,

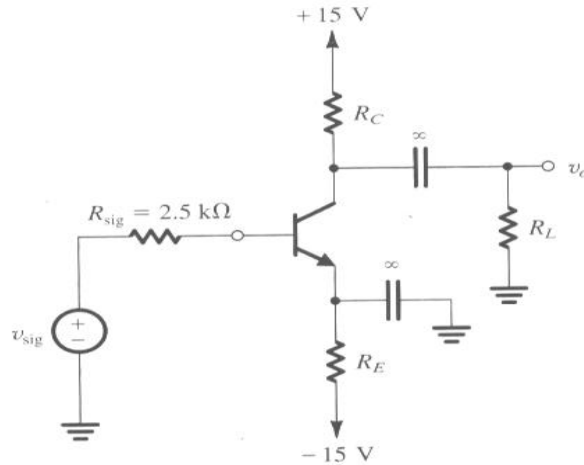


**Figure 4:**

**Q.5:** Consider the emitter-degenerated CE BJT amplifier circuit shown below. The signal source has a resistance  $R_s = 1 \text{ k}\Omega$  and the load  $R_L$  is  $5 \text{ k}\Omega$ .

Given  $V_A = \text{infinity}$ ,  $\beta = 100$ ,  $I_E = 2 \text{ mA}$ .


- What value of  $R_E$  will make  $R_{in} = 10 \text{ k}\Omega$ ?
- With the above value of  $R_E$ , what will be the overall voltage gain  $v_o/v_i$  of the system?
- If  $R_E$  is by-passed by a large capacitance (negligible reactance), what voltage gain can be obtained?

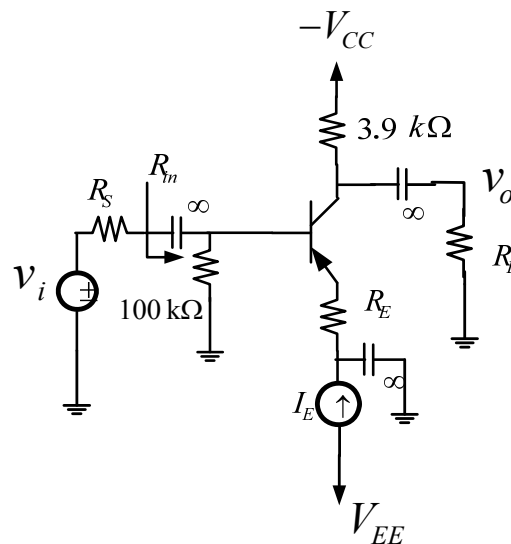

**Figure 5:**

**Q.6:** For the circuit shown (Figure 6)


- (a) Draw the ac equivalent circuit for the amplifier.
- (b) Find the voltage gain  $v_o/v_{sig}$ . Assume that the source provides a small signal  $v_{sig}$  with zero DC., and that  $\beta=100$ .
- (c) What will be the maximum  $v_{sig}$  value for which the small signal approximation will remain valid?

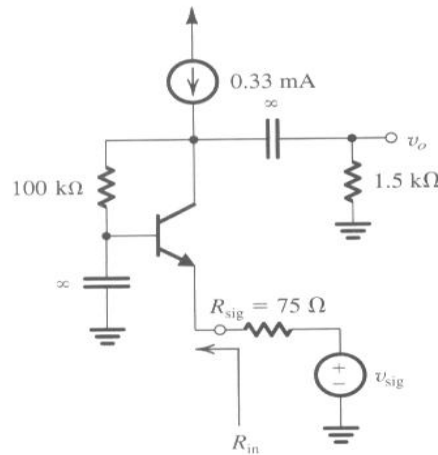

**Figure 6:**

**Q.7:** Consider the MOSFET amplifier in the figure below. Given that  $V_G=4V$ ,  $V_{DD}=10V$ ,  $R_S=1k\Omega$ . The transistor has  $V_t=1V$ , and  $k_n'(W/L)=5mA/V^2$ .

- (a) Find the bias current  $I_D$  through the MOS device.
- (b) What will be the voltage gain  $v_o/v_{sig}$ , if  $R_D=15k\Omega$ ,  $R_{G1}=2M\Omega$ ,  $R_{G2}=1M\Omega$ ,  $R_{sig}=10k\Omega$ ?

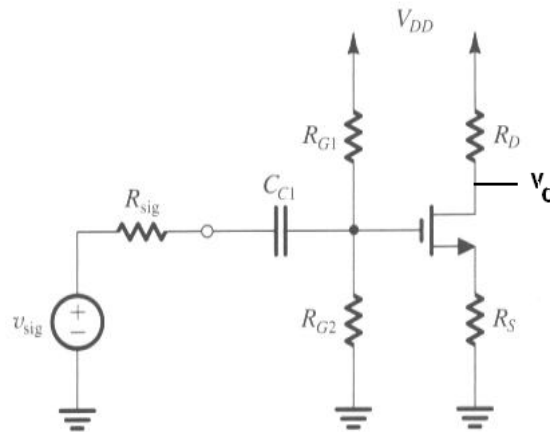

**Figure 7:**

## Some important Formulas (BJT & MOSFET)

Model Parameters in Terms of DC Bias Currents			
$g_m = \frac{I_C}{V_T}$	$r_e = \frac{V_T}{I_E} = \alpha \left( \frac{V_T}{I_C} \right)$	$r_\pi = \frac{V_T}{I_B} = \beta \left( \frac{V_T}{I_C} \right)$	$r_o = \frac{ V_A }{I_C}$
In Terms of $g_m$			
$r_e = \frac{\alpha}{g_m}$	$r_\pi = \frac{\beta}{g_m}$		
In Terms of $r_e$			
$g_m = \frac{\alpha}{r_e}$	$r_\pi = (\beta + 1)r_e$	$g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$	
Relationships Between $\alpha$ and $\beta$			
$\beta = \frac{\alpha}{1 - \alpha}$	$\alpha = \frac{\beta}{\beta + 1}$	$\beta + 1 = \frac{1}{1 - \alpha}$	

### Overdrive voltage:

$$v_{OV} = v_{GS} - V_t$$

$$v_{GS} = V_t + v_{OV}$$

### Operation in the *triode* region:

#### ■ Conditions:

$$(1) \ v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0$$

$$(2) \ v_{GD} \geq V_t \Leftrightarrow v_{DS} \leq v_{GS} - V_t \Leftrightarrow v_{DS} \leq v_{OV}$$

#### ■ $i$ - $v$ Characteristics:

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

#### ■ For $v_{DS} \ll 2(v_{GS} - V_t) \Leftrightarrow v_{DS} \ll 2v_{OV}$

$$r_{DS} \equiv \frac{v_{DS}}{i_D} = 1 / \left[ \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t) \right]$$

### Operation in the *saturation* region:

#### ■ Conditions:

$$(1) \ v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0$$

$$(2) \ v_{GD} \leq V_t \Leftrightarrow v_{DS} \geq v_{GS} - V_t \Leftrightarrow v_{DS} \geq v_{OV}$$

#### ■ $i$ - $v$ Characteristics:

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

#### ■ Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} v_{OV} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{v_{OV}}$$

#### ■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$


Course <b>Electronics I</b>	Number <b>ELEC 311/1</b>	Section <b>BB</b>
Examination <b>Final</b>	Date <b>August 17, 2012</b>	Time <b>3 hours</b>
Instructor(s) <b>Dr.R. Raut</b>		
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)		
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes		
Students are allowed to use ENCS faculty approved calculators		
<b>Special Instructions:</b>		
You MUST attempt <b>Q.1</b> ( <i>soft skill</i> component) . For <b>Q.2-Q.8</b> , answer any <b>FIVE</b> questions.		
<i>Before submitting your answer book, <b>fill in the Table below</b> indicating the answers you want to be graded. If you <b>do not fill in the Table</b>, the instructor will mark your answers as they appear one after another in the answer book</i>		
Show all steps clearly in neat and legible handwriting. Students are required <i>to return the question paper</i> together with exam booklet(s).		

**Table** (*Do not forget to fill in!*)

<b>Answers to be graded</b>	<b>Q.1 (compulsory)</b>					
Marks						

(Soft skill component- The student MUST answer this question)

**Q.1:** Figure 1 depicts two NMOS transistors each with  $V_{THN} = 0.5$  V,  $K_n = 0.5$  mA/V<sup>2</sup>, and W/L ratio of 4. The *early* voltage for M2 can be assumed to be *infinity*.

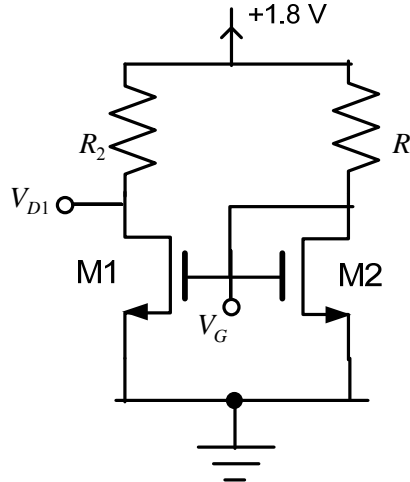

**Figure 1**


- Design  $R_1$  so that  $V_G = 0.7$  V.
- Find  $R_2$  so that M1 will be just at the edge of saturation region.
- What will be the current in M1 if it has an *early* voltage of 50 V?

(Answer **any FIVE** questions)

**Q.2:** A semiconductor junction diode **D** is used in an automatic gain control system as shown in **figure 2**. The ac resistance of the diode is dependent on the amplitude  $V_p$  of the input signal. The capacitance acts as a *short circuit* and the inductor acts as an *open circuit* for the *ac* signal.

The input signal is full-wave rectified to generate a DC voltage which drives the DC current through the diode. This DC voltage is given by  $2V_p / \pi$ . The diode is a 1 mA diode. The voltage drop across the diode changes by 100 milli volts for a decade (10 times) change in current through it. For the diode you may use the relation:  $V_2 = V_1 + 2.303nV_T \log_{10}(I_2 / I_1)$ , where  $V_T$  is the thermal voltage ( $=25$  mV). The DC resistance of the diode can be neglected.


If the input ac signal has a peak amplitude of 10 volts, what will be the output signal magnitude  $v_o$ ?

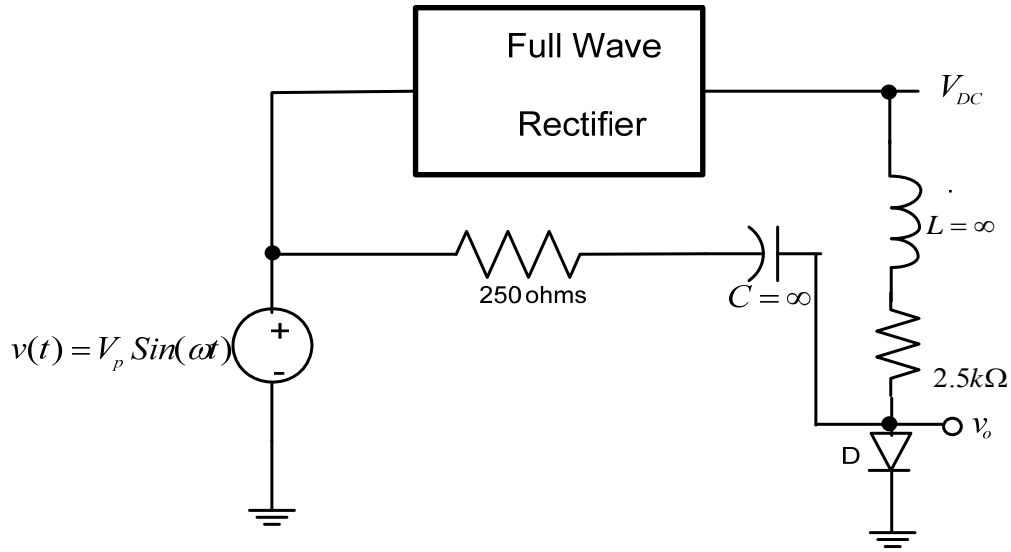

**Figure 2**


**Q.3:** The bridge-rectifier circuit in **figure 3** with a filter capacitor has  $R_L = 200$  ohms. The secondary transformer delivers a sinusoid of 15 V (rms) and has a frequency of 60 Hz. The diodes have  $V_D = 0.8$  V each.

- What will be the value of the filter capacitor so that the ripple voltage is limited to below 0.5 volts peak-to-peak?
- What is the DC voltage at the output of the system?
- What should be the PIV rating for the diodes?

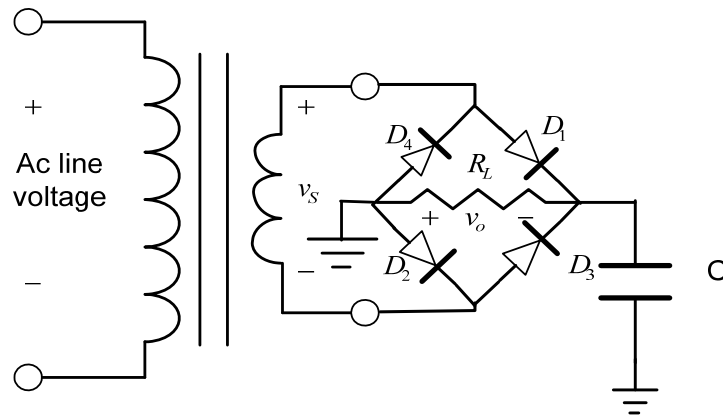

**Figure 3**


**Q.4:** Calculate the small signal gain  $v_o/v_s$  for the BJT amplifier circuit in **figure 4**. Assume transistor parameters of  $\beta = 80$ ,  $V_{BE}(\text{on}) = 0.7 \text{ V}$ ,  $V_A = 50\text{V}$ .

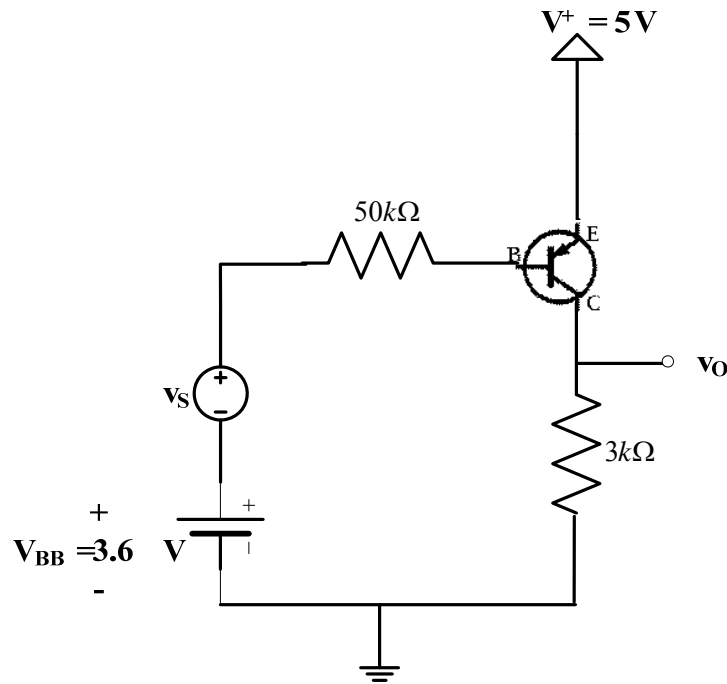

**Figure 4**

**Q.5:** Design (i.e., design the resistor values) a bias-stable PNP-BJT amplifier stage of **figure 5** to meet the following specifications.

The transistor Q-point values are to be:  $V_{ECQ} = 6 \text{ V}$ ,  $I_{CQ} \approx 0.5 \text{ mA}$  and  $V_{RE} \approx 2 \text{ V}$ . Assume transistor parameters of  $\beta = 99$  and  $V_{BE}(\text{ON}) = 0.7 \text{ V}$ .

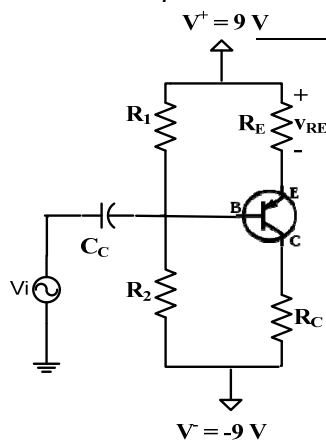

**Figure 5**


Find  $R_1$ ,  $R_2$ ,  $R_E$ , and  $R_C$ .

**Q.6:** For the circuit shown in **figure 6** find

(a) the input resistance  $R_{in}$ , and

(b) the voltage gain  $v_o/v_s$ . Assume that the source provides a small signal  $v_{sig}$  and that  $\beta = 100$ .

(c) What will be the maximum  $v_s$  value for which the small signal approximation will remain valid?

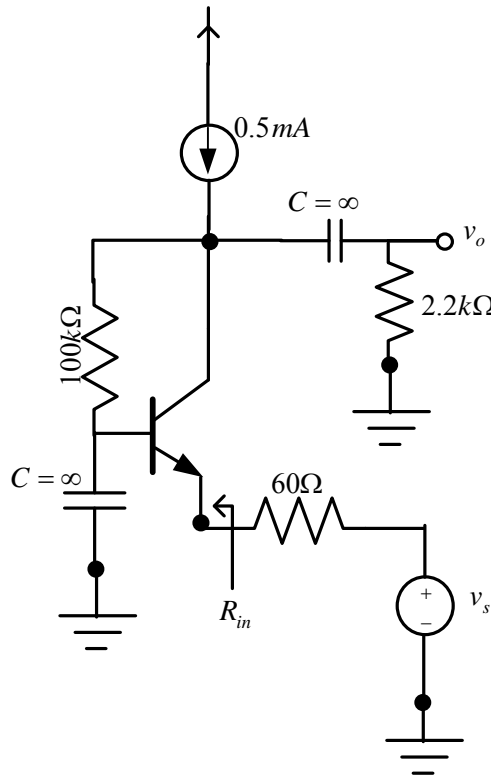

**Figure 6**

**Q.7:** A Common Source (CS) MOSFET amplifier is biased at  $I_D = 0.25$  mA with a current source connected at the Source terminal of the MOSFET. The transistor has  $V_{OV} = 0.3$  V, and a drain resistance of  $R_D = 15$  k $\Omega$  connected to the DC supply of 15 V. The device has  $V_A = 50$  V. The amplifier is capacitively fed from a source with internal resistance  $R_{sig} = 100$  k $\Omega$ , and a 20 k $\Omega$  load is capacitively coupled to the drain of the amplifier.

(a) Draw the schematic for the amplifier system.

(b) Calculate the voltage gain of the system.

**Q.8:** Consider **figure 8**. Calculate the labeled node voltages  $V_1$  and  $V_2$ , given that the MOSFETs have  $V_{THN} = 1$  V, and  $K_n \frac{W}{L} = 3$  mA/V<sup>2</sup>.

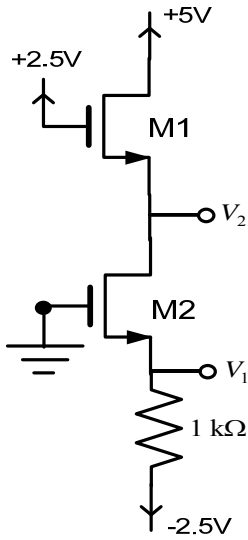


Figure 8

(Some formulae and equivalent circuits)

$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, \quad r_e = \frac{r_\pi}{\beta + 1}$ $I_C = I_S \exp(V_{BE} / V_T)$
$I_D = k \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ <p style="text-align: center;">(linear region)</p>	$I_D = k \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$ <p style="text-align: center;">(saturation region)</p>	$g_m = k \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2kI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$
<p style="text-align: center;">BJT hybrid pi</p>	<p style="text-align: center;">BJT T</p>	
<p style="text-align: center;">MOS hybrid pi</p>	<p style="text-align: center;">MOS T</p>	

Course	Number	Section	
Electronics I	ELEC 311/2	F,U	
Examination	Date	Time	# of pages
Final	December 13, 2012	3 hours	8
Instructor(s)			
Dr.R. Raut, Dr. V. Ramachandran			

Materials allowed:  No  Yes (Please specify)

Calculators allowed:  No  Yes

Students are allowed to use ENCS faculty approved calculators

Special Instructions:

You are required to answer SIX questions

You MUST attempt **Q.1** (*soft skill* component) : **6 marks**

From **Q.2-Q.6**, answer any **THREE** questions.: **8 marks** (each)

From **Q.7-Q.10** answer any **TWO** questions: **10 marks** (each)

Before submitting your answer book, **fill in the Table below** indicating the answers you want to be graded.

(If you **do not** fill in the Table, the instructor will mark your answers as they appear one after another in the answer book)

Show all steps clearly in neat and legible handwriting.

Students are required to return the question paper together with exam booklet(s).

(STUDENT) NAME:

ID #

Table


Answers to be graded	<b>Q.1 (compulsory)</b>					
Marks						

(Some important formulae)

$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, r_e = \frac{r_\pi}{\beta + 1},$  $I_C = I_S \exp(V_{BE} / V_T)$
$I_D = K \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$  (linear region)	$I_D = K \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2$  (saturation region, excluding Early effect)	$g_m = K \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2KI_D W}{L}}$  $r_o = \frac{V_A}{I_D}$

**Section I (Compulsory):** Soft skill component- *The student **MUST** answer this question*

**Q. 1:** The NMOS transistor in the circuit of Figure 1 have  $V_{THN} = 1 \text{ V}$ ,  $K = 120 \mu\text{A}/\text{V}^2$ ,  $\lambda = 0$ , and  $L_1 = L_2 = L_3 = 1.5 \mu\text{m}$ . Find the required values of gate width for each of  $M_1, M_2$ , and  $M_3$  to obtain the voltage and current values indicated. **(6 marks)**.

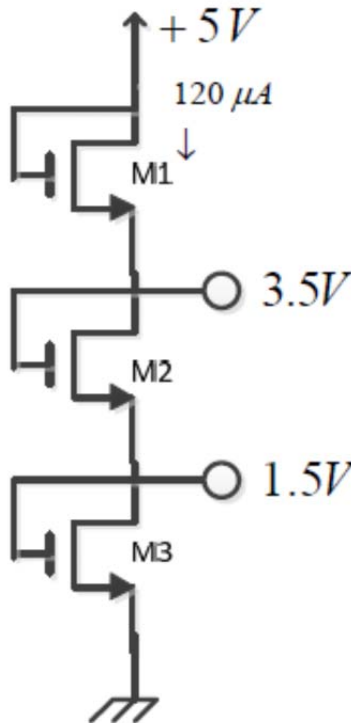

**Figure 1:**

**Section II** (From **Q.2-6**, answer ONLY three questions)

**Q.2:** The current-voltage relationship of a diode is given by

$$i_D = I_s e^{\frac{v_D}{V_T}}$$


where  $I_s$  is the scale current of the diode,

$V_T$  is the thermal voltage = 25 mV at room temperature,

$v_D$  is the voltage across the diode.


- What is the mA rating of the diode, given  $I_s = 10^{-15}$  amperes?
- Assuming that  $V_i = 0.7$  V and  $v_s = 0.05 \sin(360t)$  are applied to the diode (see Fig.2), draw the corresponding (i) DC model and (ii) the *ac* model of the diode.
- Using the above equivalent circuits, obtain the output voltage across the diode configured as in Fig.2.

**(8 marks)**

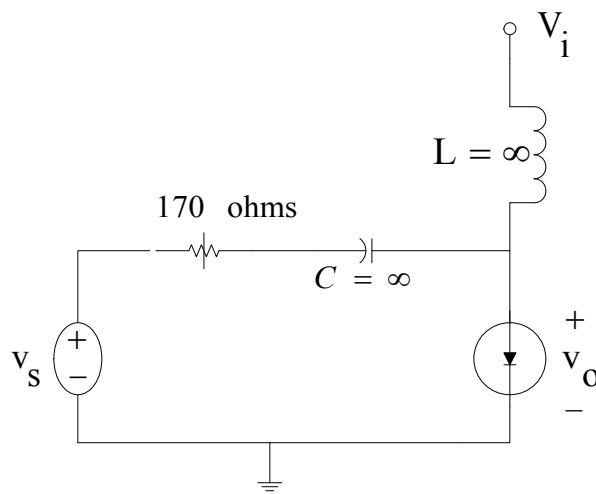

**Figure 2:**

**Q.3:** . Figure 3 shows an electronic amplifier employing a power *npn* BJT device.

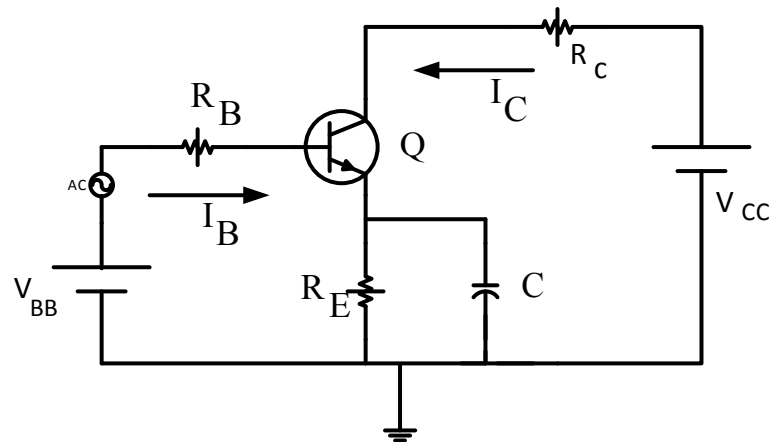


**Figure 3:**

It is given that  $V_{BB} = 6\text{ V}$ ,  $V_{BE} = 0.7\text{ V}$ ,  $V_{CC} = 80\text{ V}$ ,  $R_B = 10,000\text{ ohms}$ ,  $R_C = 5000\text{ ohms}$ ,  $R_E = 10,000\text{ ohms}$ ,  $C \rightarrow \infty$  and  $\beta$  of the transistor is 29.

- Verify that the transistor is in the active region.
- Draw the *ac* equivalent circuit, given  $V_A = 200\text{ V}$ . Label the calculated *ac* parameters. **(8 marks)**

**Q.4(a)** Figure 4(a) shows a half-wave rectifier circuit. The diode *D* can be considered ideal.

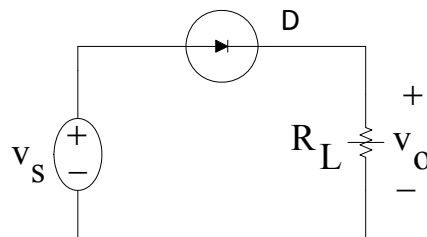


**Figure 4(a):**

The system data are:  $v_s(t) = 60 \cos[(120\pi t)]$  Volts and  $R_L = 100\text{ kilo ohms}$ .

- Obtain the DC component of  $v_o(t)$
- What is the peak inverse voltage across the diode?

(b) In the system shown in **Fig.4(a)**, a capacitor of value  $10\ \mu\text{F}$  is connected across  $R_L$ , as shown in **Fig.4(b)**.

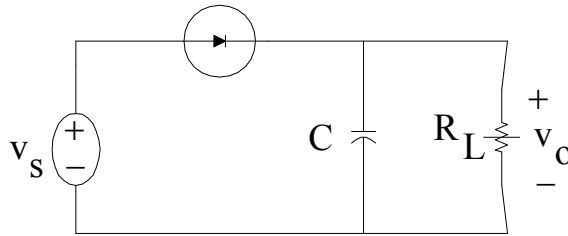


**Figure 4(b):**

- (i) Sketch the waveform of  $v_o(t)$  and label the various values. Find the *ripple* voltage.
- (ii) Determine the DC component of  $v_o(t)$ .
- (iii) What is the peak inverse voltage across the diode?
- (iv) What should be the new value of  $C$ , if the *ripple* found in (i) is to be reduced to half the value?

**(8 marks)**

**Q.5:** Figure 5 shows a MOSFET circuit.

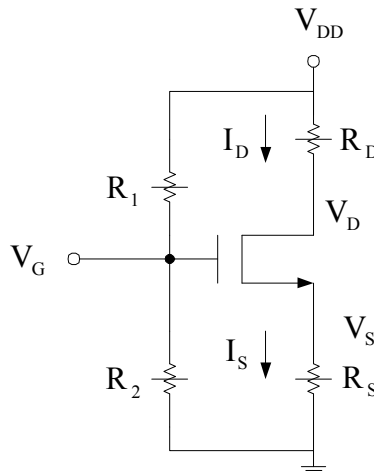

**Figure 5:**

The various component values are given by:  $R_1 = 200$  kilo ohms,  $R_2 = 150$  kilo ohms,  $R_D = 6$  kilo ohms,  $R_S = 4.5$  kilo ohms,  $V_{DD} = 10$  volts. For the transistor,  $K = 200\ \mu\text{A}/\text{V}^2$ ,  $(W/L) = 5$ ,  $V_{GS} = 1.1\ \text{V}$ ,  $V_{THN} = 0.7\ \text{V}$ .

- (a) Verify that the MOSFET is in the saturation region.
- (b) Draw the complete *ac* equivalent circuit of Fig.5.

(8 marks)


**Q.6:** For the circuit shown in figure 6 assume that the source  $v_s$  provides a small signal  $v_{sig}$  and that the BJT has  $\beta=100$ .

Find:

(a) the input resistance  $R_{in}$ .

(b) What will be the maximum  $v_s$  value for which the small signal approximation will remain valid?

(8 marks)

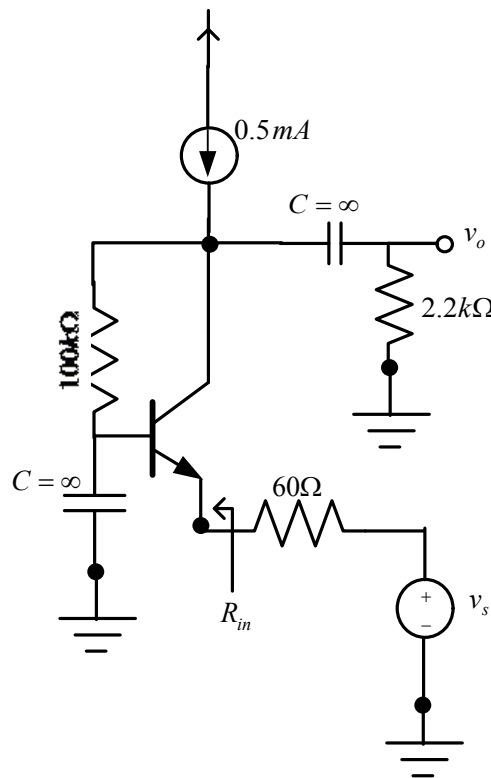

**Figure 6:**

**Section III** (From **Q.7-10**, answer ONLY two questions)

**Q.7:** Design (i.e., design the resistor values) a bias-stable PNP-BJT amplifier stage of figure 7 to meet the following specifications.

The transistor Q-point values are to be:  $V_{ECQ} = 6 \text{ V}$ ,  $I_{CQ} \approx 0.5 \text{ mA}$  and  $V_{RE} \approx 2 \text{ V}$ . Assume transistor parameters of  $\beta = 99$  and  $V_{EB}(\text{ON}) = 0.7 \text{ V}$ .

(10 marks)

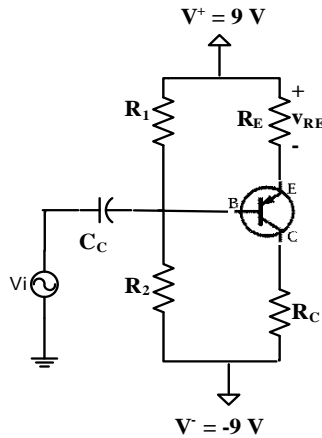



Figure 7:

**Q.8:** Consider the emitter-degenerated CE BJT amplifier circuit shown in figure 8. The signal source has a resistance  $R_s = 1 \text{ k}\Omega$  and the load  $R_L$  is  $5 \text{ k}\Omega$ .

Given  $V_A = \text{infinity}$ ,  $\beta = 100$ ,  $I_E = 2 \text{ mA}$ .

- What value of  $R_E$  will make  $R_{in} = 10 \text{ k}\Omega$ ?
- With the above value of  $R_E$ , what will be the overall voltage gain  $v_o/v_i$  of the system?
- If  $R_E$  is by-passed by a large capacitance (negligible reactance), what voltage gain can be obtained?

(10 marks)

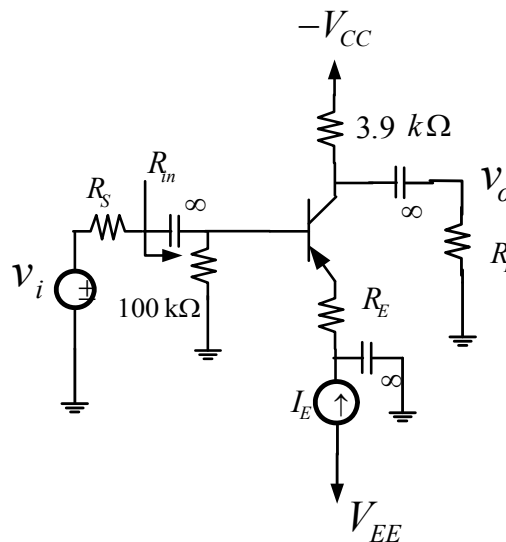

**Figure 8:**

**Q.9:** A Common Drain (CD) MOSFET amplifier is biased at  $I_D = 0.25$  mA with a current source connected at the Source terminal of the MOSFET. The transistor has  $V_{OV} = 0.3$  V, and a load resistance of  $15$  k $\Omega$  is connected to the source terminal via a coupling capacitance of *infinite* value. The device has  $V_A = 50$  V. The amplifier is fed from a source with internal resistance  $R_{sig} = 100$  k $\Omega$  via a coupling capacitor of *infinite* value.

- (a) Draw the schematic diagram for the amplifier system.
- (b) Calculate the voltage gain of the system.


**(10 marks)**

**Q.10:** Figure 10 presents a Common Gate MOS amplifier as an integrated circuit. The transistor M0 provides a bias current of  $0.5$  mA. The output resistance of M0 can be *assumed as infinity*. Assume that for M2,  $K_p = 100$   $\mu\text{A}/\text{V}^2$ , and for M1,  $K_n = 300$   $\mu\text{A}/\text{V}^2$ . Further, for M2,  $V_{Ap} = -40$  V, and for M1,  $V_{An} = 30$  V. Given that  $V_{THN} = |-V_{THP}| = 1$  V, and  $W/L = 2$  for all the transistors. The body transconductance  $g_{mb}$  of M1 can be ignored.

M1 is the *driver* transistor, and M2 serves as the active load.  $V_{DD} = |-V_{SS}| = 10$  V.

Draw the *ac* equivalent circuit, and then find the voltage gain  $v_o/v_{in}$  for the amplifier.

**(10 marks)**

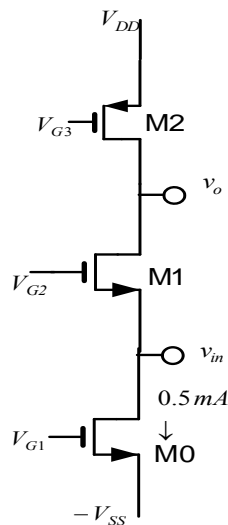

**Figure 10:**

Course	Number	Section
Electronics I	ELEC 311/1	BB
Examination	Date	Time
Final	August 21, 2013	3 hours
Instructor(s)	# of pages	
Dr.R. Raut	7	

Materials allowed:  No  Yes (Please specify)

Calculators allowed:  No  Yes

Students are allowed to use **ONLY** ENCS faculty approved calculators

Special Instructions:

You are required to answer SIX questions

You MUST attempt **Q.1** (soft skill component) : **5 marks**

From **Q.2-Q.8**, answer any **FIVE** questions.: **9 marks** (each)

Before submitting your answer book, **fill in the Table below** indicating the answers you want to be graded.

(If you **do not** fill in the Table, the instructor will mark your answers as they appear one after another in the answer book)

Show all steps clearly in neat and legible handwriting.

Students are required to return the question paper together with exam booklet(s).

**(STUDENT) NAME:**

**ID #**

**Table**

Answers to be graded	<b>Q.1 (compulsory)</b>					
Marks						

(Some important formulae)

$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, r_e = \frac{r_\pi}{\beta + 1},$ $I_C = I_S \exp(V_{BE} / V_T)$
$I_D = K \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ (linear region)	$I_D = K \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2$ (saturation region, excluding Early effect)	$g_m = K \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2KI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$

**Section I (Compulsory):** Soft skill component- *The student **MUST** answer this question*

**Q. 1:** For the MOS circuit shown in **Fig.1**, find  $V_1$ , and  $V_2$ . For the NMOS transistors  $V_{TH}=1V$ ,  $K = 1mA/V^2$ ,  $W/L=8$ .


(5 marks).

**Figure 1:**

**Section II** (From **Q.2-8**, answer ONLY FIVE questions)

**Q.2:** A given shunt regulator system is driven by a raw DC voltage source of 10 V (nominal) with a variation of  $\pm 1$  V. The diode is a 6.8 V Zener at an operating current of 5 mA, with  $r_z = 20 \Omega$ , and  $I_{ZK(\text{Min})} = 0.2$  mA. The line resistance used is  $500 \Omega$ . Calculate the following, with supporting circuit analysis. A circuit model for the diode is shown in **Fig.2**.


- Draw the equivalent circuit for the whole system.
- Calculate the line regulation and the amount of fluctuation of the output voltage when the input fluctuates by  $\pm 1$  V.
- Find the output voltage if a  $500 \Omega$  resistance is connected as the load to the system.

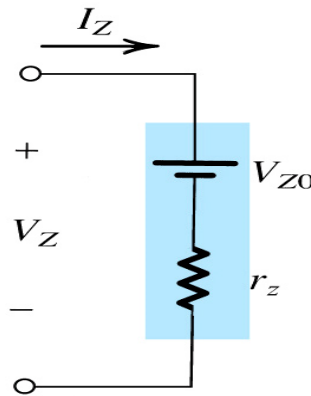

**Figure 2:**

**(9 marks)**

**Q.3(a) :** Figure 3(a) shows a half-wave rectifier circuit. The diode D can be considered ideal.

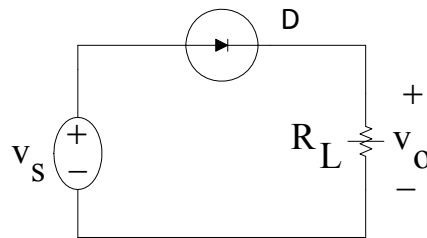


**Figure 3(a):**

Given:  $v_s(t) = 60 \cos[(120\pi t)]$  Volts and  $R_L = 100$  kilo ohms.

- Obtain the DC component of  $v_o(t)$
- What is the peak inverse voltage across the diode?

**Q.3(b):** In the system shown in **Fig.3(a)**, a capacitor of value  $10\ \mu\text{F}$  is connected across  $R_L$ , as shown in **Fig.3(b)**.

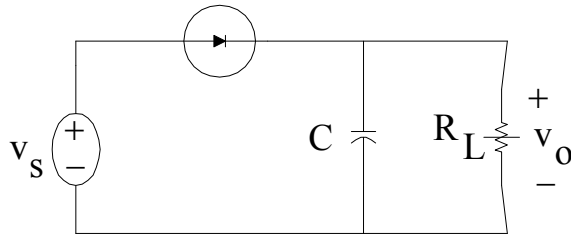


**Figure 3(b):**

- (i) Sketch the waveform of  $v_o(t)$  and label the various values. Find the *ripple* voltage.
- (ii) Determine the DC component of  $v_o(t)$ .
- (iii) What should be the new value of  $C$ , if the *ripple* found in (i) is to be reduced to half the value?

**(9 marks)**

**Q.4:** Calculate the small signal gain  $v_o/v_s$  for the BJT amplifier circuit in **Fig. 4**. Assume transistor parameters of  $\beta = 99$ ,  $V_{BE}(\text{on}) = 0.7\ \text{V}$ ,  $V_A = 50\ \text{V}$ .

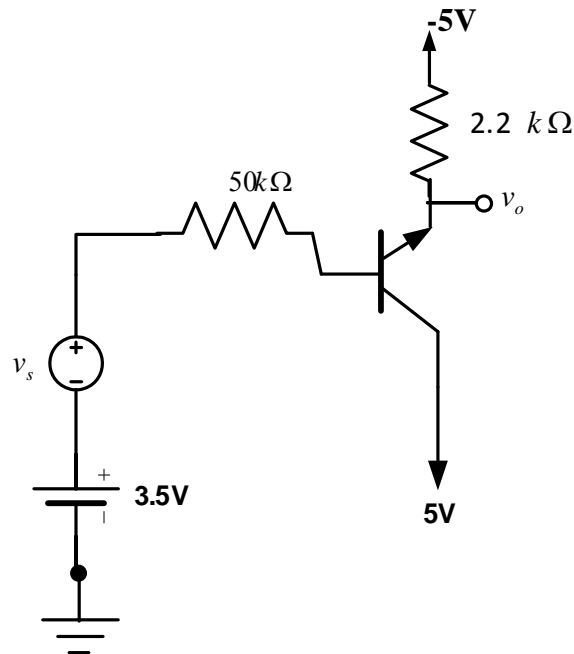


**Figure 4**

**(9 marks)**

**Q.5:** For the circuit shown in figure 5 assume that the source  $v_s$  provides a small signal  $v_{sig}$  and that the BJT has  $\beta = 49$ . Find:

(a) the input resistance  $R_{in}$ .

(b) What will be the maximum  $v_s$  value for which the small signal approximation will remain valid for the operation of the BJT?

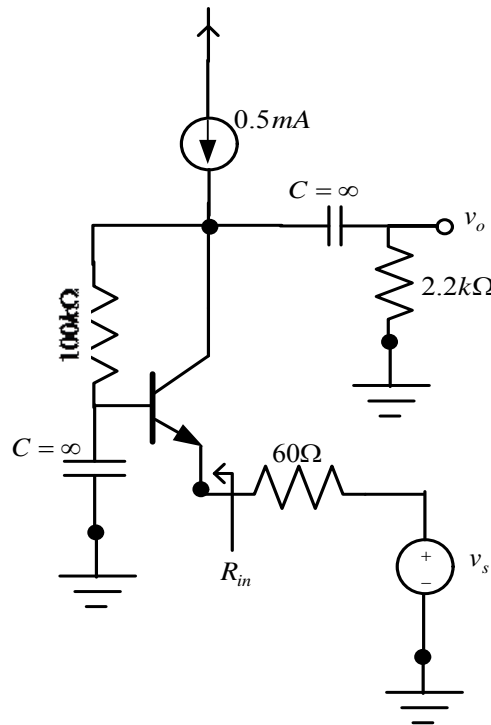

**Figure 5:**

**(9 marks)**

**Q.6:** A common emitter amplifier uses a BJT device with  $\beta = 100$ , *Early* voltage = 50 V, and is biased by a current source at  $I = 5$  mA. The amplifier operates between a voltage source with  $R_{sig} = 10,000$  ohms, and a resistance  $R_C$  of 1000 ohms at the collector. Figure 6 shows the schematic diagram.

(a) Draw the *ac* equivalent circuit and find the voltage gain of the system.

(b) What is the *small signal* current gain of the system?

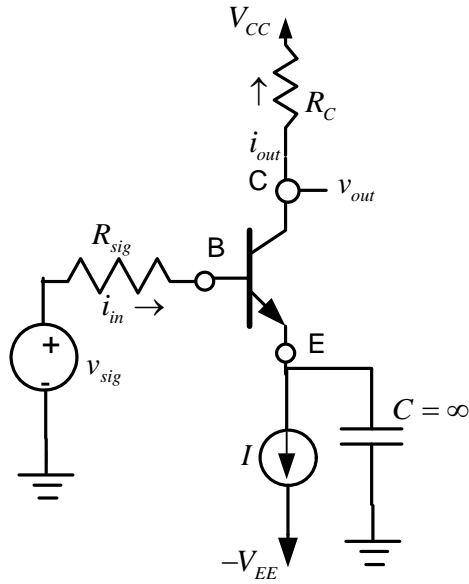


Figure 6

(9 marks)

Q.7: Consider figure 7 as the conceptual model of a MOSFET circuit operating as a common source amplifier. Given that  $V_{TH}=0.5V$ ,  $K=5 \text{ mA/V}^2$ ,  $W/L=2$ ,  $V_{GS}=0.7V$ ,  $V_{DD}=2V$ ,  $R_D=5000$  ohms, and  $V_A$  (Early voltage) =50V;

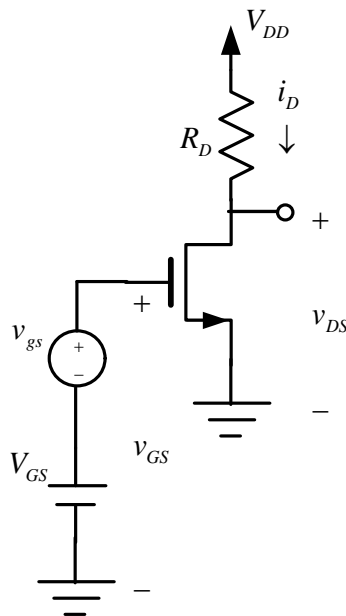



Figure 7

Calculate:

- (a) The *ac* transconductance of the MOS device
- (b) The small signal voltage gain of the system.

**(9 marks)**

**Q.8:** Figure 8 presents a common gate MOS amplifier as an integrated circuit. The transistor M0 provides a bias current of 0.5 mA. The body transconductance  $g_{mb}$  is approximately  $0.2g_m$  of the transistor M1, which is the *driver* transistor. M2 serves as an active load. Find the voltage gain  $v_o/v_{in}$  for the amplifier in terms of the *ac* equivalent circuit parameters.

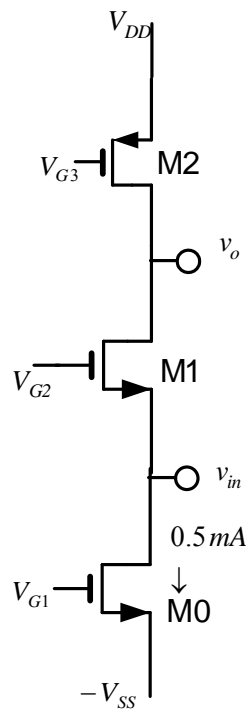

**Figure 8**

**(9 marks)**

# Examination Cover Sheet

<b>COURSE:</b> ELEC	<b>NUMBER:</b> 311	<b>SECTION(S):</b> F	
<b>EXAMINATION:</b> <input checked="" type="checkbox"/> <b>FINAL</b> <input type="checkbox"/> <b>ALTERNATE</b> <input type="checkbox"/> <b>DEFERRED</b> <b>VERSION:</b> _____	<b>DATE:</b> Dec.16, 2014	<b>TIME:</b> 14:00-17:00  <b>Exam Length:</b> 3 hours	<b>PAGES:</b> Including cover  Seven
<b>INSTRUCTOR(S):</b> R. Raut		<b>DIVISION:</b>	
<b>MATERIALS ALLOWED:</b> <input checked="" type="checkbox"/> Booklets <input type="checkbox"/> IBM (Scantron) <input type="checkbox"/> Blue <input type="checkbox"/> Green <input type="checkbox"/> Printed Translation Dictionary Other _____ <input checked="" type="checkbox"/> Calculator <input checked="" type="checkbox"/> ENCS Approved <input type="checkbox"/> Other _____		<b>INSTRUCTIONS:</b> <input checked="" type="checkbox"/> Return all <input type="checkbox"/> Answer on Exam <input type="checkbox"/> Open book <input type="checkbox"/> Crib sheet Details _____	

**Please print your name, I.D. number and section in the appropriate spaces below.**

**STUDENT NAME:** \_\_\_\_\_

**I.D. NO.** \_\_\_\_\_ **SECTION:** \_\_\_\_\_

**SPECIAL INSTRUCTIONS:**  
(on next page)

	Course <b>Electronics I</b>
	Examination <b>Final</b>
	Date <b>December 16, 2014</b>
	Instructor(s) <b>Dr.R. Raut</b>
	<p>Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)</p> <p>Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes</p> <p>Students are allowed to use ENCS faculty approved calculator</p> <p>Special Instructions:          You are required to <u>answer SIX questions</u>          You MUST attempt <b>Q.1</b> (<i>soft skill</i> component) : <b>5 marks</b>          From <b>Q.2-Q.8</b>, answer any <b>FIVE</b> questions.: <b>9 marks</b> (each)  <i>Before submitting your answer book, <b>fill in the Table below</b> in</i>  <i>(If you <b>do not fill in the Table</b>, the instructor will mark your answer book)</i>          Show all steps clearly in neat and legible handwriting.          Students are required to <i>return the question paper</i> together with</p>

**(STUDENT) NAME:**


**ID #**

**Table**

Answers to be graded	<b>Q.1 (compulsory)</b>					
Marks						

**Section I (Compulsory): Soft skill component- The student **MUST** answer this question**

**Q. 1:** Consider **figure 1**. Calculate the labeled node voltages  $V_1$  and  $V_2$ , given that the MOSFETs have  $V_{THN} = 1\text{ V}$ , and  $K \frac{W}{L} = 5\text{ mA/V}^2$ . ( 5 marks )

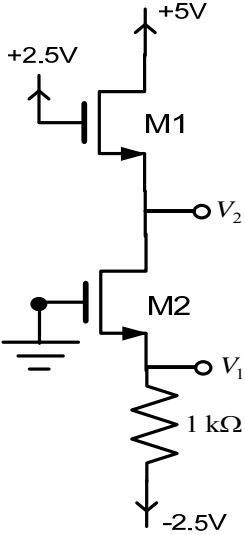

**Figure 1**


**(Some important formulae)**

BJT	$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, r_e = \frac{r_\pi}{\beta + 1},$ $I_C = I_S \exp(V_{BE} / V_T)$
MOS	$I_D = K \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ (linear region)	$I_D = K \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2$ (saturation region, excluding Early effect)	$g_m = K \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2KI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$

**Section II** (From Q.2-8, answer ONLY FIVE questions)

**Q.2:** Consider the BJT amplifier in Fig.2.

Find the DC operating points (i.e.,  $I_C$ ,  $I_E$ ) for the amplifier stage. The transistor has  $\beta=75$ . Assume  $V_{BE}=0.7V$ . **(9 marks)**

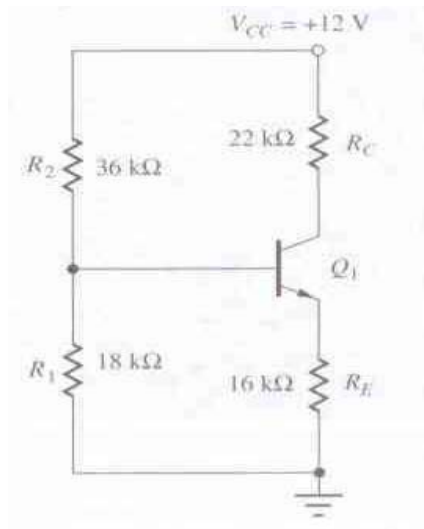


**Figure 2:**

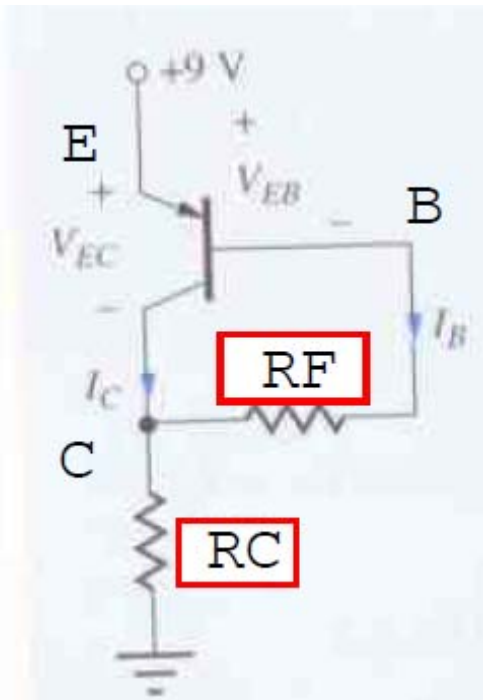
**Q.3:** In Fig.3(a) the resistor  $R_F$  and  $R_C$  establish the DC operating point for the amplifier.

(a) Design  $R_C$  and  $R_F$  so that  $I_C = 6\text{ mA}$  is achieved. Given  $V_{EB} = 0.7V$ , and  $\beta = 50$ .

(b) The amplifier of Fig 3(a) is connected between a signal voltage source  $V_S$  and a load resistance of 5000 ohms as in Fig 3(b). The terminals B,C,E in Fig. 3(b) correspond to the identical terminals in Fig. 3(a). Using the *small signal* ac equivalent circuit for the BJT find the *small* signal voltage gain  $V_O/V_S$ . The capacitors  $C_X$  and  $C_Z$  can be assumed to be very large (i.e., *infinity*) in values. **(9 marks)**



(a)

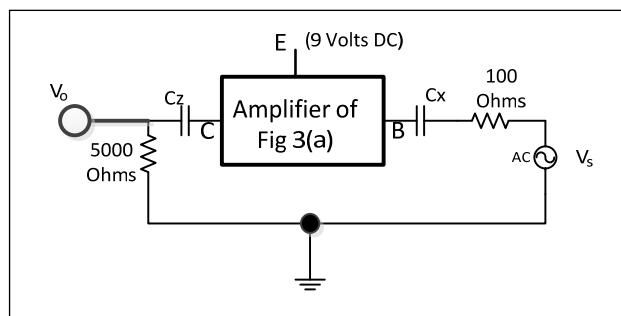

(b)

**Figure 3:**

**Q.4:** Consider the emitter-follower BJT amplifier circuit of Fig.4. Find  $R_{in}$ ,  $R_{out}$  and the voltage gain  $v_o/v_{sig}$ . Given  $R_{sig} = 10\text{ k}\Omega$ ,  $R_B = 40\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $\beta=49$ , and  $V_A = 100\text{ V}$ . The bias current source is *ideal* with  $I = 5\text{ mA}$ . Further  $V_{CC} = |-V_{EE}| = 10\text{ volts (DC)}$ .

( 9 marks)

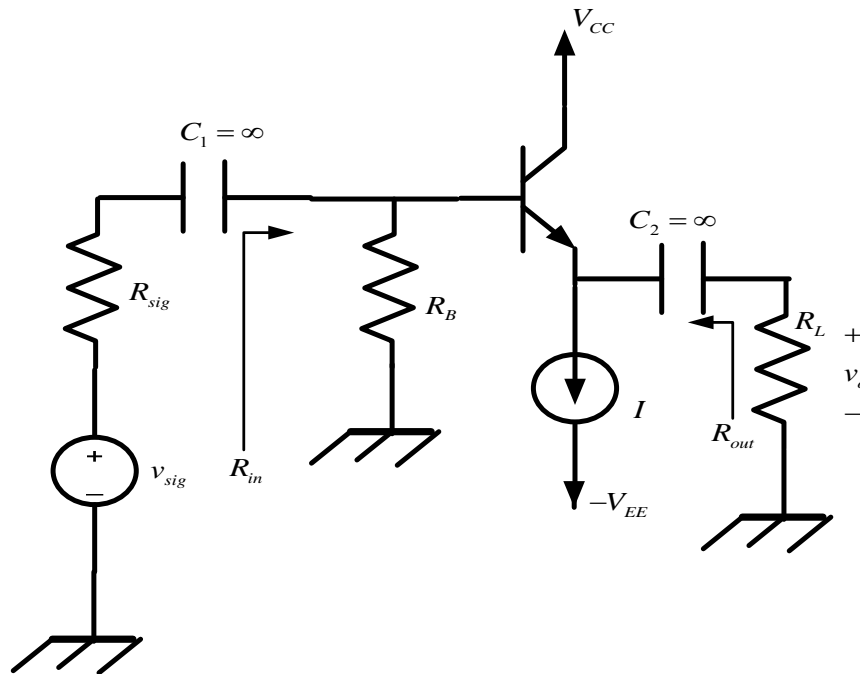


Figure 4:

(Some important formulae)


BJT	$I_C = \beta I_B, I_E = (\beta + 1)I_B$	$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m}, \alpha = \frac{\beta}{\beta + 1}$	$r_o = \frac{V_A}{I_C}, r_e = \frac{r_\pi}{\beta + 1},$ $I_C = I_S \exp(V_{BE} / V_T)$
-----	---	--	---

**Q.5:** Figure 5 shows a *common source* MOSFET amplifier circuit with the DC quantities shown alongside the schematic.

(9 marks)

(Some important formulae)

MOS	$I_D = K \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ (linear region)	$I_D = K \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2$ (saturation region, excluding Early effect)	$g_m = K \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2KI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$
-----	---	--	--

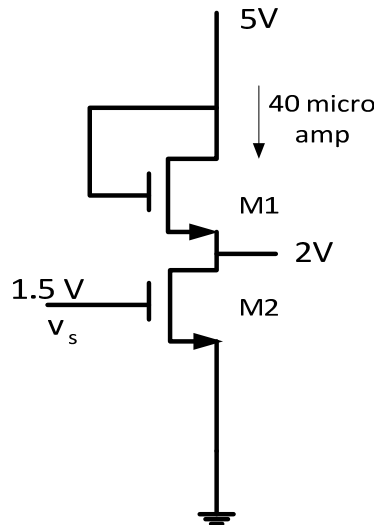

**Figure 5:**


For the NMOS transistors,  $K = 40 \mu\text{A}/\text{V}^2$ ,  $V_{\text{THN}} = 1 \text{ V}$ .

- Verify that the MOSFET is in the saturation region.
- Find the width  $W$  values for M1 and M2, given that  $L=1$  micro meters for each of the transistors.
- Draw the complete *ac* equivalent circuit associated with the schematic. Ignore the *body* transconductance.

**Q.6:** The bridge-rectifier (see Fig.6) circuit with a filter capacitor has  $R_L = 100$  ohms. The secondary transformer delivers a sinusoid of 15 V (rms) and has a frequency of 60 Hz. The diodes have  $V_{\text{DO}} = 0.7$  V each.

- What will be the value of the filter capacitor so that the ripple voltage is limited to below 500 mV peak-to-peak?
- What is the DC voltage at the output of the system?
- What is the conduction angle for each diode in the system? Explain with appropriate sketches.

**(9 marks)**

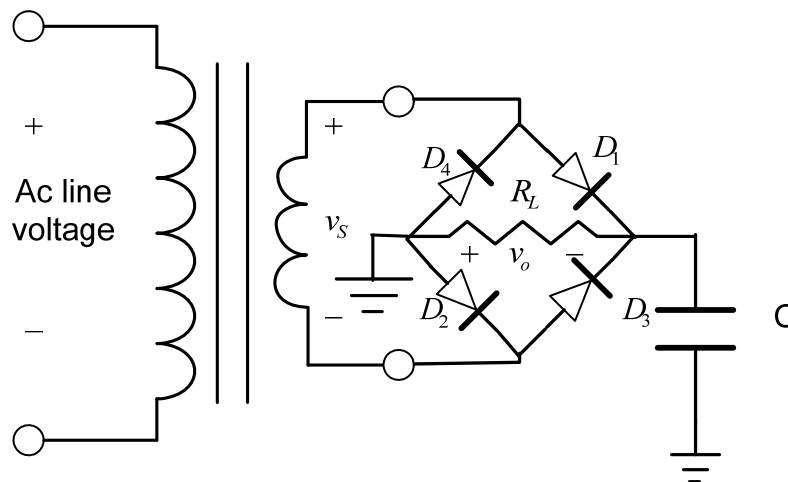

**Figure 6:**

**Q.7:** A Common Source (CS) MOSFET amplifier is biased at  $I_D = 0.25$  mA with a current source connected at the Source terminal of the MOSFET. The transistor has  $V_{OV} = 0.3$  V, and a drain resistance of  $R_D = 15$  k $\Omega$  connected to the DC supply of 15 V. The device has  $V_A = 50$  V. The amplifier is capacitively fed from a source with internal resistance  $R_{sig} = 100$  k $\Omega$ , and a 20 k $\Omega$  load is capacitively coupled to the drain of the amplifier.

- (a) Draw the schematic for the amplifier system.
- (b) Calculate the voltage gain of the system.

(9 marks)


**(Some important formulae)**

MOS	$I_D = K \left( \frac{W}{L} \right) \left( (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right)$ <p style="text-align: center;">(linear region)</p>	$I_D = K \left( \frac{W}{2L} \right) (V_{GS} - V_{TH})^2$ <p style="text-align: center;">(saturation region, excluding Early effect)</p>	$g_m = K \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) = \sqrt{\frac{2KI_D W}{L}}$ $r_o = \frac{V_A}{I_D}$
-----	---	--	---

**Q.8:** A semiconductor junction diode **D** is used in an automatic gain control system as shown in **figure 8**. The ac resistance of the diode is dependent on the amplitude of the input ac signal. The capacitance acts as a *short circuit* and the inductor acts as an *open circuit* for the ac signal.

The input signal is full-wave rectified to generate a DC voltage which drives the DC current through the diode. This DC voltage is given by  $2V_p / \pi$ , where  $V_p$  is the peak value of the signal. The diode is a 1 mA diode. For the diode you may use the relation:  $V_2 = V_1 + 2.303V_T \log_{10}(I_2 / I_1)$ , where  $V_T$  is the thermal voltage (=25 mV). The DC resistance of the diode can be neglected.

If the input ac signal has a peak amplitude of 15 volts, what will be the output ac signal amplitude  $v_o$ ? (9 marks)

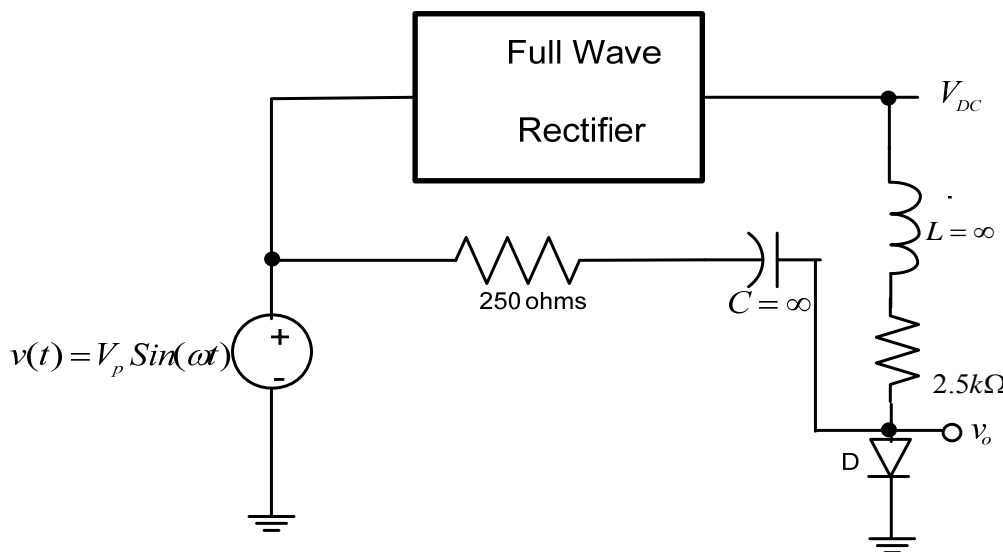

**Figure 8:**