

Name: _____

Student #: _____

Section: _____

CARLETON UNIVERSITY

FINAL
EXAMINATION
April 12, 2002

Question	Max Marks	Score
1	10	
2	20	
3	25	
4	25	
5	20	
Total	100	

Duration: 3 hours

Department name and course number: Electronics 97.257

Course Instructor(s): R. Achar, N. Tait Number of students: 380

AUTHORIZED MEMORANDA:

NON-PROGRAMMABLE CALCULATOR

Students **MUST** count the number of pages in this examination paper before beginning to write, and report any discrepancies immediately to a proctor. **This question paper has 12 pages.**

This examination question paper **MAY NOT** be taken from the examination room.

This exam consists of 5 questions, which should be answered on this exam paper in the space provided. Attempt all questions. Marks allocated to each question are indicated (total marks = 100).

Note: The solution must be clearly indicated. Multiple solutions or solutions that are not clearly identified, will be marked incorrect. Using approximate relations (unless they are given below or specified in a question) is not accepted. Clearly state all assumptions made. Clearly mark the units for final answers. **SHOW YOUR WORK!**

Diode:

Forward current: $I_D \approx I_S (e^{V_D/nV_T})$

Small signal resistance: $r_d = \frac{nV_T}{I_D}$

$V_T = \frac{kT}{q} = 25mV$ at room temperature

Bipolar Transistor:

Active mode operation: $V_{BE} = 0.7V$

Saturation mode operation: $V_{CEsat} = 0.2V$

$i_C = \beta i_B$ $i_C = \alpha i_E$ $i_E = i_B + i_C$

$g_m = \frac{I_C}{V_T}$ $r_\pi = \frac{\beta}{g_m}$ $r_o = \frac{V_A}{I_C}$

$r_e = \frac{\alpha}{g_m} = \frac{r_\pi}{\beta + 1}$ $\alpha = \frac{\beta}{\beta + 1}$

Operational Amplifier:

$V_o = A(V_+ - V_-)$; $R_i = \infty$; $R_o = 0$

MOSFET:

$I_{DS} = k' \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$

$I_{DS} = k' \frac{W}{L} \frac{(V_{GS} - V_T)^2}{2}$ $k' = \mu C_{ox}$

$V_{DS,sat} = V_{GS} - V_T$ $g_{mb} = \chi g_m$

$g_m = k' \frac{W}{L} (V_{GS} - V_T) = \sqrt{2k' \frac{W}{L} I_{DS}}$

$r_{DS,triode} = \left[k' \frac{W}{L} (V_{GS} - V_T) \right]^{-1}$; $r_o = \frac{V_A}{I_D}$

1) -A) Answer the following questions by filling in the corresponding circles with your selection *a or b or c or d (5 marks)*.

(i) An important advantage of bipolar transistors over MOS transistors is that,

- a) they have higher transconductance
- b) they have higher input impedance
- c) they have higher electron mobility
- d) they emit light when biased.

(ii) For a PMOS enhancement transistor to be in triode mode

- a) $V_{GS} > V_T; V_{DS} < V_{GS} - V_T$
- b) $V_{GS} > V_T; V_{DS} > V_{GS} - V_T$
- c) $V_{GS} < V_T; V_{DS} < V_{GS} - V_T$
- d) $V_{GS} < V_T; V_{DS} > V_{GS} - V_T$

(iii) The buffer (impedance matching) stages in electronic circuits can be designed with

- a) Common Emitter Configurations using BJTs
- b) Common Base Configurations using BJTs
- c) Common Collector Configurations using BJTs
- d) Common Gate Configurations using FETs

(iv) In general, the open circuit voltage gain of a common base amplifier configuration

- a) is independent of bias current
- b) is independent of load resistance
- c) is larger than unity
- d) is smaller than unity

(v) A common use for a current mirror circuit is


- a) to turn on diodes in AC rectifiers
- b) to act as gates in logic circuits
- c) to decrease the input resistance of small signal amplifier circuits
- d) to bias transistors in integrated circuits

1) -B) Answer the following questions by entering TRUE or FALSE in the space provided **(5 marks)**.

- i) A p-channel MOSFET uses a n-type substrate or well. _____
- ii) Conduction in a MOSFET channel is due primarily to majority carriers. _____
- iii) Early effect is generally used estimate the input impedance of transistors. _____
- iv) In saturation, the collector current in a bipolar transistor is mainly controlled by V_{CE} . _____
- v) A reverse biased diode acts like a voltage dependent capacitor. _____

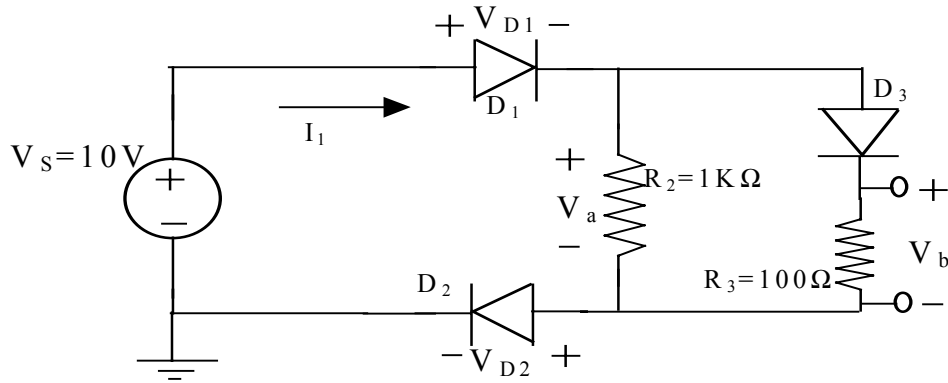- 2) **Diodes:** For the circuit shown below, the following data is given:
Both diodes D_1 and D_2 have $n = 1.75$ and their reverse saturation currents are such that $I_{s1} = 10I_{s2}$.
The forward drop across diode D_1 is given to be $V_{D1} = 0.7V$.

The diode D_3 is represented by linear piecewise model [Battery = $0.7V$, Resistance = $60\ \Omega$].



Using the above data, compute the following (12 marks):

i) Find V_{D2} :

$V_{D2} =$ _____

ii) Find V_a :


$V_a =$ _____

ii) Find V_b :


$V_b =$ _____

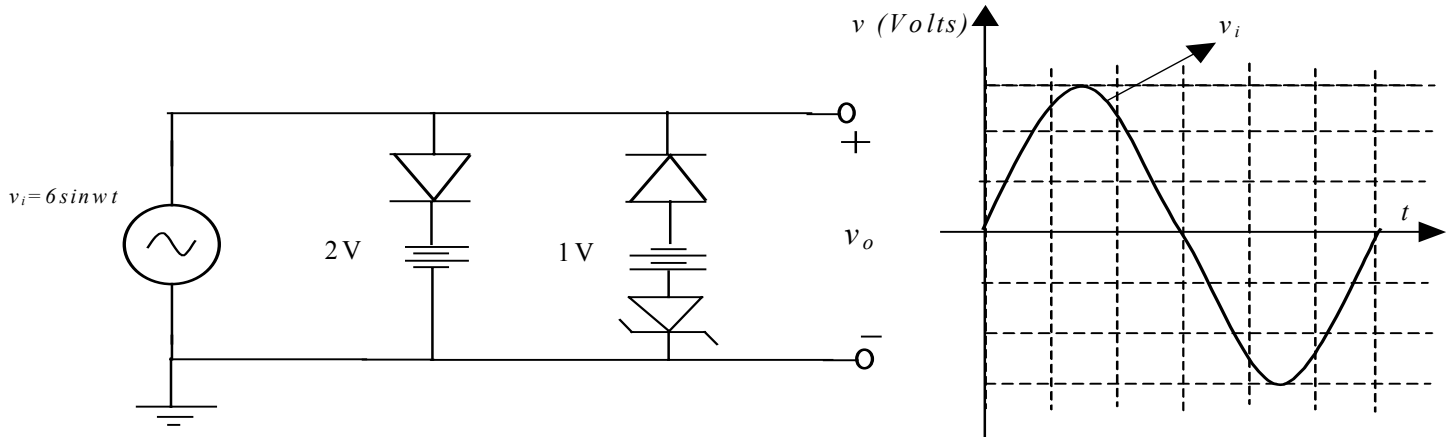1) b) **Diodes (continued...):**

In the following circuit, assume that the diodes D_1 and D_2 are ideal and the zener diode D_3 has a reverse breakdown voltage of 3Volts. If the input is $V_i = 6\sin(\omega t)$, what are the Peak-to-peak values for the output voltage? Sketch the output waveform on the graph shown on left side. **(4 Marks)**.




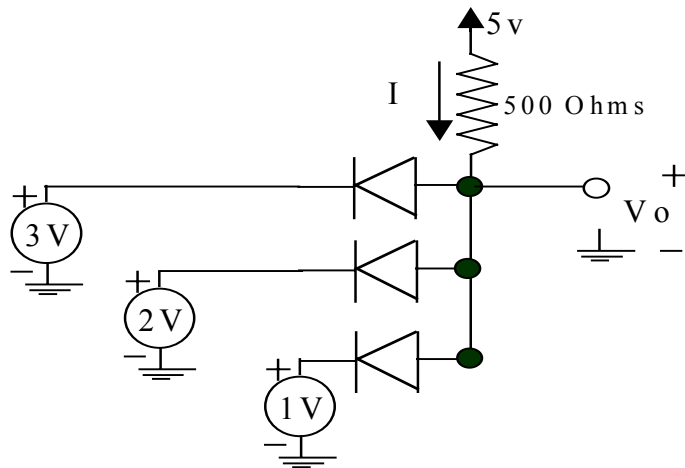c) Assuming that the forward drop across the diodes is 0.5Volts, what is the value of the current I and output voltage V_o in the following circuit? **(4 Marks)**



$I =$ _____
 $V_o =$ _____

3.) **Bipolar Junction Transistor**

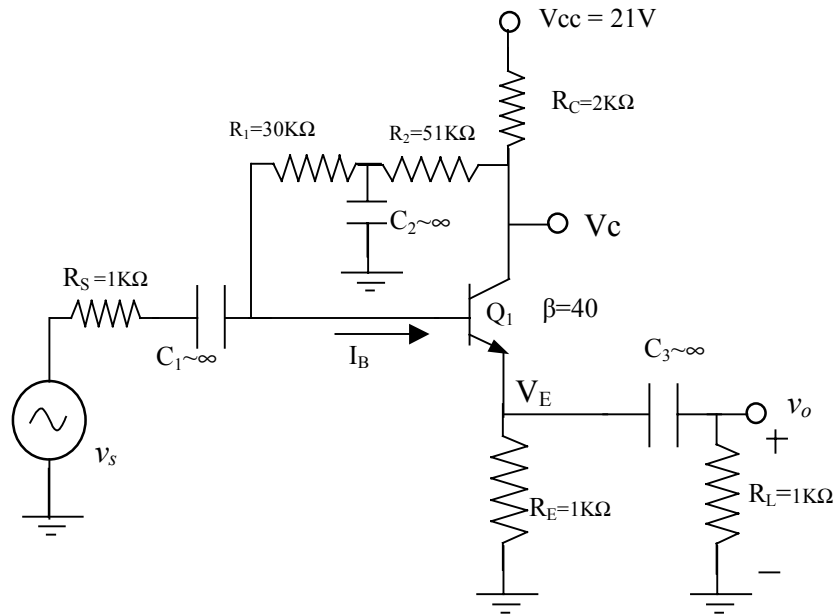

a) For the circuit shown above: i) Draw the D. C. Equivalent Circuit (2 Marks)


ii) Compute I_B , V_C and V_{CE} (8 Marks)

$I_B =$ _____

$V_C =$ _____

$V_{CE} =$ _____

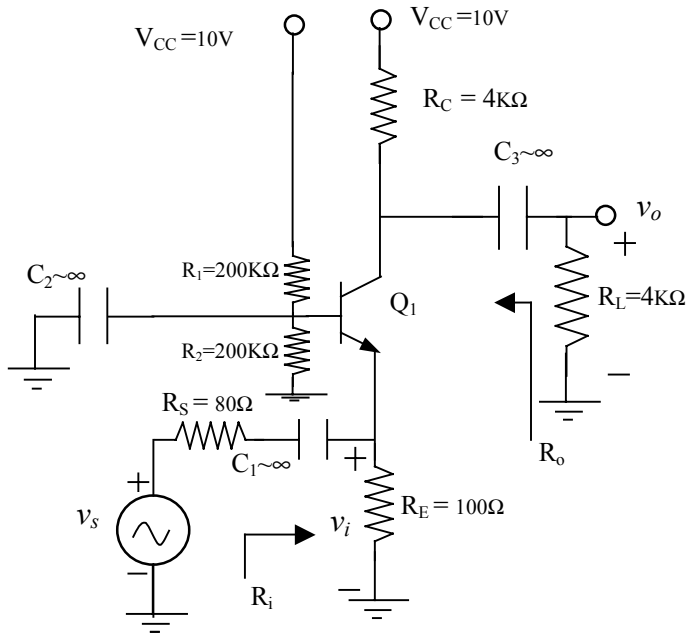3) b) **Bipolar Junction Transistor** (continued....)



For the BJT, assume that $r_e = 25$ Ohms and $\beta=50$. Using these data, answer the following:

i) Draw the equivalent circuit for small signal AC analysis (*preferably, use T-Model for BJT*) (3 marks)

ii) Find the output resistance R_o , input resistance R_i for the circuit (3 marks):

$R_o =$ _____

$R_i =$ _____


- iii) Find the voltage gain $A_{v1}=v_i/v_s$, voltage gain $A_{v2}=v_o/v_i$ and the overall voltage gain $A_v=v_o/v_s$.
Show the derivation of necessary expressions in your computations (9 marks):

$$A_{v1} = \underline{\hspace{2cm}}$$

$$A_{v2} = \underline{\hspace{2cm}}$$

$$A_v = \underline{\hspace{2cm}}$$

4) **MOSFET.**

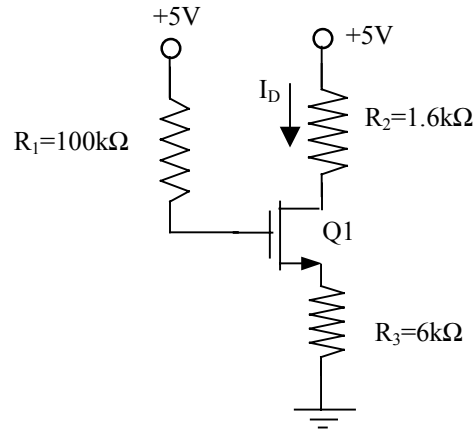

a) In the figure above, the transistor has $V_t=1V$, $V_A=30V$, $k_n'=100\mu A/V^2$, $L=1\mu m$ and $W=10\mu m$.


i) Find the bias current I_D (5 marks):

$I_D =$ _____

ii) Verify the mode of operation of the transistor and state what mode the transistor is in (3 marks):

Mode = _____

4) b) MOSFET (continued....)

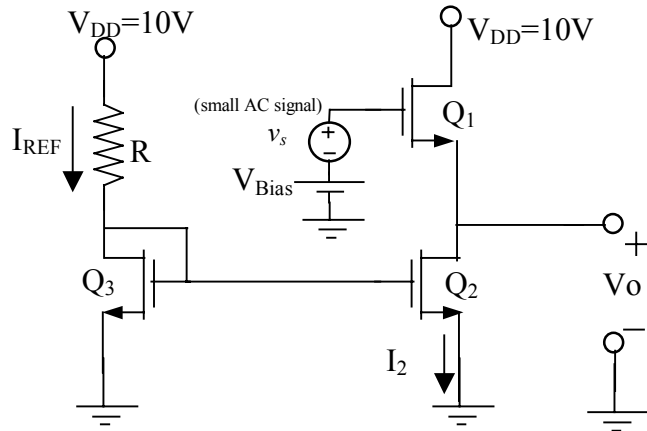

For the figure on the left, the transistors have

$V_t=1V, V_A=30V,$
 $k_n'=100\mu A/V^2,$
 $L_1=1\mu m, W_1=10\mu m,$
 $L_2=1\mu m,$
 $L_3=1\mu m, W_3=10\mu m.$

Using these data compute the following:

i) If $I_{REF}=1mA$, find R (5 marks):

R = _____

ii) If $I_2=0.5mA$, find W_2 (3 marks):

$W_2 =$ _____

iii) What is the minimum value of V_o for which $I_2=0.5mA$ (3 marks):

Minimum $V_o =$ _____

Name: _____
97.257

Student #: _____
Final Examination, April 12 2002


Section: _____
Page: 10/10

iv) Draw the small signal equivalent circuit (2 marks):

v) If $I_2=0.5\text{mA}$, $\chi=0.1$ and Q_1 is in saturation, find $A_v=v_o/v_s$ (4 marks):

$A_v =$ _____


5) Operational Amplifier

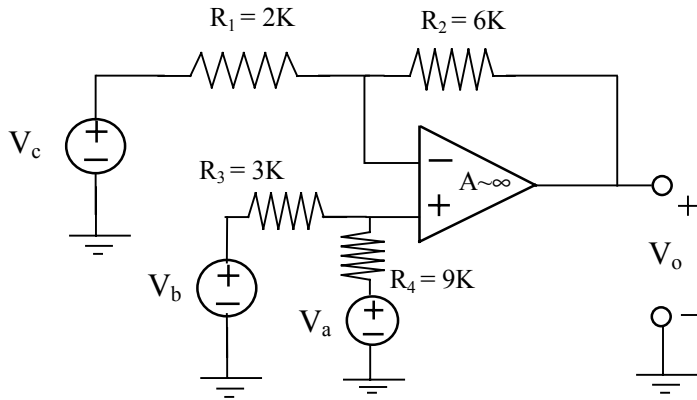

- a) For the circuit shown, find the expression for V_o as a function of V_a , V_b and V_c (assume the op amp is ideal) (10 Marks)

$V_o =$ _____

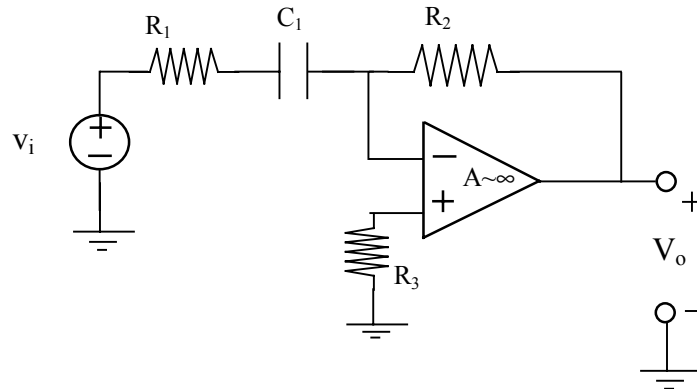5) b) Operational Amplifier (continued....)



i) For the above circuit, assuming ideal op-amp, derive the gain $H(j\omega) = V_o(j\omega) / V_i(j\omega)$. Show the steps. **(6 Marks)**

ii) If $R_1 = 5K\Omega$, $R_2 = 15K\Omega$, $R_3 = 10K\Omega$, $C_1 = 1\mu F$ and frequency is 1MHz, compute the gain-magnitude in DBs and gain-phase in degrees. **(3 Marks)**

$|H(j\omega)| =$ _____ DBs

$\angle H(j\omega) =$ _____ Degrees

iii) What class of filter does the above circuit belong to? **(1 Mark)**
