

Name: R Achar

Student #: _____

Section: _____

SOLUTIONS

CARLETON UNIVERSITY

**FINAL EXAMINATION
April 12, 2002**

Question	Max Marks	Score
1	10	
2	20	
3	25	
4	25	
5	20	
Total	100	

Duration: 3 hours

Department name and course number: **Electronics 97.257**

Course Instructor(s): **R. Achar, N. Tait** Number of students: **380**

AUTHORIZED MEMORANDA:

NON-PROGRAMMABLE CALCULATOR

Students **MUST** count the number of pages in this examination paper before beginning to write, and report any discrepancies immediately to a proctor. **This question paper has 12 pages.**

This examination question paper MAY NOT be taken from the examination room.

This exam consists of 5 questions, which should be answered on this exam paper in the space provided. Attempt all questions. Marks allocated to each question are indicated (total marks = 100).

Note: The solution must be clearly indicated. Multiple solutions or solutions that are not clearly identified, will be marked incorrect. Using approximate relations (unless they are given below or specified in a question) is not accepted. Clearly state all assumptions made. Clearly mark the units for final answers. **SHOW YOUR WORK!**

Diode:

Forward current: $I_D \approx I_S (e^{V_D/nV_T})$

Small signal resistance: $r_d = \frac{nV_T}{I_D}$

$V_T = \frac{kT}{q} = 25mV$ at room temperature

Bipolar Transistor:

Active mode operation: $V_{BE} = 0.7V$

Saturation mode operation: $V_{CE(sat)} = 0.2V$

$i_c = \beta i_b$ $i_c = \alpha i_e$ $i_E = i_B + i_C$

$g_m = \frac{I_C}{V_T}$ $r_\pi = \frac{\beta}{g_m}$ $r_o = \frac{V_A}{I_C}$

$r_c = \frac{\alpha}{g_m} = \frac{r_\pi}{\beta + 1}$ $\alpha = \frac{\beta}{\beta + 1}$

Operational Amplifier:

$V_o = A(V_i - V_-)$; $R_i = \infty$; $R_o = 0$

MOSFET:

$I_{DS} = k' \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$

$I_{DS} = k' \frac{W}{L} \frac{(V_{GS} - V_T)^2}{2}$ $k' = \mu C_{ox}$

$V_{DS(sat)} = V_{GS} - V_T$ $g_{m0} = \chi \chi_m$

$g_m = k' \frac{W}{L} (V_{GS} - V_T) = \sqrt{2k' \frac{W}{L} I_{DS}}$

$r_{DS(sat)} = \left[k' \frac{W}{L} (V_{GS} - V_T) \right]^{-1}$; $r_o = \frac{V_A}{I_D}$

1) -A) Answer the following questions by filling in the corresponding circles with your selection *a* or *b* or *c* or *d* (5 marks).

(i) An important advantage of bipolar transistors over MOS transistors is that,

a

- a) they have higher transconductance
- b) they have higher input impedance
- c) they have higher electron mobility
- d) they emit light when biased.

(ii) For a PMOS enhancement transistor to be in triode mode

d

- a) $V_{GS} > V_T; V_{DS} < V_{GS} - V_T$
- b) $V_{GS} > V_T; V_{DS} > V_{GS} - V_T$
- c) $V_{GS} < V_T; V_{DS} < V_{GS} - V_T$
- d) $V_{GS} < V_T; V_{DS} > V_{GS} - V_T$

(iii) The buffer (impedance matching) stages in electronic circuits can be designed with

c

- a) Common Emitter Configurations using BJTs
- b) Common Base Configurations using BJTs
- c) Common Collector Configurations using BJTs
- d) Common Gate Configurations using FETs

(iv) In general, the open circuit voltage gain of a common base amplifier configuration

c, b

- a) is independent of bias current
- b) is independent of load resistance
- c) is larger than unity
- d) is smaller than unity

(v) A common use for a current mirror circuit is

d


- a) to turn on diodes in AC rectifiers
- b) to act as gates in logic circuits
- c) to decrease the input resistance of small signal amplifier circuits
- d) to bias transistors in integrated circuits

1) -B) Answer the following questions by entering TRUE or FALSE in the space provided (5 marks).

- i) A p-channel MOSFET uses a n-type substrate or well. TRUE
- ii) Conduction in a MOSFET channel is due primarily to majority carriers. TRUE
- iii) Early effect is generally used estimate the input impedance of transistors. FALSE
- iv) In saturation, the collector current in a bipolar transistor is mainly controlled by V_{CE} . FALSE
- v) A reverse biased diode acts like a voltage dependent capacitor. TRUE

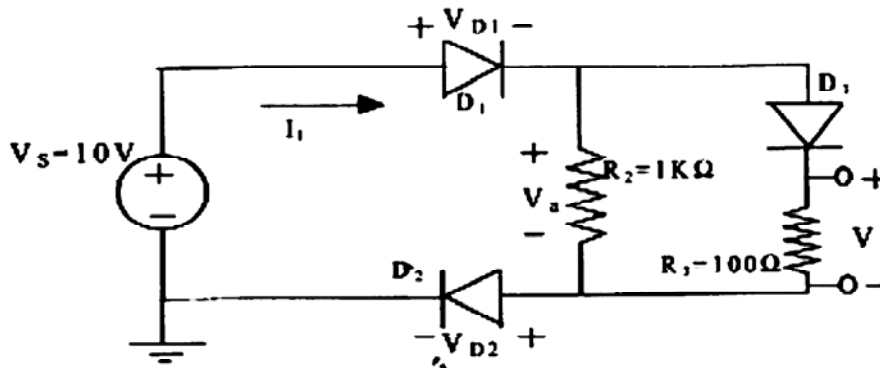2) **Diodes:** For the circuit shown below, the following data is given:
Both diodes D_1 and D_2 have $n = 1.75$ and their reverse saturation currents are such that $I_{s1} = 10I_{s2}$.
The forward drop across diode D_1 is given to be $V_{D1} = 0.7V$.

The diode D_3 is represented by linear piecewise model [Battery = $0.7V$, Resistance = $60\ \Omega$].



Using the above data, compute the following (12 marks):

i) Find V_{D2} : Given: $n = 1.75$, $I_{s1} = 10I_{s2}$, $V_{D1} = 0.7$ $V_{D2} = \underline{0.8}$


As $I_{D1} = I_{D2}$
 $I_{s1} e^{V_{D1}/nV_T} = I_{s2} e^{V_{D2}/nV_T}$
 $\frac{I_{s1}}{I_{s2}} = e^{(V_{D2} - V_{D1})/nV_T}$

$nV_T \cdot \ln[10] = V_{D2} - V_{D1}$
 $V_{D2} = V_{D1} + nV_T \ln[10]$
 $= 0.7 + 1.75 \times 25 \times 10^{-3} \times 2.3$
 $= 0.7 + 0.1 = \underline{0.8V}$

ii) Find V_a : KVL for the first loop: $V_a = \underline{8.5V}$

$V_s - V_{D1} - V_a - V_{D2} = 0$
 $\therefore 10 - 0.7 - 0.8 = V_a$
 $V_a = 8.5V$



ii) Find V_b : $V_b = \underline{4.88V}$

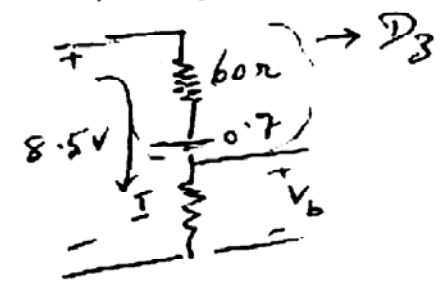

$I = \frac{8.5 - 0.7}{60 + 100}$
 $= \frac{7.8}{160} = 0.0488$
 $\therefore V_b = 100 \times 0.0488 = \underline{4.88V}$

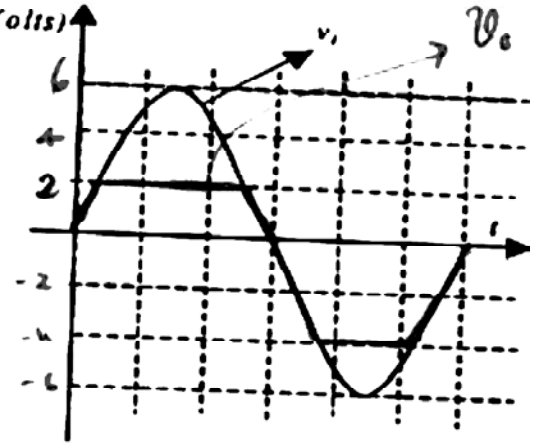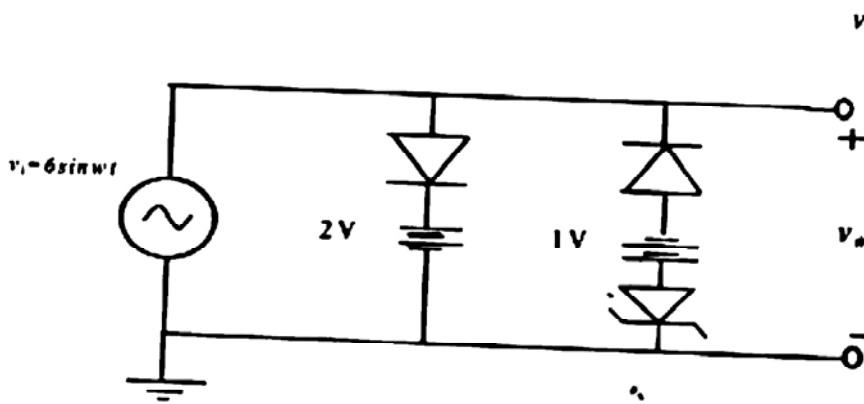
1) b) Diodes (continued...):

In the following circuit, assume that the diodes D_1 and D_2 are ideal and the zener diode D_3 has a reverse breakdown voltage of 3Volts. If the input is $V_i = 6\sin(\omega t)$, what are the Peak-to-peak values for the output voltage? Sketch the output waveform on the graph shown on left side. (4 Marks).



$V_o \rightarrow +2 \text{ v} \quad \text{to} \quad -4 \text{ v}$

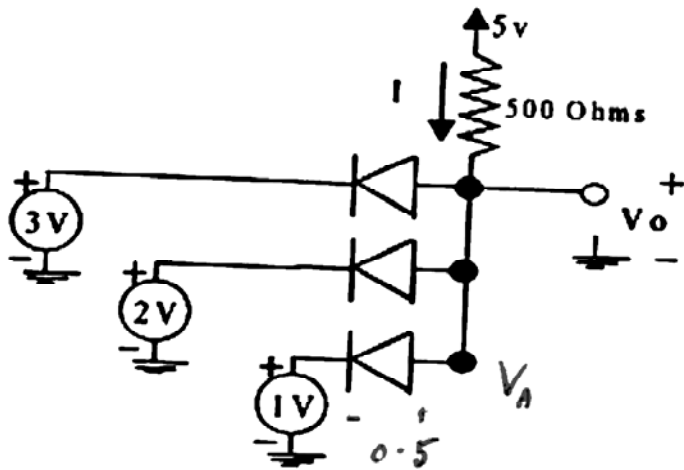c) Assuming that the forward drop across the diodes is 0.5Volts, what is the value of the current I and output voltage V_o in the following circuit? (4 Marks)




$V_A = 0.5 + 1V = 1.5V = V_o$


$I = \frac{5V - 1.5V}{500\Omega} = \frac{3.5}{500} = 0.7 \times 10^{-2} = \underline{7mA}$

$I = \underline{7mA}$
 $V_o = \underline{1.5V}$

3.) Bipolar Junction Transistor

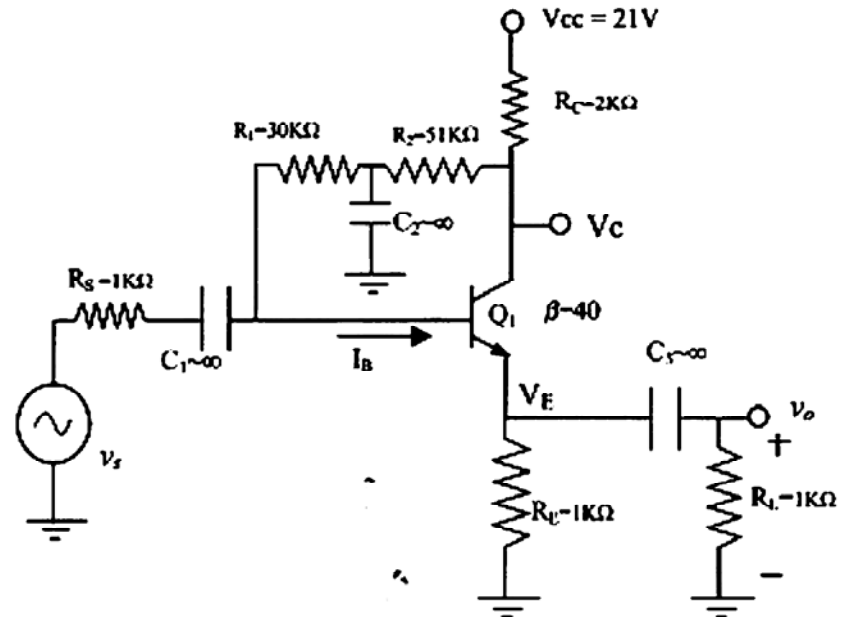

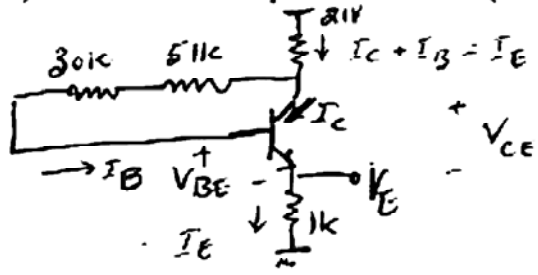a) For the circuit shown above: i) Draw the D. C. Equivalent Circuit (2 Marks)



ii) Compute IB, VC and VCE (8 Marks)

$$V_{CC} - (I_C + I_B) R_C - I_B (R_1 + R_2) - V_{BE} - I_E R_E = 0$$

$$V_{CC} - V_{BE} = I_B (R_1 + R_2) + (\beta + 1) I_B (R_E + R_C) = 0$$

$$I_B = \frac{21 - 0.7}{30k + 51k + 41(2k)} = \frac{20.3}{204k} = 0.0995 \text{ mA} \approx 0.1 \text{ mA} \quad I_B = \underline{0.0995 \text{ mA}}$$


$$I_C = \beta I_B = 40 \times 0.0995 \times 10^{-3} = 3.98 \text{ mA} \approx 4 \text{ mA} \quad V_C = \underline{12.8 \text{ V}}$$

$$I_E = (\beta + 1) I_B = 41 \times 0.0995 \times 10^{-3} = 4.08 \text{ mA} \approx 4.1 \text{ mA} \quad V_{CE} = \underline{8.76 \text{ V}}$$

$$V_C = V_{CC} - (I_C + I_B) R_C = 21 - 4.08 \times 2 = 12.84 \text{ V} \approx 12.8 \text{ V}$$


$$V_{CE} = V_C - V_E = V_C - I_E R_E = 12.84 - 4.08 = \underline{8.76 \text{ V}}$$

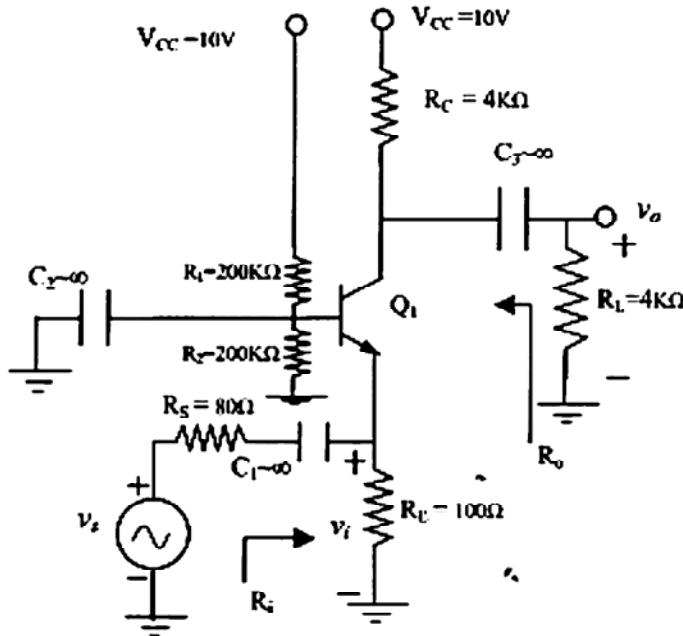3) b) Bipolar Junction Transistor (continued....)



For the BJT, assume that $r_e = 25 \text{ Ohms}$ and $\beta = 50$. Using these data, answer the following:

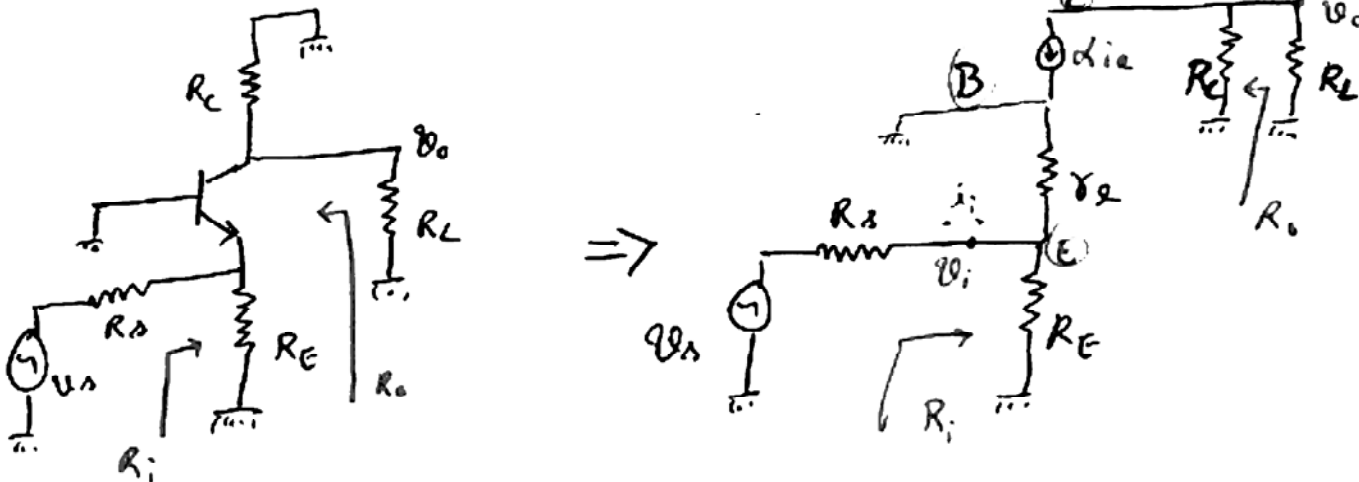i) Draw the equivalent circuit for small signal AC analysis (preferably, use T-Model for BJT) (3 marks)




ii) Find the output resistance R_o , input resistance R_i for the circuit (3 marks):

$$R_o = R_c = 4 \text{ k}\Omega$$

$$R_o = \underline{4 \text{ k}\Omega}$$

$$\underline{R_i} = \frac{v_i}{i_i}$$

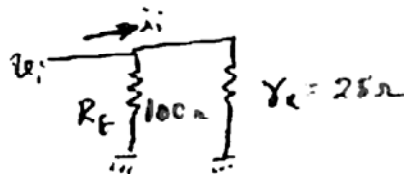

$$R_i = \underline{20 \Omega}$$

$$= R_c \parallel r_e = \frac{100 \times 25}{100 + 25} = \underline{20 \Omega}$$