

Carleton University: Department of Electronics
ELEC 3509 Midterm Exam

October 26, 2012

Prof. J. Rogers (jrogers@doe.carleton.ca)


Duration: 1 hour

Total 25 Marks

Instructions:

- This is a closed book exam.
- Attempt all questions.
- Unless otherwise stated, use the simplified hybrid- π or T-model for all analysis (i.e. $r_{\mu} = r_o = \infty$ for both Q_1 and Q_2).
- Show all analysis and assumptions that you make.

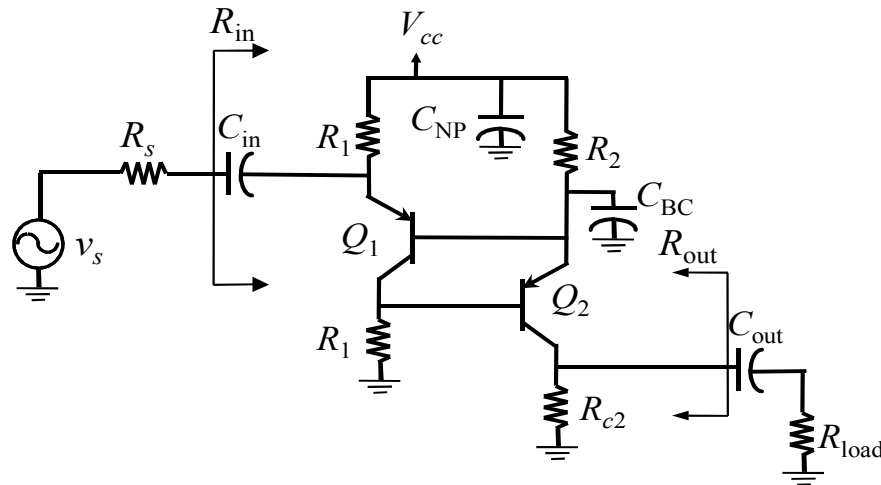- 1) Draw the small-signal equivalent circuit. (3 marks).
- 2) Find the mid-band gain A_v . (4 marks)
- 3) Find the mid-band R_{in} . (2 marks)
- 4) Find the mid band R_{out} (include r_{o2} and $r_{\mu2}$). (4 marks)
- 5) Find the ω_L 's for C_{in} , C_{NP} , C_{BC} , and C_{out} . (4 marks)
- 6) Find the ω_H 's for the circuit. (4 marks)
- 7) Assume that $V_{cc} = 15V$, $V_{CEsat} = 0.7V$, and $\beta = \text{big}$. Set the values of all resistors necessary so that the collector current in Q_1 is 1mA and the collector current in Q_2 is 2mA. After this is done maximize the output swing. (4 marks)



$$r_{\pi} = \frac{\beta}{g_m}, r_{\pi} = (\beta + 1)r_e, \alpha = \frac{\beta}{\beta + 1}, g_m = \frac{I_C}{V_T}, V_T = 25mV @ 20^{\circ}C. \omega_L \approx \omega_{L1} + \omega_{L2} + \omega_{L3} + \dots \text{ and}$$

$$\frac{1}{\omega_H} \approx \frac{1}{\omega_{H1}} + \frac{1}{\omega_{H2}} + \frac{1}{\omega_{H3}} + \dots \text{ Miller's Theorem: } Y_1 = Y \left(1 - \frac{v_2}{v_1} \right), Y_2 = Y \left(1 - \frac{v_1}{v_2} \right) I_c = I_s e^{\frac{V_{BE}}{V_T}}$$