

# EECE 376

## Electromechanics

Spring 2015

Instructor: Dr. Juri Jatskevich

Class Webpage: <http://courses.ece.ubc.ca/eece376>

### Module 3 (Read Chap. 3):

### Part 1: Brushed DC Motors Fundamentals and Steady-State Analysis

#### Learning Objectives & Important Topics and Concepts

- Construction of DC machines, fundamentals
- Induced voltage and torque
- Equivalent circuit
- Basic types of dc machines, their characteristics
- Starting

1

## DC Machines

### Range of Sizes

- Miniature dc motors – mW range
- Fractional HP (1HP = 746W)
- Medium Size – 1 ... 500 HP
- Large DC Machines – 500 HP and up

### Applications

- Very popular and easy to use in various applications
- Tools, robotics, toys, medical, automotive & other industries

### General Properties

- Very easy to control !
- Good torque-speed performance
- Brushes is a weak point of design
  - Limits the application
  - Limits the lifetime
  - Maintenance

Small Motors



Gear-head Motors 2

# Motor (Machine) Speed

Transmitting power through the mechanical shaft

Source

(Prime Mover)

Load



Commonly used units of speed

$$\omega_m - [\text{rad/sec}]$$

$$m = \frac{\omega}{2\pi} [\text{rev/sec}]$$

$$n = 60 \frac{\omega}{2\pi} = \frac{30}{\pi} \omega [\text{rev/min}]$$

RPM = >Most commonly used

3

# Mechanical Speed and Torque

Electric Motor

Mechanical Load



Electromagnetic torque  $T_e$

Useful mechanical torque on the shaft  $T_m$


Torque balance 
$$T_e = J \frac{d\omega_r}{dt} + T_m + T_{mech\_loss}$$

Total moment of inertia (motor and load combined) 
$$J = J_{dc\_machine} + J_{mech\_load}, \quad [\text{kg} \cdot \text{m}^2]$$

Mechanical loss (friction) 
$$T_{mech\_loss} = T_{fric} = D_m \omega_r$$

4


# DC Machine Motoring and Generating

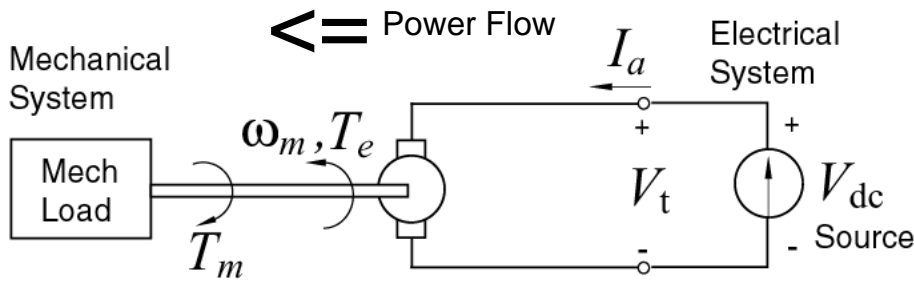

Mechanical load torque is applied in the direction opposite to rotation

$$P_{out} = \omega_m T_m = P_m$$

$$V_t I_a = P_{in}$$

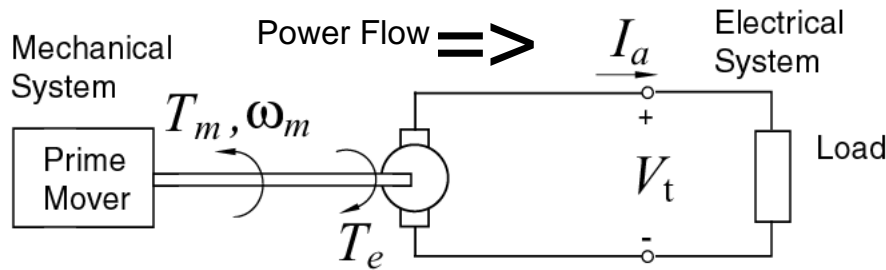



Mechanical torque is applied in the direction of rotation

$$P_{in} = \omega_m T_m = P_m$$

$$V_t I_a = P_{out}$$

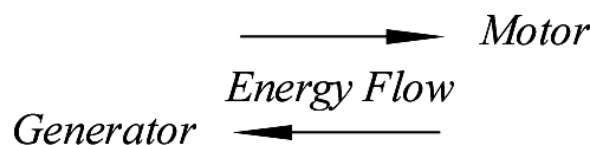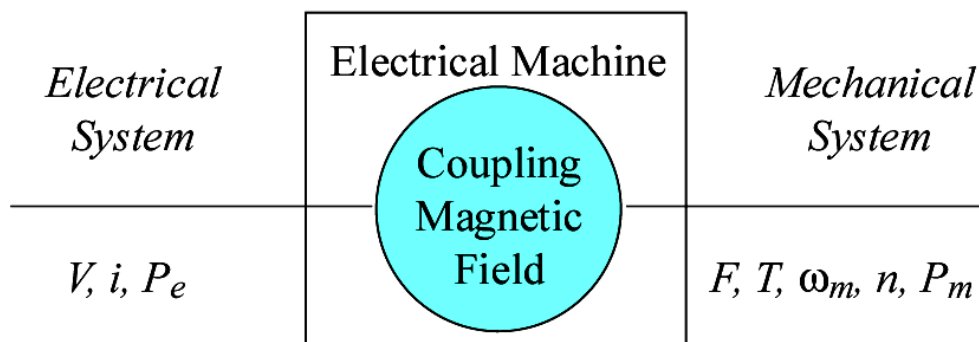
## Electromechanical Interaction

- Current-carrying conductor in magnetic field  
=> mechanical force
- Conductor moves in magnetic field  
=> voltage induced, emf



# Force & Torque

Consider a conductor frame (single-coil)

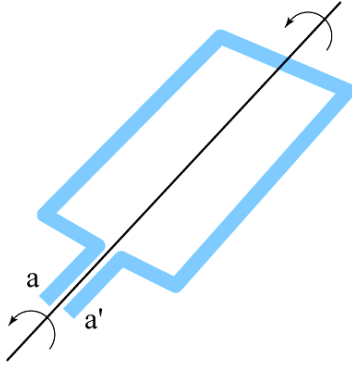


Lorentz Force  $F = lBi_a$

Torque  $T_e = 2RlBi_a \cos(\theta)$   
 $= ABi_a \cos(\theta) = \Phi_p i_a \cos(\theta)$

NOTE: Maximum torque is when  $a - axis \perp B$


and  $T_e \sim \Phi_p i_a$

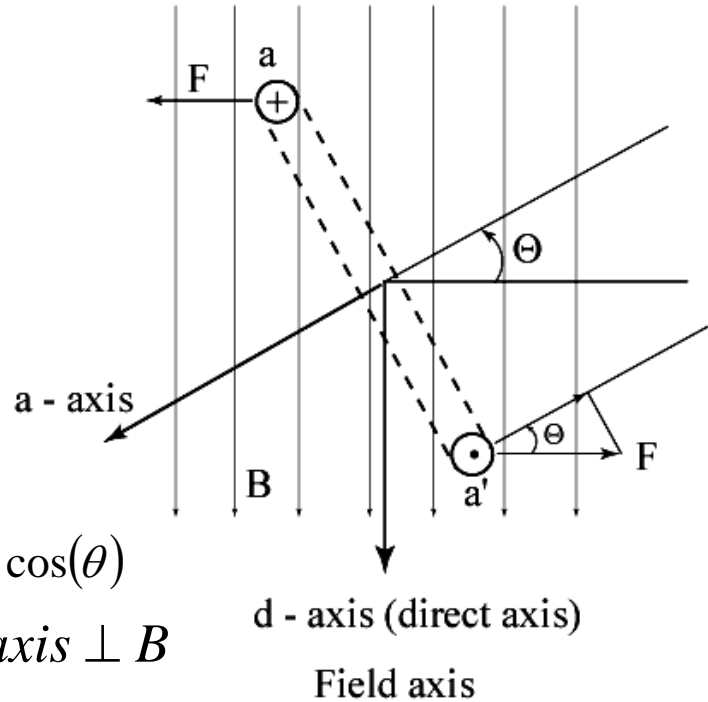

7

# Induced Voltage

Consider a conductor frame (single-coil)

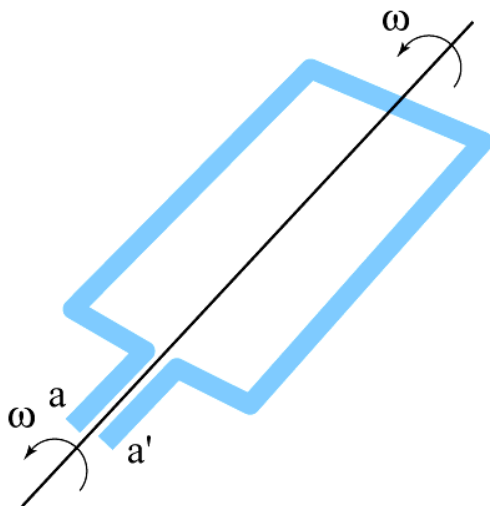

Faraday's Law  $e = \frac{d\Phi}{dt}$

$$\Phi = BA \sin(\theta) = B2Rl \sin(\theta)$$

Let us rotate the frame with speed  $\omega$

$$\theta = \omega t$$


$$\Phi = BA \sin(\omega t) = \Phi_p \sin(\omega t)$$

$$e = \frac{d\Phi}{dt} = \omega \Phi_p \cos(\omega t) \Rightarrow e \sim \omega \Phi_p$$

8

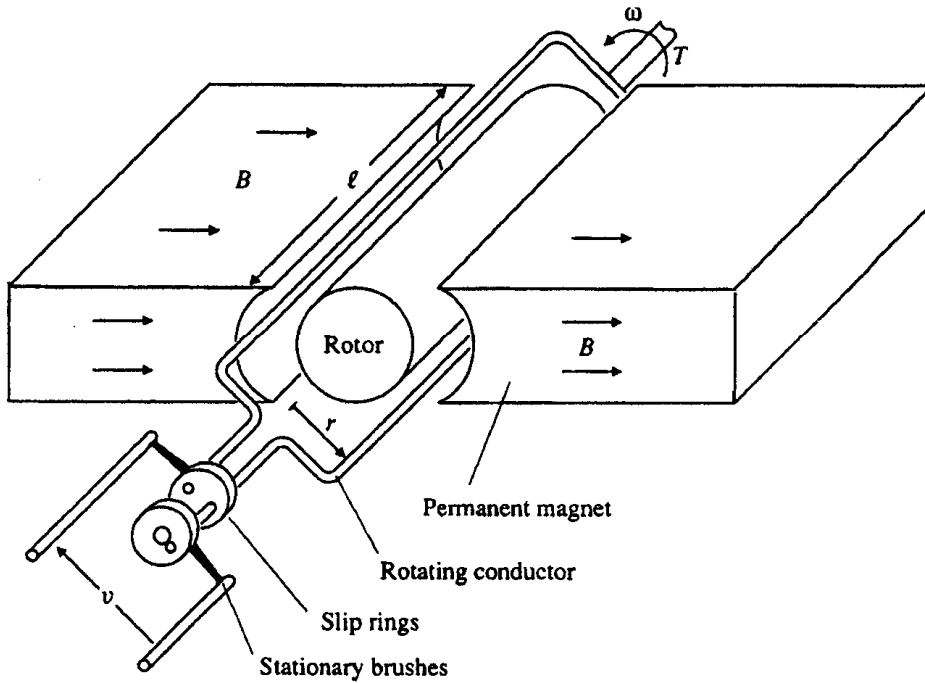
# Conductor Frame (1-turn coil)

Consider a conductor frame placed on a rotor between magnetic poles



# Elementary DC Machine

Consider a two-pole case

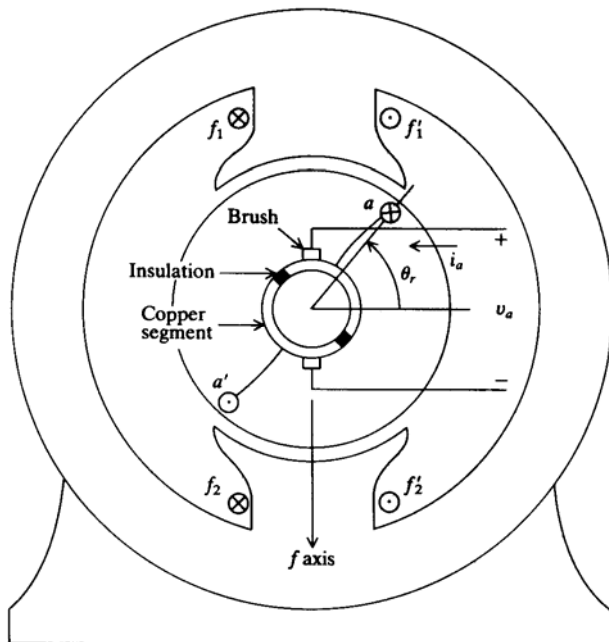

Voltage Equations

$$v_f = r_f i_f + \frac{d\lambda_f}{dt}$$

$$v_a = r_a i_a + \frac{d\lambda_a}{dt}$$

Flux linkages


$$\lambda_f = L_{ff} i_f + L_{fa} i_a$$

$$\lambda_a = L_a i_a + L_{af} i_f$$

Approximate the mutual inductance

$$L_{af} = L_{fa} = -L \cos(\theta_r)$$

# Commutation of Elementary DC Machine

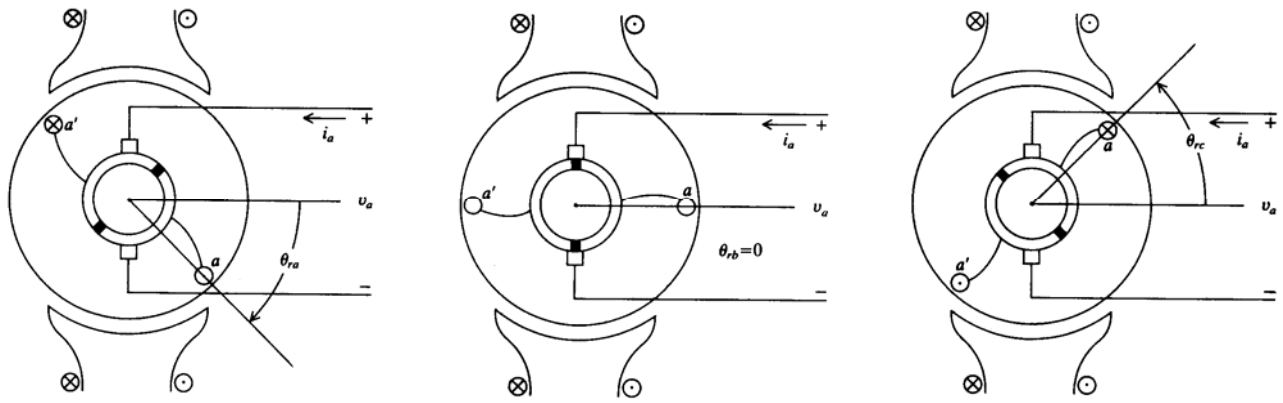

Induced voltage

$$e_a = \omega_r L i_f \sin(\theta_r)$$

$$v_a = r_a i_a + \frac{d\lambda_a}{dt}$$



Assume

$$i_a = 0 \text{ and } \theta_r = \omega_r t$$

$$\lambda_a = L_a i_a + L_{af} i_f$$


# More Realistic DC Machine

Resulted Winding Connection

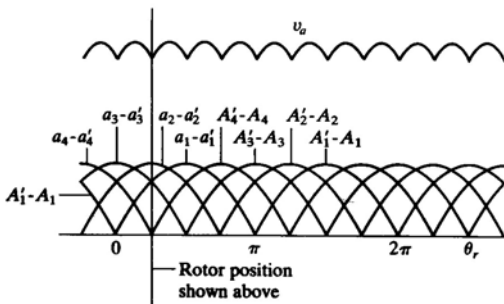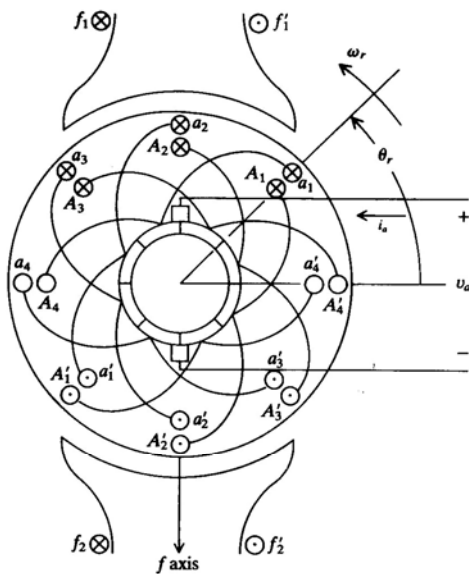


# More Realistic DC Machine

Resulted Winding Connection

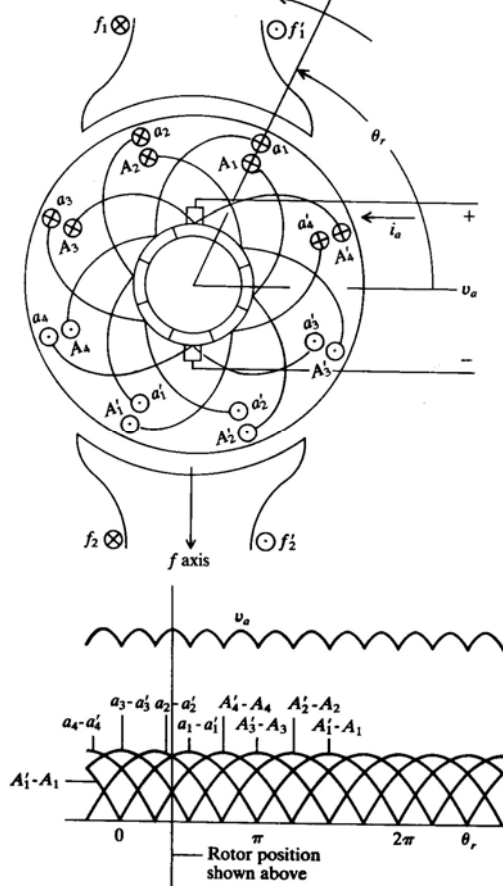


# DC Machine Construction



DC machine with field winding

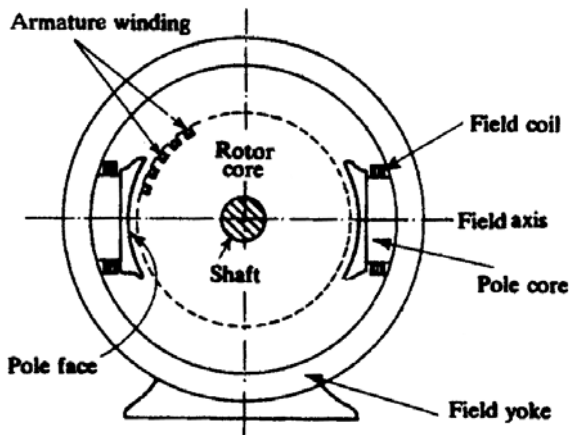


Permanent Magnet (PM) DC machine

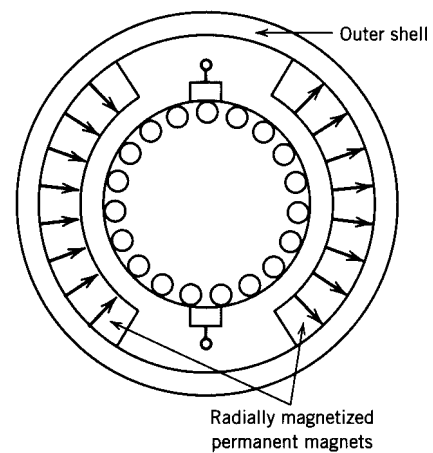

Rotor construction

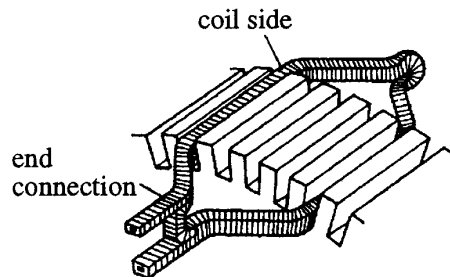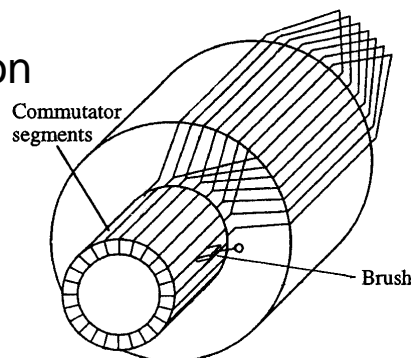


# Cutaway View of a Two-Pole DC Machine

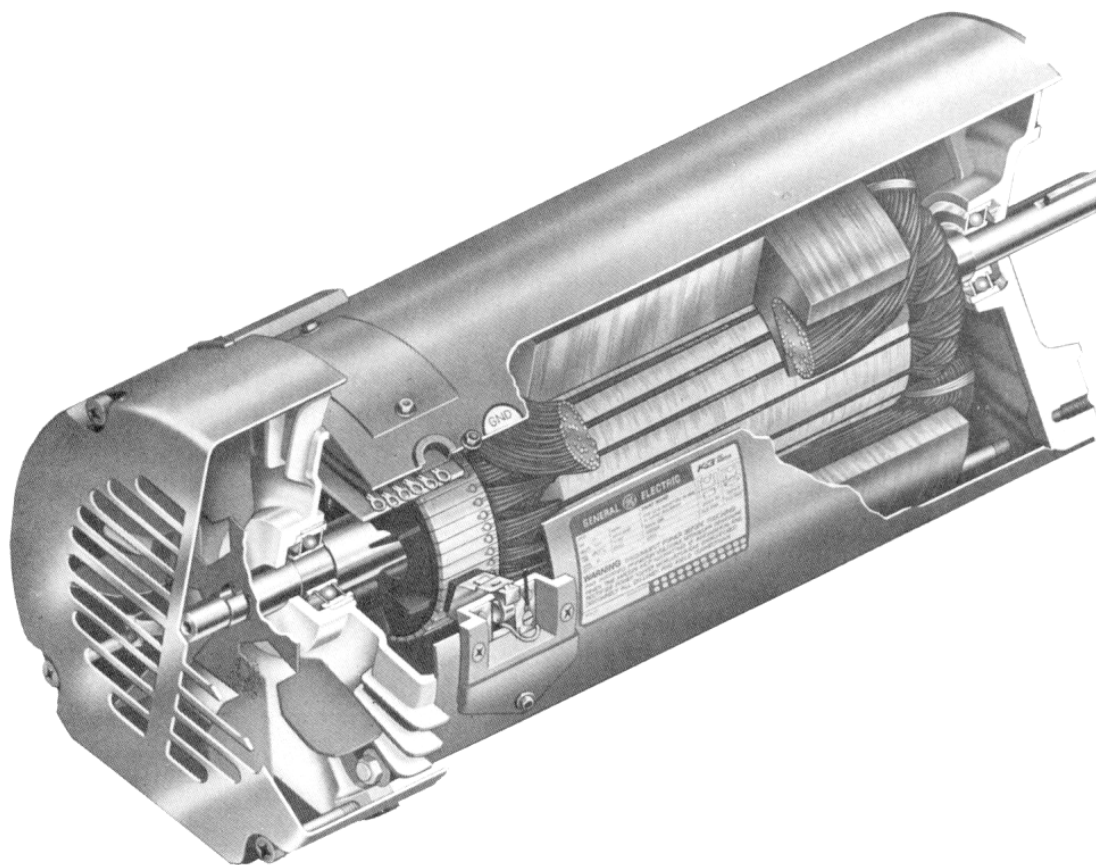

15

## Equivalent Circuit

EECE 376, S-15 M-3

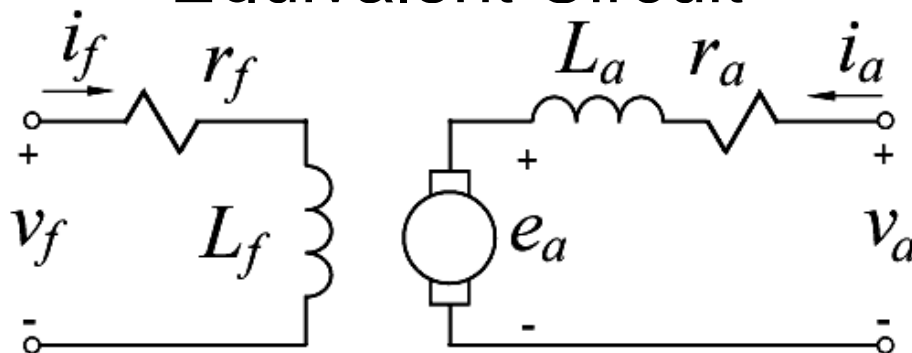

$v_f$  - is the field voltage

$i_f$  - is the field current

$r_f$  - field winding resistance

$L_f$  - field winding inductance

$v_a$  - applied terminal voltage

$i_a$  - is the armature current

$L_a$  - armature winding inductance

$r_a$  - armature winding + brush resistance

$e_a$  - Induced back emf (voltage)

16

# Dynamic Equivalent Circuit

Field Winding Equations

$$v_f = r_f i_f + \frac{d\lambda_f}{dt}$$

$$\lambda_f = N_f \Phi_p = L_f i_f$$

Armature Equations

$$v_a = r_a i_a + L_a \frac{di_a}{dt} + e_a$$

$$e_a = k_1 \omega_r \Phi_p$$

Electromagnetic Torque  $T_e = k_2 \Phi_p i_a$

Power balance  $T_e \omega_r = k_2 \Phi_p i_a \omega_r = e_a i_a = k_1 \omega_r \Phi_p i_a$

17

# Equivalent Circuit

Recall flux  $\Phi_p = \frac{\lambda_f}{N_f} = \frac{L_f}{N_f} I_f$

Induced voltage

$$e_a = k \Phi_p \omega_r = k \frac{L_f}{N_f} i_f \omega_r$$

Torque

$$T_e = k \Phi_p i_a = k \frac{L_f}{N_f} i_f i_a$$

Define  $L_{af} = k \frac{L_f}{N_f}$

- is the mutual inductance between field and rotating armature winding

$$L_{af} = \frac{N_a N_f}{\mathfrak{R}}$$

Re-define expression for back emf and torque


$$e_a = L_{af} i_f \omega_r = k_v \omega_r$$

$$T_e = L_{af} i_f i_a = k_t i_a$$

Machine voltage/torque constant for PM machine  $k_v = k_t = L_{af} i_f$

18

# Steady-State

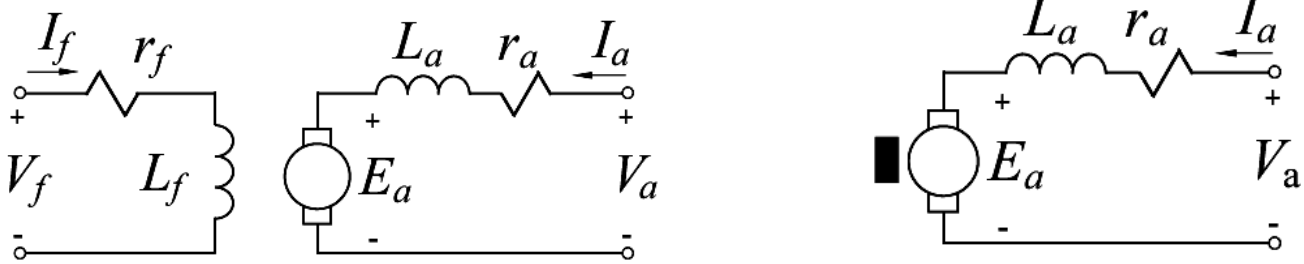

Field Winding Equations

$$V_f = R_f I_f$$

$$\lambda_f = N_f \Phi_p = L_f I_f$$

Armature Equations

$$V_a = r_a I_a + E_a$$


$$E_a = \omega_r k_v = \omega_r L_{af} i_f$$

Electromagnetic torque  $T_e = L_{af} I_f I_a = k_t I_a$

Torque balance  $T_e = T_m + T_{mech\_loss}$

19

## Example 1: No Load Test PM Motor

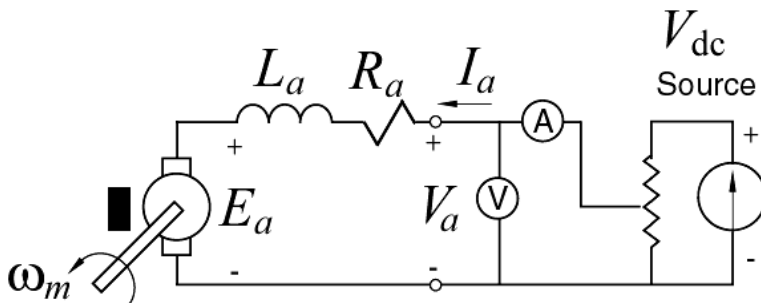

Assume you know  $R_a$

Measure  $I_a, V_a, \omega_r$

$$T_e = k_v I_a$$

$$E_a = k_v \omega_r$$

$k_t = k_v$  Torque / voltage  
machine constant

$$V_a = R_a I_a + E_a$$

$$P_e = I_a E_a = \omega_r T_e$$

$$T_e = T_{friction} = \omega_r K_{friction}$$

20

# Example 2: PM DC Motor

Consider a small PM DC Motor with the following parameters:

$V_{t, \text{rated}} = 6\text{V}$ ,  $I_{\text{no\_load}} = 0.15\text{A}$ ,  $R_a = 7\Omega$ , and torque constant  $K_t = 0.014$  [Vs/rad].  
Find no-load speed  $n_{nl}$  [rpm], back emf  $E_a$ , and friction torque  $T_{\text{fric}}$  at  $V_t = 6\text{V}$

$$V_t = R_a I_a + E_a = R_a I_a + K_t \cdot \omega$$

$$\omega_{nl} = \frac{V_t - R_a I_a}{K_t} = \frac{6 - 7 \cdot 0.15}{0.014} = 353.57 \text{ rad/sec}$$

$$n_{nl} = \frac{30}{\pi} \omega_{nl} = 3,376.4 \text{ rpm}$$

$$\text{Back emf } E_a = K_t \cdot \omega = 0.014 \cdot 353.57 = 4.95 \text{ V}$$

Electromagnetic torque

$$T_e = K_t \cdot I_a = 0.014 \cdot 0.15 = 0.0021 \text{ N}\cdot\text{m}$$

$$T_e = \frac{P_e}{\omega} = \frac{I_a \cdot E_a}{\omega} = \frac{0.15 \cdot 4.95}{353.57} = 0.0021 \text{ N}\cdot\text{m}$$


$$T_{\text{fric}} = T_e = 0.0021 \text{ N}\cdot\text{m}$$

21

# Basic Types of DC Machines

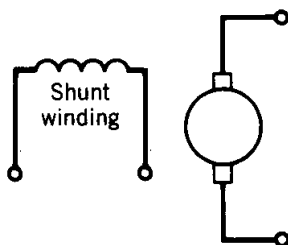
## Basic DC Machines

- Shunt or Series field windings are possible




Separately  
Excited  
DC Machine

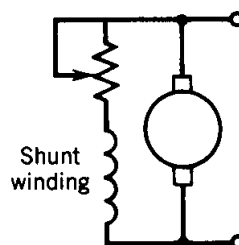- Field winding is designed for up to rated armature voltage
- Field winding has large number of turns
- Field current is small compared to armature current



Shunt DC  
Machine

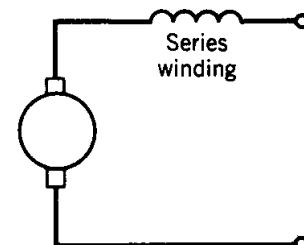

Series DC  
Machine


- Field winding is designed for up to rated armature current
- Field winding has small number of turns
- Field current is the same as the armature current

22


# Basic Types of DC Machines
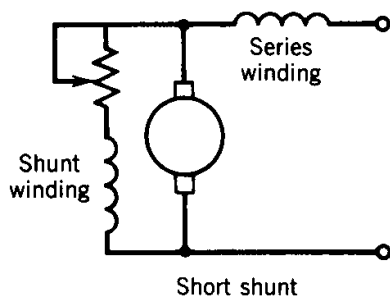
## Compound DC Machines

- Both Shunt and Series field windings are present



Short-Shunt  
Compound  
DC Machine

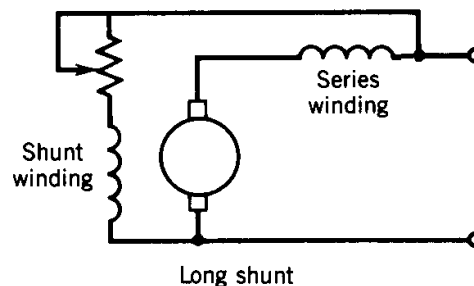


Long-Shunt  
Compound  
DC Machine

23

## Parameters of DC Machine

- Locked-Rotor Test (DC Measurements)

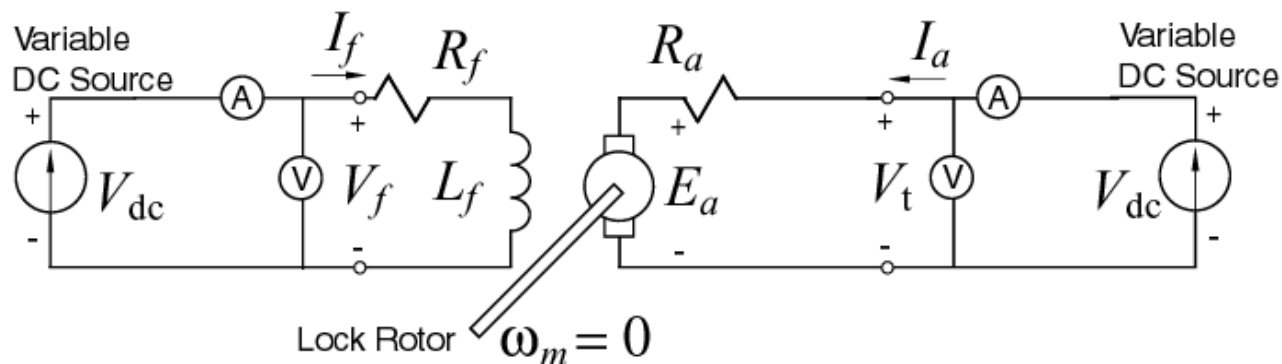

$$R_f = \frac{V_f}{I_f}$$


$$R_a = \frac{V_t}{I_a}$$

(armature + brush combined resistance at no speed!)

24
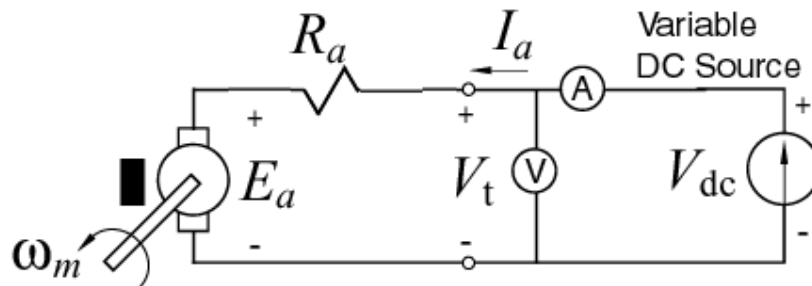
# Parameters of DC Machine

- No Load Test for PM Motors (Friction vs. Speed)



Assume you know  $R_a$

Measure  $I_a, V_t, \omega_m$

$$V_t = R_a I_a + E_a$$

$$T_e = K_a \Phi_p I_a = K_t I_a$$

$$P_e = I_a E_a = \omega_m T_e$$

$$E_a = K_a \Phi_p \omega_m = K_v \omega_m$$

$$T_e = T_{fric}(\omega_m) = \omega_m K_{fric}$$


$$K_t = K_v \quad \text{Torque / voltage machine constant}$$

Measure Friction Torque-Speed Characteristic

25
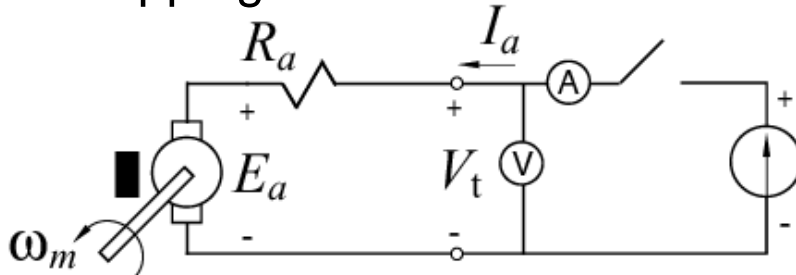
# Parameters of DC Machine

- Stopping Transient for Determining Inertia




Assume you know  $T_{fric}(\omega_m)$

Measure & Record  $I_a, V_t, \omega_m$

$$T_e = T_m + T_{fric}(\omega_m) + J \frac{d\omega_m}{dt}$$

$$E_a = K_a \Phi_p \omega_m = K_v \omega_m$$

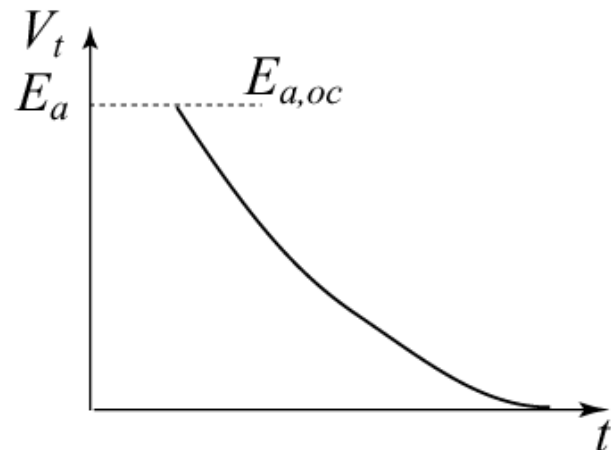
$$T_{fric}(\omega_m) = -J \frac{\Delta\omega_m}{\Delta t} = -J \frac{\Delta E_a}{K_v \Delta t}$$



26
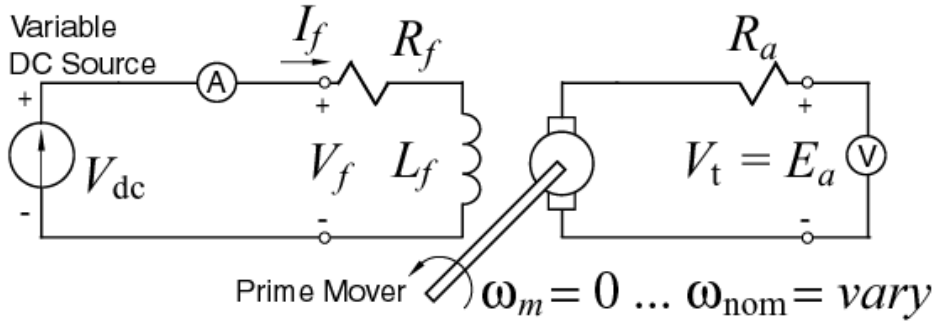
# Parameters of DC Machine


- Open-Circuit Test (Generated Voltage vs. Speed)



$$E_a = K_a \Phi_p \omega_m = K_a \frac{L_f}{N_f} I_f \omega_m$$


$$= L_{af} I_f \omega_m$$

$$= K_v \omega_m$$

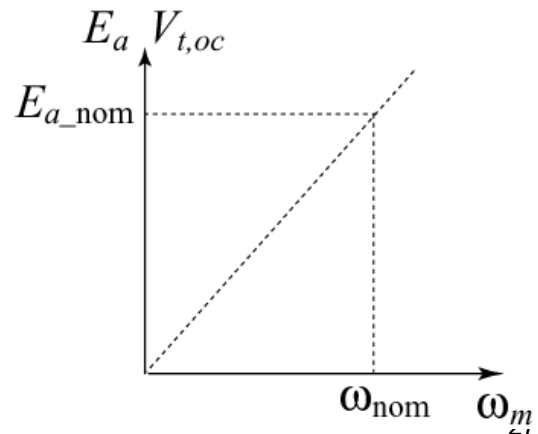
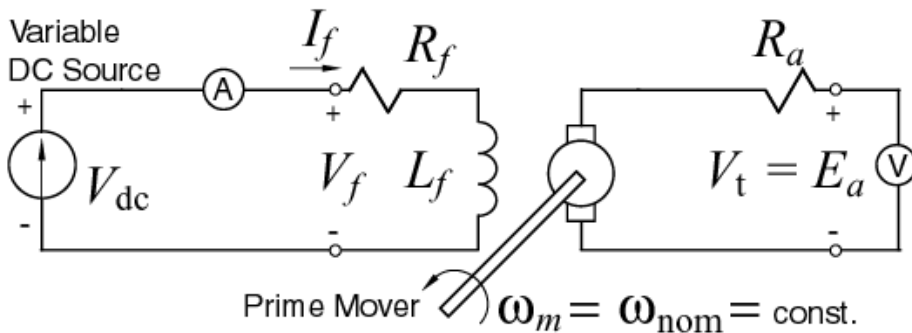
# Parameters of DC Machine

- Open-Circuit Test (Generated Voltage vs. Field Currents)




$$L_{af} = \frac{E_a}{I_f \omega_m}$$

$$\Phi_p = \frac{\lambda_f}{N_f} = \frac{L_f}{N_f} I_f$$


$$E_a = K_a \Phi_p \omega_m = K_a \frac{L_f}{N_f} I_f \omega_m$$

$$= L_{af} I_f \omega_m$$

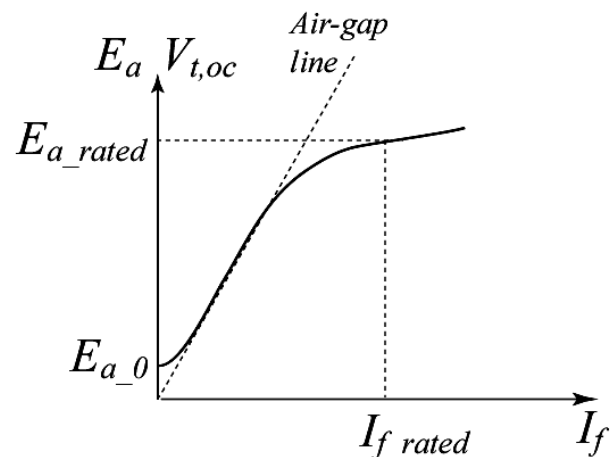


# DC Machines Characteristics:

## Speed Regulation (for Motors)

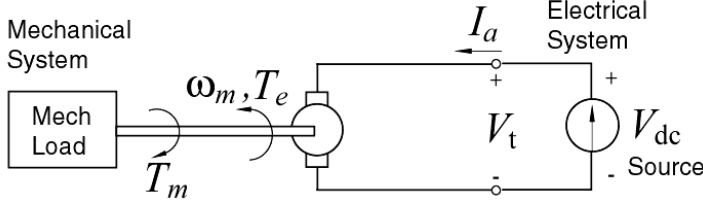


$$SR = \frac{\omega_{m,no\_load} - \omega_{m,load}}{\omega_{m,load}} 100\% = \frac{n_{no\_load} - n_{load}}{n_{load}} 100\%$$

## Speed-Torque Characteristic

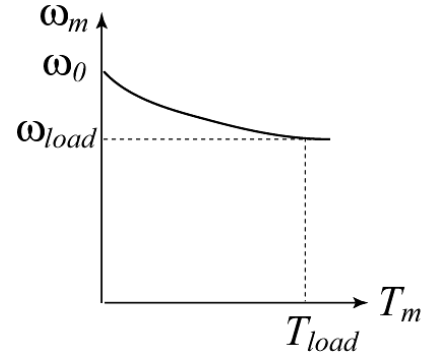


## Voltage Regulation (for Generators)

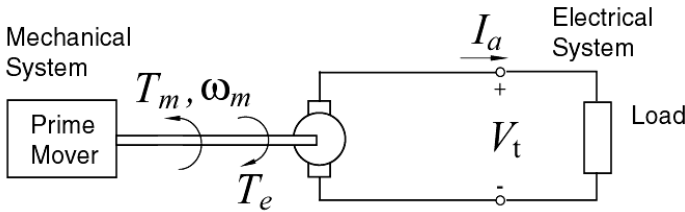

$$VR = \frac{V_{t,oc} - V_{t,load}}{V_{t,load}} 100\% = \frac{V_{no\_load} - V_{nom}}{V_{nom}} 100\%$$


## Load-Voltage Characteristic

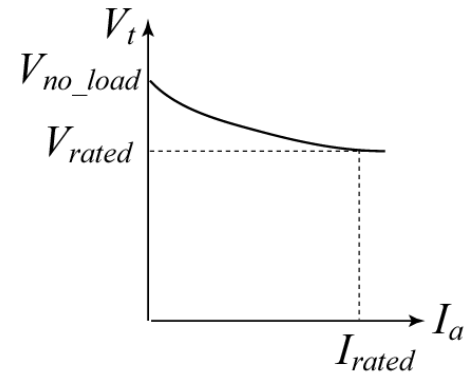

29

# Separately Excited

Field Winding Equations

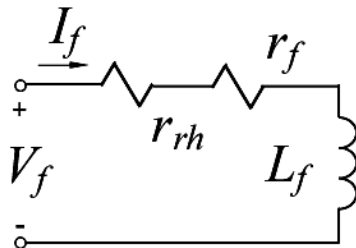

$$R_f = r_f + r_{rh}$$


$$V_f = R_f I_f$$

$$\lambda_f = N_f \Phi_p = L_f I_f$$

Electromagnetic torque  $T_e = L_{af} I_f I_a = k_t I_a$

Torque balance  $T_e = T_m + T_{mech\_loss}$



Armature Equations

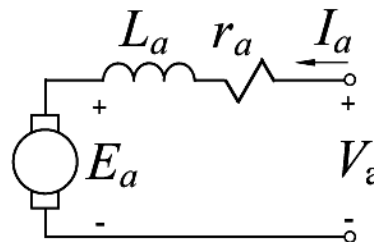

$$V_a = r_a I_a + E_a$$

$$E_a = \omega_r k_v = \omega_r L_{af} i_f$$

# Separately-Excited DC Motor

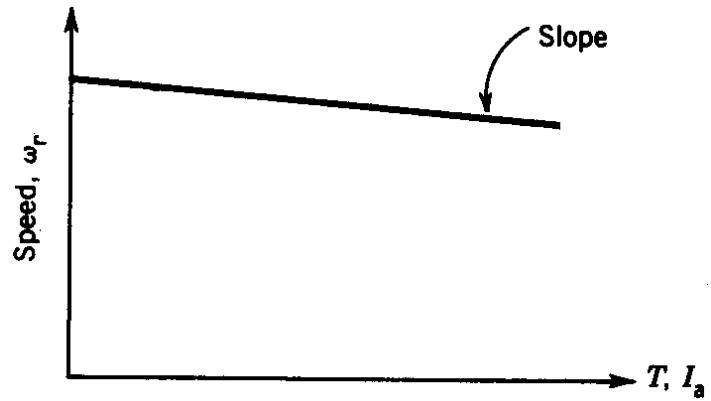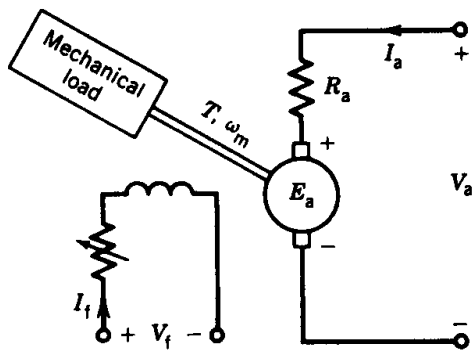

Speed-Torque Characteristic

$$V_a = E_a + R_a I_a$$

$$T = L_{af} I_f I_a = k_t I_a$$



$$E_a = L_{af} I_f \omega_r = k_v \omega_r$$

$$\omega_r = \frac{V_a - I_a R_a}{k_v}$$

$$\omega_r = \frac{V_a}{k_v} - \frac{R_a}{k_v^2} T$$

31

# Shunt DC Motor

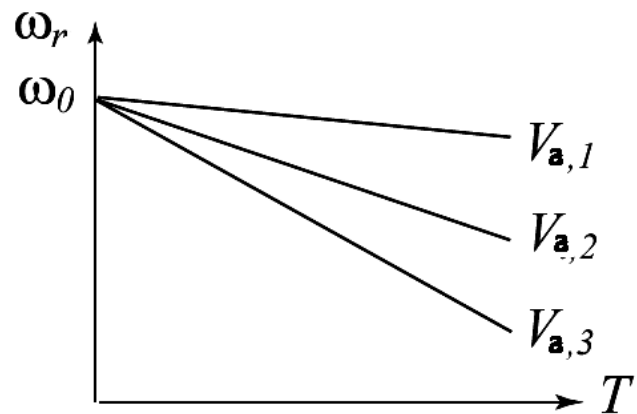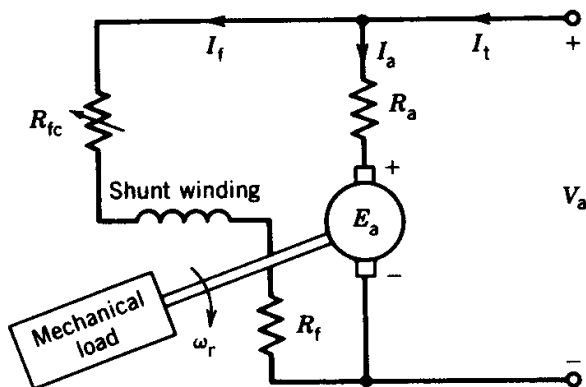

Speed-Torque Characteristic



$$\omega_r = \frac{V_a}{k_v} - \frac{R_a}{k_v^2} T$$

$$k_v = L_{af} I_f = \frac{L_{af} V_a}{R_f + R_{fc}}$$

$$\omega_r = \frac{R_{f,total}}{L_{af}} - \frac{R_a R_{f,total}^2}{(L_{af} V_a)^2} T$$

32

# Series DC Motor

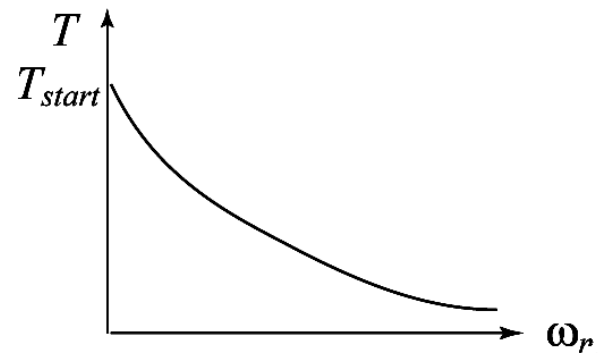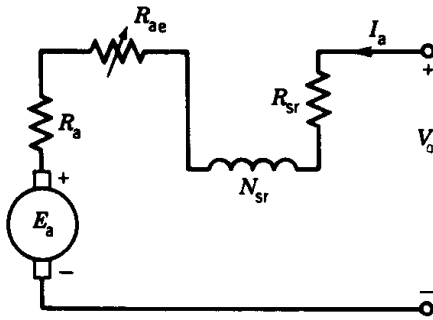

Torque-Speed Characteristic

$$V_t = I_a (R_a + R_{sr} + R_{ae}) + L_{af} I_a \omega_m$$

$$I_a = \frac{V_a}{R_a + R_{sr} + R_{ae} + L_{af} \omega_m}$$

$$T = \frac{L_{af} V_a^2}{(R_a + R_{sr} + R_{ae} + L_{af} \omega_m)^2}$$

$$T_e = L_{af} I_a^2$$

33

## Starting Considerations

Consider a 1.2kW, 120V, Shunt DC Motor with  $R_a = 2\Omega$ , and  $I_{a\_max} = 20A$

$$\text{Rated current } I_{a,rated} = \frac{1200}{120} = 10A$$

$$\text{Starting current } I_{a,start} = \frac{V_a - E_a}{R_a} = \frac{120 - 0}{2} = 60A$$

Too high ! =>  
Burn the motor !

1. Use additional starting resistor in series with armature
2. Use reduced voltage
3. Use Power Electronic Drive & Controller

34

# Part 2: Brushed DC Motor Drives and Dynamics

## Important Topics & Concepts

- Basic types of dc motor drives
- DC to DC choppers (Chap. 3.8)
- AC to DC controlled rectifiers
- Dynamic (State) equations of the separately-excited motor
- Possible model & implementation/solution
- Dynamic (State) equations of the PM motor
- Possible model & implementation/solution

35

## Speed/Torque Control of DC Motors

Recall the Separately Excited DC Motor


$$k_v = L_{af} i_f$$

$$v_a = r_a i_a + k_v \omega_r$$

$$T_e = k_v i_a$$

$$\omega_r = \frac{v_a - i_a r_a}{k_v}$$
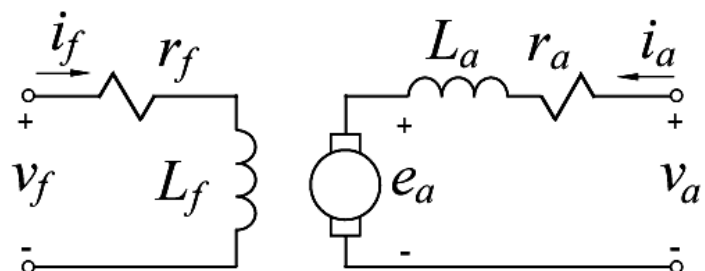
$$\omega_r = \frac{v_a}{k_v} - \frac{r_a}{k_v^2} T_e$$



Control methods:

1. Varying the armature resistance
2. Varying the field
3. Varying the terminal voltage
4. Varying the armature current

36

# Solid-State Converters for DC Motors

DC-DC Converters (Choppers) – used with small & large motors

- Voltage Source (VS) (Pulse Width Modulation – PWM)
  - One-quadrant
  - Two-quadrant
  - Four-quadrant
- Current Source (CS) (Hysteresis & Delta Modulation)
  - One-quadrant
  - Two-quadrant
  - Four-quadrant


AC-DC Controlled Rectifiers – used with large motors

- Single-Phase
  - Half-wave
  - Full bridge (full wave)
- Three-Phase
  - Half-wave
  - Full bridge (full wave)


37
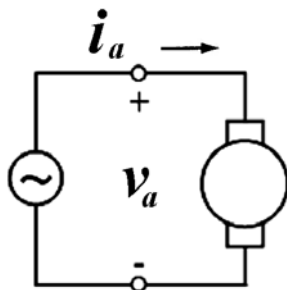
## DC-DC Converters (Choppers)

Assume a dc voltage source wherein the averaged output voltage can be controlled



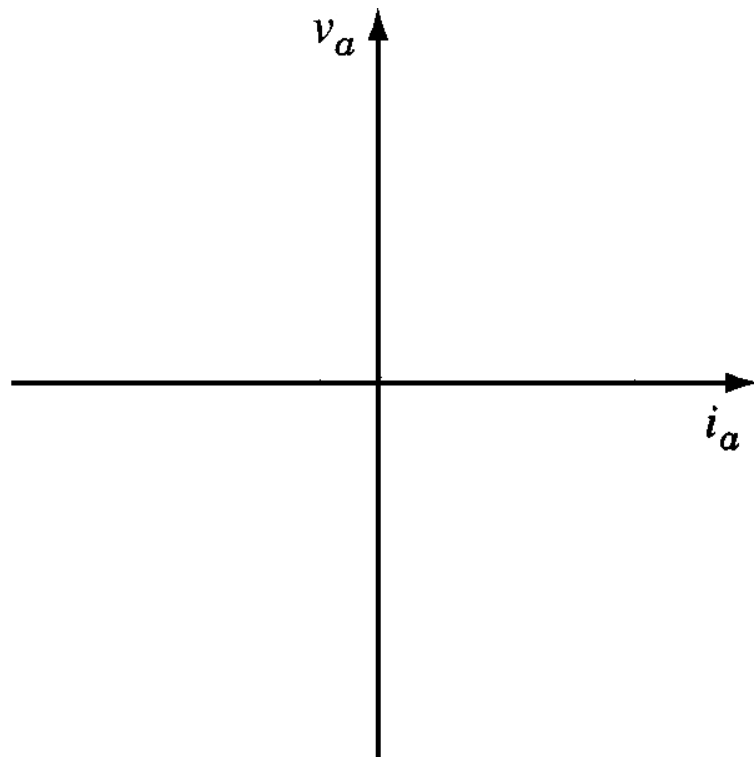
$$\bar{V}_a = \frac{1}{T} \int_0^T V_a(t) dt$$




38

# One-Quadrant VS DC-DC Converter

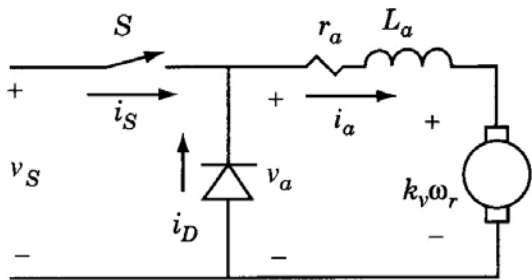


## Pulse Width Modulation (PWM)

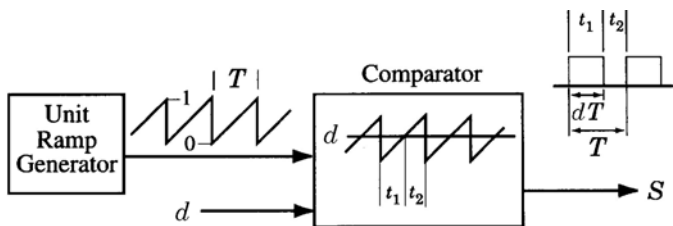


Switch can be realized using:

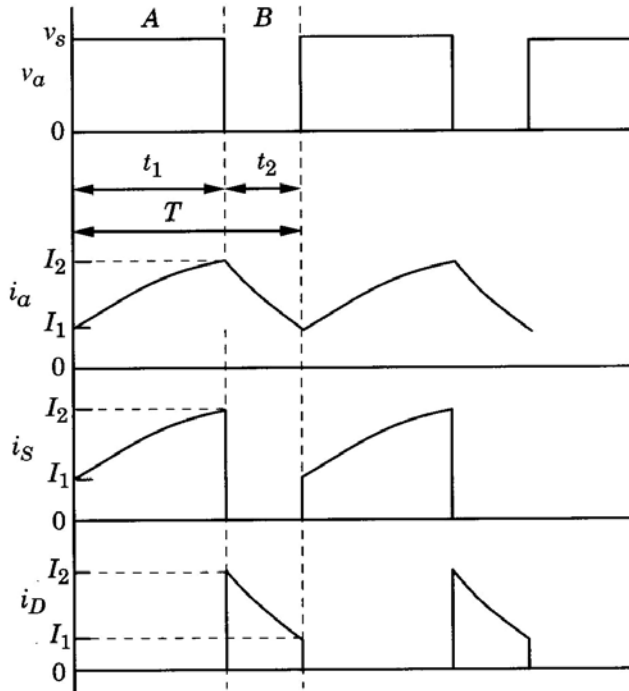- Bipolar Junction Transistor (**BJT**)
- Insulated Gate Bipolar Transistor (**IGBT**)
- Metal Oxide Semiconductor Field Effect Transistor (**MOSFET**)




$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = \frac{t_1}{t_1 + t_2} V_s$$



# Two-Quadrant VS DC-DC Converter

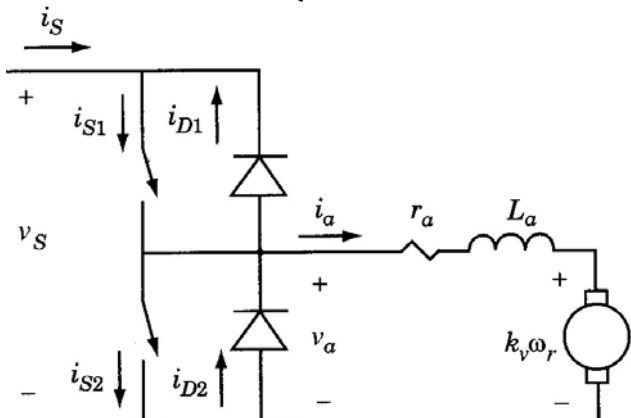

## Pulse Width Modulation (PWM)

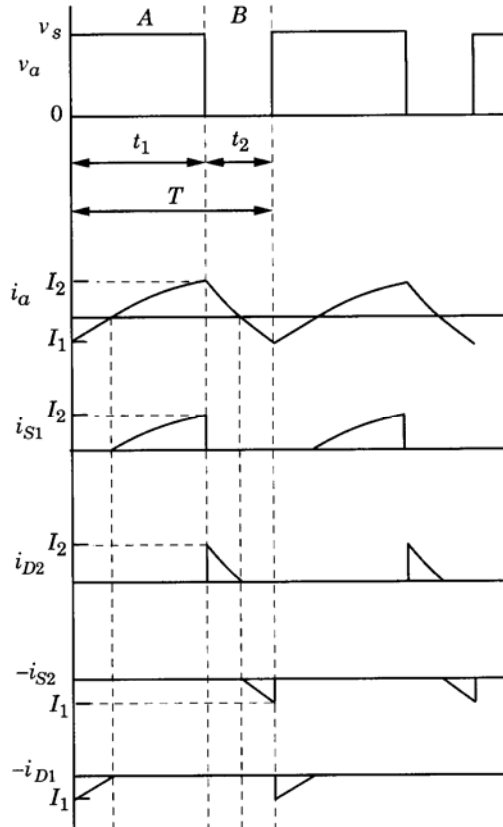

# Four-Quadrant VS DC-DC Converter


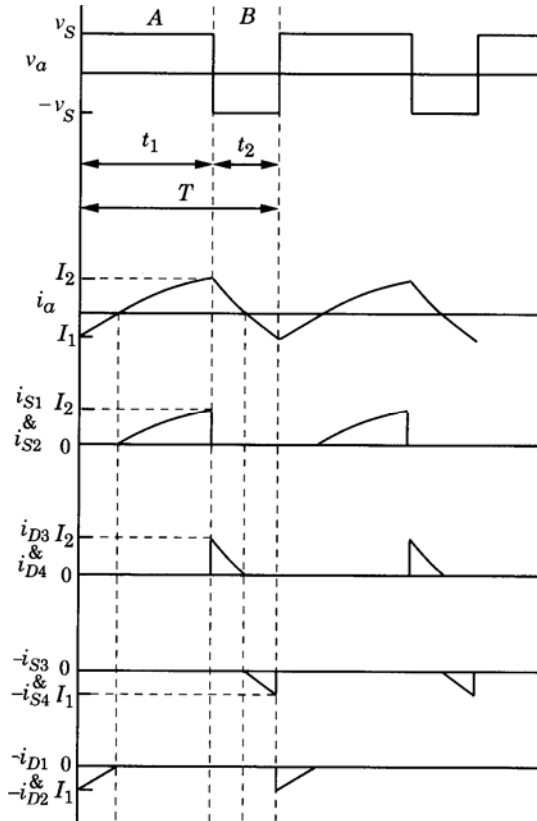
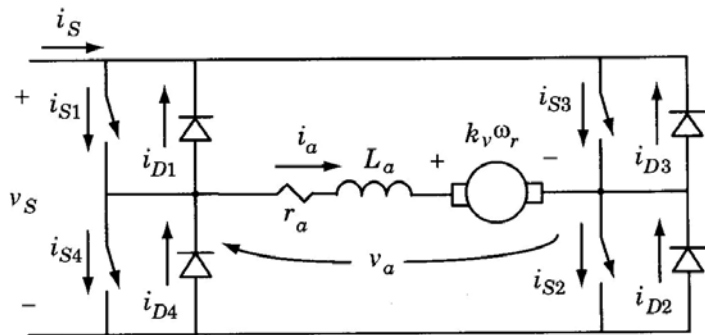


Pulse Width Modulation (PWM)

$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = dV_s$$

# Current Source DC-DC Converter

Hysteresis Modulation (HM)

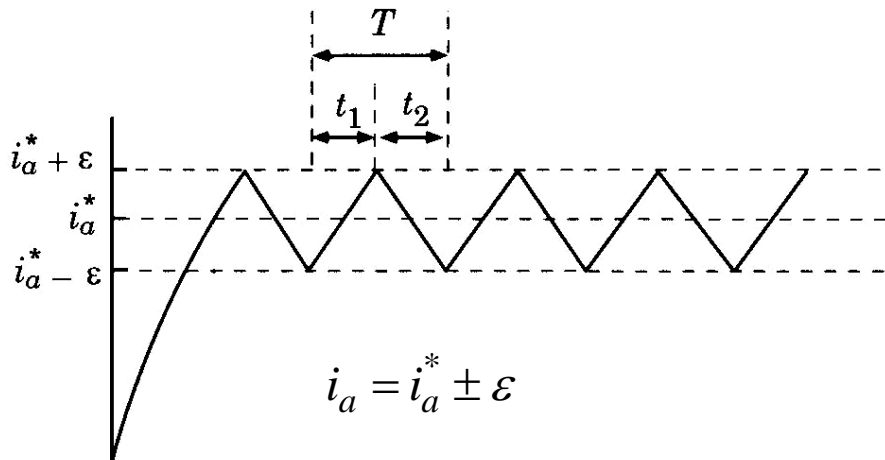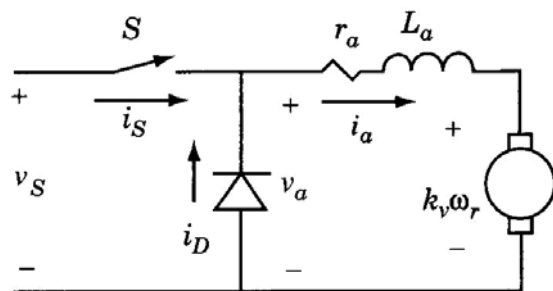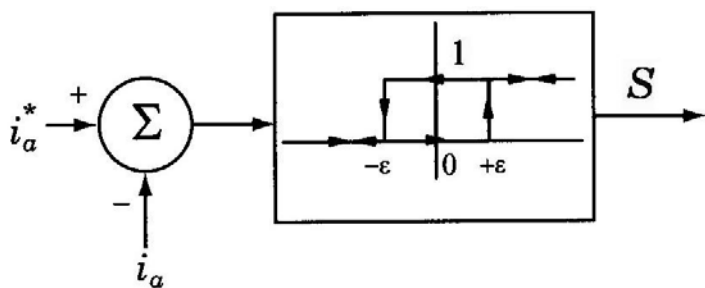


The same modulation can be applied to two- and four-quadrant choppers

# Thyristor Controlled Rectifiers

Control the Averaged Output Voltage

a) Single-phase, half-wave

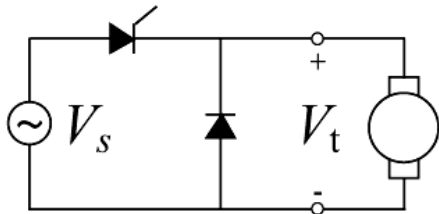


$$V_s = \sqrt{2}V_{rms} \sin(\omega t)$$

$$\bar{V}_t = \frac{1}{T} \int_0^T V_t(t) dt = \frac{V_{rms}}{\sqrt{2}\pi} (1 + \cos(\alpha))$$

$$0 \leq \alpha \leq \pi$$
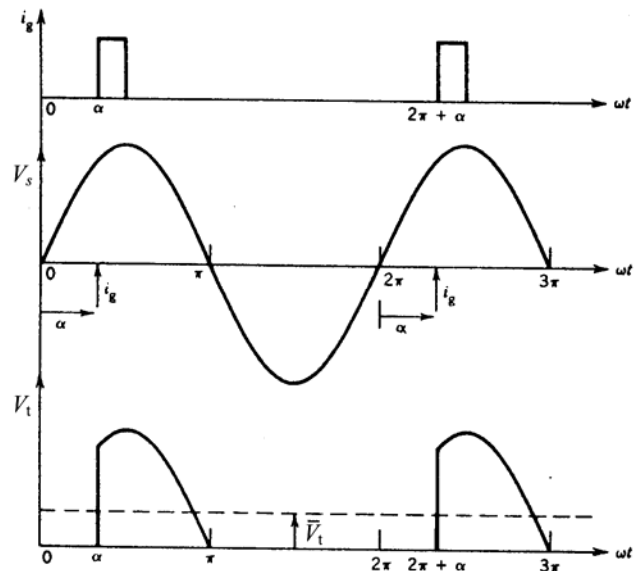
$$0 \leq \bar{V}_t \leq \frac{\sqrt{2}}{\pi} V_{rms}$$




43

# Thyristor Controlled Rectifiers

Control the Averaged Output Voltage

b) Single-phase, full-wave

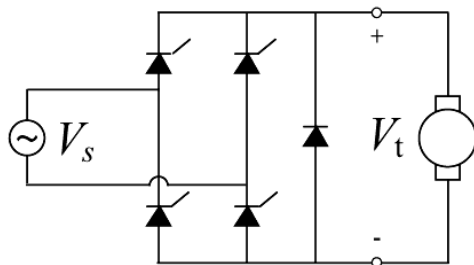


$$V_s = \sqrt{2}V_{rms} \sin(\omega t)$$

$$\bar{V}_t = \frac{1}{T} \int_0^T V_t(t) dt = \frac{\sqrt{2}V_{rms}}{\pi} (1 + \cos(\alpha))$$

$$0 \leq \alpha \leq \pi$$
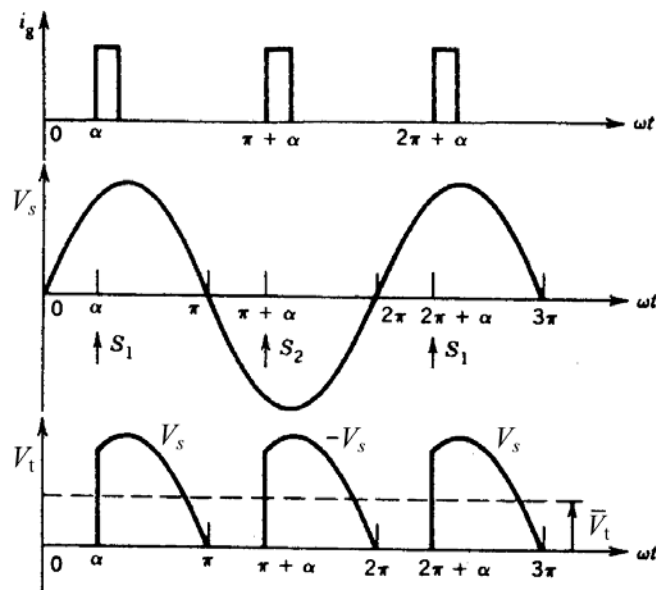
$$0 \leq \bar{V}_t \leq \frac{2\sqrt{2}}{\pi} V_{rms}$$



44

# Thyristor Controlled Rectifiers



Control the Averaged Output Voltage

d) Three-phase, full-wave

$$V_A = \sqrt{2}V_{rms} \sin(\omega t)$$

$$V_B = \sqrt{2}V_{rms} \sin(\omega t - 120^\circ)$$

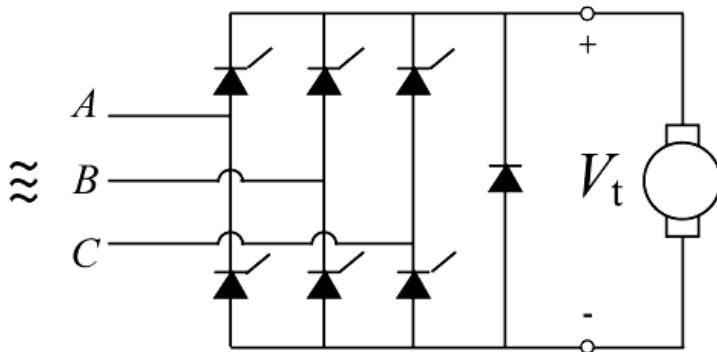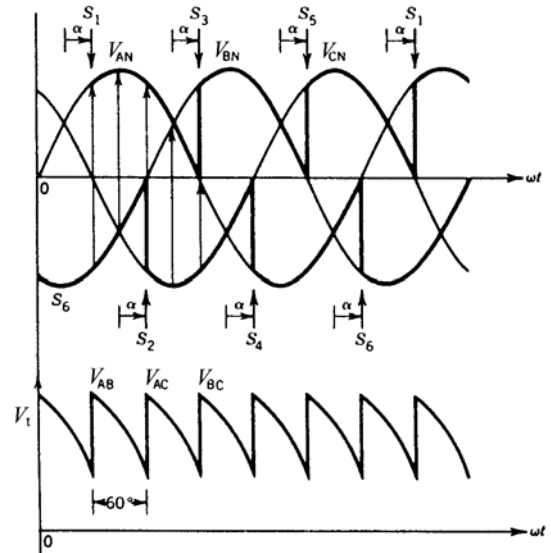
$$V_C = \sqrt{2}V_{rms} \sin(\omega t + 120^\circ)$$



$$\bar{V}_t = \frac{1}{T} \int_0^T V_t(t) dt \quad 0 \leq \alpha \leq \pi$$


$$0 \leq \bar{V}_t \leq \frac{3\sqrt{6}}{\pi} V_{rms}$$

# Closed-Loop Electric Drive System

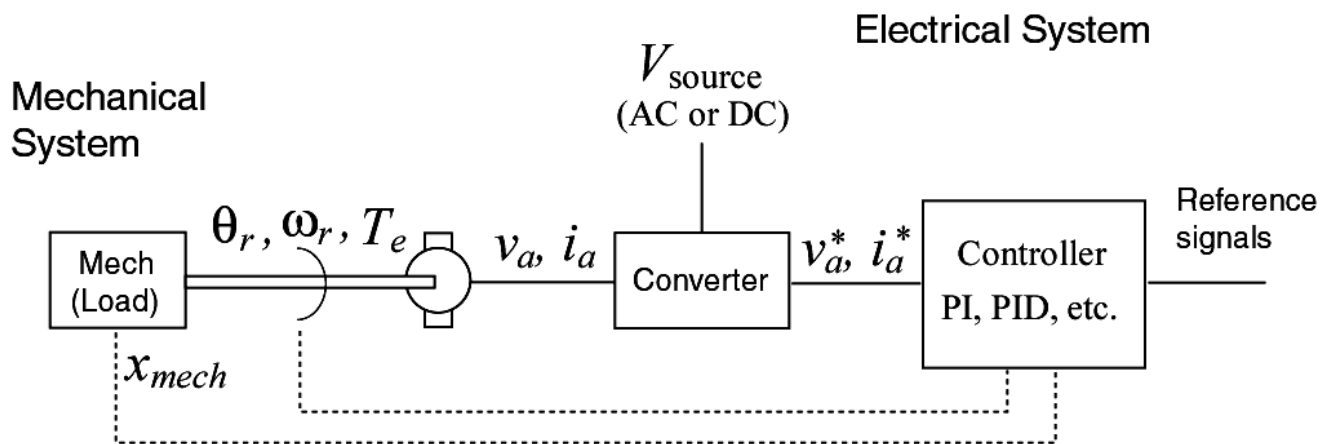

# Dynamic Modeling

Circuit is valid for transient analysis

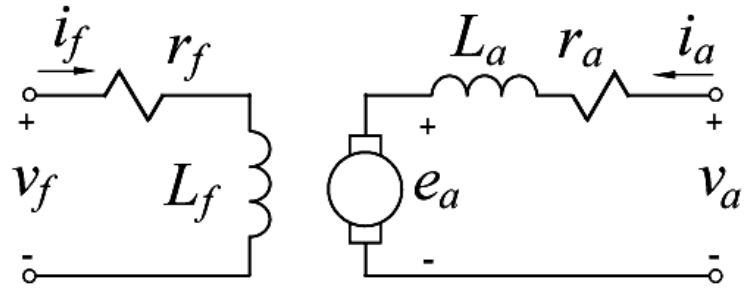

Voltage Equations

$$v_a = r_a i_a + \frac{d\lambda_a}{dt} + e_a = r_a i_a + e_a + L_a \frac{di_a}{dt}$$

$$v_f = r_f i_f + \frac{d\lambda_f}{dt} = r_f i_f + L_f \frac{di_f}{dt}$$

Speed Equation

$$T_e = J \frac{d\omega_r}{dt} + T_m + D_m \omega_r$$

Coupling Terms

$$e_a = \omega_r L_{af} i_f$$

$$T_e = L_{af} i_f i_a$$

47

## Re-Write the Equations to Express Derivatives

State Equations

$$\frac{di_a}{dt} = -\frac{r_a}{L_a} i_a - \frac{1}{L_a} e_a + \frac{1}{L_a} v_a$$

$$\frac{di_f}{dt} = -\frac{r_f}{L_f} i_f + \frac{1}{L_f} v_f$$

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m)$$

Coupling Terms

$$e_a = \omega_r L_{af} i_f$$

$$T_e = L_{af} i_f i_a$$

Are these equations coupled or decoupled ?

Are these equations linear or non-linear ?


How do we solve these equations ?

48
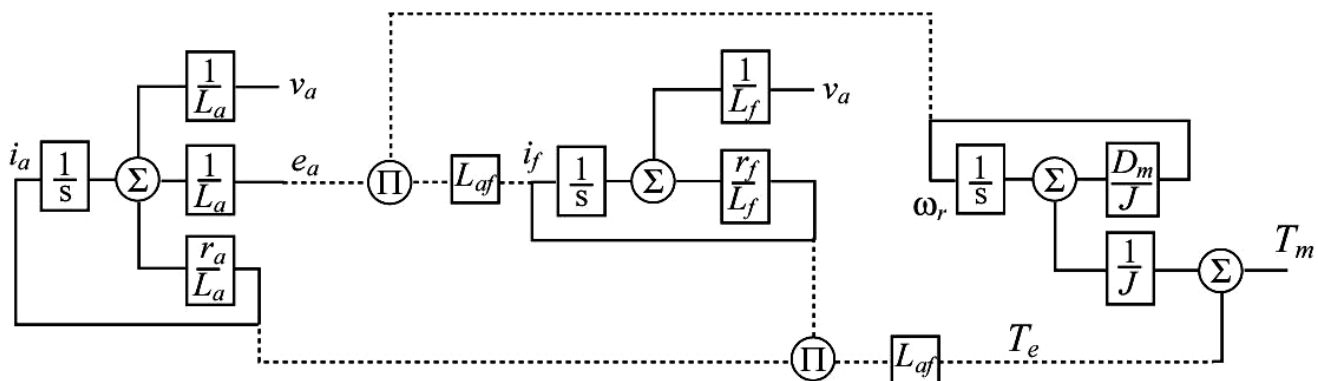
# Implementation of State Equations

$$\frac{di_a}{dt} = -\frac{r_a}{L_a}i_a - \frac{1}{L_a}e_a + \frac{1}{L_a}v_a$$

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J}\omega_r + \frac{1}{J}(T_e - T_m)$$



$$e_a = \omega_r L_{af} i_f$$

$$\frac{di_f}{dt} = -\frac{r_f}{L_f}i_f + \frac{1}{L_f}v_f$$


$$T_e = L_{af} i_f i_a$$

Try to implement it in Simulink ?

Is this a unique implementation ?

49

# Implementation of State Equations

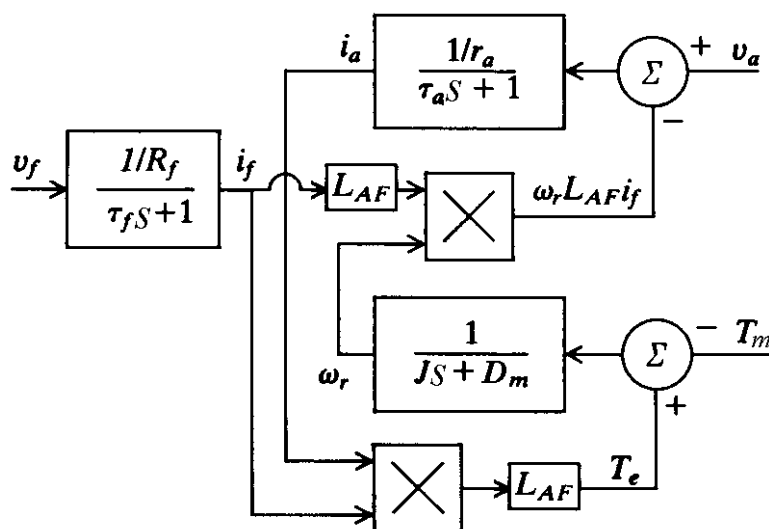

Re-write the equations

$$v_f = r_f (1 + \tau_f s) i_f$$

$$v_a = r_a (1 + \tau_a s) i_a + e_a$$

$$e_a = \omega_r L_{af} i_f$$

$$T_e - T_m = (D_m + J s) \omega_r$$



$$T_e = L_{af} i_f i_a$$

Define time constants

$$\tau_a = \frac{L_a}{r_a} \quad \tau_f = \frac{L_f}{r_f}$$

50

# 5-HP Shunt DC Motor Simulink Model

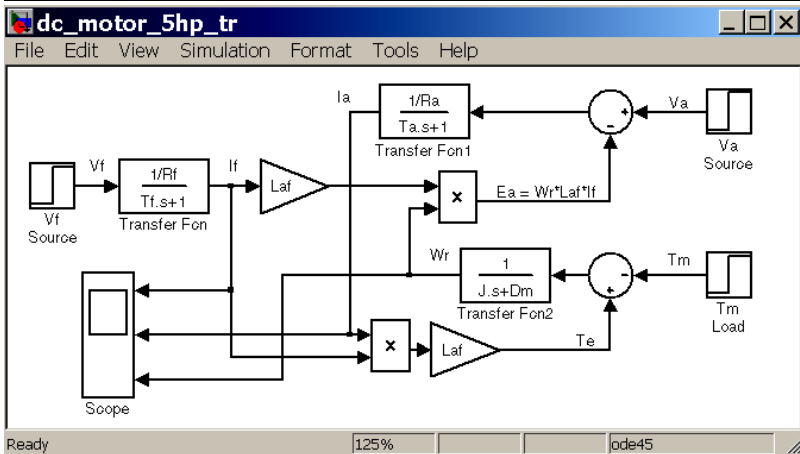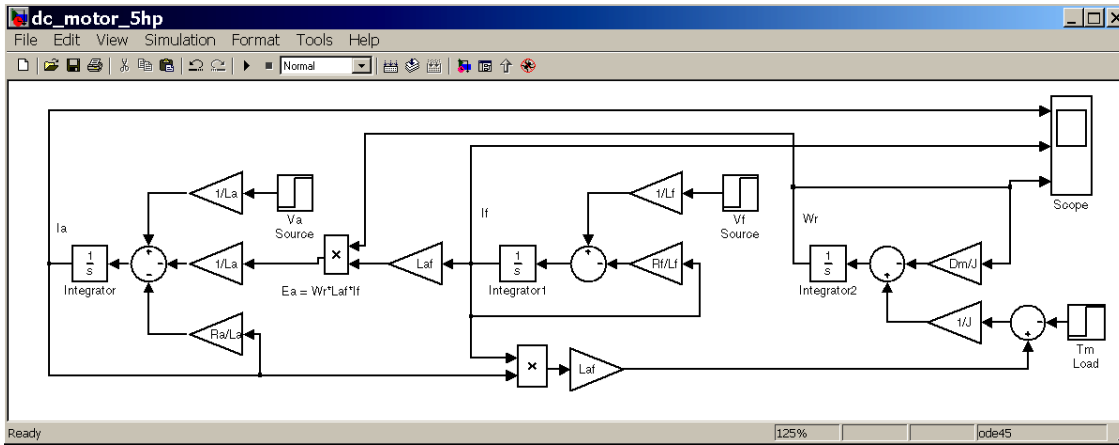

Try to do it yourself !

## Dynamic Response of a 5-HP DC Motor

Motor parameters:

$V_a = V_f = 240V$ ,  $R_f = 240\Omega$ ,  $L_f = 120H$ ,  $R_a = 0.6\Omega$ ,  $L_a = 0.012H$ ,  $L_{af} = 1.8H$ ,  
 $J = 1kg \cdot m^2$ ,  $D_m = 1e-4 N \cdot m \cdot s$ ,  $T_m = 29.2 N \cdot m$


In this computer study:

Zero initial conditions assumed

Step-1: field winding is energized

Step-2: armature is energized

Step-3: load torque is applied

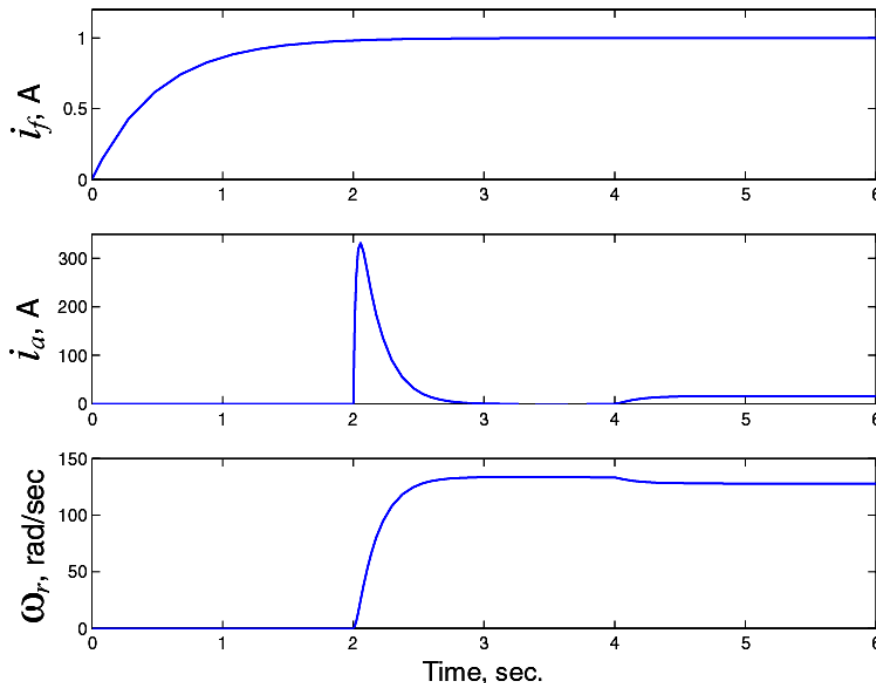

# PM DC Motor Dynamics

## State Equations

$$\frac{di_a}{dt} = -\frac{r_a}{L_a}i_a - \frac{1}{L_a}e_a + \frac{1}{L_a}v_a$$

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J}\omega_r + \frac{1}{J}(T_e - T_m)$$

## Coupling Terms

$$e_a = k_v\omega_r \quad T_e = k_v i_a$$

Are these equations coupled or decoupled ?

Are these equations linear or non-linear ?

How do we solve these equations ?

## Standard State-Space Form

$$\frac{d}{dt} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} = \begin{bmatrix} -\frac{r_a}{L_a} & -\frac{k_v}{L_a} \\ \frac{k_v}{J} & -\frac{D_m}{J} \end{bmatrix} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} + \begin{bmatrix} \frac{1}{L_a} \\ -\frac{1}{J} \end{bmatrix} \begin{bmatrix} v_a \\ T_m \end{bmatrix}$$

$$\frac{d\mathbf{x}}{dt} = \mathbf{Ax} + \mathbf{Bu}$$

53

# PM DC Motor Implementations

## State Equations

$$\frac{di_a}{dt} = -\frac{r_a}{L_a}i_a - \frac{1}{L_a}e_a + \frac{1}{L_a}v_a$$

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J}\omega_r + \frac{1}{J}(T_e - T_m)$$


## Coupling Terms

$$e_a = k_v\omega_r \quad T_e = k_v i_a$$

Are these equations coupled or decoupled ?


Are these equations linear or non-linear ?

How do we solve these equations ?

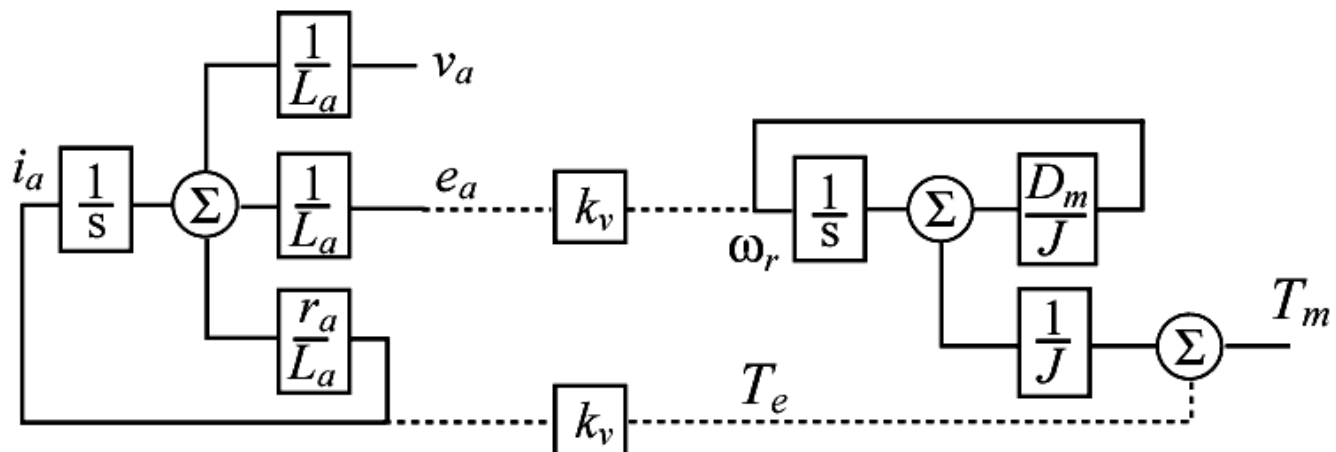

54

# Implementation of State Equations

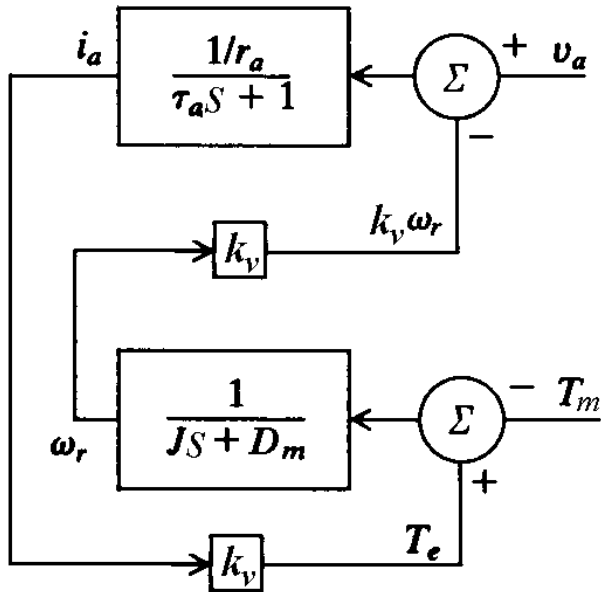

Re-write the equations

$$v_a = r_a (1 + \tau_a s) i_a + e_a$$

$$e_a = k_v \omega_r$$

$$T_e - T_m = (D_m + Js) \omega_r$$


$$T_e = k_v i_a$$

Define time constants

$$\tau_a = \frac{L_a}{r_a} \quad \tau_f = \frac{L_f}{r_f}$$

55

# Simulink Model of a PM DC Motor

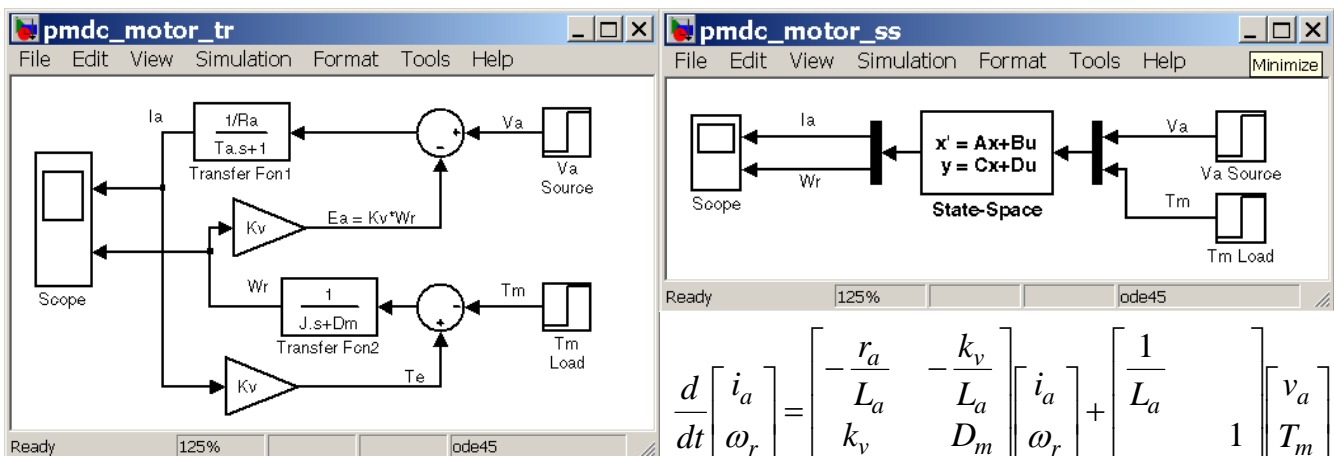

$$\frac{d}{dt} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} = \begin{bmatrix} -\frac{r_a}{L_a} & -\frac{k_v}{L_a} \\ \frac{k_v}{J} & -\frac{D_m}{J} \end{bmatrix} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} + \begin{bmatrix} \frac{1}{L_a} \\ -\frac{1}{J} \end{bmatrix} \begin{bmatrix} v_a \\ T_m \end{bmatrix}$$

$$i_a = \frac{1}{r_a (1 + \tau_a s)} (v_a - e_a)$$

$$e_a = k_v \omega_r$$

$$\omega_r = \frac{1}{D_m + Js} (T_e - T_m)$$

$$T_e = k_v i_a$$

$$\begin{bmatrix} i_a \\ \omega_r \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_a \\ T_m \end{bmatrix}$$

56

# Dynamic Response of a 6V PM DC Motor

Motor parameters:

$V_a = 6V$ ,  $R_a = 7\Omega$ ,  $L_a = 120mH$ ,  $K_v = 0.0141 \text{ N}\cdot\text{A}/\text{m}$ ,  $J = 1.06e-6 \text{ kg}\cdot\text{m}^2$ ,

$D_m = 6.01e-6 \text{ N}\cdot\text{m}\cdot\text{s}$ ,  $T_m = 3.53e-3 \text{ N}\cdot\text{m}$

In this computer study:

Zero initial conditions assumed

Step-1: voltage is applied

Step-2: load torque is applied

