

$$1/ (a) \quad \bar{S}_1 = 10 \times (0.8 + j0.6) \text{ kVA} = 8 + j6 \text{ kVA} \quad (2)$$

$$\bar{S}_2 = P_2 + jQ_2 \quad \text{where } P_2 = 10 \text{ kW}$$

$$\text{and } S_2 = \frac{P_2}{\text{pf}_2} = \frac{10}{0.8} = 12.5 \text{ kVA}$$

$$\Rightarrow Q_2 = 12.5 \sin \phi = 12.5 \times 0.6 = 7.5 \text{ kVAR} \quad (3)$$

$$\therefore \bar{S}_f = P_1 + P_2 + j(Q_1 + Q_2) \quad (5)$$

$$= \underline{18 + j13.5 \text{ kVA}} = \underline{22.5 \angle 36.9^\circ \text{ kVA}}$$

$$(b) \quad \bar{I}_f = \left(\frac{\bar{S}_f}{\bar{V}_f} \right)^* = \frac{(18 - j13.5) \times 10^3}{477} = \underline{37.7 - j28.3 \text{ A}} \quad (3)$$


$$= \underline{47.2 \angle -36.9^\circ \text{ A}}$$

(c) By inspection, we need $\underline{Q_{\text{cap}} = -13.5 \text{ kVAR}}$ to make $\bar{S}'_f = 18 + j0 \text{ kVA}$ (ie. $\text{pf} = 1$). (4)

$$(d) \quad \bar{I}'_f = \left(\frac{\bar{S}'_f}{\bar{V}_f} \right)^* = \frac{18 \times 10^3}{477} = \underline{37.7 + j0 \text{ A}} \quad (3)$$

$$= \underline{37.7 \angle 0^\circ \text{ A}}$$

(e)

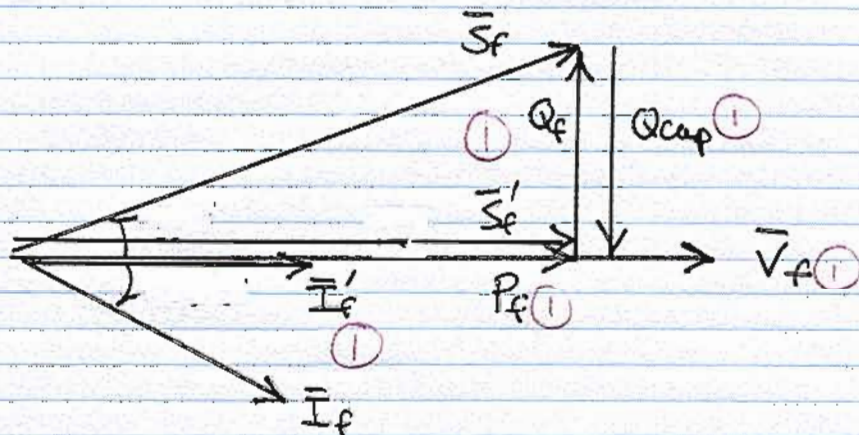

① For currents

① For S 's

① For Q 's

✓

2/ (a) $\bar{S}_{\text{load}} = 3 \bar{V}_{\text{phase}} \bar{I}_{\text{phase}}^*$ using rated load

info: $60 \times 10^3 (0.9 + j0.44) = 3 \cdot 600 \cdot \left(\frac{\bar{V}_{\text{phase}}}{\bar{Z}} \right)^*$ (5)

$$\Rightarrow \bar{Z} = \frac{3 \cdot 600 \cdot 600}{60 \times 10^3 (0.9 - j0.44)} = \underline{\underline{16.1 + j7.9 \ \Omega}} \quad (7)$$

$$= \underline{\underline{18.0 \angle 26.1^\circ \ \Omega}}$$

(b) In a delta-connected load: $V_{\text{line}}^{\text{load}} = V_{\text{phase}}^{\text{load}}$.

Also, the voltage given for the sources is a phase voltage

$$V_{\text{line}}^{\text{load}} = V_{\text{line}}^{\text{source}} = \sqrt{3} \cdot V_{\text{phase}}^{\text{source}}$$

$$= \sqrt{3} \cdot 312 = \underline{\underline{540 \text{ V}}} \quad (2)$$

$$\therefore V_{\text{phase}}^{\text{load}} = \underline{\underline{540 \text{ V}}} \quad \text{too} \quad (1)$$

(c) The phase current in one of the branches of the load is:

$$\bar{I}_{\text{phase}}^{\text{load}} = \frac{\bar{V}_{\text{phase}}^{\text{load}}}{\bar{Z}} = \frac{540 \angle 0^\circ}{18.0 \angle 26.1^\circ} = 30.0 \angle -26.1^\circ \quad (3)$$

$$\therefore \bar{I}_{\text{line}}^{\text{source}} = \sqrt{3} \bar{I}_{\text{phase}}^{\text{load}} \quad \text{for a } \Delta\text{-load.}$$

$$= \underline{\underline{520 \text{ A}}} \quad (2)$$

(d) Three phase complex power:

$$\bar{S}_{\text{load}} = 3 \cdot \bar{V}_{\text{phase}}^{\text{load}} (\bar{I}_{\text{phase}}^{\text{load}})^* \quad (2)$$

$$= 3 \cdot 540 \angle 0^\circ \cdot 30.0 \angle +26.1^\circ = 48.6 \angle 26.1^\circ$$

$$= \underline{\underline{43.7 + j21.2 \text{ kVA}}} \quad (3)$$

$$\begin{aligned}
 \textcircled{1} \quad \bar{V}_p &= \bar{V}_s' + [(R_s' + R_p) + j(X_s' + X_p)] \bar{I}_s' \quad \textcircled{3} \\
 &= 2400 + [11.6 + j58] [3.3 - j2.5] \\
 &= \underline{2583.3 + j162.4} \text{ V} \quad \textcircled{2} \\
 &= \underline{2588 / 3.6^\circ} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \bar{I}_p &= \bar{I}_s' + \frac{\bar{V}_p}{R_c' + jX_m'} \quad \textcircled{3} \\
 &= 3.3 - j2.5 + \frac{2583.3 + j162.4}{(46 + j23) \times 10^3} \\
 &= 3.3 - j2.5 + \underline{0.0463 - j0.0196} \\
 &= 3.35 - j2.52 \text{ A} \quad \bar{I}_\phi \\
 &= \underline{4.19 / -37.0^\circ} \text{ A} \quad \textcircled{2}
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{2} \quad \bar{E} &= \bar{V}_s' + (R_s' + jX_s') \bar{I}_s' \\
 &= 2400 + (5.8 + j29)(3.3 - j2.5) \\
 &= 2492 + j81.2 \text{ V} = 2493 / 1.9^\circ \quad \textcircled{2}
 \end{aligned}$$

$$\Rightarrow \bar{I}_c' = \frac{\bar{E}}{R_c'} = \frac{2493 / 1.9^\circ}{46 \times 10^3} = 0.054 / 1.9^\circ \text{ A} \quad \textcircled{2}$$

$$\bar{I}_m' = \frac{\bar{E}}{jX_m'} = \frac{2493 / 1.9^\circ}{23 \times 10^3 / 90^\circ} = 0.108 / -88.1^\circ \text{ A}$$

$$\Rightarrow P_{\text{loss, core}} = R_c' |\bar{I}_c'|^2 = 46 \times 10^3 \times 0.054^2 = 134 \text{ W}$$

$$\begin{aligned}
 \bar{V}_p &= \bar{E} + (R_p + jX_p)(\bar{I}_s' + \bar{I}_c' + \bar{I}_m') = \bar{E} + (R_p + jX_p) \bar{I}_p \\
 &= 2492 + j81.2 + (5.8 + j29)(3.3 - j2.5 + 0.054 + j0.002 \\
 &\quad + 0.004 - j0.108) \quad 4/
 \end{aligned}$$

$$\Rightarrow \bar{I}_p = \underline{3.36 - j2.61} \quad A = \underline{4.25 \angle -37.8^\circ} \quad A \quad (2)$$

$$\bar{V}_p = \underline{2587 + j164} \quad V = \underline{2592 \angle 3.6^\circ} \quad V \quad (2)$$

ii. From method (1)

$$P_{\text{loss, core}} = \frac{|\bar{V}_p|^2}{R_c} = \underline{146} \quad W \quad (2)$$

From (exact) method (2)

$$P_{\text{loss, core}} = \underline{134} \quad W. \quad (2)$$

iii. From method (1)

$$P_{\text{loss, copper}} = |\bar{I}_s'|^2 (R_s' + R_p) = \underline{199} \quad W \quad (3)$$

From (exact) method (2)

$$\begin{aligned} P_{\text{loss, copper}} &= |\bar{I}_p|^2 R_p + |\bar{I}_s'|^2 R_s' \\ &= 105 + 99 = \underline{204} \quad W \quad (3) \end{aligned}$$

(c) From method (1)

• \bar{V}_p with or without the mag: branch is the same. \Rightarrow No error. (2)

$$\begin{aligned} \text{• } \bar{I}_p: \text{ error} &= \left(1 - \frac{\bar{I}_p \text{ w/o}}{\bar{I}_p \text{ with}} \right) \times 100\% = \left(1 - \frac{I_s'}{\bar{I}_p} \right) \times 100\% \\ &= \left(1 - \frac{4.14}{4.19} \right) \times 100\% = 1.2\% \quad (3) \end{aligned}$$

From method (2)

$$\text{• } \bar{V}_p: \text{ error} = \left(1 - \frac{\bar{V}_p \text{ w/o}}{\bar{V}_p \text{ with}} \right) \times 100\%$$

$$= \left(1 - \frac{V_p \text{ method ①}}{V_p \text{ method ②}} \right) \times 100\%$$

$$= \left(1 - \frac{2588}{2592} \right) \times 100\% = \underline{\underline{0.15\%}} \quad \textcircled{2}$$


$$\circ \bar{I}_p: \text{ error} = \left(1 - \frac{\bar{I}_p \text{ w/o}}{\bar{I}_p \text{ with}} \right) \times 100\%$$

$$= \left(1 - \frac{\bar{I}_s'}{\bar{I}_p \text{ with}} \right) \times 100\% \quad \textcircled{3}$$

$$= \left(1 - \frac{4.14}{4.25} \right) \times 100\% = \underline{\underline{2.6\%}}$$

4/ (a) As $\mu \rightarrow \infty$ for the core, its reluctance is negligible. Moreover, the mmf contributed by the air gap winding does not affect the net core flux (because of its orientation).

So,

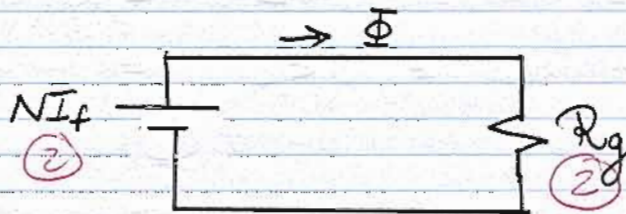

① Sketch + flux direction

$$\text{where } NI_f = 1000 I_f; \quad R_g = \frac{l_g}{\mu_0 A}$$


$$\textcircled{5} \quad NI_f = \mathcal{R}_g \Phi = \mathcal{R}_g BA \quad \textcircled{2}$$

$$\begin{aligned} \therefore I_f &= \frac{\mathcal{R}_g A}{N} B \\ &= \frac{l_g A}{N \mu_0 A} B \end{aligned}$$

$$= \frac{0.1}{1000 \times 4\pi \times 10^{-7}} \cdot 0.5 = \underline{\underline{39.8 A}} \quad \textcircled{3}$$


6/

(c)

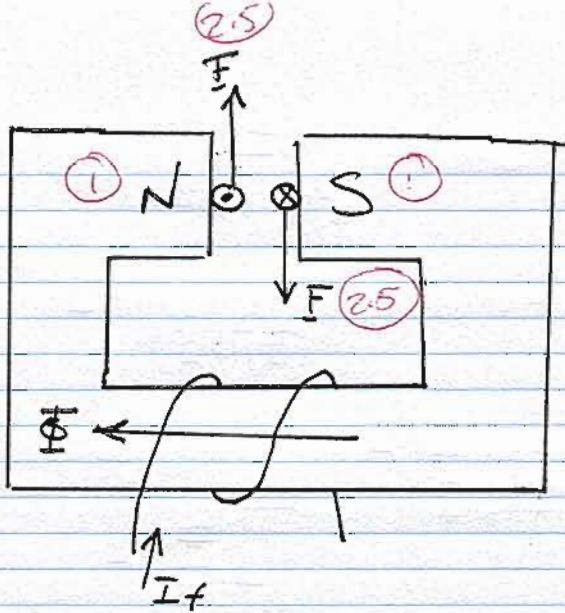

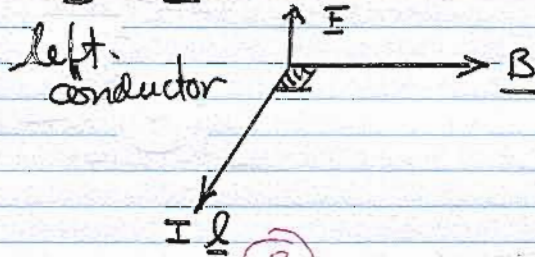(d) For each conductor:

$$\underline{F} = I \underline{l} \times \underline{B} \text{ where:}$$



$$\therefore |\underline{F}| = I l B = 100 \times 0.1 \times 0.5 = \underline{\underline{5 \text{ N}}} \text{ (1)}$$

The force is identical in magnitude on each conductor.

(e) See (c).