
Chapter 4

Combinational Logic

Combinational logic circuits

- outputs logical functions of inputs
- new outputs appear shortly after changed inputs (propagation delay)
- no feedback loops
- no clock

 


Fig. 4-1 Block Diagram of Combinational Circuit

Design Procedure

Design a circuit from a specification.

1. Determine number of required inputs and outputs.
2. Derive truth table (or K-Map)
3. Obtain simplified Boolean functions
4. Draw logic diagram (circuit) and verify correctness

Example: Code Converter

- A circuit that translates one binary code to another
- Example 3-2: **BCD to Excess-3 Code Converter**
 - Excess-3 code: decimal code + 3
 - BCD inputs 1010 to 1111 are don't care conditions

Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

1111100

Simplification with K-map

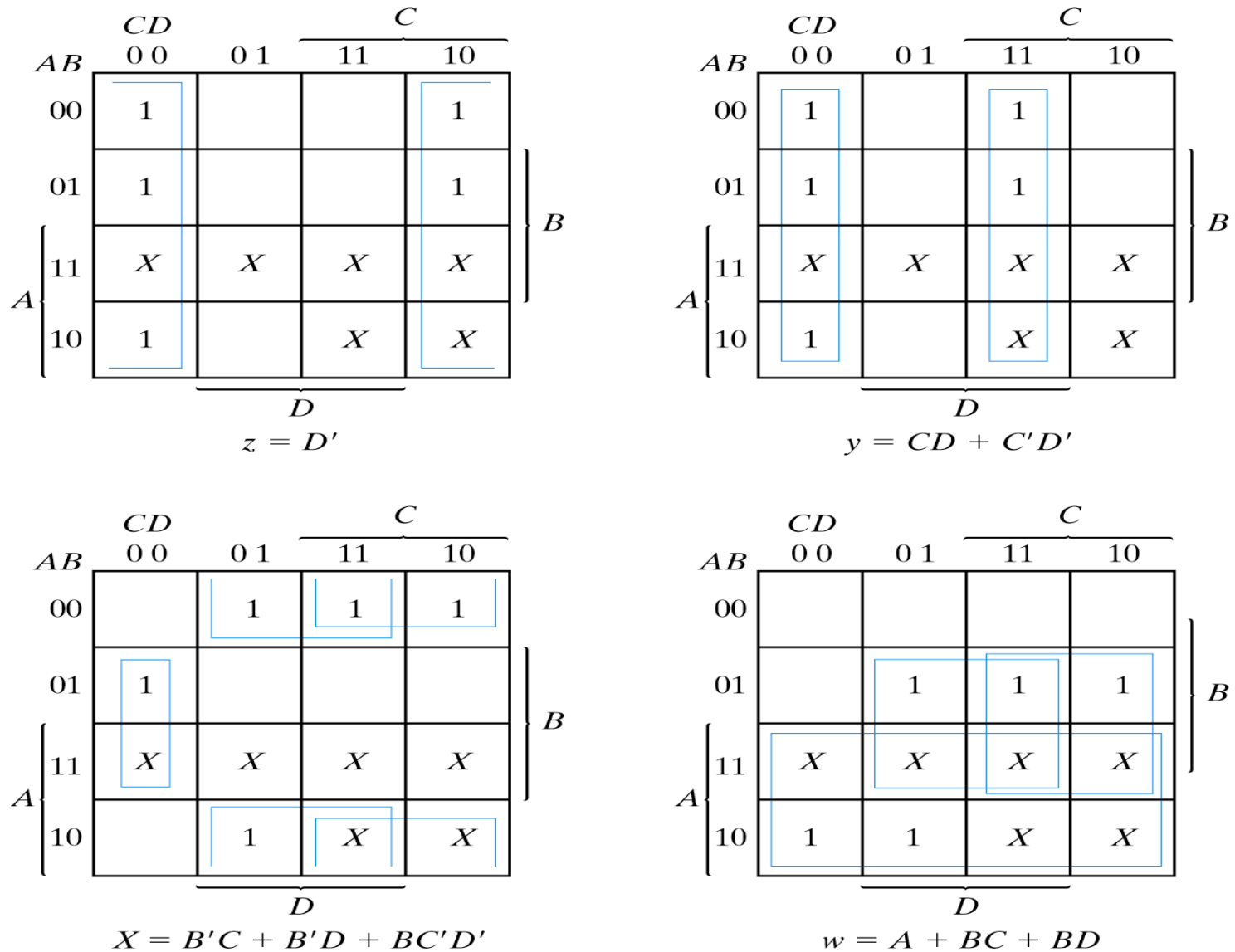


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

Further manipulation of simplified expressions

- Two-level AND-OR implementation for the circuit can be obtained directly from the Boolean expression derived from the K-MAPS.
- Further manipulation can be done on the function to allow use of common gates for **multiple-output circuits**.
- Thus there are several possibilities for the implementation. The following shows the implementation with 3 levels of gates.

$$W = A + BC + BD = A + B(C + D)$$

$$\begin{aligned} X &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C+D) + B(C+D)' \end{aligned}$$

$$Y = CD + C'D' = CD + (C + D)'$$

$$Z = D'$$

Three Level Implementation

 


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter
ITI1100


Binary Adder -Subtractor

Half Adder

→ The half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs: a sum bit and a carry bit.

Truth Table


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Half-Adder (see other implementations in Chap. 2)

Truth Table

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


Some of products


$$S = x'y + xy'$$

$$C = xy$$

Half-Adder-Implementation

 

$$(a) S = xy' + x'y$$
$$C = xy$$

 


$$(b) S = x \oplus y$$
$$C = xy$$

Fig. 4-5 Implementation of Half-Adder

Full Adder (see other implementations in Chap. 2)

Truth Table				
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 → The Full-adder is combinational circuit



Full Adder (see other implementations in Chap. 2)

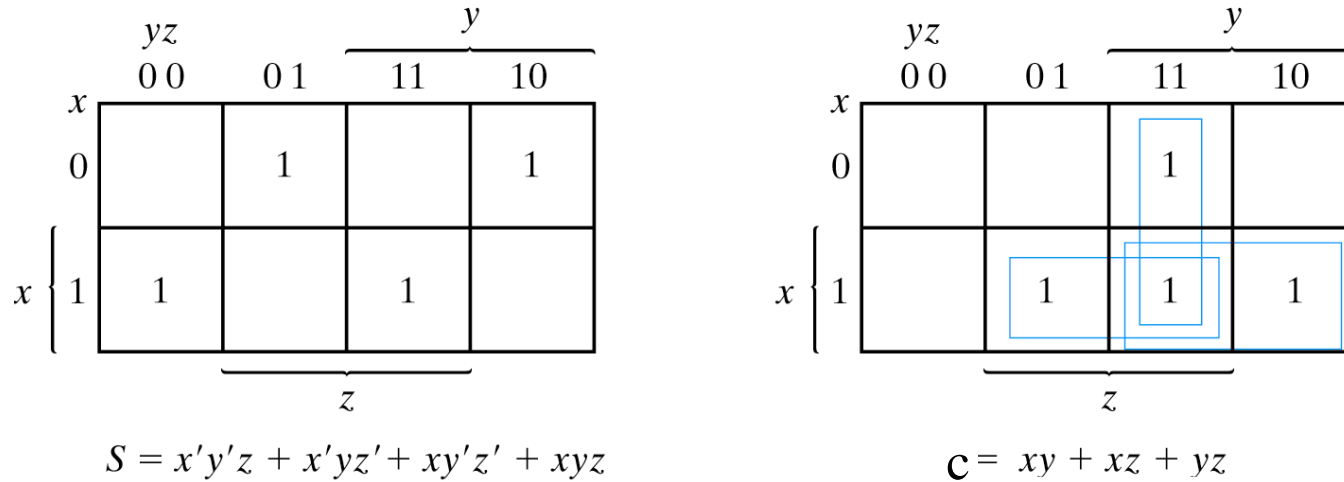


Fig. 4-6 Maps for Full Adder

Full Adder (see other implementations in Chap. 2)

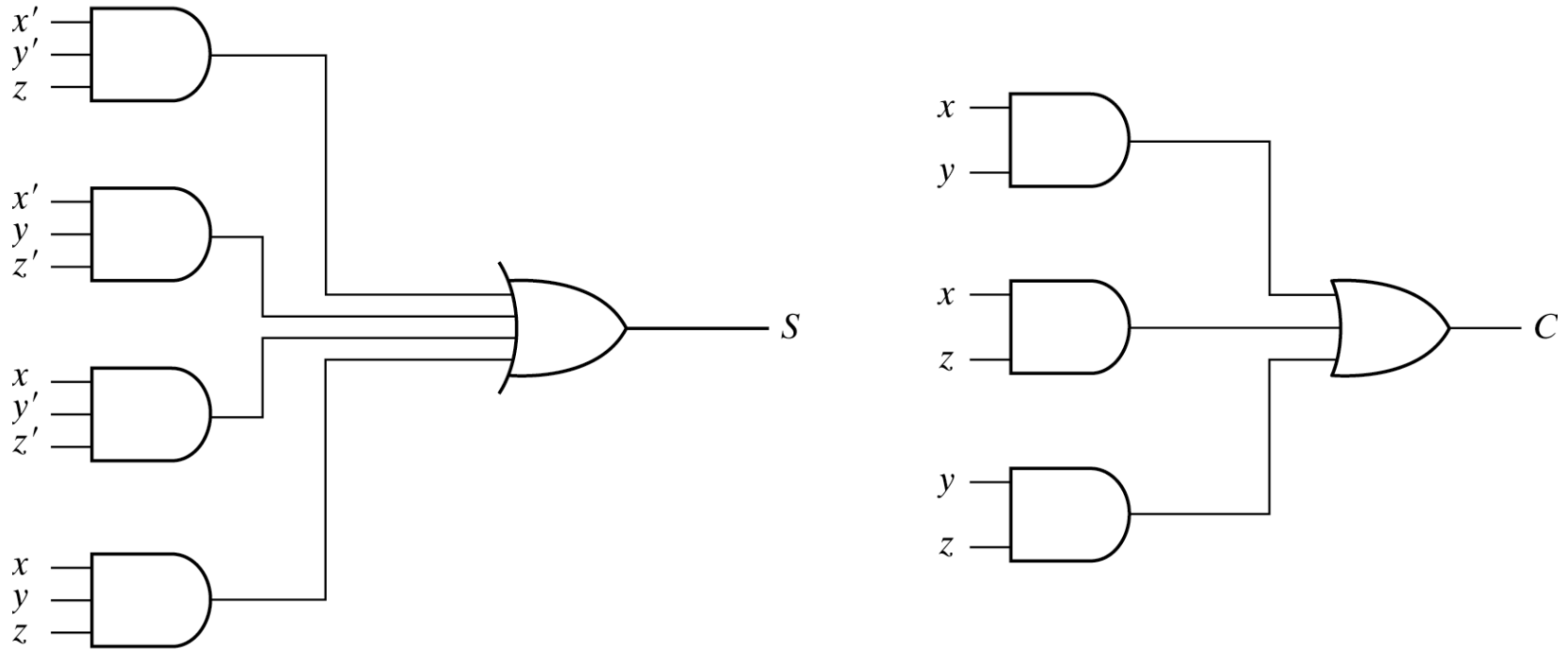


Fig. 4-7 Implementation of Full Adder in Sum of Products

Full Adder (same as in Chap. 2)


 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Decoder -Example

 a BCD to Seven Segment Decoder inputs data in BCD form and converts it to a seven segment output



(a) Segment designation





(b) Numerical designation for display

A- BCD to Seven Segment Decoder

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	0	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

Don't care terms

  

K-MAP

		CD			
		00	01	11	10
AB	00	1		1	1
	01		1	1	1
	11				
	10	1	1		

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1		1	
	11				
	10	1	1		

$a =$

$b =$





		CD			
		00	01	11	10
AB	00	1	1	1	
	01	1	1	1	1
	11				
	10	1	1		

		CD			
		00	01	11	10
AB	00	1		1	1
	01		1		1
	11				
	10	1	1		

$c =$

ITI1100

$d =$

    


g		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	1	1	0	1
	11	d	d	d	d
	10	1	1	d	d

$$g = BC' + B'C + CD' + A$$

Decoder

 - A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. \rightarrow n -to- 2^n decoder
- If the n -bit coded information has unused combinations \rightarrow less than 2^n outputs.
 \rightarrow n -to- m decoder, $m \leq 2^n$, Example: BCD-to-7-segment decoder, where $n=4$ and $m=7$



2-to-4 Decoder

→ A 2-to-4 decoder operates according to the following truth table.

- The 2-bit input is called S_1S_0 , and the four outputs are Q_0 - Q_3 .
- If the input is the binary number i , then output Q_i is uniquely true.

S_1	S_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- For example, if the input $S_1 S_0 = 10$ (decimal 2), then output Q_2 is true, and Q_0 , Q_1 , Q_3 are all false.
- This logic circuit “decodes” a binary number into a “one-of-four” code.

Building a 2-to-4 decoder?

- Same design procedure as for the combinational logic circuit (see previous slides). From the truth table, we can derive equations for each of the four outputs (Q0-Q3), based on the two inputs (S0-S1).

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- There is not much to be simplified. the equations are:

$$Q0 = S1' S0'$$


$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

Implementation of 2-to-4 decoder

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

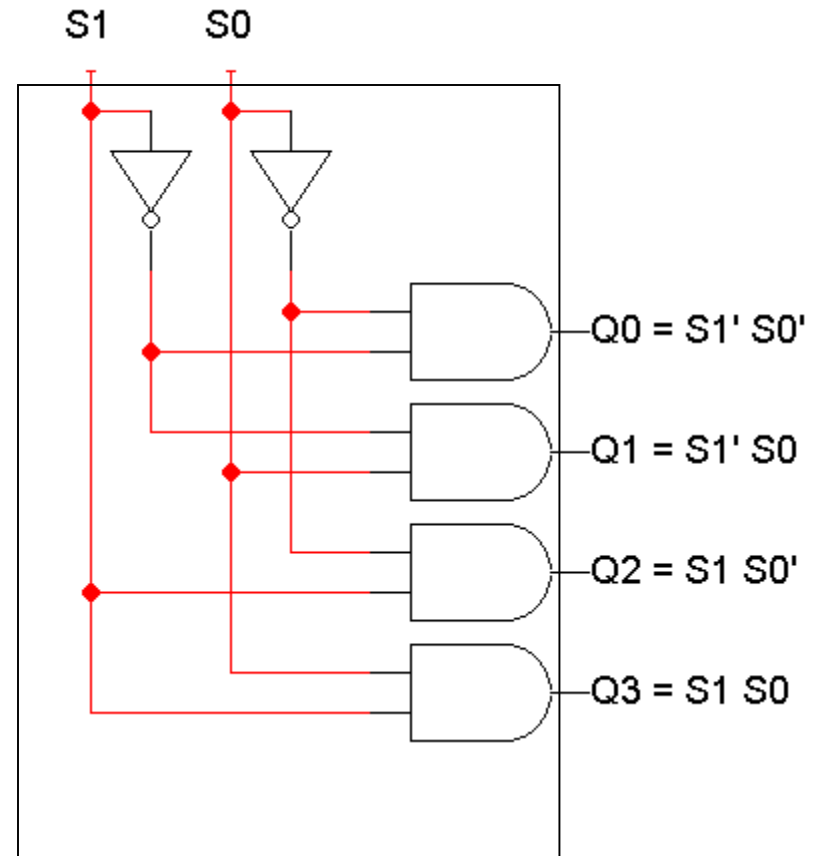

Enable inputs

- Many devices have an additional **enable input**, which is used to “activate” or “deactivate” the device.
- For a decoder,
 - EN=1 activates the decoder, so it behaves as specified earlier. Exactly one of the outputs will be 1.
 - EN=0 “deactivates” the decoder. By convention, that means *all* of the decoder’s outputs are 0.
- We can include this additional input in the decoder’s truth table:

EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

abbreviated truth tables

- In this table, note that whenever $EN=0$, the outputs are always 0, *regardless* of inputs $S1$ and $S0$.

EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

- We can abbreviate the table by writing x's in the input columns for $S1$ and $S0$.

EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Decoder- a Minterm Generator

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$Q0 = S1' S0'$$

$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$


$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**.
 - For each of the input combinations, exactly one output is true.
 - Each output equation contains all of the input variables.
 - These properties hold for all sizes of decoders.
- Therefore we can implement arbitrary functions with decoders.
→ **from a sum of minterms equation** for a function, we can use a decoder (a **minterm generator**) to implement that function.

3- to- 8 line Decoder

- Three inputs, x , y , z , are decoded into eight outputs, $D0$ through $D7$
- Each output D_i represents one of the **minterms** of the 3 input variables.
- $D_i = 1$ when the binary number $xyz = i$
- Shorthand: $D_i = m_i$
- The output variables are mutually exclusive; exactly one output has the value 1 at any time, and the other seven are 0.

3- to- 8 line Decoder

 


D6 is selected
D6 = 1 all others = 0

Fig. 4-18 3-to-8-Line Decoder

3- to- 8 line Decoder

Inputs			Outputs							
2	x_1	x_0	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

(b)

 

(c)

A 3-to-8-line decoder. (a) Logic diagram. (b) Truth table

Implementing Boolean Functions Using Decoders

- Any combinational circuit can be constructed using **decoders and OR gates!** Why?

→ **Here is an example:**

Implement a full adder circuit with a decoder and two OR gates.

Recall full adder equations, and let X, Y, and Z be the inputs:

$$S(X, Y, Z) = \Sigma m(1, 2, 4, 7)$$


$$C(X, Y, Z) = \Sigma m(3, 5, 6, 7).$$

- **Since there are 3 inputs and a total of 8 minterms, we need a 3-to-8 decoder.**

Implementing Boolean Functions Using Decoders


$$S(X,Y,Z) = \Sigma m(1,2,4,7)$$

$$C(X,Y,Z) = \Sigma m(3,5,6,7)$$

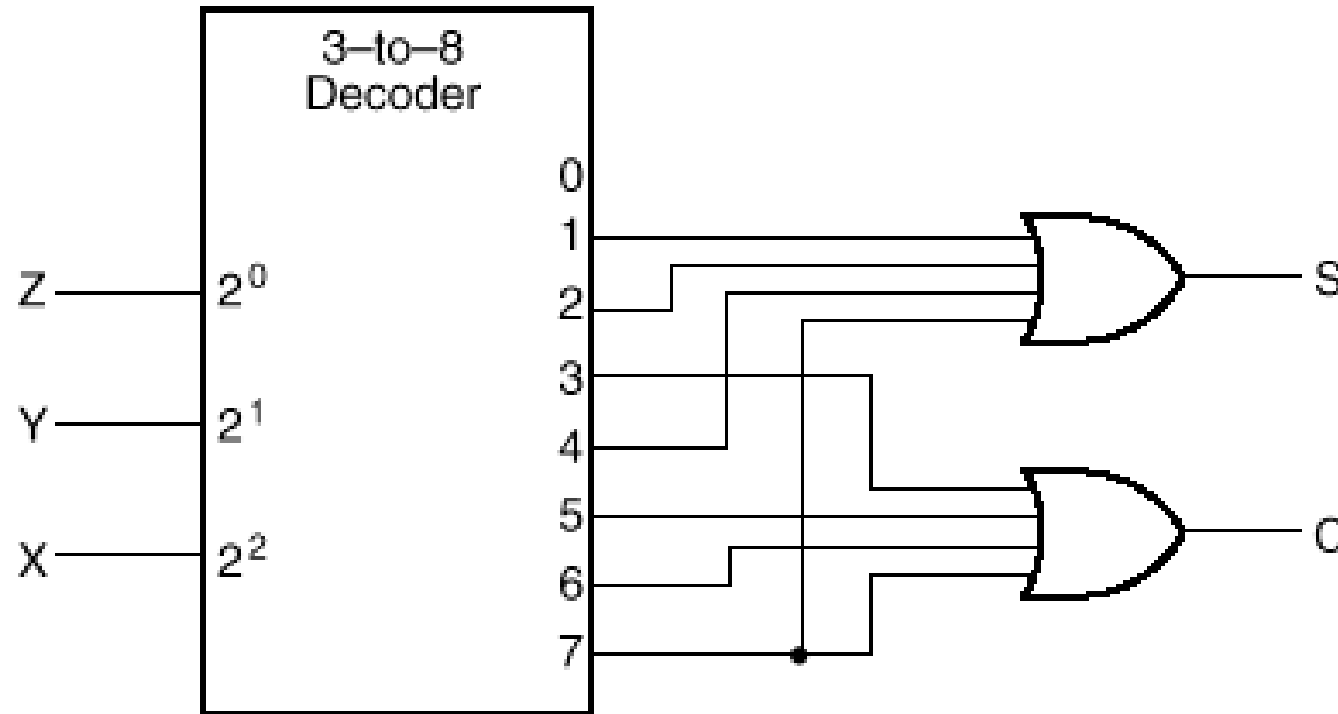


Implementing a decoder with NAND gates

 - The decoders studied so far are **active-high** decoders (i.e. implemented **with AND gates**)



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 
- Active-low decoders** are implemented **using NAND gates** (i.e. with an inverted EN input and inverted outputs).



EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1


Active-High and Active-Low decoders

 - Active-high decoders generate *minterms*, as we have already seen.




$$\begin{aligned} Q3 &= S1 S0 \\ Q2 &= S1 S0' \\ Q1 &= S1' S0 \\ Q0 &= S1' S0' \end{aligned}$$

 - Active-low decoders generate *Maxterms*.



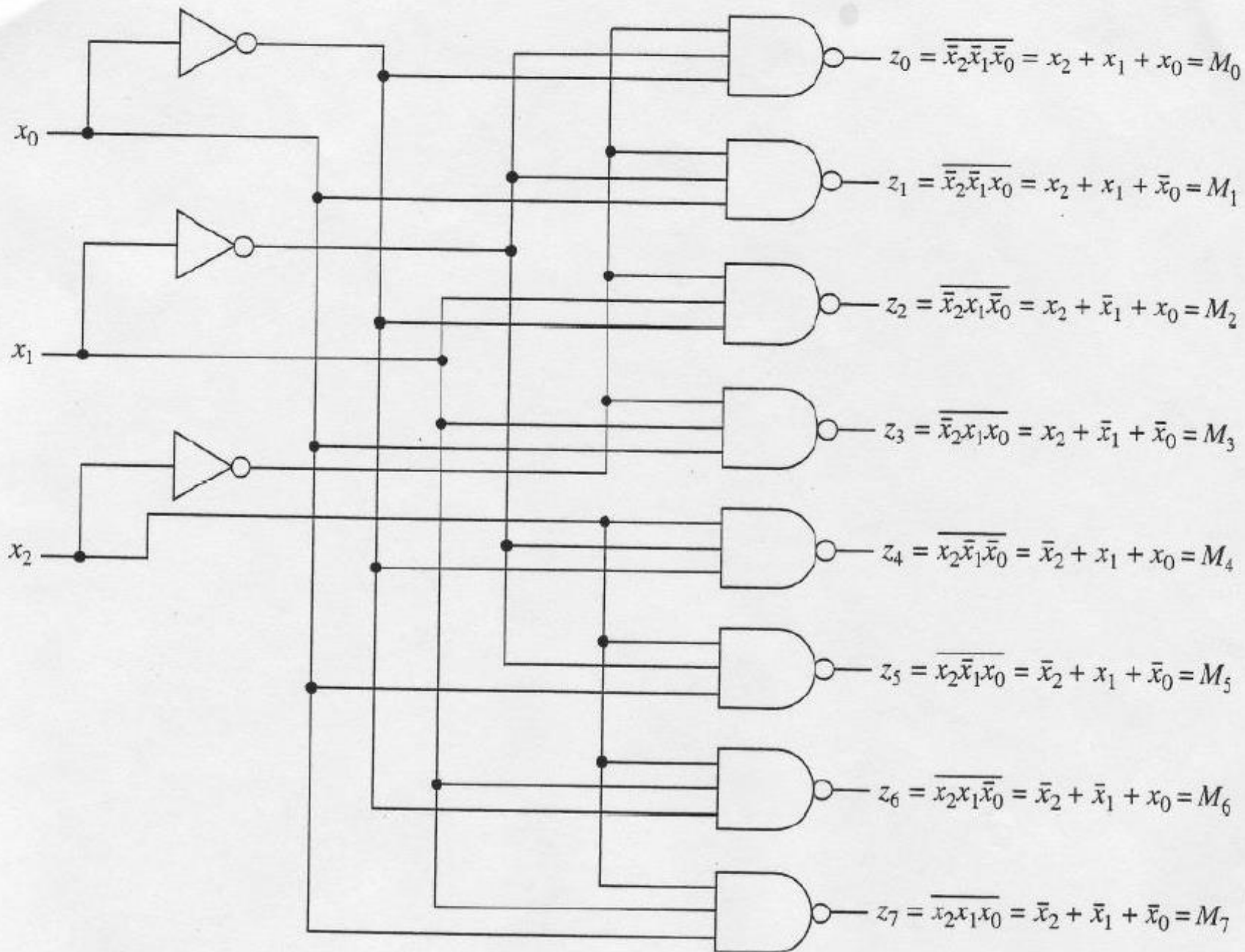
$$\begin{aligned} Q3' &= (S1 S0)' = S1' + S0' \\ Q2' &= (S1 S0')' = S1' + S0 \\ Q1' &= (S1' S0)' = S1 + S0' \\ Q0' &= (S1' S0')' = S1 + S0 \end{aligned}$$



Inputs			Outputs							
x_2	x_1	x_0	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	0

(b)

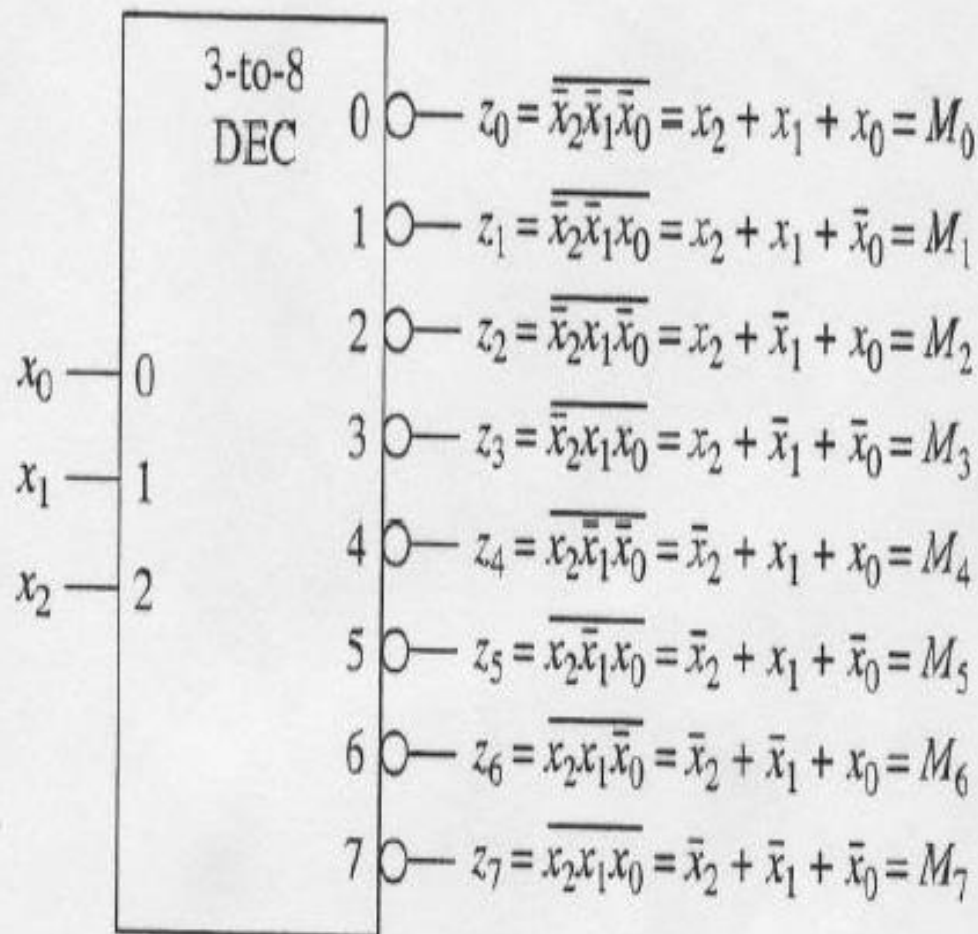

(c)

: A 3-to-8-line decoder using nand-gates. (a) Logic diagram.
 (b) Truth table. (c) Symbol.

Building a 3-to-8 decoder with two 2-to-4 decoders

- Another way to design a 3-to-8 decoder is to use two 2-to-4 decoders.
- from the truth table of 3-8 decoder we can notice some patterns:
 - When $S_2 = 0$, outputs Q_0 - Q_3 are generated as in a 2-to-4 decoder.
 - When $S_2 = 1$, outputs Q_4 - Q_7 are generated as in a 2-to-4 decoder.
- S_2 can be used as an **Enable input** that activates/deactivates the 2-to-4 decoders.

S_2	S_1	S_0	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q_0 = S_2' S_1' S_0' = m_0$$

$$Q_1 = S_2' S_1' S_0 = m_1$$

$$Q_2 = S_2' S_1 S_0' = m_2$$

$$Q_3 = S_2' S_1 S_0 = m_3$$

$$Q_4 = S_2 S_1' S_0' = m_4$$


$$Q_5 = S_2 S_1' S_0 = m_5$$

$$Q_6 = S_2 S_1 S_0' = m_6$$

$$Q_7 = S_2 S_1 S_0 = m_7$$

Building a 3-to-8 decoder with two 2-to-4 decoders

 
- We can use enable inputs to string decoders together. 3-to-8 decoder constructed from two 2-to-4 decoders:



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


Active-low decoder example

 - We can use active-low decoders to implement arbitrary functions as a product of maxterms.
- For example, here is an implementation of the function $f(x,y,z) = \prod M(4,5,7)$, using an active-low decoder.



- The “ground” symbol connected to EN represents logical 0, so this decoder is always enabled.
- We need an AND gate for a product of sums.

Another example of active-low decoder

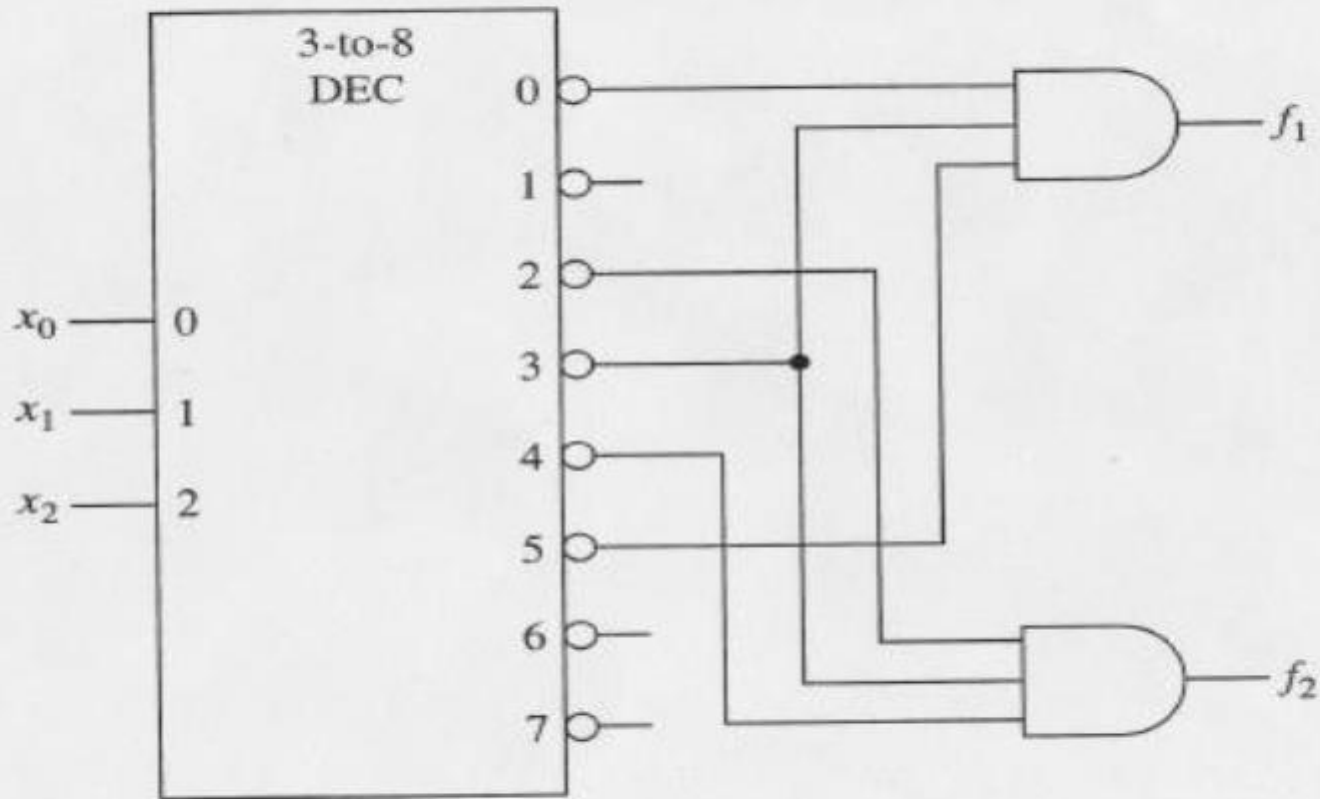

Realization of the pair of maxterm canonical expressions $f_1(x_2, x_1, x_0) = \Pi M(0, 3, 5)$ and $f_2(x_2, x_1, x_0) = \Pi M(2, 3, 4)$ with a 3-to-8-line decoder and two and-gates.

Decoder Expansions

- Larger decoders can be constructed using a number of smaller ones.

→ HIERARCHICAL design

- *Example:*

A 6-to-64 decoder can be designed using **four 4-to-16** and **one 2-to-4** decoders. How? (tip: Use the 2-to-4 decoder to generate the enable signals to the four 4-to-16 decoders).

4-input tree decoder

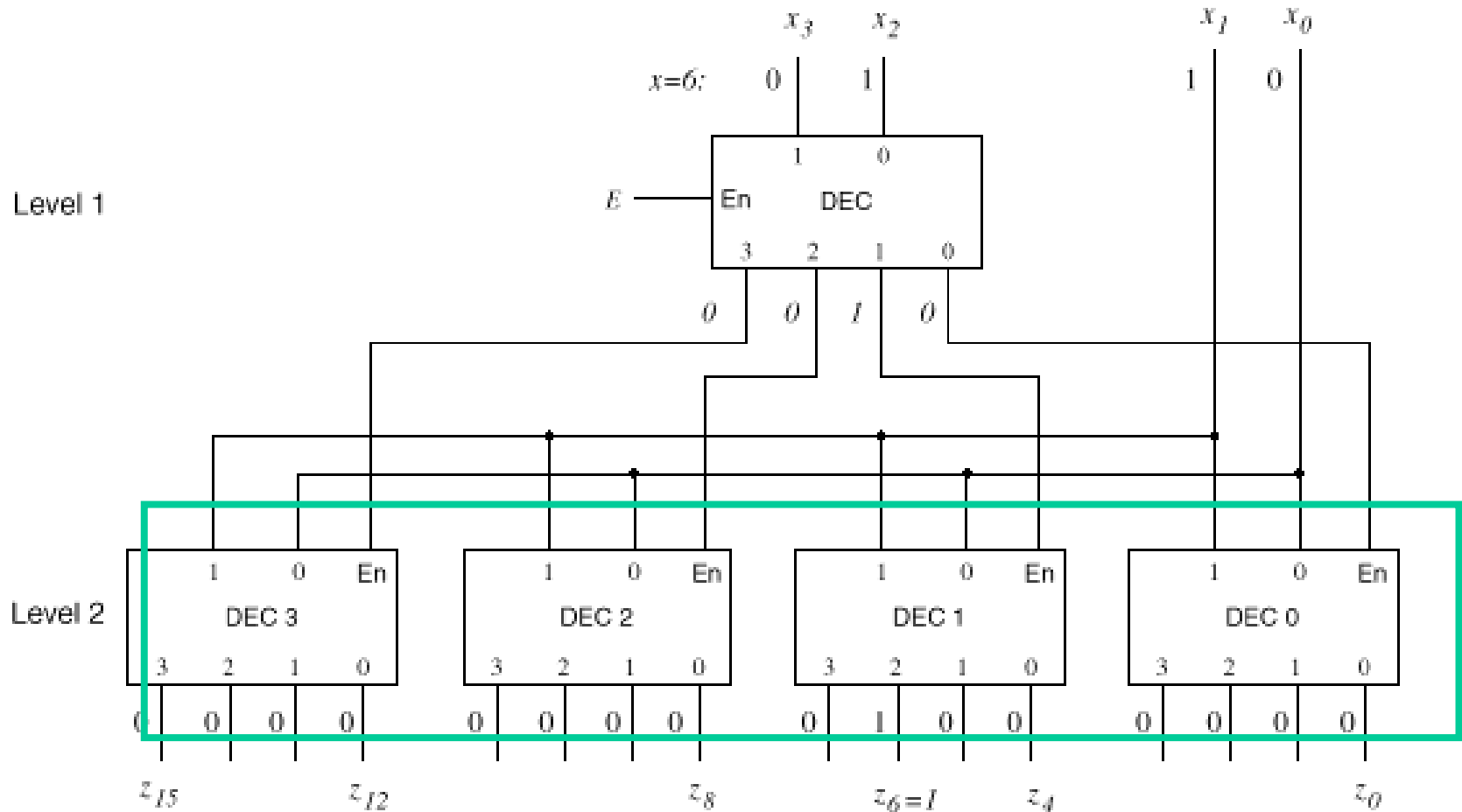


Figure 9.8: 4-input tree decoder

X3	X2	X1	X0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Binary Encoder

- An encoder has a number of input lines, only one of which is activated at a given time.
- The opposite of the decoding process.
- takes ALL its data inputs one at a time and then converts the one whose value is equal to "1" into a single encoded output


 


Figure 9.12: 2ⁿ-input binary encoder.

Binary Encoder

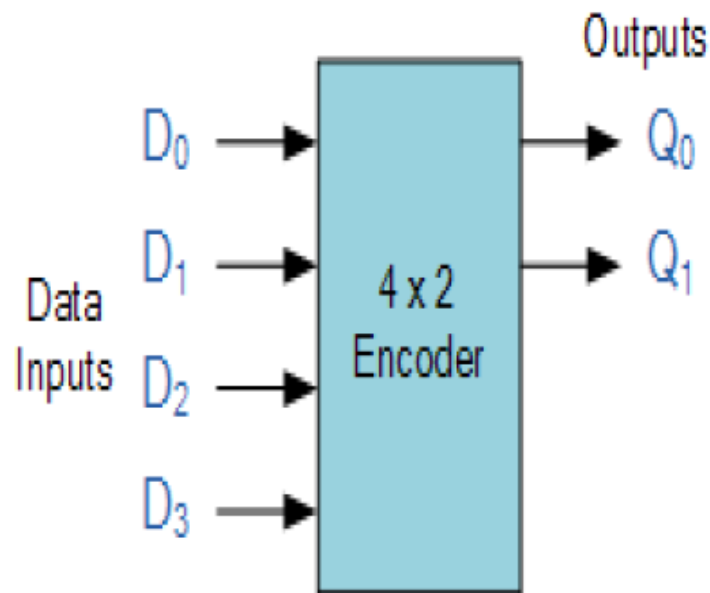- Encoders produce outputs of 2-bit, 3-bit or 4-bit codes (function of number of Data Inputs)
- An "n-bit" binary encoder has 2^n input lines and n-bit output lines with common types that include 4-to-2, 8-to-3 and 16-to-4 line configurations.



Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

Encoder

- An encoder has a number of input lines, **only one of which is activated at a given time.**
- The opposite of the decoding process.

 


Figure 9.12: 2^n -input binary encoder.

Binary Encoder

Example: 8-to-3 Encoder

x_7	x_6	x_5	x_4	x_3	x_2	x_1	x_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Binary Encoder

 


Figure 9.13: Implementation of an 8-input binary encoder.

Binary Encoder

- In the previous truth table each line selected (line 0 through 7) generates its own binary code such as a 1 is a 001, 5 is a 101 and so on.
- Boolean functions for Outputs

$$y_2 = x_4 + x_5 + x_6 + x_7$$

$$y_1 = x_2 + x_3 + x_6 + x_7$$

$$y_0 = x_1 + x_3 + x_5 + x_7$$

Simple Encoder Design Issues

- There are two ambiguities associated with the design of a simple encoder:
 - Only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination (for example, if x_3 and x_6 are 1 simultaneously, the output of the encoder will be 111. (110 and 011))
 - An output with all 0's can be generated when all the inputs are 0's, or when x_0 is equal to 1.

Priority Encoders

- Solves the ambiguities multiple assigned inputs are allowed; **one has priority over all others.**
- Separate indication of **not assigned** inputs (all inputs are 0s).



Example: 4-to-2 Priority Encoder Truth Table

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


4-to-2 Priority Encoder (cont.)

- The operation of the priority encoder is such that:
 - If two or more inputs are equal to 1 at the same time, the input in the highest-numbered position will take precedence.
 - A *valid output indicator*, designated by V , is set to 1 only when one or more inputs are equal to 1. $V = D_3 + D_2 + D_1 + D_0$ by inspection.

4-to-2 Priority Encoder (cont.)

  


4-to-2 Priority Encoder (cont.)

 


Multiplexer (MUX): Data Selectors

 - A multiplexer selects one of several input signals and passes it on to the output.
- Routing of selected data input to the output is controlled by SELECT inputs.



Multiplexer

 
- Multiplexers, or muxes, are used to choose between resources.
- A real-life example: in the old days before networking, several computers could share one printer through the use of a switch.



Multiplexer (MUX): Data Selectors [2]

- A combinational circuit with 2^n *data inputs*, 1 data output and a number of bit *control input* that select one of the data inputs

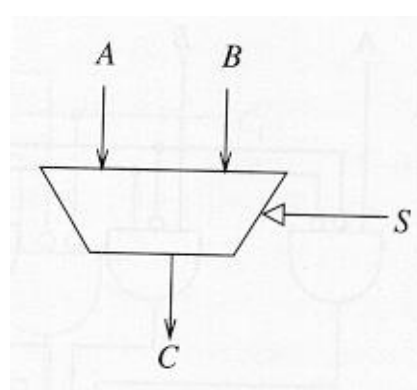C takes the value of A or B depending on the value of S



2-to-1 Multiplexer

S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


2-to-1 Multiplexer

When $S=0 \rightarrow C=A$, when $S=1 \rightarrow C=B$


$$C = S'AB' + S'AB + SA'B + SAB$$
$$= S'A + SB$$

Inputs			Output
S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Two level implementation

 

4 – 1 Multiplexer (MUX)

 

if $(S_1 S_0)_2 = 0$ Then $Y = I_0$

$$Y = S_1' S_0' I_0$$


if $(S_1 S_0)_2 = 1$ Then $Y = I_1$

$$Y = S_1' S_0 I_1$$

and so on, thus we have

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

4-1 MUX- Two level Implementation

 

(a) Logic diagram


s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

Fig. 4-25 4-to-1-Line Multiplexer

Demultiplexer (DEMUX): Data Distributor

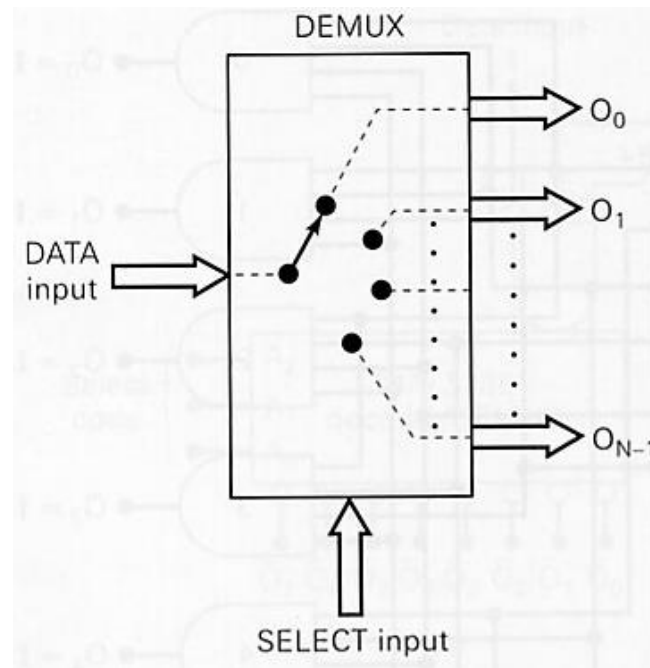
- Demultiplexer (DEMUX) takes a single input and distributes it over several outputs.



1-line-to-8-line Demultiplexer

SELECT code			OUTPUTS							
S_2	S_1	S_0	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

1-line-to-8-line Demultiplexer

 


Implementing functions with multiplexers

- Multiplexers can be used to implement arbitrary functions.
- One way to implement a function of n variables is to use an n -to-1 multiplexer
 - For each minterm m_i of the function, connect 1 data input D_i . Each data input corresponds to one row of the truth table.
 - Connect the function's input variables to select inputs. These are used to indicate a particular input combination.

Example, $f(x,y,z) = \sum m(1,2,6,7)$ can be implemented as follows


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Simplified Implementation (more efficient)

- We can actually implement $f(x,y,z) = \Sigma m(1,2,6,7)$ with just a 4-to-1 mux, instead of an 8-to-1.
- Step 1: Find the truth table for the function, and group the rows into pairs. Within each pair of rows, x and y are the same, so f is a function of z only.
 - When $xy=00$, $f=z$
 - When $xy=01$, $f=z'$
 - When $xy=10$, $f=0$
 - When $xy=11$, $f=1$
- Step 2: Connect the first two input variables of the truth table (here, x and y) to the select bits S1 S0 of the 4-to-1 mux.
- Step 3: Connect the equations above for f(z) to the data inputs D0-D3.


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Use of multiplexer to implement Boolean functions

x	y	z	F	
0	0	0	0	
0	0	1	1	$F = z$
0	1	0	1	
0	1	1	0	$F = z'$
1	0	0	0	
1	0	1	0	$F = 0$
1	1	0	1	
1	1	1	1	$F = 1$

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

Use of multiplexer to implement Boolean functions

- Implement the following Boolean function with a multiplexer

- $f(A,B,C,D) = \Sigma m (1,3,4,11, 12,13, 14,15)$

Use of multiplexer to implement Boolean functions

- $f(A,B,C,D) = \sum m (1,3,4,11, 12,13, 14,15)$ $n-1$ selection and 2 power $n-1$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	
0	0	0	1	1	$F = D$
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	$F = 0$
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

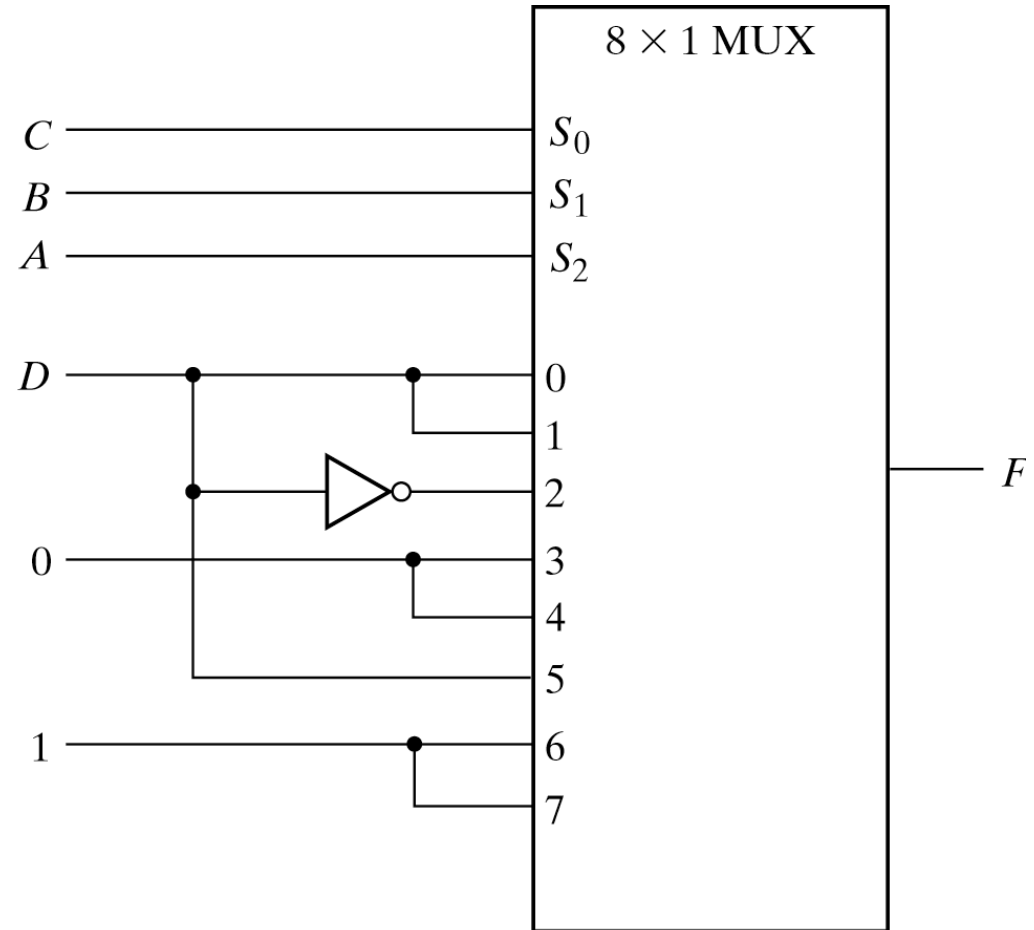


Fig. 4-28 Implementing a 4-Input Function with a Multiplexer

Examples- Combinational logic circuit

- Design a code converter that converts a decimal digit from the 8,4,-2,-1 to 8,4,2,1 code
 - Truth table
 - K-map for SOP

dec	<u>8 4 - 2 - 1</u>				<u>8 4 2 1</u>			
	A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	0	0
1	0	1	1	1	0	0	0	1
2	0	1	1	0	0	0	1	0
3	0	1	0	1	0	0	1	1
4	0	1	0	0	0	1	0	0
5	1	0	1	1	0	1	0	1
6	1	0	1	0	0	1	1	0
7	1	0	0	1	0	1	1	1
8	1	0	0	0	1	0	0	0
9	1	1	1	1	1	0	0	1

3/

	CD			
AB	00	01	11	10
00		X	X	X
01				
11	X	X	1	X
10	1			

X

	CD			
X	00	01	11	10
00		X	X	X
01	1			
11	X	X		X
10		1	1	1

y/

	CD			
AB	00	01	11	10
00		X	X	X
01		1		1
11	X	X		X
10		1		1

$$W = AB + AC'D'$$

$$X = B'C + B'D + BC'D'$$

$$y = CD' + C'D$$

$$z = D \text{ (by inspection)}$$

Example – Previous Exam Questions

Consider the following truth table

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	x
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	x
1	1	1	1	x

1- Obtain product of sums for F.


2- Simplify F in its Product of sums from using K-Map

3- Obtain the circuit diagram for F using NAND gates only.
Use gates with multiple inputs when needed.

Use of decoder to implement Boolean functions

- A combinational circuit is specified by the following three Boolean functions:
- $f_1(A,B,C) = \Sigma m(2,4,7)$
- $f_2(A,B,C) = \Sigma m(0,3)$
- $f_3(A,B,C) = \Sigma m(0,2,3,4,7)$

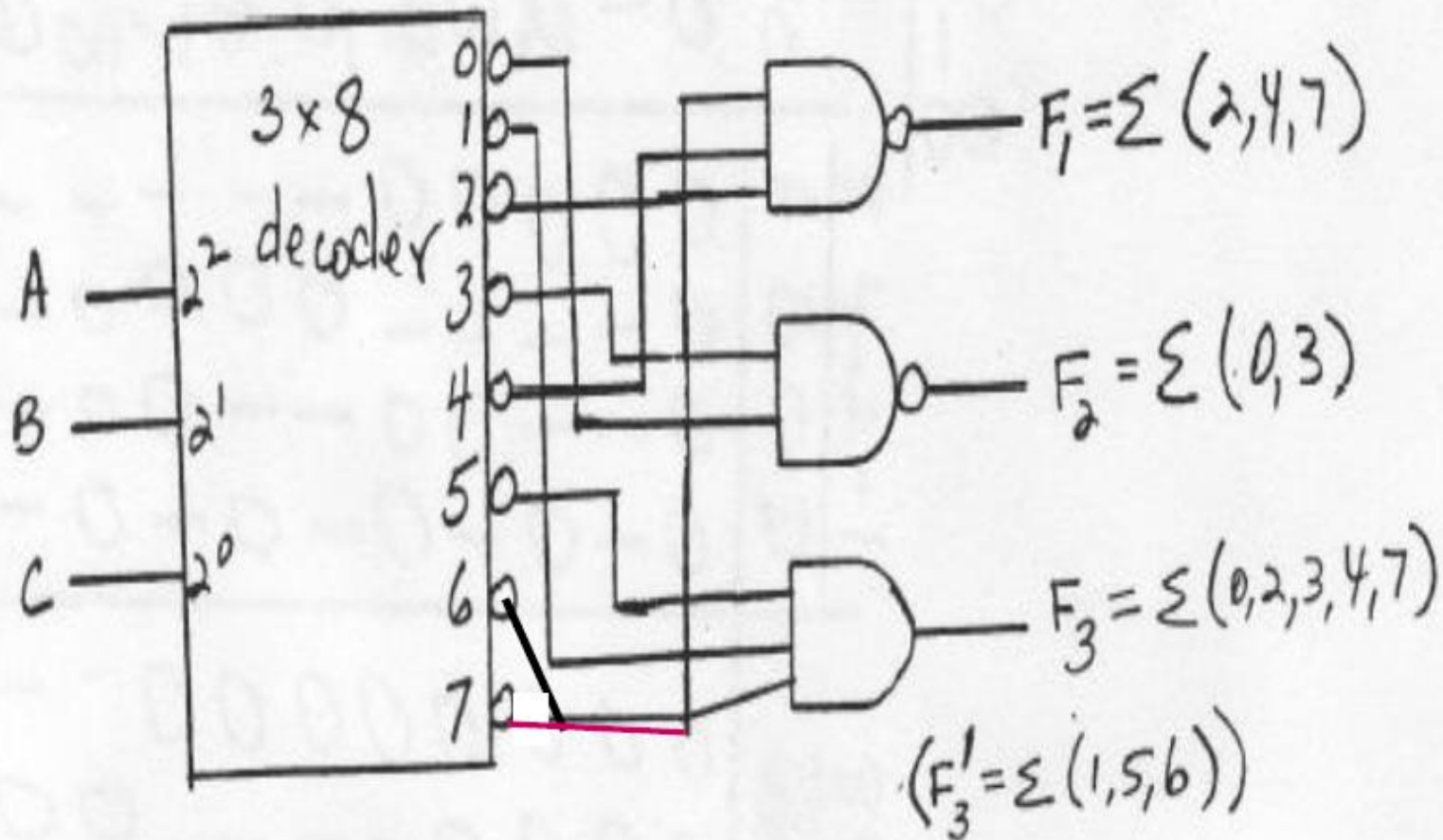Implement the circuit with an active low decoder (constructed with NAND) and NAND or AND gates connected to the decoder outputs. Use the block diagram for the decoder and minimize the number of inputs in the external gates



Other Combinational circuit examples

The following examples will be done in the DGD


- 4 bit Magnitude Comparator
- 4 bit by 3 bit Binary Multiplier
- Decimal Adder
- 7 segment decoder (started in the class) will be explained in lab 3

Analyzing digital circuits

- Important concept – analyzing digital circuits
 - Given a circuit
 - Create a truth table
 - Create a minimized circuit
- Approaches
 - Boolean expression approach
 - Truth table approach


From a logic circuit to equation/ Truth table

 - How can we convert from a circuit drawing to an equation or truth table?
- Two approaches
 - Create intermediate equations
 - Create intermediate truth tables



Label Gate Outputs


1. Label all gate outputs that are a function of input variables.
2. Label gates that are a function of input variables and previously labeled gates.
3. Repeat process until all outputs are labeled.

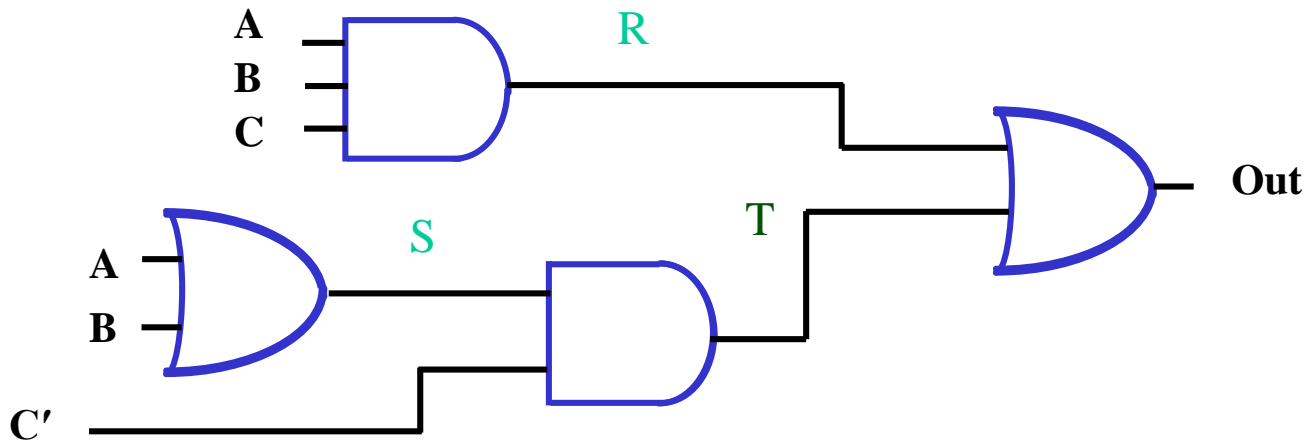

Approach 1: Create Intermediate Equations

➤ **Step 1: Create an equation for each gate output based on its input.**

- **$R = ABC$**
- **$S = A + B$**
- **$T = C'S$**
- **$Out = R + T$**

 


Approach 1: Substitute in sub expressions

➤ Step 2: Form a relationship based on input variables

(A, B, C)


- $R = ABC$
- $S = A + B$
- $T = C'S = C'(A + B)$
- $\text{Out} = RT = ABC + C'(A+B)$

 

Approach 1: Substitute in sub expressions

➤ Step 3: Expand equation to SOP final result


- **Out = ABC + C'(A+B) = ABC + AC' + BC'**

 

Approach 2: Truth Table

- **Step 1: Determine outputs for functions of input variables.**

A	B	C	R	S
0	0	0	0	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

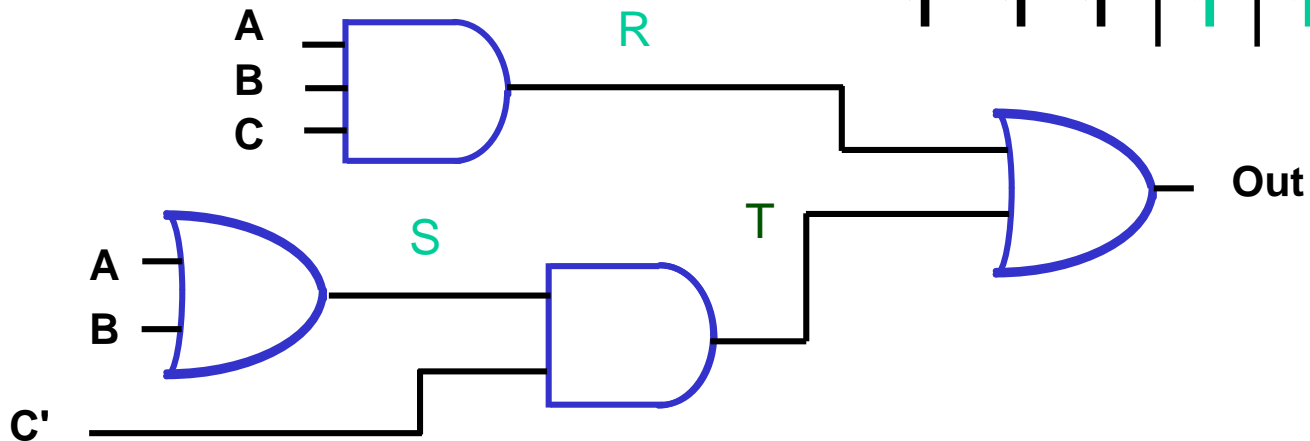


Approach 2: Truth Table

- **Step 2: Determine outputs for functions of intermediate variables.**

$$T = S C'$$

A	B	C	C'	R	S	T
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	1	1	0

 


Approach 2: Truth Table

- Step 3: Determine outputs for function.

$$R + T = \text{Out}$$

A	B	C	R	S	T	Out
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	0	1	1	1
1	1	1	1	1	0	1

 

More Difficult Example

➤ **Note labels on interior nodes**

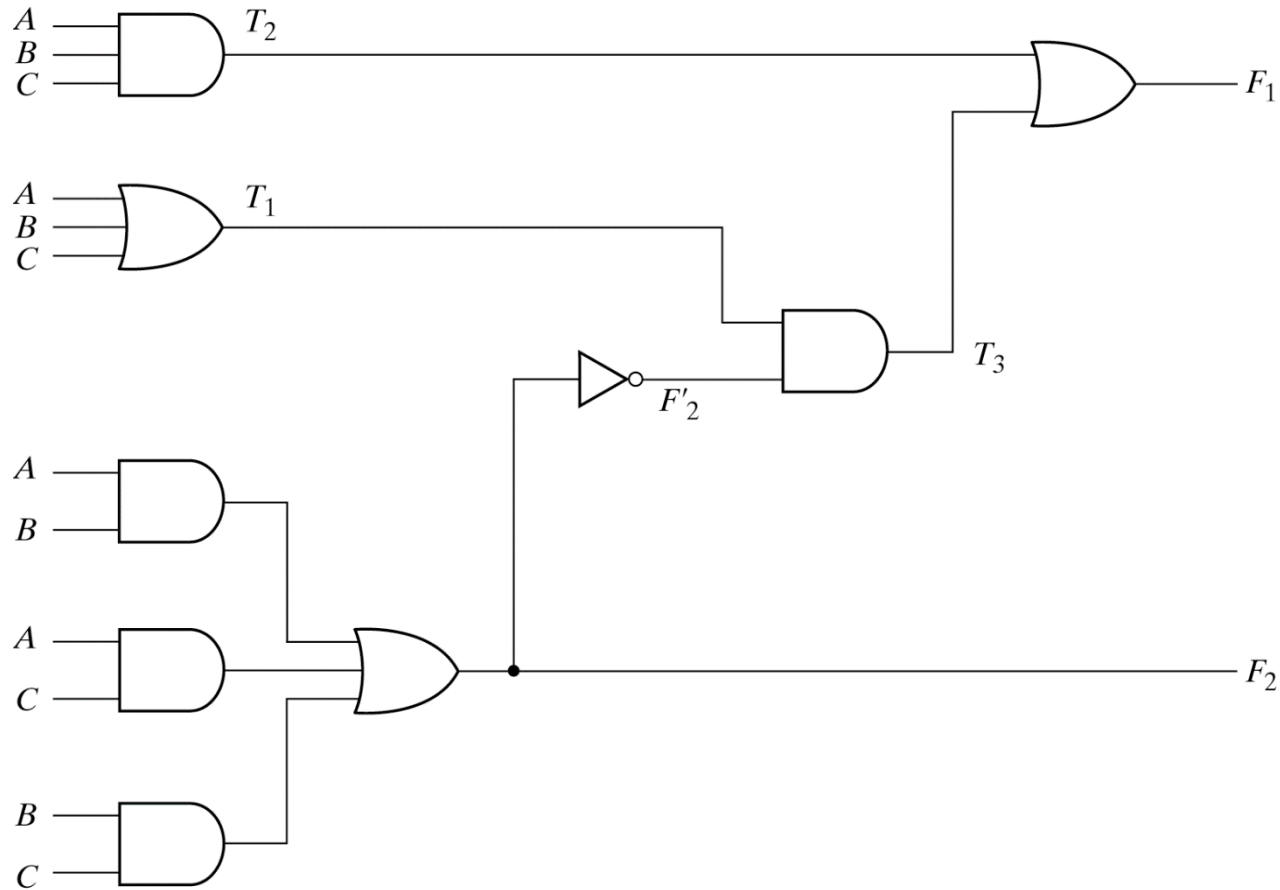


Fig. 4-2 Logic Diagram for Analysis Example


More Difficult Example: Truth Table

- Remember to determine intermediate variables starting from the inputs.
- When all inputs are determined for a gate, determine output.
- The truth table can be reduced using K-maps.

A	B	C	F_2	F'_2	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1



Parallel Adder

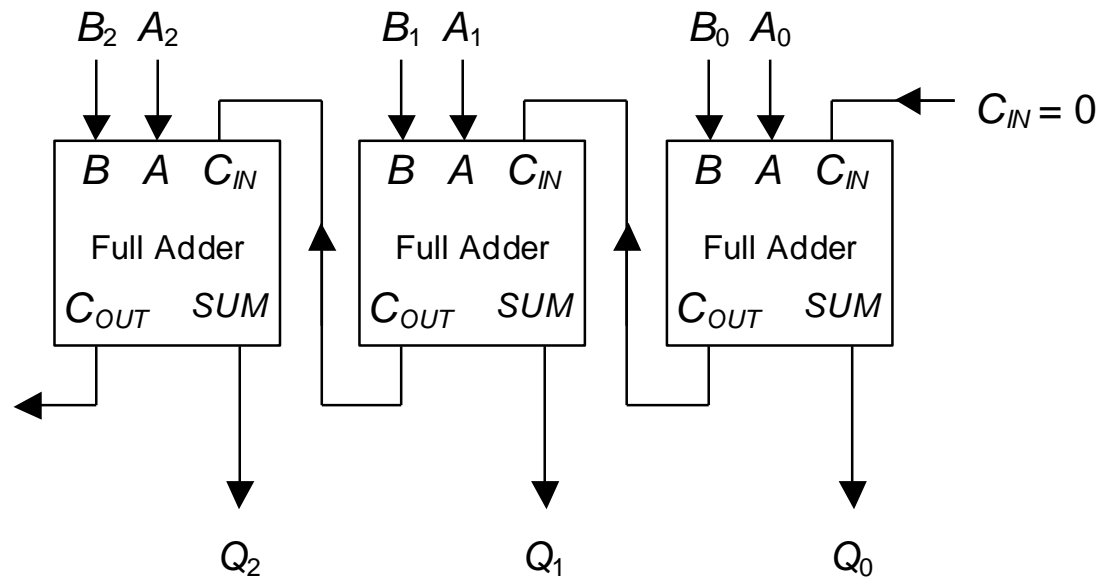- Recall that to add two n -bit numbers together, n full-adders should be cascaded.
- Each full-adder represents a column in the long addition.
- The carry signals ‘ripple’ through the adder from right to left.





Propagation Delay

  - All logic gates take a non-zero time delay to respond to a change in input.
- This is the *propagation delay* of the gate, typically measured in tens of nanoseconds.




Full Adder (Quartus)

 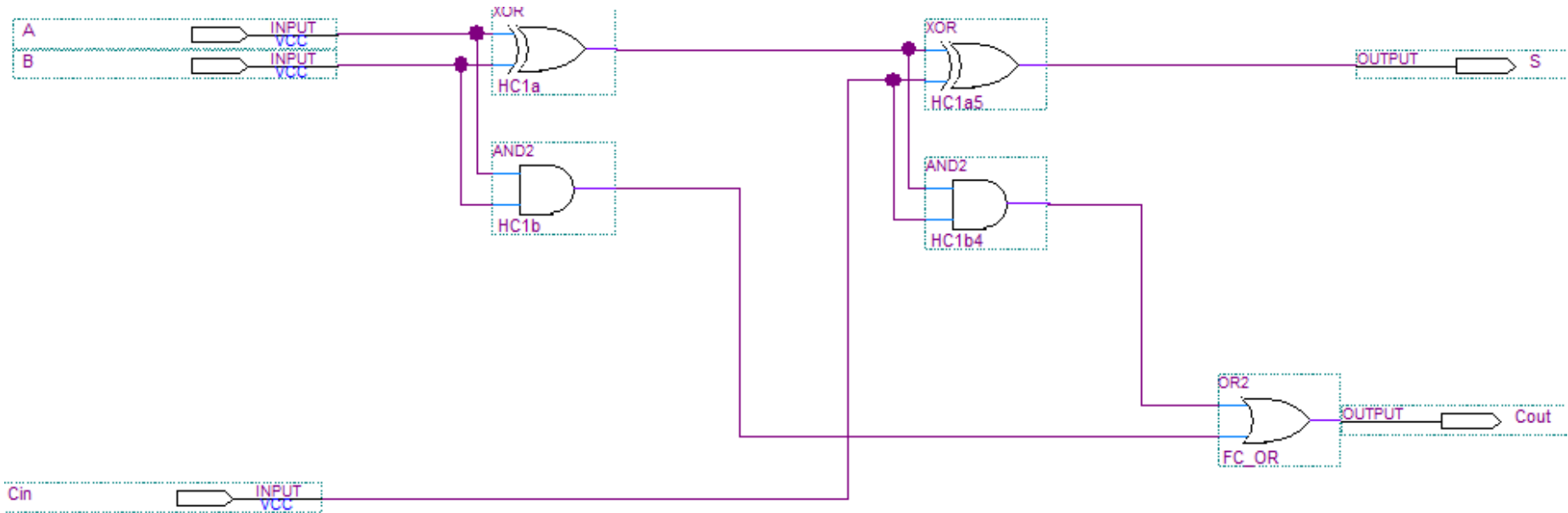

Carry Ripple

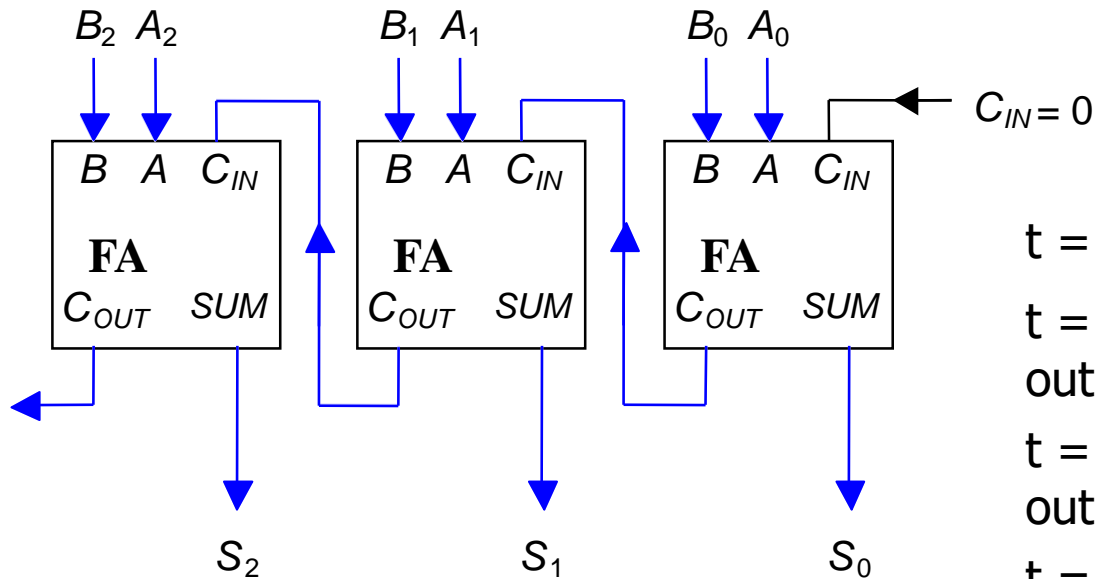- A and B inputs change, corresponding changes to C_{IN} inputs 'ripple' through the circuit.




$t = 0$, A & B change

$t = 30 \text{ ns}$, Adder 0
outputs respond

$t = 60 \text{ ns}$, Adder 1
outputs respond

$t = 90 \text{ ns}$, Adder 2
outputs respond

Carry Ripple Delay (8 bit Adder)

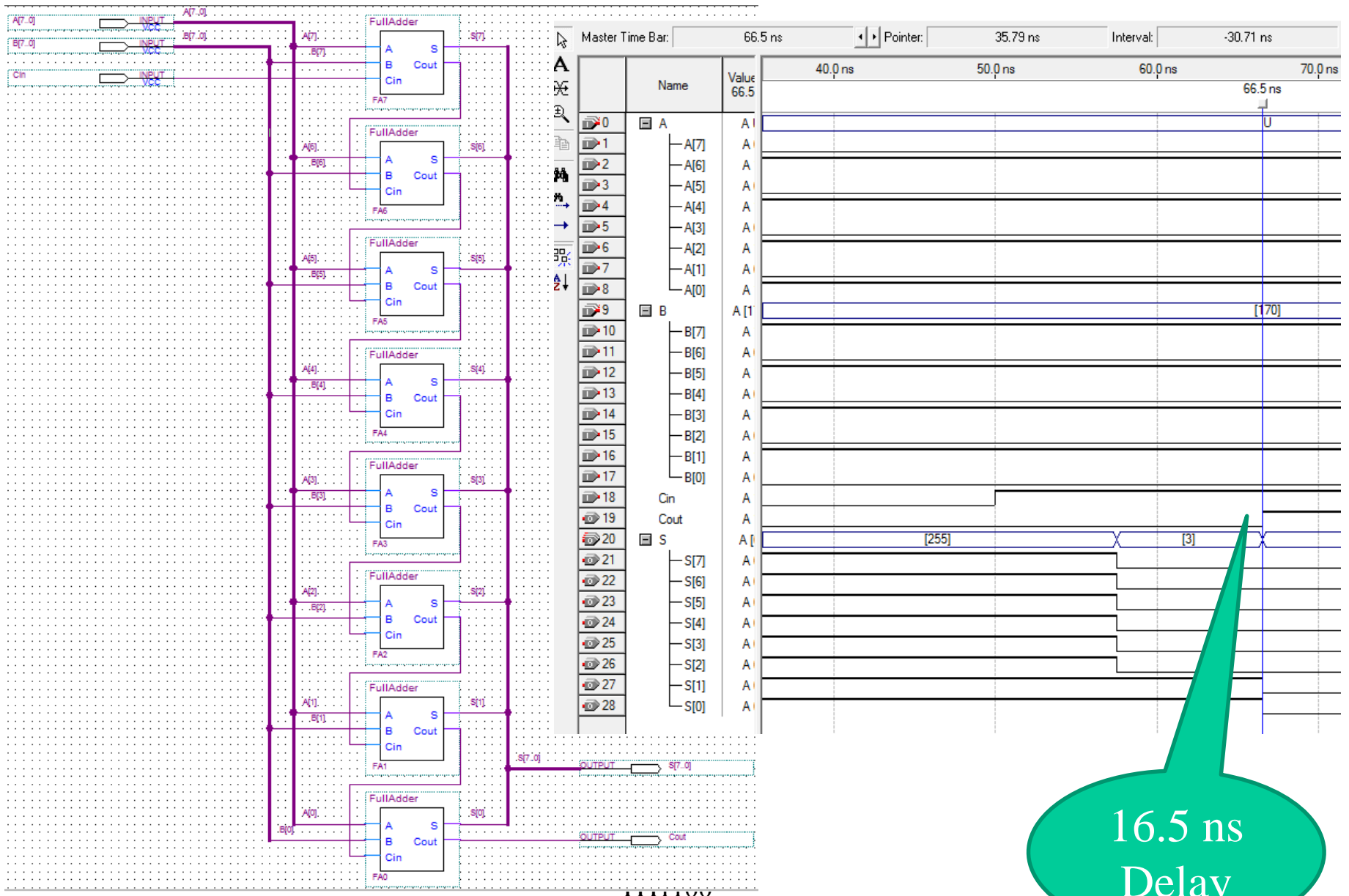


16.5 ns
Delay

Carry-Look-Ahead

- The accumulated delay in large parallel adders can be very large.
- Example : 16 bits using 30 ns full-adders :
$$16 \times 30 \text{ ns} = 480 \text{ ns}$$
- Solution : Generate the carry-input signals directly from the A and B inputs rather than using the ripple arrangement.

Designing a Carry-Look-Ahead Circuit

 

$$C_{IN0} = C_{IN}$$

$$C_{IN1} = C_{OUT0}$$

$$= C_{IN}(A_0 + B_0) + A_0B_0$$

$$C_{IN2} = C_{OUT1}$$

$$= C_{IN1}(A_1 + B_1) + A_1B_1$$

$$= [C_{IN}(A_0 + B_0) + A_0B_0](A_1 + B_1) + A_1B_1$$

Binary Multiplier Circuit

$$\begin{array}{r} B_1 \\ A_1 \\ \hline A_0 B_1 B_0 \\ A_1 B_1 B_0 \\ \hline C_3 C_2 C_1 \\ C_1 \\ C_0 \end{array}$$

- The AND gates produce the partial products.
- For a 2-bit by 2-bit multiplier, we can just use two half adders to sum the partial products.
- Here C3-C0 are the product, not carries!

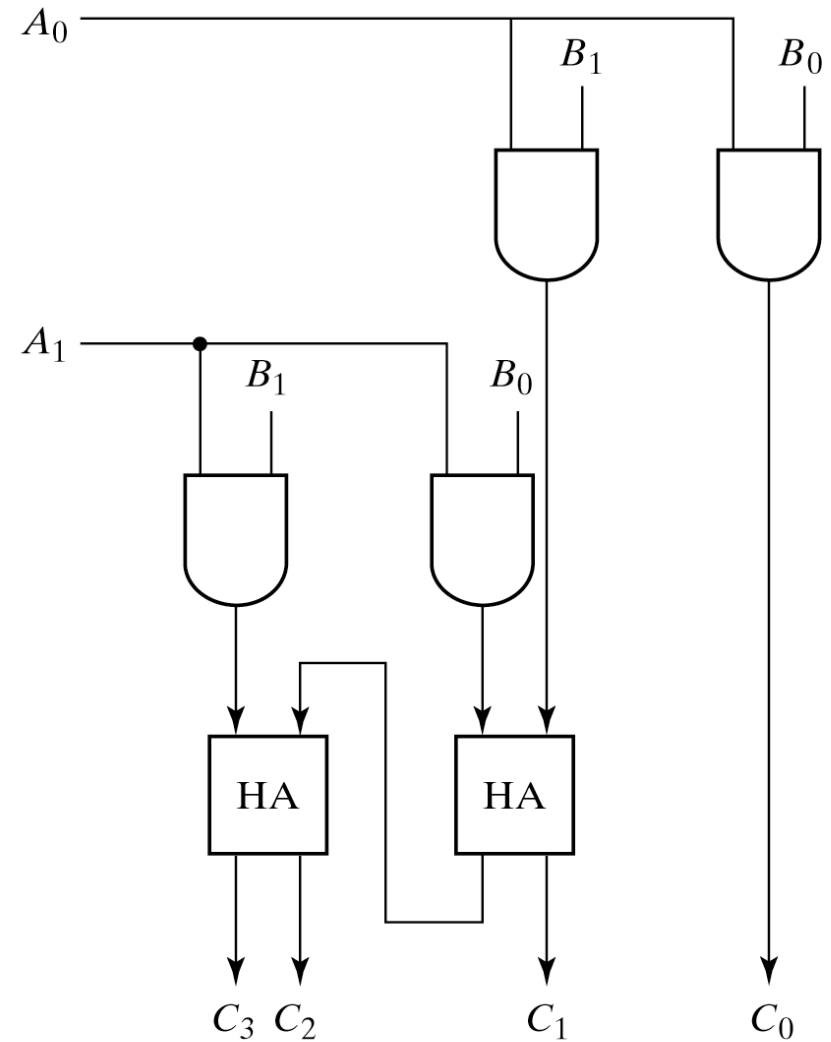


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier
ITI1100

4-bit by 3-bit binary multiplier

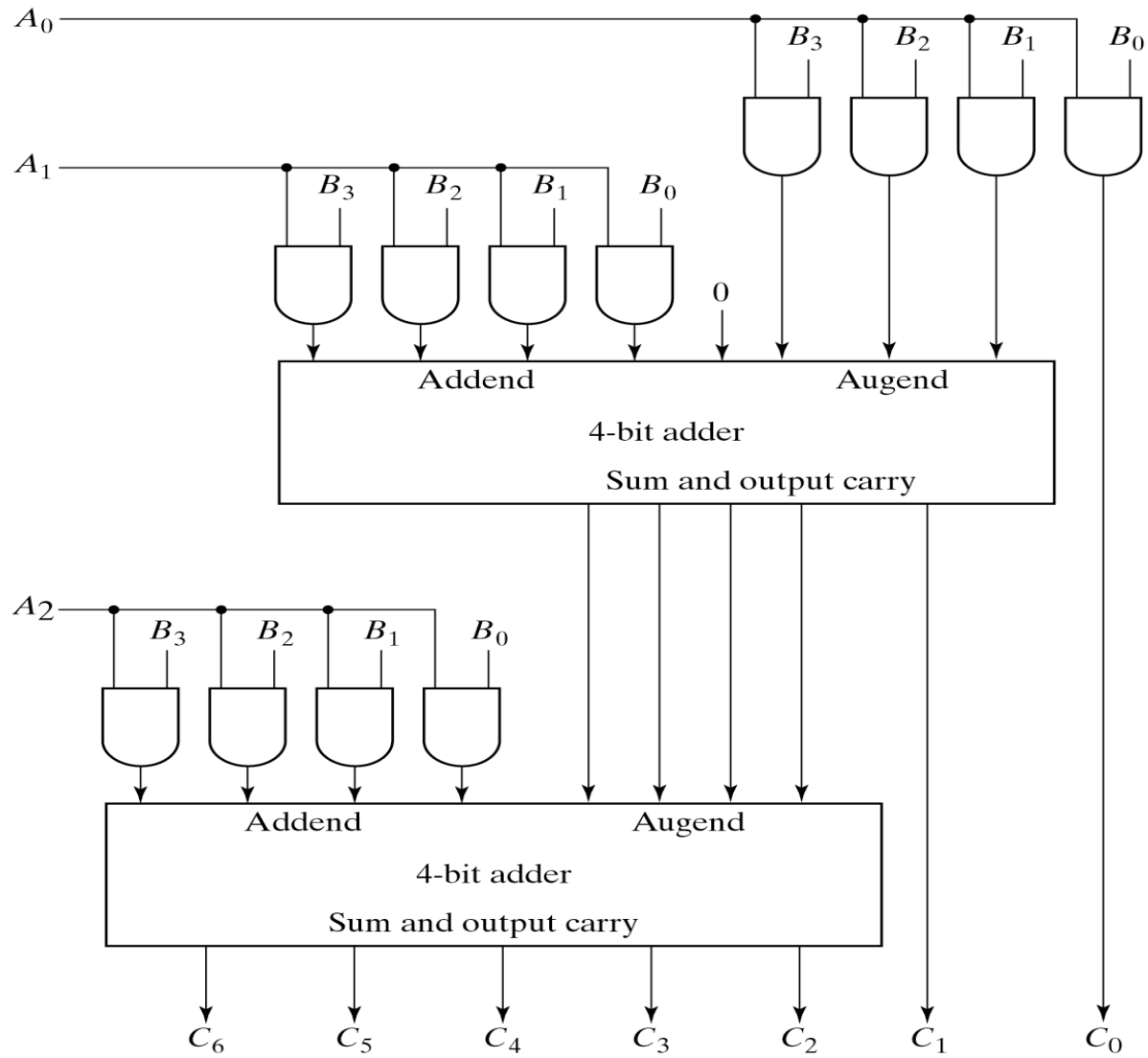


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier
ITI1100

Conclusions

- Combinational Circuits
- Techniques for design of combinational circuits
 - Boolean algebra
 - K-Maps
 - And ???
- Useful Combinational Circuits for Design of other Circuits
 - Decoders
 - Multiplexors
- Circuits Studied
 - Arithmetic circuits (adder, subtractor, multiplier, magnitude comparator)
 - Decoders/Encoders
 - Multiplexers/Demultiplexers
- Next up: Sequential Circuits – Lets see what feedback and time can do for us.