

Ryerson University
 Department of Electrical and Computer Engineering
Final Examination, EES512 Electric Circuits
Duration: Bonus Test: 1.5 Hours, Optional Test: 2 Hours
 April 2012

Student's Name:..... Student Number:

NOTES:

- This is a **closed book, and closed course note examination.**
- **There are 9 questions. Answer all questions.** Marks for each question and its parts are mentioned. **Hand in this exam questionnaire with your solution booklet.**
- This exam is very clear in its contents and intentions. **NO QUESTIONS is allowed.** If doubt exists as to the interpretation of any question, you are urged to submit with the answer, a clear statement of any logical assumptions made.

Question	Mark	Mark obtained
Q1	10	
Q2	10	
Q3	10	
Q4	5	
Q5	3	
Q6	12	
Q7	10	
Q8	10	
Q9	10	
Total	80	

=====

Student's Name:.....


Student Number:.....

Signature:.....


Name:

I.D.:


for time to frequency Conversion

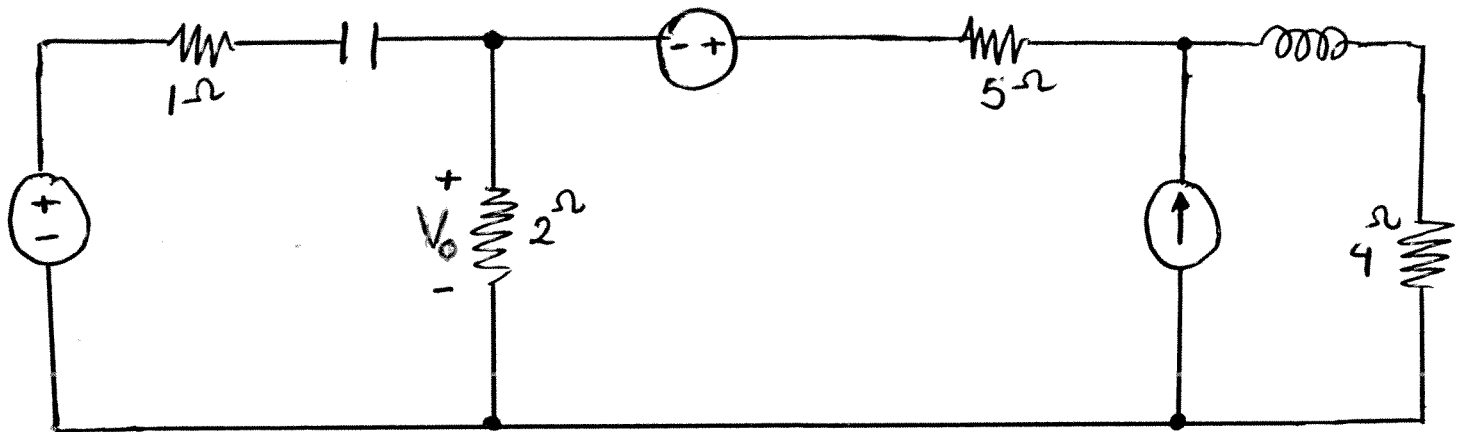

for Mesh or Super mesh:

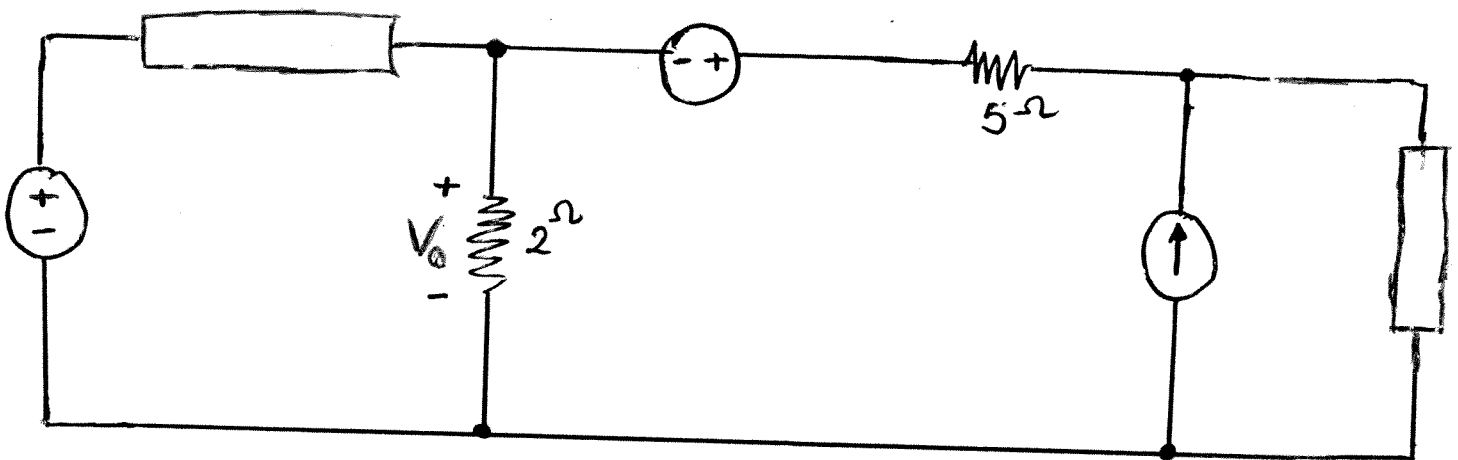

for Nodal or Super node:

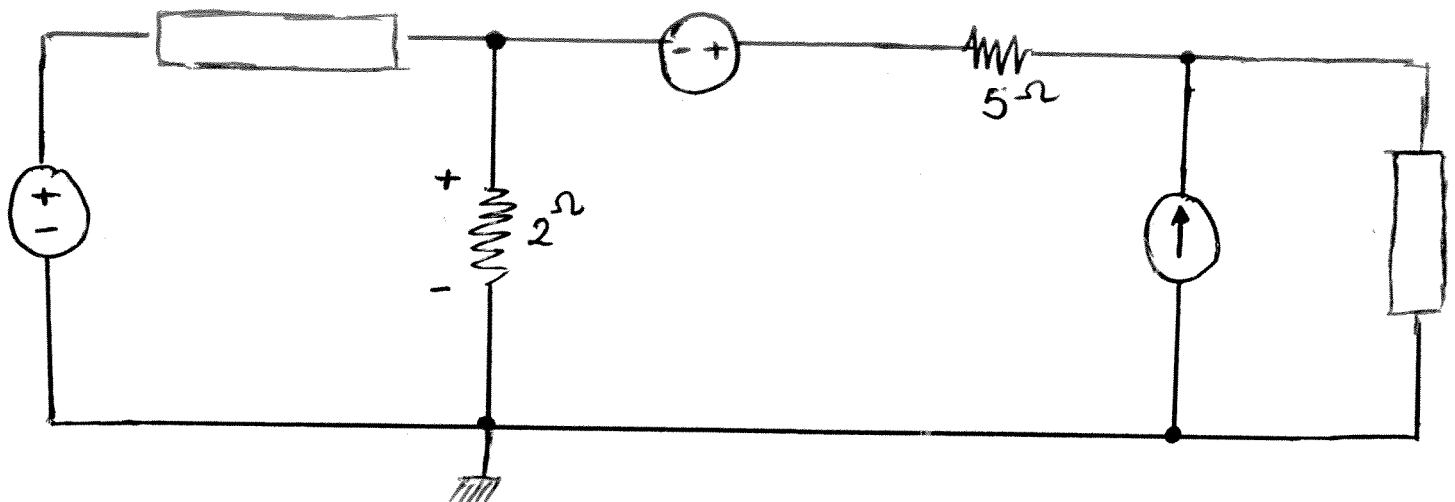

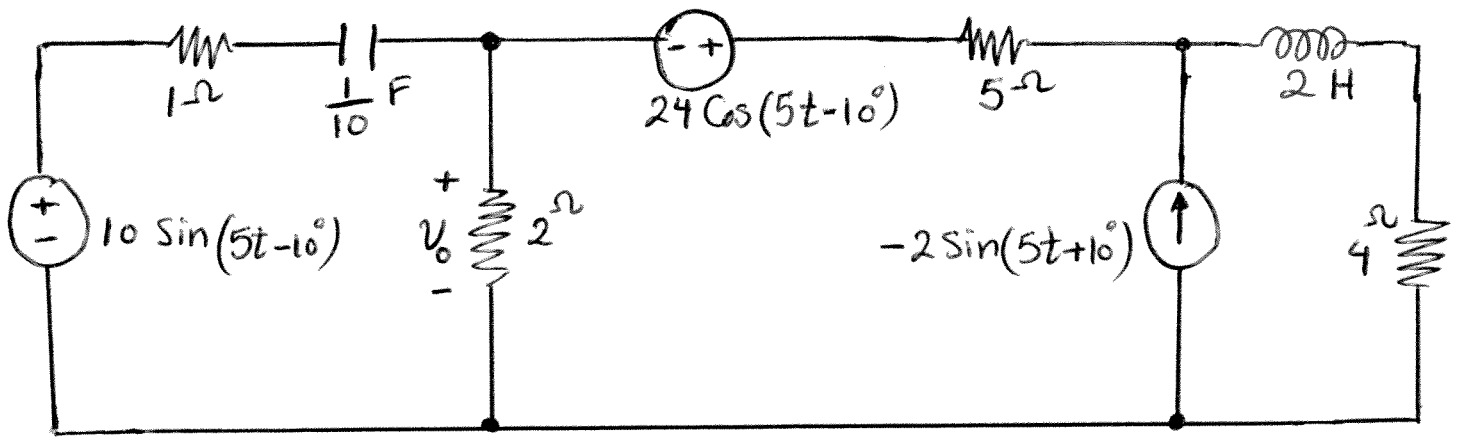


Fig. 1: (Mesh/Superposition/Nodal/Source Transformation)

Note: Find the answers to questions 1 to 4 in frequency domain (complex values).

Q1: (Super-Mesh): Find complex value of V_o in Fig. 1 using Mesh technique.

- Write the mesh equations for the loops. Assign the loops **clockwise**. (3 marks)
- Simplify the equations you wrote in part (A). (2 marks)
- Solve the simplified system in part (B). Provide numerical answers. (2 marks)
- Provide numerical complex value for V_o . (3 marks)

Q2: (Superposition): Find complex value of V_o in Fig. 1 using superposition technique.

- We have **3** independent sources. Draw the **3** circuit configurations required for superposition. (2 marks)
- Find V_{o1} due to the current source only. (2 marks)
- Find V_{o2} due to the voltage source at the left only. (2 marks)
- Find V_{o3} due to the voltage source on top only. (2 marks)
- What is the total V_o due to both independent sources? (2 marks)

Q3: (Super-Node): Find V_o in Fig. 1 using Nodal technique. **The reference node is at the bottom of the circuit.**

- Write the nodal equations for the non-reference nodes. (3 marks)
- Simplify the equations you wrote in part (A). (2 marks)
- Solve the simplified system in part (B). Provide numerical answers. (2 marks)
- Express V_o (in complex form) in terms of node voltages. (3 marks)

Q4: (Source Transformation): Find complex value of V_o in Fig. 1 using source transformation.

- Use source transformation at least once and create a simple circuit. (3 marks)
- Use Voltage and/or Current divider or Ohm's laws to get V_o . (2 marks)

Q5: (Complex domain to Time domain conversion)

- A. Find the value of v_o of Fig. 1 in time domain. The answers to Q1 to 4 are supposed to be the same. If you have not found similar answers, you may use any of the solutions you have found in Questions 1 to 4 to perform this task. (3 marks)

Q6: (Maximum Power Transfer):

- A. Find the Thevenin equivalent circuit (V_{th} and R_{th}) seen from the load perspective in Fig 2. (8 marks)
- B. Calculate the value of R_L for maximum power transfer. Determine the maximum power absorbed by R_L . (4 marks)

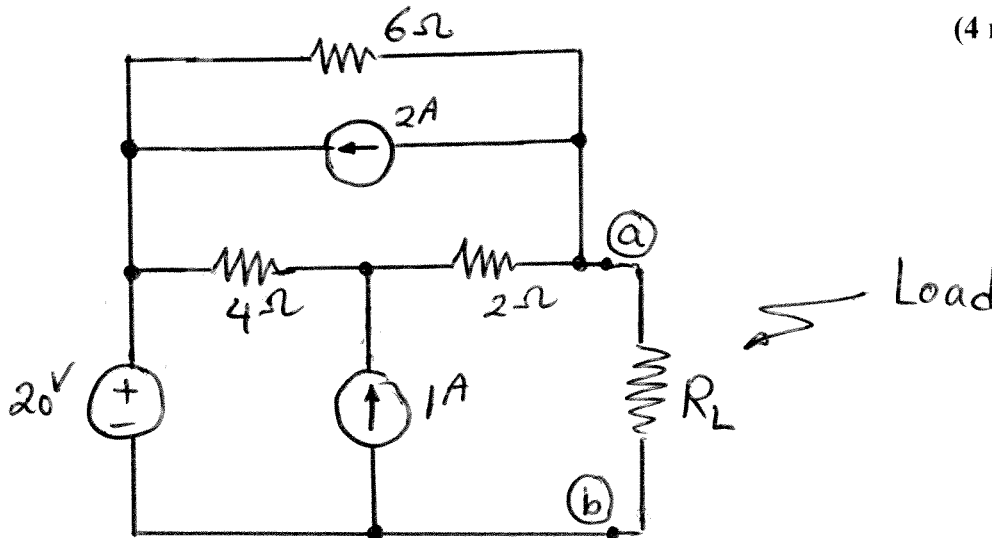


Fig. 2: (Maximum Power Transfer)

- Q7: (Wheatstone Bridge/Norton):** Find the Norton equivalent seen from terminals a-b in Fig. 3. (10 marks)

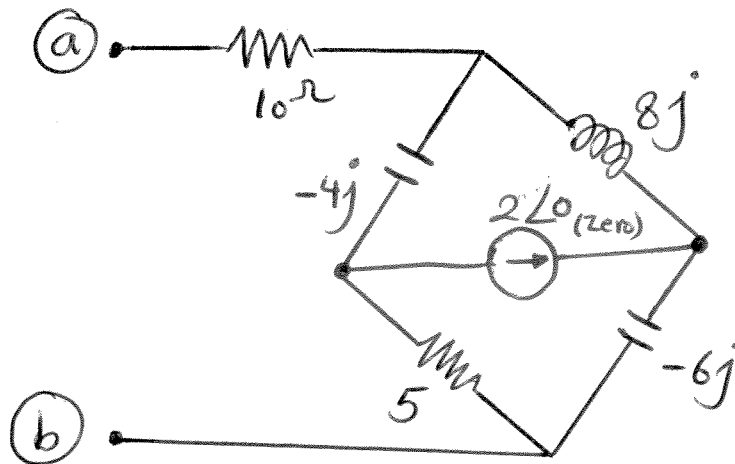


Fig. 3: (Wheatstone Bridge/Norton)

Q8: (RC): The switch in Fig. 4 has been in position (A) for a long time. At $t=0$, the switch moves from position (A) to (B). Find $v(t)$. (10 marks)

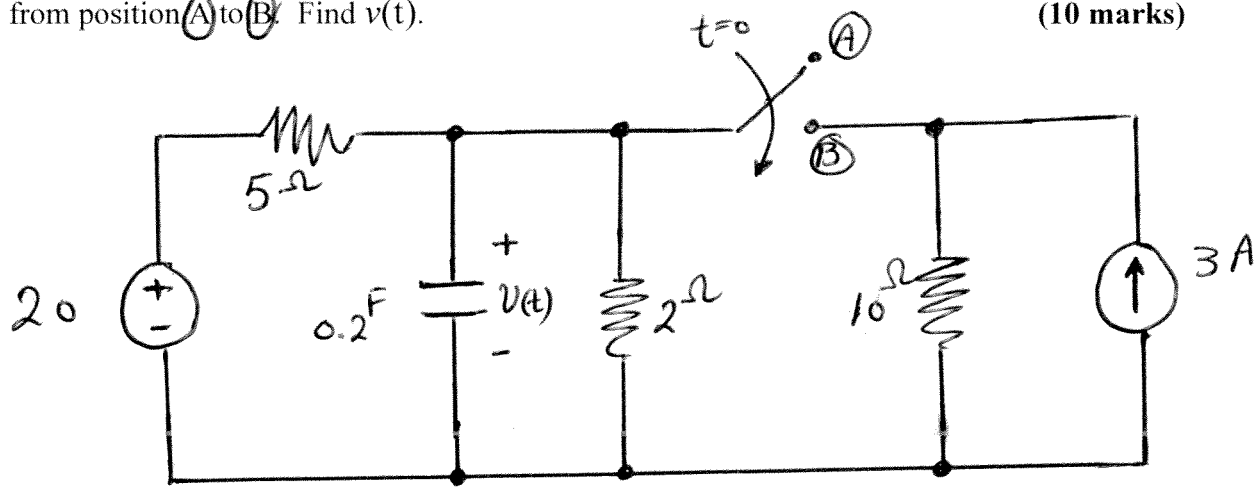


Fig. 4: (RC Circuit with DC excitation)

Q9: (RL): The switch in Fig. 5 has been in position (A) for a long time. At $t=0$, the switch moves from position (A) to (B). Find $i(t)$. (10 marks)


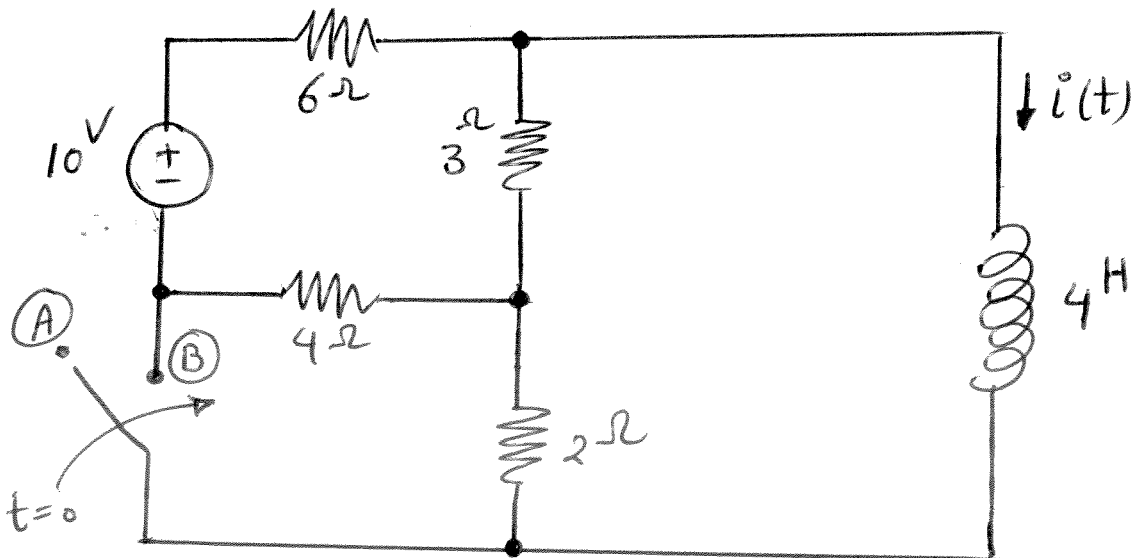


Fig. 5: (RL Circuit with DC excitation)



First Step: Time to Freq. Transformation

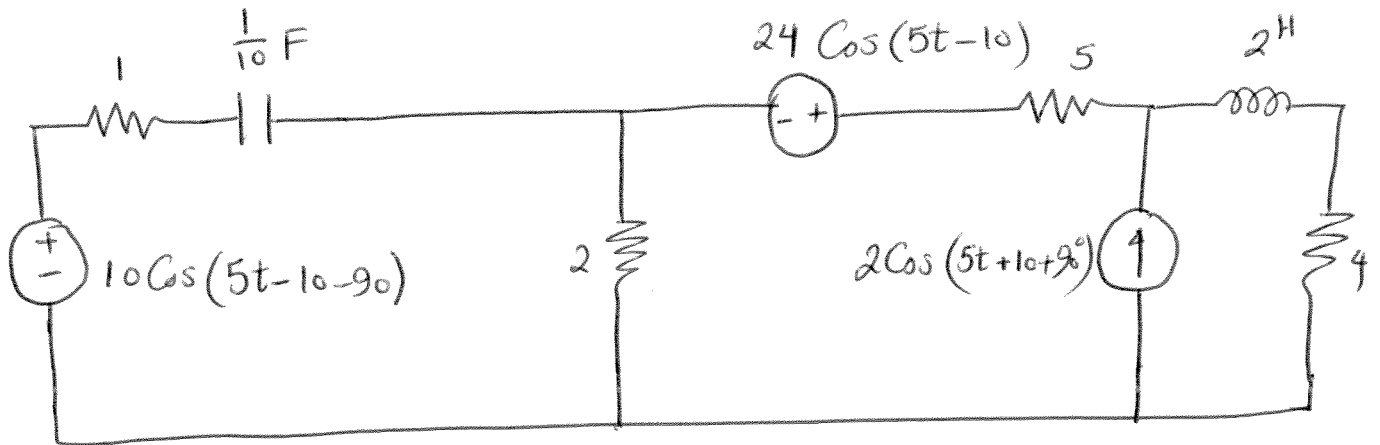


$\omega = 5$

$$\frac{1}{10} F \longrightarrow \frac{1}{C\omega j} = \frac{1}{5 \times \frac{1}{10} j} = \frac{1}{\frac{j}{2}} = \frac{2}{j} = -2j$$
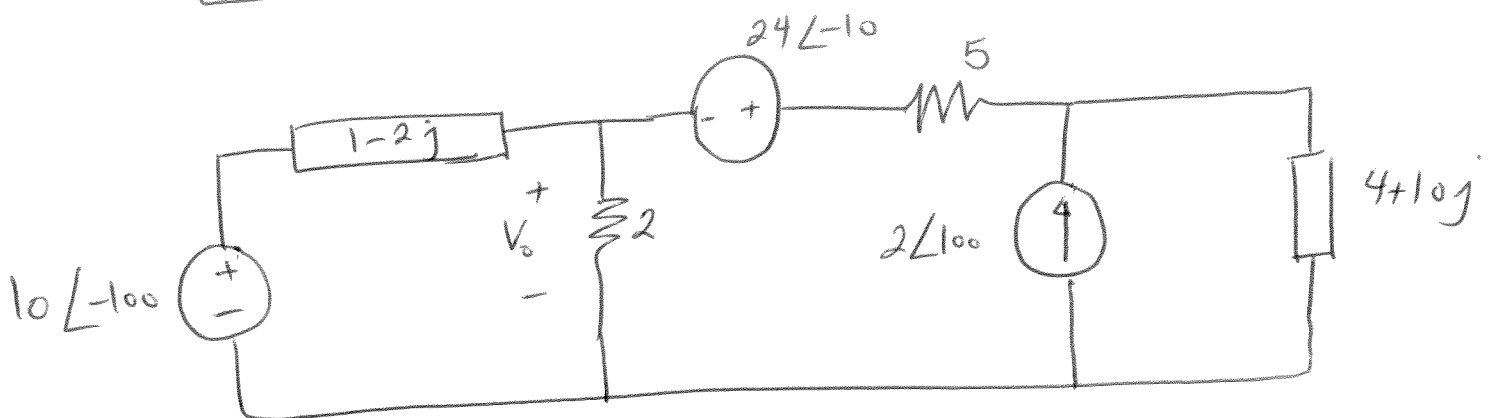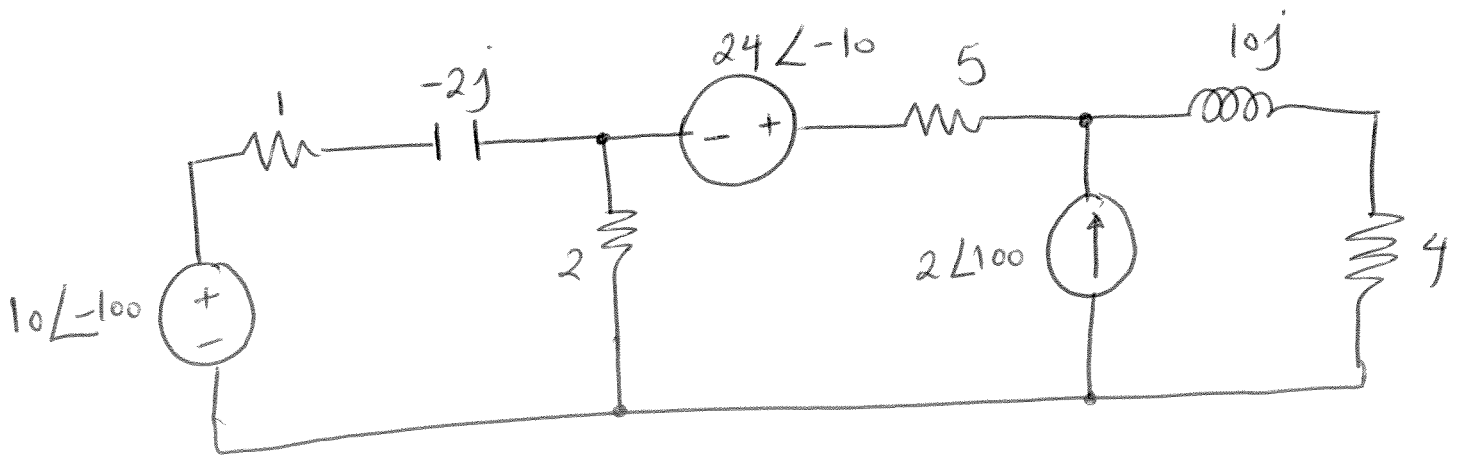
$$2 H \longrightarrow L\omega j = 2 \times 5j = 10j$$



① Super mesh: (one possible solution)

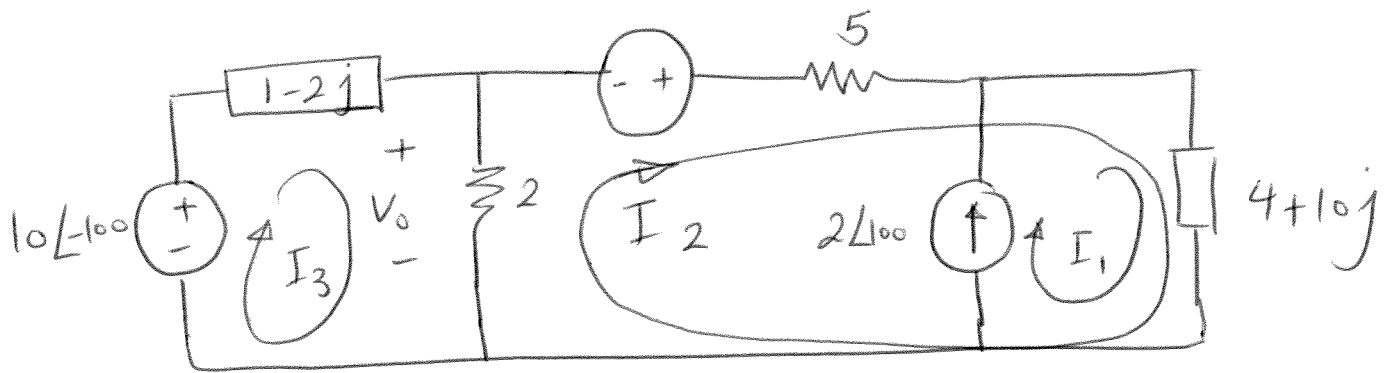

$$\begin{cases} I_1 = 2 \angle 100 \\ 2(I_2 - I_3) - 24 \angle -10 + 5I_2 + (4+10j)(2\angle 100 + I_2) = 0 \\ 2(I_3 - I_2) - 10 \angle -100 + (1-2j)(I_3) = 0 \end{cases}$$

$$\begin{cases} (2+5+4+10j) I_2 - 2 I_3 = (24 \angle -10) - (4+10j)(2\angle 100) \\ (-2) I_2 + (2+1-2j) I_3 = 10 \angle -100 \end{cases}$$

$$\begin{cases} (11+10j) I_2 - 2 I_3 = 44.721 - 8.5731j \\ -2 I_2 + (3-2j) I_3 = 10 \angle -100 \end{cases}$$

$$\Delta = \begin{vmatrix} 11+10j & -2 \\ -2 & 3-2j \end{vmatrix} = -(11+10j)(3-2j) - (-2)(-2) \\ = 49 + 8j$$

$$\Delta_{I_2} = \begin{vmatrix} 44.721 - 8.5731j & -2 \\ 10 \angle -100 & 3 - 2j \end{vmatrix}$$

$$= (44.721 - 8.5731j)(3 - 2j) - (-2)(10 \angle -100)$$

$$= 113.54 - 134.85j$$

$$\Delta_{I_3} = \begin{vmatrix} 11 + 10j & 44.721 - 8.5731j \\ -2 & 10 \angle -100 \end{vmatrix}$$

$$= (11 + 10j)(10 \angle -100) + 2(44.721 - 8.5731j)$$



$$= 168.82 - 142.84j$$

$$I_2 = \frac{\Delta_{I_2}}{\Delta} = \frac{113.54 - 134.85j}{(49 + 8j)} = 1.82 - 3.049j$$

$$I_3 = \frac{\Delta_{I_3}}{\Delta} = \frac{(168.82 - 142.84j)}{(49 + 8j)} = 2.892 - 3.38j$$

$$V_o = 2(I_3 - I_2) = 2(1.07266 - 0.338j) = 2.145 - 0.6758j$$


Superposition:

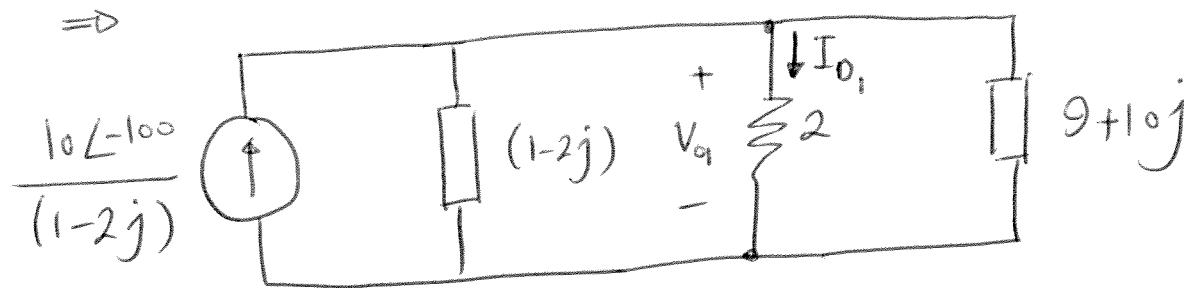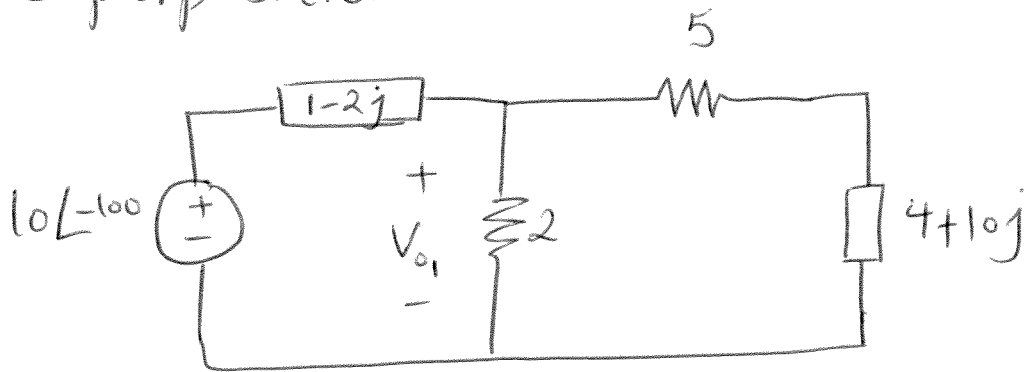


$$I_{o1} = \frac{\frac{1}{2}}{\left(\frac{1}{2} + \frac{1}{(1-2j)} + \frac{1}{(9+10j)}\right)} \times \frac{(10 \angle -100)}{(1-2j)}$$

$$= 1.303 - 2.376j$$

$$V_{o1} = 2 I_{o1} = 2.606 - 4.752j$$



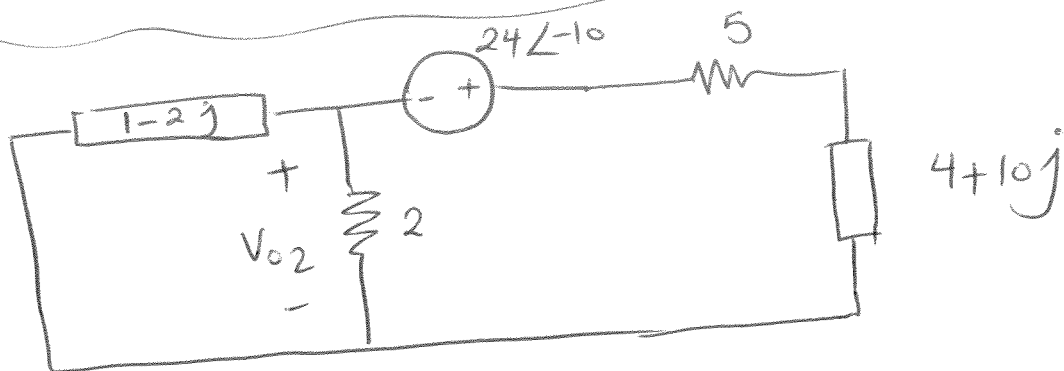


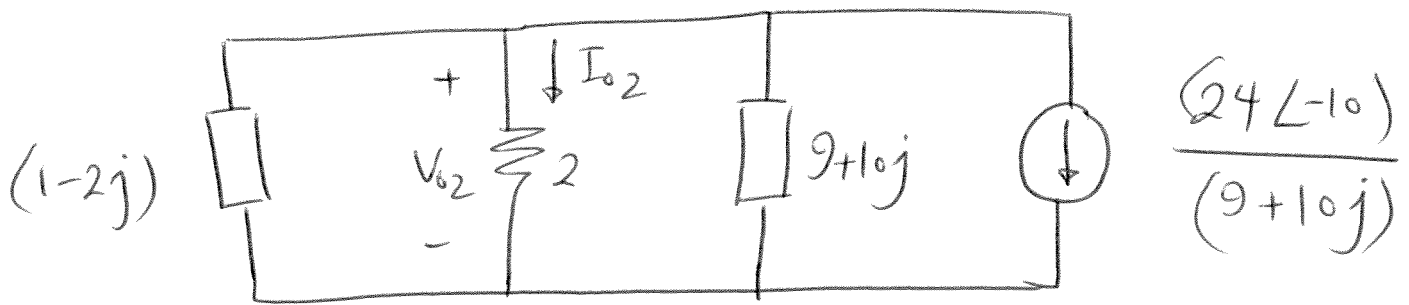

$$-I_{o2} = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{1-2j} + \frac{1}{9+10j}} \times \left(\frac{(24 \angle -10^\circ)}{(9+10j)} \right)$$

$$= 0.1372 - 1.072j$$
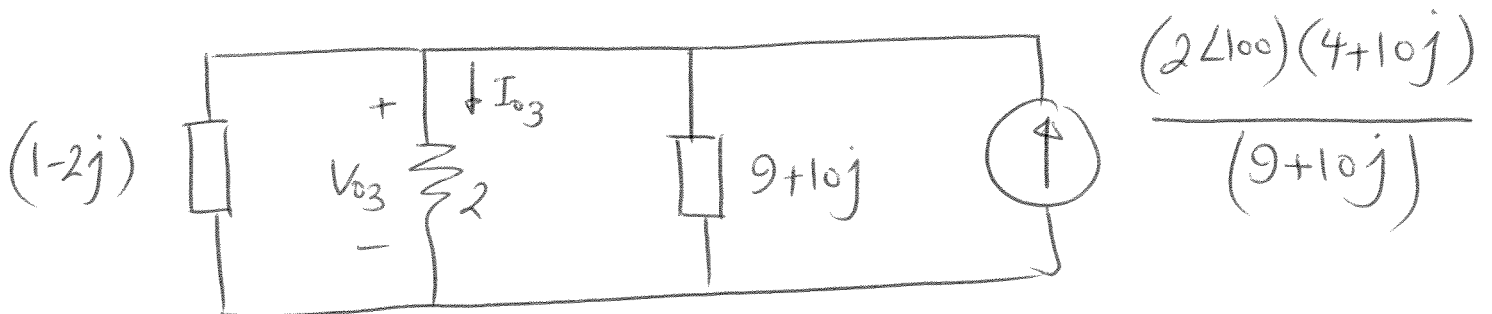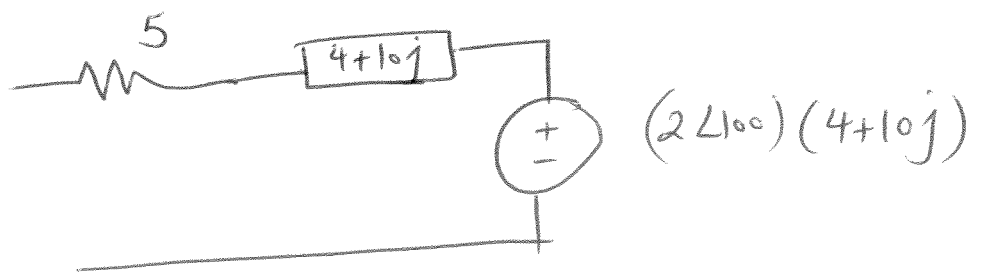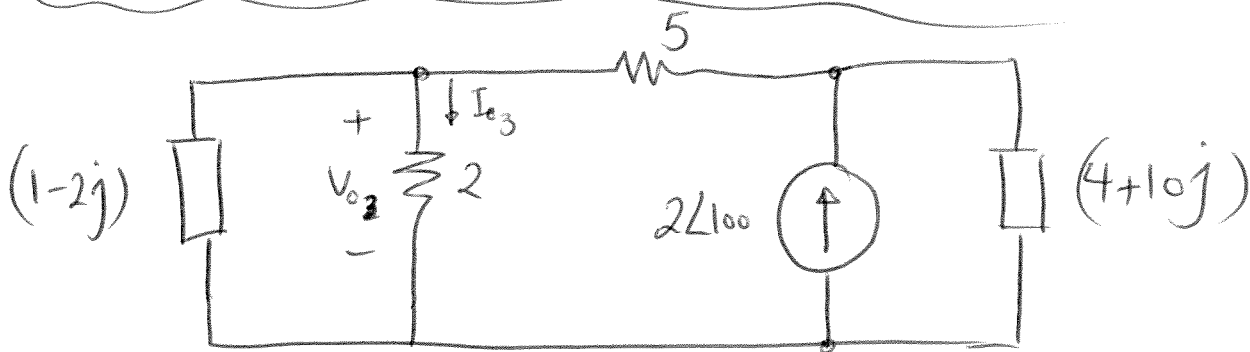
$$V_{o2} = 2 I_{o2} = 2 (-0.1372 + 1.072j) = -0.2744 + 2.144j$$




$$I_{o3} = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{(1-2j)} + \frac{1}{(9+10j)}} \times \frac{(24100)(4+10j)}{(9+10j)}$$
$$= -0.093 + 0.966j$$

$$V_{o3} = 2 I_{o3} = -0.1856 + 1.932j$$

$$V_{oT} = V_{o1} + V_{o2} + V_{o3} = (2.606 - 4.752j) +$$
$$(-0.27441 + 2.1443j) +$$
$$(-0.1856 + 1.932j)$$
$$= 2.146 - 0.6757j$$

Super node:

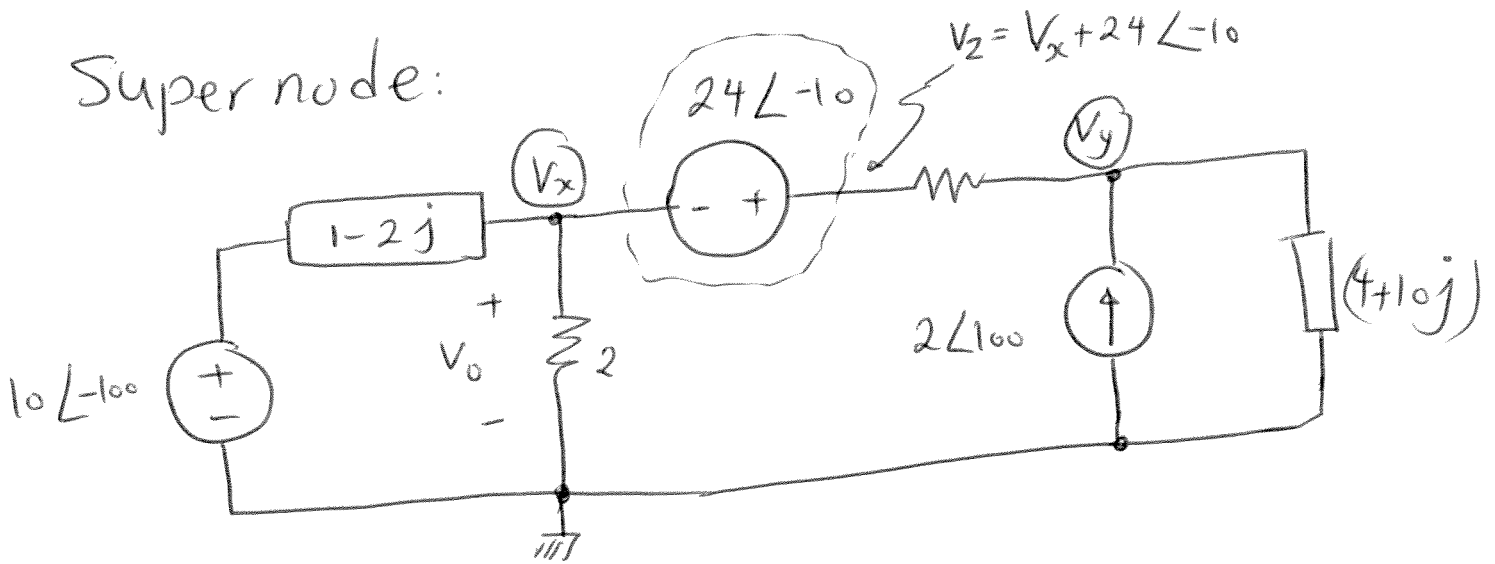

$$\left\{ \begin{aligned} \frac{V_x - (10 \angle -100)}{(1-2j)} + \frac{V_x - 0}{2} + \frac{(V_x + 24 \angle -10) - V_y}{5} &= 0 \\ \frac{V_y - (V_x + 24 \angle -10)}{5} + \frac{V_y - 0}{(4+10j)} - 2 \angle 100 &= 0 \end{aligned} \right.$$

$$\left\{ \begin{aligned} V_x \left(\frac{1}{1-2j} + \frac{1}{2} + \frac{1}{5} \right) + V_y \left(\frac{-1}{5} \right) &= \frac{10 \angle -100}{(1-2j)} - \frac{(24 \angle -10)}{5} \\ V_x \left(\frac{-1}{5} \right) + V_y \left(\frac{1}{5} + \frac{1}{4+10j} \right) &= \frac{24 \angle -10}{5} + 2 \angle 100 \end{aligned} \right.$$

$$\Delta = \begin{vmatrix} \frac{1}{1-2j} + \frac{1}{2} + \frac{1}{5} & \frac{-1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{4+10j} \end{vmatrix} = \left(\frac{1}{1-2j} + \frac{1}{2} + \frac{1}{5} \right) \left(\frac{1}{5} + \frac{1}{4+10j} \right) - \left(\frac{1}{25} \right)$$

See next page.
No space here.

$$= \left(\frac{1}{1-2j} + \frac{1}{2} + \frac{1}{5} \right) \left(\frac{1}{5} + \frac{1}{4+10j} \right) - \left(\frac{-1}{5} \right) \left(\frac{-1}{5} \right)$$

$$= 0.2055 + 0.01621j$$

$$\Delta V_x = \begin{vmatrix} \frac{10 \angle -100}{(1-2j)} - \frac{24 \angle -10}{5} & \frac{-1}{5} \\ \frac{24 \angle -10}{5} + 2 \angle 100 & \frac{1}{5} + \frac{1}{(4+10j)} \end{vmatrix}$$





$-1.135 - 1.83j$
 $-0.424 - 0.33j$

$4.3798 + 1.136j$


$$\Delta V_x = 0.452 - 0.1042j$$

$$V_x = \frac{\Delta V_x}{\Delta} = \frac{0.452 - 0.1042j}{0.2055 + 0.01621j} = 2.146 - 0.67j$$

Source Transformation

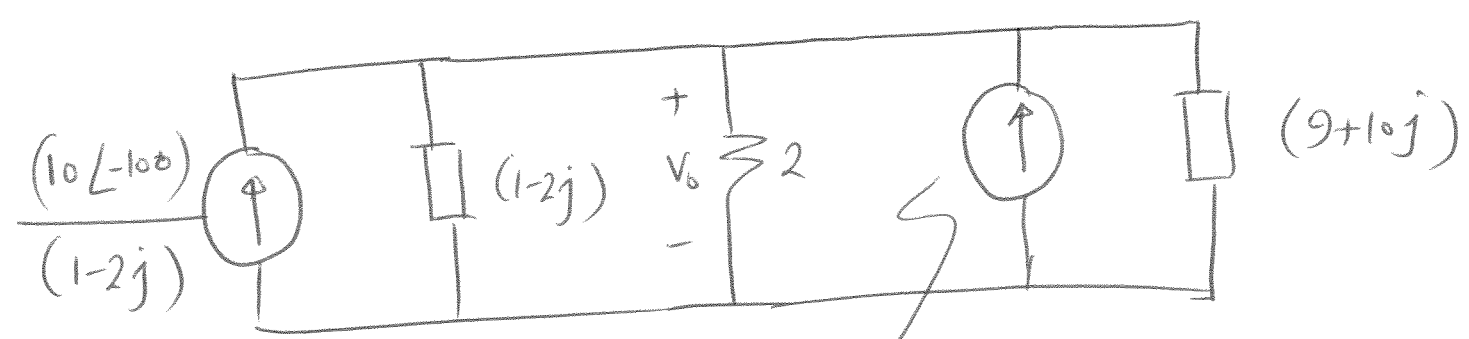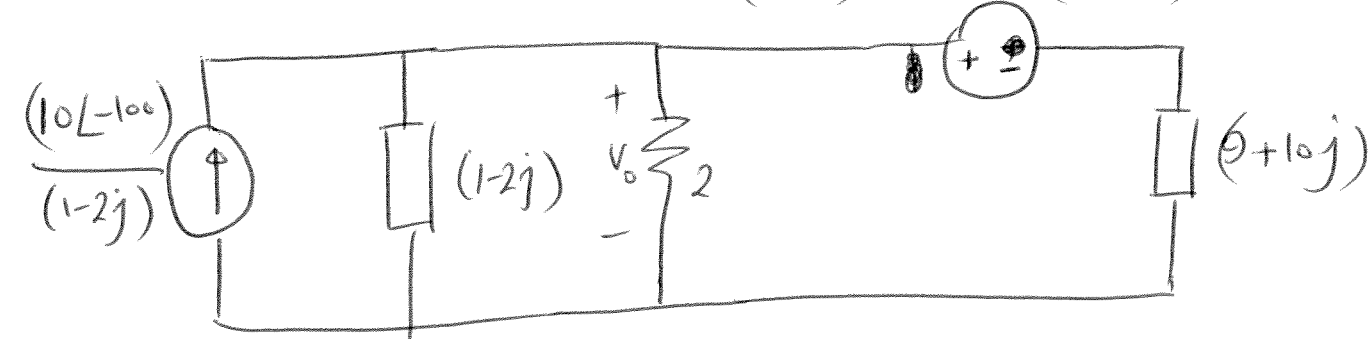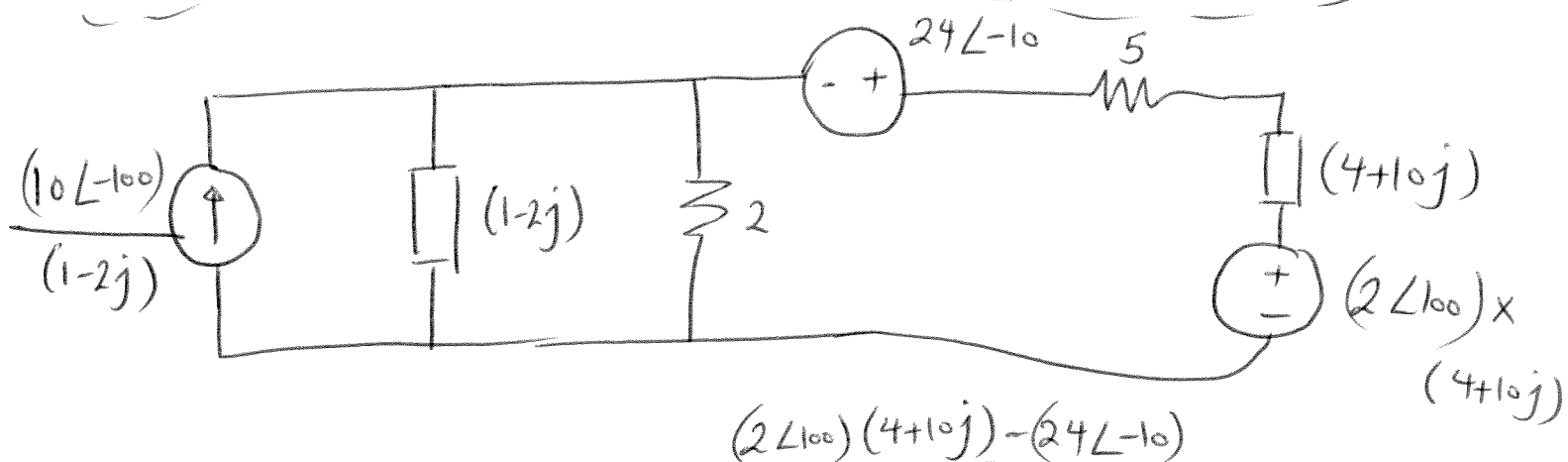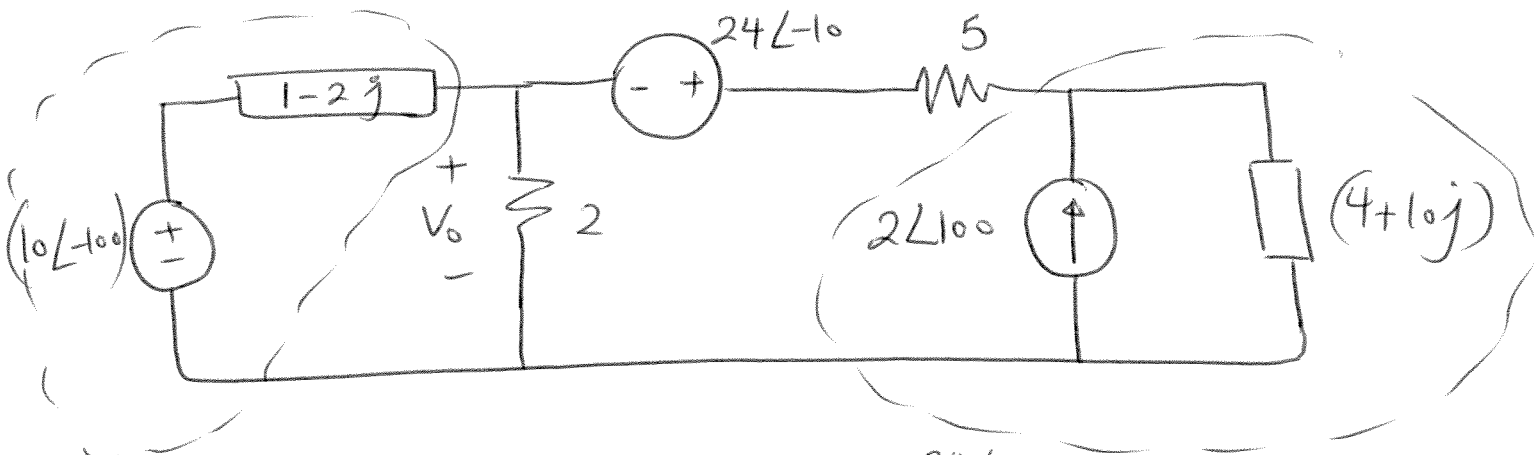
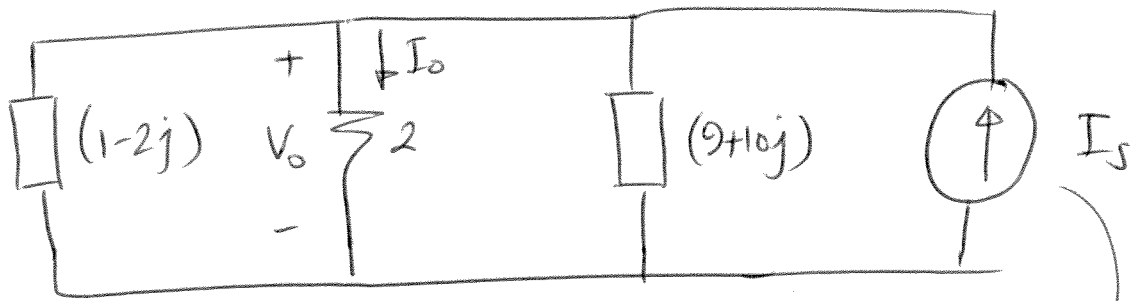
$$\frac{(2\angle 100)(4+10j) - (24\angle -10)}{(9+10j)}$$



$$I_s = \frac{(2 \angle 100^\circ)(4 + 10j) - (24 \angle -10^\circ)}{(9 + 10j)} + \frac{(10 \angle -100^\circ)}{(1 - 2j)} =$$

$$I_s = 1.842 + 0.233j$$

$$I_0 = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{(1-2j)} + \frac{1}{(9+10j)}} \times I_s$$


$$= 1.073 - 0.338j$$

$$V_0 = 2 I_0 = 2.1458 - 0.676j$$

Q5 Complex to Time domain:




$$2.146 - 0.67j = 2.25 \angle -17.34^\circ$$
$$= 2.25 \cos(5t - 17.34^\circ)$$

Q6:

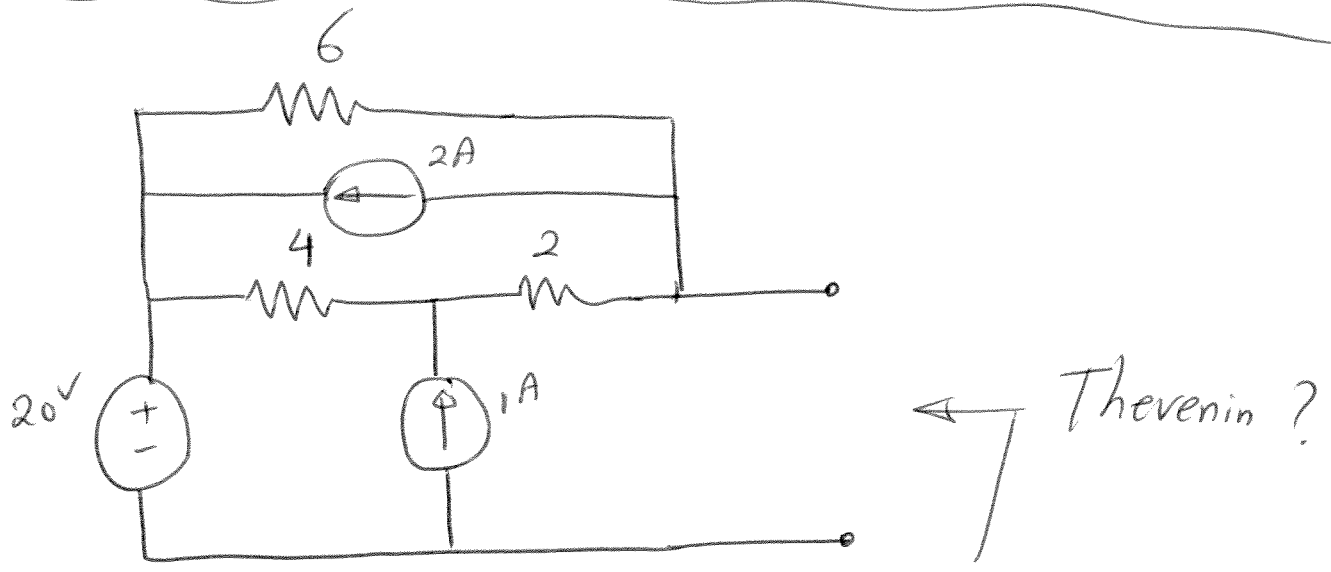

← Thevenin ?

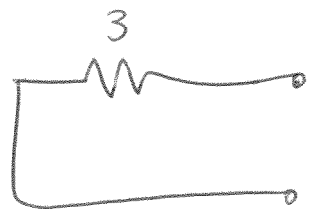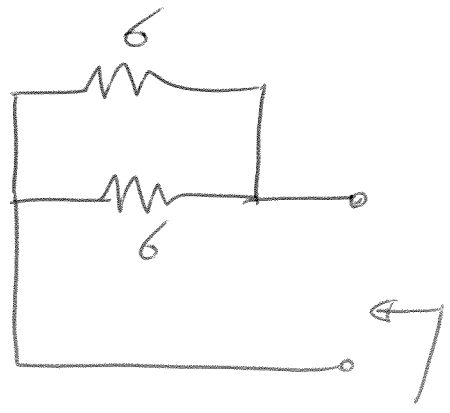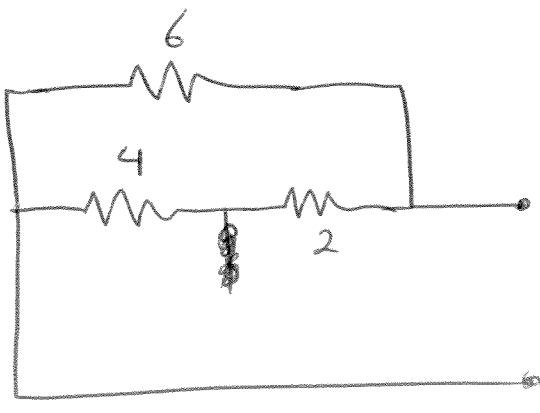
R_{th} : Set independent sources to zero.



$$\Rightarrow R_{th} = 3 \Omega$$

Find $V_{open} = V_{th}$:

Using Nodal:

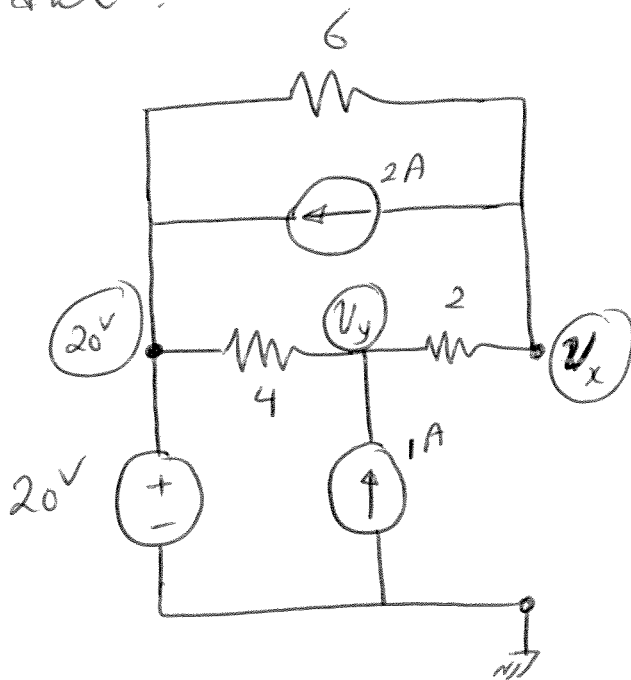

Node (x):


$$\frac{V_x - 20}{6} + 2 + \frac{V_x - V_y}{2} = 0$$

Node (y):

$$\frac{V_y - 20}{4} + \frac{V_y - V_x}{2} - 1 = 0$$

$$\begin{cases} V_x \left(\frac{1}{2} + \frac{1}{6} \right) + V_y \left(-\frac{1}{2} \right) = \frac{20}{6} - 2 \\ V_x \left(-\frac{1}{2} \right) + V_y \left(\frac{1}{2} + \frac{1}{4} \right) = \frac{20}{4} + 1 \end{cases}$$

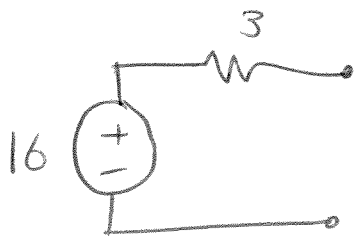Calculator
 $\Rightarrow V_x = 16, V_y = 18.667$
 $V_{th} = V_{open} = V_x$




$\Rightarrow R_{th} \xrightarrow[\text{Power Transfer}]{\text{for Max}} R_L$

$$\Rightarrow R_L = 3 \Omega$$

$$(P_L)_{max} = \frac{(V_{th})^2}{4 R_L} = \frac{(16)^2}{4 \times 3} = \frac{(16)^2}{12}$$

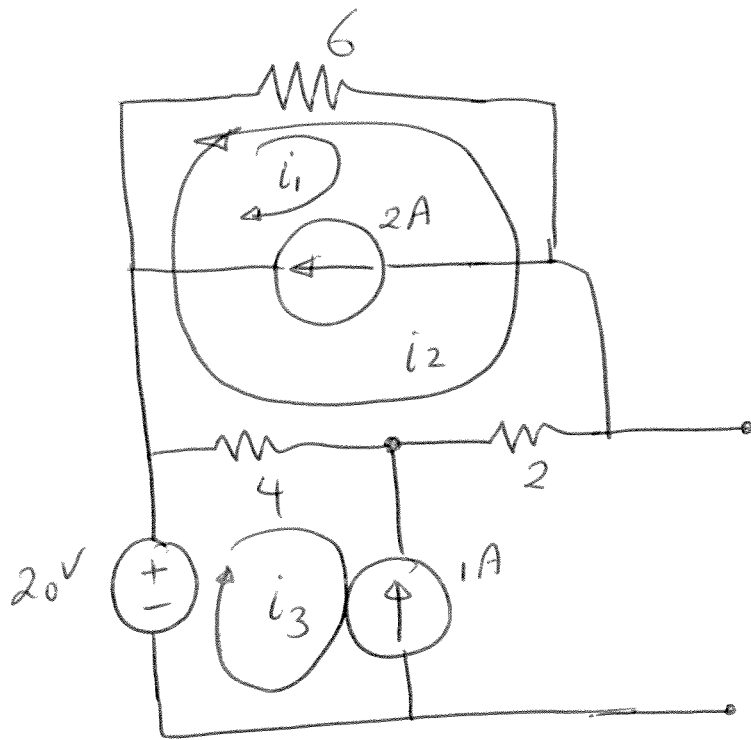We can also find V_{th} using mesh tech. as shown next.



$$i_1 = 2A$$

$$i_3 = -1A$$


$$6(i_1 + i_2) + 2i_2 +$$

$$4(i_2 - i_3) = 0$$

$$\Rightarrow 6(i_2 + 2) + 2i_2 +$$

$$4(i_2 - (-1)) = 0$$
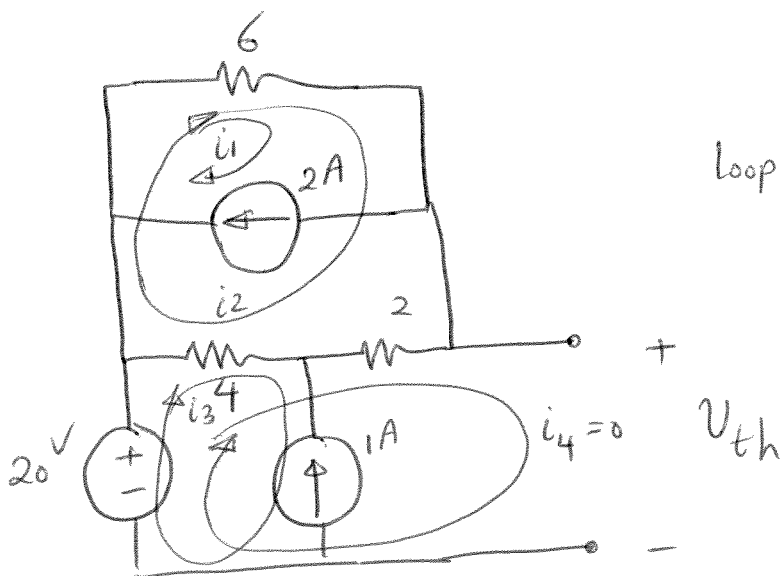
$$\Rightarrow i_2 = -\frac{16}{12} = -\frac{4}{3}$$





Loop (4):

$$+V_{th} - 20 + 4(0 + i_3 - i_2) + 2(0 - i_2) = 0$$

$$V_{th} - 20 + 4(-1 + \frac{4}{3}) + 2(\frac{4}{3}) =$$

$$V_{th} = 16 \checkmark$$

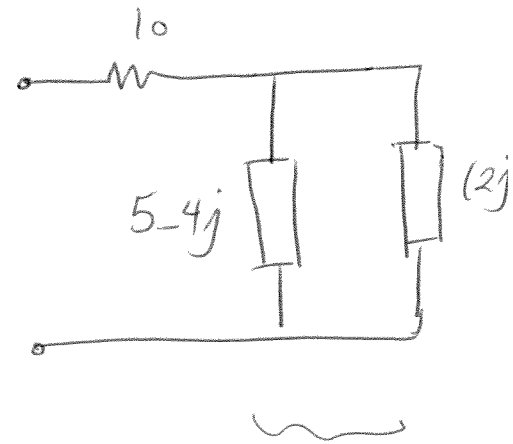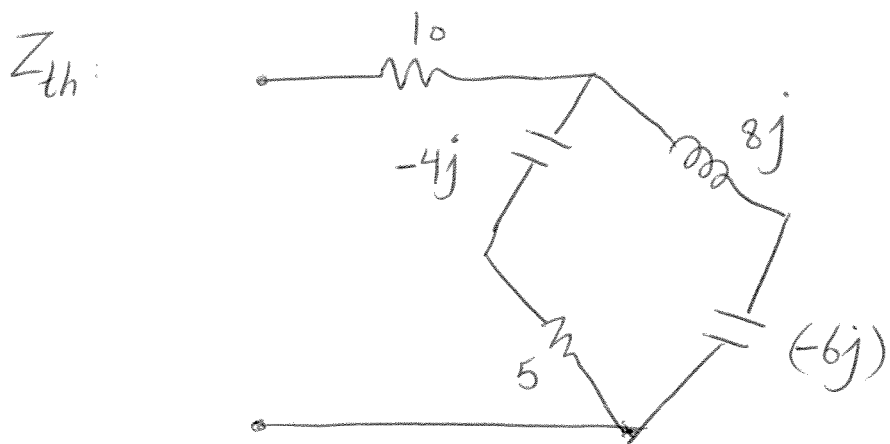Q7: Find Thevenin first, then transform it for Norton.



$$Z_{th} = 10 + \frac{(2j)(5-4j)}{(2j) + (5-4j)} = 10 + 2.2758j$$

← worked this way

For V_{th} , since the output is open, the current through 10Ω is zero.


Using Mesh: $I_1 = -2 \angle 0^\circ = -2$


$$(8j)(I_1 + I_2) + (-6j)(I_2) + 5(I_2) + (-4j)(I_1 + I_2) = 0$$

$$I_2(8j - 6j + 5 - 4j) + [(8j) + (-4j)](I_1) = 0$$


$$I_2(5 - 2j) = -(4j)(-2) = +8j \Rightarrow I_2 = -0.552 + 1.379j$$
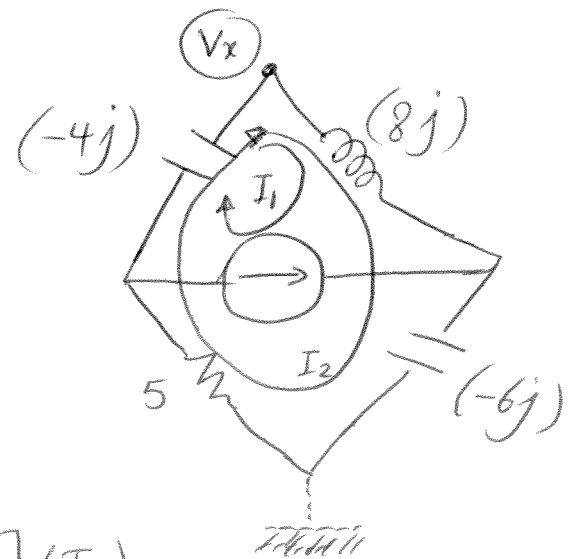
$$V_{th} = V_x = (-4j)(-I_1 - I_2) + 5(-I_2) = -8j + I_2(-5 + 4j) = -2.7586 - 17.10j$$



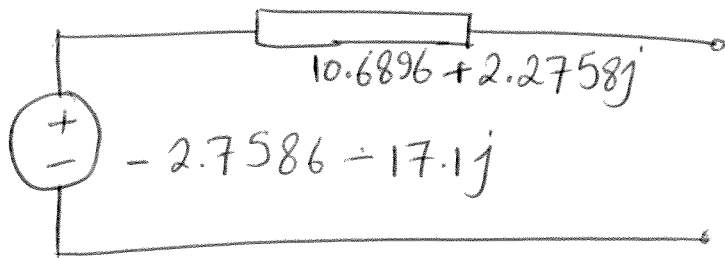

Thevenin

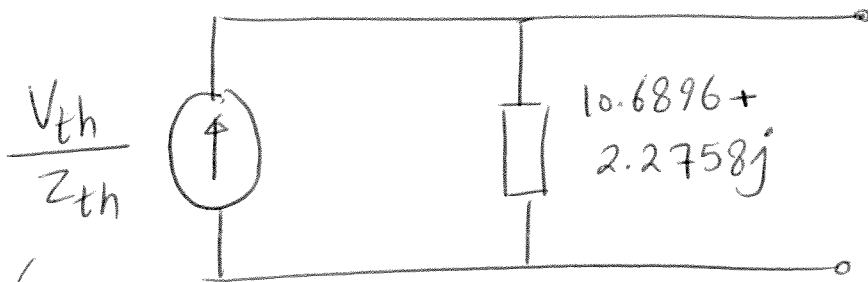


Norton

$\rightarrow -0.573 \angle -1.4781j$

If you have gone to find I_{short} , here it is.

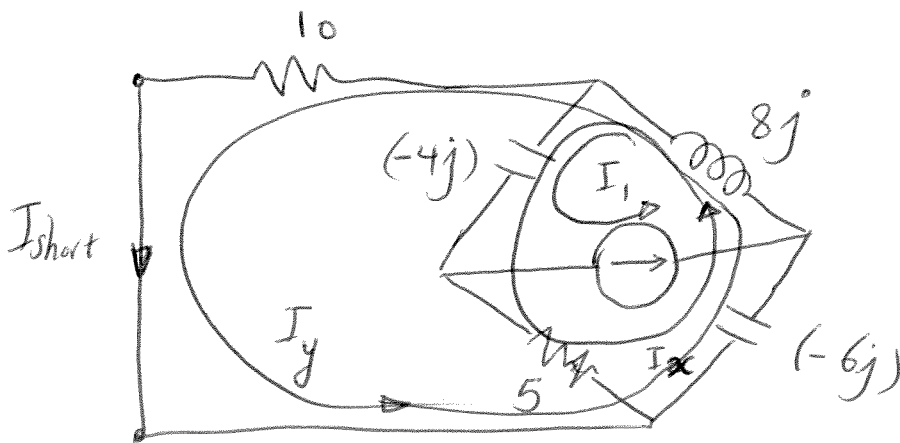I choose counter-clockwise to match I_{short} direction



$$I_1 = 2 \angle 0 = 2$$

$$\begin{cases} (-4j)(2 + I_x) + 5I_x + (-6j)(I_x + I_y) + (8j)(I_x + I_y + 2) = 0 \end{cases}$$

$$\begin{cases} 10I_y + (-6j)(I_x + I_y) + (8j)(I_x + I_y + 2) = 0 \end{cases}$$

$$\begin{cases} I_x(-4j - 6j + 8j + 5) + I_y(8j - 6j) = 8j - 16j \end{cases}$$

$$\begin{cases} I_x(-6j + 8j) + I_y(10 - 6j + 8j) = -16j \end{cases}$$

$$\begin{cases} I_x (5 - 2j) + I_y (2j) = -8j \\ I_x (2j) + I_y (10 + 2j) = -16j \end{cases}$$


$$\Delta = \begin{vmatrix} 5 - 2j & 2j \\ 2j & 10 + 2j \end{vmatrix} = (5 - 2j)(10 + 2j) + 4 \\ = 58 - 10j$$

$$\Delta_{I_y} = \begin{vmatrix} 5 - 2j & -8j \\ 2j & -16j \end{vmatrix} = -48 - 80j$$

$$I_y = I_{\text{short}} = \frac{\Delta_{I_y}}{\Delta} = \frac{-48 - 80j}{58 - 10j} = -0.573 - 1.478j$$


Q8:

$t < 0$

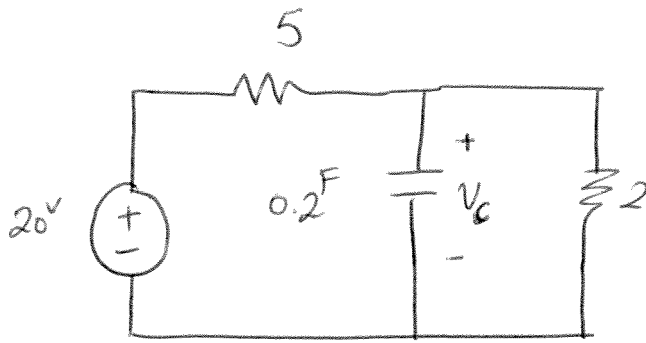

Long time:


Capacitor acts like open.

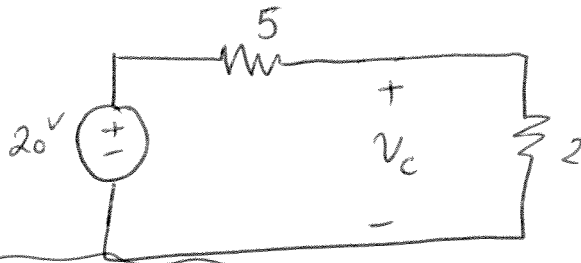


$$\Rightarrow V_c(t^-) = \frac{2}{2+5} \times 20V$$

$$= \frac{40}{7} = 5.71V$$


$t > 0$

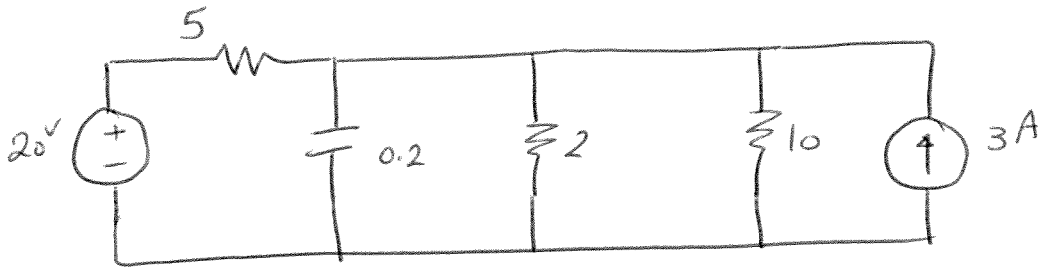

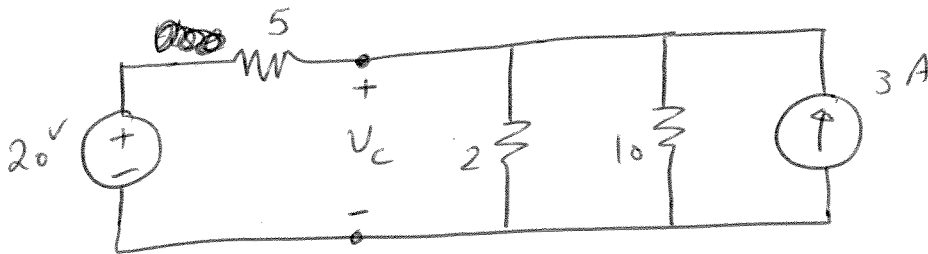
long time: Capacitor acts like an open line.



Source Transformation:

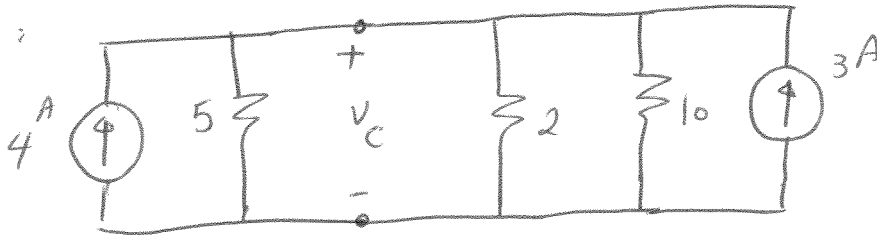

Combine sources:

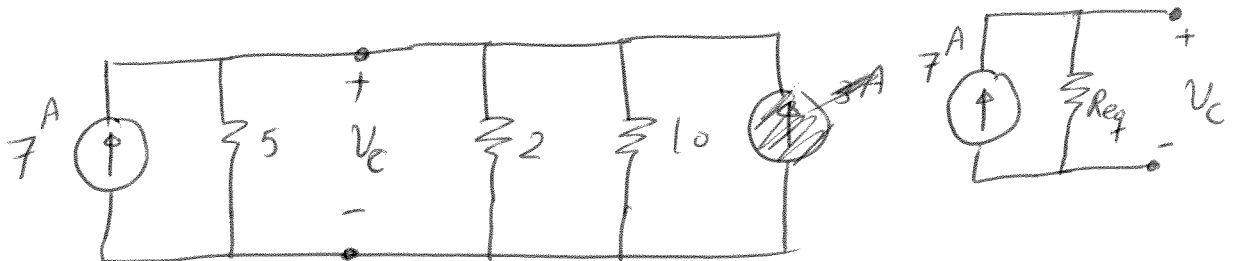


$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{5} + \frac{1}{10} \Rightarrow R_{eq} = 1.25$$

$$V_C(\infty) = 7^A \times (1.25) = 8.75^V$$



$$\tau_c = R_{eq} \cdot C = (1.25)(0.2) = 0.25^{sec}$$

$$V_C(t) = 8.75 + (5.71 - 8.75) e^{-\frac{t}{0.25}}$$



Q9 :

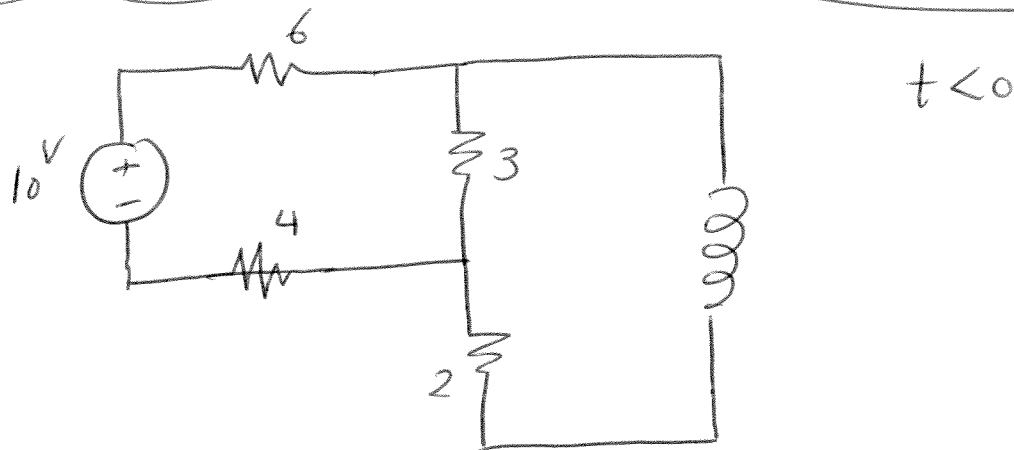

long time:
Inductor is short.

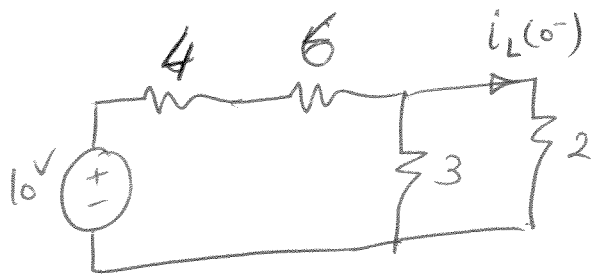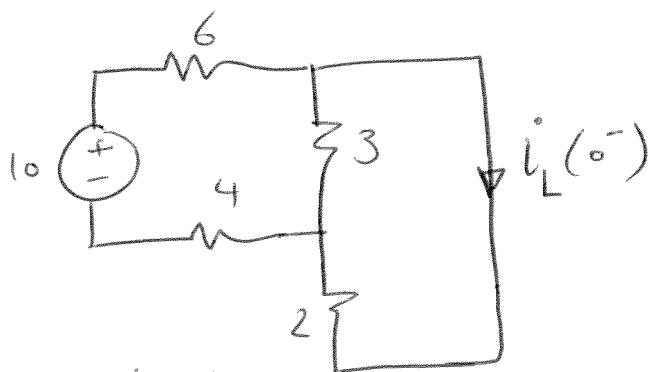


\Rightarrow

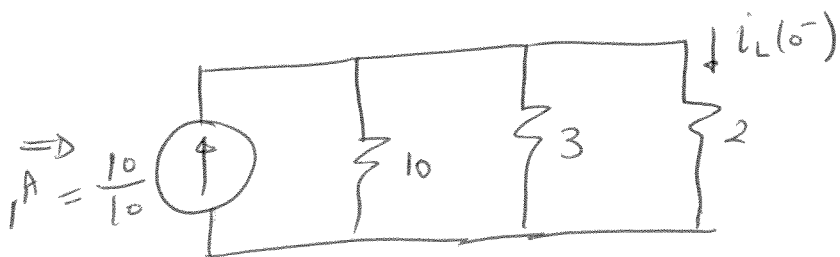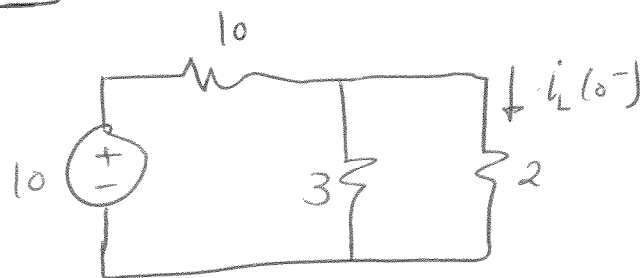





$$i_L(0^-) = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{3} + \frac{1}{10}} \times 1^A$$

$$= 0.5357 \text{ Amp}$$

$t > 0$

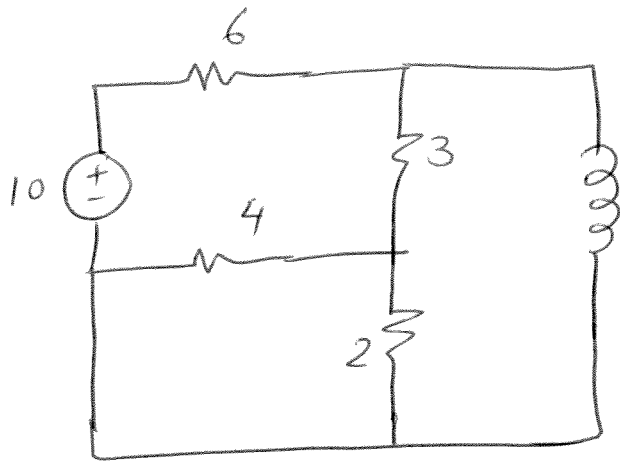

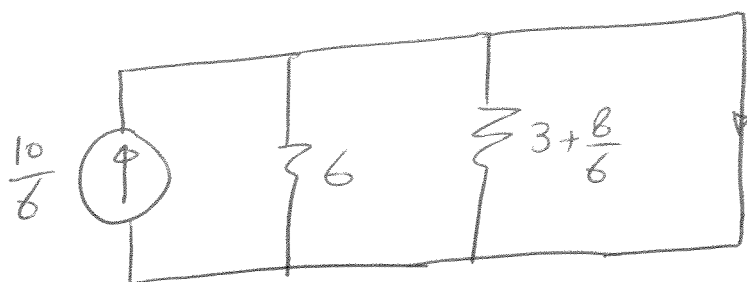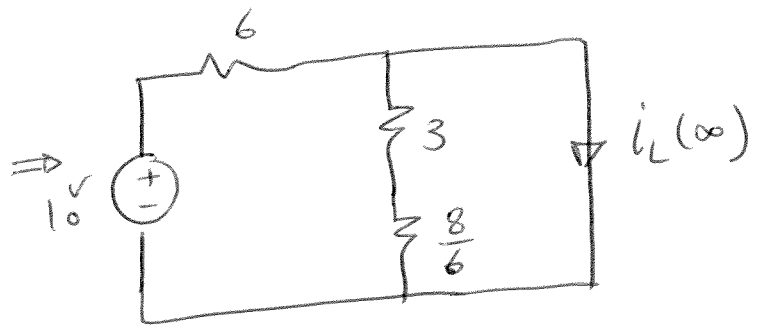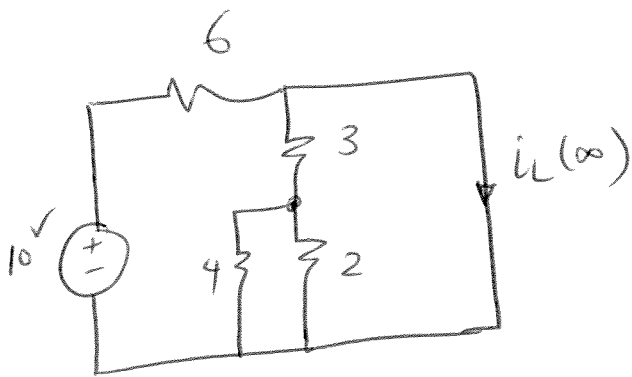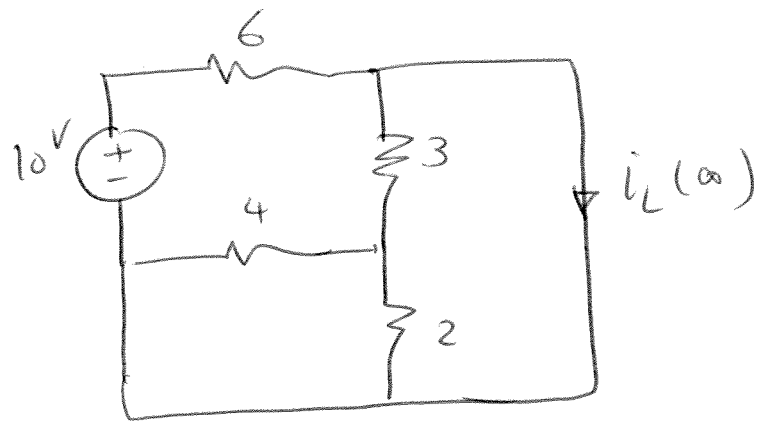Long time:
Inductor Acts like ~~an~~ a short line.



$$i_L(\infty) = \frac{10}{6} \text{ Amp}$$

$$R_{eq} = \frac{(3 + \frac{8}{6})(6)}{(3 + \frac{8}{6}) + (6)} = 2.516$$

$$\tau = \frac{L}{R} = \frac{4}{R_{eq}} = \frac{4}{2.516} = 1.5897$$

$$i_L(t) = \frac{10}{6} + \left[0.5357 - \frac{10}{6} \right] e^{-\frac{t}{1.5897}}$$