


**P1**

$$R_L = \frac{2}{0.025} = 80 \Omega$$

$$5 \times 10^{-3} = \frac{12 + R_L}{R_1 + (12 + R_L)} (30 \times 10^{-3})$$

so

$$R_1 = 460 \text{ ohms}$$

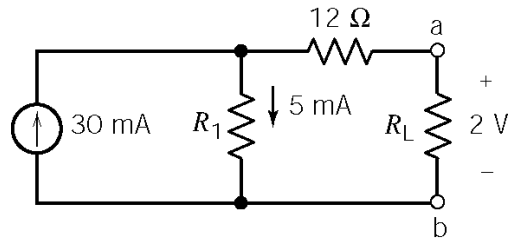


**P2**

Label the node voltages.

First,  $v_2 = 10 \text{ V}$  due to the independent voltage source. Next, express the controlling current of the dependent source in terms of the node voltages:
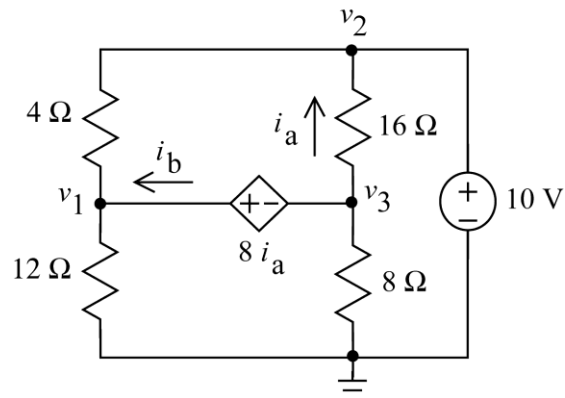
$$i_a = \frac{v_3 - v_2}{16} = \frac{v_3 - 10}{16}$$



Now the controlled voltage of the dependent source can be expressed as

$$v_1 - v_3 = 8 i_a = 8 \left( \frac{v_3 - 10}{16} \right) \Rightarrow v_1 = \frac{3}{2} v_3 - 5$$

Apply KCL to the supernode corresponding to the dependent source to get

$$\frac{v_1 - v_2}{4} + \frac{v_1}{12} + \frac{v_3 - v_2}{16} + \frac{v_3}{8} = 0$$

Multiplying by 48 and using  $v_2 = 10 \text{ V}$  gives

$$16v_1 + 9v_3 = 150$$

Substituting the earlier expression for  $v_1$

$$16 \left( \frac{3}{2} v_3 - 5 \right) + 9v_3 = 150 \Rightarrow v_3 = 6.970 \text{ V}$$

Then  $v_1 = 5.455 \text{ V}$  and  $i_a = -0.1894 \text{ A}$ . Applying KCL at node 2 gives

$$\frac{v_1}{12} = i_b + \frac{10 - v_1}{4} \Rightarrow 12 i_b = -3 + 4 v_1 = -30 + 4(5.455)$$

So

$$i_b = -0.6817 \text{ A.}$$

Finally, the power supplied by the dependent source is

$$p = (8 i_a) i_b = 8(-0.1894)(-0.6817) = 1.033 \text{ W}$$

**P3**

$$(a) \quad 50(i_3 - i_2) + R_3 i_3 + 32 = 0 \Rightarrow 50(0.0770 - 0.7787) + R_3(0.0770) + 32 = 0$$

$$\Rightarrow R_3 = 40 \Omega$$

$$i_1 R_1 + 20 i_2 + 50(i_2 - i_3) - 24 = 0 \Rightarrow R_1(-2.2213) + 20(0.7787) + 50(0.7787 - 0.0770) = 24$$

$$\Rightarrow R_1 = 12 \Omega$$

(b)


$$I_s = i_2 - i_1 = 0.7787 - (-2.2213) = 3 \text{ A}$$

The power supplied by the current source is

$$p = I_s (24 - R_1 i_1) = 3(24 - 12(-2.2213)) = 152 \text{ W}$$

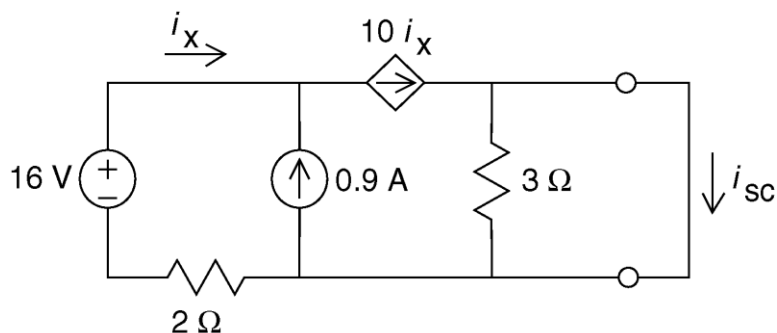**P4**

Find  $R_t$  by finding  $i_{sc}$  and  $v_{oc}$ :




The current in the  $3 \Omega$  resistor is zero because of the short circuit. Consequently,  $i_{sc} = 10 i_x$ . Apply KCL at the top-left node to get

$$i_x + 0.9 = 10i_x \Rightarrow i_x = \frac{0.9}{9} = 0.1 \text{ A}$$

so

$$i_{sc} = 10i_x = 1 \text{ A}$$

Next

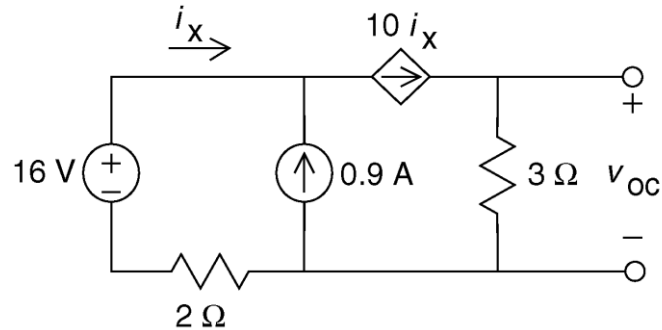

Apply KCL at the top-left node to get

$$i_x + 0.9 = 10i_x \Rightarrow i_x = \frac{0.9}{9} = 0.1 \text{ A}$$

Apply Ohm's law to the  $3 \Omega$  resistor to get

$$v_{oc} = 3(10i_x) = 30(0.1) = 3 \text{ V}$$

For maximum power transfer to  $R_L$ :

$$R_L = R_t = \frac{v_{oc}}{i_{sc}} = \frac{3}{1} = 3 \Omega$$

The maximum power delivered to  $R_L$  is given by

$$p_{\max} = \frac{v_{oc}^2}{4R_t} = \frac{3^2}{4(3)} = \frac{3}{4} \text{ W}$$