

Assignment #4

$$1. a) \frac{8 \times 10^{-6} \text{ C}}{\pi(10^{-3} \text{ m})(10^3 \text{ m})} = 2.546 \text{ C/m}^2$$

$$b) (\text{Electron density}) (3 \times 10^8) (1.6 \times 10^{-19}) = 8 \times 10^{-6}$$

$$\text{Electron density} = \frac{8 \times 10^{-6}}{(3 \times 10^8)(1.6 \times 10^{-19})}$$

$$= 166666.67 \text{ electron/m}^2$$

$$c) \frac{8 \times 10^{-6}}{1.6 \times 10^{-19}} = 5 \times 10^{-13} \text{ electron per second.}$$

$$\frac{6.023 \times 10^{23}}{5 \times 10^{-13}} = 1.2046 \times 10^{10} \text{ seconds}$$

$$2. R = \frac{\rho L}{A} \quad v = LA$$

$$R_1 = \frac{\rho \cancel{L}}{(A/\cancel{L})} = \frac{\rho \cancel{L}}{A} = \rho R$$

$$3. R = \rho_{cu} \frac{L}{A_{cu}} \quad R = \rho_{Al} \frac{L}{A_{Al}}$$

$$= \rho_{cu} \frac{L}{\pi(r_{cu})^2} \quad = \rho_{Al} \frac{L}{\pi(r_{Al})^2}$$


$$\frac{\pi r^2 R}{\pi r^2} = \frac{\rho L}{\pi r^2} \cdot \pi r^2$$

$$\sqrt{r^2} = \sqrt{\frac{\rho L}{\pi R}}$$

$$r = \sqrt{\frac{\rho L}{\pi R}}$$

$$\frac{r_{Al}}{r_{Cu}} = \frac{\sqrt{\frac{\rho_{Al} L}{\pi R}}}{\sqrt{\frac{\rho_{Cu} L}{\pi R}}} = \frac{\sqrt{2.62 \times 10^{-8} \Omega}}{\sqrt{1.7 \times 10^{-8} \Omega}}$$

$$r_{Al} : r_{Cu} = 1.3$$

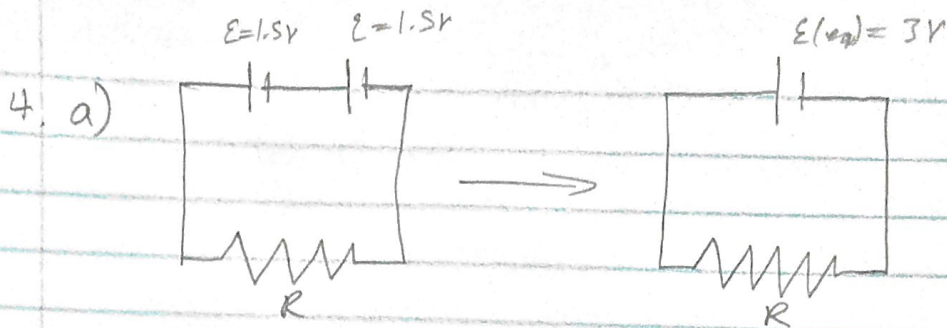

$$P = \frac{E_{eq}^2}{R} = 0.53 \text{ W}$$

$$b) E = Pt_{seconds} = (0.53)(5.1)(3600) = 9700 \text{ J}$$

$$c) P_R = \frac{P_0}{2}$$

$$I^2 R = \frac{1}{2} \frac{(E_{eq})^2}{R}$$

$$\Rightarrow \left(\frac{E_{eq}}{r+R} \right)^2 R = \frac{(E_{eq})^2}{2R}$$

$$\Rightarrow \frac{1}{(r+R)^2} = \frac{1}{2R^2}$$

$$\Rightarrow r = (\sqrt{2} - 1)R = 7.04 \Omega$$

$$5. a) I_1 = (I_2) (R_2) = (3.00)(4.00) = 12.00 \text{ V}$$

$$\frac{V}{R_1} = I_1 = \frac{12.00 \text{ V}}{3.00 \text{ V}} = 4.00 \text{ A}$$

$$R_3 = I_1 + I_2 = I_3 = 4.00 + 6.00 = 10 \text{ A}$$

$$b) \text{ Voltage drop across } R_3 = V_3 = I_3 (R_3) \\ = (10.00)(3.00) \\ = 30 \text{ V}$$

$$\text{Battery emf} = V_3 + V_2 = 30 \text{ V} + 12 \text{ V} \\ = 42 \text{ V}$$

6. $(3 \parallel 6) + (12 \parallel 4)$ is the equivalent resistance.

$$= 2 + 3 = 5$$

$$\text{So, total } I = \frac{60}{5} = 12 \text{ A}$$

$$7. a) ① I_R = I_4 + I_4 + I_{L1}$$

$$② I_{L1} = I_{L2} + I_3$$

$$③ I_{L3} = I_6 + I_R$$

Subbing 2 into 3 we get

$$I_{L1} = I_6 + I_R + I_3$$

We can further sub this result into 1 and obtain

$$\therefore I_R = I_4 + I_6 + I_R + I_3 = I_3 = -(I_4 + I_6) = -8.00 \text{ A}$$

Which means that the current is going the opposite direction relative to the assumed one.

b) To find the unknown emf we apply the loop rule and obtain.

$$E_2 = -I_3 R_3 + I_6 R_6 = (8.00 \times 3.00 + 5.00 \times 6.00) \text{ V} = 54.00$$

$$E_1 = -I_3 R_3 + I_4 R_4 = (8.00 \times 3.00 + 3.00 \times 4.00) \text{ V} = 36.00 \text{ V}$$

c) Applying the loop rule to the uppermost rule we get

$$I_R R = E_2 - E_1 \Rightarrow R = \frac{E_2 - E_1}{I_R} = \frac{54.00 - 36.00}{2.00} \Omega \\ = 9.00 \Omega$$

8. a) $C_{15} || C_{20} = 35 \mu\text{F} = 35 \times 10^{-6} \text{ F}$
 $R_{30} + R_{45} = 75 \Omega$

$$V = V_0 \times e^{(-t/RC)}$$

$$10 \text{ V} = 45 \text{ V} \times e^{(-t/(75)(35 \times 10^{-6}))}$$

$$\frac{10 \text{ V}}{45 \text{ V}} = e^{(-t/(75)(35 \times 10^{-6}))}$$

$$\ln(0.222222) = -t / ((75)(35 \times 10^{-6}))$$

$$(-1.5041) ((75)(35 \times 10^{-6})) = -t$$

$$t = 0.003948262 \text{ seconds}$$

$$= 3.448262 \text{ milliseconds}$$

b) $\frac{10 \text{ V}}{75 \Omega} = 0.133333 \text{ Ampere} = 133.333 \text{ milliAmpere}$