

Alternating Current Circuits

Chapter 33

AC Sources (of generators)

$$\Delta v = \Delta V_{\max} \sin \omega t$$

max output voltage, or voltage amplitude

ω = angular frequency

$$= 2\pi f = 2\pi / T$$

frequency
in Hz


Period in
s.

Symbol for AC source:



Resistor in AC circuit

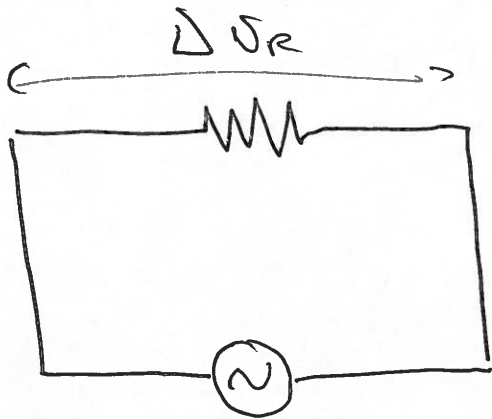(of small letters v, i, q, \dots
 \Rightarrow instantaneous values
varying with time t)




$$\Delta v = V_{\max} \sin(\omega t)$$


Kirchhoff's loop rule: $\Delta v - i_R R = 0$

$$\Rightarrow i_R = \frac{\Delta v}{R} = \frac{\Delta V_{\max}}{R} \sin \omega t = \underline{\underline{I_{\max} \sin(\omega t)}}$$

$$\Rightarrow I_{\max} = V_{\max} / R$$

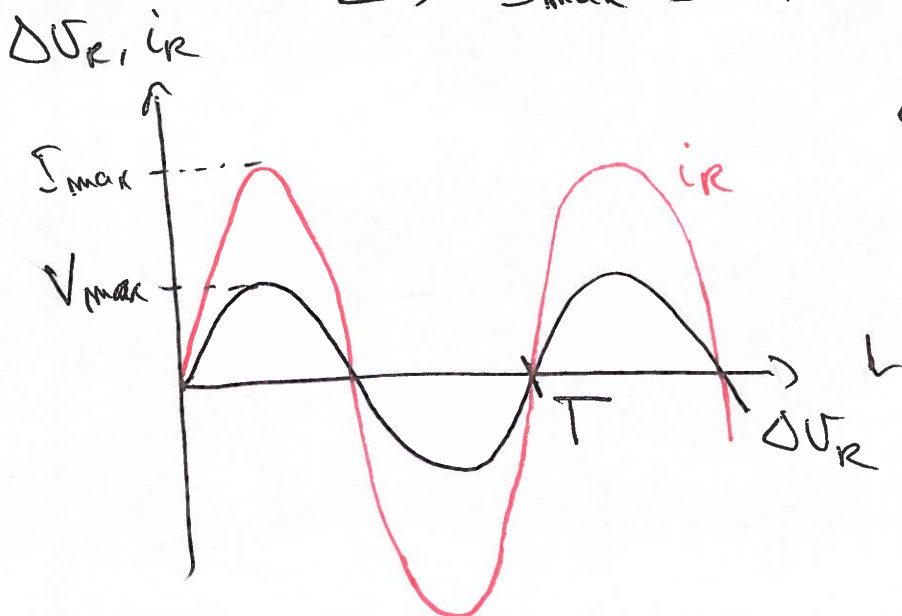

Phasor diagram

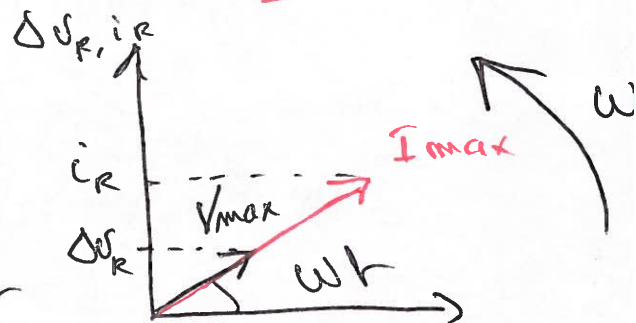

The energy transferred as internal energy in R is the same whatever is the direction of the current $\Rightarrow P = R i^2$

12

DC current of value $I_{\max} \Rightarrow P = R I_{\max}^2$

for AC current P is less because the current oscillates


"RMS current"

"Root-Mean-Square"

$$I_{\text{RMS}} = \sqrt{(i^2)_{\text{avg}}}$$

average of the square of the current

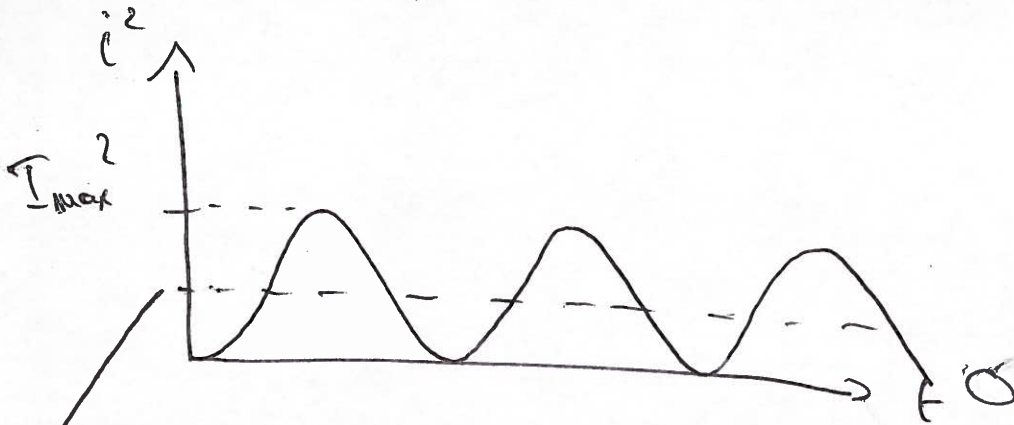Note: $\underline{\underline{i_{\text{avg}} = 0}}$



$$(i^2)_{\text{avg}} = \frac{1}{2} I_{\max}^2$$

$$\Rightarrow I_{\text{RMS}} = \frac{I_{\max}}{\sqrt{2}} = 0,707 I_{\max}$$

In AC \Rightarrow we usually provide rms value


$$\| P_{avg} = R I_{rms}^2$$

Similarly $\Delta V_{rms} = \frac{\Delta V_{max}}{\sqrt{2}} = 0,707 \Delta V_{max}$

Note an outlet providing 120V means $\Delta V_{rms} = 120V$
 \Rightarrow Therefore for home outlets $\Delta V_{max} = \underline{\underline{170V}}$

Note 2: in AC, voltmeters and ammeters are providing
rms values

Inductra in AC circuits

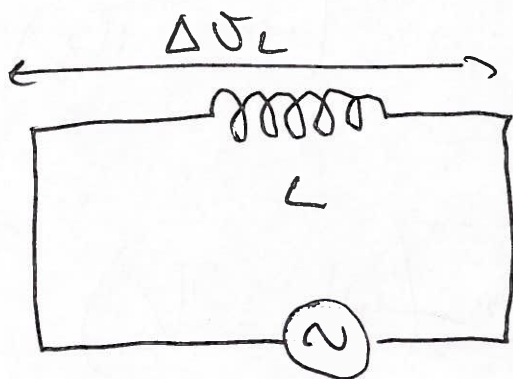

$$\Delta V = V_{max} \sin \omega t$$

$$\Delta V + \Delta V_L = 0$$

$$\Leftrightarrow \Delta V - L \frac{di_L}{dt} = 0$$

$$\Leftrightarrow \Delta V = L \frac{di_L}{dt} = \Delta V_{max} \sin \omega t$$

$$\Rightarrow di_L = \frac{\Delta V_{max}}{L} \sin \omega t dt$$

$$\downarrow \quad i_L = \frac{\Delta V_{max}}{L} \int \sin \omega t dt = -\frac{\Delta V_{max}}{\omega L} \cos \omega t$$

(note: we neglect the constant that depends on initial values only)


We have : $\cos \omega t = -\sin(\omega t - \pi/2)$
 $\Rightarrow -\cos \omega t = \sin(\omega t - \pi/2)$

$\Rightarrow i_L = \frac{\Delta V_{\max}}{\omega L} \sin(\omega t - \pi/2)$


\downarrow
 I_{\max}

i_L and ΔV_L are out of phase by

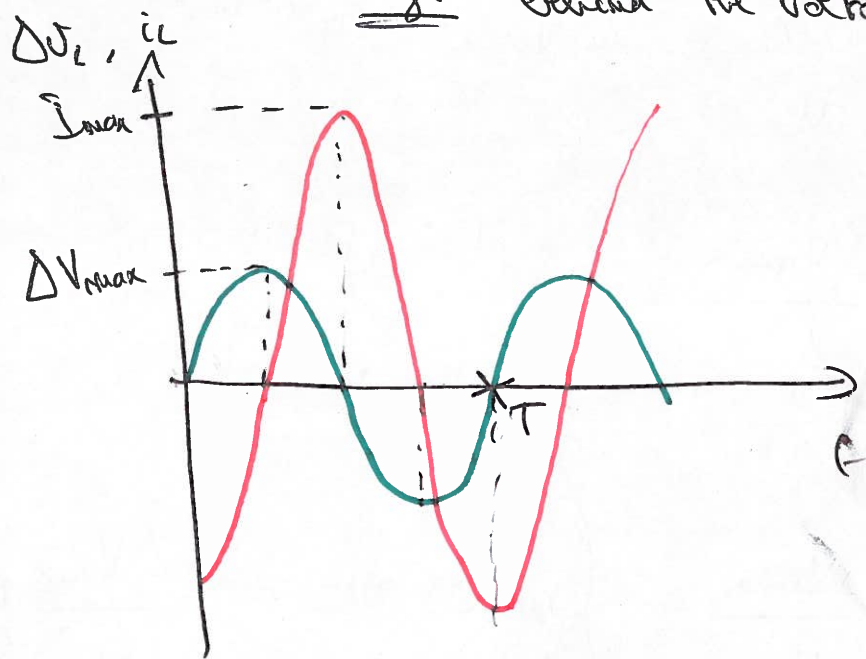The current lags $\pi/2$ rad = 90° behind the voltage



Phasor diagram

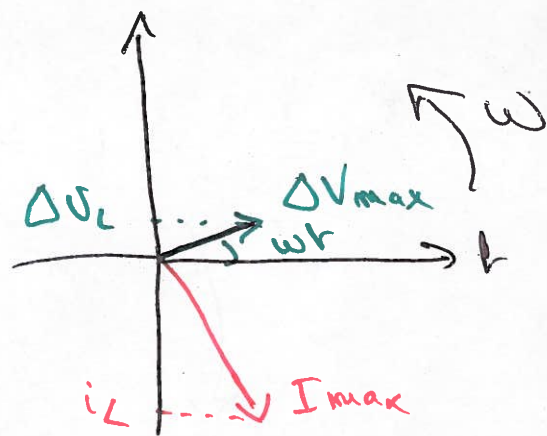

When i_L is max, no change $\Rightarrow \Delta V_L = 0$
 when i_L is 0, max rate change $\Rightarrow \Delta V_L = \max$

$$I_{max} = \frac{\Delta V_{max}}{\omega L}$$

f in DC $\Rightarrow I = \frac{\Delta V}{R}$

$\Rightarrow X_L \equiv \omega L$: Inductive reactance


$$I_{max} = \frac{\Delta V_{max}}{X_L}$$

$$I_{rms} = \frac{\Delta V_{rms}}{X_L}$$

When f (or ω) $\uparrow \Rightarrow X_L \uparrow \Rightarrow$ current \downarrow

(of Faraday law $\Rightarrow \uparrow$ rate of change $\Rightarrow \uparrow$ back emf)

Capacitors in AC circuits

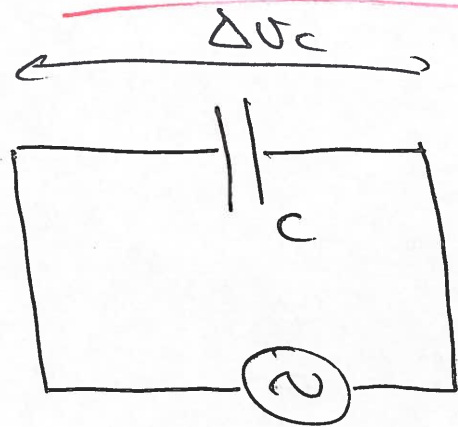

$$\Delta V = V_{\max} \sin \omega t$$

Kirchhoff's loop rule

$$\Delta V + \Delta V_c = 0$$

$$\Delta V - \frac{q}{C} = 0$$

$$\Rightarrow q = C \Delta V_{\max} \sin \omega t$$



$$i_c = \frac{dq}{dt} = \omega C \Delta V_{\max} \cos \omega t$$

We have $\cos \omega t = \sin \left(\omega t + \frac{\pi}{2} \right)$

$$i_c = \omega C \Delta V_{max} \sin(\omega t + \pi/2)$$

i_c and ΔV_c are out of phase

i_c precedes ΔV_c

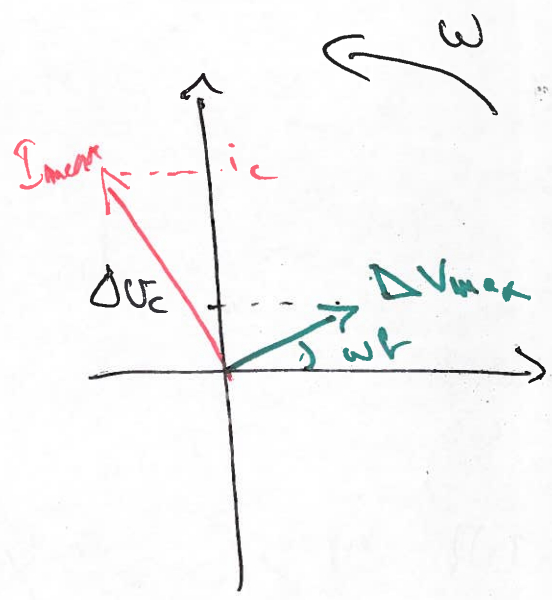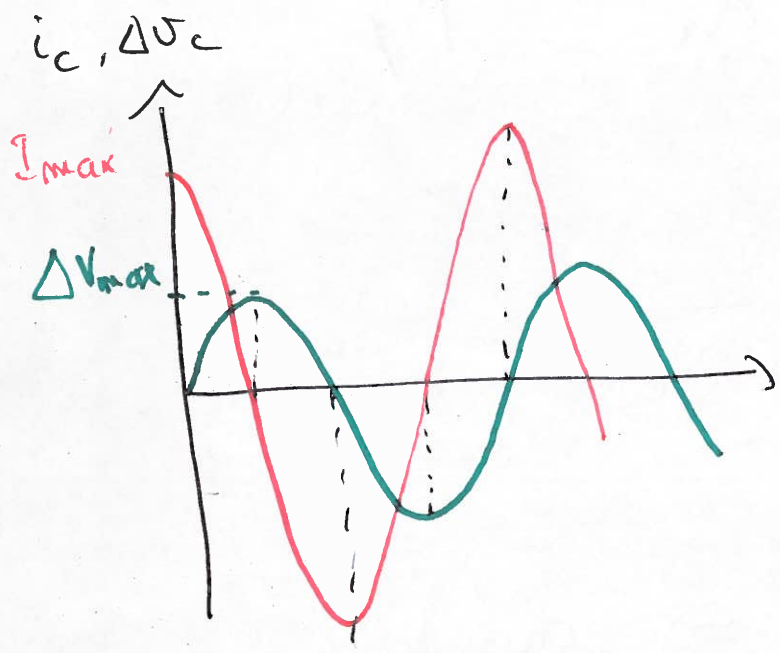

at $\Delta V = \Delta V_{max} \Rightarrow C$ fully charged $\Rightarrow \underline{i_c = 0}$

when $i_c = max \Rightarrow \Delta V_c$ is fully discharge and starts changing polarity

$$I_{\max} = \omega C \Delta V_{\max} = \frac{\Delta V_{\max}}{(1/\omega C)}$$
$$I = \frac{\Delta V}{R}$$

Capacitive Reactance

$$X_c = 1/\omega C$$

$$\Rightarrow I_{\max} = \frac{\Delta V_{\max}}{X_c}$$

When $f \uparrow \Rightarrow X_c \downarrow \Rightarrow$ current \uparrow


When $f \downarrow \Rightarrow X_c \uparrow \Rightarrow$ when f close to 0

open circuit

(of steady state)

The RLC series circuit

15

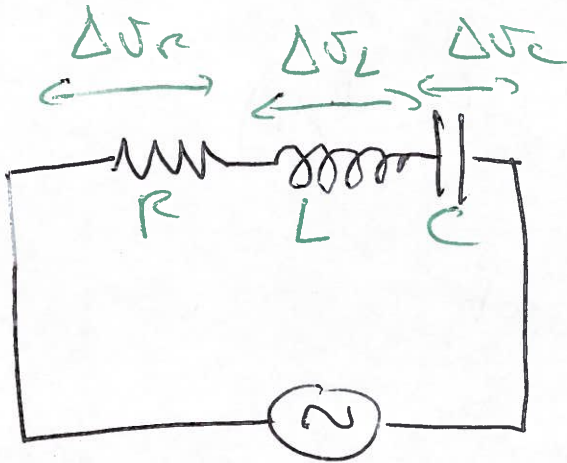

$$\Delta V = \Delta V_{\max} \sin \omega t$$

$$\Rightarrow i = I_{\max} \sin(\omega t - \phi)$$

\Downarrow
phase angle

3 elements in serie \Rightarrow the current should be the same everywhere

* ΔV_R is in phase with the current

$$\begin{aligned} \Rightarrow \Delta V_R &= R I_{\max} \sin(\omega t) \\ &= \Delta V_R \sin(\omega t) \end{aligned}$$


* ΔV_L leads the current by 90° ($\pi/2$)

$$\begin{aligned} \Rightarrow \Delta V_L &= I_{\max} X_L \sin(\omega t + \pi/2) \\ &= \Delta V_L \cos(\omega t) \end{aligned}$$


* ΔV_c lags behind the current by $90^\circ (\pi/2)$

$$\Delta V_c = I_{max} X_c \sin(\omega t - \pi/2)$$


$$= -\Delta V_c \cos \omega t$$

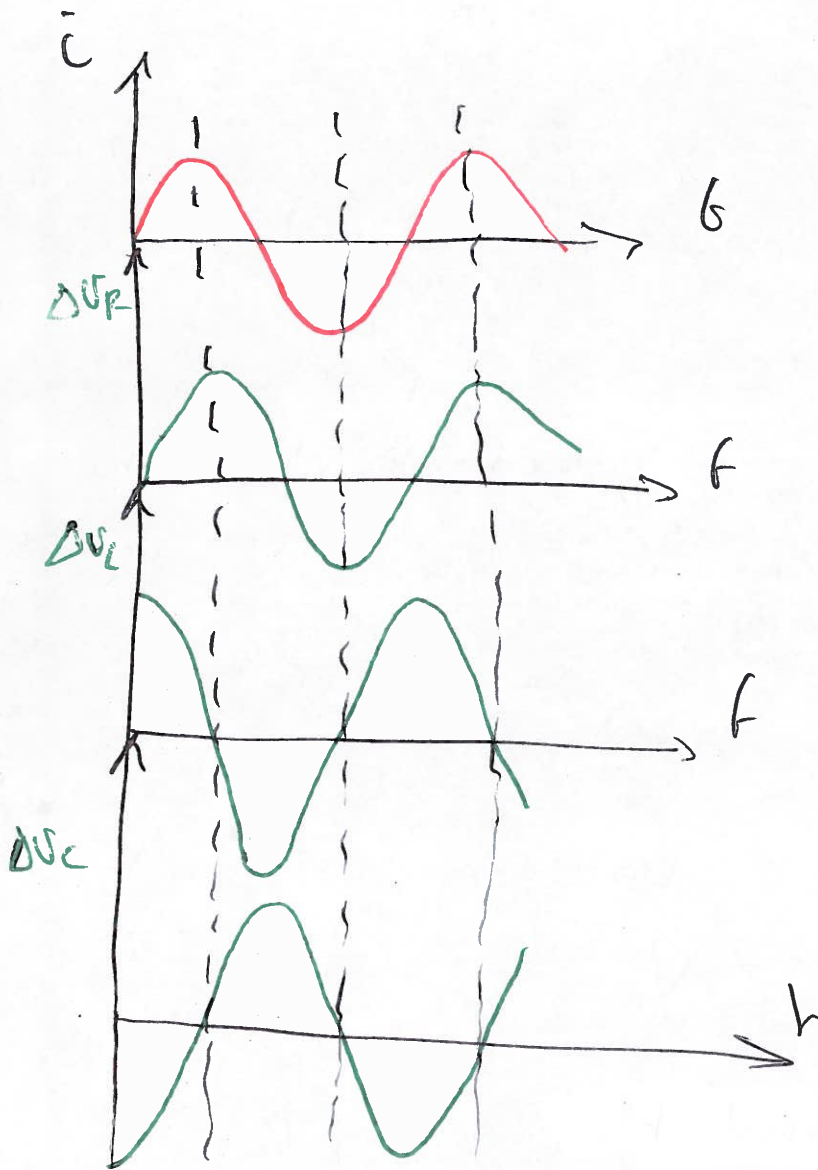

Phasor

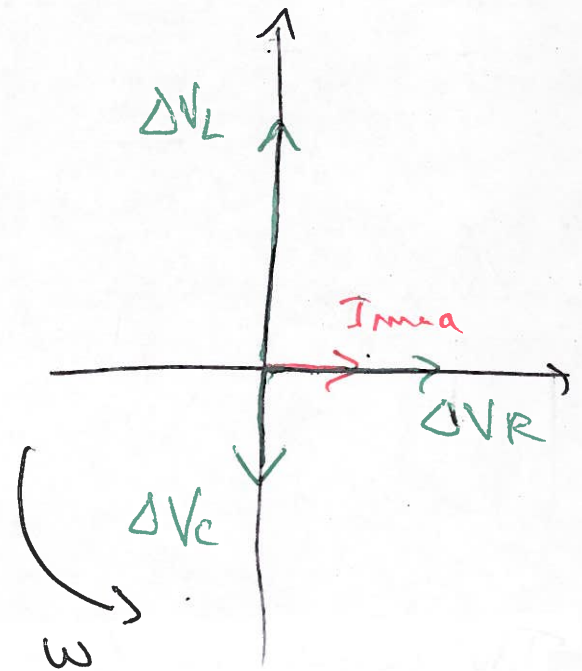

(at an instant at which $i=0$)

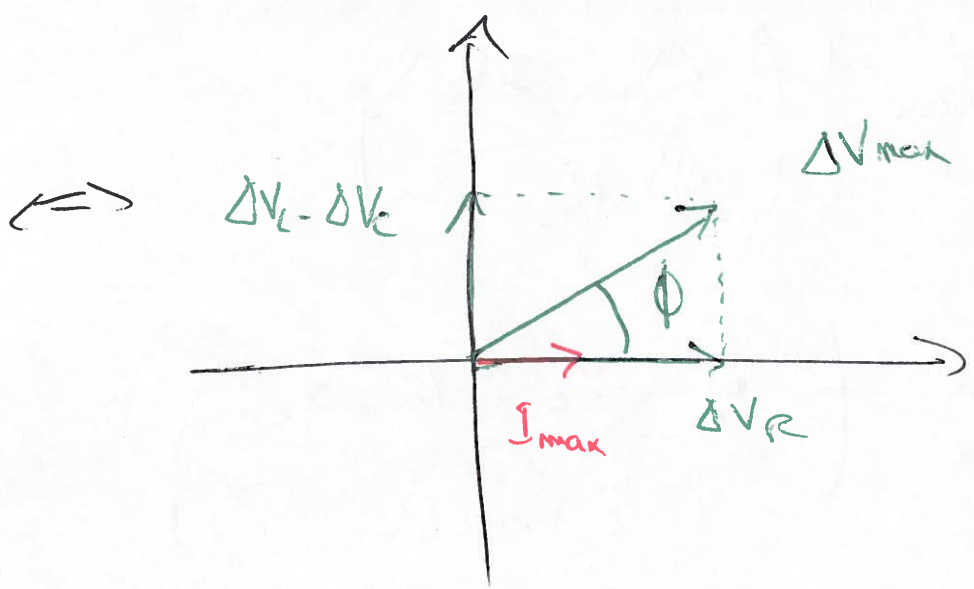

⇒ Vectorial summation $\Delta U = \Delta U_R + \Delta U_L + \Delta U_C$

$$\begin{aligned} \Rightarrow \Delta V_{max} &= \sqrt{\Delta V_R^2 + (\Delta V_L - \Delta V_C)^2} \\ &= \sqrt{(I_{max} R)^2 + (I_{max} X_L - I_{max} X_C)^2} \\ &= I_{max} \sqrt{R^2 + (X_L - X_C)^2} \end{aligned}$$

Impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$ in ohm

$$I_{max} = \frac{\Delta V_{max}}{Z} \Rightarrow I_{rms} = \frac{\Delta V_{rms}}{Z}$$

$$\phi = \tan^{-1} \left(\frac{\Delta V_L - \Delta V_C}{\Delta V_R} \right)$$

$$= \tan^{-1} \left(\frac{I_{\max} X_L - I_{\max} X_C}{I_{\max} R} \right)$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$X_L > X_C$, at higher frequencies $\Rightarrow \phi > 0$
 \Rightarrow the current lags behind the voltage

\Rightarrow the circuit is more inductive than capacitive

$X_L < X_C$, at lower frequencies $\Rightarrow \phi < 0$

\Rightarrow the current leads the applied voltage

\Rightarrow the circuit is more capacitive than inductive

$X_L = X_C \Rightarrow$ circuit purely resistive

Power in an AC circuit

18

Instantaneous power

$$P = i \Delta v = I_{\max} \sin(\omega t - \phi) \Delta V_{\max} \sin(\omega t)$$

$$P = \underline{I_{\max} \Delta V_{\max}} \sin(\omega t) \sin(\omega t - \phi)$$

↳ average power over one or more cycles

We are using: $\sin(\omega t - \phi) = \sin \omega t \cos \phi - \cos \omega t \sin \phi$

$$\Rightarrow P = I_{\max} \Delta V_{\max} \sin^2 \omega t \cos \phi - I_{\max} \Delta V_{\max} \sin \omega t \cos \omega t \sin \phi$$

Average of $\sin^2 \omega t$ over 1 or more cycles $\Rightarrow \underline{\underline{1/2}}$

Average of $\sin \omega t \cos \omega t$ over one or more cycles

$$\Rightarrow \sin \omega t \cos \omega t = \frac{1}{2} \sin 2\omega t \Rightarrow \text{average} = \underline{\underline{0}}$$

$$\Rightarrow P_{\text{avg}} = \frac{1}{2} I_{\max} \Delta V_{\max} \cos \phi \rightarrow \text{power factor}$$

$$P_{\text{avg}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi$$

From phasor diagram

$$\cos \phi = \Delta V_R / \Delta V_{\max} = R I_{\max} / \Delta V_{\max}$$

$$\Rightarrow \cos \phi = R / Z$$

$$\Rightarrow P_{\text{avg}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi$$

$$= I_{\text{rms}} \Delta V_{\text{rms}} \left(\frac{R}{Z} \right)$$

$$= I_{\text{rms}} \left(\frac{\Delta V_{\text{rms}}}{Z} \right) R = R I_{\text{rms}}^2$$

$\underbrace{\hspace{10em}}_{I_{\text{rms}}}$

$$P_{\text{avg}} = R I_{\text{rms}}^2$$

average power converted into internal energy in the resistor, as in DC circuit

When $\phi = 0$, $\cos \phi = 1 \Rightarrow P_{\text{avg}} = I_{\text{rms}} \Delta V_{\text{rms}}$

\Rightarrow no power losses associated with pure capacitor and pure inductor

of: the capacitor charges and discharge L9

twice over each cycle \Rightarrow average energy = 0

Idem for the inductor

Resonance in a serie RLC circuit

Circuit in resonance \Rightarrow the driving frequency is such that the rms current is max

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = \frac{\Delta V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}}$$


I_{rms} maximum at ω_0 at which $X_L = X_C$
($X_L - X_C = 0$)

$$X_L = X_C \Leftrightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

$$\Leftrightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Resonance frequency

=
natural oscillation of an LC circuit

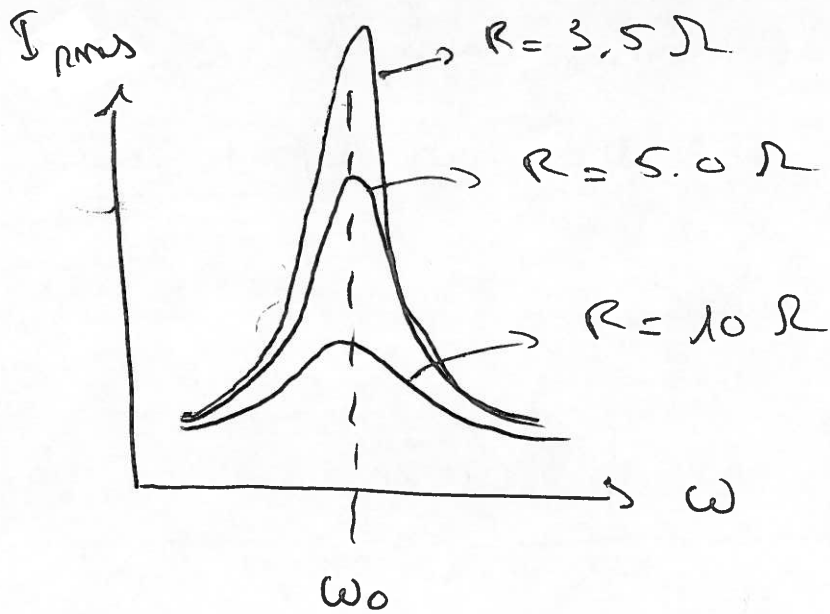


$$\begin{aligned}
 P_{\text{avg}} &= I_{\text{rms}}^2 R = \frac{(\Delta V_{\text{rms}})^2}{Z^2} R \\
 &= \frac{(\Delta V_{\text{rms}})^2 R}{R^2 + (X_L - X_C)^2}
 \end{aligned}$$

$$X_L = \omega L, \quad X_C = 1/\omega C, \quad \omega_0^2 = 1/LC$$

$$\begin{aligned}
 (X_L - X_C)^2 &= \left(\omega L - \frac{1}{\omega C} \right)^2 \\
 &= \frac{L^2}{\omega^2} (\omega^2 - \omega_0^2)^2
 \end{aligned}$$

$$\Rightarrow P_{avg} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$

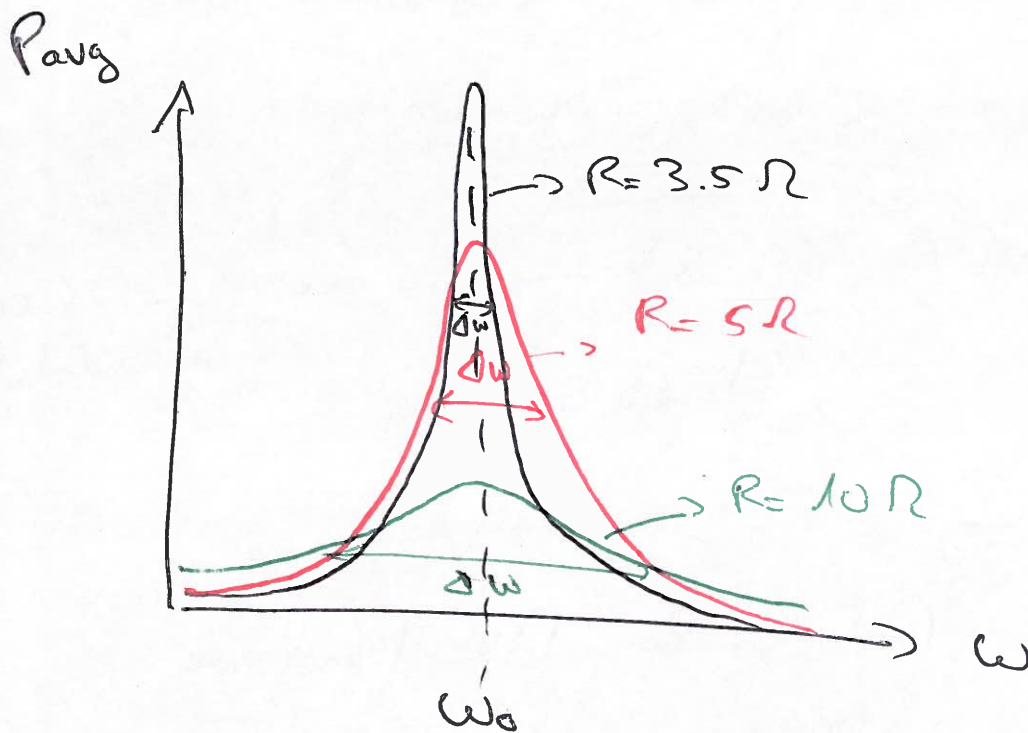\Rightarrow P_{avg} is maximum when $\omega = \omega_0$
 and has the value $(\Delta V_{rms})^2 / R$



$$\Delta \omega \Rightarrow \text{half power point} \\ = R/L$$

Quality factor $\parallel Q = \frac{\omega_0}{\Delta \omega} = \frac{\omega_0 L}{R}$

\Rightarrow eg. Radio. receiving circuit

The radio is tuned by varying a capacitor, which changes $\omega_0 \Rightarrow$ signal passes through amplifier and speakers

⇒ high-Q circuits are needed to eliminate unwanted signals (from other radio stations)


Transformer and Power transmission

To minimize RI^2 loss in transmission lines

⇒ high voltage transmission

Usually 350 or 765 kV → 20,000 V → 4,000 V (residential area)
→ 120 V
240 V at customer's site.

Role of the AC transformer

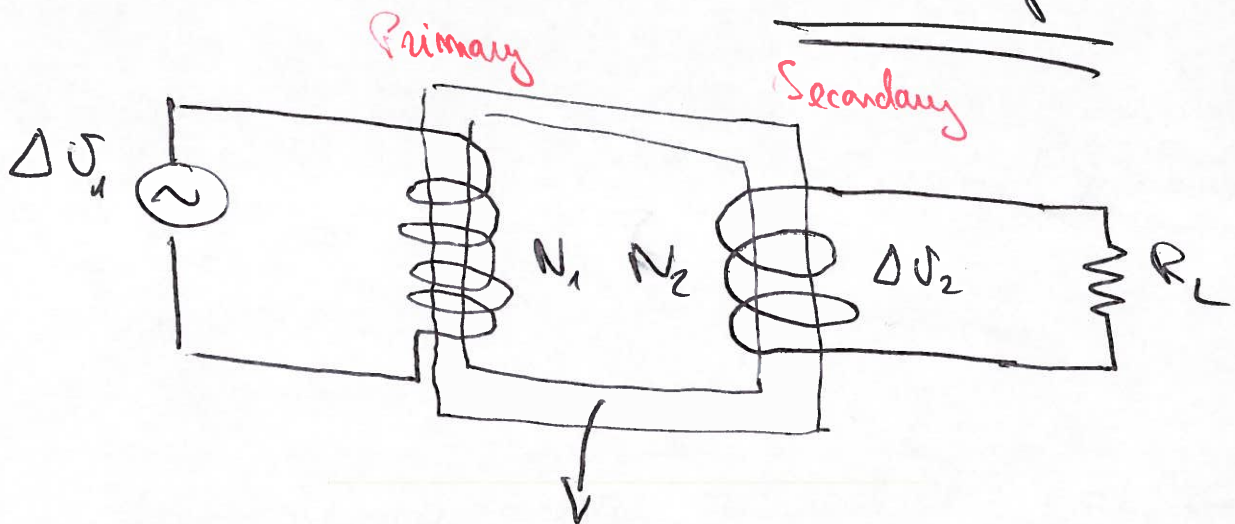

iron core to ↑ magnetic flux
through the coils ⇒ all magnetic field lines inside the core ⇒ laminated core to ↓ eddy currents

$$\Delta V_1 = - N_1 \frac{d\phi_B}{dt}$$

$$\Delta V_2 = - N_2 \frac{d\phi_B}{dt}$$

same $d\phi_B/dt$ because of the iron core

$$\Rightarrow \Delta V_2 = \frac{N_2}{N_1} \Delta V_1$$

$N_2 > N_1$: step up transformer

$N_1 > N_2$: step down transformer.

Ideal transformer \Rightarrow no loss in power through transmission

$$I_{1\text{ rms}} \Delta V_{1\text{ rms}} = I_{2\text{ rms}} \Delta V_{2\text{ rms}}$$

$$\Rightarrow I_{L\text{ rms}} = \frac{\Delta V_{2\text{ rms}}}{R_L} = \frac{I_{1\text{ rms}} \Delta V_{1\text{ rms}}}{\Delta V_{2\text{ rms}}}$$

$$\Leftrightarrow \frac{(\Delta V_{L\text{ rms}})^2}{R_L} = I_{1\text{ rms}} \Delta V_{1\text{ rms}}$$

$$\Leftrightarrow \frac{(N_2/N_1)^2 \Delta V_{1, rms}}{R_L} = I_{1, rms} \Delta V_{1, rms}$$

$$\Rightarrow \Delta V_{1, rms} = \left(\frac{N_1}{N_2} \right)^2 R_L I_{1, rms}$$

$R_{eq} \Rightarrow$ equivalent resistance view
from the primary circuit

$R_{eq} = \left(\frac{N_1}{N_2} \right)^2 R_L \Rightarrow$ a transformer is matched
the resistance between the
primary circuit and the load

\Rightarrow max power transfer

ex: A transformer to connect a 1 k Ω output of the audio amp
to a 8 Ω speaker.

\Rightarrow Impedance matching


Rectifier and filters

To convert AC to DC for most devices (radios, laptop, ...) => Rectifier

Use of a diode




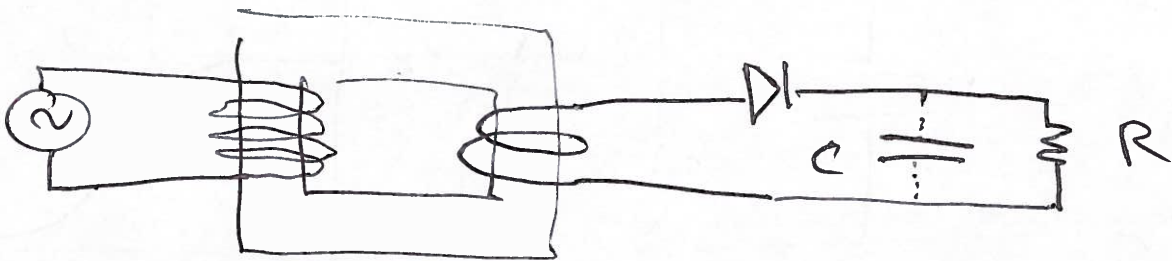low resistance in the direction of the arrow, high resistance in the other direction.




One need to remove small 60 Hz oscillat: (ripple)

RC high pass filter

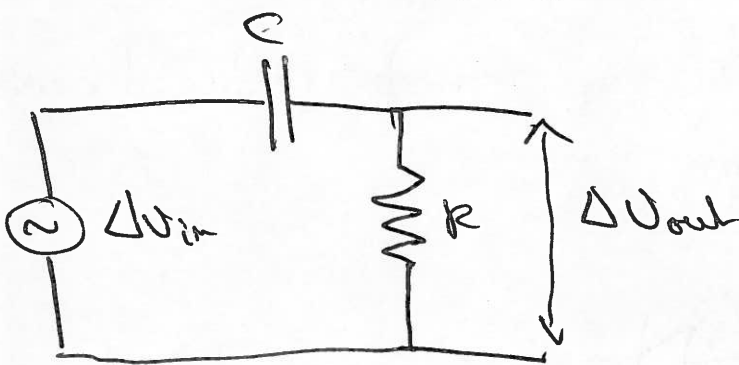


$\Delta V_{out} / \Delta V_{in}$

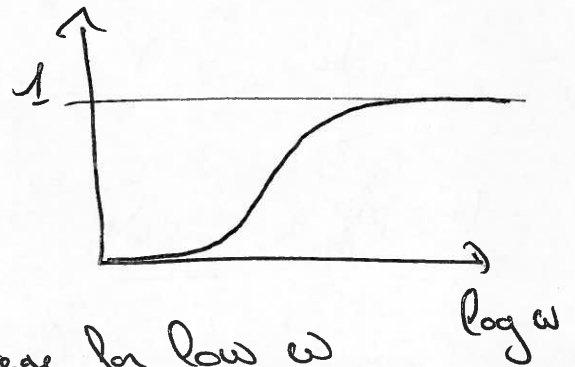


of: $X_c = 1 / \omega$, large for low ω

RC Low Pass filter

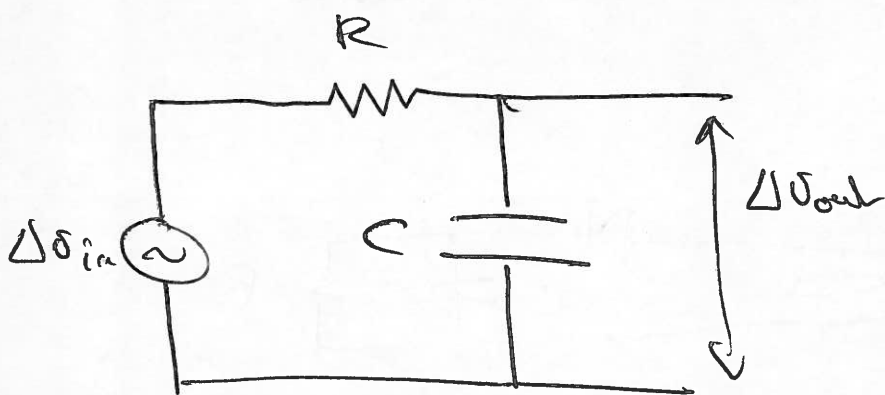

$\Delta V_{out} / \Delta V_{in}$

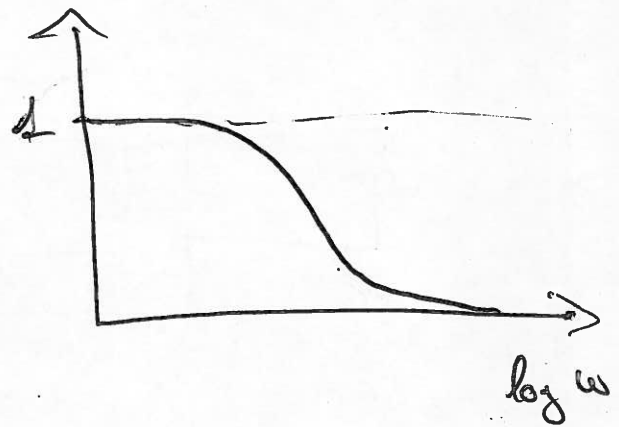

of: low pass \Rightarrow "woofer" speaker

high pass \Rightarrow "tweeter" speaker