

Midterm 2 Examination

ECSE 330: Introduction to Electronics

March 10, 2017

11:35 AM – 12:55 PM


Professor: David V. Plant

Pertinent Information:


- 1) This is a closed-book examination, no notes permitted.
- 2) The examination consists of 4 problems and 36 total possible points.
- 3) Only the Faculty Standard Calculator is permitted.
- 4) This paper will NOT be collected. Write all answers in the answer booklet only.
- 5) You must show all your work. An answer by itself is worth zero points.

Question #1 [8 points]

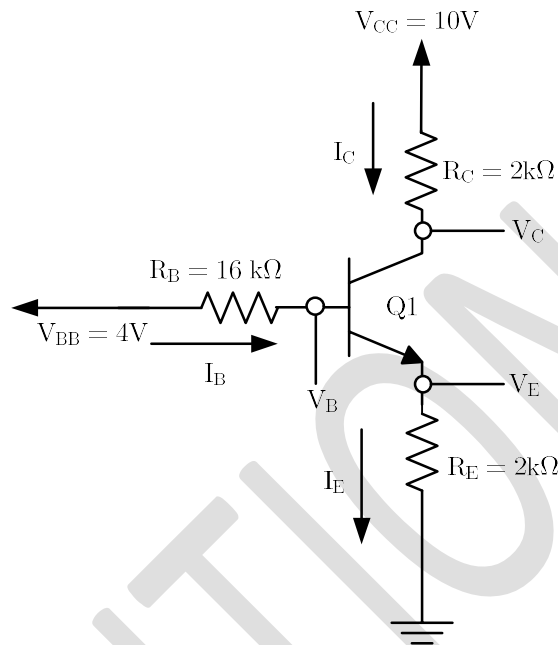- (a) [6 points] In the circuit shown below, find the values of the following voltages and currents (1 point per answer): V_B , V_E , V_C , I_B , I_C , and I_E . Clearly state your assumptions and check their validity. The transistor has $\beta = 100$ and $V_{BCon} = 0.4 \text{ V}$.



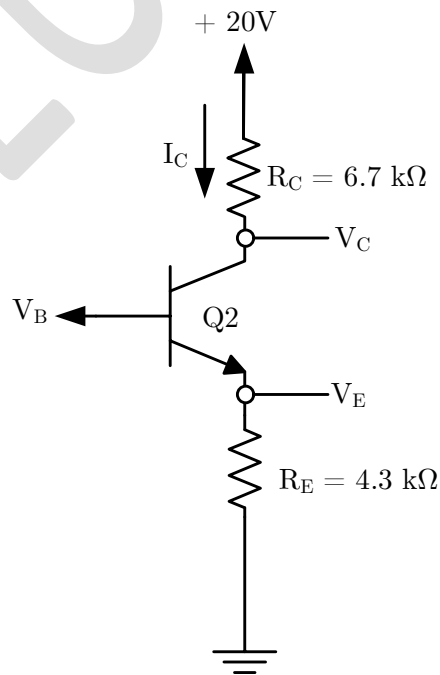
- (b) [2 points] For the circuit shown below, find the highest voltage to which the base can be raised while the transistor remains in active mode. The transistor has $\alpha = 1$ ($\beta \rightarrow \infty$) and $V_{BCon} = 0.4 \text{ V}$.



Question # 1

* Assume active mode of operation ($V_{BC} < 0.4V$)

(a)

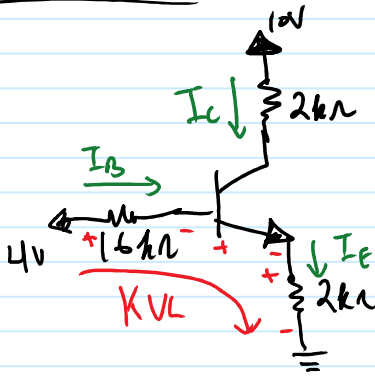

$$4V - I_B 16k\Omega - 0.7V - I_E 2k\Omega = 0 \quad \leftarrow \text{loop, 2 unknowns}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{I_E}{101}$$

$$4V - \frac{I_E}{101} 16k\Omega - 0.7V - I_E 2k\Omega = 0 \quad \leftarrow \text{now, 1 eqn, 1 unknown}$$

$$-I_E \left(\frac{16k\Omega}{101} + 2k\Omega \right) = -4V + 0.7V$$

$$I_E = \frac{4V - 0.7V}{\frac{16k\Omega}{101} + 2k\Omega} = \frac{3.3V}{2.1589k\Omega} = 1.53mA$$

$$I_E = 1.53mA$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{1.53mA}{101} = 0.015mA$$

$$I_B = 0.015mA$$

$$I_C = \beta I_B = 100(0.015mA) = 1.514mA$$

$$I_C = 1.514mA$$

$$V_E = I_E 2k\Omega = V_E = 3.06V$$

$$V_B = 4V - I_B 16k\Omega = 4V - (0.015mA)(16k\Omega) = V_B = 3.76V$$

$$V_C = 10V - I_C(2k\Omega) = 10V - 1.514mA(2k\Omega) = V_C = 6.97V$$

$V_{BC} < V_C + 0.4V$
 $3.76V < 6.97V$
 $\therefore Q_1$ is indeed in active mode ✓

b) for active mode, need transistor on AND $V_{BC} < V_{BC(on)}$
 $V_{BC} < V_{BC(on)} + V_C$

$$V_B < V_{BC(on)} + V_C$$

at edge of saturation & active

$$V_B = V_{BC(on)} + V_C$$

Ohm's law

$$V_C = V_{CC} - I_C R_C$$

Since $\alpha = 1$ ($\beta \rightarrow \infty$) $I_C = \alpha I_E$ [and $I_B = 0$]
 $I_C = I_E$

$$I_C = I_E = \frac{V_B - V_{BE}}{R_E}$$

Substitute in V_C

$$V_C = V_{CC} - \left[\frac{V_B - V_{BE}}{R_E} \right] R_C = V_{CC} - \frac{R_C}{R_E} (V_B - V_{BE})$$

$$V_B = V_{Bcon} + V_c$$

$$V_B = V_{Bcon} + V_{cc} - \frac{R_c}{R_E} (V_B - V_{BE})$$

$$V_B = V_{Bcon} + V_{cc} - \frac{R_c}{R_E} V_B + \frac{R_c}{R_E} V_{BE}$$

$$V_B \left(1 + \frac{R_c}{R_E}\right) = V_{Bcon} + V_{cc} + \frac{R_c}{R_E} V_{BE}$$

$$V_B = \frac{V_{Bcon} + V_{cc} + \frac{R_c}{R_E} V_{BE}}{\left(1 + \frac{R_c}{R_E}\right)}$$


$$V_B = \frac{0.4V + 20V + \frac{6.7k\Omega}{4.3k\Omega} 0.7V}{\left(1 + \frac{6.7k\Omega}{4.3k\Omega}\right)}$$

$$\left(\frac{R_c}{R_E} = \frac{6.7k\Omega}{4.3k\Omega} = 1.558\right)$$

$$V_B = 8.40V$$

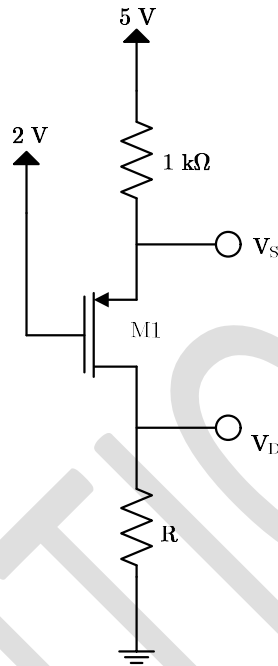Question #2 [9 points]

Consider the transistor biasing arrangement shown below. For all parts of this question, the transistor has $k'_p = 100 \mu\text{A}/\text{V}^2$, $V_{tp} = -1 \text{ V}$, and assume that the body effect and the channel length modulation effect can be ignored, i.e., $\lambda = 0$. The voltages V_S and V_D , the current, resistor R , and the other parameters of the transistors are distinct for each subpart of the question.



- (a) If the transistor is in the saturation region and given that $(W/L) = 20$ and $R = 1 \text{ k}\Omega$, determine:
- [1 point] the source voltage V_S
 - [1 point] the drain current I_D
 - [1 point] the drain voltage V_D
- (b) [2 points] Consider another biasing scheme for the circuit above, where the width of the transistor, the ratio W/L , and the resistor R are unknown. The desired drain current I_D is $200 \mu\text{A}$ and drain voltage V_D is 1 V . Given that $L = 0.2 \mu\text{m}$, determine
- [1 point] the value required for R and the mode of operation of the transistor, and
 - [1 point] the value required for the width of the transistor W
- (c) Given that $(W/L) = 20$ and $V_S = 4 \text{ V}$.
- [2 points] Find the condition on the value of R for the transistor to be in the triode regime.
 - [2 points] Given $R = 3.5 \text{ k}\Omega$, find the drain current I_D in the triode region.

Question #2

$k'_p = 100 \mu A/V^2$ $V_{tp} = -1V$

a) in saturation mode $\therefore I_D = \frac{1}{2} k'_p \frac{W}{L} (V_{GS} - V_{tp})^2 = \frac{1}{2} k'_p \frac{W}{L} (V_G - V_S - V_{tp})^2$
 $\begin{matrix} W/L = 20 \\ R = 1k\Omega \end{matrix}$
 $\begin{matrix} \hookrightarrow 20 \\ = \frac{1}{2} (100 \times 10^6) (20) (2V - V_S - (-1V))^2 \\ I_D = 1 \times 10^{-3} A/V^2 (3V - V_S)^2 \rightarrow 2 \text{ unknowns} \end{matrix}$

MOSFET $\therefore I_D = I_S = \frac{5 - V_S}{1k\Omega}$

$\frac{5V - V_S}{1k\Omega} = 1 \times 10^{-3} A/V^2 (3V - V_S)^2 \rightarrow \text{now, 1 unknown}$

$5 - V_S = 1 A/V^2 (3V - V_S)^2$

$5 - V_S = 9V - 6V_S + V_S^2$

$0 = V_S^2 - 5V_S + 4V \Rightarrow$ factors of +4 that add up to -5 are -4 & -1

$0 = (V_S - 4)(V_S - 1)$

$\begin{matrix} V_S = 4 & \hookrightarrow V_S = 1 \\ \downarrow & \downarrow \\ V_{GS} = 2V - 4V = -2V & V_{GS} = 2V - 1V = +1V \Rightarrow \text{PMOS would be off} \rightarrow \text{bad solution} \\ \text{good solution} & \end{matrix}$

(i) $V_S = 4V$

(ii) $I_D = I_S = \frac{5V - 4V}{1k\Omega} = 1mA$ $I_D = 1mA$

(iii) $V_D = I_D R = 1mA (1k\Omega) = 1V$ $V_D = 1V$

b) $I_D = 200\mu A$, $V_D = 1V$, $L = 0.2\mu m$

(i) $R = \frac{V_D}{I_D} = \frac{1V}{200\mu A} = 5k\Omega$ $R = 5k\Omega$

for saturation mode $V_{DS} \leq V_{GS} - V_{tp}$
 $V_D - V_S \leq V_G - V_S - V_{tp}$

$V_D \leq V_G - V_{tp}$
 $\leq 2V - (-1V)$
 $1V \leq 3V$

(Note: V_D & V_G same as in part (a) \therefore if (a) is in saturation, so is (b))

\therefore transistor is in saturation mode

(ii) Since transistor in saturation mode: $I_D = \frac{1}{2} k'_p \frac{W}{L} (V_{GS} - V_{tp})^2$
 $\begin{matrix} \uparrow & \uparrow & \uparrow \\ 200\mu A & 100\mu A/V^2 & V_G = 2V \\ & & L = 0.2\mu m \\ & & -1V \end{matrix}$

need V_S , $V_f = 5V - I_S(1k\Omega) = 5V - 0.2mA(1k\Omega) = 4.8V$ " $I_D = 200\mu A$ "

$$V_{GS} = 2V - 4.8V = -2.8V$$

$$I_D = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_{tp})^2$$

$$W = \frac{L \cdot I_D \cdot 2}{k_p (V_{GS} - V_{tp})^2} = \frac{0.2\mu m \cdot 200\mu A \cdot 2}{100\mu A/V^2 (-2.8V - (-1V))^2} = \frac{80\mu m \cdot \mu A}{100\mu A/V^2 \cdot 3.24V^2} = 0.247\mu m$$

$$W = 0.25\mu m$$

(c) $W/L = 20$ & $V_S = 4V$

(i) transistor in triode when $V_{DS} \geq V_{GS} - V_{tp}$

$$V_{DS} \geq V_{GS} - V_{tp}$$

$$V_D - V_S \geq V_G - V_S - V_{tp}$$

$$V_D \geq V_G - V_{tp}$$

$$V_D \geq 2V - (-1V)$$

need $V_D \geq 3V$ for triode mode

$$V_D = I_D R$$

$$I_D R \geq 3V$$

$$R \geq \frac{3V}{I_D}$$

$$I_D = I_S = \frac{5V - V_S}{1k\Omega} = \frac{5V - 4V}{1k\Omega} = 1mA$$

$$\therefore R \geq \frac{3V}{1mA} = 3k\Omega$$


want $R > 3k\Omega$

(ii)

if $V_S = 4V$, then $I_D = I_S = \frac{5V - 4V}{1k\Omega} = 1mA$ (\Rightarrow 2 easy points \smile)

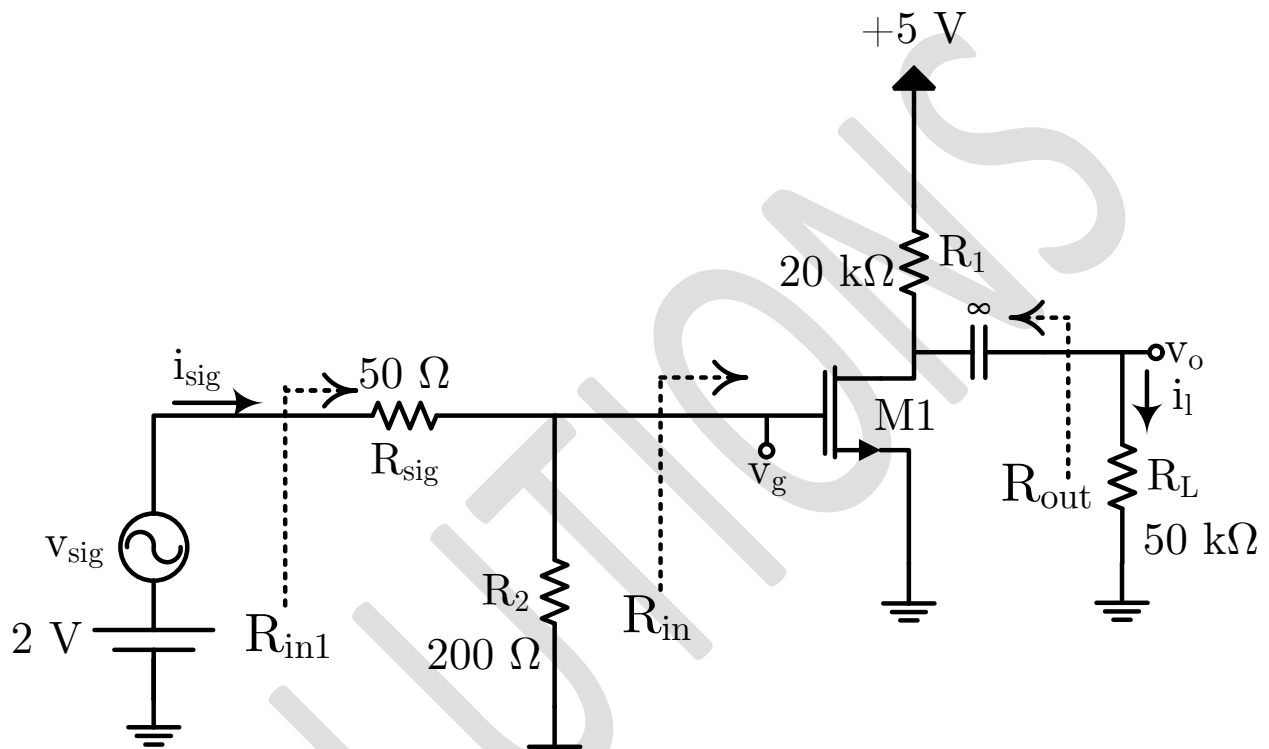
Question #3 [9 points]

The following figure depicts an amplifier circuit with the resistances indicated in the figure, infinitely large capacitances, and where v_{sig} is an AC-only signal source. The transistor is in saturation mode and has $k_n = 200 \mu\text{A}/\text{V}^2$, $V_{tn} = 0.5 \text{ V}$, an output resistance r_o of $413.2 \text{ k}\Omega$ due to the channel-length modulation (CLM) effect and a DC drain current I_D (including the CLM effect) of $127.24 \mu\text{A}$.



- (a) [2 points] Draw the small-signal equivalent circuit and determine the small-signal parameter g_m .
- (b) [3 points] Find the resistance seen at the voltage source (R_{in}), at the gate (R_{in1}), and at the output (R_{out}). Provide both the expression and the numerical value.
- (c) [4 points] Determine the following small-signal voltage gains (i) $\frac{v_g}{v_{sig}}$, (ii) $\frac{v_o}{v_g}$, (iii) the overall voltage gain $\frac{v_o}{v_{sig}}$, and (iv) the overall current gain $\frac{i_l}{i_{sig}}$. Provide both the expression and the numerical value.

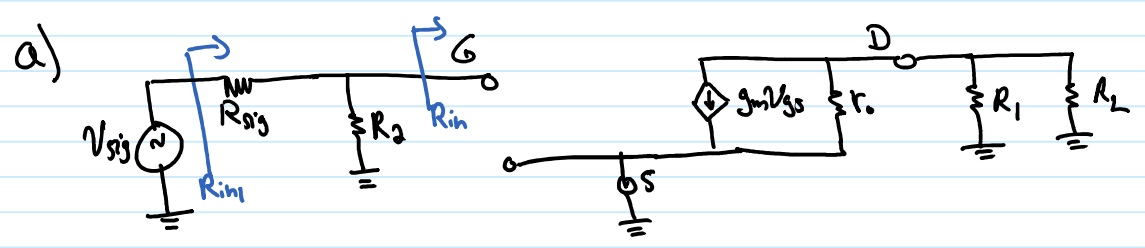Question 3 \Rightarrow has channel-length modulation, must include effect of r_o
 [M1 has source at AC ground, v_o is final to include]



$$g_m = \frac{2 I_D}{V_{GS} - V_{th}} \Rightarrow \text{need to find } V_{GS}, \text{ quick DC analysis}$$

$$V_{GS} = \frac{R_2}{R_{sig} + R_2} (2V) = 1.6V$$

$$g_m = \frac{2(127.24 \mu A)}{1.6V - 0.5V} = g_m = 0.23134 \text{ mA/V} \quad [231.34 \mu A/V]$$

b) because of oxide (insulator) at gate

$$R_{in} = \infty$$

at source:

$$R_{in1} = R_{sig} + R_2 \parallel R_{in} \approx \infty$$

$$= R_{sig} + R_2$$

$$= 50\Omega + 200\Omega$$

$$R_{in1} = 250\Omega$$

* Note! typo in question sheet R_{in} & R_{in1} answers could be flipped

$R_{out} \Rightarrow$ turn off signal source, $v_{sig} = 0 \Rightarrow V_{GS} = 0 \Rightarrow g_m v_{gs} = 0$ [VDCS is open circuit]

$$R_{out} = R_1 \parallel R_L = 20 \text{ k}\Omega \parallel 413.2 \text{ k}\Omega = 19.08 \text{ k}\Omega = v_o$$

c) (i) $\frac{v_g}{v_{sig}} \Rightarrow$ voltage divider $= \frac{R_2}{R_{sig} + R_2} = \frac{200\Omega}{200\Omega + 50\Omega} = 4/5 = 0.8$

$$\frac{v_o}{v_{sig}} = 0.8$$

(ii) $\frac{v_o}{v_g} \Rightarrow v_o = -g_m v_{gs} (r_o \parallel R_1 \parallel R_L)$

$$v_{gs} = v_g \text{ because source terminal is at AC ground}$$

$$\frac{v_o}{v_g} = -g_m (r_o \parallel R_1 \parallel R_L)$$

$$r_o \parallel R_1 \parallel R_L = \left(\frac{1}{413.2 \text{ k}\Omega} + \frac{1}{20 \text{ k}\Omega} + \frac{1}{50 \text{ k}\Omega} \right)^{-1} = 13.808 \text{ k}\Omega$$

$$\frac{v_o}{v_g} = (-0.231 \text{ mA/V})(13.808 \text{ k}\Omega) = -3.19 \text{ V/V} \quad \frac{v_o}{v_g} = -3.19 \text{ V/V}$$

$$(ii) \frac{v_o}{v_{sig}} = \frac{v_o}{v_b} \times \frac{v_b}{v_{sig}} = (-3.19 \text{ V/V})(0.8 \text{ V/V}) = -2.56 \text{ V/V}$$


$$\frac{v_o}{v_{sig}} = -2.56 \text{ V/V}$$

$$(iv) \frac{v_o}{v_{sig}} = \frac{i_L R_L}{i_{sig} R_{in2}} \Rightarrow \frac{i_L}{i_{sig}} = \frac{R_{in2}}{R_L} \left(\frac{v_o}{v_{sig}} \right) = \frac{250 \Omega}{50000 \Omega} (-2.56 \text{ V/V})$$

$$\frac{i_L}{i_{sig}} = -0.0128 \text{ A/A}$$

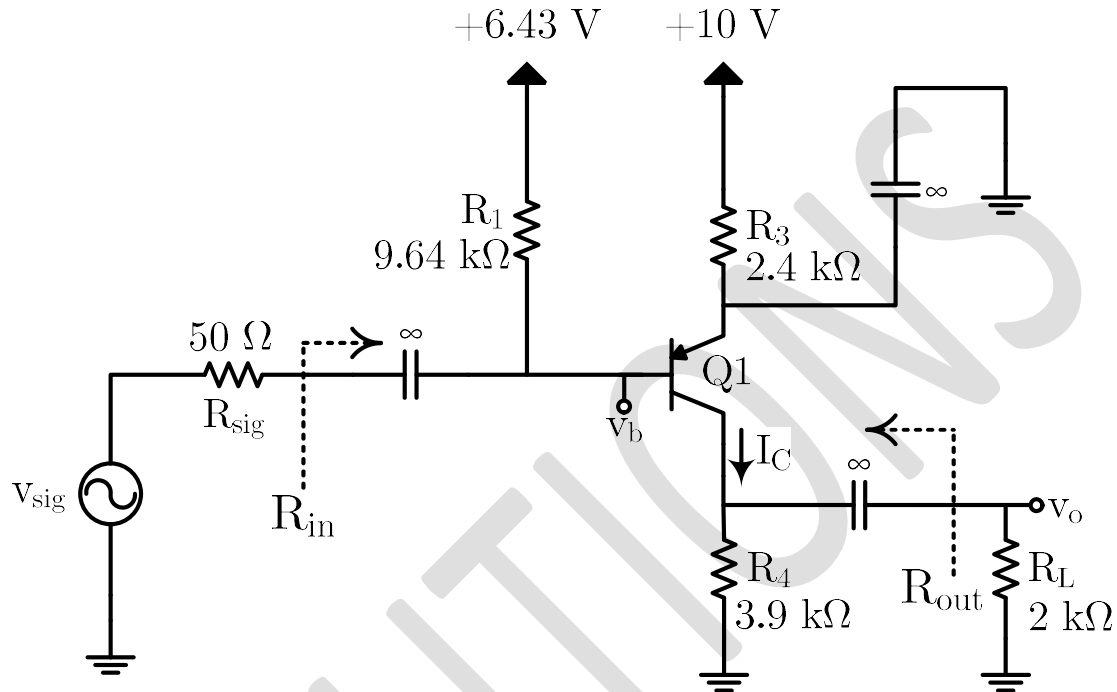Question #4 [10 points]


The following figure depicts an amplifier circuit with the resistances indicated in the figure, infinitely large capacitances, and where v_{sig} is an AC-only signal source. The transistor is in active mode and has $\beta = 100$.




- [2 points] Perform a DC analysis and determine the current flowing through the collector (I_c).
- [3 points] Draw the small-signal equivalent circuit, and determine the small-signal parameters g_m and r_π or r_e . Provide both the expression and the numerical value.
- [2 points] Calculate the small-signal resistance seen at the input (R_{in}) and at the output (R_{out}), as drawn in the schematic above. Provide both the expression and the numerical value.
- [3 points] Determine the following small-signal voltage gains (i) $\frac{v_b}{v_{sig}}$, (ii) $\frac{v_o}{v_b}$, and (iii) the overall voltage gain $\frac{v_o}{v_{sig}}$. Provide both the expression and the numerical value.

Question 4

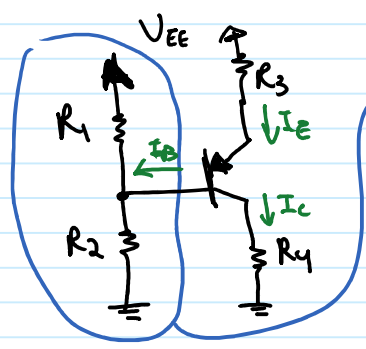a) DC analysis: caps \rightarrow dc, AC sources off




Thevenin equivalent

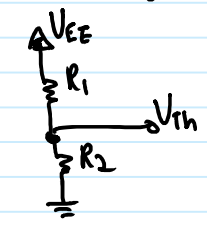


$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{EE} = \frac{27k\Omega}{27k\Omega + 15k\Omega} (10V)$$

$$V_{TH} = 6.4286 V$$

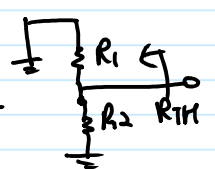

$$R_{TH} = R_1 || R_2 = \frac{15k\Omega \cdot 27k\Omega}{15k\Omega + 27k\Omega} = 9.6429 k\Omega$$

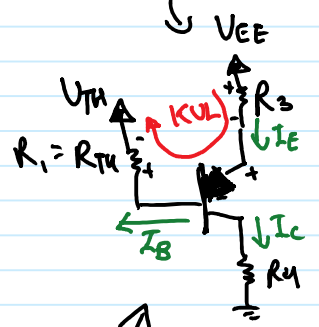

KVL: $V_{EE} - I_E R_3 - V_{EB} - I_B R_{TH} = V_{TH}$

$$I_B = \frac{I_E}{\beta + 1} = \frac{I_E}{101}$$

(Or put both I_B & I_E in terms of I_C and solve directly for I_C)

$$V_{EE} - I_E R_3 - V_{EB} - \frac{I_E R_{TH}}{\beta + 1} = V_{TH}$$

$$-I_E \left(R_3 + \frac{R_{TH}}{\beta + 1} \right) = V_{TH} + V_{EB} - V_{EE}$$


$$I_E = \frac{V_{EE} - V_{TH} - V_{EB}}{\left(R_3 + \frac{R_{TH}}{\beta + 1} \right)} = \frac{10V - 6.4286V - 0.7V}{2.4k\Omega + \frac{9.6429k\Omega}{101}} = \frac{2.8714V}{2.4955k\Omega}$$

$$I_E = 1.15 mA$$

Note: to save time changed Q4 to start from this point

$$I_C = \alpha I_E = \left(\frac{\beta}{\beta + 1} \right) I_E = 1.139 mA = 1.14 mA \Rightarrow I_C = 1.14 mA$$

b)

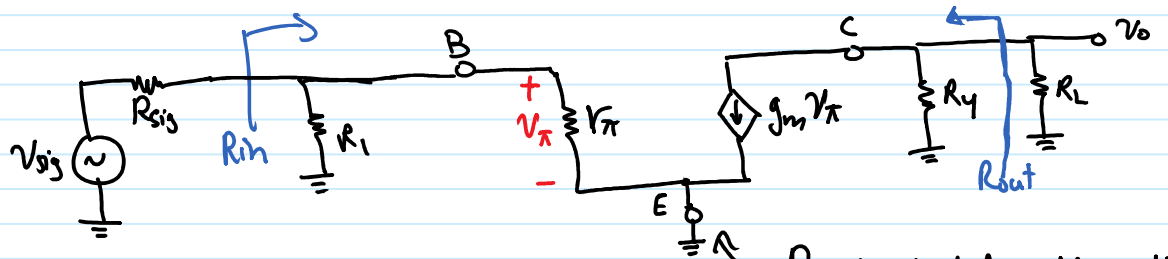

R_3 is shorted out by path to AC ground via capacitor

from (a)

$$g_m = \frac{I_C}{V_T} = \frac{1.14 mA}{25 mV} = g_m = 0.0456 A/V$$

$$r_{\pi} = \beta \frac{V_T}{I_C} = (100) \frac{25 \text{ mV}}{1.14 \text{ mA}} = 2192.98 \Omega = 2.193 \text{ k}\Omega$$

$$r_{\pi} = 2.19 \text{ k}\Omega$$

$$c) R_{in} = R_1 \parallel r_{\pi} = \frac{2.19 \text{ k}\Omega \cdot 9.64 \text{ k}\Omega}{2.19 \text{ k}\Omega + 9.64 \text{ k}\Omega} = 1.78 \text{ k}\Omega$$

$$R_{in} = 1.78 \text{ k}\Omega$$

$R_{out} \Rightarrow$ turn off signal source $\therefore V_{sig} = 0 \Rightarrow v_{\pi} = 0 \Rightarrow g_m v_{\pi} = 0$, i.e., VDCS is off open-circuit

$$R_{out} = R_4 = 3.9 \text{ k}\Omega$$

d)

$$(i) v_b = \frac{r_{\pi} \parallel R_1}{r_{\pi} \parallel R_1 + R_{sig}} v_{sig} = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig} \Rightarrow \frac{v_b}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{1.78 \text{ k}\Omega}{1.78 \text{ k}\Omega + 0.05 \text{ k}\Omega}$$

$$\frac{v_b}{v_{sig}} = 0.97 \text{ V/V}$$

$$(ii) \frac{v_o}{v_b} \Rightarrow v_o = -g_m v_{\pi} (R_4 \parallel R_L) \Rightarrow \frac{v_o}{v_b} = -g_m (R_4 \parallel R_L)$$

$v_b = v_{\pi}$ because emitter of A1 ground

$$R_4 \parallel R_L = 1.322 \text{ k}\Omega$$

$$\frac{v_o}{v_b} = -(0.0456 \text{ A/V})(1322.03 \text{ V/A}) = -60.285 \text{ V/V}$$

$$\frac{v_o}{v_b} = -60.29 \text{ V/V}$$

(iii) overall voltage gain

$$\frac{v_o}{v_{sig}} = \frac{v_o}{v_b} \times \frac{v_b}{v_{sig}} = -60.285 \text{ V/V} \times 0.9722 \text{ V/V} = -58.645 \text{ V/V}$$

$$\frac{v_o}{v_{sig}} = -58.65 \text{ V/V} \approx -58.48 \text{ V/V}$$