



• PNP
• $\beta = 100$

Active mode
 $\hookrightarrow V_C < V_B$

1) Active mode

$$I_E = (\beta + 1) I_B$$

$$I_C = \beta I_B$$

$$V_E = 3 - 3.3k(I_E)$$

$$= 3 - 3.3k(-0.167 \text{ mA})$$

$$V_E = 3.55 \text{ V}$$

$$V_B = V_E - 0.7$$

$$V_B = 2.85 \text{ V}$$

$$V_C = -3 - 3.3k(I_C)$$

$$V_C = -2.45 \text{ V}$$

KVL at BE loop

$$\hookrightarrow -3 \text{ V} + 3.3k \cdot I_E + 0.7 + 91k \cdot \frac{I_E}{\beta + 1} + 3 \text{ V} = 0$$

$$\hookrightarrow -0.7 = 3.3k(I_E) + 91k \cdot \frac{1}{\beta + 1} (I_E)$$

$$\hookrightarrow -0.7 = I_E \left[3.3k + 91k \cdot \frac{1}{101} \right]$$

$$-0.7 = I_E (4201)$$

$$\bullet I_E = -0.167 \text{ mA}$$

$$\bullet I_B = \frac{I_E}{101} = -0.00167 \text{ mA}$$

$$\bullet I_C = 100 (-0.00167 \text{ mA})$$

$$= -0.167 \text{ mA}$$

Active mode as $V_C < V_B$

Hilroy

Part 2

1) Edge between active and saturation

$$\hookrightarrow V_B = V_C$$

$$V_E - 0.7 = V_C \rightarrow 3 - R_E I_E - 0.7 = -3 - R_C (I_C)$$

KVL on right loop

$$\hookrightarrow 3V - I_C (R_C) - 0.7 - I_E (R_E) + 3V = 0$$

$$5.3V = 100 I_B (R_C) + 101 I_B (R_E)$$

$$100 I_B \approx 101 I_B$$

$$5.3 = 100 I_B (R_C + R_E)$$

$$\hookrightarrow 0.053 = I_B (R_C + R_E) \rightarrow \text{eq 1}$$

from KCL on left branch

$$\hookrightarrow I_B + \frac{3}{41k} + \frac{-3}{150k} = 0$$

$$\hookrightarrow I_B = -0.013 \text{ mA}$$

$$\text{eq 2} \rightarrow 4077 \Omega = R_C + R_E$$

KVL at top loop

$$\hookrightarrow -3 + R_E \cdot (101 I_B) + 0.7 + (I_B) 41k + 3 = 0$$

$$\hookrightarrow -0.7 = I_B (R_E \cdot 101 + 41k)$$

$$\text{where } I_B = -0.013 \text{ mA}$$

$$\hookrightarrow 53846 = 101 R_E + 41k$$

$$R_E = 368 \Omega$$

$$R_C = 4077 - 368 \Omega \rightarrow R_C = 3.7 \text{ k}$$