

**ITI1100A**  
**Assignment # 4**  
**SOLUTIONS**


4.1

(a)  $T_1 = B'C, T_2 = A'B, T_3 = A + T_1 = A + B'C,$   
 $T_4 = D \oplus T_2 = D \oplus (A'B) = A'BD' + D(A + B') = A'BD' + AD + B'D$   
 $F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D$   
 With  $A + AD = A$  and  $A + A'BD' = A + BD'$ :  
 $F_1 = A + B'C + BD' + B'D$   
 Alternative cover:  $F_1 = A + CD' + BD' + B'D$



$F_2 = T_2 + D' = A'B + D'$

(b)

ABCD	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	T <sub>4</sub>	F <sub>1</sub>	F <sub>2</sub>
0000	0	0	0	0	0	1
0001	0	0	0	1	1	0
0010	1	0	1	0	1	1
0011	1	0	1	1	1	0
0100	0	1	0	1	1	1
0101	0	1	0	0	0	1
0110	0	1	0	1	1	1
0111	0	1	0	0	0	1
1000	0	0	1	0	1	1
1001	0	0	1	1	1	0
1010	1	0	1	0	1	1
1011	1	0	1	1	1	0
1100	0	0	1	0	1	1
1101	0	0	1	1	1	0
1110	0	0	1	0	1	1
1111	0	0	1	1	1	0

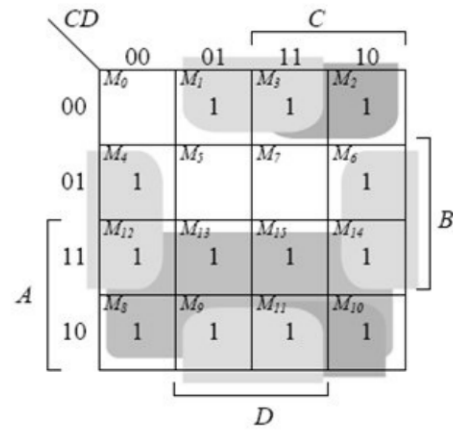


(c)

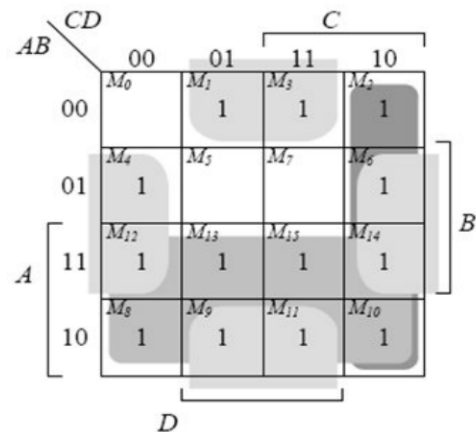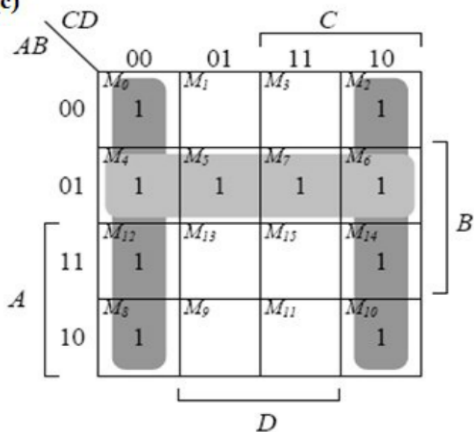




4.9


ABCD	a	b	c	d	e	f	g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

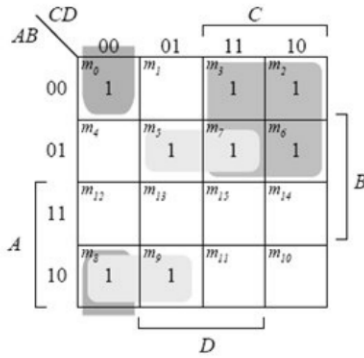

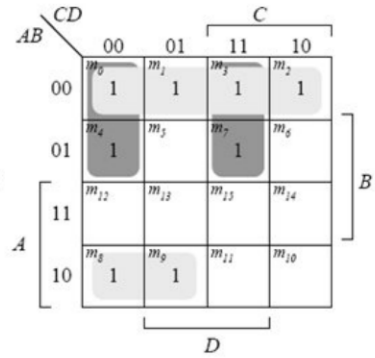
$a = A'C + A'BD + AB'C' + A'B'D'$  or  $a = A'C + A'BD + B'C'D' + AB'C'$




$b = A'B' + B'C' + A'CD' + A'CD$

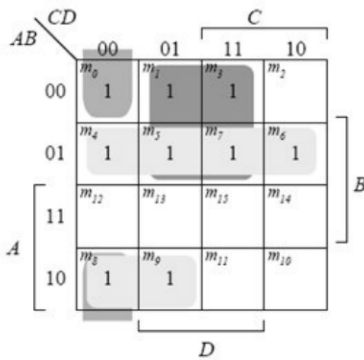


$c = A'B + A'D + B'C'$

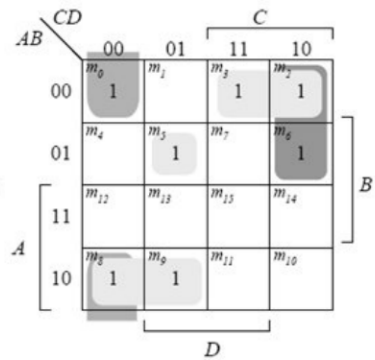

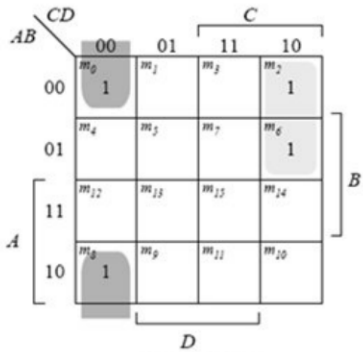$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$




$e = A'CD' + B'C'D'$

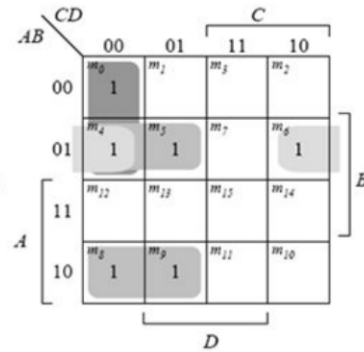

$f = A'BC' + A'CD' + A'BD + AB'C'$


or  $f = A'BC' + AB'C' + A'BD' + B'C'D'$

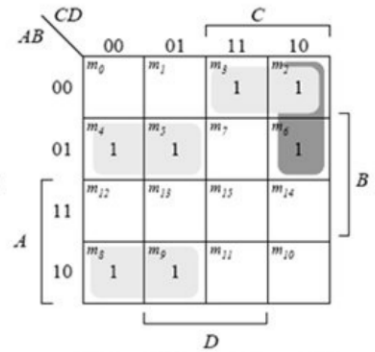

$g = A'CD' + A'B'C + A'BC' + AB'C'$

or  $g = A'BC' + AB'C' + A'B'C + A'BD'$

4.21

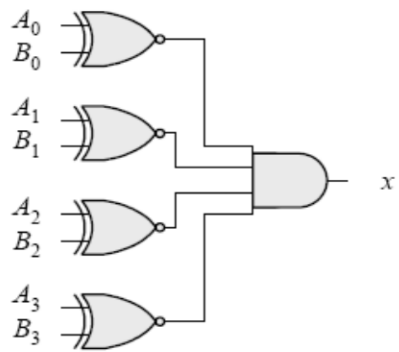

$$x = (A_0 \oplus B_0)'(A_1 \oplus B_1)'(A_2 \oplus B_2)'(A_3 \oplus B_3)'$$

4.23

$$D_0 = A_1'A_0'E = (A_1 + A_0 + E)' \text{ [NOR]}$$

$$D_1 = A_1'A_0E = (A_1 + A_0' + E)' \text{ [NOR]}$$

$$D_2 = A_1A_0'E = (A_1' + A_0 + E)' \text{ [NOR]}$$



$$D_3 = A_1A_0E = (A_1' + A_0' + E)' \text{ [NOR]}$$

$$D_0' = (A_1'A_0'E)' \text{ [NAND]}$$

$$D_1' = (A_1'A_0E)' \text{ [NAND]}$$

$$D_2' = (A_1A_0'E)' \text{ [NAND]}$$

$$D_3' = (A_1A_0E)' \text{ [NAND]}$$

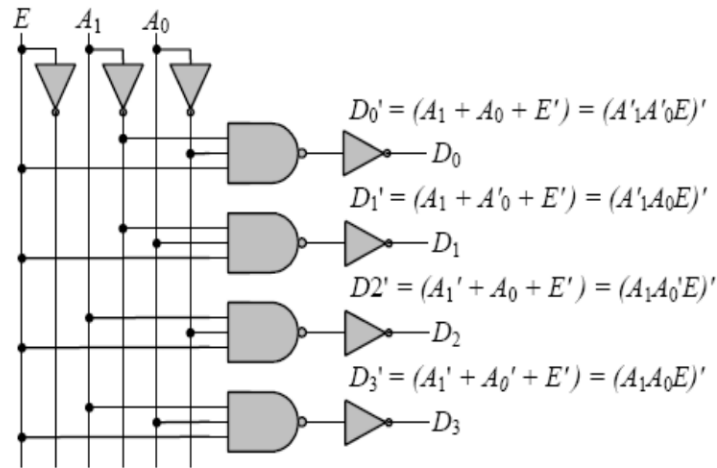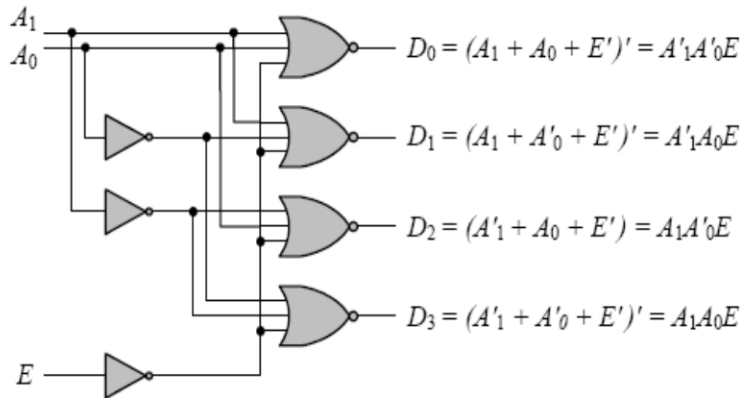


4.27

$$F_1(A,B,C) = \sum(1,4,6) = A'B'C + AB'C' + ABC' = (A'B'C)'(AB'C')'(ABC')'$$

$$F_2(A,B,C) = \sum(3,5) = A'BC + AB'C = (A'BC)'(AB'C)'$$
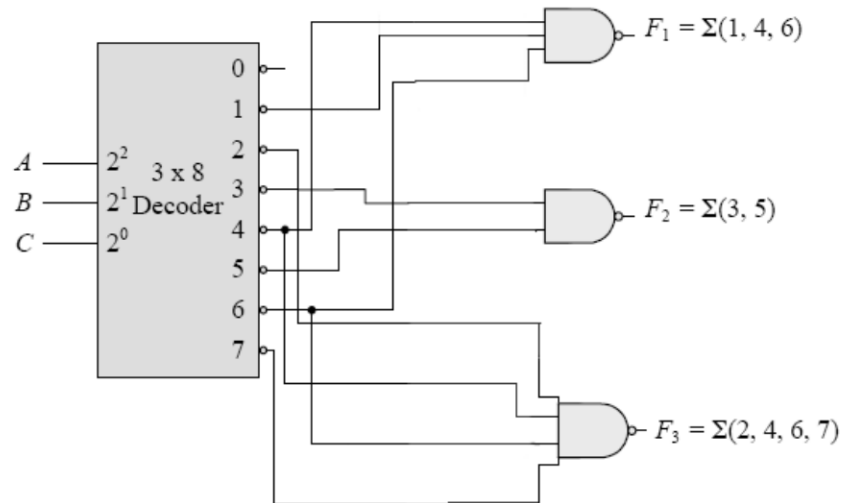
$$F_3(A,B,C) = \sum(2,4,6,7) = A'BC' + AB'C + ABC' + ABC = (A'BC)'(AB'C)'(ABC)'(ABC)'$$




4.28

(a)

$$F_1 = x(y + y')z + x'yz' = xyx + xy'z + x'yz' = \Sigma(2, 5, 7)$$

$$F_2 = xy'z' + x'y = xy'z' + x'yz + x'yz' = \Sigma(2, 3, 4)$$
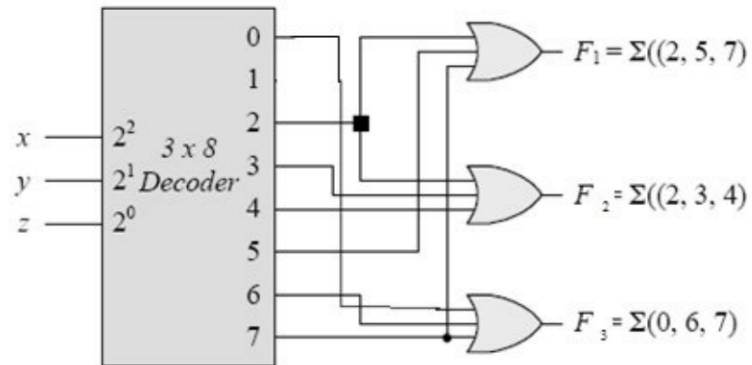
$$F_3 = x'y'z' + xy(z + z') = x'y'z' + xyz + xyz' = \Sigma(0, 6, 7)$$




(b)

$$F_1 = (Y'+X)Z = X'Y'Z + XY'Z + XYZ$$

$$F_2 = Y'Z + XY' + YZ = XY'Z' + X'Y'Z' + XY'Z + XYZ' + X'YZ'$$

$$F_3 = (X'+Y)Z = X'YZ + X'Y'Z + XYZ$$

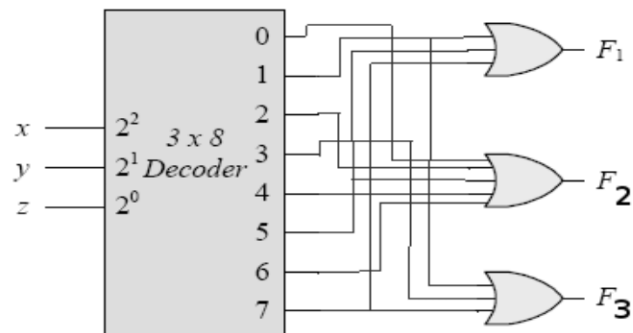

4.33

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

$S$	$I_0$	$I_1$	$I_2$	$I_3$	$C$	$I_0$	$I_1$	$I_2$	$I_3$
$x'$	0	1	2	3	$x'$	0	1	2	3
$x$	4	5	6	7	$x$	4	5	6	7
	$x$	$x'$	$x'$	$x$		0	$x'$	$x'$	1

