

## LAB 3: Transient Response of a Series RC Circuit.

### PURPOSE

To introduce and verify the theory of a series RC circuit response to square wave excitation. Lectures on this topic will follow at the end of the term.

### EQUIPMENT

- (i) Oscilloscope – Tektronix 3012.
- (ii) Oscillator – Wavetek 182A.
- (iii) Multimeter – Wavetek DM15XL.
- (iv) Prototyping board.
- (v) 10kΩ resistor.
- (vi) 0.01μF capacitor.

### PRELAB ( /2)

For this prelab, use the component values as given in Part 1, step 1.2.

1. ( /0.5) Figure 1 shows the basic series RC circuit. The input signal to the circuit is a square wave, as shown in Figure 2. For the theory of the series RC circuit response to square wave excitation, refer to Example 6 on transients at the back of the lab manual.

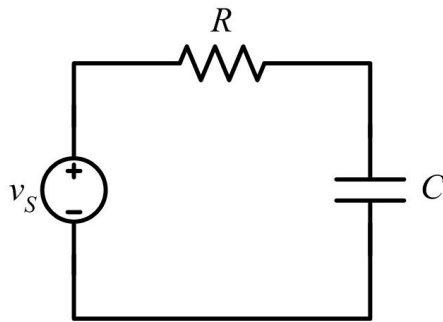


Figure 1. Basic series RC circuit.

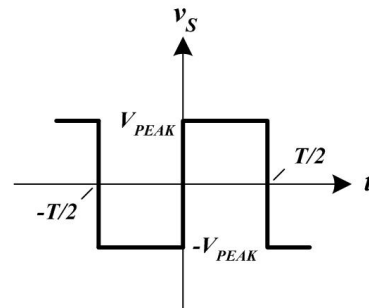


Figure 2. Squarewave input signal.

The voltage across the capacitor in the circuit shown in Figure 1 is given by the following equation:

$$v_C(t) = V_F + (V_I - V_F)e^{-\frac{t}{RC}} \quad (1)$$

where  $V_I$  is the initial value and  $V_F$  is the final value of the voltage on the capacitor as it is being charged. In this case,  $V_F = +V_{PEAK}$  and, when the period of the input waveform is long enough to allow the capacitor to fully charge,  $V_I = -V_{PEAK}$ . Thus equation (1) becomes:

$$v_C(t) = V_{PEAK} (1 - 2e^{-\frac{t}{RC}}) \quad (2)$$

By KVL, the voltage across the resistor becomes:

$$v_R(t) = 2V_{PEAK} e^{-\frac{t}{RC}} \quad (3)$$

Using equations (2) and (3), calculate and tabulate the values for  $v_C$  and  $v_R$  for the positive half-period of a square wave with  $v_S = 1$  V peak and a period  $T = 2000$   $\mu\text{sec}$ : divide the half-period of the waveform into 8 equal intervals, and for each time instant calculate the values of  $v_C$  and  $v_R$ . Complete the table below.

Interval (positive half-period)	t ( $\mu\text{s}$ )	$v_C$ (volts)	$v_R$ (volts)
1			
2			
3			
4			
5			
6			
7			
8			

2. (/\_/0.5) For the negative half-period, repeat question 1 using  $V_I = +V_{PEAK}$  and  $V_F = -V_{PEAK}$ , and assuming the time origin is at  $T/2$  by using the same values of  $t$  from question 1.


Interval (negative half-period)	t ( $\mu\text{s}$ )	$v_C$ (volts)	$v_R$ (volts)
1			
2			
3			
4			
5			
6			
7			
8			

3. (/\_/0.5) Plot accurately to scale on a sheet of graph paper one full period of the waveform  $v_C$  by combining the results obtained in questions 1 and 2. Make sure your plot matches the general shape of  $v_C$  as shown in Example 6 on transients at the back of the lab manual.
4. (/\_/0.5) Plot accurately to scale on a sheet of graph paper one full period of the waveform  $v_R$  by combining the results obtained in questions 1 and 2.

## PROCEDURE (/\_/8)

### Part 1. Series RC Circuit Response

- 1.1 Connect the oscilloscope across the output of the oscillator, and adjust the oscillator voltage to give a square wave signal with an amplitude of 2 V peak-to-peak and a period of  $T = 2000$   $\mu\text{sec}$  ( $f = 500$  Hz). **Readjust the amplitude to 2 V peak-to-peak whenever you change the frequency of the input signal.**
- 1.2 Connect the circuit shown in Figure 3.

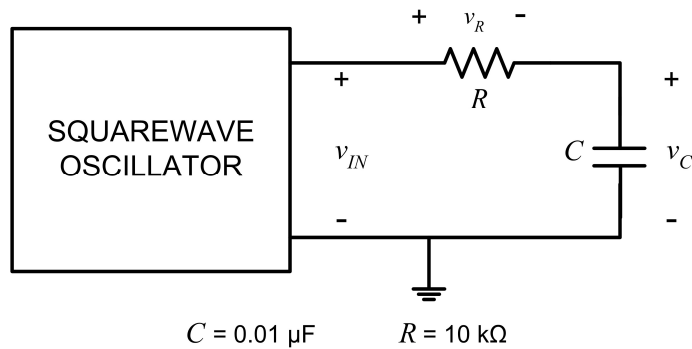

**Figure 3. Circuit configuration for step 1.2.**

- 1.3** Connect channel 1 of the oscilloscope across the oscillator output, and channel 2 across the capacitor. Since the oscilloscope only has two channels, we cannot display  $v_{IN}$ ,  $v_C$ , and  $v_R$  all at the same time. However, note that by KVL,  $v_R = v_{IN} - v_C$ , therefore we can use the 'MATH' menu of the oscilloscope to display  $v_R$ :
- Press the pink 'MATH' button on the oscilloscope panel.
  - Set the operator to '-'.
  - Set 1<sup>st</sup> source to channel 1 and 2<sup>nd</sup> source to channel 2

You should now be able to see three waveforms on the screen ( $v_{IN}$ ,  $v_C$ , and  $v_R$ ). Make sure the vertical scales of the three waveforms are the same (scales are displayed at the bottom left of the screen).

- 1.4** In this step, our goal is to obtain the  $v_C$  waveform and compare it to the plot produced in the prelab. In order to ensure that the rising edge of the  $v_C$  waveform starts at  $t = 0$  like in the prelab, we need to set the trigger settings to an external trigger. To do this, perform the following steps:
- Make sure there is a cable connected between the 'SYNC OUT' output of the oscillator and the 'EXT TRIG' input of the oscilloscope.
  - Press the 'menu' button at the bottom of the 'TRIGGER' area on the oscilloscope panel.
  - Select 'EXT' from the list on the screen.
  - Consider using 'Invert ON'.

Verify that the  $v_C$  waveform on the oscilloscope is similar to the waveform plotted in the prelab.

- 1.5** (/\_1) Using the 'cursors' menu on the oscilloscope, record the values of  $v_C$  in the table at the of this handout for the same time instants used in the prelab. Plot accurately the waveform for  $v_C$  on the same plot that was produced in the prelab. Only one cycle of the waveforms is needed, and eight readings are required for each of the positive and the negative halves of the waveform.
- 1.6** (/\_1) Repeat step 1.5 for the  $v_R$  waveform.
- 1.7** (/\_1) Compare the experimental waveforms obtained in steps 1.5-1.6 to the waveforms plotted in the prelab.
- 1.8** (/\_2) Change the oscillator to give an input signal with a period of  $T = 200 \mu\text{sec}$  ( $f = 5 \text{ KHz}$ ) and amplitude of 2 V peak-to-peak. Repeat the external trigger settings from step 1.4. Record and plot accurately the waveforms for  $v_C$  and  $v_R$ . Only one cycle of the waveforms is needed, and eight readings are required for each of the positive and the negative halves of the waveform. Observe that the  $v_C$  and  $v_R$  waveforms obtained here are actually the first 10% of the period of the waveforms obtained in steps 1.5-1.6.

1.9 (/\_/2) Repeat step 1.8 for  $T = 20 \mu\text{sec}$  ( $f = 50 \text{ KHz}$ ). Observe that the  $v_C$  and  $v_R$  waveforms obtained here are actually the first 10% of the period of the waveforms obtained in step 1.8, and the first 1% of the waveforms obtained in steps 1.5-1.6.

1.10 (/\_/1) Explain why the shapes of  $v_C$  and  $v_R$  waveforms change as the period of the input signal is varied.

Use the following tables to record your readings as required from steps 1.5 to 1.9

Waveform	Suggested Points ( $\mu\text{s}$ )	Measured t ( $\mu\text{s}$ )	$T = 2000 \mu\text{sec}$	
			$v_C$ (volts)	$v_R$ (volts)
Positive half-period	0			
	125			
	250			
	375			
	500			
	625			
	750			
Negative half- period	875			
	1000			
	1125			
	1250			
	1375			
	1500			
	1625			
	1750			
	1875			
	2000			


Waveform	Suggested Points ( $\mu\text{s}$ )	Measured t ( $\mu\text{s}$ )	$T = 200 \mu\text{sec}$	
			$v_C$ (volts)	$v_R$ (volts)
Positive half-period	0			
	12.5			
	25.0			
	37.5			
	50.0			
	62.5			
	75.0			
Negative half- period	87.5			
	100.0			
	112.5			
	125.0			
	137.5			
	150.0			
	162.5			
	175.0			
	187.5			
	200.0			

Waveform	Suggested Points ( $\mu\text{s}$ )	Measured t ( $\mu\text{s}$ )	$T = 20 \mu\text{sec}$	
			$v_C$ (volts)	$v_R$ (volts)
Positive half-period	0			
	1.25			
	2.50			
	3.75			
	5.00			
	6.25			
	7.50			
	8.75			
Negative half- period	10.00			
	11.25			
	12.50			
	13.75			
	15.00			
	16.25			
	17.50			
	18.75			
	20.00			


---

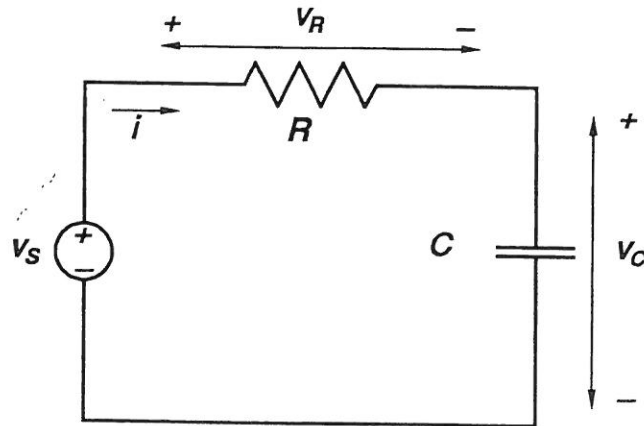Example 6

$v_s$  is a "square wave" (periodic) as shown below. Determine and sketch the waveform of the voltage  $v_c$  across the capacitor.



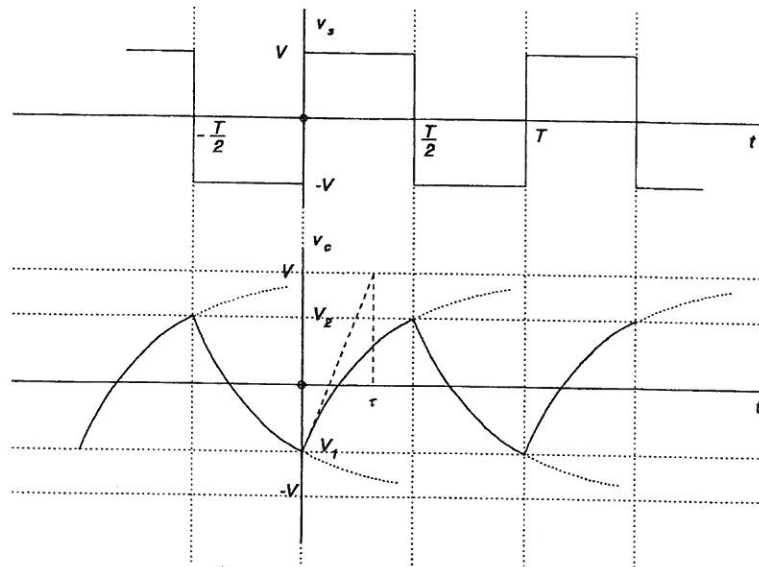In general, since the capacitor voltage  $v_c$  cannot change instantaneously at the times where  $v_s$  suddenly changes (i.e. at  $t = 0, t = T/2$  etc.), the waveform of  $v_c$  must be as illustrated below:



$v_c$  increases exponentially from  $V_1$  to  $V_2$  while  $v_s$  is constant at the value  $V$ , and decreases exponentially from  $V_2$  to  $V_1$  while  $v_s$  is constant at the value  $-V$ . In each successive half-period, the capacitor charges towards either  $V$  or  $-V$  but does not reach either value before  $v_s$  changes. If we assume that the circuit has been operating in the manner described for a long period so that its behaviour is cyclical, we can assign  $V_2$  and  $V_1$  as the maximum and minimum voltages respectively, on the capacitor. The voltages  $V_1$  and  $V_2$  are to be determined so that the waveform of  $v_c$  can be determined. It is clear that the values  $V_1$  and  $V_2$  must depend on the

values of the time-constant,  $\tau$  the period of the squarewave,  $T$  and the amplitude,  $v_s$ .

Since the squarewave is symmetrical i.e.  $|V| = |-V|$ , it follows that:

$$V_1 = -V_2 \quad (1)$$

and the capacitor voltage changes by  $2V_1$  (or  $2V_2$ ) in each half period of  $v_s$ , reaching the same fraction of  $V$  or  $-V$ . In general, the waveform can be described as:

$$f(t) = (\text{Initial value}) + (\text{Final} - \text{Initial value})(1 - e^{-t/\tau}) \quad (2)$$

The equation for the waveform of  $v_c$  for the period:

(a)  $0 \leq t' \leq T/2$  is:

$$v_c = V_1 + [V - V_1][1 - e^{-t'/\tau}] \quad (3)$$

Substituting  $-V_2$  for  $V_1$  from (1),

$$v_c = -V_2 + [V + V_2][1 - e^{-t'/\tau}] \quad (4)$$

(b)  $T/2 \leq t' \leq T$  (or  $0 \leq t'' \leq T/2$ ) the equation of the waveform is:

$$v_c = V_2 + [(-V) - V_2][1 - e^{-t''/\tau}] \quad (5)$$

This may be written as:

$$v_c = V_2 - [V + V_2][1 - e^{-t''/\tau}] \quad (6)$$

#### Note

(i) The variable  $t'$  in (4) is equal to zero at the origin while the variable  $t''$  in (6) is equal to zero at the instant when  $v_s$  switches from  $V$  to  $-V$  i.e. at  $t' = T/2$ .

(ii) The voltage across the capacitor when  $t' = T/2$  has to be the same as when  $t'' = 0$ .

From (4), when  $t' = T/2$ ,  $v_c = V_2$ . We can therefore write:

$$V_2 = -V_2 + [V + V_2][1 - e^{-T/2\tau}] \quad (7)$$

or

$$V_2 = \frac{V(1 - e^{-\frac{T}{2\tau}})}{(1 + e^{-\frac{T}{2\tau}})} \quad (8)$$

The value of  $V_2$  depends on the relative values of  $T/2$  and  $\tau$ , that is on the degree to which the capacitor can charge in the half-

period  $T/2$ . If  $T/2 \gg \tau$

$$V_2 = V \quad (9)$$

and the charging of  $C$  to  $V$  or  $-V$  is virtually completed in each half-period. If on the other hand  $T/2 \ll \tau$ ,  $V_2 \ll V$  and very little charging of  $C$  occurs in each half-period.