

Name: \_\_\_\_\_ Student Number: \_\_\_\_\_

**ELEC 4602, Electrical Power Engineering, Test #2, Fall 2015**

Time: One Hour

Test #1 contains 3 questions

Authorized Memoranda: Calculator, Course Pack 2015, Course Text – Chapman

**#1 <8 Marks>**

A three-phase transformer bank is formed by interconnecting three single-phase transformers. The high-voltage terminals are connected to a three-phase 69 kV feeder, and the low-voltage terminals are connected to a three-phase load rated at 1000 kVA and 4.16 kV. Specify the voltage and current ratings, high-voltage and low-voltage windings, for each transformer for the following connections:

(a) wye-wye, (b) wye-delta, (c) delta-wye, (d) delta-delta./

Connection	Voltage High-voltage Winding	Current High-voltage Winding	Voltage Low-voltage Winding	Current Low-voltage Winding
(a) wye-wye	40 kV	8.3 A	2.4 kV	138.8 A
(b) wye-delta	40 kV	8.3 A	4.16 kV	80.1 A
(c) delta-wye	69 kV	4.8 A	2.4 kV	138.8 A
(d) delta-delta	69 kV	4.8 A	4.16 kV	80.1 A

$\frac{1}{2}$  MARK FOR  
EACH CORRECT  
ENTRY

$$\frac{69 \text{ kV}}{\sqrt{3}} = 40 \text{ kV} \quad \frac{4.16 \text{ kV}}{\sqrt{3}} = 2.4 \text{ kV}$$

++ ++ ++

$$1000 \text{ kVA} @ 69 \text{ kV} \Rightarrow 8.3 \text{ A}$$

$$\frac{8.3}{\sqrt{3}} = 4.8 \text{ A}$$

++ ++ ++

$$1000 \text{ kVA} @ 4.16 \text{ kV} \Rightarrow 138.8 \text{ A}$$

$$\frac{138.8}{\sqrt{3}} = 80.1 \text{ A}$$

8/8

TOTAL MARKS - 8.

## #2 <12 Marks>

The low-voltage terminals of a 10 MVA, 66 kV – 7.2 kV single phase transformer are short-circuited and a voltage of 2640 volts is applied to the high voltage terminals with results as follows.

Voltage =  $V_{sc} = 2640$  volts

Power =  $P_H = 9850$  watts

Current =  $I_H = 72$  amps

(a) Calculate the total series resistance and the total series reactance referred to the high-voltage side.

(b) Calculate %IR and %IX for the transformer.

(c) If the core loss at rated voltage is 40 kW, calculate the full-load efficiency of the transformer if the power factor of the load is 0.85 lag.

$$(a) \quad R_{eH} = \frac{P_H}{I_H^2} = \frac{9850}{72^2} = \underline{1.9 \Omega} \quad (2)$$

$$Z_{eH} = \frac{V_{sc}}{I_H} = \frac{2640}{72} = \underline{36.67 \Omega} \quad (2)$$

$$X_{eH} = \sqrt{Z_{eH}^2 - R_{eH}^2} = \sqrt{36.67^2 - 1.9^2} = \underline{36.62 \Omega} \quad (2)$$

$$(b) \quad I_{Full\ Load\ HV} = \frac{10,000}{66} = 151.5 \text{ Amps}$$

$$\%IR = \frac{I_1 R_{eH}}{V_1} \times 100 = \frac{151.5 \times 1.9}{66000} \times 100 = \underline{0.436\%} \quad (2)$$

-OR-

$$\%IR = \frac{Z(\Omega) \times KVA_{MVA}}{KV_{BHV}^2 \times 1000} = \frac{1.9 \times 10,000}{66^2 \times 1000} = 0.00436$$

$$\therefore \%IR = \underline{0.436\%}$$

$$\%IX = \frac{I_1 X_{eq1} \times 100}{V_1} = \frac{151.5 \times 36.12 \times 100}{66000} = \underline{\underline{8.4\%}} \quad (2)$$

R -

$$Z_{pq} = \frac{2(\Omega) \times KVA_{Base}}{KV_{Base}^2 \times 1000} = \frac{36.12 \times 10,000}{66^2 \times 1000} = 0.084$$

$$\therefore \%IX = \underline{\underline{8.4\%}}$$

(c)


Copper Loss:	$151.5^2 \times 1.9$	=	43.6 kW
Core Loss			40.1 kW
TOTAL Loss			<u>83.6 kW</u>

$$\therefore \frac{P}{T} = \text{Power out} = 10,000 \times 0.85 = 8500 \text{ kW}$$

$$\therefore \eta = \frac{8500}{8500 + 83.6} \times 100 = \underline{\underline{99\%}} \quad (2)$$

TOTAL 12 MARKS

3. <10 Marks>

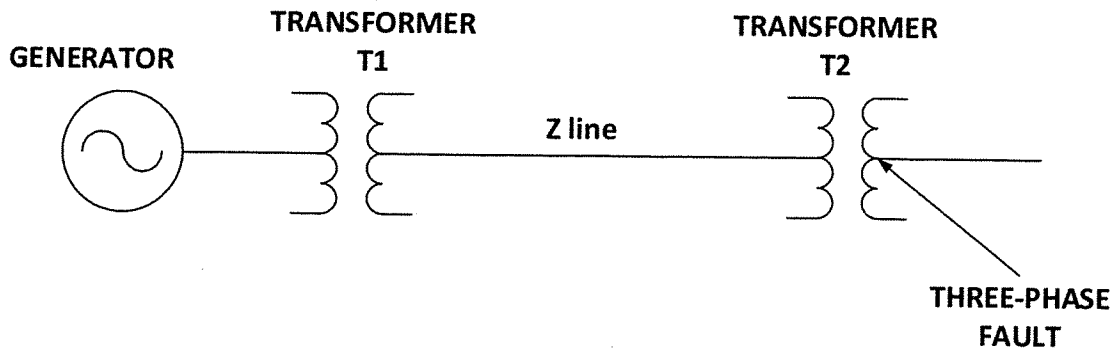

Following are the data for the system shown above.

GENERATOR: 50 MVA, 13.8 kV, %IX = 15%
TRANSFORMER T1: 25 MVA, 13.2 – 161 kV, %IX = 10%
Z line: (10 + j10) ohms
TRANSFORMER T2: 15 MVA, 161 – 13.8 kV, %IX = 10%

Using the per unit method with basis of 100,000 kVA and 13.8 kV, the generator voltage, calculate the symmetrical short circuit current and the short circuit kVA at the low voltage terminals of Transformer T2.

$$Z_{pu\ new} = Z_{pu\ old} \left( \frac{KV_{base\ old}}{KV_{base\ new}} \right)^2 \left( \frac{KVA_{base\ new}}{KVA_{base\ old}} \right)$$

GENERATOR:

$$Z_{pu\ g} = 0.15 \left( \frac{13.8}{13.8} \right)^2 \left( \frac{100,000}{50,000} \right) = j0.30\ pu \quad (1)$$

TRANSFORMER T1

$$Z_{pu\ T1} = 0.10 \left( \frac{13.2}{13.8} \right)^2 \left( \frac{100,000}{25,000} \right) = j0.366\ pu \quad (1)$$

LINE voltage base =  $\frac{161}{13.2} \times 13.8 = 168.3\ kV \quad (1)$

$$Z_{base} = \frac{(KV_{base})^2 \times 1000}{KVA_{base}} = \frac{(168.3)^2 \times 1000}{100,000} = 283.2\ \Omega$$

$$\therefore Z_{pu\ line} = \frac{10 + j10}{283.2} = (0.035 + j0.035)\ pu \quad (2)$$

## TRANSFORMER T<sub>2</sub>

$$V_{B2} = 168.3 \text{ kV}$$

$$Z_{pu T2} = 0.10 \left( \frac{161}{168.3} \right)^2 \left( \frac{10,000}{15,000} \right) = j 0.61 \text{ pu.} \quad (1)$$

TOTAL PU. IMPEDANCE TO FAULT

$$\text{GENERATOR: } 0 + j 0.30$$

$$T_1 \quad 0 + j 0.366$$

$$\text{LINE} \quad 0.038 + j 0.038$$

$$T_2 \quad 0 + j 0.61$$

$$\text{TOTAL} \quad 0.038 + j 1.311 \Rightarrow 1.311 \angle \text{pu} \quad (1)$$

$$V_{\text{BASE AT FAULT}} = \frac{13.8}{161} \times 168.3 = 14,426 \text{ kV}$$

$$\therefore I_{\text{BASE AT FAULT}} = \frac{KVA_{\text{BASE}}}{\sqrt{3} V_{\text{BASE}}} = \frac{100,000}{\sqrt{3} \times 14,426} = 4002 \text{ AMP} \quad (1)$$

$$\therefore \underline{I_{SC}} = \frac{I_{\text{BASE}}}{Z_{pu}} = \frac{4002}{1.311} = \underline{3,053 \text{ AMPS}} \quad (1)$$

$$KVA_{SC} = \frac{KVA_{\text{BASE}}}{Z_{pu}} = \frac{100,000}{1.311} = \underline{76,278 \text{ KVA}} \quad (1)$$

TOTAL MARKS 10