

Nodal and mesh analysis.  
(wikipedia.org).

ENGG 2450: Electric Circuits

Professor: Dr. Christopher Collier

MODULE 3.0

UNIVERSITY  
of GUELPH

Methods of Analysis

$$\begin{bmatrix} 1 & 2 \\ 3 & 4 \\ 5 & 6 \end{bmatrix}$$

Matrix algebra is often used to solve circuits with  
nodal and mesh analysis (freestockphotos.com).

## 3.0 Fundamentals of Electric Circuits 6<sup>th</sup> Ed. corresponding textbook material for this module.

### *Chapter 1 Basic Concepts*

- 1.1 Introduction
- 1.2 Systems of Units
- 1.3 Charge and Current
- 1.4 Voltage
- 1.5 Power and Energy
- 1.6 Circuit Elements
- 1.7 Applications
- 1.8 Problem Solving
- 1.9 Summary

### *Chapter 2 Basic Laws*

- 2.1 Introduction
- 2.2 Ohm's Law
- 2.3 Nodes, Branches, and Loops
- 2.4 Kirchhoff's Laws
- 2.5 Series Resistors and Voltage Division
- 2.6 Parallel Resistors and Current Division
- 2.7 Wye-Delta Transformations
- 2.8 Applications
- 2.9 Summary

### *Chapter 3 Methods of Analysis*

- 3.1 Introduction**
- 3.2 Nodal Analysis**
- 3.3 Nodal Analysis with Voltage Sources**
- 3.4 Mesh Analysis**
- 3.5 Mesh Analysis with Current Sources**
- 3.6 Nodal and Mesh Analyses by Inspection
- 3.7 Nodal Versus Mesh Analysis
- 3.8 Circuit Analysis with PSpice
- 3.9 Applications: DC Transistor Circuits
- 3.10 Summary

### *Chapter 4 Circuit Theorems*

- 4.1 Introduction
- 4.2 Linearity Property
- 4.3 Superposition
- 4.4 Source Transformation
- 4.5 Thevenin's Theorem
- 4.6 Norton's Theorem
- 4.7 Derivations of Thevenin's and Norton's Theorems
- 4.8 Maximum Power Transfer
- 4.9 Verifying Circuit Theorems with PSpice
- 4.10 Applications
- 4.11 Summary

### *Chapter 5 Operational Amplifiers*

- 5.1 Introduction
- 5.2 Operational Amplifiers
- 5.3 Ideal Op Amp
- 5.4 Inverting Amplifier
- 5.5 Noninverting Amplifier
- 5.6 Summing Amplifier
- 5.7 Difference Amplifier
- 5.8 Cascaded Op Amp Circuits
- 5.9 Op Amp Circuit Analysis with PSpice
- 5.10 Applications
- 5.11 Summary

### *Chapter 6 Capacitors and Inductors*

- 6.1 Introduction
- 6.2 Capacitors
- 6.3 Series and Parallel Capacitors
- 6.4 Inductors
- 6.5 Series and Parallel Inductors
- 6.6 Applications
- 6.7 Summary

### *Chapter 7 First-Order Circuits*

- 7.1 Introduction
- 7.2 The Source-Free RC Circuit
- 7.3 The Source-Free RL Circuit
- 7.4 Singularity Functions
- 7.5 Step Response of an RC Circuit
- 7.6 Step Response of an RL Circuit
- 7.7 First-Order Op Amp Circuits
- 7.8 Transient Analysis with PSpice
- 7.9 Applications
- 7.10 Summary

### *Chapter 8 Second-Order Circuits*

- 8.1 Introduction
- 8.2 Finding Initial and Final Values
- 8.3 The Source-Free Series RLC Circuit
- 8.4 The Source-Free Parallel RLC Circuit
- 8.5 Step Response of a Series RLC Circuit
- 8.6 Step Response of a Parallel RLC Circuit
- 8.7 General Second-Order Circuits
- 8.8 Second-Order Op Amp Circuits
- 8.9 PSpice Analysis of RLC Circuits
- 8.10 Duality
- 8.11 Applications
- 8.12 Summary

### *Chapter 9 Sinusoids and Phasors*

- 9.1 Introduction
- 9.2 Sinusoids
- 9.3 Phasors
- 9.4 Phasor Relationships for Circuit Elements
- 9.5 Impedance and Admittance
- 9.6 Kirchhoff's Laws in the Frequency Domain
- 9.7 Impedance Combinations
- 9.8 Applications
- 9.9 Summary

### *Chapter 10 Sinusoidal Steady-State*

- 10.1 Introduction
- 10.2 Nodal Analysis
- 10.3 Mesh Analysis
- 10.4 Superposition Theorem
- 10.5 Source Transformation
- 10.6 Thevenin and Norton Equivalent Circuits
- 10.7 Op Amp AC Circuits
- 10.8 AC Analysis Using PSpice
- 10.9 Applications
- 10.10 Summary

### *Chapter 11 AC Power Analysis*

- 11.1 Introduction
- 11.2 Instantaneous and Average Power
- 11.3 Maximum Average Power Transfer
- 11.4 Effective or RMS Value
- 11.5 Apparent Power and Power Factor
- 11.6 Complex Power
- 11.7 Conservation of AC Power
- 11.8 Power Factor Correction
- 11.9 Applications
- 11.10 Summary

### *Chapter 12 Three-Phase Circuits*

- 12.1 Introduction
- 12.2 Balanced Three-Phase Voltages
- 12.3 Balanced Wye-Wye Connection
- 12.4 Balanced Wye-Delta Connection
- 12.5 Balanced Delta-Delta Connection
- 12.6 Balanced Delta-Wye Connection
- 12.7 Power in a Balanced System
- 12.8 Unbalanced Three-Phase Systems
- 12.9 PSpice for Three-Phase Circuits
- 12.10 Applications
- 12.11 Summary

### *Chapter 13 Magnetically Coupled Circuits*

- 13.1 Introduction
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.7 Three-Phase Transformers
- 13.8 PSpice Analysis of Magnetically Coupled Circuits
- 13.9 Applications
- 13.10 Summary

### 3.1 Nodal analysis.


In nodal analysis, circuits are analysed by investigating the current into/out of nodes. Here, a series of equations can be setup with fewer (or equal) unknowns than the number of equations. Problems of this nature are typically solved by solving this series of equations. This method can be applied using three steps:

1. Select node as reference node (often ground) and assign voltages to other nodes.  
 → Voltages are references with respect to the reference node
2. Apply KCL to each non-reference node  
 → Use Ohm's law to express currents as node voltages.
3. Solve equations to get unknown node voltages.

**Example.** For the circuit, find  $v_1$  and  $v_2$ .

1. Set node c to be reference node.

2. KCL at node a:

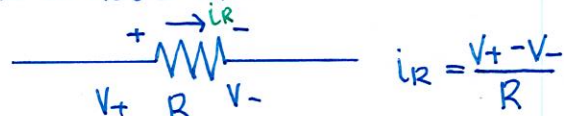

$$i_R = \frac{V_+ - V_-}{R}$$

$$\text{KCL: } i_1 + i_2 = i_3 + i_4$$

$$\left( \frac{0 - v_1}{10} + \frac{0 - v_1}{5} = \frac{v_1 - v_2}{2} + 6 \right) \cdot 10$$

$$\Rightarrow -v_1 - 2v_1 = 5v_1 - 5v_2 + 60$$

$$-3v_1 - 5v_1 = -5v_2 + 60$$

$$\textcircled{1} \quad -8v_1 + 5v_2 = 60 \Rightarrow v_2 = \frac{60 + 8v_1}{5}$$

KCL at node b:


$$i_3 + i_4 + i_5 + i_6 = 0$$

$$\left( \frac{v_1 - v_2}{2} + 6 + \frac{0 - v_2}{4} + 3 = 0 \right) \cdot 4$$

$$2v_1 - 2v_2 + 24 - v_2 + 12 = 0$$

$$\textcircled{2} \quad -2v_1 + 3v_2 = 36$$

\*Tail minus head\*

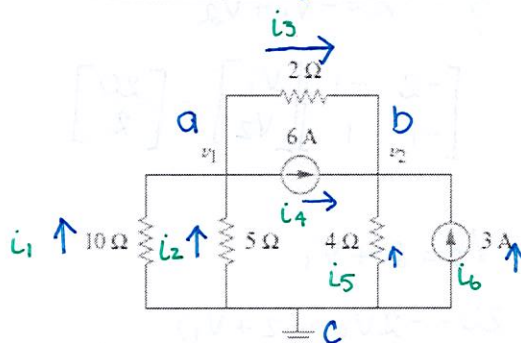

(Fundamentals of electric circuits, 5th Ed.)

$$\begin{bmatrix} -8 & 5 \\ -2 & 3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 60 \\ 36 \end{bmatrix}$$

substitution:

$$-2v_1 + 3 \left( \frac{60 + 8v_1}{5} \right) = 36$$

$$\boxed{v_1 = 0V}$$

$$v_2 = \frac{60 + 8(0)}{5} = 12$$

$$\boxed{v_2 = 12V}$$

### 3.2 Nodal analysis with voltage sources.

Nodal analysis gets slightly more complex when voltage sources are involved. Voltage sources can be thought of as a special type of node called a **supernode**. In this case, the nodal analysis can be supplemented with Kirchhoff's Voltage Law.

**Supernode:** a dependent or independent voltage source between two non-reference nodes.

**Example.** For the circuit, find  $v_1$  and  $v_2$ .

Supernode is 2V source, node 1 & 2 and 10-Ω resistor

Apply KCL to supernode:

$$\left( 2 + \frac{0 - v_1}{2} = 7 + \frac{(v_2 - 0)}{4} \right) 4$$

$$8 - 2v_1 = 28 + v_2$$

$$\textcircled{1} \quad 20 = -2v_1 - v_2$$

KVL around centre loop:

$$v_1 + 2V - v_2 = 0$$

$$\textcircled{2} \quad 2 = -v_1 + v_2$$

$$\begin{bmatrix} -2 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 2 \end{bmatrix}$$

$$v_2 = 2 + v_1$$

$$20 = -2v_1 - (2 + v_1)$$


$$20 = -2v_1 - 2 - v_1$$

$$22 = -3v_1$$

$$v_1 = -\frac{22}{3} \text{ V} = -7.33 \text{ V}$$

$$v_2 = 2 + v_1$$

$$v_2 = -5.33 \text{ V}$$

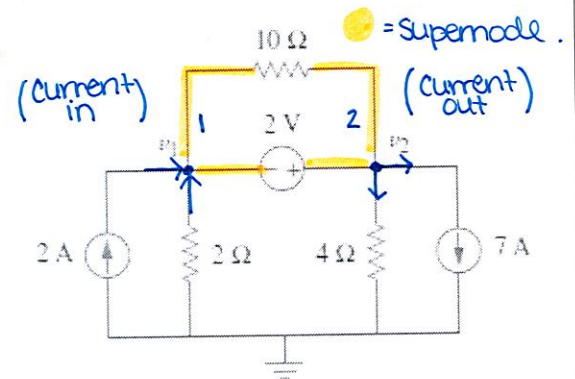

(Fundamentals of electric circuits, 5<sup>th</sup> Ed.)

**Example.** For the circuit, find  $v_1$  and  $v_2$ .

KCL to top node:

$$i_1 + i_2 + i_3 = 0$$

$$20 \left( \frac{v_1 - 0}{2k\Omega} + \frac{v_2 - 0}{5k\Omega} + \frac{v_0}{4k\Omega} \right) = 0 \quad \text{Equation 1}$$

KVL to Loop 1:


$$20V - v_0 + v_2 = 0 \quad \text{Equation 2}$$

KVL to Loop 2:

$$30V - v_0 + v_1 = 0 \quad \text{Equation 3}$$

$$\begin{bmatrix} 10 & 4 & 5 \\ 0 & 1 & -1 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_0 \end{bmatrix} = \begin{bmatrix} 0 \\ -20 \\ -30 \end{bmatrix} \Rightarrow$$
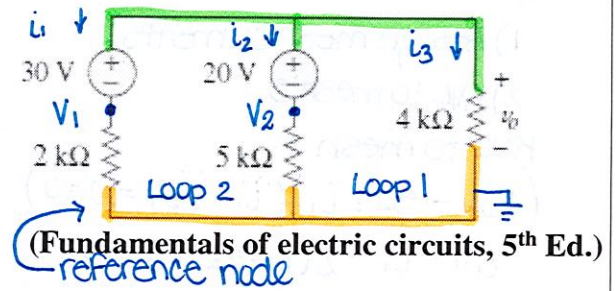
$$\begin{aligned} v_0 &= 20V \\ v_1 &= v_0 - 30 = -10V \\ v_2 &= v_0 - 20 = 0V \end{aligned}$$



### 3.3 Mesh analysis.

Recall that nodal analysis used KCL and solved for unknown voltages. One can also, use KVL and solve for unknown currents. This is called **mesh analysis**. These meshes are the smallest contained loops in a circuit (i.e., they do not have other loops within them). Here, a series of equations can be setup with fewer (or equal) unknowns than the number of equations. Problems of this nature are typically solved by solving this series of equations.

**Mesh:** loop that is not containing another loop.

This method can be applied using **three steps**:

- 1) Assign the mesh currents to the  $n$  meshes (typically clockwise)
- 2) Apply KVL to each  $n$  mesh  $\rightarrow$  use Ohm's Law to express voltages in terms of mesh currents.
- 3) Solve resulting  $n$  equations, simultaneously to get mesh currents.

**Example.** For the circuit, find  $I_1$ ,  $I_2$ , and  $I_3$ .

1) Assign mesh currents

2) KVL to mesh's

KVL to mesh 1:

$$(15V - 5i_1 - 10(i_1 - i_2) - 10 = 0) \div 5$$

$$3V - i_1 - 2(i_1 - i_2) - 2 = 0$$

$$\text{Eq. 1} \quad 1 = 3i_1 - 2i_2$$


KVL to mesh 2:

$$(10 - 10(i_2 - i_1) - 6(i_2) - 4(i_2) = 0) \div 10$$

$$\text{Eq. 2} \quad -1 = i_1 - 2i_2$$

$$\begin{bmatrix} 3 & -2 \\ 1 & -2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 = 1A \\ i_2 = 1A \\ i_3 = 0 \end{bmatrix}$$

$$* i_3 = i_1 - i_2$$

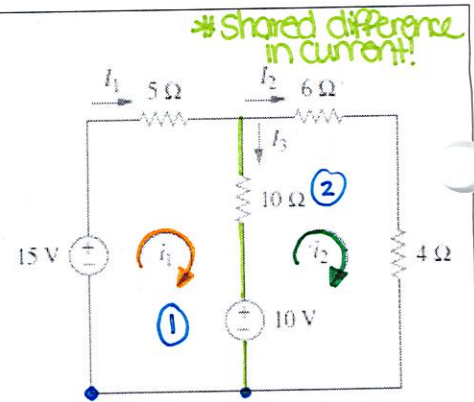

(Fundamentals of electric circuits, 5<sup>th</sup> Ed.)

**Example.** For the circuit, find  $i_1$ ,  $i_2$ , and  $i_3$ .

Mesh 1 KVL:

$$(24V - 10(i_1 - i_2) - 12(i_1 - i_3) = 0) \div 2$$

$$\text{Eq. 1} \quad 12 = 11i_1 - 5i_2 - 6i_3$$

Mesh 2 KVL:

$$(-24i_2 - 4(i_2 - i_3) - 10(i_2 - i_1) = 0) \div 2$$

$$\text{Eq. 2} \quad 5i_1 - 19i_2 + 2i_3 = 0$$

Mesh 3 KVL:

$$-2(i_3 - i_1) - 4(i_3 - i_2) - 4i_0 = 0$$

$$\text{Eq. 3} \quad i_1 + i_2 - 2i_3 = 0$$


$$\begin{bmatrix} 11 & -5 & -6 \\ 5 & -19 & 2 \\ 1 & 1 & -2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\text{Solve: } i_1 = 2.25A$$

$$i_2 = 0.75A$$

$$i_3 = 1.5A$$

$$* i_0 = i_1 - i_2$$

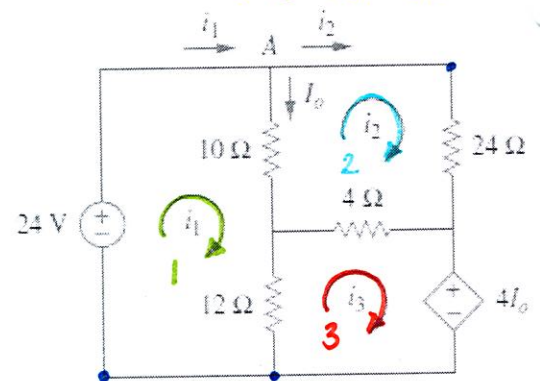

(Fundamentals of electric circuits, 5<sup>th</sup> Ed.)

### 3.4 Mesh analysis with current sources.

Mesh analysis gets slightly more complex when current sources are involved. If the current source is only in one mesh, the current is known in that wire. If two meshes share the same source, there is a **supermesh**. Here, the source and any element in series with it can be excluded from the analysis.


**Supermesh:** two meshes that have a (dependent or independent) current source in common

**Example.** For the circuit, find  $i_1$  and  $i_2$ .

\*2 variables... 2 equations

Note: No Supermeshes in this circuit

KVL of mesh 1:

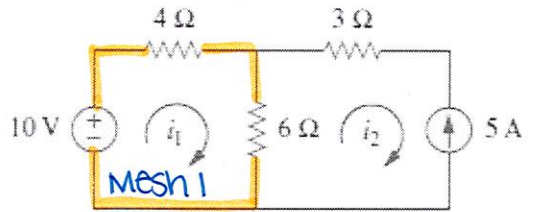

(Fundamentals of electric circuits, 5th Ed.)

$$10V - 4i_1 - 6(i_1 - i_2) = 0$$

$$(-10i_1 + 6i_2 = 10V) \div 2$$

$$5 - 5i_1 + 3i_2 = 0 \text{ Eq. 1}$$

$$i_2 = -5A \text{ Eq. 2}$$

Substitution:

$$5 - 5i_1 - 3(5) = 0$$

$$i_1 = -2A$$

\* Note: If a current source is given, it is the same across the circuit.

**Example.** For the circuit, find  $I_1$ ,  $I_2$ , and  $I_3$ .

\*4 variables... 4 equations

Note: There are 2 supermeshes:

↳ They intersect so they can combine

KVL of Large Supermesh

$$-2i_1 - 4i_3 - 8(i_3 - i_4) - 6i_2 = 0$$

$$(-2i_1 - 4i_3 - 8i_3 + 8i_4 - 6i_2 = 0) \div 2$$

$$-i_1 - 3i_2 - 6i_3 + 4i_4 = 0 \text{ Eq. 1}$$

KCL

$$\text{node p: } 5A = i_2 - i_1 \text{ Eq. 2}$$

KCL

$$\text{node q: } 3I_0 + i_3 = i_2$$

$$\rightarrow I = -i_4$$


$$i_2 - i_3 - 3(i_4) = 0$$

$$i_2 - i_3 + 3i_4 = 0 \text{ Eq. 3}$$

KVL

$$i_4 \text{ loop: } -2i_4 - 10V - 8(i_4 - i_3) = 0$$

$$-4i_3 + 5i_4 = -5 \text{ Eq. 4}$$

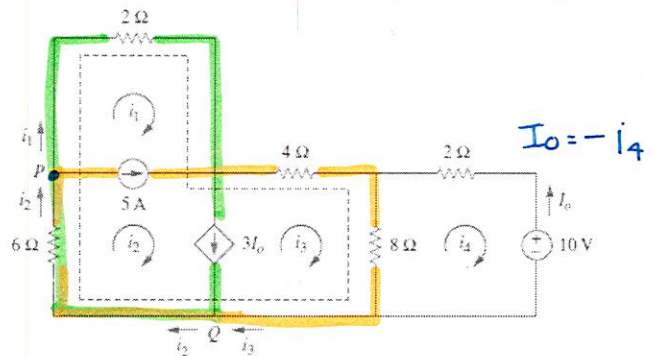

(Fundamentals of electric circuits, 5th Ed.)

$$\begin{bmatrix} -1 & -3 & -6 & 4 \\ -1 & 1 & 0 & 0 \\ 0 & 1 & -1 & 3 \\ 0 & 0 & -4 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ 0 \\ -5 \end{bmatrix} \Rightarrow$$

$$I_1 = -7.5A$$

$$I_2 = -2.5A$$

$$I_3 = 3.93A$$

$$I_4 = 2.143A$$